

DALLAS
SEMICONDUCTOR

Application Note 303
DS2151/DS2153 PCM Interface,
Interfacing to the ADSP-2181

Interconnections between the DS2151 or DS2153 parallel port and the Analog Devices ADSP-2181 non-multiplexed I/O port are shown in Figure 1. Refer to the

"INTERFACING TO A NON-MULTIPLEXED BUS" application note for further information.

TRANSCEIVER – ADSP2181 INTERCONNECTIONS Figure 1

