

ROBOTICS • MICROCONTROLLERS • COMPUTER CONTROL • LASERS

# Nuts & Volts

THE PREFERRED MAGAZINE OF THE  
ELECTRONICS HOBBYIST/INDUSTRY

[www.nutsvolts.com](http://www.nutsvolts.com)

February 2002

Vol. 23 No.2

## In This Issue

Tutorial on Triacs

Lots of Robotics

Microcontrollers

FRS Radios

Lasers

Q&A

Much More!



Build the BLAB BUSTER and  
keep those loud TV commercials  
on the straight and level

U.S. \$5.50 CANADA \$9.25



# AUCTION BLOWOUT!

*Over 2,000 Items on Ebay! Many from Distressed or Bankrupt Dot-Coms!*



**24GB Ultra SCSI DAT Tape Drives**  
*No Minimum Bids!*



**Cisco Routers and Hubs**  
*Bids Start at \$50*



**Sun Workstations and File Servers**  
*No Minimum Bids!*



**15,000 RPM Ultra 160 Hard Drives**  
*\$10 Minimum Bid*

Disk drives cost too much. Take advantage of dot-com closeouts and bankruptcies. We're liquidating thousands of PCs, hard drives, and accessories. Visit [www.scsidrives.com](http://www.scsidrives.com) and name your own price! Join our mailing list for advance notice when special sale items arrive!



**CORPORATE SYSTEMS CENTER**

3310 Woodward Avenue, Santa Clara, CA 95054 (408) 588-1110

### Wall Wart Special!

- ◆ 12VAC, 1600mA Class 2 transformer
- ◆ In: 120VAC, 60Hz, 26W w/coaxial plug
- ◆ Plug: 2.1mm dia center, 5mm sleeve
- ◆ Available by the case - 3000 available
- ◆ Case of 25 - (29 lbs)
- ◆ New units - 90-day warranty



**HSC# 18524 \$29.50**

### Variable Transformer

- ◆ Model AECC-2090
- ◆ 0 - 130 VAC output @ 20A
- ◆ Measures 8" x 10" x 8" tall
- ◆ Meter, illuminated switch
- ◆ New...90-day warranty



**HSC# 80461 \$95.00**

### Analog VOM!

- ◆ 20 KOHM per Volt Multitester
- ◆ 0-1KVDC/VAC, 0-50uA, 5-500 mA
- ◆ 0-20 MOhm, -20 dB to 56 dB
- ◆ Std banana jacks, 3.5" x 5.25" x 1.5"
- ◆ Mirrored dial, damped meter movement
- ◆ New...90-day Warranty. Batteries not incl.



**HSC# 18260 \$9.95**

### DMM w/tilt-display!


- ◆ AECC-2890 DMM with extras!
- ◆ AC/DC volts, Ohms, Current, Capacitance
- ◆ Frequency, Temperature, hFE
- ◆ Wide range measurements
- ◆ Compare at \$70, \$80 +!
- ◆ New, w/test leads, temp probe, cradle



**HSC# 80504 \$39.95**
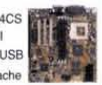
### Pentium M/B

- ◆ Asus Model No. P599VM
- ◆ For Intel P55C-MMX/P54C/P54CS
- ◆ AMD K6-2/K6-III, IBM/Cyrix Mill
- ◆ 3-DIMM, 3-PCI, 1-ISA, SIO/PIO/USB
- ◆ BMB AGP, 2MB Flash, 1MB cache
- ◆ Much more!! 90-day warranty



**HSC#P599VM \$39.50**

### 56K modem/hub

- ◆ Four-port hub card, with 56K V90 modem
- ◆ For multi-PC web access!
- ◆ ISA-type, OEM package
- ◆ 90-day warranty



**HSC# 18942 \$17.50**

### Variable Transformer

- ◆ Model AECC 590
- ◆ 0 - 130 VAC output @ 5A
- ◆ 7" dia. (8.5" w/ext.), 6.5" tall
- ◆ Illuminated switch, meter
- ◆ New...90-day warranty



**HSC# 80474 \$45.00**

### Disk Drive Deals!

- 2.1GB IDE Laptop**
- ◆ Model No. DCRA-22160
  - ◆ 4200 cyl, 16 heads, 63 sec/T
  - ◆ 5VDC @ 520mA. (peak)
  - ◆ HSC 90-day warranty
- HSC# 19220**



**\$39.95**

### 4.3GB SCSI 1/2 HEIGHT

- ◆ ST15150N hard drive
  - ◆ 21 Hds, 11 Disks, 3,711 Cyl.
  - ◆ 7,200 RPM, 9.0 mS avg. seek
  - ◆ HSC 90-day warranty
- HSC# 18412**



**\$24.95**

### 9.1GB SCSI ULTRA-W

- ◆ Seagate ST19171WC
  - ◆ 7200RPM, 4.6mS av. latency
  - ◆ 80-pin connector
  - ◆ HSC 90-day warranty
- HSC# 18753**



**\$39.95**

### External CD-R/W!

- ◆ HP 7200 series CD-R/W
- ◆ Shares printer port
- ◆ 2X write, up to 6x read
- ◆ EIDE-(ATAPI) interface
- ◆ Power supply not included
- ◆ Refurbished, 90-day HSC warranty



**HSC# 19036 \$49.50**

## HSC Web Specials!

You can find these in the "Specials" area of our on-line shopping pages at [www.halted.com](http://www.halted.com)...check them out and use our secure site to place your order.

- 4-Port hub card  
**HSC# 18489 \$9.95**



- Mouse, 2-button  
**HSC# 18731 \$3.95**



- 10-Base T card, ISA  
**HSC# 18943 \$4.95**



- Tower, cabinet, 7-bay  
**HSC# 80544 \$42.50**



- SCSI Controller, PCI  
**HSC# 18218 \$9.95**



- Mouse, w/ keypad  
**HSC# 80539 \$4.95**



- Color camera, digital  
**HSC# 17503a \$9.95**



- SCSI Controller, ISA  
**HSC# 17995 \$7.50**



- Motherboard, 486DX4 AT  
**HSC# 18529 \$9.95**



- Batt charger, NiMH  
**HSC# 19151 \$17.50**



- AC Inverter 100W  
**HSC# 19021 \$14.95**



- A/V 'Firewire' card,  
**HSC# 80613 \$45.00**



Check out our  
Weekly Specials!  
[www.halted.com](http://www.halted.com)

- Networking Kit, ISA card  
**HSC# 80599 \$29.95**



- Solder Pot, 600W  
**HSC# 80611 \$97.50**



- 12VDC 40 AH, lead/acid  
**HSC# 18917 \$29.50**



- ATX, 145W Power Supply  
**HSC# 18350 \$9.95**



- Pixie2 Tranciever Kit  
**HSC# pixie \$9.95**



- Tablet PC Combo  
**HSC# 80604 \$99.00**



- Advanced Clamp Meter  
**HSC# 80609 \$110.00**



- Joystick, "FX2000"  
**HSC# 18772 \$3.00**



- Server Cabinet, ATX  
**HSC# 80541 \$149.95**



- Four-port hub card  
**HSC# 18944 \$14.50**



- Bargain DMM  
**HSC# 80370 \$14.95**



- ATX 200W Power Supply  
**HSC# 18665 \$14.95**



### PCMCIA Ethernet!

- ◆ EPSON Type II PCMCIA interface card
  - ◆ 10Base2 & 10BaseT cables included!
  - ◆ For notebooks/PCs with Type II slots
  - ◆ For Windows 3.1, 95/98
  - ◆ No jumpers or switches - Two LED status lights
  - ◆ New, boxed, diskette & manual, 90-day warranty
- HSC# 19125 \$9.95**



### PCMCIA SCSI!

- ◆ EPSON PCMCIA interface card
  - ◆ Epson/Adaptec APA-460B
  - ◆ Up to 2MB/sec. bus rate
  - ◆ For DOS, Win3.1, 95/98 & NT
  - ◆ OEM pack, w/DB-25 cable
  - ◆ 90-day warranty
- HSC# 19160 \$49.50**



For secure, online  
shopping...  
[www.halted.com](http://www.halted.com)  
Plus...more info...  
..BIGGER pictures!

### Clamp Meter

- ◆ Model No. AECC-2891
- ◆ AC Volt: 200/600 - DC Volt: 2-600
- ◆ AC Current: 200/600 Amps
- ◆ Diode/Continuity Test, Date Hold
- ◆ Up to 2 Meg Ohm, w/test probe
- ◆ New, 90-day warranty



**HSC# 80608 \$45.00**

### Handy Solder Pot!

- ◆ AECC-10P - handy compact desktop unit
- ◆ 110VAC, 60Hz - perfect for small jobs
- ◆ Adj. temp - 300 to 430 deg. C
- ◆ Bath: 36mm. dia x 30mm. deep
- ◆ New, OEM box, 90-day HSC warranty



**HSC# 80610 \$32.00**

### Lab Power Supply!

- ◆ AECC-350, 0-50VDC @ 3 Amp
- ◆ 110VAC, 60Hz - 150VA
- ◆ Digital voltage/current display
- ◆ Short-circuit protected
- ◆ New, w/IEC power cord, manual, 90-day warranty



**HSC# 80606 \$129.00**

# HSC Electronic Supply

3 Retail/Wholesale Locations in California:  
Main Office - Mail Orders...  
3500 Ryder St. Santa Clara, CA 95051

Santa Clara 1-408-732-1573  
Sacramento 1-916-338-2545  
Rohnert Park 1-707-585-7344

Since 1963!...  
Silicon Valley's  
Electronic Marketplace

Order Toll-Free:  
1-800-4-HALTED (442-5833)  
or...ONLINE, AT: [www.halted.com](http://www.halted.com)


Terms: Some quantities limited; all items are subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped by UPS Surface unless otherwise specified. \$6.00 UPS charge added for COD. Visit our website for detailed information on domestic and international shipping methods.


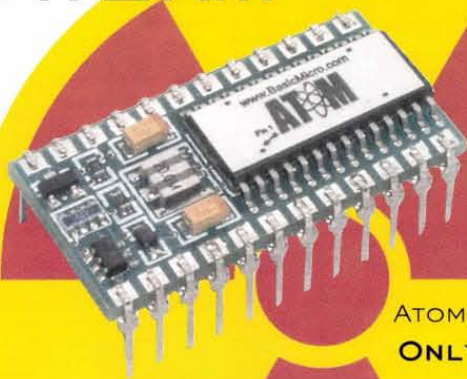
# MORE POWER...

The New Basic Micro Atom, offers more in the same package you are already familiar with. Built-in features like upgradeable firmware, Analog to Digital, Hardware Serial, In Circuit Debugging, 32 Bit Math, 32 Bit Floating Point Math and more !

The Atom includes powerful expanded BS2p syntax compatible software with commands such as; OWout, OWin, ADin, LCDwrite, If..Then..Elseif..Else..Endif, LCDread, HPWM, Hserout, Hserin, Do..While, Repeat..Until and more !



ATOM-IC MODULE  
ONLY \$59.95

## POWERFUL SOFTWARE

Easy to use multi document interface. Open as many files as you want all in the same interface. Easily navigate your files with the built-in explorer window.




## IN CIRCUIT DEBUGGING

Watch your program run step-by-step as the Atom executes each line of code. Easily debug your code. Bring your programs to life quicker than you ever thought possible !


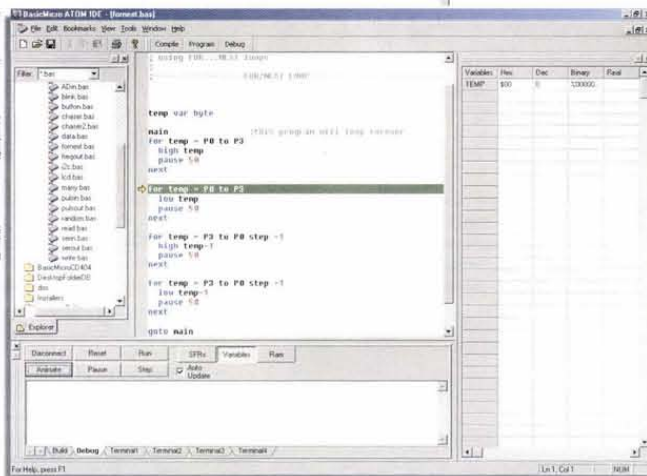
## WATCH IT COME TO LIFE


No more strategically placing debug statements throughout your program! Not only can you watch your program execute live, you can keep an eye on every variable and ram location as they are affected by your program. Each program variable is displayed in binary, hexadecimal and its real values.



## FEATURES

- Graphical Debugging (ICD)
- More Software Commands
- 32 Bit Integer Math
- 32 Bit Floating Point Math
- BS2p Compatible Syntax
- Expanded BASIC library
- Firmware upgradeable
- Unlimited Support
- Free Software Updates
- Plus More!
- Over 300 Bytes of RAM
- 256 Bytes of Data EEPROM
- External & Internal Interrupts
- 3 10 bit A/D Converters
- 2 Capture and Compare
- Internal Adjustable Vref
- + / - External Vref
- 3 Timers, 2 PWM
- UARTS, I2C, SPI
- Plus More!

## DEVELOPMENT KITS

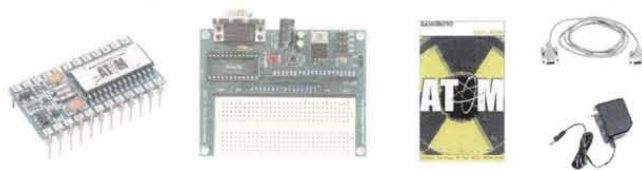

Kit Includes: Development Board, Atom, Manual, Cable and power supply

ONLY \$129.95

**BASIC MICRO inc**  
Microcontrollers Made Easy™

TO ORDER VISIT [WWW.BASICMICRO.COM](http://WWW.BASICMICRO.COM) OR CALL US AT 734-425-1744 M-F 10 AM TO 6 PM

The Atom is a registered trademark of Basic Micro Inc.

# Nuts & Volts

VOLUME 23 • NO. 2 • FEBRUARY 2002



## 9 LEARNING RVK-BASIC — PART 2

This session introduces a program that will use a small AVR to generate two different output frequencies simultaneously.  
**By Bob Van Kannon**

## 29 TRIAC PRINCIPLES AND CIRCUITS — PART I

Take a look at basic triac principles and some practical triac circuits. **By Ray Marston**

## 37 BUILD AN ANTIQUE ROBOT

Learn how to take an antique Erector Set and combine it with modern sensors, actuators, RC servos, and electronics to make totally "cawl" robots. Plus, much of the BASIC Stamp

BS2-based robotics software can be used with just a few modifications. **By Daniel Ramirez**

## 53 MUFFLE THE LOUDMOUTHS!

Keep those loud TV commercials on the straight and level with the Blab Buster — an automatic volume control device.  
**By TJ Byers**

## 68 KRONOS CRAWLER PHASE 2 — THE IR CONNECTION

It's time to add sensors to our robotic friend, but with an infrared remote control system. **By Michael Simpson**

## 75 NO-LICENSE HANDHELDS


If you are planning a ski trip or winter camping trip, bring along handheld radios for safety and staying in touch. But remember, not all handheld radios qualify for cold weather land adventures. Find out what's hot and what's not.  
**By Gordon West**



## COLUMNS
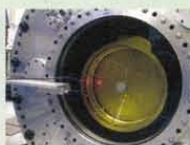
### TECHKNOWLEDGEY 2002

Spaceborne instruments capture solar wind; Lobsters provide design ideas for sensors; New operating system on its way; Another "World's Most Powerful" computer; Free program teaches arithmetic; Rotary position sensor only 2.1mm thick; and Zilog nearing the end?  
**By Jeff Eckert**



### ELECTRONICS Q & A

What's Up: Use your PC to help in the fight to find a cure for cancer. Answers concerning temperature sensors, controllers, non-contact sensing, and thermal imaging. Need to design a squarewave

6

oscillator? Got your numbers. And Gordon Moore's legacy. **By TJ Byers**

### LASER INSIGHT

Take a look at another kind of laser system that has deeply penetrated our industrial lives — the laser marker. **By Stanley York**

24

### STAMP APPLICATIONS

Weather on the Wire: Utilizing the 1-Wire weather station with the BS2p. **By Jon Williams**

46



### AMATEUR ROBOTICS

Learn how to wire and test the Power Drive Module (PDM) chassis for Heavy Iron. **By Robert Nansel**

62

## DEPARTMENTS

NV Bookstore	8
Reader Feedback	13
News Bytes	16
Tech Forum	33
Events Calendar	50
Classified Ads	57
Classified Ad Info	61
Dealer Directory	73
Advertiser's Index	74
Electronics Showcase	78
Prize Drawing	80
New Product News	81
New Books	83

# TechKnowledge 2002

Events, Advances, and News From the Electronics World

by Jeff Eckert

## Advanced Technologies

### Spaceborne Instruments Capture Solar Wind

**G**enesis, a remote-controlled space mission, went into orbit Nov. 16 around the Lagrange 1 (L1) point, a place nearly one million miles from the earth where the gravitational pulls of the earth and sun are equal. In December, its instruments began capturing particles of solar wind. Genesis will remain in this location for nearly 2.5 years and then return to earth. During this time, Genesis' instruments will collect samples of the solar wind to reveal the make-up of the cloud that formed the solar system nearly five billion years ago, which will help scientists understand the origin of the solar system.

Conventional wisdom is that the solar system was formed from a solar nebula (a cloud of gas and dust) that collapsed in on itself. Most of it formed the sun, but outlying particles became planets, moons, and comets. We have a general understanding of how that happened, but the composition of the initial nebula remains a mystery. However, its history is thought to be preserved in the outer layers of the sun, and the solar wind provides a continuous flow of that material into space. By analyzing this material (with a particular focus on oxygen content), it is believed that we can learn more about the nebula.

Los Alamos designed and built a solar wind concentrator to collect a high concentration of oxygen and return the sample back to earth for analysis. The

concentrator takes solar wind and passes it through a series of electrically charged grids into a bowl-shaped mirror. The mirror reflects a filtered stream of elements heavier than hydrogen upward into a centrally-poised collector tile where oxygen and other elements embed themselves.


Also aboard Genesis are solar wind ion and electron monitors. Genesis' ion and electron monitors instantaneously determine the speed, density, temperature, and approximate composition of the solar wind and translate that knowledge into actions for the solar wind concentrator and solar wind collector arrays.

Genesis will collect just 10 to 20 micrograms of solar wind, the equivalent of a few grains of salt. The extraterrestrial material will return to earth in 2004 for study by scientists around the world.
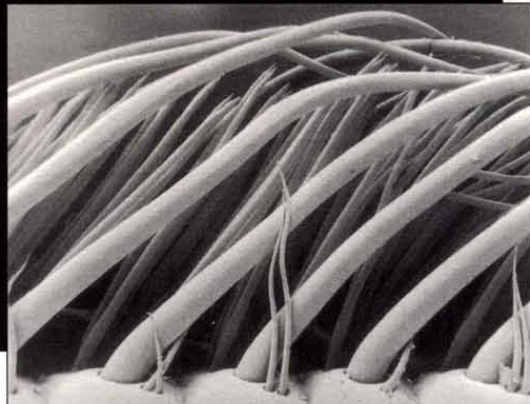
### Lobsters Provide Design Ideas for Sensors

**S**tudies being performed by researchers at the University of California, Berkeley ([www.berkeley.edu](http://www.berkeley.edu)) and Stanford University ([www.stanford.edu](http://www.stanford.edu)) are aimed at reverse engineering the olfactory sensors used by spiny lobsters to "sniff" their way around in the sea. According to Mimi A. R. Koehl, professor of integrative biology at UC Berkeley, "If you want to build unmanned vehicles or robots to go into toxic sites where you do not want to send a scuba diver, and if you want those robots to locate something by smell, you need to design noses or olfactory antennae for them. We are learning how animal antennae capture odor molecules from the water around them."

A scanning electron micrograph of the chemosensory hairs on the end of the antennules of the spiny lobster, *Panulirus argus*. The hairs sensitive to odors are in the center, protected by a phalanx of strong guard hairs. Courtesy of Jeff Goldman/Duke University, Oxford University Press©.



We want to understand

which designs of odor-catching antennae work successfully in nature so that they could provide inspiration for man-made antennae."

Lobsters and other crustaceans sniff by flicking a pair of antennules, dragging them through the water to bring chemosensory hairs on the ends of the antennules into contact with odor molecules. On the outer edge of one of the split ends of each antennule is a brush of hairs sensitive to chemicals. Understanding exactly how the lobsters collect and process data could provide a blueprint for electronic sensors that accomplish the same thing. The next step will be to work with neuroscientists who can help relate odor concentration in the hairs to electrical signals triggered by the hairs.

## Computers and Networking

### New Operating System On Its Way

**I**n 1998, Michael Robertson founded MP3.com, Inc., the well-known Internet music service provider. Now, he intends to shake up the personal computer world with a new company, **Lindows.com, Inc.** ([www.lindows.com](http://www.lindows.com)). While the product was not commercially available as of this writing, LindowsOS is described as a low-cost (under \$100.00) that can run both Linux® and Windows® programs. It is based on a Linux core, but will run Windows applications without any additional software. LindowsOS offers the usual graphical user interface (GUI) and will run on computer systems that


use a Pentium or AMD processor and have a minimum of 64 MB RAM and 1 GB of hard drive space. The product will be available for purchase directly from the company's web site.

According to Robertson, "Putting another choice on the shelf for consumers is the ultimate tonic for high prices, restrictive licenses, and intrusive security measures. The power to choose means consumers will be in the driver's seat and not beholden to the policies of one company."


Is anyone taking this little start-up company in San Diego, CA, seriously? One indication might be that Microsoft has already filed a trademark infringement complaint against Lindows.com. You see, Microsoft thinks that its 384 million users might be confused and unable to tell the difference between the two names, LindowsOS and Windows XP.
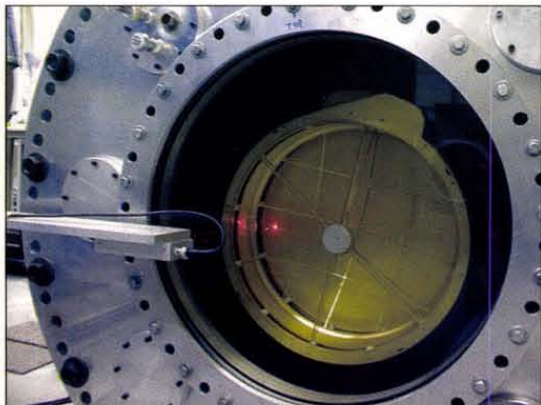
### Another "World's Most Powerful" Computer

**L**ogic tells us that there can be only one world's most powerful computer at any one time, but there are several hundred supercomputers whose owners proclaim them to be the "world's most powerful." This is accomplished by modifying the claim to include only a particular task. For example, the machine on my desk is the world's fastest computer used to generate these columns. And IBM ([www.ibm.com](http://www.ibm.com)) is assembling a system that is being touted as the "world's most powerful weather supercomputer." Marketing hyperbole aside, the "Blue Storm" system, being produced for the European



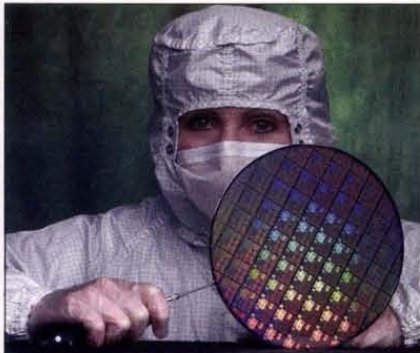The solar wind concentrator undergoes testing inside a vacuum chamber. A laser sensor located on the arm in front of the vacuum window is being used to check the flatness of the thin, high-voltage screens (invisible in this photo) that stretch across the front of the instrument. Courtesy of Los Alamos National Laboratory.



Software engineer Daria Dooling examines a wafer of IBM Power4 chips destined for the company's eServer p690 computer. Each Power4 chip contains 174 million transistors. The Power4 chip functions like an individual computer and contains two high-speed processors, a system switch, memory, and I/O functions. Information

flows between the memory and the processor at nearly 125 GB per second. Courtesy of International Business Machines Corporation. Unauthorized use not permitted.

Centre for Medium-Range Weather Forecasts (**ECMWF**, [www.ecmwf.com](http://www.ecmwf.com)), is a formidable machine, based on an IBM eServer Cluster 1600 supercomputer built with multiple eServer p690 enterprise UNIX servers and code-named "Regatta." The computer will provide advanced weather information to help with activities that include early warning of severe floods, navigation assistance for ships at sea, and planning of family picnics. ECMWF researchers will access Blue Storm via an IBM IntelliStation workstation running Linux, and others in Europe will be able to access it via a wide area network. According to an ECMWF representative, the system will offer advancements in three areas:

It will take better advantage of information provided by an enhanced network of satellite observation systems. Blue Storm will help scientists more accurately determine the initial state of the atmosphere and oceans, thus significantly improving the Centre's forecasts.

It will offer enhanced representation of heating and cooling, cloud formation and dissipation, rain, snow, and other processes in the Centre's model of the global atmosphere. The model uses 21 million grid points distributed throughout the atmosphere between the surface and a height of 65 km.

It will improve the techniques developed by the Centre, based on chaos theory, to estimate the uncertainty in the forecasts and the probabilities of alternative developments over the coming week, month, and season.

The system, to be delivered in stages from 2002 through 2004, will be based on a cluster of p690 enterprise servers initially capable of seven teraflops. This will be expanded to 20 teraflops in the final installation. Also included will be a range of data storage products. The price of the system was not announced.

## Free Program Teaches Arithmetic

**A**t the other end of the scale of computational requirements is a free arithmetic education program available from Argonne National Laboratories. "The ArithmAttack" is designed to answer the provocative question, "How many randomly generated arithmetic problems can your elementary-school children answer in 60 seconds?" The game randomly creates problems using numbers that the user sets between 0 and 25. Users can focus exclusively on addition, subtraction, multiplication, or division, or random combinations of these. You can download the free software ([www.anl.gov/OPA/attack.htm](http://www.anl.gov/OPA/attack.htm)) and play the game on any computer running a Windows 95 or higher operating system. For non-Windows computers, an earlier version, written in JavaScript, can be played or downloaded on the World Wide Web at [www.dep.anl.gov/aattack.htm](http://www.dep.anl.gov/aattack.htm) or downloaded free for use on individual computers. The JavaScript version runs as a Web page on Microsoft Internet Explorer, version 3.0 or higher, and Netscape Navigator, version 3.0 or higher.

## Circuits and Devices

### Rotary Position Sensor Only 2.1 mm Thick

**M**urata Electronics North America ([www.murata.com](http://www.murata.com)) has introduced a new contact rotary position sensor (PVS1 series) for the automotive and entertainment markets. Using highly resistive materials and wipers, the surface mount rotary position sensor is said to have a rotational life of one million cycles. Murata also claims a greater level of accuracy and reliability than in competitive products, and a very thin design profile of only 2.1 mm. The PVS1

series is designed for use in a variety of industries. Among its applications for the automotive market are automatic seat and mirror position adjustments, as well as trunk opening and climate control regulation. The sensor works by detecting the angle and position of equipment through a change in the output voltage. In addition to automotive applications, the sensor is suited for use in the entertainment industry. The sensor can be used in robotic pets, electronic motor driven bicycles, and radio-controlled toys. The PVS1 series also provides lead-free construction, making it suitable for the high peak temperature re-flow soldering process and compliant with environmental regulations. It also incorporates sealed construction, giving it a stable performance, as well as a D-formation through-hole rotor (which enables the selection of many kinds of gear shapes). The series is available in a tape-and-reel package. The sample price for the PVS1 series is approximately 50 cents. The lead time for volume purchases is eight to nine weeks.

## Industry and the Profession

### Zilog Nearing the End?

**I**n the early 1980s, when IBM executives still believed that the personal computer was a passing fad, most microcomputers ran Digital Research's CP/M operating system and were driven by Zilog's venerable Z-80 processor. Prominent among them were

RadioShack's TRS-80 (affectionately known as the "Trash-80"), the Osborne 1, and various Kaypro models. But when IBM finally awoke, the company decided to demolish the existing competition by basing its machines on Microsoft's MS-DOS operating system and Intel's 8086 microprocessor, thus imposing a new industry standard. (Had IBM decided to develop its own operating system, Bill Gates would probably be selling home appliances at a Sears store now, but never mind.) The result was a relatively quick death for Osborne, Kaypro, Digital Research, et al. However, because the Z-80 was essentially a very nice piece of hardware that could also be adapted for use in a range of low-end microcontroller applications, Zilog managed to hang on.

The company is still breathing, but it recently announced plans to enter Chapter 11 bankruptcy after defaulting on an interest payment on its \$280 million debt. Creditors have agreed to trade the \$280 million owed to them for a \$30 million unguaranteed note, which could put the company on firmer financial ground. "We have made significant progress in returning Zilog to full financial health," said Jim Thorburn, chief executive officer. "We have a cash flow positive business and, on approval of this plan, we will substantially strengthen our balance sheet, with the elimination of our senior notes." But will the company continue to survive with a small niche in a very competitive market? Well, maybe. **NV**

## Tools for the Imagination

### Micro Modules



### Specialty Products




### RTC Processor Boards

With dozens of embedded controllers and countless configurations, we can help you turn your imagination into reality. For a complete look at our product line, visit our website at [www.micromint.com](http://www.micromint.com).


**Micromint**

[www.micromint.com](http://www.micromint.com)


(800) 635-3355

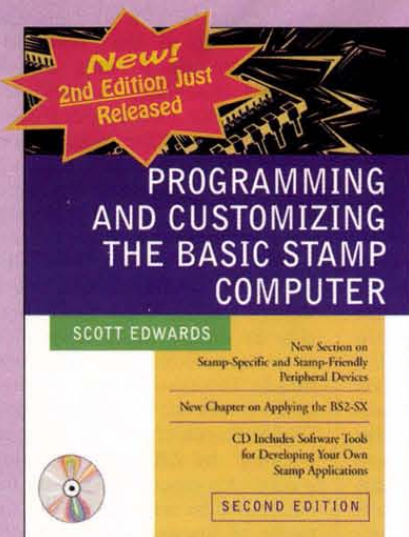

\$39.95 List **\$35.95** Subscriber

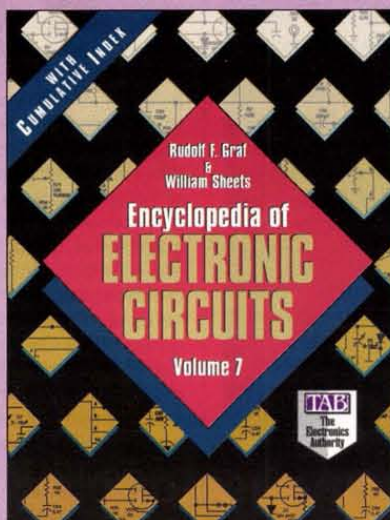

\$39.95 List **\$35.95** Subscriber

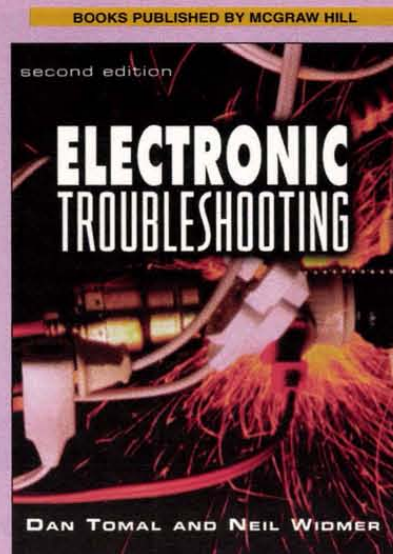


\$34.95 List **\$31.45** Subscriber

# 10% OFF


**ON SELECTED TITLES  
FOR PAID SUBSCRIBERS**
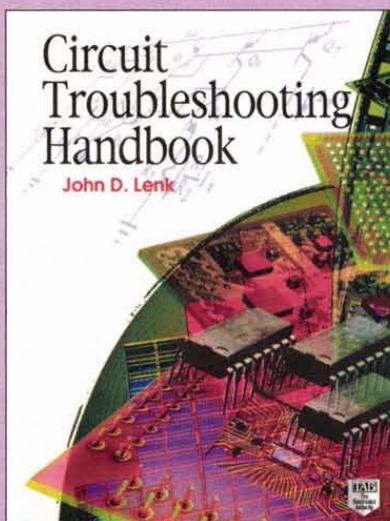
## Nuts & Volts Book Store


*Now you can order  
on-line! Check out  
our Book Store at  
[www.nutsvolts.com](http://www.nutsvolts.com)  
for a complete listing  
of available titles.*




\$39.95 List **\$35.95** Subscriber

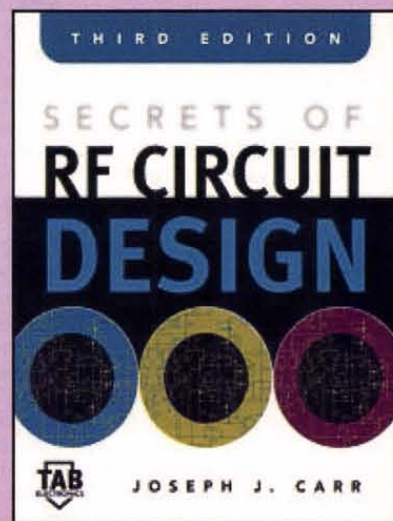

\$39.95 List **\$35.95** Subscriber

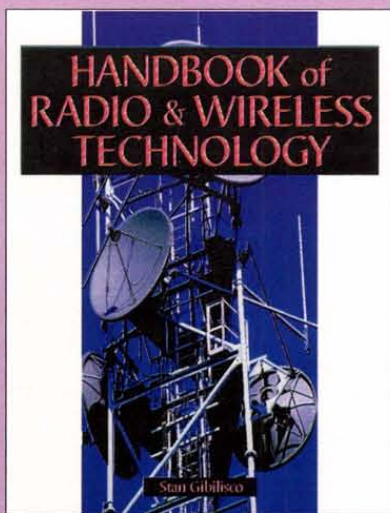

\$44.95 List **\$40.45** Subscriber

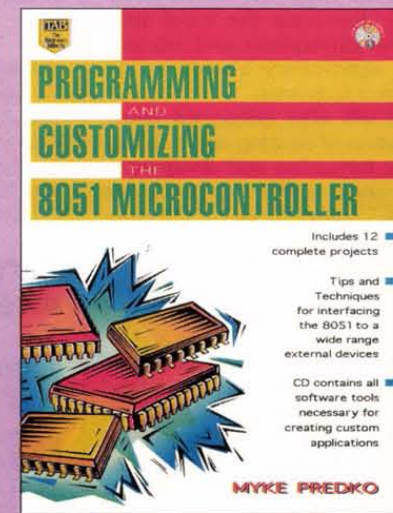

\$49.95 List **\$44.45** Subscriber

**Call 1-800-783-4624 today!**

**WE ACCEPT VISA, MASTERCARD, AMERICAN EXPRESS**

Send check or money order to Nuts & Volts, 430 Princeland Court, Corona, CA 92879. Include a complete shipping address (no P.O. Boxes, please). Shipping & handling \$4.50. CA residents add 7.75% sales tax. Or, call our toll-free order-only line at 1-800-783-4624 and use your MasterCard or Visa. Or order on-line at [www.nutsvolts.com](http://www.nutsvolts.com). **ALL ORDERS MUST BE PREPAID.**

# Learning RVK-Basic

## Part 2

By Bob Van Kannon

**R**VK-Basic is a free Basic compiler for the Atmel AVR line of microcontrollers. You can download a copy of this compiler from the *Nuts & Volts* web site. With this compiler you can write and compile very fast, efficient programs for most of the AVR microcontrollers.


In this lesson, we are going to introduce a program that will use a small AVR to generate two different output frequencies simultaneously. You will want to build this one and get it working and keep it around because it will be very useful for checking out the code in the third article of this series.

By all means, do not be alarmed if you do not understand all of this program at this point in your learning process. It really is too much program for some rookies at this point, but I am giving this to you now so

that you will be able to use the working device as a stimulus for the next article in the series.

The idea behind this design is that we will use the counter-timer (called TIMER 0) on the chip to establish a time-base. Using this time-base, our software will vary the two output frequencies according to an eight-bit DIP switch. This will allow the user to change either of the two output frequencies independently by throwing switches.

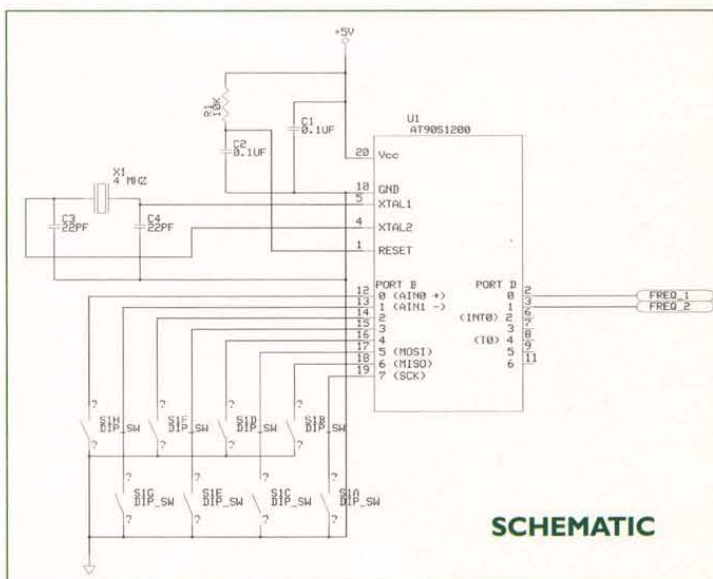TIMER0 is a free-running counter. It is a piece of hardware on the chip that will count continuously in real time without any software intervention. In software, we can read this timer any time we want to. To help clarify the idea, the following picture shows a real-time picture of the TIMER and the two outputs when one output is half the TIMER frequency and the other is 1/6 of the



[WWW.POLARISUSA.COM](http://WWW.POLARISUSA.COM)

OVER 700 DIFFERENT PRODUCTS IN STOCK!!!

800-752-3571

LIPSTICK CAMERAS • DIGITAL RECORDERS • CALL OR CHECK ON-LINE TO ORDER YOUR FREE COLOR VIDEO CATALOG • MICRO CAMERAS • WIRELESS VIDEO


B/W INFRARED LIPSTICK CAMERA	DIGITAL MONITORING & RECORDING SYSTEM	1/3" COLOR OUTDOOR CAMERA					
<p>Designed for surveillance applications, the LP-850W B/W Infrared Camera operates in extreme low-light conditions. Recently developed technology allows this camera to see in total darkness up to 20 feet away with built-in LEDs. Excellent for mounting on a wall or ceiling. Infrared light is controlled by an auto-sensing photo cell.</p> <p><b>LP-850W - \$99.95</b></p> <p>Call today for more information!</p>	<p><b>"YOUR WEB BROWSER IS YOUR REMOTE EYE!"</b></p> <p>The PV-140 Series PCI cards are the solution for digital security using a PC. Turn your own PC into a commercial grade digital security system in a few minutes. The system brings together several separate components that priced individually could send a small business or home owner to a loan officer.</p> <p>The PV-140 Series integrates a color quad processor, multiple zone video motion detector, multiplexer, and a real time digital video recorder (DVR).</p> <p>✓ TCP/IP ✓ MODEM ✓ LAN/WAN</p> <p><b>PV-140-A - \$299.95</b></p> <p>Works Great With Our Wireless Receivers, Too!</p> <p><b>PV-140-B</b> Each card can connect up to 4 cameras.</p> <p><b>PV-140-D</b></p> <p><b>GFR-2400 - 2.4GHz Receiver</b></p>	<p>This camera merges the gap between bullet or lipstick cameras and full-size housings with cameras. Unlike bullet or lipstick cameras with limited features, this unit has many features only found on larger, cased cameras. The AV-48WC8 keeps the best part of the bullet/lipstick line in that they install quickly and come pre-assembled, ready for installation. Auto iris and var-focal lens options are available upon request. We have 5 different configurations to meet your requirements for outdoor or indoor self-contained cameras.</p> <p><b>AV-48WC8 - \$235.95</b></p> <p>8 Configurations</p> <ul style="list-style-type: none"> <li>B/W: Regular, Auto Iris, Var-Focal Lens</li> <li>Color: Regular, Auto Iris, Var-Focal Lens</li> </ul> <p>Industrial "O" Ring Sealed, Aluminum Case</p> <p>Made in the USA</p>					
<p><b>2.5" COLOR TFT FLAT SCREEN MODULE</b></p> <p>Our new color 2.5" TFT module can be used for a variety of purposes such as: custom automotive dash installations, boat installations, covert ultra-compact surveillance packages, and more.</p> <p><b>TFT-M25 - \$139.95</b> (Driver board not shown)</p> <p><b>UNIT IS ONLY 5.8mm THICK!</b></p> <p>Dimensions: 61.6(W) x 49.3(H) x 5.8(D)mm</p>	<p><b>TIME LAPSE RECORDER</b></p> <p>The CTR-024 is a 4 head Helical Scan Azimuth System which offers 350/300 TV lines of resolution (B/W / Color). Maximum recording times are adjustable and include 2/12/24 hours. There are five different programmable recording modes that are built-in to the CTR-024 which include: Alarm, Series, Repeat, 1-Shot, Timer. Each unit has a time/date display and a 30 day Battery Backup. This is an excellent recorder for the price!</p> <p><b>CTR-024 - \$299.95</b></p> <p>Call today for more information or visit our website to see our entire selection of time-lapse and real time recorders.</p> <p>(Portable 12V DC Models Available)</p>	<p><b>5" COLOR WIRELESS OBSERVATION SYSTEM</b></p> <p>ADD UP TO 3 ADDITIONAL CAMERAS!</p> <p>Now you can enjoy peace of mind with our new wireless observation system. Comes with a 5" wireless color monitor, a wireless color camera, Just Plug-&amp;Play for perfect wireless video any time! Great for around the house, office or technical field work.</p> <p><b>2.4GHz</b></p> <p><b>GW-2400SA - \$379.95</b></p>					
<p><b>MICRO VIDEO HEAD "SNAKE" CAMERA</b></p> <p><b>VIDEO HEAD IS ONLY 7MM IN DIAMETER!</b></p> <p>The MH-SC01 features a fully adjustable focus from 0.5 inches to infinity. It contains a true color CCD chip rather than a CMOS type sensor for excellent resolution. Each comes complete with a 20' camera head cable and power cable.</p> <p><b>MH-SC01 - \$479.95</b></p>	<p><b>MICRO BOARD CAMERAS - MANY MODELS TO CHOOSE FROM!</b></p> <table border="1"> <tr> <td><b>MB-1250HRVF</b> Color Varifocal 4mm-8mm Lens 1.26" x 1.26" x 2.38" \$169.95</td> <td><b>MB-1250HRP</b> Hi-Res Color Pinhole 5.0mm Lens 1.27" x 1.27" \$109.95</td> <td><b>MB-650U</b> B/W Audio 4.3mm Lens 1.18" x 1.18" \$39.95</td> <td><b>MB-1250P</b> Color Pinhole 5.0mm Lens 1.27" x 1.27" \$89.95</td> <td><b>MB-810B</b> Infrared B/W 3.6mm Lens 1.7" x 1.7" \$69.95</td> </tr> </table>	<b>MB-1250HRVF</b> Color Varifocal 4mm-8mm Lens 1.26" x 1.26" x 2.38" \$169.95	<b>MB-1250HRP</b> Hi-Res Color Pinhole 5.0mm Lens 1.27" x 1.27" \$109.95	<b>MB-650U</b> B/W Audio 4.3mm Lens 1.18" x 1.18" \$39.95	<b>MB-1250P</b> Color Pinhole 5.0mm Lens 1.27" x 1.27" \$89.95	<b>MB-810B</b> Infrared B/W 3.6mm Lens 1.7" x 1.7" \$69.95	<p><b>VDM-01 - 199.95</b> Back Panel View</p> <p>The VDM-01 is the answer to watching from in front of a monitor searching for the event that occurred. This 4-zone video detection unit will allow you to place 4 areas of interest on the camera screen. The sensitivity can also be adjusted so false triggers do not set your VCR to record. Imagine a zone on the cash box or a zone on just one bin box in your inventory room. No more watching hours of uneventful video on your surveillance tapes. Set-up one of these systems as part of your office or company wide security system and you will be amazed. This is a great management tool for revealing the non-productive habits in the office. This system is compatible with any time-lapse or real time recorder with alarm inputs.</p>
<b>MB-1250HRVF</b> Color Varifocal 4mm-8mm Lens 1.26" x 1.26" x 2.38" \$169.95	<b>MB-1250HRP</b> Hi-Res Color Pinhole 5.0mm Lens 1.27" x 1.27" \$109.95	<b>MB-650U</b> B/W Audio 4.3mm Lens 1.18" x 1.18" \$39.95	<b>MB-1250P</b> Color Pinhole 5.0mm Lens 1.27" x 1.27" \$89.95	<b>MB-810B</b> Infrared B/W 3.6mm Lens 1.7" x 1.7" \$69.95			

800-752-3571  
Tech 404-872-0722 • Fax 404-872-1038

[WWW.POLARISUSA.COM](http://WWW.POLARISUSA.COM)

**POLARIS INDUSTRIES**  
470 Armour Drive NE • Atlanta GA 30324-3943
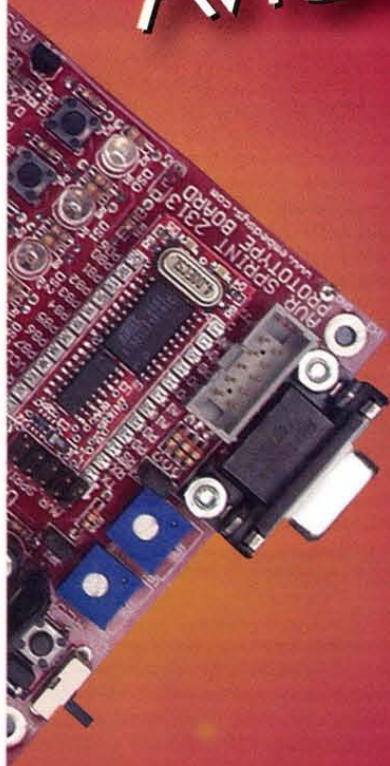
# Lick the Stamp<sup>™</sup> with AVRSPRINT<sup>™</sup>



## Speed

10x faster than the Stamp  
Up to 20 MIPS

## Freedom

Royalty Free Code

## Flexibility

Program in BASIC, 'C',  
or Assembler

## Seamless

Edit, Compile, then  
Download to Target

### AVR Sprint 8535 Development System \$189.95

- AVR Sprint 8535 module Program the Sprint in circuit.
- AVR Sprint Experimentation Station II<sup>™</sup> Includes programming cable, power supply, CD with Sprint Basic (full version) and C compiler, printed Sprint Basic manual, and complete device descriptions manuals.

### AVR Sprint 2313 Development System \$134.95

- AVR Sprint 2313 Microprocessor Module Program the Sprint in circuit.
- AVR Sprint 2313 Experimentation Station Includes 1 AMP regulated power supply, programming cable, 8 LED's and 8 switches. Includes reset switch, connector for output to standard LCD displays, 2 analog voltage sources, in addition to a prototyping area, and wall power supply.
- Sprint Basic Compiler<sup>™</sup> Plus the GNU 'C' Compiler.

See our Web site for additional AVR Sprint products.

# Embedsys.com

(763) 767-2748 • ESI 11931 Highway 65 NE, Mpls., MN 55434

AVR Sprint, Sprint Basic, and "Lick the Stamp" are registered trademarks of ESI. AVR<sup>™</sup> is a registered trademark of Atmel<sup>™</sup>, Inc. IFC is a registered trademark of Philips Electronics NV. Other trademarks are the trademark of their respective companies.

timer frequency. The top output changes on every change in TIMER0. The lower output changes on every third change in TIMER0. The numbers across the top are the states of TIMER0 and the waveforms are the resulting outputs.

In order to use TIMER0 we need to use the TIMER0 statement in RVK-Basic to turn it on. The statement will

take the form `TIMER0 ON N`, where N is 1, 8, 64, 256, or 1024. N is called a prescaler because it scales the AVR's clock down by dividing its frequency by N. So if N is 64 and the processor is running at 4 MHz, TIMER0 will be running at 4 MHz divided by 64, or 62.5 KHz.

Another statement we will use is the `PAUSE` statement. This simply

```
DEVICE 1200
MHZ 4
REVISION FGEN 011016.1-RVK
```

```
DIRPORT D,OUT
'DIRPORT B,IN
OUTPUT B,&HFF
```

```
'= B is input port. Bottom four bits control output1. =
'= top four bits control output2. =
'= On startup, the bottom four bits control the freq =
'= range. =
'= Output3 is set to timer0 freq / 2. =
```

```
EQU "D,0","OUT1"
EQU "D,1","OUT2"
EQU "D,2","OUT3"
```

```
PAUSE 50 '..allow system to settle
```

```
IMPORT sftcnt,B
INCR sftcnt '..a software frequency divide by sftcnt
... 1 <= sftcnt <= 256 ....
```

```
TIMER0 ON 64 '..TIMER FREQ IS 62500 Hz...
 '..Max OUTPUT is 31250 HZ/sftcnt...
 '..Min OUTPUT is 1953 HZ/sftcnt...
```

```
I1 = 10 '..logical frequency divider for output1
I2 = 11 '..logical frequency divider for output2
```

```
'-----BEGIN MAIN LOOP-----
```

```
MAIN: DO
 '..toggle output 1?...
DECR I1
IF I1 = 0 THEN
IMPORT temp,B
I1 = temp AND &H0F
INCR I1
TOGGLE "OUT1"
END IF
```

```
'..toggle output 2?...
DECR I2
```

```
IF I2 = 0 THEN
IMPORT I2,B
SHIFT I2,4,RIGHT
INCR I2
TOGGLE "OUT2"
END IF
```

```
FOR temp = 1 TO sftcnt
 '..wait for next timer tick...
TIMER0 READ ctime
WHILE ctime = oldtime
TIMER0 READ ctime
WEND
oldtime = ctime
TOGGLE "OUT3" '..OUTPUT3 runs at TIMER0/2 freq...
NEXT
LOOP
```

```
'-----END MAIN LOOP-----
```

You can run this program on an STK200 or STK500 board, to see it work. To compile this program, put FGEN.BAS in the directory where the compiler is and enter:

```
RB FGEN
```

What you do next depends on how you intend to program the device. If you are using Windows software to program through a serial cable, enter:

```
ASMHEX FGEN
```

The file you need for programming will be in FGEN.HEX. If you are using the parallel described in RBP.TXT, enter

```
ASM FGEN
RBP FGEN /1200/Y
```

causes the program to wait for the number of milliseconds specified after the word "PAUSE." In our case here, I will insert a 50 millisecond pause after power up to allow the voltages on the input switches to stabilize before we read them.

Another new idea in this program is the OUTPORT command for an input port. PORT D is our output port where the frequencies come out and PORT B is the port where we will read the DIP switches. When we write a 1 out to any bit of a port which is in an input state, we turn on a pull-up current source for that port. By doing this to all eight pins of PORT B, we allow the DIP switches to be connected without any further need for external pull-up resistors. L1 and L2 in this program are byte variables used for storing the commands for each output frequency.

SFTCNT is a byte variable that controls the scaling of the frequencies. It is read only at power up and thereafter remains fixed until the next power cycle. Before you turn power on to the unit, set the switches to control SFTCNT.

Where F is the frequency of the processor clock and B is the number on the DIP switch at power up, the maximum frequency of either output will be:

$$F_{max} = F / 2 / (B + 1)$$

The minimum frequency out of either output will be

$$F_{min} = F / 32 / (B + 1)$$

Other statements new to the student in this program are "INCR," "IF," "END IF," "WHILE," and "WEND." These will be explained in detail in further articles, but to see the details of their usage now, look them up in the file RB.TXT that comes with the compiler.

In the following program (which I have named FGEN.BAS), we read the DIP switches into SFTCNT, set up the TIMER0 to run at the processor clock divided by 64, and set L1 and L2 to temporary values which will be in effect only until the first transition on each output. Thereafter, the output frequencies are set by the last

known state of the DIP switches.

In the MAIN loop of the program, we first decrement the output control variable (I1 or I2) and check to see whether we have reached 0 yet. When we reach 0, we toggle the output line and read in the control variable again.

The SHIFT I2, 4, RIGHT statement causes the upper four bits of the DIP switch to move to the lower four bit positions of I2, thereby making the upper four switches behave for output 2 exactly like the lower four control output 1. The SHIFT command will be treated in more detail in a later lesson, but you could look it up now in RB.TXT.

After we've finished toggling or skipping each output, we come to a

FOR statement (see RB.TXT again). This is a simple counting loop that counts from 1 to SFTCNT. Inside the loop, we have a WHILE loop that waits until we see a change in the TIMER0 state. So the FOR loop will delay the program for SFTCNT transitions in TIMER0.

Toward the bottom of the FOR loop, you will notice that I have placed a command to TOGGLE the D2 pin. This is there solely for debug. No matter where you have the switches set, the D2 pin should be

running at a constant frequency of the processor clock divided by 128. Check out the complete program listed in the shaded box.

In our next installment, we will need two separate frequency inputs. So if you don't happen to have to signal generators laying around, you will want to build a piece of hardware to run this program. I am including a schematic that you could use to do this. Program your processor on your development board and then plug it into the board you build according to

the schematic.

You'll notice that there is no power supply on the schematic and no output connector. These are details left up to you. You could decide to put a three-terminal regulator on this board if you wanted to. Do make certain that you have power and ground correctly connected to the processor before you actually insert a processor.

You get this one going and I'll be back with a device that measures frequencies next time. NV

# ALL ELECTRONICS CORPORATION

QUALITY Parts  
FAST Shipping  
DISCOUNT Pricing

CALL, WRITE, FAX  
or E-MAIL For A  
Free 96 Page  
CATALOG.  
Outside the U.S.A.  
send \$3.00 postage.

## Cheap LED Flasher

The simplest electronic flasher ever. Great for attention getting displays, party decorations, night time warning signals. A red 5mm LED with flasher chip is attached to a battery snap that snaps onto a 2 AA cell battery holder. Will flash for months on a set of batteries. Flash rate, approximately 120 flashes per minute. Batteries not included.

CAT# FSH-10  
**\$1.00** each  
100 for 70¢ each  
500 for 60¢ each  
1000 for 50¢ each

## Special Purchase! 5 Vdc 1.9A Switching Power Supply

Autec # DT25-1004  
Input 100-240 Vac  
Output: 5 V @ 1.9 Amp, 8 V @ 1.1 Amp, 15 V @ 0.36 Amp, -15V @ 0.09 Amp. If you need a constant regulated output for scanners, cameras or sensitive equipment, have a look at this inexpensive benchtop supply. 3.25" x 6.39" x 2.35" high. 7" 6" output cord is terminated to custom Molex-type connector. Requires detachable IEC power cord like our CAT# LCAC-60. UL, CSA listed.

CAT# PS-531  
**\$5.00** each  
10 for \$4.50 each  
50 for \$4.00 each  
100 for \$3.50 each

## LED Tester

Pocket size led tester. Makes it easy to check functionality, color, brightness and uniformity. Plug any leaded LED into one of 12 positions on the socket strip to test at current ratings from 2-50mA. The seven middle positions on the strip are set at 10 mA allowing comparison of LEDs in those spaces. Requires 9 v battery (not included).

CAT# LT-100  
**\$8.95** each

## Nickel-Metal Hydride 4.8V 850 mA/h Battery Pack

Philips # 25733. New, rechargeable pack manufactured for cell phones. Contains four 1.2 Volt, 850 mA/h cells. Each cell is 1.8" x 0.65" x 0.3". With little effort you can remove the cells from the enclosed battery pack and reconfigure them to suit your needs.

CAT# NMH-53  
**\$2.00** each  
10 for \$17.50

## 1.38" Piezo Disc

Kyocera. 35mm brass piezo element with exciter circuit. Three 2" wire leads. CAT# PE-44  
**\$1.00** each  
10 for \$8.50  
100 for \$60.00

## Video / RF Modulator

Converts audio and video line level signals to RF which can be inputted to any television on channel 3 or 4. Channel 3-4 selector switch. Video, audio and power inputs are through a 7 foot cable terminated with a mini-DIN plug which generally needs to be cut off so connections can be made directly to conductors in cable. We supply a hook-up diagram. Requires a 4.5 - 6 Vdc, 50 mA power supply or wall adapter (not included).

Large quantity available. **\$5.00** each  
CAT# MOD-6  
10 for \$4.50 each

## CCFT Lamp 3.2mm X 250mm

3.2 mm diameter X 250 mm long. White. JKL BF3250-20B. CAT # BF-3250  
**\$7.50** each  
100 for \$6.00 each

## Inverter, 5 Vdc Input

TDK-2090. Inverter for small to medium CCFT lamps. Operates on 3-5 Vdc. No official specs available at this time. Our tests indicate that it lights lamps of 250mm length or less. Module is 2.17" x 1.1" x 0.4" high. PC pins on 2" x 0.84" centers. Large quantity available. CAT# INV-7  
**\$5.00** each

## 16 Character X 2 Line LCD with LED Backlight

Alesis Corp. G8 LCD 16 x 2 LCD. Module size: 4.85" x 1.7". Display size: 3.67" x 1.05". Black bezel around the display, 4" x 1.46". Input through 16 pin male header, 2 x 8 pins on 0.1" centers. LED backlight operates on 5 Vdc. No spec or hook-up sheet available. CAT # LCD-68  
**\$5.00** each

## Lithium Ion Battery Pack

Audiovox# BTE-600 7.2 V 1000 mAh lithium ion battery pack. Great for use in any applications requiring rechargeable power. Lithium batteries have no "memory-effect" and do not need to be discharged before recharging. Consists of two cells in a fully-enclosed plastic case with a protective cover. Each cell is 2" long x 0.80" dia. Battery pack size: 2.45" x 1.92" x 0.95" thick. CAT# BTE-600  
**\$3.50** each  
10 for \$3.00 each

ORDER TOLL FREE 1-800-826-5432  
Shop ON-LINE [www.allelectronics.com](http://www.allelectronics.com)

MAIL ORDERS TO:  
ALL ELECTRONICS CORP.  
P.O. BOX 567 • VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524  
E-MAIL [allcorp@allcorp.com](mailto:allcorp@allcorp.com)

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$6.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

**LINEAR SLIDE, from THOMSON.**  
Type: ACCUGLIDE RD10HL0836, with 33" RAIL  
Recirculating, miniature series, supplied  
with three type CD10AAAH carriages  
per rail. Like new, removed from lab  
equipment. Load bearing in all  
directions. Accurate to  $\pm 0.04$  mm  
typical. Rail Size: 0.39" W x 33" L x 0.35" H. Slide size: 1.02" W x 1.58" L x 0.52" H  
**These are really nice. Very limited quantity. Thompson-33.....\$95ea.**

**NEW, "STEALTH CAM", MICRO, with AUDIO!**  
The sleek aluminum housing fits like a glove! Removable mounting bracket and a 1.3M cable with BNC vid., RCA aud., (interf. mid) & DC barrel jack for, no sweat hook up. Why fool around with an open P.C. board? Now you can have the "STEALTH CAM": 1/3" CCD, 410 Lines, 0.3 Lux, AGC, Auto Shutter. Pwr. from 9 to 12VDC @110mA, 250k pixels, Std. model, 4mm, 78° FOV lens, Pinhole model, 90° FOV. A real glass lens. Focus from 10mm to infinity. NTSC video out. Only 1.7 ounce! SENSITIVE to IR. Size Std: 30mm sq. x 29mm d. PH is 16mm d.  
**WARNING:** Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS  
**GM-2000S-STD, w/audio.....\$69 OR GM-2000S-PH, w/audio .....\$69**

**IEE, 1X20 VACUUM FLUORESCENT DISPLAY MODULE**  
New, model S03601-82-02C series module includes, VFD, microcomputer and driver. Connects directly to the system bus via 8 bit, TTL compatible input. Display up to 20 dot matrix, 5 x 7 characters (96 character U.S. ASCII-7), 5mm H x 3.5mm W with cursor. Display is green at 505nm. Brightness is 1700L. Weight: 4 oz. Size: 6.63" L x 2.2" H x 0.6" thick. 5VDC @ 366mA. Perfect for any high visibility display requirement. With data. **IEE-VFD20..\$12ea. 4 for \$39**

**B&W QUAD PROCESOR,** The GM4-BQ is an unbeatable value. Four camera inputs with loop through. Full screen image, REAL TIME display, high resolution: 960 x480, brightness adj., for each chan. Alarm time 11-20 sec. 1.4 alarm inputs. Auto Sequencing mode with adj. dwell-1.4 sec. Quality video processing. Specs: 4 video inputs, 1 monitor out and VCR in/out, 4 alarm inputs, Buzzer #2 Alarm Out #Dim: 239 x166 x55 mm. **GM4-BQ QUAD.....\$169**

**NEW, GM960R TIME LAPSE VIDEO RECORDER**  
Finally a brand new, 4 head, T/L recorder with all the features at a price you can afford. Features: • Up to 960 hours on a standard T-120 VHS tape. • 12 different modes for record and playback • Audio recording in the 12H and 24H mode. • 30Day memory backup • Easy mode setting. • On-screen menus • Auto-repeat recording mode • Serial or One-shot recording • Time, Date, speed, and Alarm indicators on screen. These deluxe units are front loading and are 14"W x 3.5"H x 12.2"D, 110VAC powered. **SPECIAL, GM960R-VCR .....\$379ea.**

**A VIDEO MICROSCOPE in the PALM of your HAND!**  
**NEW, MAGCAM, VIDEO INSPECTOR, OFFERS HIGH POWER and LOW COST.**  
Two optical magnifications at the flick of a lever. Choose either 40X or 140X.  
A high quality, digital, color CCD camera, with dual optical magnification settings and built in object illumination via two ultra bright, white LED's. Entire system is fully integrated into a rugged and ergonomically designed, hand held unit only 2.7" W x 3" H x 1.8" D. Video output is standard NTSC via a RCA jack. 12VDC powered. CCD provides 380 lines of resolution and 0.8 lux sensitivity. Complete with power supply and 3 foot RCA cable. A fantastic and useful device for inspection, diagnostics and observation of small objects. Perfect for SMT inspection.  
**SPECIAL, GM-MAGCAM.....\$199ea.**

**NEW, 470 LINE, DSP COLOR Micro CAM**  
**The HIGHEST PERFORMANCE available.**  
**MICRO SIZED PACKAGE too!** Yes 470 lines with a 60dB S/N ratio to back it up! That's 16X better than a typical 460 standard camera! The GM-4500, CCD camera with its' DSP technology provides high speed white balance with no color rolling. Auto shutter speed of 1/60 to 1/120,000 second. Truly state of the art. Sleek cast aluminum housing protects the 18mm x 26mm pc board inside. Mounting bracket & 18" cable with BNC video and DC pwr. jack for, no sweat hook up. requires only 12VDC @ 65mA. Optional mirror function available. Why fool around with an open P.C. board? This camera has it all. • 1/4" CCD • 1 Lux • AGC • Auto Shutter • 270k pixels • Std. 3.7 mm, 68° FOV lens • Focus: 10mm to infinity • 3-ounce! • Size (mm): 33W x 29H x 30D. **GM-4500-STD, SPECIAL..\$99ea.**

**NEW! 0.005 Lux, COLOR NIGHT VISION CAMERA!**  
**UNBELIEVABLE LOW LIGHT PERFORMANCE.**  
**State of the Art Video, Exclusive ON SCREEN, menu driven setup of all camera parameters!**  
For covert, military & scientific applications that must be color, this is it. Unbelievable 0.005Lux @ f1.2 performance is enhanced through low speed electronic shuttering, digital frame integration and advanced DSP. Auto sensitivity mode starts as it becomes dark. 24 hour surveillance is possible with the optional f1.2 auto iris lens shown below. Seven Gain/Shutter modes are user selectable. Normal, X4, X8, X16, X24, X32, X64. These provide frame rates of 60, 15, 8, 4, 3, 2 and 1 per second. Auto/Man. white balance 3200° to 10000°K, auto/man BLC. S/N >52dB. Mirror on/off. Gain on/off, auto electronic shutter 1/60 to 1/120,000 sec. Alum. housing, dual 1/4x20 mtg. Specs: 1/2" CCD, 768H x 494V, with 380K pixels, 470 Lines, 12VDC  $\pm 1V$  @ 200mA, Std. video out on BNC. Size: 51mm x 51mm x 115mm long. Regulated power adapter included. All functions can be externally controlled. Use standard C-mount lens not included.  
**GMV-3K-OSD.....\$449ea.**  
**High performance auto iris lens, 12mm, f1.2...\$199ea.**

**SONY, ROBOTIC COLOR CAMERA, 450Line, 8X ZOOM, NTSC & S-VIDEO OUT, Serial Control of Pan, Tilt and Zoom, Auto Iris and Auto Focus too!** Five user presets allow one click "go-to" scenes with pan, tilt and zoom for each in memory. (Under software control) Like having your own R2D2. Intended for use in fortune 500 board rooms. The video performance is stunning. Superior to almost anything we have seen. Camera and lens is an integral assembly. Excellent condition. Rugged black ABS enclosure. 8 pin mini-DIN & Std. 5VHS jack. Size: 8"D x 6.5"H. With software and serial cable for remote control. Regular price over \$4K. Limited quantity. How more could you want?  
**PICTEL-4K \$399ea. or 2 for \$699**

**KOLLMORGEN, ServoDisc MOTOR with 2500rpm optical encoder, S6M4H Type.**  
Rugged, ironless, low inertia rotor for high acceleration and zero cogging. Very compact 3.4" diameter x 4.2" high including the encoder. Peak torque 214 oz-in, rated speed 3000 RPM, cont. torque, 21 oz-in. Power output 46W, Max. speed 6000 rpm, Peak acceleration: 251 KRad/s<sup>2</sup>. Rated voltage 17.7V @ 5.2amps, Weight 2.3lbs. A fantastic servomotor. Removed from new equipment.  
**KOLL-S6M4H.....\$99ea.**

**CARL ZEISS, 5-PLANAR LENS,**  
GCA type 37, 1.4/75, M1:5nA=0.30,  
A fantastic lens with a current replacement cost of \$20K. Extremely flat field and extremely high quality. Removed from water-lithography system, excellent condition. **ZEISS-PLANAR.....\$495**

**WEATHER RESISTANT and HEATED Outdoor, Camera Enclosure,**  
Solid, extruded aircraft aluminum. Glass window. Strain reliefs for cables. Size: 3.5" x 3.7" x 1.4", New. Perfect for our new "Night vision cameras"  
**GM-10H.....\$69ea.**  
**Adjustable Heavy Duty Mount.....\$19ea.**

**TEKTRONIX, TDS 744A, 4 CHANNEL, Digitizing Oscilloscope.**  
**500MHz Bandwidth and Sampling to 2 GS/s... WOW!**  
**A super color LCD display provides crisp digital accuracy.**  
Some specs include: Max sample length 50K points, Vertical sens. of 1mV/div., Rise time 700ps, Main time base 500ps/div to 10S/div., Minimum glitch trigger: 1ns. Parallel, GPIB and RS-232 ports. Test pattern storage of up to 10 patterns. Built in floppy disk drive. External video output. Size: 17.5" W x 7.6" H x 17"D, weight 31lbs. Option 5, 13, 1M, 1F, 2F Units just removed from service and in mint condition. No manual or probes.  
**Reg. Price: \$20K SPECIAL TEK-744A .....\$5895**

**BRAND NEW, VIDEO MOTION SENSOR.** The model VM-10 connect to any standard video signal and you've got an electronic "watchman" diligently watching the entire scene. Or any adjustable sized area within the scene. Such as a doorway or even a drawer or cabinet. A state of the art security aid. The unit will close a contact when it senses a change. Auto or manual reset. Internal buzzer with volume control and adjustable on time. VCR record and VCR stop output. Use with time lapse VCR. 110VAC powered. Adjustable sensitivity. Video loop through. **NEW, VM10.....\$179ea.**

**NEW! 6.8" LCD COLOR, TFT, ACTIVE MATRIX DISPLAY, A huge 23sq. inch VIEWABLE AREA, Super Deal. 2.8X the VIEWING AREA of a 4" WOW!** We wish you could see the color saturation and resolution of this superior LCD display. Excellent contrast ratio, high quality, full color images are comparable to a CRT. Perfect, portable, general purpose color monitor for standard NTSC color or B&W video. Fully compatible with all our cameras as well as Camcorders, VCR's, DVD's etc. OEM "component" style unit has no outer cabinet. Designed to be installed in YOUR housing via four mounting tabs as shown. Specs: Resolution, 1152H x 234V, 270K Pixels! Viewing angle, Top 10°, Down 30°, Left 45°, Right 45°. Brightness, 300 nit, Size: W x H x D (mm/in), 157.2 x 122.6 x 8.0, 6.2" x 4.83" x 1.1". Weight, 10oz. Supplied with 30" input cable. Video input via BNC jack, 12VDC input via a standard barrel connector.  
**BRAND NEW, FIRST QUALITY. GMTFT68.....\$169ea.**  
**Regulated 12 VDC/110VAC power supply.....\$8.95ea.**

**ORDERS. 800.810.4070**  
**Tech 603.668.2499**  
**RESOURCES UN-LTD.**  
**Fax 603.644.7825, All CCards, COD,**  
**300 Bedford St. Manchester, NH 03101**  
**WWW.RESUNLTD4U.COM**

**NEW! WEATHERPROOF B&W mini TUBE CAMERA**  
**Industrial strength, solid machined housing.**  
Sleek black anodized, BRASS, housing is O-Ring sealed & WATERPROOF. Adjustable mount included. Specs: 1/3" CCD, 400 Lines resolution, 0.05 Lux sensitivity, AGC, Auto Shutter. Operates on 12VDC @200mA, 4mm, 78° FOV lens. A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR. Ultra small size. 1.25" diam. X 2" long. With 60 ft. cable. Great for outdoor use too.  
**NEW, GM300K-N.....\$99**

**NEW, lower cost, High quality, MINI BOARD CAM,**  
1/3" CCD, 420 Lines Res., 0.3 Lux sens., AGC, Pwr. from 9 to 12VDC @100mA, 266k PIXELS, 3.7mm, 92° FOV lens. A real glass lens. Auto shutter from 1/60 to 1/100,000 sec. Focus from 10mm to infinity. Std. NTSC video out. 1/2 ounce! SENSITIVE to IR. Size: 1.25" sq. x 1" d. Connections via a 3" pigtail with PC board connector. **GM-1000B-STD.....\$45ea.**

**PULNIX, TMCT INDUSTRIAL 1/2", COLOR CCD CAMERA, with Pentax Lens. For No Compromise Performance.**  
Specs: 1/2" CCD, 460 Lines resolution, 768H x 494V Pixels, 2 Lux sens. @f1.4, Auto/Man AGC, Auto/Man Shutter. 1/60 to 1/10,000 remotely controllable via 6 pin connector (not incl.) Auto/Man white balance, Manual gain and hue controls are external. Complimentary color filter. 12VDC @320mA, Pwr supply incl. Pentax, 16mm f1.4 lens. A real glass lens. Included. Std. NTSC video out on BNC. 1/3" C/S-Video output available on 12 pin connector supplied. Superior construction. Compact size only: 1.6" W x 1.25" H x 5.5" long. Perfect for use in process monitoring, medical, surveillance and microscopy. Use, excellent condition. Regular price \$600. Limited quantity.  
**PULNIX, TMC-7.....\$149ea. or 2 for \$249**

**NEW! 4 or 8 CHANNEL, VIDEO AUTO SWITCHERS**  
Connect four or eight std. video signals and they will be sequentially output to the dual rear panel BNC outputs. Front panel user adjustable, variable dwell 1 to 15 sec per channel. Auto/manual switching with channel bypass. Compact only 8.6" W x 3.7" D x 1.75" H, ac powered. Video loop through. **GM-34, 4 Chan.....\$65, GM38, 8 Chan.....\$75**

**NEW, DAY/NIGHT TECHNOLOGY, OPTIMIZED COLOR / IR OPTICS**  
**DSP technology and 10 Automatic LED's.**  
**Weather Tight GM450K-IR Makes it Happen**  
Features include:  
Interactive infrared illuminator with 10 high power, wide angle LEDs @ 880nm. See objects 60 feet away during total darkness. A super quality 5 element, glass lens, specially coated with a 100 layer optical coating. For perfect focus with white light and a crisp image under infrared. Normally impossible due to the different focal point for IR and visible light. Solid state infrared optical switch provides day time IR cut filter for excellent color. At night infrared filter will turn off to allow infrared to pass. Also, night time IR LEDs will gradually turn on with proper amount of illumination. You can also see color images such as lights and signs at night. Fog free cover glass. Specs: 0.5 lux color sensitivity. 60dB S/N ratio typical. 12" I/O cable with BNC video and DC barrel jack. 120 dB smear rejection ratio. Adjustable mount and C power adapter included. **GM450K-IR.....\$199ea.**

**NEW! 0.01 Lux, COLOR NIGHT VISION CAMERA!**  
**FANTASTIC LOW LIGHT PERFORMANCE. Exclusive ON SCREEN, menu driven setup of all camera parameters.**  
**NEW, STATE of the ART, GMV-35KOSD**  
Perfect for covert, military & scientific applications that must be color. Unbelievable 0.01Lux @ f1.2 performance is enhanced through low speed electronic shuttering, digital frame integration & advanced DSP. Auto sensitivity mode starts as it becomes dark. 24 hour surveillance is possible with the optional f1.2 lens shown below. Specs: Shutter speed auto or manual, 1/60 to 1/120,000, 60dB S/N ratio, 154dB Smear rejection!, AGC gain 0 dB to 18 dB. Digital gain 0dB to 12dB. Digital zoom continuous from 1x to 2X in 0.1X steps. Masking mode allows hiding 4 programmable zones for privacy protection. Camera on screen name. Choose your own name for the camera and display it on monitor for easy identification. 1 White balance modes. Auto tracking, one push or selection from 3200K, 4800K, 5600K, 7800K, and "double white balance" independent white balance circuit for both bright and dark zone, maintains correct white balance even with combined indoor and outdoor lighting. Programmable 48 zone back light compensation mode for difficult lighting situation. Negative mode for negative film reading. Mirror image and up/down selection for rear view and camera mounted upside down. Seven Gain/Shutter modes are user selectable. Normal, X2, X4, X8, X16, X24, X32, X64. These provide frame rates of 60, 30, 15, 8, 4, 3, 2, and 1 per second. Alum. housing, dual 1/4x20 mtg. Specs: 1/3" CCD, 811H x 508V, with 412K pixels, 470 Lines, 12VDC  $\pm 1V$  @ 250mA, Std. video out on BNC. Std 5-Video out on 4Pin connector. Size: 2" H x 2" W x 4.5" L. Regulated power adapter included. C-mount lens not included. **GMV-35KOSD.....\$399ea.**  
**High performance lens, 4mm, f1.3...\$49ea.**

**SPECIAL PRICE, 350MHz, TEKTRONIX 2467, MICRO CHANNEL PLATE CRT! with 4 Channels, 500ps per div. in normal room light.**  
Displays intermittent variations as they happen. Captures the slowest one shot events with 4ns per division a 100 fold increase in the visual writing rate over conventional CRT. Features: 1 ns rise time, 500ps/Div time base, 2mV/Div vertical sensitivity at 350MHz, 20ps time interval resolution, 1Mohm / 50-ohm input, 500MHz trigger bandwidth, four channels. On-screen waveform cursors provide vertical & horizontal scale factors, trigger level, voltage, time, freq., phase, ratio values and mode indication. With 2 probes, pouch and manual. EX. cond. 90 day warranty.  
**New..\$12K Now SALE, TEK 2467.....\$1995.**

Published Monthly By  
**T & L Publications, Inc.**  
 430 Princland Court  
 Corona, CA 92879-1300  
 (909) 371-8497  
 FAX (909) 371-3052

E-Mail — editor@nutsvolts.com  
 URL — http://www.nutsvolts.com

Subscription  
 Order ONLY Line  
 1-800-783-4624

PUBLISHER  
 Jack Lemieux N6ZTD

EDITOR  
 Larry Lemieux KD6UWV

MANAGING EDITOR  
 Robin Lemieux KD6UWS

#### CONTRIBUTORS

Robert Nansel  
 Jon Williams  
 Jeff Eckert  
 TJ Byers  
 Stanley York  
 Gordon West  
 Bob Van Kannon  
 Michael Simpson  
 Ray Marston  
 Daniel Ramirez

ON-THE-ROAD EXHIBIT  
 COORDINATOR  
 Audrey Lemieux N6VXW

STAFF  
 Natalie Sigafus  
 Mary Gamar

Copyright 2002 by  
**T & L Publications, Inc.**  
 All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princland Court, Corona, CA 92879.

## Reader Feedback

Dear Nuts & Volts:

I am 75 years old and for almost 50 years my interest and my passion has been regenerative radios. I hope we never lose this link to our electronic past.

I have built hundreds of these little "signal grabbers" and most are my own designs. I would like the opportunity to share some of these circuit designs to those with similar interests. I am not interested in profit and would just like to share my ideas with others. Almost all of my circuits are in the aircraft frequencies of the general aviation band, as well as the military band. These are the super regen types (too lazy to wind tickler coils even if they would work at these frequencies).

Do you think electronic hobbyists are still interested in building simple electronic projects that can be completed in a few hours, have the joy of seeing them work or be dismayed at having to start over? Even when the projects are unsuccessful, they are a learning experience and patience and perseverance will help you find and correct the error.

**W.T. (Bill) Stratton**  
 1211 New Hope Rd.  
 Columbus, MS 39702

Dear Nuts & Volts:

I've read through the article from TJ Byers on his Versatile AC Power Supply, and have a couple of questions:

1) He briefly mentions some surge absorbers used (PC1, -2 and -3) and they are included in the parts list, but without part num-

bers or a source. How should these be spec'd and where can we procure them?

2) In the schematic, F2 is shown as fusing the neutral side of the AC mains. I thought that this was not good practice, since, with both F1 and F2 fuses being the same value and effectively in series, it becomes a 'crap shoot' as to which one will go first in the event of a fault. This can still leave a 'hot' chassis for an unsuspecting experimenter in spite of a blown fuse, if the neutral fuse goes first. It would be better, I think, to leave out F2 and just have F1. If I'm all wet here, please set me straight. Thanks. Thought I'd mention these items.

**Dan P via internet**

Dear Nuts & Volts:

In the last issue of your magazine, TJ Byers published a schematic for a battery maintenance charger at the request of another subscriber.

I built same but cannot not get the first stage (multivibrator) to oscillate. Manually triggered, the second stage works fine. Is the schematic correct ???, or am I missing something?

**Anonymous**

The first stage (multivibrator) is voltage triggered. Measure the voltage on pin 2 of the first stage while monitoring the output. When the voltage on pin 2 goes below 2 volts, the multivibrator oscillates at about 100 Hz. When the input voltage exceeds 2 volts, the oscillator stops. The output from this stage is used to trigger the second (timer) stage. If you are trying to monitor a voltage other than 13 volts, you will need to adjust the value of the 5.6k resistor up or down, accordingly. — TJ

## SolderingDesoldering.Com

Your SMD Rework Specialist  
**800-394-1984**

Mr. NiCd		WINTER SPECIALS!		THE BEST BATTERIES IN AMERICA!	
Packs & Charger for YAESU FT-50R / 40R / 10R:					
FNB-40xh	slim-NiMH	7.2v	650mAh	\$41.95	
FNB-47xh	(NiMH)	7.2v	1800mAh	\$49.95	
FNB-41xh	(5w NiMH)	9.6v	1000mAh	\$49.95	
For YAESU FT-51R / 41R / 11R:					
FNB-38	pack (5w)	9.6v	700mAh	\$39.95	
For YAESU FT-530 / 416 / 816 / 76 / 26:					
FNB-26	pack (NiMH)	7.2v	1500mAh	\$32.95	
FNB-27S	(5w NiMH)	12.0v	1000mAh	\$45.95	
For YAESU FT-411 / 470 / 73 / 33 / 23:					
FNB-11	pack (5w)	12.0v	600mAh	\$24.95	
FBA-10	6-Cell AA case			\$14.95	
Packs for ALINCO DJ-580 / 582 / 180 radios:					
EBP-20ns	pack	7.2v	1500mAh	\$29.95	
EBP-22nh	pk (5w)	12.0v	1000mAh	\$36.95	
EDH-11	6-Cell AA case			\$14.95	
For ICOM IC-21A / T22-42A / W31-32A / T7A:					
FNB-180xh	pk (NiMH)	7.2v	1000mAh	\$39.95	
BP-173	pack (5w)	9.6v	700mAh	\$49.95	
For ICOM IC-W21A / 2GXAT / V21AT (Black or Gray):					
BP-132S	(5w NiMH)	12.0v	1500mAh	\$49.95	
For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:					
BP-83	pack	7.2v	600mAh	\$23.95	
For ICOM 02AT etc & Radio Shack HTX-202 / 404:					
BP-8h	pack	8.4v	1400mAh	\$32.95	
BP-202s	pack (HTX-202)	7.2v	1400mAh	\$29.95	
For KENWOOD TH-79A / 42A / 22A:					
PB-32xh	pack (NiMH)	6.0v	1000mAh	\$29.95	
PB-34xh	pack (5w NiMH)	9.6v	1000mAh	\$39.95	
For KENWOOD TH-78 / 48 / 28 / 27:					
PB-13	(original size)	7.2v	700mAh	\$26.95	
For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:					
PB-6x	(NiMH w/chg plug)	7.2v	1200mAh	\$34.95	
Mail, phone, & Fax orders welcome! Pay with Mastercard / VISA / DISCOVER / American Express					
Call 608-831-3443 / Fax 608-831-1082					
Mr. NiCd - E. H. Yost & Company					
2211-D Parview Road, Middleton, WI 53562					
CALL OR WRITE FOR OUR FREE CATALOG!					
Cellular / Laptop / Videocam / Commercial & Aviation packs too!					
E-mail: ehyst@midplains.net					

# DMOS & JFETS & MOSFETS & TRANSISTORS

@  
**LINEAR SYSTEMS**

Second Source Replacements  
 for Interfet, Motorola,  
National, Siliconix

- ◆ Custom Screening
- ◆ Die, SMT, Thru-Hole

**LINEAR SYSTEMS**

Full Service U.S. Manufacturer  
 of Specialty Linear Products

4042 Clipper Court  
 Fremont, CA 94538  
 (TEL) 510-490-9160  
 (FAX) 510-353-0261  
 JFETS@LINEARSYSTEMS.COM  
 WWW.LINEARSYSTEMS.COM

Circle #77 on the Reader Service Card.

## NEW INTEGRATED STEREO TUBE AMP KIT \$139.95\*



ALL TUBE DESIGN RIVALS SOUND  
 OF \$1000 HIGH END AMPLIFIERS

Power Output: 8 Watts per channel  
 Frequency Response: 20 TO 20,000 Hz  
 Distortion: Less than 1% at 1 Watt  
 Input Impedance: 100K Ohms  
 Output Impedance: 8 Ohms  
 Minimum Input: 0.5 V for full output

Uses type 11MS8 tubes included in kit  
 with circuit board, base board and all  
 parts, including transformers, power  
 cord, etc. and easy to follow assembly  
 instructions.

\*Assembled and tested \$169.95.

Add \$10 for shipping and handling.  
 Order K-012M from:

**S-5 ELECTRONICS**  
 1625 TWIN ACRES  
 CHANDLER, AZ 85249

Phone: 480-895-2521, Fax: 480-895-4164

Circle #76 on the Reader Service Card.



# WE BUY AND SELL

Inquiries 307-635-2269 • Fax 307-635-2291

Orders 800-538-1493

2701 Westland Court, Unit B, Cheyenne, Wyoming 82001

## OSCILLOSCOPES & ACCESSORIES

### OSCILLOSCOPES

TEKTRONIX 2430-opt.05, 11100 MS/s Dual Channel Oscilloscope, TV trig., GPIB ..... \$1000.00

### PROBES

TEKTRONIX 1101 Accessory Power Supply, for FET probes ..... \$175.00  
TEKTRONIX A6902B Voltage Isolator, DC-20 MHz, 20 mV-500 V/division ..... \$500.00  
TEKTRONIX P6201 900 MHz 1X/ 10X/ 100X FET Probe ..... \$400.00  
TEKTRONIX P6202 500 MHz 10X FET Probe ..... \$150.00

## WAVEFORM GENERATORS

### FUNCTION GENERATORS

HP 3310A 5 MHz Function Generator ..... \$250.00  
HP 3312A 13 MHz Function Generator ..... \$500.00  
HP 3325A-001 21 MHz Synthesizer/Function Generator, OCXO ref. .... \$1100.00  
HP 3325A-002 21 MHz Synthesizer/Function Generator, high voltage ..... \$1200.00  
HP 3325B-002 Synthesizer/Function Generator, 1 uHz-21 MHz, HP1B ..... \$4000.00  
TEKTRONIX AWG5102 Arb. Waveform Gen., 20 MS/s, 12 bits, 50 ppm synthesis <1MHz ..... \$650.00  
TEKTRONIX AWG5102-opt.2 Arbitrary Waveform Generator, dual channel option ..... \$800.00  
TEKTRONIX DD501 Digital Delay & Burst Gen., for function & pulse gen's ..... \$200.00  
TEKTRONIX FG5010 Programmable 20 MHz Function Generator, TM5000 series ..... \$600.00  
TEKTRONIX FG502 11 MHz Function Generator, TM500 series ..... \$275.00  
TEKTRONIX FG503 3 MHz Function Generator, TM500 series ..... \$250.00  
TEKTRONIX RG501 Ramp Generator, TM500 series ..... \$175.00  
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB ..... \$650.00

### PULSE GENERATORS

BERKELEY NUC. 7085B Digital Delay Gen., 0-100 mS, 1 nS res., 5 Hz-5 MHz ..... \$400.00  
HP 214B 10 MHz Pulse Generator, up to 50V/ 50 Ohms ..... \$1200.00  
HP 214B-001 10 MHz Pulse Generator, pulse counting option ..... \$1400.00  
HP 8007B 100 MHz Pulse Generator ..... \$450.00  
HP 8012B 50 MHz Pulse Generator, variable transition time ..... \$600.00  
HP 8013A 50 MHz Dual Output Pulse Generator ..... \$500.00  
HP 8013B 50 MHz Dual Output Pulse Generator ..... \$600.00  
HP 8112A 50 MHz Pulse Generator, HP1B ..... \$3000.00  
HP 8116A-001 50 MHz Pulse/Function Generator, burst & log sweep option ..... \$3500.00  
TEKTRONIX PG502 250 MHz Pulse Generator, TM500 series ..... \$500.00  
TEKTRONIX PG508 50 MHz Pulse Generator, TM500 series ..... \$350.00

## VOLTAGE & CURRENT

### VOLTMETERS

FLUKE 845AR High Impedance Voltmeter / Null Detector ..... \$350.00  
HP 3456A 6-1/2 digit Voltmeter, HP1B ..... \$450.00  
HP 3457A 7-1/2 digit Voltmeter, HP1B ..... \$1000.00  
HP 3478A 5-1/2 digit Multimeter, HP1B ..... \$450.00  
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB ..... \$675.00  
TEKTRONIX DM5010 4-1/2 digit Multimeter, TM5000 series ..... \$300.00  
TEKTRONIX DM501A 4-1/2 digit Multimeter, TM500 series ..... \$225.00

### CALIBRATION

FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA ..... \$450.00  
FLUKE 5220A Transconductance Amplifier, DC-5 kHz, 0-20 A ..... \$1250.00

### VOLTAGE SOURCES

HP 6114A Precision Power Supply, 0-20 V 2 A/ 0-40 V 1 A ..... \$650.00  
HP 6115A Precision Power Supply, 0-50 V 0.8 A/ 0-100 V 0.4 A ..... \$650.00  
TEKTRONIX PS5004 Precision Power Supply, 0-20 V 0-300 mA, 1 mV res. .... \$950.00

### CURRENT METERS & SOURCES

HP 4140B DCV Source / Picoammeter, HP1B ..... \$3500.00  
HP 6177C DC Current Source, to 50 V, 500 mA ..... \$500.00  
HP 6181C DC Current Source, to 100 V, 250 mA ..... \$500.00  
KEITHLEY 225 Current Source, 0.1 uA-100 mA, 10-100 V compliance ..... \$450.00  
TEKTRONIX P6022 AC Current Probe, 935 Hz-120 MHz, 6 A peak ..... \$250.00  
VALHALLA 2500 AC/DC Current Calibrator, 2 uA-2 A, DC-10 kHz ..... \$500.00

## IMPEDANCE & COMPONENT TEST

### L.C.R.

BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH ..... \$500.00  
BOONTON 72BD 1 MHz Capacitance Meter, 2-2000 pF f.s. 3 digits ..... \$800.00  
BOONTON 72C 1 MHz Capacitance Meter, 1-3000 pF f.s. analog ..... \$800.00

GENERAL RADIO 1658 RLC DigiBridge, 120 Hz / 1 kHz ..... \$1000.00  
HP 4262A 3-1/2 digit LCR Meter, 120 Hz/ 1 kHz/ 10 kHz ..... \$950.00  
HP 4274A 5-1/2 digit LCR Meter, 100 Hz-100 kHz, HP1B ..... \$3250.00

### STANDARDS

E.S.I. SR-1 Standard Resistor, various values ..... \$125.00  
E.S.I. SR1010 Resistance Transfer Standards, 1 Ohm-100 K/step ..... \$500.00  
GENERAL RADIO 1406-series Standard Air Capacitors, GR900 connector, 0.1% acc ..... \$275.00  
GENERAL RADIO 1409-series Standard Capacitors, 0.001-1.0 uF values available ..... \$150.00  
GENERAL RADIO 1433-J 4-Decade Resistor, 0-11.11 Kilohms, 1 Ohm steps ..... \$150.00  
GENERAL RADIO 1433-K 4-Decade Resistor, 0-1.11 Kilohms, 0.1 Ohm steps ..... \$150.00  
GENERAL RADIO 1433-P 5-Decade Resistor, 0-1.1111 Megohms, 10 Ohm steps ..... \$200.00  
HP 4440B Decade Capacitor, 40 pF-1.2 uF ..... \$750.00

### HI & LO RESISTANCE

HP 4329A High Resistance Meter, 500 Kilohms-2x 10e16 Ohms ..... \$875.00  
T.D.R.  
TEKTRONIX 1503B-03, 04 TDR, 0-50,000 feet; chart rec. & battery options ..... \$2500.00

## POWER SUPPLIES

### SINGLE OUTPUT

HP 6002A-001 0-50 V / 0-10 A / 200 Watts max. Supply, HP1B ..... \$650.00  
HP 6011A 0-20 V / 0-120 A / 1000 Watts max. CV/CC Supply ..... \$1800.00  
HP 6028A 0-60 V / 0-10 A / 200 Watts max. Autorangeing Supply ..... \$1000.00  
HP 6033A 0-20 V / 0-30 A / 200 Watts max. Supply, HP1B ..... \$1200.00  
HP 6038A 0-60 V / 0-10 A / 200 Watts max. Supply, HP1B ..... \$1200.00  
HP 6203B 0-7.5 V 0-3 A CV/CC Power Supply ..... \$175.00  
HP 6205C Dual Power Supply, 0-40 V 300 mA/ 0-20 V 600 mA ..... \$300.00  
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply ..... \$200.00  
HP 6263B 0-20 V 0-10 A CV/CC Power Supply ..... \$375.00  
HP 6266B 0-40 V 0-5 A CV/CC Power Supply ..... \$375.00  
HP 6267B 0-40 V 0-10 A CV/CC Power Supply ..... \$550.00  
HP 6271B 0-60 V 0-3 A CV/CC Power Supply ..... \$375.00  
HP 6274B 0-60 V 0-15 A CV/CC Power Supply ..... \$650.00  
HP 6384A 4.0-5.5 V at 8 A CV/CL Power Supply ..... \$125.00  
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply ..... \$375.00  
HP 6525A 0-4000 V 0-50 mA CV/CC Power Supply ..... \$650.00  
HP 6552A 0-20 V 0-25 A CV/CC Power Supply ..... \$1000.00  
HP 6643A 0-35 V 0-6 A CV/CC Power Supply, HP1B ..... \$1200.00  
HP 6651A 0-8 V 0-50 A CV/CC Power Supply, HP1B ..... \$1500.00  
HP 6652A 0-20 V 0-25 A CV/CC Power Supply, HP1B ..... \$1875.00  
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply ..... \$300.00  
LAMBDA LK-352-FM 0-60 V 0-15 A CV/CC Power Supply ..... \$600.00  
SORENSEN SRL 20-12 0-20 V 0-12 A CV/CC Power Supply ..... \$350.00  
SORENSEN SRL 60-8 0-60 V 0-8 A CV/CC Power Supply ..... \$450.00

### MULTIPLE OUTPUT

HP 6228B Dual Power Supply, 0-50 V 0-1 A, CV/CC ..... \$375.00  
HP 6236B Triple Output Supply, +/-20 V 0.5 A & 0-6 V 2.5 A ..... \$375.00  
HP 6237B Triple Output Supply, +/-20 V 0.5 A & 0-18 V 1 A ..... \$375.00  
HP 6253A Dual Power Supply, 0-20 V 0-3 A, CV/CC ..... \$375.00  
HP 6254A Dual Power Supply, 0-40 V 0-1.5 A, CV/CC ..... \$375.00  
TEKTRONIX PS503A Dual Power Supply, TM500 series ..... \$200.00

### MISCELLANEOUS

ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max. .... \$300.00  
ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max. .... \$350.00  
HP 6827A Bipolar Power Supply / Amplifier, +/-100 V +/-500 mA ..... \$900.00  
KEPCO BOP 50-2M Bipolar Amplifier/Power Supply, to 50 V, 2 A ..... \$400.00  
TRANSISTOR DEV DAL-50-15 10 Programmable Load, 0-50 V, 0-15 A, 100 Watts max. .... \$200.00

## TIME & FREQUENCY

### UNIVERSAL COUNTERS

HP 5314A 100 MHz/ 100 nS Universal Counter ..... \$175.00  
HP 5315A 100 MHz/ 100 nS Universal Counter ..... \$350.00  
HP 5315A-003 100 MHz/ 100 nS Counter, 1 GHz C-channel ..... \$450.00  
HP 5315B 100 MHz/ 100 nS Universal Counter ..... \$375.00  
HP 5316A 100 MHz/ 100 nS Universal Counter, HP1B ..... \$450.00  
PHILIPS PM6672/ 411 120 MHz/ 100 nS Universal Counter, 1 GHz C-channel ..... \$300.00

TEKTRONIX DC5004 100 MHz/ 100 nS Counter/ Timer, TM5000 series ..... \$200.00

TEKTRONIX DC5009 135 MHz/ 10 nS Counter/ Timer, TM5000 series ..... \$350.00

TEKTRONIX DC503A 125 MHz/ 100 nS Universal Counter, TM500 series ..... \$250.00

TEKTRONIX DC509 135 MHz/ 10 nS Universal Counter, TM500 series ..... \$275.00

### FREQUENCY COUNTERS

EIP 548A-06 26.5 GHz Frequency Counter & mixers for 26-60 GHz ..... \$3950.00  
EIP 578-02, 05 26.5 GHz Source Locking Counter, ..... \$3950.00

GPIB & power meter ..... \$2750.00  
HP 5342A 18 GHz Frequency Counter ..... \$900.00  
HP 5343A-001 26.5 GHz Frequency Counter, OCXO reference ..... \$2500.00  
HP 5345A/55A/56B 26.5 GHz CW/ Pulse Frequency Counter ..... \$3500.00  
HP 5352B-010 40 GHz Frequency Counter, OCXO reference option ..... \$7500.00  
HP 5384A 225 MHz Frequency Counter, HP1B ..... \$450.00  
XL MICROWAVE 3401 40 GHz Source Locking Frequency Counter, GPIB ..... \$5500.00

### STANDARDS

HP 105B Quartz Oscillator, 0.1/ 1.0/ 5.0 MHz, battery pwr. .... \$1100.00

## AUDIO & BASEBAND

### SPECTRUM ANALYSIS

HP 3586C Selective Level Meter, 50 Hz-32.5 MHz, 50k & 75 Ohms ..... \$1000.00

### DISTORTION ANALYZERS

HP 8903A Audio Analyzer, 20 Hz-100 kHz, HP1B ..... \$1200.00  
HP 8903B-001, 010, 053 Audio Analyzer, 20 Hz-100 kHz, HP1B ..... \$1850.00  
HP 8903E Audio Analyzer, 20 Hz-100 kHz, HP1B ..... \$1650.00

### RMS VOLTMETERS

FLUKE 8922A True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz ..... \$450.00

### OSCILLATORS

TEKTRONIX SG502 Sine/ Square Osc., 5 Hz-500 kHz, 70 dB step atten., TM500 ..... \$200.00  
TEKTRONIX SG505-opt.2 Oscillator, 10 Hz-100 kHz; IM test & 50/150/600 Ohms ..... \$800.00  
WAVETEK 98 1 MHz Synthesized Power Oscillator, GPIB ..... \$750.00

### MISCELLANEOUS

HP 3575A Phase-Gain Meter, 1 Hz-13 MHz, single display ..... \$600.00  
HP 3575A-001 Phase-Gain Meter, 1 Hz-13 MHz, dual display ..... \$750.00  
HP 467A Power Amplifier ..... \$375.00  
KROHN-HITE 3200 High Pass / Low Pass Filter, 20 Hz-2 MHz ..... \$275.00  
KROHN-HITE 3202 Dual HP/LP/BP/BR Filter, 20 Hz-2 MHz ..... \$450.00  
ROCKLAND 852 Dual Highpass/Lowpass Filter, 0.1 Hz-11 kHz ..... \$650.00  
TEK AM502 1 MHz Differential Amplifier, TM500 series ..... \$450.00

## RF & MICROWAVE

### SPECTRUM ANALYZERS

HP 11517A/19A/20A Mixer Set, 18-40 GHz, for HP 8555A / 8569A ..... \$475.00  
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz ..... \$1000.00  
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz ..... \$1000.00  
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz ..... \$1400.00  
HP 11970U WR19 Harmonic Mixer, 40-60 GHz ..... \$1600.00  
HP 11971A WR28 Harmonic Mixer, 26.5-40 GHz, for 8569B ..... \$800.00  
HP 11971K WR42 Harmonic Mixer, 18.0-26.5 GHz, for 8569B ..... \$800.00  
HP 8562A Spectrum Analyzer, 1 kHz-22 GHz, 100 Hz min. res. BW ..... \$16000.00  
HP 85640A Tracking Generator, 300 kHz-2.9 GHz, for HP 8560 series ..... \$4000.00  
HP 8565A-100 Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. BW ..... \$3000.00  
HP 8569B Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. BW ..... \$4500.00  
TEKTRONIX WM782V WR15 Harmonic Mixer, 50-75 GHz ..... \$1500.00

### NETWORK ANALYZERS

HP 11650A Network Analyzer Accessory Kit ..... \$500.00  
HP 11650A Network Analyzer Accessory Kit, APC7 ..... \$600.00  
HP 11665B Modulator, 0.15-18.0 GHz, for HP 8755/6/7 ..... \$250.00  
HP 11665B Modulator, 0.15-18 GHz, for HP 8755/6/7 ..... \$250.00  
HP 3577B Network Analyzer, 5 Hz-200 MHz ..... \$9500.00  
HP 4191A RF Impedance Analyzer, 1-1000 MHz, 1 milliohm-100 Kilohms ..... \$3750.00  
HP 4193A Vector Impedance Meter, 400 kHz-110 MHz, 10 Ohms-100 K ..... \$4500.00  
HP 8502B 75 Ohm Transmission/ Reflection Test Unit, 0.5-1300 MHz ..... \$675.00  
HP 85044B 75 Ohm Transmission/ Reflection Test Unit, 300 kHz-2 GHz ..... \$1250.00  
HP 85054A Type N Calibration Kit, for HP 8510 series ..... \$1800.00  
HP 8717B-001 Transistor Bias Supply ..... \$350.00  
HP 8751A-001, 002 Network Analyzer, 5 Hz-500 MHz ..... \$12500.00  
HP 8756A Scalar Network Analyzer, HP1B ..... \$1375.00

### SIGNAL GENERATORS

FLUKE 6060B/AK Signal Generator, 0.1-1050 MHz, 10 Hz res. .... \$1250.00  
FLUKE 6060B-130,830 Signal Generator, 0.1-1050 MHz, 10 Hz res., GPIB ..... \$1600.00  
GIGATRONICS 1018 Signal/Sweep Gen., 0.05-18 GHz, 1 kHz res., +8 dBm ..... \$5000.00  
GIGATRONICS 600/ 6-12 Synthesized Source, 6-12 GHz, 1 MHz res., GPIB ..... \$1500.00



# 90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



GIGATRONICS 6000/ 8-16 Synthesized Source, 8-16 GHz, 1MHz res., GPIB	\$2250.00
GIGATRONICS 6061A-830 Signal Generator, 0.1-1050 MHz, 10 Hz res., AM, FM, GPIB	\$1900.00
GIGATRONICS 900/2-8 Signal/ Sweep Generator, 2-8 GHz, 1 MHz res., GPIB	\$1750.00
HP 11707A Test Plug-in, for HP 8660 series	\$400.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio	\$450.00
HP 8642M Signal Generator, 0.1-2100 MHz, 1 Hz res., GPIB	\$3750.00
HP 8656B-001 Signal Generator, 0.1-990 MHz, 10 Hz res., GPIB, OXCO	\$2750.00
HP 8657A Signal Generator, 0.1-1040 MHz, 10 Hz res., AM, FM, GPIB	\$3000.00
HP 8660C/603A/633B Signal Generator, 1-2600 MHz, 1 or 2 Hz res., AM, FM	\$3250.00
HP 8660D/8660A-002 Signal Generator, 1-2600 MHz, 1 or 2 Hz res., phase modulation	\$6000.00
HP 8672A Signal Generator, 2-18 GHz, 1-3 kHz res., AM, FM, +3 dBm	\$4500.00
HP 8672A-008 Signal Generator, 2-18 GHz, 1-3 kHz res., AM, FM, +8 dBm	\$5000.00
HP 8673H-212 Signal Generator, 2.0-12.4 GHz, 1 kHz res., AM, FM, +8 dBm	\$8500.00
HP 8673M Signal Generator, 2-18 GHz, 1 kHz res., AM, FM, +8 dBm	\$9500.00
HP 8683B Signal Generator, 2.3-6.5 GHz, cavity tuned, AM/ WBFM/ Pulse	\$2250.00
HP 8683D Signal Generator, 2.3-13.0 GHz, cavity tuned, AM/ WBFM/ Pulse	\$3750.00
HP 8684B Signal Generator, 5.4-12.5 GHz, cavity tuned, AM/ WBFM/ Pulse	\$2250.00
HP 8684D Signal Generator, 5.4-18.0 GHz, cavity tuned, AM/ WBFM/ Pulse	\$3750.00
MARCONI 2019 Signal Generator, 80 kHz-1040 MHz, 10 or 20 Hz res.	\$850.00
WAVETEK 952 Signal Generator, 1-4 GHz, +10 dBm, AM, FM	\$750.00
WAVETEK 955 Signal Generator, 7.5-12.4 GHz, +7 dBm, AM, FM	\$750.00
WAVETEK 957 Signal Generator, 12-18 GHz, +7 dBm, AM, FM	\$750.00

## SWEEP GENERATORS

HP 8350B/ 83522A Sweep Oscillator, 10-2400 MHz, +13 dBm levelled	\$3750.00
HP 8350B/ 83525A Sweep Oscillator, 10 MHz-8.4 GHz, +13 dBm levelled	\$5000.00
HP 8350B/ 83540A-002 Sweep Oscillator, 2.0-8.4 GHz, 70 dB step atten.	\$3250.00
HP 8350B/ 83545A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step atten.	\$3750.00
HP 8350B/ 83570A Sweep Oscillator, 18.0-26.5 GHz, +10 dBm levelled	\$7000.00
HP 8350B/ 83592A Sweep Generator, 10 MHz-20 GHz, +10 dBm levelled	\$9000.00
HP 8350B/83570A-H22 Sweep Oscillator, 17-24 GHz, +10 dBm levelled	\$5000.00
HP 8620C Sweep Oscillator Frame	\$500.00
HP 86222B-002 RF Plug-in, 10-2400 MHz, +13 dBm, 70 dB step atten.	\$1250.00
HP 86222B-E69/8620C Sweep Osc. & frame, 0.01-2 GHz & 2-4 GHz bands	\$1200.00
HP 86240B RF Plug-in, 2.0-8.4 GHz, +13 dBm levelled	\$450.00
HP 86241A RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled	\$300.00
HP 86245A RF Plug-in, 5.9-12.4 GHz, +16 dBm levelled	\$350.00
HP 86251A RF Plug-in, 7.5-18.6 GHz, +10 dBm levelled	\$500.00
HP 86260A RF Plug-in, 12-18 GHz, +10 dBm levelled	\$400.00
HP 86260A-H04 RF Plug-in, 10-15 GHz, +10 dBm levelled	\$400.00
HP 86290B RF Plug-in, 2.0-18.6 GHz, +10 dBm levelled	\$1500.00
HP 86290C RF Plug-in, 2.0-18.6 GHz, +13 dBm levelled	\$1750.00
WAVETEK 2001 Sweep Generator, 1-1400 MHz, +10 dBm, 70 dB atten.	\$750.00
WAVETEK 2002B Sweep Generator, 1-2500 MHz, +13 dBm, GPIB	\$1750.00
WILTRON 6647M Sweep Generator, 10 MHz-20 GHz, +10 dBm, GPIB	\$4500.00
WILTRON 6717B-20 Synthesizer/ Sweeper, 10 MHz-8.4 GHz, +13 dBm, GPIB	\$6000.00

## POWER METERS

BOONTON 42B/ 41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$400.00
HP 435B/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz	\$900.00
HP 436A-022/ 8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz, GPIB	\$1200.00
HP 436A-022/ 8482A Power Meter, -30 to +20 dBm, 100 kHz-4.2 GHz, GPIB	\$1200.00
HP 436A-022/ 8484A Power Meter, -70 to -20 dBm, 10 MHz-18 GHz, GPIB	\$1200.00
HP 436A-022/ 8485A Power Meter, -30 to +20 dBm, 50 MHz-26.5 GHz, GPIB	\$1500.00
HP 436A-022/ 8485D Power Meter, -70 to -20 dBm, 50 MHz-26.5 GHz, GPIB	\$1700.00
HP 438A Dual Channel Power Meter	\$3000.00
HP 8477A Power Meter Calibrator, for HP 432 series	\$400.00
HP 8487D High Sensitivity Sensor, -70 to -20 dBm, 50 MHz-50 GHz, 2.4mm	\$1850.00
HP 8900D/84811A Peak Power Meter, 0.1-18 GHz, 0-20 dBm peak	\$2500.00

HP Q8486A Power Sensor, 33-50 GHz, -30 to +20 dBm, for 435/67/7/8	\$1500.00
HP R8486A Power Sensor, 26.5-40 GHz, -30 to +20 dBm, for 435/67/7/8	\$1500.00

## RF MILLIVOLTMETERS

BOONTON 92C RF Millivoltmeter, 3 mV-3 V f.s., 10 kHz-1.2 GHz	\$500.00
RACAL-DANA 9303 RF Millivoltmeter, -70 to +20 dBm, 10 kHz-2 GHz, GPIB	\$750.00

## AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RESEARCH 4W1000 Amplifier, 40 dB gain, 4 Watts, 1-1000 MHz	\$950.00
BOONTON 82AD Modulation Meter, AM/ FM, 10-1200 MHz	\$500.00
C.PI. ZC6961K1 TWT Amplifier, 35 dB gain, 4-8 GHz, 20 Watts	\$3500.00
ENI 2100L Amplifier, 50 dB gain, 10 kHz-12 MHz, 100 Watts	\$3500.00
ENI 525LA Amplifier, 50 dB gain, 1-500 MHz, 25 Watts	\$3250.00
HP 11713A Switch / Attenuator Driver, GPIB	\$800.00
HP 11729B-003 Carrier Noise Test Set, 5 MHz-3.2 GHz	\$1900.00
HP 3730B/3738B Downconverter, 5.9-8.9 GHz & 8.7-11.7 GHz	\$1200.00
HP 415E SWR Meter	\$200.00
HP 8347A RF Amplifier, 25 dB gain, 100 kHz-3 GHz, +20 dBm, GPIB	\$2750.00
HP 8403A-002 Pulse Modulator, 0.8-2.4 GHz, 80 dB dynamic range	\$450.00
HP 8406A Comb Generator, 1/ 10/ 100 MHz increments, to 50 GHz	\$500.00
HP 8447A-001 Dual Amplifier, 20 dB, 0.1-400 MHz, +6 dBm Po, NF <7 dB	\$650.00
HP 8447E Amplifier, 22 dB, 0.1-1300 MHz, +13 dBm output	\$650.00
HP 8447F-H64 Dual Amp., 0.01-50 MHz 28 dB & 0.1-1300 MHz 25 dB	\$900.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz, GPIB \$1350.00	
HP 8901B-001 Modulation Analyzer, 150 kHz-1300 MHz, GPIB \$1900.00	
HUGHES 8010H13F000 TWT Amplifier, >30 dB gain, 3-8 GHz, 10 Watts	\$2500.00
RACAL 9009 Modulation Meter, 30-1500 MHz, AM, 1.5-10 kHz pk FM	\$350.00
RF POWER LABS ML50 Amplifier, 2-30 MHz, 47 dB gain, 50 Watts, metered, 28 V	\$200.00
ROHDE&SCHWARZ ESH2 Test Receiver, 9 kHz-30 MHz	\$3250.00

## COAXIAL & WAVEGUIDE

AEROWAVE 28-3000/10 WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$300.00
AMERICAN NUC. AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) "NEW"	\$95.00
AVANTEC AMT-400X2 WR28 Active Doubler, +10 dBm in & out	\$450.00
BIRD 8201 500 Watt Oil Dielectric Load, DC-2.5 GHz	\$350.00
FXR/MICROLAB SL-03N Stub Stretchers, 0.3-6.0 GHz, 100 Watts max., N(m/f)	\$75.00
GENERAL RADIO 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$400.00
HP 11590A-001 Bias Network, 1.0-18.0 GHz, APC7	\$450.00
HP 11691D Directional Coupler, 22 dB, 2-18 GHz, N connectors	\$450.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$800.00
HP 33327L-006 Prog. Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm	\$1000.00
HP 778D-011 Dual Dir. Coupler, 20 dB, 0.1-2.0 GHz, APC7	\$450.00
HP 87300C-020 Directional Coupler, 20 dB, 1.0-26.5 GHz, 3.5mm	\$475.00
HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$450.00
HP K752A WR42 Directional Coupler, 3 dB, 18.0-26.5 GHz	\$450.00
HP K752C WR42 Directional Coupler, 10 dB, 18.0-26.5 GHz	\$450.00
HP K752D WR42 Directional Coupler, 20 dB, 18.0-26.5 GHz	\$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$250.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$650.00
HP R422A WR28 Crystal Detector, 26.5-40 GHz	\$400.00
HP R752A WR28 Directional Coupler, 3 dB, 26.5-40 GHz	\$450.00
HP R752D WR28 Directional Coupler, 20 dB, 26.5-40 GHz	\$450.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$250.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz	\$750.00
HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz	\$650.00
HP X870A WR90 Slide Screw Tuner	\$150.00
HUGHES 45322H-1110/1120 WR22 Directional Couplers, 10 or 20 dB, 33-50 GHz	\$350.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz	\$750.00
HUGHES 45714H-1000 WR15 Frequency Meter, 50-75 GHz	\$900.00
HUGHES 45721H-2000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 G	\$1000.00

HUGHES 45722H-1000 WR22 Direct Reading Attenuator, 0-50 dB, 33-50 GHz	\$1000.00
HUGHES 45724H-1000 WR15 Direct Reading Attenuator, 0-50 dB, 50-75 GHz	\$1000.00
HUGHES 45732H-1200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz	\$250.00
HUGHES 45752H-1000 WR22 Direct Reading Phase Shifter, 0-360, 33-50 GHz	\$1400.00
HUGHES 45772H-1100 WR22 Thermistor Mount, -20 to +10 dBm, 33-50 GHz	\$400.00
HUGHES 47316H-1111 WR10 Tunable Detector, 75-110 GHz, pos. polarity	\$600.00
HUGHES 47741H-2310 WR28 Phase Locked Gunn Osc., 32 GHz, +18 dBm	\$2000.00
HUGHES 47742H-1210 WR22 Phase Locked Gunn Osc., 42 GHz, +18 dBm	\$2750.00
KRYTAR 201020010 Directional Detector, 1-20 GHz, SMA(f)/SMC	\$200.00
KRYTAR 2616S Directional Detector, 1.7-26.5 GHz, K(f)/m/SMC	\$200.00
M/A-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, +40 dBm	\$450.00
NARDA 3000-series Octave Band Directional Couplers, N connectors	\$150.00
NARDA 3020A Bi-Directional Coupler, 50-1000 MHz	\$500.00
NARDA 3022 Bi-Directional Coupler, 20 dB, 1-4 GHz	\$450.00
NARDA 3024 Bi-Directional Coupler, 0-20 dB, 4-8 GHz	\$375.00
NARDA 3090 Precision High Directivity Couplers	\$225.00
NARDA 368BMM Coaxial Hih Power Load, 500 Watts, 2-18 GHz, N(m)	\$500.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz	\$900.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz	\$950.00
NARDA 4000-series Octave Band Directional Couplers, SMA connectors	\$75.00
NARDA 4247-20 Directional Coupler, 20 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 5070-series Precision Reflectometer Couplers	\$300.00
NARDA 562 DC Block, 10 MHz-12.4 GHz, 100 V max., N(m/f)	\$65.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f)	\$165.00
NARDA 791FM Variable Attenuator, 0-37 dB, 2.0-12.4 GHz	\$500.00
NARDA 792FM Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$375.00
NARDA 793FM Direct Reading Variable Attenuator, 0-20 dB, 4-8GHz	\$225.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8GHz	\$375.00
OMNI-SPECTRA 2085-6010-00 Crystal Detector, 1-18 GHz, neg. polarity, SMA m/f	\$50.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$250.00
SONOMA SCI. 21A3 WR42 Circulator, 20 dB, 2.0-24.8 GHz	\$75.00
TEKTRONIX 2701 Step Attenuator, 0-79 dB, DC-1 GHz	\$150.00
TRG B510 WR22 Direct Reading Attenuator, 0-50 dB, 33-50 GHz	\$900.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$600.00
TRG W510 WR10 Direct Reading Attenuator, 0-50 dB, 75-110 GHz	\$1000.00
TRG W551 WR10 Frequency Meter, 75-110 GHz	\$750.00
WAVELINE 100080 WR28 Terminated Crossguide Coupler, 30 dB	\$200.00
WEINSCHEID 150-110 Programmable Step Att., DC-18 GHz, SMA	\$450.00
WEINSCHEID DS109 Double Stub Tuner, 1-13 GHz, N(m/f)	\$150.00
WEINSCHEID DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(m/f)	\$150.00

## COMMUNICATIONS

HP 87304A-003 GPIB Extender, fiber-optic connection "unused"	\$250.00
HP 59401A GPIB Bus Analyzer	\$375.00
TAMPA MW. LAB BUC1W-02W-CST Ku band Upconverter, 1 Watt 14.0-14.5 GHz WR75 "NEW"	\$150.00
TEKTRONIX 1411R-opt.04 PAL Test Gen., w SPG12, TSG11, TSG13, 15, 16	\$1400.00
TEKTRONIX 147A NTSC Test Signal Generator, with noise test signal	\$800.00

## MISCELLANEOUS

EG&G/ P.A.R. 5302 / 5316 Lock-in Amplifier, 100 mHz-1 MHz, GPIB / RS232C	\$2250.00
FLUKE 2180A RTD Digital Thermometer	\$500.00
HP 59307A GPIB VHF Switch	\$200.00
P.A.R. 5206-95.98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB	\$1250.00
TEKTRONIX TM5003 TM5000-series 3-slot Programmable Power Module	\$450.00
TEKTRONIX TM5006 TM5000-series 6-slot Programmable Power Module	\$500.00
TEKTRONIX TM503 TM500-series 3-slot Power Module	\$150.00
TEKTRONIX TM504 TM500-series 4-slot Power Module	\$175.00
TEKTRONIX TM506 TM500-series 6-slot Power Module	\$250.00
TEKTRONIX TM515 TM500-series 5-slot Portable Power Module	\$250.00

# News Bytes

## Prime Services Group Opens DSL Consumer Equipment Sales to the Internet

Prime Services Group, Inc., a Livermore, CA-based Disabled Veterans Enterprise has announced the opening of its Internet storefront, featuring proven Small Office/Home Office and consumer DSL hardware and accessories. The web

store will offer time-tested integrated DSL and Ethernet routers from Cayman Systems, Westell and Efficient Networks DSL modems, networking products, as well as hard-to-find POTS splitters, and filters.

Prime Services Group — a pioneer in the installation of ADSL premise equipment — launched its broadband installation unit in 1997, also providing training, technical support,

and product fulfillment, shipping over 40,000 installation kits a month. The web store is a natural extension of the brick and mortar fulfillment business offering consumers and businesses a convenient way to purchase new equipment and upgrade existing installations.

Prime Services Group also provides a wide range of installation services ranging from structured cabling

and riser management to MDU/MTU broadband and central office services. Prime Services Group is an experienced provider of broadband solutions featuring Tut Systems, Telco Systems, and GoBeam broadband products, just to name a few.

## Blockbuster and RadioShack Complete Consumer Electronics Pilot

Based on Results, Blockbuster Announces Plans to Develop Home Entertainment Electronic Offering

With the completion of a pilot program that introduced "RadioShack Cool Things" stores inside 130 Blockbuster locations, Blockbuster, Inc., has announced plans to develop a home entertainment electronic offering at its stores nationwide. The decision was made based on Blockbuster's overall work in consumer electronics, including the RadioShack trial, as well as the company's successful sale of other electronics offerings, including DIRECTV, over the past 16 months.

"Through our work in consumer electronics and specifically our trial program with RadioShack, we were able to gain valuable insights in a very cost-effective manner that will enable us to establish a profitable program selling select consumer electronics that complement our core business," said John Antioco, chairman and CEO for Blockbuster.

According to Antioco, the RadioShack pilot program, which consisted of placing a miniaturized RadioShack store inside Blockbuster, included a wider breadth of product than Blockbuster customers wanted and required.

Based on results from this pilot program and other tests, Blockbuster will customize its line-up of consumer electronics with a business model that provides for minimal capital investment and a more efficient use of store space and labor than the RadioShack in-store trial required. Blockbuster anticipates being in a position to introduce a selection of consumer electronics later this year.

Blockbuster has had a history of selling consumer electronics prior to the RadioShack test. The company began selling DIRECTV in 2000, and in less than one year had become the nation's No. 2 DIRECTV retailer.

In addition, the company has sold an assortment of consumer electronics products, including home theater products, DVD, and VHS combo players and mobile phones.

In February, Blockbuster and RadioShack announced their plan to test a RadioShack store within-a-store concept inside Blockbuster locations. By July, the two companies had opened approximately 130 "RadioShack Cool Things" stores in four pilot markets. **NV**

# Test Equipment Connection Corporation

Test Equipment Connection is looking to purchase your excess or underutilized electronic test and measurement equipment. We buy the largest variety of electronic test equipment in the industry.

# WE BUY TEST EQUIPMENT



RENT

REPAIR



TRADE

SELL



CALL: 800.615.8378

FAX: 800.819.8378

WWW.TestEquipmentConnection.COM

Specialist in Hewlett-Packard, Tektronix, and many more manufacturers.

Circle #78 on the Reader Service Card.

## AMAZING DEVICES

See and Order from Our "Action" Web Site at [www.amazing1.com](http://www.amazing1.com)

### Laser Window Bounce Listener

Powerful listening system, yet simple in operation. You shine a laser at a window and intercept the reflected beam with our ultrasensitive filtered optical receiver. Vibrations on the window from internal sounds and voices are now clearly heard. Range can be up to several hundred meters depending on laser power and optics used.

LWB9 Plans for 3 Laser Window Bounce Systems.....\$20.00

LWB6K Kit of 100' visible red for Science Project.....\$129.95

High performance modules require housing and simple alignment to make a field worthy LASER WINDOW BOUNCE unit. Shows test tone circuitry, optics and our lab method of a completed assembly.

LWB90 Assembled receiver, 10 mw IR laser, collimator etc. \$449.95

### PLASMA FIRE SABERS

Kits, Parts and Accessories  
Duplicates effect in the motion picture epic of the century.

Specify blue, gm, pur, red or yell.  
Moving light appears to evaporate into space.  
Blades screw into handle for easy replacement.

We stock all size and color blades, mauler adapters, tubes digital drivers, and parts for authentic designs. Wireless interactive sound modules change tone with motion.

SAB15 Assembled with 15" Blade.....\$39.95

SAB24 Assembled with 24" Blade.....\$79.95 SAB24K Kit.....\$59.95

SAB36 Assembled with 36" Blade.....\$149.95 SAB36K Kit.....\$129.95

### Take Control!! Electronic Hypnosis

Electronic circuitry places subject under your control! Induces ALPHA relaxed mind states.

HYP2 Plans.....\$10.00

HYP2K Kit/Plans.....\$49.95

HYP20 Ready to Use.....\$69.95

MIND2 Plans for Mind Control.....\$15.00

MIND2K Kit/Plans.....\$49.95

MIND20 Ready to Use.....\$79.95

### 6 Transmitter Kits

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter.
- 2 1 Mile+ Telephone Transmitter.
- 3 Line Powered Phone Transmitter Never Needs Batteries!!
- 4 Tracking/Homing Beacon Beeping Transmitter.
- 5 Video/Audio Rebroadcast 1 Mi.
- 6 TV/FM Radio Disrupter. Neat Prank! Discretion Required.

Includes Hints Using Wireless Devices

COMBOX Above 6 Kits/Plans.....\$59.95

COMBOP Above 6 Plans Only.....\$10.00

### Pain Field Pistol

Caution! Do not aim at people! Blast out rodents with high power ultrasonics.

Handheld and battery operated with all controls.

Rental units available.

PPP1 Plans.....\$8.00

PPP1K Kit/Plans.....\$49.95

PPP10 Ready to Use.....\$79.95

### Jacob's Ladder

A 1/2" arc expands to over 4' as it travels up the Jacobs Ladder evaporating in space.

Adjustable arc control  
Uses safe high frequency  
Safety shock shut down

Full 20" ladder length

110/220 vac 150 watts

JACK3K Kit.....\$149.95

JACK30 Ready to Use.....\$249.95

### 30" Spark Tesla Coil

Create a spectacular display of nature's own lightning. Many amazing experiments possible.

See coil in action on our website!

BTC4 Plans.....\$20.00

BTC4K Kit.....\$899.95

BTC40 Ready to use.....\$1199.95

Smaller Version (8-10" Sparks)

BTC3 Plans.....\$15.00 BTC3K Kit.....\$349.95

BTC30 Ready to Use.....\$449.95

MINI TESLA COIL Lights 4' light tube!

MT1C1 Plans.....\$5.00 MTC1K Kit.....\$19.95

MTC10 Assembled for 12 volts.....\$34.95

### Hover Board

28 pages of data related to the most revolutionary advance in transportation. Cutting edge R&D.

HOVER Plans and Data.....\$25.00

### Anti Gravity

Float an object using anelectric force field. With handbook.

GRA3 Plans/book.....\$20.00

GRA3K Kit/Pwr Sup.....\$99.95

GRA30 Assembled above.....\$149.95


Information Unlimited PO Box 716 Amherst N.H. U.S.A. 03031 E-mail [info1@xtdl.com](mailto:info1@xtdl.com)

1 800 221 1705 Orders/Catalogs Only! Fax 1 603 672 5406 Information 1 603 673 4730 Free Catalog on Request

Pay by MC, VISA, Cash, Check, MO. Add \$5.00 S&H Overseas Contact for Proforma

Circle #79 on the Reader Service Card.
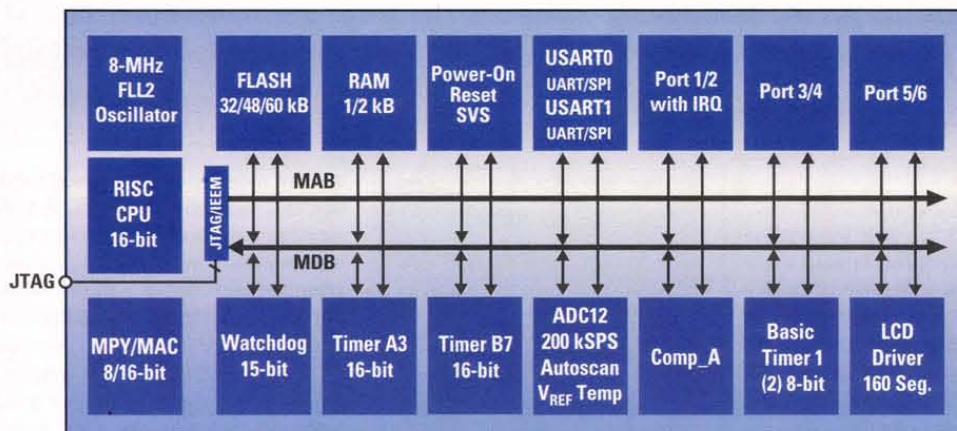
## MSP430F449: Imagine the possibilities.



### Features:

- Ultralow-power Flash MCU with high-performance 200-kSPS ADC and LCD driver on one chip
- Power consumption of <1  $\mu$ A in standby mode extends battery life
- Modern 16-bit RISC CPU enables new applications at a fraction of the code size
- In-system programmable Flash permits last-minute code changes, field upgrades and data logging to Flash

### MSP430 – the choice in ultralow-power Flash MCUs

Experience the ultimate SOC solution for battery-powered measurement. A flexible clock system switches from ultralow-power standby to high-performance signal processing in less than 6  $\mu$ s. Embedded emulation reduces design cycle time. Get your design started today with the easy-to-use MSP-FET430P440 Flash emulation tool.

Device	Flash Memory	Price 1K
MSP430F449	60 kB	\$7.03
MSP430F448	48 kB	\$6.47
MSP430F447	32 kB	\$5.71

Device	Flash Memory	Price 1K
MSP430F437	32 kB	\$4.90
MSP430F436	24 kB	\$4.70
MSP430F435	16 kB	\$4.45



MSP-FET430P440 development tool-\$99

Contact us to request:  
development tools  
product bulletin (SLAB034C)  
MSP430F44x data sheets

[www.ti.com/sc/hpa7227u](http://www.ti.com/sc/hpa7227u)

1-800-477-8924, ask for ext. 7227

# Electronics Q&A

With TJ Byers

*In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist.*

*Feel free to participate with your questions, as well as comments and suggestions.*

*You can reach me at: [TJBYSERS@aol.com](mailto:TJBYSERS@aol.com) or by snail mail at Nuts & Volts Magazine, 430 Princland Ct., Corona, CA 92879.*

## What's Up:

Use your PC to help in the fight to find a cure for cancer. Answers concerning temperature sensors, controllers, non-contact sensing, and thermal imaging. Need to design a squarewave oscillator? Got your numbers. And Gordon Moore's legacy.

## Point-and-Shoot Thermometers

**Q** • I've seen non-contact thermometers, but I have little knowledge about how they work. From what I've gathered, the human body radiates energy at around 9-10 microns. How does a passive IR device measure so accurately in such a narrow bandwidth? Would a mirror reflect "object" readings, or indicate its own temperature under this kind of test? What kind of sensor reads down in the "basement regions" and differentiates the frequencies so well? How does it differ from the sensors in FLIR systems?

Les KA9GLW  
via Internet

**A** • Let's first put these two topics into their proper perspective. FLIR (forward looking infrared) is an infrared camera that takes a snapshot of an object using the heat it radiates to produce an image, as shown in the picture below of two mugs filled with hot coffee.

A non-contact IR thermometer, on the other hand, is something like a radar gun, in that it can measure the temperature of a distant object by pointing the "pistol" and pulling the trigger.

All matter — animate or inanimate — with a temperature above absolute zero (273.1 degrees below zero C) emits thermal energy with its surroundings in the form of electromagnetic radiation. The characteristic spectrum of the radiation depends on the object and its surrounding temperatures. By analyzing this spectrum, the temperature of an object can be measured without the need for direct contact.

Without delving into quantum mechanics and Planck packets, suffice it to say that each temperature has its own characteristic spectrum pattern. As the temperature increases, so does the energy level contained within the spectrum envelope, and the more pronounced is the peak frequency.

The heat spectrum — the part we are interested in — extends from 0.7um (700nm) to about 30um. And yes, the temperature of the human body has a peak wavelength between 9um and 10um. By analyzing the peaks and energy levels of the emitted spectrum, the temperature of the body can be accurately measured. That's what an IR thermometer — a.k.a., radiation thermometer — does.

A radiation thermometer consists of an optical system and detector. The optical system focuses the energy emitted by an object onto the detector; the output of the detector is proportional to the amount of energy radiated by the target object (less the amount absorbed by the optical system), and the response of the detector to the specific radiation wavelengths. Three types of detectors are commonly used: thermal, photon, and pyroelectric.

Thermal detectors, which generate an output voltage when heated,



are the most commonly-used radiation thermometer detectors. A thermopile consists of one or more thermocouples in series, usually arranged in a radial pattern so the hot junctions form a small circle. These detectors have lower sensitivity compared to other detector types, and the speed of their response is limited by their mass. However, they are less affected by changes in the radiated wavelengths and can be found for under \$100.00. For an in-depth look at this fascinating technology, go to

Omega Engineering's web site at


[www.omega.com/literature/transactions/volume1/historical1.html](http://www.omega.com/literature/transactions/volume1/historical1.html).

## IBM Sound Card Connector

**Q** • I have a model MM55 monitor made by IBM that came with my Aptiva PC. Inside this monitor is an excellent Bose speaker system that I can't use with this computer because there is no cable that connects to the monitor's seven-pin DIN socket and the PC's sound cards. What I need to know is the pinout of the DIN connector so that I may fabricate a cable of my own.

Burton Daggett, Sr.  
Shelton, WA

**A** • Here it is.

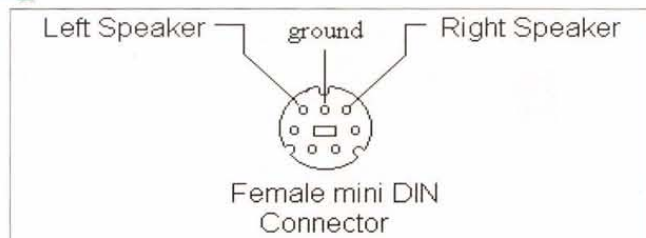


## Hard Drive Cooler Thermostat


**Q** • I purchased a hard drive cooler from Jameco (#170595) which came without a temperature control switch, which means the three fans stay on constantly when the PC is turned on. I would like to add a MAX6510 temperature control switch as shown in the Jul. 2001 issue (page 27), but I want it to be powered from the 12-volt source that powers the fans (no external battery). Can this be done? Also, what type of diode is used in the original diagram?

Dan Ghergher  
via Internet

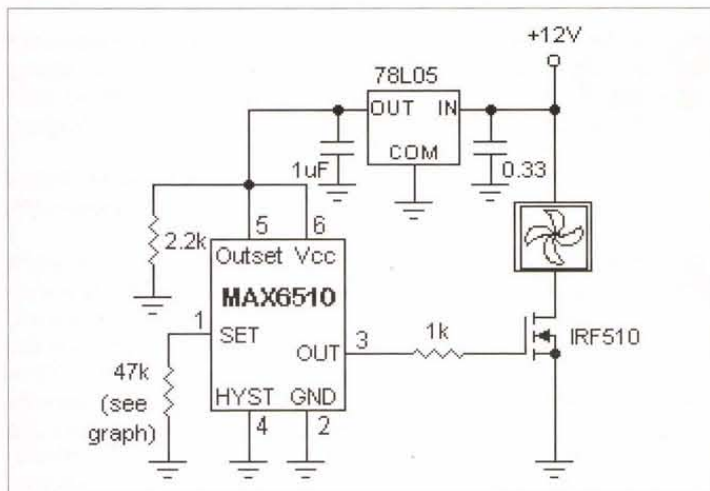**A.** Now that I know the exact voltage and current ratings of your motors, I can streamline the design. First, the relay is replaced by an IRF 510 transistor, which also eliminates the "mystery" diode (1N4001) and 2N2222A transistor. The FET can handle loads up to 5.6 amps.



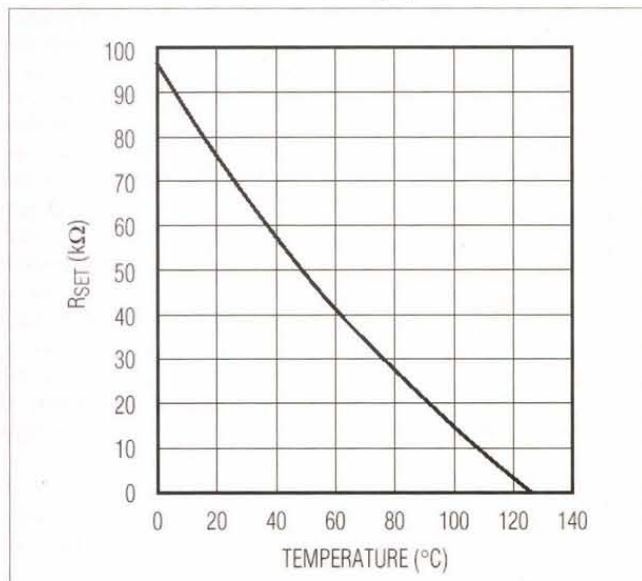Next, a 78L05 regulator is added to power the MAX6510 controller from the PC's 12-volt line, and the setpoint pot has been replaced with a fixed Rset resistor. The value of the resistor sets the temperature at which the fans kick in, as shown in the graph below.



## Two PCs, One Monitor, One Switch

**Q.** I have a Pentium PC that I use daily and an old 486 computer that I use on occasion — but only one monitor. This usually requires switching the monitor from one PC to the other by swapping cables. Is there a way to safely switch on the fly? I was thinking I could build a circuit switch with voltage-follower op amps with a switch in the center. Or is there a better way to do this?

**Matthew Flynn**  
via Internet


**A.** This is a common request — so common, in fact, that several manufacturers make switch boxes just for this purpose. Some of the switch boxes are buffered with video amplifiers, while others (at the bottom of the line, and less expensive) are simple A/B switches. Prices range from over \$200.00 to as little as \$11.00. **Jameco (800-831-4242; [www.jameco.com](http://www.jameco.com))** has a good selection of switch boxes of different types and prices.

## Trucker Keeps His Cool

**Q.** After many years of fighting overheating problems with my truck, I installed an oversized radiator that requires a twin-motor electric cooling fan assembly that draws over 15 amps per motor. Since it has knocked out two alternators in short order — the second being a higher amperage unit — I would like to find a temperature-controlled, time-delay circuit to keep both fans from starting at the same time. I would prefer using a Type-J thermocouple as the sensor, as I have lots of these, but a thermistor would be fine. The two outputs should be able to operate 12-volt relays with 72-ohm coils, another part I have on hand.

**Tim LeMaster**  
via Internet

**A.** This circuit can be quite simple if we use a radiator switch (which you probably already have installed) instead of a thermocouple. Although the triggering temperature will be fixed, it eliminates the design problems associated with using low-voltage sensors in a harsh environment found under the hood of a car. But this is a small price to pay for a protector that lessens the burden on your electrical system.

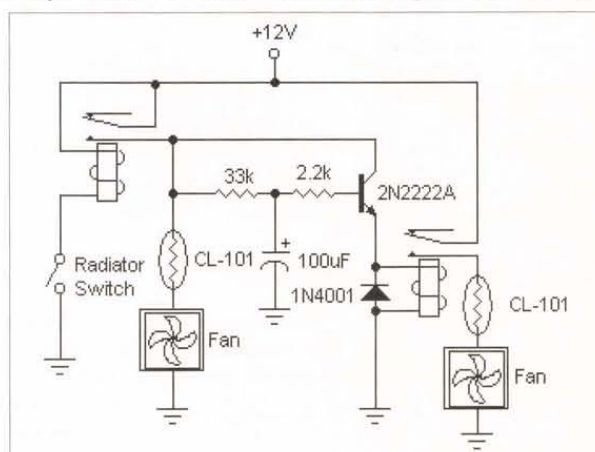

The radiator switch turns on the first relay when the water temperature exceeds the preset limit, typically 195 degrees (F). This applies power to the first fan and the second relay timer circuit, which consists of a 2N2222A transistor, timing capacitor, and timing resistors. When power is applied, the capacitor begins to charge. About five seconds later, the voltage across the capacitor turns on the transistor and engages the second relay. Both motors have an inrush current limiter, an NTC (negative temperature coefficient) thermistor, that prevents the alternator from being hit with a big surge of starting current. As the thermistor heats up, its internal resistance decreases and delivers full power to the now-spinning fan. The delay time between fan #1 and fan #2 can be increased or decreased by changing the value of the timing resistor — more capacitance means a longer delay.

## Cool Web Sites!

Would you like to help in the search for a cure for childhood leukemia or Alzheimer's Disease? In conjunction with participating scientific organizations, Intel has formed a philanthropic program that lets you share your PC's resources to help fight these and other life-threatening diseases. To participate, log on to their secured site.  
[www.intel.com/cure](http://www.intel.com/cure)

Iron Pyrites Negative Resistance Oscillator  
<http://home.earthlink.net/~lenyr/iposc.htm>

Free magazines!  
[www.motionnet.com/cgi-bin/search.exe?a=cat&no=1947](http://www.motionnet.com/cgi-bin/search.exe?a=cat&no=1947)


If you're searching for a magazine article you've read in the past, or need to find related articles using keywords, check out FindArticles.  
[www.findarticles.com](http://www.findarticles.com)

## Gordon Moore's Legacy

**Q** • What is Moore's Law? I can't find it anywhere in my reference books.

Barbara Brant  
via Internet

**A** • Well, it's not a law in the truest sense of the word like Ohm's Law. Instead, it's an observation set forth by Gordon Moore, cofounder of Intel, which predicted that the number of transistors per integrated circuit would double every 18 months. He forecast that this trend would continue through 1975. However, Moore's Law has lasted far longer than expected, and still holds true to this day despite accelerated advances in chip technology.

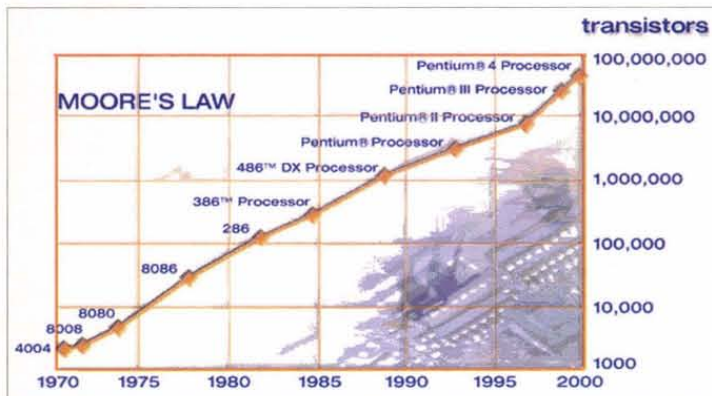


## Fan Speed Senses Temperature

**Q** • I'm currently taking an engineering course in electronic design and want to do a circuit that controls the speed of a fan with respect to the temperature. Please explain how this is done.

Peter Moses  
via Internet

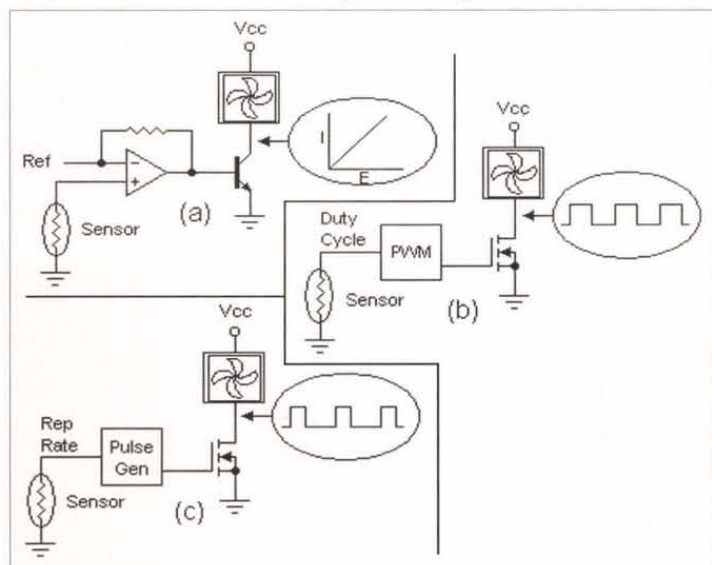**A** • Do I get the credits if you pass the class? Seriously, this is something you have to do on your own. However, I will suggest three methods that are commonly used for this application. It's then up to you to decide on the method and design a working circuit.



The top circuit (a) is a linear amplifier that drives a power transistor to control the voltage and current flowing through the fan. The next two circuits are pulse modulated, which adds to the efficiency of the controller (i.e., less power dissipated (wasted) by the power transistor). The first (b) uses PWM (pulse-width modulation) where the duty cycle of the squarewave determines the power applied to the fan. The smaller the

duty cycle, the slower the fan spins. The bottom circuit (c) uses a pulse generator with a variable pulse rate. The higher the pulse rate, the more average power applied to the fan, and the faster it spins.


## Squarewave Oscillator Designs

**Q** • In the following figures are two oscillators. I want to replace the top oscillator with the bottom circuit (it's an upgrade to an existing instrument). What I need to do is find the frequency of circuit (a), then calculate the values needed for circuit (b) so that it's the same frequency. Can you help me out?

Craig Kendrick Sellen  
Simpson, PA


**A** • Before we start, let me point out that your second circuit isn't a good replacement for your application, so I took the liberty of substituting an equivalent circuit for figure (b). Your original circuit is a veteran of many wars, and has served the industry well. But the days of discrete transistor designs are all but over, and making the move to ICs is logical. This astable multivibrator has no stable state, which means as the feedback capacitors charge and discharge, the transistors' bias point shift the collector currents on and off. If the timing capacitors and resistors are perfectly matched, the output will be a square wave. However, this is seldom the case, resulting in a duty cycle that is less than symmetrical. Moreover, this design is voltage and temperature sensitive, which leads to frequency drift. The frequency can be calculated using the formulas shown below — 4.83 kHz, for the values listed.

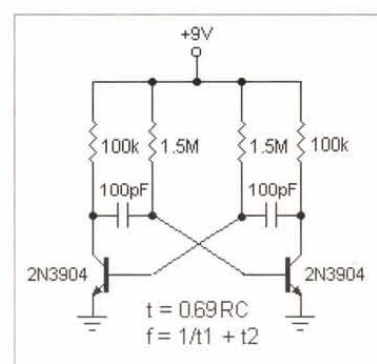The next step is to calculate the values for the new CMOS oscillator. Unlike the transistor version, the new circuit uses a single timing resistor



and capacitor to provide good squarewave symmetry. The circuit is also less sensitive to voltage and temperature variations, and uses one-half the number of components. Only one resistor, one capacitor, and two gates are needed; the extra resistor (1M) and gate provide buffering that sharpens up the squarewave. Substituting the values listed in circuit (b) results in a calculated frequency of 4.54 kHz; an actual breadboard version

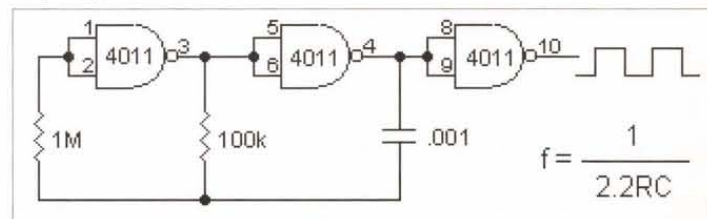measured a frequency of 4.71 kHz — close enough to the original frequency.



## EchoStar, Where Are You?

**Q** • I'd like information on hardware and software to "steer" an 18-inch TV satellite dish. The purpose is to scan the sky for 2.0 to 2.5 GHz signals. An inexpensive servo system would make sense, similar to that used with telescopes.

John Wax  
via Internet

**Q** • Do you have any ideas for a simple field strength meter to help set up direct satellite systems? Nothing fancy, just something that I can aim at the sky to get within the ballpark.

B. Mcphee  
via Internet



**A**. In the last few months, a unique instrument has appeared on retail shelves and several web sites. Generically dubbed satellite finders, these devices are field strength meters operating in the 950 to 2,000+ MHz range. Prices range

from \$19.00 up to \$49.00. Simply wire the meter between the dish and the receiver, turn on your equipment (it provides power to the meter), and adjust the satellite dish until the meter indicates optimum signal strength.

Satellite finding software is mostly written by members of radio clubs and amateur astronomers. Unlike satellite finder meters, the software uses mathematics to plot the position of satellites using celestial and/or terrestrial maps. Here are a couple of promising web sites.

## RealityNET

<http://translate.google.com/translate?hl=en&sl=fr&u=http://www.reality.be/telecom/satellite/calc.htm&prev=/search%3Fq%3Dsatellite%2Bfinder%26hl%3Den%26sa%3DG>

## Satellite Finder

[www.arachnoid.com/satfinder/](http://www.arachnoid.com/satfinder/)

## Satellite Hunting

<http://fathom.org/Stephen/sathunt.html>

## Engine, Engine Number 9

**Q**. As a locomotive engineer, I sometimes spend a lot of time sitting on a side track waiting for trains coming from the opposite direction to pass. In other words, I have a lot of time to kill, which is why I bring my laptop with me. My conductor and myself play games while we wait. The problem is that we often run down the battery. On a locomotive, in the cab, is a source of 74 volts DC, generated by an auxiliary generator to maintain the 64-volt starter batteries (just like your automobile, but 64 volts instead of 12 volts). What I need is a small DC-to-DC converter to drop the 74 volts down to 14 volts at about 1.2 amps that will replace the wallwart.

Unsigned  
via Snailmail

**A**. At first I thought of using an off-line switching IC, like the NCP1001 from ON Semiconductors (formerly Motorola). But for something as simple as substituting a laptop wallwart, it's overkill. A

Here is a short list of suppliers.

### Lashen Electronics

[www.lashen.com/vendors/JVI/sf20.asp](http://www.lashen.com/vendors/JVI/sf20.asp); 973-627-3783

### Sat-City (UK)

[www.sat-city.com/TST-Dynapacific-SF2300](http://www.sat-city.com/TST-Dynapacific-SF2300)

### Smarthome

[www.smarthome.com/775381.html](http://www.smarthome.com/775381.html)

### Trianglecables

[www.trianglecables.com/ansatfinmetw.html](http://www.trianglecables.com/ansatfinmetw.html)

### Yahoo! Shopping

<http://shop.store.yahoo.com/1soular/dirtvsatfint.html>

We accept Visa,  
Mastercard, AmEx,  
and Discover

# Attention: TECHIESTUDS

Fax: 318-424-9771

To Order Call 1-800-227-3971 [www.shrevesystems.com](http://www.shrevesystems.com)

## A MONITOR FOR ANY BUDGET!

14" Voxon VGA NEW  
ONLY....\$59!!!  
15" Voxon VGA NEW  
ONLY....\$89  
16" Rasterops fixed 832 X 624  
ONLY....\$79

Hot Deals  
on New  
Monitors!!!

H.P. 17" fixed res  
832 X 724  
ONLY....\$79  
H.P. 17" fixed res  
640 X 480  
ONLY....\$79  
14" VGA refurb ONLY....\$29

I'm  
only  
\$29!

15" 640x870  
Raster Full  
Page Display  
Refurbished  
Macs  
ONLY....\$49



Color Composite  
Display  
Great for  
Surveillance  
Refurbished  
NTSC Connectors

**\$39** VST External  
Firewire Case  
Accepts  
any IDE  
Hard  
Drive!

AS LOW AS  
\$59!

Be sure to check us out on the web at <http://www.shrevesystems.com> for the best prices on Vintage Mac gear!

**Peltier Junction Blowout!**  
with heat sink, works on 5V & 12V  
1 3/16" x 1 3/16"



Less Than \$5 Each or 4 for \$19

**Paper Shredders**  
On Sale!  
Protect your Privacy!  
Requires 12V



ONLY \$2

**Global Village**

Bronze  
External  
Modem  
2400  
Bps/9600  
Fax



ONLY \$0.50

CMS SCSI Case  
Holds 4 5.25 SCSI  
full ht. drives



Only \$49



**PDA Genuine Leather**  
Carry Case  
Let your palm pilot  
lead the life of luxury!  
Stock up now!

ONLY \$3



**PAS16 Audio**  
Spectrum  
For Mac LC Family16  
Bit Sound Editing Card

\$10

**Apple II 256K**  
Memory  
Expansion Kit  
HM51256P-10  
ONLY \$1

**RAM**  
1 MB 30 Pin 4 For \$1  
4 MB 72 Pin 2 For \$5

Miscellaneous	
Apple 8 bit Video Card	\$19
LaserWriter IINT	\$149
Apple ADB Keyboard	\$19
1.44 Super Drive	\$19
Clone ADB MouseII	\$19
Quicktake 100 Camera	\$99
Bernouli 90 MB EXT	\$10
44MB SyQuest Ext	\$10
88MB SyQuest Ext	\$19


**20/30 GB External**  
Firewire Hard Drives  
Starting at \$169!

Huge inventory! Huge savings!  
\$25 minimum order.

**Shreve Systems**  
1200 Marshall st  
Shreveport, La 71101

Prices reflect a 2% cash discount and are subject to change without notice. Returns are subject to a 15% restocking fee. Not responsible for typographical errors.

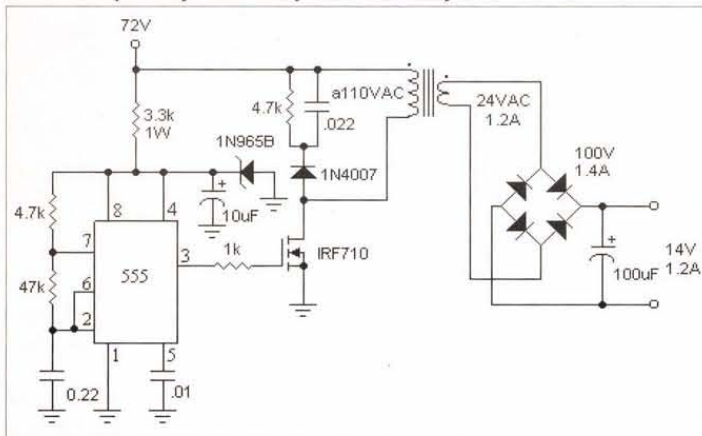simple step-down power transformer is plenty good enough. What got me to thinking along this line was the fact that the voltage ratio between 74 volts and 14 volts is about 5:1, which means an ordinary 24 VAC power transformer will work. All we have to do is apply a squarewave across the primary and rectify the secondary.



A 555 timer chip running as a squarewave generator switches the IRF710 HEXFET transistor on and off at a rate of 60 Hz, which generates about 14 VAC in the secondary. The diode-resistor-capacitor network across the primary acts as a snubber that removes unwanted har-

monics to prevent RFI and destructive high-voltage spikes. A 1N965B zener diode holds the Vcc of the 555 steady at 15 volts. At the other side of the transformer, a bridge rectifier turns the AC voltage into DC — and that's all there is. Simple, clean, and reliable.

## MAILBAG

Dear TJ:

I think you got scammed by the submission of the 90# AT&T technician story. This story is only partially true. Here is AT&T's official statement.

**David Nelson**  
Colorado Springs, CO

### Find out about the 9-0-# phone scam.

The 9-0-# scam has been around for years and is directed at businesses, hospitals, government agencies, and other organizations that use telephone switching equipment called private branch exchanges (PBXs) to handle their calls.

This type of fraud involves a perpetrator who calls an office and cons an unsuspecting worker into transferring him or her to an outside line. The perpetrator then starts dialing calls that are charged to the owner of the PBX. In this latest version, the caller claims to be an AT&T service technician "repairing" the phone lines and convinces the recipient of the call to help out by transferring him to an outside line and then hanging up.

Below are some points about this scam worth remembering:

- This scam doesn't affect residential customers; its target is businesses.
- An AT&T service technician would never call customers and ask them to help check phone lines.
- The scam is generating a lot of interest in the media and over the Internet, but our network fraud experts report no increase in the number of fraud cases as a result of this notoriety.
- The best prevention against this type of fraud is for business managers to make their office staffs aware of it and to review what to do if it happens.
- If someone receives such a call, he or she should ask the "technician" for a call-back number or for the name and number of the caller's supervisor. Then hang up.
- To report this or any other phone scams, AT&T business customers should call their account representatives. You also can call the AT&T Business Customer Care Center at **1-800-222-0400**, or report the scam to your local law enforcement agency.

## EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- [www.m2l.com](http://www.m2l.com)

**Fast** - Programs 27C010 in 23 seconds

**Portable** - Connects to PC Parallel Port

**Versatile** - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

**Inexpensive** - Best for less than \$200

- Correct implementation of manufacturer specified algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters listed below.


### Available Adapters

EP-PIC (16C55x, 61, 62x, 71, 84)	\$49.95
EP-PIC64 (16C62-5, 72-4)	\$39.95
EP-PIC12 (12C500)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751, C51)	\$39.95
EP-11E (68HC11 E/A)	\$59.95
EP-11D (68HC711D3)	\$39.95
EP-16 (16bit EPROMs)	\$49.95
EP-Z8 (Z86E02, 3, 4, 6, 7, 8)	\$39.95
EP-SEE2 (93x24x, 25x, 85x)	\$39.95
EP-750 (87C750, 1, 2)	\$59.95
EP-PEEL (IC22x10, 18x)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95

Many Other Adapters Available

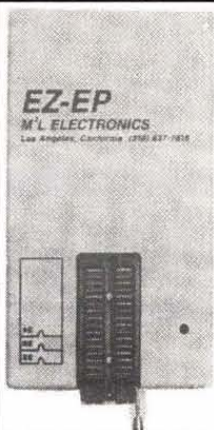**M<sup>2</sup>L Electronics**

970/259-0555  
Fax: 970/259-0777  
250 CR 218  
Durango, CO 81301  
CO orders please add 7% sales tax  
<http://www.m2l.com>



Circle #30 on the Reader Service Card.

## Stepper Motor Book

### Easy Step'n

- For the experimenter.
- Determine surplus stepper motor specs using simple easy to build test equipment.
- Design and build microcontroller-based control systems (flow charts and code examples included).
- Design and build stepper motor driver circuits.
- Analyze the mechanical characteristics of stepper motor-driven devices.
- The book is full of experiments, circuits and code.
- 8.5x11 format. 205 pages. \$34.95

Table Of Contents And Ordering Information On Web Site

<http://www.stepperstuff.com>

## SQUARE 1 ELECTRONICS

P.O. Box 501, Kelseyville, CA 95451  
Voice (707) 279-8881 Fax (707) 279-8883

We have been selling on the Internet since 1996. We will ship the day we receive your order or the next business day.

## PICmicro® PIC16F87x Series and ICD Book

### Easy Debug'n

- Features of PIC16F87x microcontrollers
- In-circuit debugging using Microchip ICD
- Companion for our PIC'n book series
- 8.5x11 format.
- 72 pages. \$12.95

Table Of Contents And Ordering Information On Web Site

<http://www.sq-1.com>

## PICmicro® BOOKS

### LEARN ABOUT MICROCONTROLLERS

<b>Easy PIC'n - Beginner</b>	\$29.95
<ul style="list-style-type: none"> <li>• Programming Techniques</li> <li>• Instruction set, addressing modes, bit manipulation, subroutines, loops, lookup tables, interrupts</li> <li>• Using a text editor, using an assembler, using MPLAB</li> <li>• Timing and counting (timer 0), interfacing, I/O conversion</li> </ul>	
<b>PIC'n Up The Pace - Intermediate</b>	\$34.95
<ul style="list-style-type: none"> <li>• Serial communication - PICmicro to peripheral chips</li> <li>• Serial EEPROMS</li> <li>• LCD interface and scanning keypads</li> <li>• D/A and A/D conversion - several methods</li> <li>• Math routines</li> </ul>	
<b>PIC'n Techniques - Intermediate</b>	\$34.95
<ul style="list-style-type: none"> <li>• 8-pin PICmicros</li> <li>• Timer 1, timer 2 and the capture/compare/PWM (CCP) module</li> <li>• Talking to a PICmicro with a PC using a terminal program</li> <li>• Test equipment and data logger experiments</li> </ul>	
<b>Serial PIC'n - Advanced</b>	\$49.95
<ul style="list-style-type: none"> <li>• Synchronous - bit-bang, on-chip UART, RS-232</li> <li>• Asynchronous - I2C (Philips Semiconductor)</li> <li>• SPI (Motorola), Microwire (National Semiconductor)</li> <li>• Dallas Semiconductor 1-Wire bus</li> </ul>	

PICmicro and MPLAB are trademarks of Microchip Technology Inc.

Table Of Contents And Ordering Information On Web Site

<http://www.sq-1.com>

**CALL TOLL-FREE**

(800) 292-7711 Orders  
Only

Se Habla Español

# C&S SALES

Secure On-line Ordering @ [cs-sales.com](http://cs-sales.com)

CALL OR WRITE  
FOR OUR  
**FREE**

64 PAGE CATALOG!  
(800) 445-3201

## Digital Multimeters

### Elenco Model M-1740



**\$19.95**

- 11 Functions:**
- Freq. to 20MHz
  - Cap. to 20µF
  - AC/DC Voltage
  - AC/DC Current
  - Beeper
  - Diode Test
  - Transistor Test
  - Meets UL-1244 safety specs.

### Elenco Model LCR-1810



**\$89.95**

- Cap. 0.1pF to 20µF
- Inductance 1µH to 20H
- Resistance 0.01Ω to 2,000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Freq. up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

### Elenco Model LCM-1950



**\$65**

- Large 1 3/4 Digit LCD
- Autorangeing Freq. to 4MHz
- Cap. to 400µF
- Inductance to 40H
- Res. to 4,000MΩ
- Logic Test
- Diode & Transistor Test
- Audible Continuity Test

## LCR Bridge

### B&K Model 878



**\$229**

- Accurately measures capacitance, resistance, and inductance.
- Measures dissipation factor of capacitors and Q of inductors.
- Simultaneously displays measures, value, and Q or dissipation factor.

## Deluxe Soldering Stations

### Elenco SL-5 Series

Electronically controlled, ideal for professionals, students, and hobbyists. Available in kit form or assembled.

As Low As  
**\$24.95**

Works w/ any iron! Turn any soldering iron into a variable iron.

#### Features:

- Cushion Grip Handle
- Soldering Iron (optional) with Grounded Tip for Soldering Static-Sensitive Devices. Easily Replaceable. Uses Long-Life, Plated Conical Tip.
- Heavy Steel, Non-Slip Base.
- Iron Holder Funnel - Reversible, left or right side.
- Steel Tray for Sponge Pad.
- Sponge Pad.

**Quantity Discounts Available**

### Ordering Information:

Model SL-5 - No iron. (Kit SL-5K) **\$24.95**

Model SL-5-40 - Includes 40W UL iron. (Kit SL-5K-40) **\$29.95**

### Elenco Model SL-30



**\$79.95**

- Tip temperature changeable from 300°F (150°C) to 900°F (480°C).
- Temperature is maintained within +10°F of its preset temperature.
- The tip is isolated from the AC line by a 24V transformer.
- The tip is grounded to eliminate static charges.

SL-10 - Same as SL-30 w/o digital display **\$59.95**

### Weller® Low Cost Soldering Iron Model WLC100



- Variable power control produces 5-40 watts.
- Ideal for hobbyists, DIYers and students.
- Complete with 40W iron.

**\$54.95**

## Test Equipment

### Elenco Four Functions in One Instrument Model MX-9300B

#### Features:

- One instrument with four test and measuring systems:
  - 1.3GHz Frequency Counter
  - 2MHz Sweep Function Generator
  - Digital Multimeter
  - Digital Triple Power Supply



**\$450**

### Elenco 3MHz Sweep Function Generator with built-in 60MHz Frequency Counter Model GF-8046

**\$199.95**



Generates square, triangle, and sine waveforms, and TTL, CMOS pulse. GF-8025 - Without Counter **\$139.95**

### 20MHz Sweep / Function Generator with Frequency Counter Model 4040A

- 0.2Hz to 20MHz
- AM & FM Modulation
- Burst Operation
- External Frequency Counter to 30MHz
- Linear and Log Sweep



10MHz Model 4017A **\$325**  
5MHz Model 4011A **\$259**  
2MHz Model 4010A **\$225** **BK PRECISION**

### Elenco Handheld Universal Counter 1MHz - 2.8GHz Model F-2800



**\$99**

- Sensitivity:**
- <1.5mV @ 100MHz
  - <5mV @ 250MHz
  - <5mV @ 1GHz
  - <10mV @ 2.4GHz

Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter.

C-2800 Case w/ Belt Clip.....**\$14.95**

### Elenco RF Generator with Counter (100kHz - 150MHz) Model SG-9500



**\$225**

Features internal AM mod. of 1kHz, RF output 100mV - 35MHz. Audio output 1kHz @ 1V RMS. SG-9000 (analog, w/o counter) **\$119**

### Elenco Quad Power Supply Model XP-581

4 Fully Regulated Power Supplies in 1 Unit



**\$75**

4 DC Voltages: 3 fixed: +5V @ 3A, +12V @ 1A, 1 variable: 2.5 - 20V @ 2A • Fully Regulated & Short Protected • Voltage & Current Meters • All Metal Case

### Elenco Power Supply Model XP-603



**\$75**

• 0-30VDC @ 3A Output  
• 3A Fused Current Protection  
• Current Limiting Short Protection  
• 0.025Ω Output Impedance

### Elenco 10Hz - 1MHz Digital Audio Generator Model SG-9300



**\$225**

Features built-in 150MHz frequency counter, low distortion and sine/square waves. SG-9200 (w/o counter) **\$119**

## Elenco Oscilloscopes

Free Dust Cover and 2 Probes



S-1325 25MHz Dual Trace **\$325** S-1345 40MHz Delayed Sweep **\$549**  
S-1330 25MHz Delayed Sweep **\$439** S-1360 60MHz Delayed Sweep **\$725**  
S-1340 40MHz Dual Trace **\$475** S-1390 100MHz Delayed Sweep **\$895**

### Deluxe 29pc. Computer Service Tool Kit \$36.95 Elenco Model TK-1200

Includes Soldering Iron, Solder, Long Nose Pliers, Diagonal Pliers, 11 pc. Screwdriver Bit Set, Wire Stripper, IC Extractor, Screwdriver, Phillips Screwdriver, Desoldering Pump, and more!



## Elenco Educational Kits

### Model XK-150

Digital / Analog Trainer



**\$89.95**

### OWI Model OWI-007

Robotic Arm Trainer



**\$82.50**

### Model AM-780K

Two IC Radio Kit



**\$9.95**

### Model AK-700

Pulse/Tone Telephone Kit  
Flashing Neon Lights  
Great School Project



**\$14.95**

### Model RCC-7K

Radio Control Car Kit



**\$27.95**

- 7 Functions
- Transmitter Included

### Model M-1005K

DMM Kit



**\$18.95**

### Model K4001

7W Amplifier



**\$12.95**

## Electronic Science Lab

### Maxitronix 500-in-1 Electronic Project Lab Model MX-909

Everything you need to build 500 exciting electronic projects:

- Learn the basics of electronics. 500 different electronic experiments, special lighting effects, radio transmitter and receivers, sound effects, cool games and MORE!
- Includes built-in breadboard and an LCD.
- Explore amplifiers, analog and digital circuits plus how to read schematic diagrams.
- Includes 11 parts.
- Lab-style manual included.
- Requires 6 "AA" batteries.



MX-908 - 300-in-1 Lab **\$59.95**  
MX-907 - 200-in-1 Lab **\$44.95**  
MX-906 - 130-in-1 Lab **\$29.95**  
EP-50 - 50-in-1 Lab **\$18.95**

**\$149**

## Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 5% (Minimum \$5.00)

OTHERS CALL FOR DETAILS

IL Residents add 8.25% Sales Tax

**SEE US ON THE WEB**

## C&S SALES, INC.

150 W. CARPENTER AVENUE  
WHEELING, IL 60090  
FAX: (847) 541-9904 (847) 541-0710  
<http://www.cs-sales.com>



## 15 DAY MONEY BACK GUARANTEE

## 2 YEAR FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

# LASER INSIGHT

By Stanley York

**T**his month, we're going to look at another kind of laser system that has deeply penetrated our industrial lives — the laser marker. Some people call them laser engravers or laser etching systems, so I'll be different and use all three terms interchangeably. Laser markers are fascinating to watch in operation (through safety goggles, of course), and mere words cannot convey adequately the impression that these machines will leave on your mind.

In looking at how the laser marker works, we are going to be revisiting some old ground, but we'll also be exploring new territory.

## Why a laser marker?

For many years, a number of different marking methods have been in use in industry for identifying and serializing products coming off the production lines. Among them are acid etch, inkjet, paint jet, pin stamping, rotary tool engraving,

and so on ...

However, each of these methods leaves something to be desired. In recent years, the EPA has come down hard and heavy on industrial pollution. The results of the crackdown show up in the cost of the finished product (after all, somebody has to pay to dispose of the chemical waste from these machines).

Waste products from acid etch, paint marking, and inkjet carry a high price for disposal. Therefore, these methods have begun to lose favor in recent years. Not only through the expense of disposal, but also through lost time due to worker injuries, and general health issues evolving from the various inks and chemicals used in these processes.

These marking methods are also slow and messy, and require extensive clean-up between batches of product. They also require masks for each character, to shield the unmarked portions of the product. Serializing by acid-etch, inkjet, or paint jet requires a new mask for

every product.

If you have ever seen pin stamping performed, you will understand why this is not a popular method. It's relatively cheap, and produces no waste, but the machines are noisy, dirty, and require a lot of maintenance to keep them running. The pins are made of tungsten, and indent the product material with a sharp point on the business end of the pin. However, they break often and jam the machine. They do not lend themselves to high-speed operation because of the mechanical nature of the machine. When the pins break, it means that the corresponding part of the marked character will be missing, and it may be difficult to tell if the character was supposed to be a number or letter. The mechanical impact of the pins can cause fragile components to break or fracture, and so they cannot be used on delicate or sensitive parts, so these items require a different process.

Rotary engravers suffer from some of the same problems as the pin stamping machine, although the appearance of the marked characters is different. After a number of engravings, the sharp burrs on the engraving tip are worn down and do not cut away material cleanly anymore, but rather abrade it, more like a grinder, but not as sharp.

Ultimately, the tool becomes so worn that it merely scratches at the surface rather than actually mark it. In addition to these problems, any kind of marking using the above-mentioned methods, requires the parts to be held firmly in place while marking is performed.

A laser, however, is much different. It is a non-contact engraving tool. There is no physical contact with the part being marked, and so there is nothing to wear out or get bent or broken. With nothing to wear out, the last engraved part is as good as the first. There are no waste products to clean up afterward, and parts being marked do not require physical clamping to a reference surface as in the other methods.

## Laser marked samples


You may be asking yourself how a laser can be made to mark (or etch, actually) various materials. You may have already seen examples of laser etching, but not realized it. A number of IC chip manufacturers use laser marking systems to engrave part numbers and date codes on their products. Soda bottling plants use a laser marker to etch date codes and bar codes on the side of those 2-liter plastic bottles that are so numerous these days. Motor vehicle manufacturers use laser engraving systems to remove opaque material from the back side of illuminated controls in your car, to let light come through from behind and show up so well in the dark.

Almost all of the marking methods mentioned above require the object to be marked to be held stationary while the mark is made. Mechanical impact from the pin stamping machines in particular, require the part to be held rigidly. This is okay as long as production volumes are low, and conveyor lines can be stopped and started while the clamping mechanism operates.

High-volume industries that have to mark or otherwise identify parts in large numbers cannot allow production lines to have a bottleneck situation over such a simple task as applying a mark.


Technology has come a long way since the first laser markers were built, and now it is possible to mark part numbers and bar codes on items that are moving at quite a high speed past a laser on a conveyor belt (known collectively as marking on-the-fly). For serializing parts, an incremental counter is used not only to count the parts going by, but also for incrementing the marker, so that consecutive parts get different serial numbers.

If there's one thing a laser is

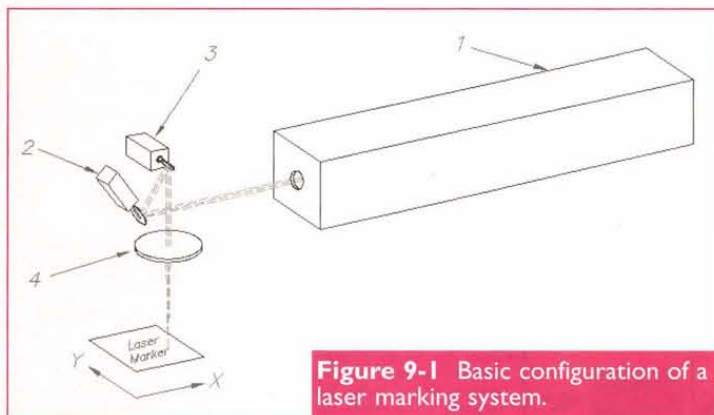

**Figure 9-1** Basic configuration of a laser marking system.

**Figure 9-2** This illustration shows the curved focal plane produced by a simple lens.

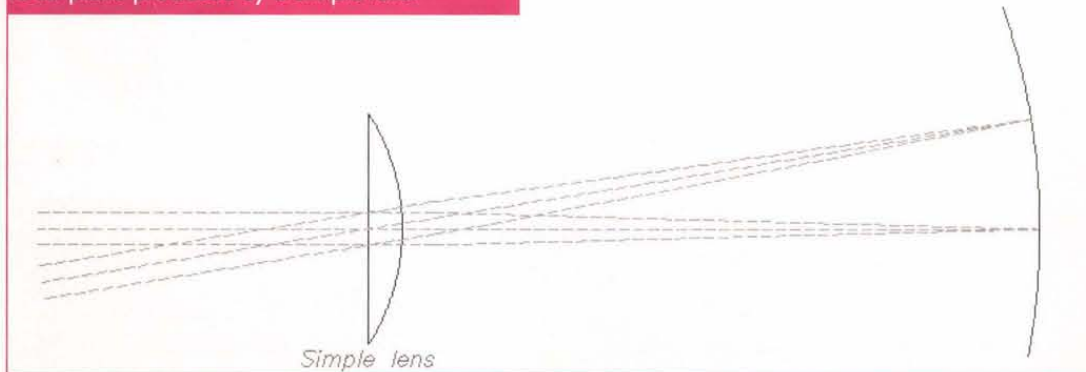

good at, it is its ability to be moved between two points very quickly, and this is where the laser marker excels. In my business, we have a laser marking system for product date code and part number identification prior to products being packed for shipment. It can engrave about 200 alphanumeric characters per second!

But it can do so much more than that. It can be programmed to produce line drawings, graphics, and company logos on chromium steel that are fascinating to watch.

Character size and font are changeable on just about all commercially available systems. Our machine can mark alphanumeric characters down to about 0.5mm in height, and still are readable without a magnifying glass (with normal eyesight, anyway).

Some machines — ours included — can also reproduce photographs on metal in grayscale. This fact can be applied to the security industry, which is a hot item these days, for making ID badges. A photograph of a security officer etched into a metal badge using a laser is unique and impossible to fake without the proper equipment.


### So, how does it work?

Figure 9-1 shows the essential parts that make up a basic laser marking system. In a laser marker system, the laser beam is usually (not always) set up for low order mode operation. What this means is that we need the energy profile of the beam to exhibit a near-Gaussian energy distribution. I covered this topic some time ago, so I won't dwell on it here. In any event, the laser beam that is focused onto the work piece will produce the smallest spot and consequently, the finest detail, if the beam is purely Gaussian. There are other things that contribute to the smallest focused spot size, and regular readers will surely be able to think of one or two more.


In Figure 9-1, when the beam leaves the laser head (1), it first impinges on the center of a small mirror mounted on a galvanometer (galvo) shaft (2). A galvanometer is a special kind of motor that has a limited amount of motion, and I briefly covered this in the article describing the light show (*Nuts & Volts*, Sept. 01).

When the galvo is energized, it causes the galvo mirror to twist in one direction. A signal voltage in the opposite sense would cause the galvo to twist in the opposite direction. In the drawing, this mirror would cause a laser beam deflection in a direction perpendicular to the laser head (Y-axis).


Those readers who built the light show project a couple of months ago are probably ahead of me already. The laser beam reflecting from this first mirror falls onto the center of a second galvo mirror (3) mounted at right angles to the first. The beam impinging on this mirror is further deflected by move-

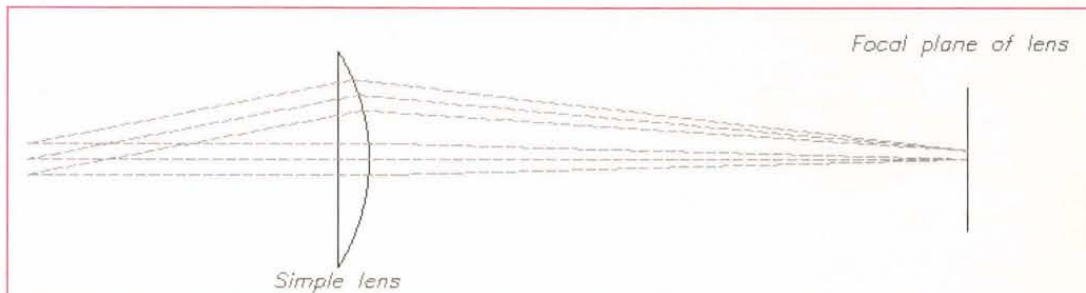

**Figure 9-3** This illustrates how a simple lens tries to restore an off-axis laser beam to the same focal point.

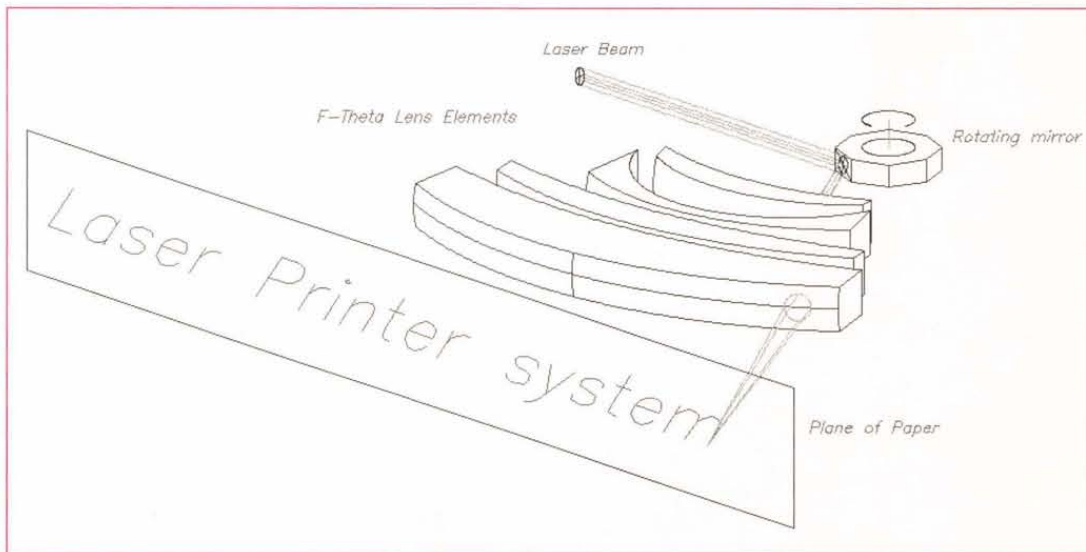

**Figure 9-4** Basic optical configuration of an F-Theta (Flat Field) lens as found in a laser printer.

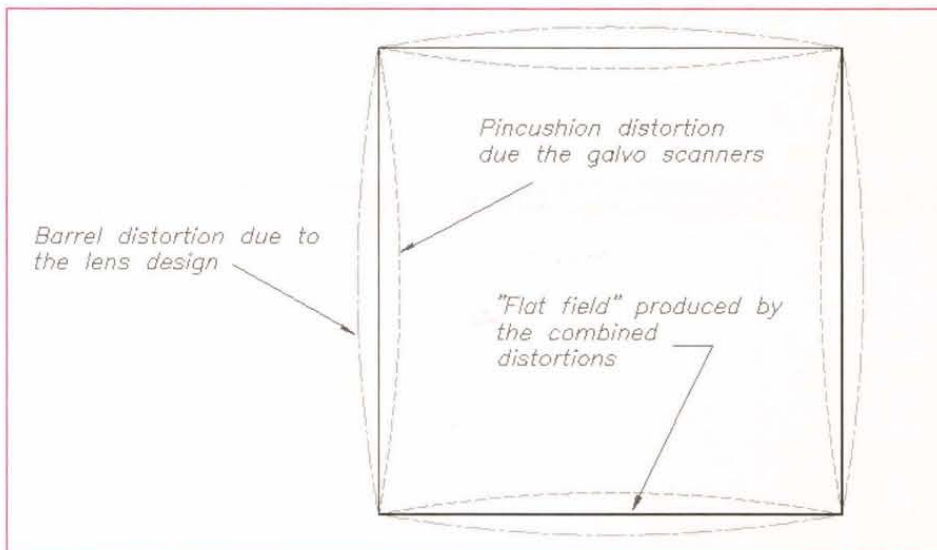

**Figure 9-5** Pincushion distortion and barrel distortion combine to form a flat field.

ment on this galvo (X-axis), so now the beam has two components of deflection that can work either together or independently.


With the proper signals, then, it would be possible to position the laser beam at any point on the focusing lens (4). Laser marking systems usually have a graphical user interface (GUI) with a computer, to allow marking information to be entered and stored. The computer then puts out two channels of DC control voltage for directly controlling the position of the galvo

mirrors.


If the lens depicted in Figure 9-1 was a regular plano-convex lens, there would be two problem situations to consider.

(1) Light rays passing through the center of the lens at an angle would tend to produce a focal 'plane' that was in fact curved, as indicated in Figure 9-2. This lens, and this method of controlling and focusing the beam would not work on a flat object because of the change in focal plane relative to the marked surface.


(2) As the laser beam moved across the lens away from the optical axis, the focusing characteristics of the lens would try to bring the focused spot back to the focal point of the lens, as indicated in Figure 9-3. In the case of light rays parallel to the optical axis, all rays would converge to the focal point of the lens. However, because the beam enters the lens at an angle rather than parallel with the optical axis, there would be a shifting of the focal point. This lens would not work for marking anything larger than a pin head.

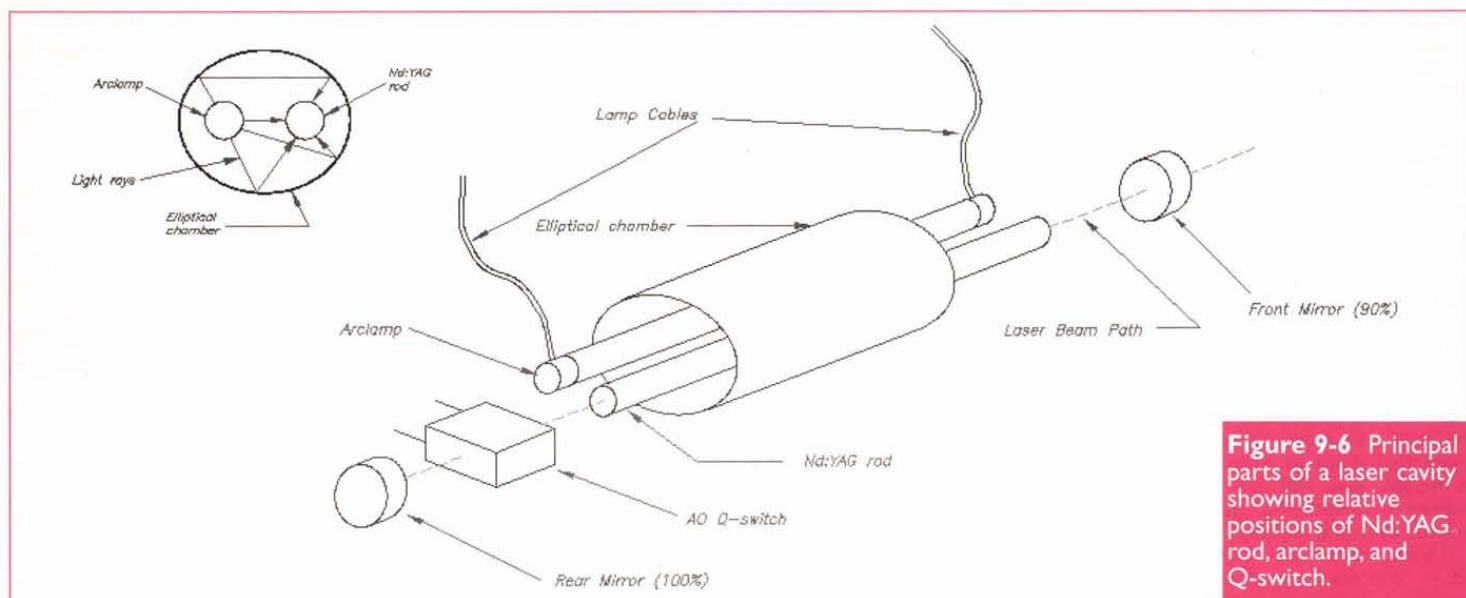

**Figure 9-6** Principal parts of a laser cavity showing relative positions of Nd:YAG rod, arc lamp, and Q-switch.

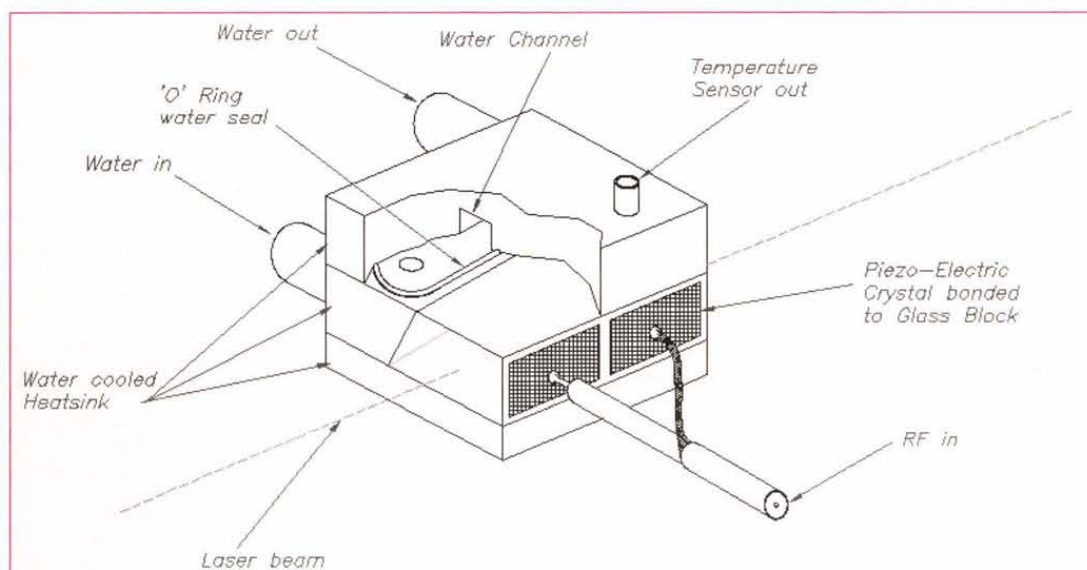

**Figure 9-7** This drawing shows the general form of an AO Q-switch.

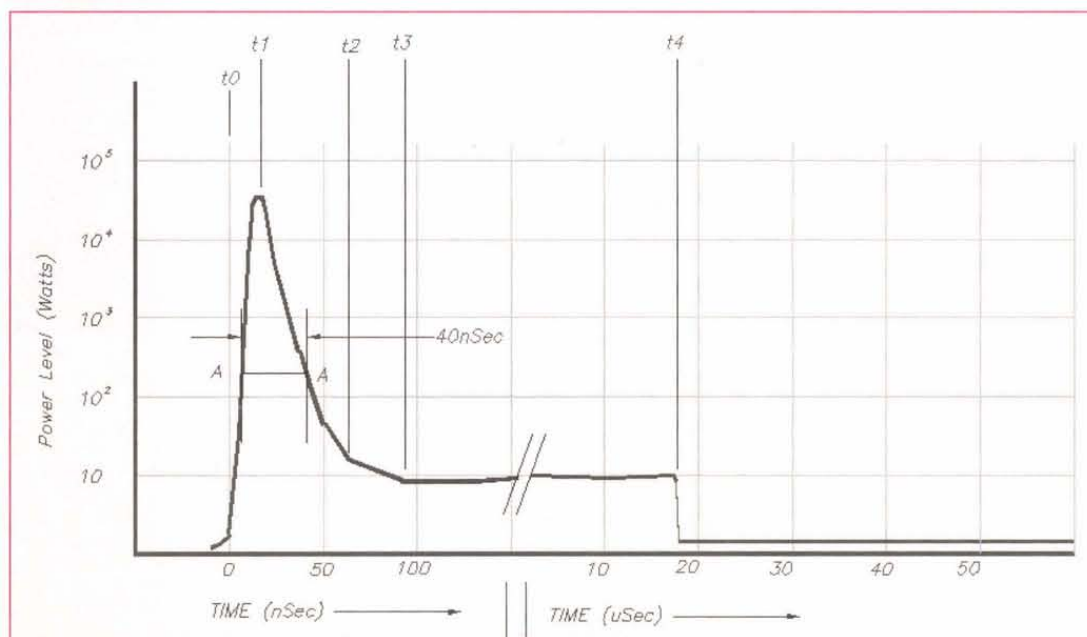

**Figure 9-8** This plot shows the relationship between the Q-switched pulse and the steady-state (CW) power levels.

Neither of these situations is good because in the first case, we want to be able to mark flat surfaces without changing the focal point of the lens. In the second case, it would be nice if we could mark an area larger than a pin head!

In order to overcome these drawbacks, we use a lens system rather than a simple lens.

This lens system has a special name, and you'll come across it if you have to work with laser printers, copiers, and other devices. It is called a flat-field lens or an f-theta lens.

You'll see what these terms mean soon. If you are lucky enough to come across a discarded laser printer, open it up and examine the optical system. You will find a series of lenses in a similar arrangement to that shown in Figure 9-4. This is the general arrangement of a typical f-theta lens as it applies to a laser printer. It may not be exactly the same as shown, and it may not be to scale, but it will be close.

As you can see, it's really quite complex, and yes, it's very expensive. The reason the focusing lens is made like this is to allow the laser focus to stay on a straight line while the rotating scanner moves the beam in an arc across the page. Using this lens, the laser beam can be swept across the width of the page, yet the beam will always be focused on the page. In a laser printer, the final lens is about the same width as the page itself, while in a laser marker, the marking field is generally larger than the lens.

Image field distortion introduced by the galvo mirrors is somewhat compensated for by the lens system described here. When the mirror system scans the laser beam, there is some inherent distortion (pincushion distortion) in the focal plane. The lens system is usually designed to compensate for this distortion by designing in barrel distortion to the lens, thereby opposing the pincushion and producing a flat field at the focal plane.

(Figure 9-5).

But it will only work correctly if the mirror/lens distances, and scanning angles are correct and satisfy the f-theta condition designed into the lens system. As the name suggests, the f-theta condition depends on the lens aperture (f), and the scanning angle of the galvo mirrors (theta).

If the unmodulated laser beam were scanned through the flatfield lens as described, it probably would not be very impressive. It most likely wouldn't mark very well either. The reason for this is really just one thing: there is not enough energy for surface reaction.

Laser markers mark best and clearest when run in a low-order mode condition. This gives us the finest focused spot. Remember what happens when we reduce the higher order TEM modes in a laser? I covered this in an earlier article.

Well, the answer is we lose some laser energy. By restricting the operating modes, and allowing only the low-order modes to resonate, we reduce the laser power to a fraction of the full power available. In the system we have at my office, the laser produces about 80W when run at full power. In a marking mode though, the output power is reduced to about 10-15W through the use of spatial filters.

This is not a real Gaussian mode, but is close enough for most purposes.

This small amount of power will not mark anything in a CW mode of operation, so it's time to introduce another concept: Q-switching.

### The AO Q-switch

Q-switching as it applies to a laser system is a very old technique, in fact acousto-optic experiments were first carried out in the 1920s, before the laser was even dreamed of! There are many forms of Q-switching, some using active components (as in the laser marker), some using passive components (I'll be covering some of these other techniques in a later column).

The most common type of active Q-switch (sometimes called a 'Q' spoiler) used in laser markers is the acousto-optic (AO) Q-switch. Those of you familiar with the term Q, know that essentially it means 'goodness,' as in the 'Q' of a resonant circuit, for instance.

Q factor tells you how good a resonant circuit is at rejecting unwanted frequencies while amplifying or passing those frequencies closest to its resonant frequency.

In a laser system, the 'Q' of the resonant cavity (i.e., between the

mirrors) depends on the optical gains and losses present in the cavity. In an Nd:YAG laser, the gain medium is the Nd:YAG rod that is continuously pumped to an excited state by an arclamp (diode-laser markers are beginning to appear on the market, but lamp-pumped systems are more commonplace at this time).

The Nd:YAG rod and the arclamp are fixed in an insulating block in such a manner that the axes of the two are parallel, and lie on the two focal points of an elliptical chamber (see Figure 9-6). All the light emitted by the arclamp is thus focused onto the rod.

In a CW laser, there are no loss elements, and so the laser energy is emitted as a continuous beam of infrared light. Remember, the light from an Nd:YAG laser lies in the near infrared band of the electromagnetic spectrum. The most common wavelength for this type of laser is 1,064nm, and is invisible to the human eye.

In a Q-switched laser system, a Q spoiler is introduced between one of the resonator mirrors (usually the 100% rear reflector) and the gain medium (the Nd:YAG rod). The Q spoiler is usually in the form of a quartz glass block, cut at a particular angle, and has a piezoelectric crystal bonded on one side (Figure 9-7). The glass is com-

pletely transparent to the laser beam when inactive. The assembly is housed with a water-cooled heatsink to keep a stable temperature, and is normally mounted on an adjustable base. It is an active device, and being so, is driven by an RF oscillator/amplifier system. As a general rule of thumb, one watt of laser power requires about 1/2-1 watt of RF power driven into the Q-switch for complete laser beam extinction (remember, I am alternating between calling it a Q-switch and a Q spoiler, but it is the same thing).

When the RF supply is energized, an acoustic standing wave is set up in the block that changes the refractive index of the material, which acts as a diffraction grating, introducing losses to the cavity, and an overall round trip gain of less than one. With insufficient gain in the resonator, the laser cannot emit any stimulated light, even if the exciting lamp is driven to maximum power.

Under normal laser conditions, the lamp excites the Nd atoms, raising the outer valence electrons into a higher than normal (metastable) state. Being unstable, they cannot stay there, and so relax back to the ground state, releasing their excess energy in the form of a photon of light. The cycle then repeats as long as the lamp



**Professional 10 HOUR RECORDER**  
"BUILT LIKE A BATTLESHIP"

- Heavy duty commercial recorder — NOT improvised from consumer models
- 12, 14, and 16 hour models also available
- BUILT-IN voice activation (add \$30)
- Applications information included
- Dimensions: 11.5 x 7.0 x 2.75"

**FREE** 48-PAGE SPECIAL EQUIPMENT CATALOG!

Factory Direct

**SPECIAL Nuts&Volts Price ..**

**\$159**

COD's OK. Sorry, no credit cards. Free catalog USA only; other countries \$5. Price Includes UPS to 48 States on Pre-Paid Orders

**Viking Systems International** 100 North Hill Drive #42, Brisbane, CA 94005  
Phone (415) 467-1220 • Fax: (415) 467-1221 • Web: [www.vikingint.com](http://www.vikingint.com)

Circle #62 on the Reader Service Card.

## Connect to the Net

Control anything over the Web!

Plug & Run Network Appliances

Relay Control

Optoisolated Control

**G2 Technology** The Next Generation in Automation

Visit us on the web at:  
[www.g2tech.biz](http://www.g2tech.biz)  
sales@g2tech.biz  
(512)-832-6651



**\$295 Special Offer**

Network Appliance with 8 Digital Outputs and Optoisolated Connector Board

Circle #66 on the Reader Service Card.

# LASERS & ACCESSORIES

**HELIUM NEON LASERS**

- ✓ Complete Systems
- ✓ Plasma Tubes
- ✓ Power Supplies

**ACCESSORIES**

- ✓ Optics
- ✓ Electro-Optics
- ✓ IR Viewers
- ✓ Books & More



**MEREDITH INSTRUMENTS**

**DIODE LASERS**

- ✓ Visible / IR
- ✓ Complete Modules
- ✓ Collimating Optics
- ✓ Drive Circuits


**WEBSITE:**  
**WWW.**  
**mi-lasers.com**

**Phone: 623-934-9387 • Fax: 623-934-9482**

Circle #64 on the Reader Service Card.

[www.gatewayex.com](http://www.gatewayex.com)

(Electronically Speaking, Gateway's Got It!)



**gateway**  
ELECTRONICS, INC.

MAIL ORDERS CALL TOLL-FREE 1-800-669-5810

Circle #67 on the Reader Service Card.

**PICmicro MCU development tools**  
from microEngineering Labs, Inc.  
[www.melabs.com](http://www.melabs.com)

**LAB-X Experimenter Boards**

Assembled development platforms. Each has RS-232 serial port, in-circuit programming connector, power supply, plus other hardware.

LAB-X1 for 40-pin (shown) - \$199.95  
LAB-X2 for 28 or 40-pin MCUs - \$69.95  
LAB-X3 for 18-pin MCUs - \$119.95



**PicBasic and PicBasic Pro Compiler**

Write programs for PICmicro MCUs in BASIC. Can be used in Windows or DOS (includes Windows editor/IDE software).

PicBasic Compiler - \$99.95  
PicBasic Pro Compiler - \$249.95

**EPIC Plus PICmicro Programmer**

Programs the following PICmicro MCUs: PIC12Cxxx, 12CExxx, 14C000, 16C505, 16C55x, 6xx, 7xx, 84, 9xx, 16CE62x, 16F62x, 7x, 8x, 87x, 17C7xx, and 18Cxxx (some MCUs require adapters). Software for Windows and DOS. Requires two 9V batteries or AC adapter (not included). Adapters available for various device packages.



Bare PCB w/software - \$34.95, Assembled - \$59.95  
Assembled w/AC adapter, cable and ZIF adapter - \$99.95

**PICProto Prototyping Boards**

\$8.95 to \$19.95

High-quality blank prototyping boards for PICmicro MCUs. Holds your microcontroller, 5-volt regulator, oscillator, capacitors, DB9-25 connector.

microEngineering Labs, Inc.

Phone: (719) 520-5323

Fax: (719) 520-1867

Box 60039, Colorado Springs, CO 80960

For product information  
or to order online,

visit our website at: [www.melabs.com](http://www.melabs.com)

Circle #63 on the Reader Service Card.

can provide enough excitation.

Under these conditions, as the photons of light from this spontaneous emission travel down the length of the resonator, they encounter other unstable electrons. The impetus provided by the photon's collision with them is enough to stimulate these other electrons to relax to the ground state, so now there are two photons traveling down the resonator.

These two photons then encounter more unstable electrons stimulating them and so on. As the light bounces back and forth between the mirrors, more and more collisions of photons and electrons can take place until equilibrium is reached. Thus we get the stimulated emission referred to in the name of the laser. Remember, it is Light Amplification by Stimulated Emission of Radiation.

With the AO Q-switch energized, there can be no laser action due to the losses imposed by the Q spoiler. Because the energy cannot escape — except as spontaneous emission — there is little release in the form of stimulated emission. Because of this, there is a build up gain in the Nd:YAG rod in the form of excess atoms in an unstable state. Consequently, when the RF field in the AO Q-switch is shut down, there is a massive release of laser energy (here, we are rapidly switching the Q of the resonant cavity, not the Q of the Q spoiler — I will discuss other ways of Q switching in a later article).

The normal CW level of laser output power may be in the order of 10-15 watts, but during a Q-switched pulse, the peak power output may easily reach several hundred kilowatts! Refer to the plot in Figure 9-8. Here, a nominally 10W CW output is producing almost 40kW pulses, and this is not uncommon in low power laser marking systems. The average pulse energy delivered during this short time period (about 40nSec) is only about 1.5 mJoule. Peak power is related to energy by the simple formula  $P = E/t$ , where  $P$  = peak power,  $E$  is the pulse energy in Joules, and  $t$  is the pulse width time in seconds.

It is generally accepted in laser circles that the pulse width is equal to the full-width, half-max (FWHM) points on the pulse outline. To get the FWHM value, simply measure the height of the pulse, divide this number in half, and measure the pulse width at that height. On this plot the FWHM points are shown as A-A, and is approximately 40nSec.

Referring to Figure 9-8:

At t0, the laser is emitting no output power, and the AO Q-switch RF drive signal is triggered to shut down to allow a pulse to form.

At t1, because of the high gain of the cavity, the initial pulse energy growth is very rapid, and reaches the peak after about 10-20 nSec.

At t2, the rapid release of laser energy drops the round trip cavity gain, and almost all the built-up energy in the cavity has been depleted.

At t3, the laser cavity settles into its steady-state CW laser mode, and produces continuous CW output at the 10 watt level about 100nSec after trigger.

At t4, RF power is reapplied to the AO Q-switch, and the CW power drops to near zero output. Typically, a Q-switch trigger pulse lasts for about 10-20uSec.

The low CW power of the laser will not mark very much, but a 40kW pulse can make a fairly deep crater in a metal surface (0.0005"-0.001"). Typically, a laser marker is made to etch a series of closely-spaced craters that to an unaided eye will look like a continuous line. Under a microscope however, the individual spots where the laser blasted away surface material are easily seen.

Laser markers can produce these high intensity pulses up to about 40-50kHz. But usually the peak power intensity starts to decline above about 2-3kHz. There is usually some pulse widening at higher frequencies too, and the combined effects of high frequency, reduced pump time, and lower overall gain each contribute to the fall-off in peak power.

The wavelength absorption properties of the material surface determine how well a laser will mark, and there are various techniques in use to allow almost any surface to produce some reaction. The Nd:YAG laser described in this article is very effective on all ferrous metals, but is poor when used on gold, copper, brass, or alloys of these materials. Silver also reacts very well to the Nd:YAG wavelength.

Most plastics can be marked to some extent with this type of laser, but some steps have to be taken to ensure good results. Colored plastic works best, depending on the density of the color. Clear Plexiglas in contrast, passes Nd:YAG wavelengths easily, and does not react at all. Window glass is also transparent.

But the opposite is true for a CO<sub>2</sub> marker system. Clear Plexiglas is easily marked with a CO<sub>2</sub> laser, also window glass. No doubt you have seen samples of wood that have had laser engraving applied. Well, those samples you saw were done with a CO<sub>2</sub> laser. An Nd:Yag laser does not react well with cellulose based materials, including paper.

I hope you found this article interesting. There is so much more I could write about these fascinating machines, but my space is limited. If you have any questions regarding lasers or optical systems in general, please feel free to send me some email, or write to this fine magazine, and I'll try my best to answer all of your questions.

One final note:

I have been looking quickly at various laser websites trying to find a reasonably good demonstration of a laser marker in action to refer to those readers who have not been fortunate enough to see one working. I didn't find a good one yet, so if there are any readers out there who have seen a good demo on the WWW, please share your find with us through this column. NV

# SolderingDesoldering.Com

Your SMD Rework Specialist  
800-394-1984

## USB DAQ



**LabJack™**  
**U12**  
**\$99**

- \* 12-bit analog inputs
- \* 10-bit analog outputs
- \* 20 digital I/O
- \* 32-bit counter
- \* Watchdog function
- \* Built-in screw terminals
- \* Easy-to-use USB
- \* Everything included
- \* Use with C, VB, LabVIEW
- \* Windows 98SE/ME/2000/XP




LabJack Corporation  
[info@labjack.com](mailto:info@labjack.com)  
(303) 942-0228

[www.labjack.com](http://www.labjack.com)
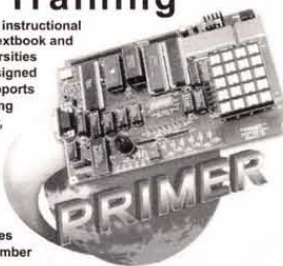
## Microprocessor Hands-On Training

The PRIMER Trainer is a flexible instructional tool featured in a Prentice Hall textbook and used by colleges and universities around the world. Ruggedly designed to resist wear, the PRIMER supports several different programming languages including Assembly, Machine Language, C, BASIC, and FORTH. A comprehensive Instruction Manual contains over 25 lessons with several examples of program design and hardware control. The Applications Manual provides theory and sample code for a number of hands-on lab projects.



### Application Projects Include:

- Scan Keypad Input & Write to a Display
- Detect Light Levels with a Photocell
- Control Motor Speed using Back EMF
- Design a Waveform Generator
- Measure Temperature
- Program EPROMs
- Bus Interface an 8255 PPI
- Construct a Capacitance Meter
- Interface and Control Stepper Motors
- Design a DTMF Autodialer / Remote Controller

The PRIMER can be purchased as an unassembled kit (\$120) or as an assembled/tested kit (\$170). Upgrades provide battery-backed RAM and PC connectivity via an RS232 serial port (shown in picture). Additional options include a heavy-duty keypad (shown in picture) and a 9V power supply — see our website. Quantity discounts are available. Satisfaction guaranteed.

Since 1985  
OVER  
**16**  
YEARS OF  
SINGLE BOARD  
SOLUTIONS

**EMAC, inc.**  
Phone 618-529-4525 Fax 618-457-0110  
2390 EMAC Way, Carbondale, Illinois 62901  
World Wide Web: <http://www.emacinc.com>

Circle #65 on the Reader Service Card.

# Triac Principles and Circuits — Part I

By Ray Marston

Ray Marston describes basic triac principles and looks at practical triac circuits in this special two-part article.

A triac is a controllable medium- to high-power semi-latching solid-state AC power switch. This two-part article explains its basic operation and shows various ways of using it. Most of the practical circuits show two sets of component values for use with normal domestic/commercial 50Hz or 60Hz AC voltage supplies with nominal values of either 240V (as used in most of Europe) or (in parenthesis) 120V (as used in most of the USA). In each design, the user must use a triac with ratings to suit his or her own particular application.

## Triac basics

A triac is a three-terminal (MT1, gate, and MT2) solid-state thyristor that uses the alternative symbols in Figure 1 and acts like a pair of SCRs wired in inverse parallel and controlled via a single gate terminal. It can conduct current in either direction between its MT1 and MT2 terminals and can thus be used to directly control AC power. It can be triggered by either positive or negative gate currents, irrespective of the polarity of the MT2 current, and it thus has four possible triggering modes or 'quadrants,' signified as follows:

- I+ Mode = MT2 current +ve, gate current +ve
- I- Mode = MT2 current +ve, gate current -ve
- III+ Mode = MT2 current -ve, gate current +ve
- III- Mode = MT2 current -ve, gate current -ve

The trigger current sensitivity is greatest when the MT2 and gate currents are both of the same polarity (either both positive or both negative), and is usually about half as great when they are of opposite polarity.

Figure 2 shows a triac used as a simple AC power switch, driving a

resistive lamp load; assume that SW2 is closed. When SW1 is open, the triac acts as an open switch and the lamp passes zero current. When SW1 is closed, the triac is gated on via R1 and self-latches shortly after the start of each half-cycle, thus switching full power to the lamp load. The triac automatically unlatches at the end of each AC half-cycle as the instantaneous supply voltage (and thus the load current) briefly falls to zero.

In Figure 2, the task of R1 is that of limiting the peak instantaneous switch-on gate current of the triac to a safe value; its resistance (combined with that of the load) must be greater than the peak supply voltage (roughly 350V in a 240V AC circuit, 175V in a 120V circuit) divided by the triac's peak gate current rating (which is usually given in the triac manufacturer's extended data sheets).


Note in Figure 2 (and in most other triac circuits shown in this mini-series) that — for safety reasons — the load is wired in series with the AC supply's neutral (N) line, and master on/off switch SW2 can isolate the entire circuit from the live (L) line.

## Triac rate effect

Most triacs, like SCRs, are susceptible to 'rate-effect' problems. Internal capacitances inevitably exist between the main terminals and gate of a triac, and if a sharply rising voltage appears on either main terminal it can — if its rate-of-rise exceeds the triac's  $dV/dt$  rating — cause enough breakthrough to the gate to trigger the triac on. This unwanted 'rate-effect' turn-on can be caused by supply line transients; the problem is, however, particularly severe when driving inductive loads such as electric motors, in which load currents and voltages are out of phase, thus making a large voltage suddenly appear on the main terminals each time the triac unlatches as its main terminal current falls to near-zero in each operating

Figure 3. Simple AC power switch with inductive load and C1-R2 snubber network to give rate-effect suppression.

Figure 1. Triac symbols.

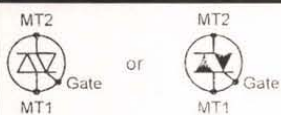

Note: MT = Main Terminal

Figure 2. Simple AC power switch with resistive (lamp) load.

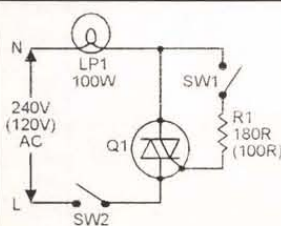


Figure 4. Basic AC lamp dimmer with RFI suppression via C1-L1.

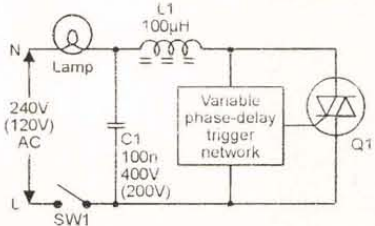


Figure 5. Diac symbol.


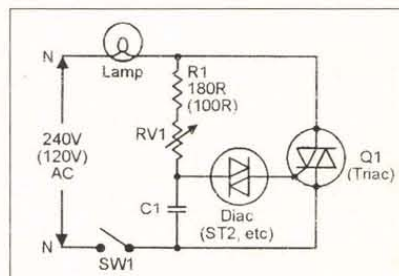
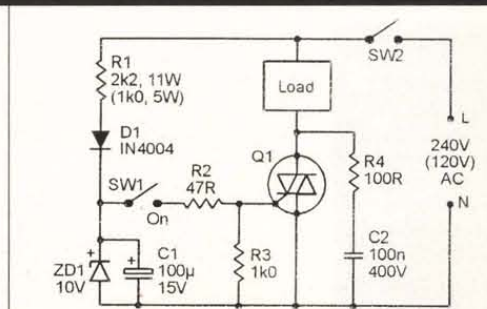


Figure 6. Basic diac-type variable phase-delay lamp dimmer circuit.

Figure 8. AC power switch with AC-derived DC triggering.

Figure 7. Quadrac symbol.

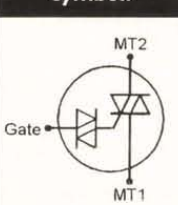

half-cycle.

Rate-effect problems can usually be overcome by wiring an R-C 'snubber' network between MT1 and MT2, to limit the voltage rate-of-rise to a safe value, as shown (for example) in the triac power switch circuit in Figure 3, where R2-C1 form the snubber network. Some modern triacs have enhanced  $dV/dt$  ratings (typically 750V/mS) and are virtually immune to rate-effect problems; these triacs are known as 'snubberless' types.

## RFI suppression

A triac can be used to give variable AC power control by using a 'phase-delayed switching' technique, in which the triac is triggered part-way through each half-cycle. Each time the triac is gated on, its load current switches sharply (in a few microseconds) from zero to a value set by its load resistance and instantaneous supply voltage values. In resistively loaded circuits such as lamp dimmers, this switching action inevitably generates a pulse of RFI, which is least when the triac is triggered close to the 0° and 180° 'zero crossing' points of the supply line waveform (at which the switch-on currents are minimal), and is greatest when the device is triggered 90° after the start of each half cycle (where the switch-on currents are at their greatest).

The RFI pulses occur at twice the supply line frequency, and can be very annoying. In lamp dimmers, RFI can usually be eliminated by fitting the dimmer with a simple L-C filter network as shown in Figure 4. The filter is fitted close to the triac, and greatly reduces the rate-of-rise of the AC power line currents.

## Diacs and quadacs

A diac is a two-terminal bidirectional trigger device; it can be used with voltages of either polarity and is usually used in conjunction with a triac; Figure 5 shows its circuit symbol. The diac's basic action is such that, when connected across a voltage source via a current-limiting load resistor, it acts like a high impedance until the applied voltage rises to about 35V, at which point it triggers and acts like a low-impedance 30V zener diode, and 30V is developed across the diac and the remaining 5V appears across the load resistor. The diac remains in this state until its forward current falls below a minimum holding value (this occurs when

the supply voltage falls below the 30V 'zener' value), at which point the diac turns off again.

The diac is most often used as a trigger device in phase-triggered triac variable power control applications, as in the basic lamp dimmer circuit of Figure 6. Here, in each power line half-cycle, the R1-RV1-C1 network applies a variable phase-delayed version of the half-cycle to the triac gate via the diac, and when the C1 voltage rises to 35V, the diac fires and delivers a 5V trigger pulse (from C1) into the triac gate, thus turning the triac on and simultaneously applying power to the lamp load and removing the drive from the R-C network. The mean power to the load (integrated over a full half-cycle period) is thus fully variable from near-zero to maximum via RV1.

In the early development days of the triac, some specialist devices were manufactured with a built-in diac in series with the triac gate; such devices were known as quadacs and used the Figure 7 circuit symbol. Quadacs were not a commercial success, and are now obsolete.

## AC power switch variations

The simplest type of triac power switch is that of Figure 2, in which the triac is gated on via R1 when SW1 is closed; only 1V or so is generated across the triac when it is on, so R1 and SW1 consume very little mean power; Figure 3 shows the same circuit fitted with a 'snubber' network. There are many useful variations of these basic circuits. Figure 8, for example, shows a version that can be triggered via an AC-derived DC supply. C1 charges (via R1-D1) to +10V on each positive AC power line half-cycle, and this charge triggers the triac when SW1 is closed. Note that R1 is subjected to almost the full AC line voltage at all times, and thus needs a fairly high power rating, and that all parts of this circuit are 'live,' making it difficult to interface to external control circuitry.

Figure 9 shows the above circuit modified to give 'isolated' interfacing to external control circuitry. SW1 is simply replaced by transistor Q2, which is driven from the phototransistor side of an optocoupler. The coupler's LED is driven via an external DC supply via R1, and the triac turns

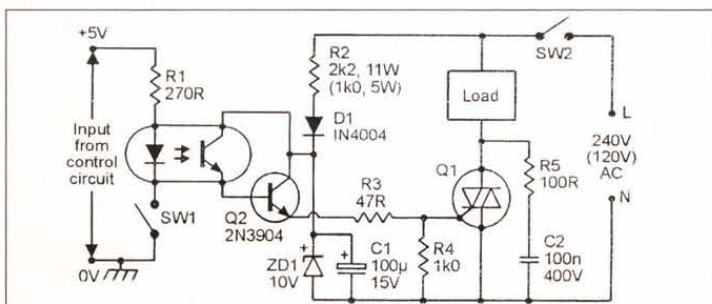


Figure 9. Isolated-input (optocoupled) AC power switch, DC triggered.

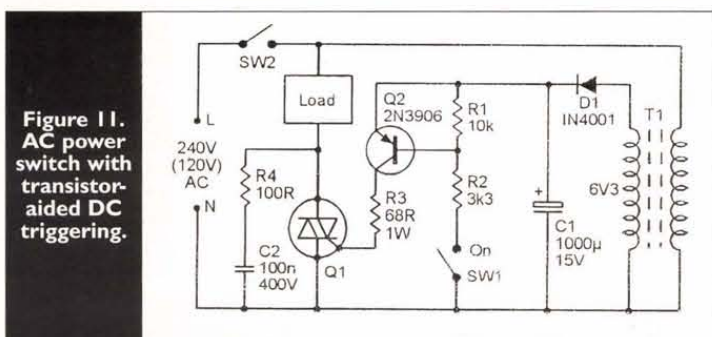


Figure 11. AC power switch with transistor-aided DC triggering.

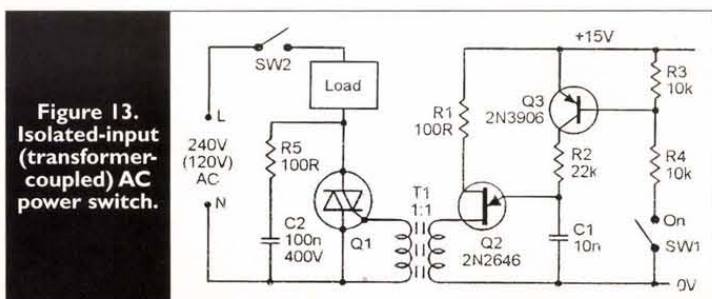


Figure 13. Isolated-input (transformer-coupled) AC power switch.

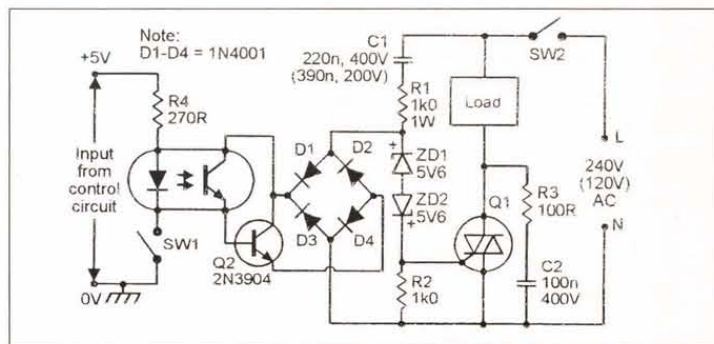


Figure 10. Isolated-input AC power switch, AC triggered.

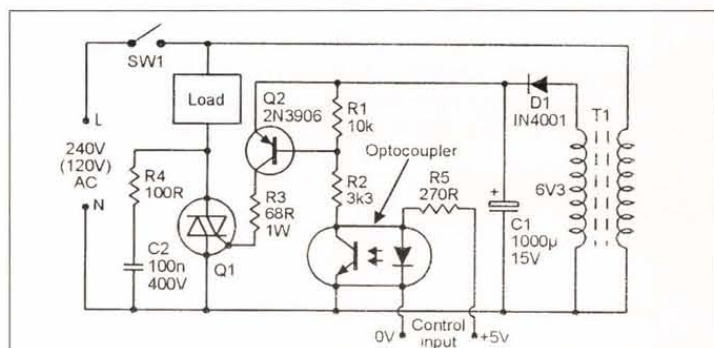


Figure 12. Isolated-input AC power switch with DC triggering.

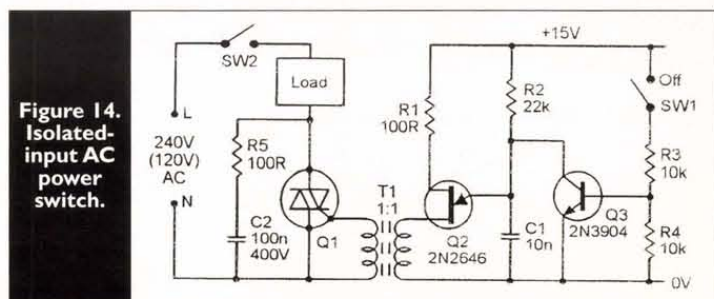


Figure 14. Isolated-input AC power switch.

on only when SW1 is closed; SW1 can be replaced by electronic switching circuitry, if desired.

Figure 10 shows a variation in which the triac is AC triggered in each half-cycle via the AC impedance of C1-R1 and via back-to-back zeners ZD1-ZD2, and C1 dissipates near-zero power. Bridge rectifier D1-D4 is wired across the ZD1-ZD2-R2 network and is loaded by Q2. When Q2 is off, the bridge is effectively open and the triac is gated on in each half-cycle, but when Q2 is on, a near-short appears across ZD1-ZD2-R2, and the triac is off. Q2 is driven via the optocoupler from the isolated external circuit, and the triac is on when SW1 is open and off when SW1 is closed.

Figures 11 and 12 show variations in which the triac is triggered via a transformer-derived DC supply and a transistor-aided switch. In Figure 11, Q2 and the triac are both driven on when SW1 is closed, and are off when SW1 is open. In practice, SW1 can be replaced by electronic circuitry, enabling the triac to be activated via heat, light, sound, time, etc. Note, however, that the whole of this circuit is 'live.' Figure 12 shows the circuit modified for optocoupler operation, enabling it to be activated via fully-isolated external circuitry.

### UJT triggering


Another way to obtain fully-isolated triac switching is via the UJT circuits in Figures 13 and 14, in which the UJT is an old 2N2646 type or a modern near-equivalent. In these circuits, the triggering action is obtained via UJT oscillator Q2, which operates at several kHz and feeds output pulses to the triac gate via pulse transformer T1, which provides the desired 'isolation.' Because of its fairly high oscillating frequency, the UJT triggers the triac within a few degrees of the start of each AC power-line half-cycle when the oscillator is active.

In Figure 13, Q3 is in series with the UJT's main timing resistor, so the UJT and triac turn on only when SW1 is closed. In Figure 14, Q3 is wired in parallel with the UJT's main timing capacitor, so the UJT and triac turn on only when SW1 is open.

### Optocoupled triacs

The gate junctions of a 'naked' triac are inherently photosensitive, and an optocoupled triac can thus be made by mounting a 'naked' triac and LED close together in a single package. Figure 15 shows the outline and lists the characteristics of a typical six-pin DIL version of such a device, in which the LED has a maximum current rating of 50mA, the triac has

Figure 15. Typical optocoupled triac outline and operating characteristics.

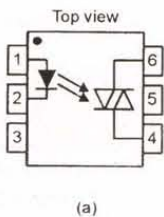

Parameter	Optocoupled triac
<b>LED characteristic</b>	
$I_F$ (max)	50mA
<b>Triac characteristic</b>	
$V_{MAX}$	400V
$I_{MAX}$ (rms)	100mA
$I_{SURGE}$ (see text)	1.2A
<b>Coupling characteristic</b>	
Isolating voltage	$\pm 1.5kV$
Input trigger current	5mA typical (20mA max)

Figure 17. High-power control via a triac slave.


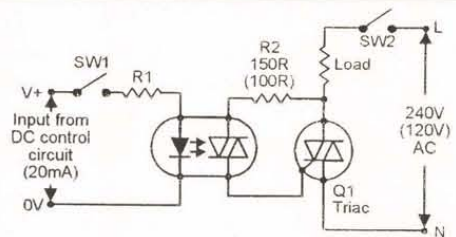


Figure 19. Synchronous zero-voltage AC power switching system.

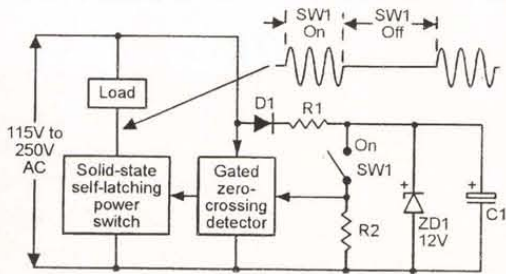

maximum ratings of 400V and 100mA RMS (and a surge current rating of 1.2A for 10ms), and the entire package has an isolating voltage rating of 1.5kV and a typical input current trigger sensitivity of 5mA.

Optocoupled triacs are easy to use and provide excellent electrical isolation between input and output. The input is used like a normal LED, and the output like a low-power triac. Figure 16 shows the device used to activate an AC line-powered filament lamp, which must have an RMS rating below 100mA and a peak inrush current rating below 1.2A.

Figure 17 shows an optocoupled triac used to activate a slave triac, thereby driving a load of any desired power rating. This circuit is suitable for use only with non-inductive loads such as lamps and heating elements. It can be modified for use with inductive loads such as electric motors by using the connections in Figure 18. Here, the R2-C1-R3 network provides a degree of phase-shift to the triac gate-drive network, to ensure correct triac triggering action, and R4-C2 form a snubber network to suppress rate effects.

### Synchronous 'zero-voltage' power switching

A synchronous 'zero-voltage' (or 'integral cycle') power switch is one in which the triac invariably turns on just after the start of each power half-cycle (i.e., near the waveform's zero-voltage point) and then turns off again automatically at the end of it, thus generating minimal RFI. In most power switching circuits shown so far in this article, the triac turns on at an arbitrary point in its initial switch-on half-cycle, thus producing a potentially high initial burst of RFI, but then gives a synchronous zero-voltage switching action on all subsequent half-cycles.

A truly synchronous zero-voltage circuit uses the switching system in

Figure 16. Low-power lamp control via an optocoupled triac.

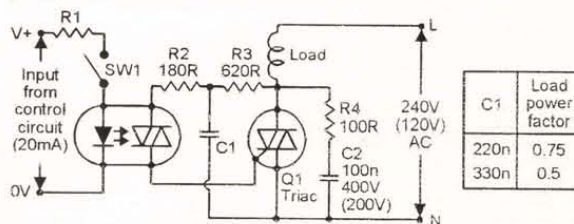
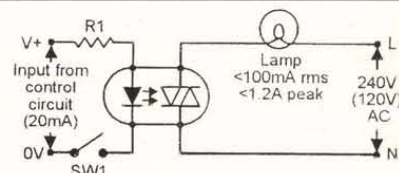


Figure 18. Driving an inductive load.

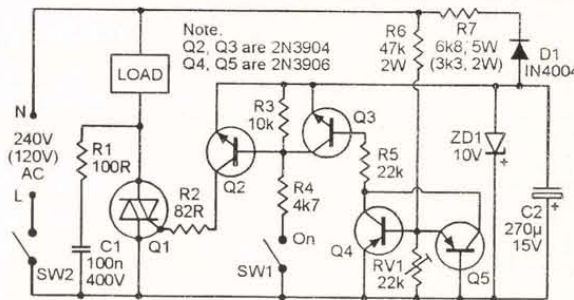


Figure 20. Synchronous AC power switch.

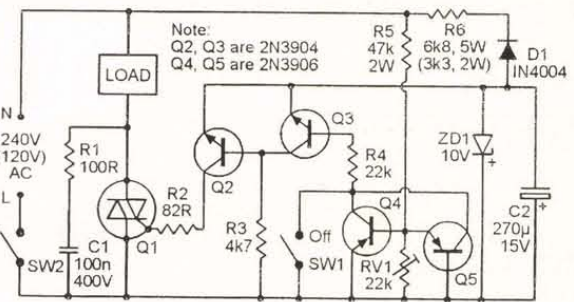


Figure 21. Alternative version of the synchronous AC power switch.

Figure 19, in which the triac can only be gated on near the start or 'zero-voltage' point of each half-cycle, and thus produces minimal RFI. This system is widely used to give on/off control of high-current loads such as electric heaters, etc.

Figure 20 shows a practical synchronous zero-voltage AC power switch; 10V DC is AC-derived via R7-D1-ZD1 and C2 and is switched to

the triac gate via Q2, which is controlled via SW1 and 'zero-voltage' detector Q3-Q4-Q5 and can supply gate current only when SW1 is closed and Q3 is off.


In the zero-voltage detector, Q4 or Q5 are driven on whenever the AC line voltage is more than a few volts (set by RV1) above or below zero, thereby driving Q3 on via R5 and inhibiting Q2. Thus, gate current can only be fed to the triac when SW1 is closed and the instantaneous AC line voltage is within a few volts of zero; this circuit thus generates minimal switching RFI.

Figure 21 shows the circuit modified so that the triac can only turn on when SW1 is open. Note in both cases that only a narrow pulse of gate current is fed to the triac, and the mean gate current is thus only 1mA or so. SW1 can be replaced by an electronic switch or optocoupler, if desired, thus enabling the load to be activated by light or temperature levels or by time, etc.

In practice, the simplest way of making a really efficient synchronous 'zero-voltage' triac-driving circuit is with the aid of a special-purpose IC that functions as an optocoupled low-power synchronous 'zero-voltage' triac that can easily be used as a slave for synchronously driving a normal high-power triac.

Next month's concluding episode will give practical details of such circuits, together with other triac-related circuits and information. **NV**

## The Pocket Programmer

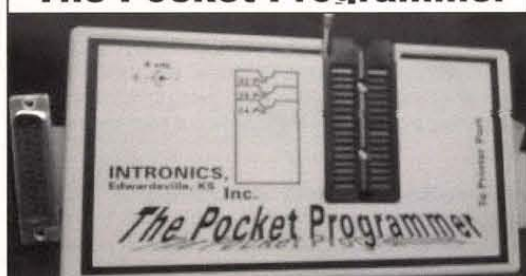

The portable programmer that uses the printer port instead of an internal card. Now with easy to use Windows software that programs E(E)prom, Flash & Dallas Ram. 25/27/28 & 29 series from 16K to 8 Megabit with a 32 pin socket. Adapters available for MCU's 874X, 875X, Pic, Atmel, 40-Pin X16, Serial Eprom's, PLCC, Bi-Prom's, Eprom Emulator to 32K X

**Only \$149.95**

Same Name, Address & Phone # for 19 Years....  
Isn't it Amazing ?

### Intronics, Inc.

Box 12723 / 612 Newton St.  
Tel. (913) 422-2094  
Fax (913) 441-1623

Add \$7.00 COD  
Add \$6.00 Shipping

**WWW.IN-KS.COM**


Visa/MC/Amex/Disc

www.nutsvolts.com
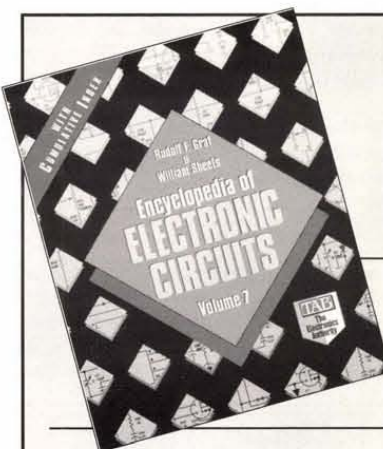
## "Encyclopedia of Electronic Circuits"

by Rudy Graff

An extensive library of 1,000 circuits from the bestselling, six-volume "Encyclopedia of Electronic Circuits."



**ONLY \$39.95!**

Available from  
the Nuts & Volts bookstore  
**www.nutsvolts.com**

## Future Horizons Advanced Technology

### Ambient Power Module

Low cost circuit provides up to 9 watts of electrical power from free-energy in the air. Can replace batteries in many devices.

#PWRM Plans- \$24.00

#PWRZ Ready to use- \$140.00

### Ion Propulsion Motor

Plans show construction of several types of ion motors. Spins by ion propulsion. Similar to NASA's ion probe spacecraft. Great for gravity research. #HIDC or #HIDZ needed to power ion motor.

#IOPM Plans- \$20.00

#IOPZ Ion Motor Ready to use- \$150.00

#HIDC 30kv power unit Plans- \$20.00

#HIDZ 30kv unit ready to use- \$250.00

#ANTI Antigravity video lecture- \$35.00

### Cordless Phone Extender

Extend your cordless phone range to 50 miles. Place calls all around town. Great alternative to cell phones.

#CPHE Plans- \$23.00

### Sonic Devestator Pistol

Creates an invisible ultrasonic force field capable of inducing intense pain and discomfort in any attacker. Effective to 20 Ft.

#SONI Plans- \$15.00

#SONZ Ready to use- \$150.00

### Traffic Light Buster

Has been known to turn traffic lights green in many cities by the touch of a button. Emergency vehicles use it to pass through traffic lights quickly. Opens security gates in gated communities too.

#TLBU Plans- \$20.00

#TLBZ Ready to use- \$250.00

Please add \$6.00 Shipping/handling

Catalogs are available for \$3.00

Po Box 125 Marquette, MI 49855  
(906) 249-5197 www.futurehorizons.net

## PRIMECELL

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT  
DON'T PITCH EM! - SEND THEM FOR REBUILDING! - SAVE \$\$

- WE INSTALL NEW NI-CAD OR NI-MH BATTERIES INTO YOUR CASE.
- WE IMPROVE PERFORMANCE TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE. / EXTEND LIFE OF OLDER EQUIPMENT
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US! EST. 1986
- WE SAVE YOU \*\*\*\* MONEY \*\*\*\* \$\$\$



WE SERVICE RECHARGEABLE BATTERY ASSEMBLIES FOR ALL TYPES OF ELECTRONICS.  
RADIO'S, SCANNERS, CORDLESS TOOLS, BAR CODE READERS, GPS, SCIENTIFIC, SURVEILLANCE

### GENERAL ELECTRIC

MPD PLS MPA 4850P \$ 34.50  
MPD PLS MPA 4860P \$ 39.50  
MPR MPS MPX 763/777 \$ 39.50  
MONOGRAM 4506P/113 \$ 37.50

MAXON SA-1155 1160 \$ 39.95

### MOTOROLA

MX300 HT600 MT1000 STX  
NTN 4555 4824 5414 \$ 37.50  
NTN 5447 5621 5645 \$ 37.50  
NLN 5960 NTN 4327 \$ 39.50

### MIDLAND

70-B10 B16 B19 B21 \$ 39.95  
B25 B26 B32 B36 B60 \$ 39.95

### UNIDEN

APX650 1050 1105 \$ 32.50  
1010 1070 1100 \$ 32.50  
1120 1200 Series \$ 32.50  
BP2500 650mAh \$ 19.50  
BP205 1600mAh \$ 22.50

### ICOM

BP2 / BP3 / BP22 \$ 19.50  
BP5 / BP23 / 24 \$ 27.50  
BP7 / CM7 / BP8 \$ 34.50  
BP157/174/180 \$ 34.50  
CM140/141/166 \$ 41.50

### YAESU

FNB 3 4 12 14 16 \$ 32.95  
FNB19 21 26 27 38 \$ 32.95  
FNB 10 1117 26 36 \$ 23.95

### RADIO SHACK

HTX 202/404 \$ 22.50  
NEW NiMH HTX pack  
8.4V 1650mAh \$ 39.50

### KENWOOD

PB2/6/3/34 \$ 28.50  
PB7/8/9/13/14/18 \$ 34.50  
KNB6/7/12/14/15 \$ 34.50  
PB10/26/28/32 \$ 24.50

### CORDESS DRILLS

50% MORE CAPACITY.  
Any brand 7.2V \$ 21.50  
Any brand 9.6V \$ 29.50  
Any brand 12.0V \$ 36.50  
Any brand 14.4V \$ 39.50  
Any brand 18.0V \$ 44.50

See our web pages about rebuilding battery packs used for Land Surveying.

## BATTERY REBUILD SERVICE

FOR INFORMATION ABOUT YOUR REQUIREMENTS ... CONTACT US:

USE THE EASY INFO. REQUEST PAGE AT <http://www.primecell.com>

PHONE OR FAX : (814) 623-7000 E-MAIL TO: [sales@primecell.com](mailto:sales@primecell.com)

SEND PACKS FOR FREE QUOTATION BY: UPS, FEDEX, OR US MAIL

CUNARD ASSOCIATES INC., 9343 US RT 220, Bedford, PA 15522



## REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Available for Canon, Epson, Hewlett Packard, Apple, Compaq, and Lexmark printers.

## HARD-TO-GET PRINTER RIBBONS



Gorilla Banana, Commodore, Texas Instruments, Centronics, Riteman, Apple, Printronix, Star

Over 300 different ribbons in stock.

All ribbons new, not re-inked.

Check our web page or write for complete price list.

## H.T. ORR Computer Supplies

249 Juanita Way, Placentia, CA 92870-2216

714-528-9822 • FAX 714-993-6216

Toll Free 1-800-377-2023

e-mail: [Htorr@aol.com](mailto:Htorr@aol.com)

<http://members.home.net/htorr/index.htm>



# TECH FORUM

## QUESTIONS

**[2021]** Does any company still support the series of mini-oscilloscopes made (15 years ago) by NonLinear Systems? I have a 30 MHz model MS-230 which appears to need a new CRT.

**Jack Meagher**  
Southern Shores, NC

This is a READER TO READER Column. All questions AND answers will be provided by Nuts & Volts readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

Send all material to *Nuts & Volts Magazine*, 430 Princland Court, Corona, CA 92879, OR fax to (909) 371-3052, OR email to [forum@nutsvolts.com](mailto:forum@nutsvolts.com)

### ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed. Be sure to include your mailing address if responding by email or we can not send payment.
- Your name, city, and state, will be printed in the magazine, unless you notify us otherwise. If you want your email address printed also, indicate to that effect.
- The question number and a short

**[2022]** I would like to build an electronic (LCD) weight scale. I would like to measure pressure caused by certain stresses anywhere from 1lb to 1000lbs. I was thinking piezo electric material for the voltage transducer and then amplified.

I took apart a cheap LCD bathroom scale to see how it works and found a small board

summary of the original question will be printed above the answer:

- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

### QUESTION INFO

#### To be considered

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

#### Information/Restrictions

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

#### Helpful Hints

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address, Phone Number, and email. Only your name, city, and state will be published with the question, but we may need to contact you.

mounted to a metal bracket that was pressed in the center by a needle directly attached to the applied weight. I don't understand how the pressure is converted to a voltage or current. The whole thing runs on a watch battery.

I appreciate any suggestions.

**Willy**  
via Internet

**[2023]** I have a Dunn MP-979 laptop, manufactured by Chicony. This system was sold under various brand names, including Chicony MP-979, Dunn MP-979, EPS MP-979, and Keydata/Keynote MP-979.

This laptop has an internal CD-ROM, but will also support an internal DVD drive in place of the CD-ROM.

I want to upgrade, but I don't know what brand or model DVD drive will fit into this system. Unfortunately, Chicony has closed down its laptop division and no longer provides any information or support.

I'd appreciate any information on what drive would fit, as well as any possible sources for the drive. Please note that I am not looking for an external DVD drive, only an internal one.

**Mike Kluger**  
Brooklyn, NY

**[2024]** Are there any die-hard Commodore 64 users out there who have used their Commodore to program the 16F84 PIC chip?

I have developed the software for the parallel programmed chips, but the serial programmed chips using the serial user port have failed.

**Richard Van Dyke**  
Charlo, MT

**[2025]** I have a Commodore MPS-803 friction feed printer. I heard that the printer can be converted to a traction feed type. Does anyone know how this can be accomplished?

**Samuel J. Ugolini**  
El Paso, TX

**[2026]** I have a US Army Signal Corp., radio receiver and transmitter set that needs batteries, to get the set in operation. The P/N for the batteries are B-A-38-"B" and B-A-37-"B" battery.

I need information on how I can get the Army manual (TM-11-235), and batteries.

**S. N. Palaski**  
Crestline, CA

## ANSWERS

### [12018 - DEC. 2001]

*I like to listen to a local AM radio station that operates on 1510 KHz.*

*The power supply of my computer puts out a signal that is about on top of the local station.*

*I would like to find or build a filter that could be attached to the power supply of my computer to eliminate this interference.*

The power supply of most computers are well shielded and enclosed in a metal case, so it is unlikely the interference is coming from the power supply.

The video display, however, is in a plastic case and the horizontal deflection is unshielded and radiating RF noise. In fact, there is a program called "Tempest\_for\_eliza," which when run will show a pattern on the screen and an AM radio placed near the computer will pick up music. If you line the video display case with aluminum foil and ground it, that should help. Be sure to punch holes in the foil where there are holes in the case for cooling.

**Russell Kincaid**  
Milford, NH

### [1021 - JAN. 2002]

*I'm trying to repair a couple of GE model 4885 clock radios with digital displays and keypad entry. The pads are defective. They use a thin foam insert under the buttons which is*

# TECH FORUM

dried up, rendering the pad useless.

*Can the pads be repaired or substituted, or is there another source for them or something similar?*

I have the GE 4880, which is nearly identical to your clock radio. Last year, mine finally succumbed to keyboard membrane rot. I removed the old membrane and used it as a template to cut a new one (a sharp hobby knife worked great). I used some closed cell shipping foam wrap. This stuff comes on a roll and is about 1/16" thick. The stuff I used was the pink anti-stat variety, but the common white type should work fine, too. I made the repair over a year ago and the keyboard still works great.

**Thomas B.  
Folsom, CA**

## [1023 - JAN. 2002]

*My 35" Zenith TV quit working. I know the tube is good and a TV shop wanted \$500.00 to replace the main board. I didn't think it was worth it so I bought a new TV.*

*I didn't want to trash the old set, and found a new main board on the internet for \$80.00.*

*I ordered and installed it, but with a very poor picture.*

*Are these new boards like the old TVs which you had to align, adjust colors, and such? I didn't see many adjustments, could it be a CMOS like the computers?*

*Should I dump it, talk to a TV shop about aligning it, or can I align it myself?*

I would dump it. The new board should have been aligned at the factory. Trying to do it your-

self, without documentation, would be an exercise in frustration. I suspect that a TV shop would charge more to align it than to replace the board.

**Russell Kincaid  
Milford, NH**

## [1022 - JAN. 2002]

*I have a Tatung autocolour TV model 1300CM. The sound is very low, even if it's on high.*

*The speaker is an eight-ohm, two-watt oval type, and tests fine outside the TV. I put it back in the set and barely a whisper. Same thing on other known working speakers.*

*The second problem is the LED which shows the channel. The leftmost digit does not show anything. So, I can go to 1 through 9 but when I go to 10, I see 0. I think the LED segment is burned out. Any fixes for this?*

In general, modern electronics are not worth fixing because parts are surface mounted and ICs are custom made and not generally available. However, this sounds like a simple problem, so if you are so inclined this is what I recommend.

Trace the speaker connections back to a component. If it is a capacitor, check to see if it is shorted or open. If it is an IC look at the identification and try to find it at [www.digikey.com](http://www.digikey.com) or [www.radioshack.com](http://www.radioshack.com).

If you can't find it, it is probably custom, but all is not lost. Some TV repair shops save defunct sets for parts, ask if they have your model and will part with it.

That also is your best bet for the LED display because it has all the digits on one board, is custom, and probably out of

## [10210 - JAN. 2002]

*I need to monitor an area with a security camera. I have the camera which is of the NTSC standard. I want to use a standard VCR and possibly a motion sensor to monitor an area. I need to know how to start the VCR without super glueing the record button. Send ideas to [junglejimie@yahoo.com](mailto:junglejimie@yahoo.com).*

**#1** I did something similar to this one time. I used a motion detector light and used the relay contacts that turn the lights on to also close a relay to start the VCR. Alternately, if it's indoors and you can use a PIR motion detector to trigger a 555 timer circuit with a relay on the output.

What I did was use a generic remote for the VCR. Since most remotes require you to hold down the record button and press the play button to start, I shorted the record button and had the relay turn on the play button. When the relay timed out, the other set of relay contacts were wired to the VCR stop button. I removed the IR LED from the remote and extended the wires so the LED was taped to the IR window of the VCR. The only problem is there is a bit of a delay to start the tape, but with

the right amount of "ON" time on the timer, you should be able to accomplish what you need to do.

**Randy Bray  
Corvallis, OR**

**#2** I too wanted to trigger a standard VCR to record when a motion detector detected movement. For a long time, I was puzzled as to how to implement my idea, until while surfing eBay one day, I came across the ideal solution. What I found was an automatic VCR controller made by Goldbeam.

First, you program it to work with your particular VCR in a manner similar to auto-search programming for a universal IR remote control. A small wired IR LED "bug" runs from the controller and is stuck to the IR receiving window of the VCR. When any of the controller's four inputs are opened, the controller sends a start-recording IR signal to the VCR. Recording continues as long as the input is open and an IR signal to stop-recording is sent 30 seconds after the input is closed.

Auctions for these controllers still show up on eBay from time to time and they usually end up selling for \$20-\$30.

**John McMichael  
Laramie, WY**

production.

**Russell Kincaid  
Milford, NH**

## [1026 - JAN. 2002]

*I have had the BASIC Stamp II and the Parallax carrier board for a few years. But now, the circuit seems dead. I have tried several things to troubleshoot, but I'm not getting anywhere.*

Things observed:

**1)** The current drain is very low - less than 1 mA.

**2)** When I either press Alt-I (show version number) or Alt-R (run program), I get the message "Error - Hardware not found."

**3)** I've checked the following with a DVM: TX: -5.0 Vdc, RX: -11.0 Vdc, ATN: -12.0 Vdc;


## Real-world connectors!

Tired of those .1 inch headers? Try our products with easy to use screw terminal block connectors.

Power supply, cable, and software included with most products - no hidden charges for "accessories"!

Stop by our web site to see our entire line of products, including the complete reference manuals.

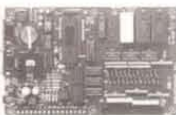
**SBC-1 \$199**  
Intel 80C51,  
EEPROM, A/D,  
RAM, RTC,  
50 digital I/O,  
industrial I/O  
connectors.



**TC51 SBC \$129**  
Atmel 89C4051, serial  
EEPROM, two 12 bit  
A/D, four digital I/O,  
high current relays,  
plus Tiny Machine Basic  
with LCD support - a  
complete control system  
for the price of an SBC.



**T51 SBC \$49**  
Atmel 89C2051,  
9 digital I/O,  
Tiny Machine  
Basic, serial  
EEPROM, plus  
T51 family  
plug-in boards.

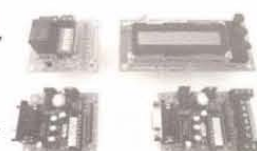

**RS51-SPR \$49**  
addressable  
and chainable  
high current  
RS-232 relay.



**IndustroLogic®**

3201 Highgate St. Charles, MO 63301 USA  
(636) 723-4000 (800) 435-1975  
[www.industrologic.com](http://www.industrologic.com)

## —AUTOTIME CORPORATION—

DON'T THROW  
AWAY THAT  
OLD LAPTOP!!

# LAPTOP RECYCLING

For Details

[www.recycleLCD.com](http://www.recycleLCD.com)

Autotime (503) 452-8577  
6605 SW Macadam, Portland, OR 97201

# TECH FORUM

[10212 - JAN. 2002]

I have a pair of US Robotics Sportster 28.8 external fax modems without power cords. I need to know what sort of power they require. There are no markings on the case that would provide any clues.

USR's website only has information on current products, mostly software.

**#1** Your US Robotics Sportster external fax/modem requires a 20V 750mA AC supply. The original supply is an Ault, Inc., T48200750A010C. You can find them at Ault at [www.aultinc.com/](http://www.aultinc.com/).

One possible replacement is the MT7114-ND from Digi-Key at [www.digikey.com](http://www.digikey.com).

**John Montalbano**  
Middletown, NJ

**#2** The US Robotics 28.8 external fax Modem uses a 9VAC, 1,000mA (one amp) wall wart. The US Robotics part number for this power supply is 1.015.1286.

You do not need to use the original manufacturer power supply; any nine-volt AC wall wart that can supply one or more amperes will work fine.

**Tim Naami**  
Poplar Grove, IL

*Editor's Note*

There were many answers submitted for this question. The consensus was about equally divided between these two answers, (20VAC and 9VAC), with no clear indication of which is correct.

TX, RX, and ATN show transient activity on the DVM (when I press ALT-I or ALT-R); PWR: +9.9 to +9.5 (tried several settings in this range); GND: 0 Vdc; RES: +5.0 Vdc; +5 Vdc: +5 Vdc.

Resistance continuity checks between the IC's pins and the serial port pins are good (TX, RX, ATN, and GND).

Your Stamp is getting power and seems to be getting signals from the PC, but less than 1mA current consumption indicates that the Stamp's oscillator is not running.

Assuming you don't have a scope, you can confirm this by carefully measuring the voltage on each end of the ceramic resonator (the light-brown component) with respect to ground. Close to zero or five volts on

either or both means that the oscillator is stopped. About 2.5 volts on both means that the oscillator is probably functioning normally, as your voltmeter sees an "average" of the 20MHz signal.

While a stopped oscillator is normal in SLEEP mode, this would not prevent programming because the pulse on the ATN line is intended to reset the Stamp, which would wake it up.

I know all this because on a dry day a few years ago, I walked across a carpet and touched a switch connected to a Stamp. I had yet to learn that "resistors are cheap insurance" as mentioned in the Jan. '02 Stamp Applications column, so static electricity fried the interpreter chip.

Assuming that the chip is, in fact dead, you can order a replacement chip from Parallax, but unless you are experienced

[1024 - JAN. 2002]

My wife uses a portable tape player to listen to books as she travels. The unit takes six C-size batteries. I would like to plug it into the car cigarette lighter, but my only problem is a regulator from 12 to 9 volts.

**#1** Although it may seem tempting to build your own 9V automotive adapter, the low cost of a store-bought solution makes such a task unnecessary. What you need is an automobile accessory DC-DC adapter, a gadget that is sold at electronic stores. RadioShack sells several and here is a sample of their offerings: #273-1805 (\$8.99), #273-1863 (\$11.99), #273-1810 (\$12.99).

**Thomas B. Folsom, CA**

**#2** You can use a National Semiconductor LM2940T-9 which is a three-terminal, one-amp voltage regulator. You will also need two capacitors: a .1µF 50V, and a 22µF 16V. All parts are available from Digi-Key ([www.digikey.com](http://www.digikey.com)).

The regulator is Digi-Key part number LM2940T-9.0-ND (\$1.71 qty. 1), the .1µF cap is part number 1109PHCT-ND (\$3.44 qty. 10), and the 22µF cap is part number P5135-ND (\$.21 qty. 1). The capacitors are not at all critical, and there are many others that will work.

The circuit is very simple — +12V (from the cigarette lighter) goes to pin 1 of the regulator,

+9V comes out of pin 3.

Both the input and the output share a common ground, which is connected to pin 2 of the regulator. The .1µF gets connected between pin 1 and ground, and the .22µF cap goes between pin 3 and ground (make sure the + side of the cap goes to pin 3).

You can get more information on National's website ([www.national.com](http://www.national.com)).

**Robert Zusman**  
Scottsdale, AZ

**#3** The LM2931CT is an adjustable voltage regulator specifically designed for the harsh automotive environment and has all the required protection features. A data sheet with all the necessary information can be downloaded from the National Semiconductor website.

You will need the IC, a fuse, two resistors, and two capacitors for approximately \$2.50. If this is too much, I'd recommend the "Far East Approach" — fuse, 1N4004, 6.8 ohm/two-watt resistor, electrolytic cap of 1,000 microfarad/16 volts to GND, bypassed by 12 x 1N4004 in series — and you've got a parallel regulator for \$0.75, providing 0.3A of current.

The disadvantage is a maximum power dissipation of about 12 watts at high voltage and no load (not much of a problem in a car, and it's flexible).

**Walter Heissenberger**  
Hancock, NH

with surface mount technology, I recommend you just bite the bullet and replace the entire Stamp.

**Tom Scarince**  
Washington, NJ

[10211 - JAN. 2002]

I need to know how to alter the number of pulses a PC sends to the stepper motors in a printer. I'm trying to convert a

## BATTERIES FOR EVERY ELECTRONIC APPLICATION

Authorized Sanyo Battery Distributor

See us at [batterystore.com](http://batterystore.com)

21 years of Battery experience

**TNR Technical, Inc.**

Sanford, FL • 800-346-0601  
Santa Ana, CA • 800-490-8418

Circle #40 on the Reader Service Card.

## ELECTRONIC MILITARY SURPLUS



## FAIR RADIO SALES

WEBSITE: [fairradio.com](http://fairradio.com)

E-MAIL: [fairradio@fairradio.com](mailto:fairradio@fairradio.com)

PHONE: 419-227-6573

FAX: 419-227-1313

1016 E. Eureka - Box 1105

Lima, OH 45802

VISA, MASTERCARD, DISCOVER

Address Dept. N/V

## 2000 WATT SOLA REGULATOR

Sola CVS 2000 Watt Constant Voltage Transformer provides a very well regulated sinusoidal waveform that is isolated from variations and disturbances in the input voltage. Also provides isolation and step-up/step-down to allow for various input/output voltages. Input 95-130/175-235/190-260/380-520 60Hz. Output 120/240VAC 60Hz. 2000VA. 17.8x11.4x9.6, 115 lbs sh. Unused, \$250 ea, 2/\$450

## WHEATSTONE BRIDGE

ZM-4 Wheatstone Bridge used to measure DC resistance. Resistance measurement range 1 ohm to 1,011 M ohms +/-0.15%. As a resistance substitution box it is adjustable in 1 ohm steps from 0-10110 ohms. The current limit of the resistors is 16-500ma depending on setting. Galvanometer indicates balance in test circuit. Requires three "D" batteries. Also 22.5 to 200 VDC for more accurate readings above 1000 ohms. 5.8x7.3x8.8, 12 lbs sh. Used Repaired, \$34.50. Used Checked, \$49.50; Manual repro, \$12.00. Allow money for shipping on merchandise.

SEND FOR OUR LATEST CATALOG !!

Circle #41 on the Reader Service Card.

Nuts & Volts Magazine/FEBRUARY 2002 35

# TECH FORUM

bubble/inkjet printer to a plotter.

Since you don't specify exactly which printer you're trying to do this with, I'm going to have to give you a generic answer — the short version which is, "you probably can't get there from here."

The PC does not directly con-

trol the printhead and paper-feed motors in the printer; rather, it sends down control codes which the printer's circuitry interprets as instructions to advance the paper by "x" number of lines or fractions of an inch, or to print dots and characters at thus-and-such a position on the line. Unfortunately, while the Epson ESC/P printer-control language

(about as close to a "standard" as you're likely to find) does define some control codes for this kind of thing, most printers — including many of Epson's own models — are incapable of moving the paper and printhead in any direction at will, and will simply ignore commands they don't physically support. Even if they do, you'll probably find that the mechanics

are not precise enough to give very good results, anyway.

If you want to give it a shot, though, the Epson ESC/P programmer's reference manual can be found at [www.ercipd.com/isv/edr\\_docs.htm](http://www.ercipd.com/isv/edr_docs.htm).

You can also find model-specific programmer's guides for many of Epson's Stylus inkjet printers there, which might help if you're trying to pull this off with an Epson printer.

**Gary Akins**  
Austin, TX

[1027 - JAN. 2002]

*My city just installed new outside readouts for our water meters. These have no face, just a small black disk. What is the technology used in these faceless readouts and would it be possible to build a reader?*

Almost every water, gas, and electric utility out there is presently at least experimenting with methods of speeding up the reading process of their meters. There are a great variety of technologies available, including electronic data port connections, "drive by" RF reading, wireless packet, cell phone, and land line phone.

It sounds from your description that they are possibly using an optical coupler that establishes a two-way serial connection by way of infrared. This optical coupler is tied to an electronic register that counts the revolutions of the water meter dial via a pickup under ground.

Building a reader brings up two problems. First, you must know the infrared wavelength, the data rate, and the data protocol. Each manufacturer devises their own protocol, and these are not open or published. Second, unauthorized data communication with electronic metering devices is considered tampering, and could lead to a misdemeanor tampering or felony theft of service charge if you happened to find a way to reset the readings in the register to some invalid value.

Some of these electronic registers have the capability of porting their data to a read-only remote display. If you have an economic reason where it would be beneficial for you to monitor your consumption as it happens, I would recommend inquiring about this to your utility.

**Phil Shewmaker**  
Louisville, KY

## RAMSEY

**GET THE NEW CATALOG TODAY!**

New Kits, New LPFM, New Cameras

[www.ramseykits.com](http://www.ramseykits.com)

### 35 WATT LPFM STEREO TRANSMITTER



- ✓ 35W RF output, VSWR protected
- ✓ Automatic audio & power controls
- ✓ Digital synthesized PLL
- ✓ Full front panel control
- ✓ 110/220VAC, 12VDC operation

Whether your application is export or LPFM, the PX1 has you covered. From the over-rated continuous duty power supply & power amplifier to the 2 line vacuum fluorescent display, your station will be the easiest to setup and the most reliable for continuous operation. Full microprocessor controls provide a "virtual engineer". Check out [www.highpowerfm](http://www.highpowerfm) for full details.

PX1 35W Professional FM Stereo Transmitter \$1,795.95

### ELECTROCARDIOGRAM HEART MONITOR



- ✓ Visible and audible display of your heart rhythm
  - ✓ Re-usable sensors included; just like visiting the hospital!
  - ✓ Bright LED "beat" indicator
  - ✓ Monitor output for oscilloscope display
- Enjoy learning about the inner workings of the heart while covering the stage by stage electronic circuit theory of ECG/EKG systems. Be heart smart and learn at the same time!

ECG1 Electrocardiogram Heart Monitor Kit \$34.95  
CECG Matching Case & Knob Set \$14.95  
AC125 110 VAC Power Adapter \$9.95  
ECGP10 Replacement Reusable Probe Patches (10-Pack) \$7.95

### PLASMA GENERATOR



- ✓ Generate 2" sparks to a hand held screwdriver!
  - ✓ Build your own plasma balls!
  - ✓ 25KV at 20 KHz from a solid state source!
- Generate really impressive sparks, build your own plasma ball, light fluorescent tubes without wires! From a solid state source, generate over 25KV at 20KHz for the most dazzling displays!

PG13 Plasma Generator Kit \$59.95  
PS12 14VAC Output Power Supply \$19.95

### ION GENERATOR



- ✓ Generates negative ions with a blast of fresh air!
  - ✓ 7.5KV DC negative, 400uA - that's a lot of ions!
  - ✓ Steady state DC voltage, constant current, not pulsed!
- Learn the basics of ion repulsion by building this ion generator! Creates a continuous blast of fresh air charged with a ton of ions. Perfect for pollution and air freshening; just smell those ions! Solid state wind generation; you'll be amazed!

IG7 Ion Generator Kit \$59.95  
AC125 110 VAC Power Adapter \$9.95

### TOUCH-TONE TONE GRABBER



- ✓ New-built-in RJ11 phone jack
  - ✓ Large memory holds over 500 numbers
  - ✓ Big bold 8 digit display, auto insertion of dashes
  - ✓ New-output latch jack
- Dial phone numbers on the radio, repeated codes, control codes, anywhere touch-tones are used, you can read and store them! All new design for 2002. Capture those tones with the TG2!

TG2 Tone Grabber Tone Reader Kit \$59.95  
CTG2 Matching Case & Knob Set \$14.95  
AC125 110 VAC Power Adapter \$9.95

### RCA TO XLR AUDIO CONVERTER



- ✓ Connect consumer outputs to XLR inputs
  - ✓ Left & right audio gain adjustments
- So you're trying to connect consumer audio outputs with RCA connectors (unbalanced) to XLR (balanced) inputs. Always a problem...Not anymore with the R2XL1!

R2XL1 Unbalanced to Balanced Audio Converter Kit \$49.95  
CR2XL Matching Case & Knob Set \$14.95  
PWR25 12VAC Power Adapter \$9.95

### AUTOMATIC COLOR/BW IR CAMERA



- ✓ Color during the day, IR B&W at night!
  - ✓ Automatically turns on IR illumination!
  - ✓ Waterproof to IP57 standards!
  - ✓ Black anodized housing with universal mount
- Best of both worlds! This video camera is a waterproof COLOR camera during the day. When the light level drops, it automatically changes to B&W and turns on its built-in IR illumination, with 10 IR LEDs. Powered by 12VDC and terminated with a professional BNC connector. B&W only model also available if color is not needed. Both in heavy anodized black housing.

CCD309 Color/B&W IR Waterproof Bullet Camera \$169.95  
CCD308 B&W IR Waterproof Bullet Camera \$109.95  
AC125 110 VAC Power Adapter \$9.95

### MINI B&W CAMERA WITH IR ILLUMINATION



- ✓ Built in IR illumination!
  - ✓ Sees in total darkness!
  - ✓ Black aluminum housing with swivel bracket
- What a deal! This miniature B&W video camera has 6 high power IR LEDs built into it to provide illumination in total darkness! No need for external IR illuminators. Attractive black aluminum housing easily mounts at any angle with the built-in swivel bracket. Runs on 12VDC, and includes professional BNC output plug-in harness.

CCD303 Mini B&W IR Illuminated Camera \$59.95  
AC125 110 VAC Power Adapter \$9.95

Check out all our other new cameras at [www.ramseykits.com](http://www.ramseykits.com)!

### PROFESSIONAL FM STEREO RADIO STATION



- ✓ Synthesized 88 to 108 MHz with no drift!
- ✓ Built-in mixer - 2 line inputs and one microphone input!
- ✓ High power module available for export use
- ✓ Low pass filter for great audio response

Our FM100 is used all over the world by serious hobbyists as well as churches, drive-in theaters, and schools. Frequency synthesized PLL assures drift-free operation with simple front panel frequency selection. Built-in audio mixer features LED bargraph meters to make setting audio a breeze. The kit includes metal case, whip antenna and built-in 110 volt AC power supply.

FM100 Super-Pro FM Stereo Radio Station Kit \$249.95  
FM100WT 1 Watt, Wired Export Version \$399.95

### SYNTHESIZED FM STEREO TRANSMITTER



- ✓ All new design & features for 2002!
  - ✓ Fully adjustable RF output
- Our #1 kit for years has just gotten better for 2002! Totally redesigned, the FM25B has all the features you've asked for. From variable RF output, F connector RF output jack, line input, loop output, and more. Includes case, power supply, whip antenna, audio cables.

FM25B Synthesized FM Stereo Transmitter Kit \$129.95

### AND...OUR FAMOUS MINI-KITS



These are easy to build kits that can be used either stand-alone or as building blocks for more complex projects.

TS4 Tickle-Stick Shocker \$9.95  
BN9 Super Snoop Amplifier Kit \$8.95  
BL1 LED Blinky Kit \$3.95  
TD1 Tone Encoder/Decoder Kit \$6.95  
TT7 Touch Tone Decoder Kit \$19.95  
CP03 Code Practice Oscillator Kit \$9.95  
UT5 Universal Timer Kit \$8.95

**RAMSEY**

RAMSEY ELECTRONICS, INC.  
793 Canning Parkway  
Victor, NY 14564  
716-924-4560  
[sales@ramseykits.com](mailto:sales@ramseykits.com)



**Order Today! 800-446-2295**

[www.ramseykits.com](http://www.ramseykits.com)

# Build An Antique Robot

By Daniel Ramirez

**R**usting in some basement or in an antique store or in some toy collector's display is a treasure trove of valuable robotic and animatronic parts. These parts come from antique Erector Sets which were originally sold as mechanical construction toys as far back as the early 1900s.

The Meccano Construction Set was invented by an Englishman named Frank Hornby in 1901 and the Gilbert Erector Set was invented by an American named Alfred Carlton Gilbert, in 1912. Gilbert's contribution to mechanical construction sets was the addition of square girders and curved metal parts. (An interesting fact for readers interested in the Olympics, was the Gold Medal that A.C. Gilbert received for Pole Vaulting at the 1908 Olympic Games.)

The Erector Sets were originally sold under the brand names Gilbert and Meccano, although other brand names such as Gabriel Erector Set, Marklin Metall, Temsi, and Exacto exist. They are highly prized by collectors and sets in good or excellent condition may be worth hundreds of dollars.

My first experience with an Erector Set was when my mother bought a used set for my brothers and me. I was eight years old at the time, and have always been intrigued by building toy models. The Gilbert Erector Set came in a large, bright red metal box with a manual that showed how to make many models including simple toys such as cars and airplanes to very complicated models such as a Ferris Wheel and a fair parachute drop ride.

My father ended up building both these models since they were far too complicated for my brothers and me to build. I remember being very impressed by the magic of a large Ferris Wheel turning under power from a powerful AC geared motor, and from this experience got the idea that I would like to build such models. Of course, I never did get the chance since we moved, and to my great disappointment had to sell the set.

From my occasional visits to antique stores, I found sitting in a dusty bin, a red box with the Gilbert Erector Set label on it. Upon opening the box lid I discovered many rusty Erector Set parts including gears, pulleys, wheels, iron rods, steel girders, aluminum plates, and other assorted steel parts of many sizes as shown in Photos 1a-1e. They all had the familiar machined holes used to fasten them to other parts. The biggest surprise was that it also contained a large AC geared motor, and upon closer inspection, I found buried under all those parts a manual containing the familiar models, including the Ferris Wheel model. I then realized that this box was very similar to the one I had many years ago. I was hooked and bought the set for \$35.00. New Meccano Erector Sets may be found on the web or at TOYS "R" US. Used Gilbert and Meccano Erector Sets can be found at antique stores, flea markets, or on the web (e-Bay).



Now, every time I go to an antique store, I purposely look for those "red" boxes shown in Photo 1b. They may also come in different packaging, including a red box with a white colored top or a plastic blue box. I have even found parts in a shoebox. I have seen them go for as little as \$15.00 and as much as \$500.00. The price you pay will depend upon how complete each Erector Set is, what condition the parts are in (damp basements cause them to rust fast), and how well you can strike a bargain.


Parts from Meccano Sets and Gilbert Erector Sets can be — for the most part — used interchangeably, except for some differences due to metric sizes with the screws used on the Meccano Set. For more detailed information on these differences, read the informative "The Metal Construction Set FAQ," written by Jeff Duntemann and located on the web at [www.robotics.com/erector.txt](http://www.robotics.com/erector.txt). Sadly, Gilbert stopped making Erector Sets years ago. The only company currently making the original Erector Set is Meccano of France. Other companies such as Exacto (Argentina) also make Erector Set parts.

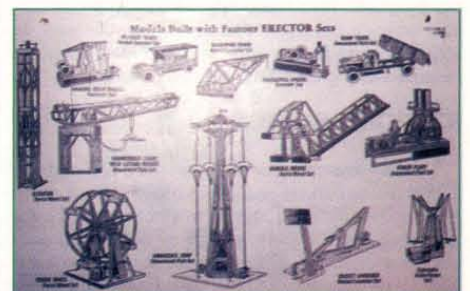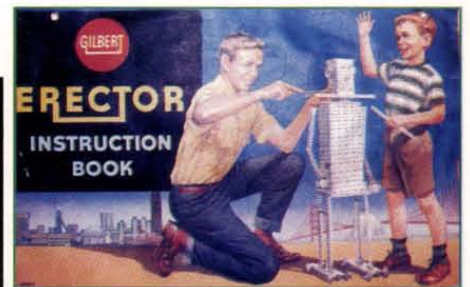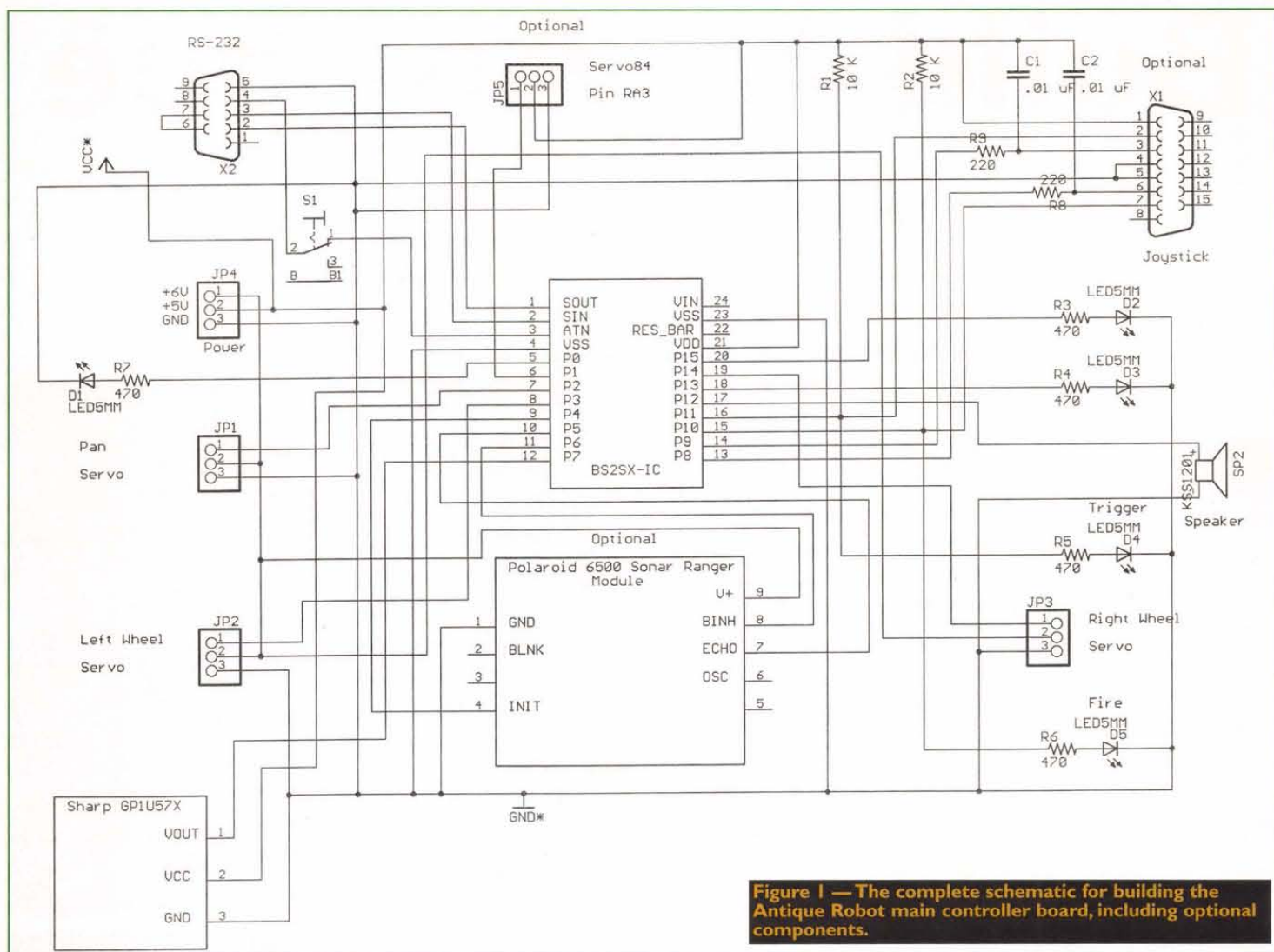Today's plastic robot construction kits do not even come close to the versatility of an Erector Set. While LEGO models are easy to build, do not rust, and are less expensive than new Meccano Erector sets, they tend to be more restrictive in the kind of robot that you can assemble due, in part, to its modular nature. They also tend to be less rugged — especially over

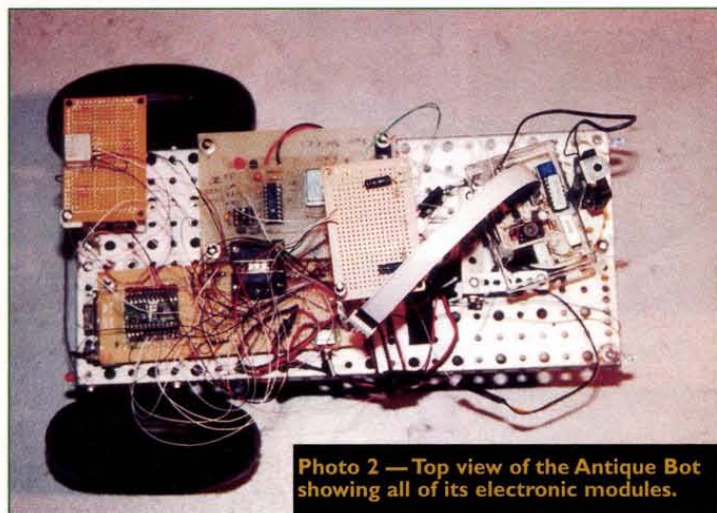


Photo 1a-e — Photos of Antique Erector Set boxes, manuals, and parts; the stuff robot dreams are made of.





**Figure 1 — The complete schematic for building the Antique Robot main controller board, including optional components.**

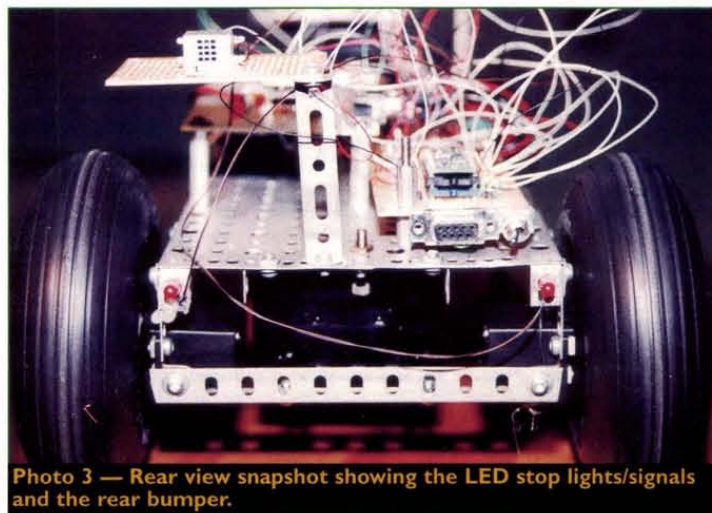


**Photo 2 — Top view of the Antique Bot showing all of its electronic modules.**

rough terrain — than those made with Erector Sets unless they are permanently glued. New materials, including those made of lightweight ABS plastic and poly-carbonates, are now available and would make great robot construction sets if they were molded into shapes similar to Meccano and were fastened using standard nuts and bolts.

## RETRO-ROBOTICS

A DIY low-cost Boe-Bot that may be used to demonstrate advanced robotic behaviors can be easily put together in a couple of evenings, using antique Erector Set parts as shown in Photos 2-4. This robot is not just a rusted toy. Serious robotic experiments may be carried out with it as I will show throughout the remainder of this article. It can roam around any room under control of a TV remote while all the time scanning for obstacles with the Polaroid 6500

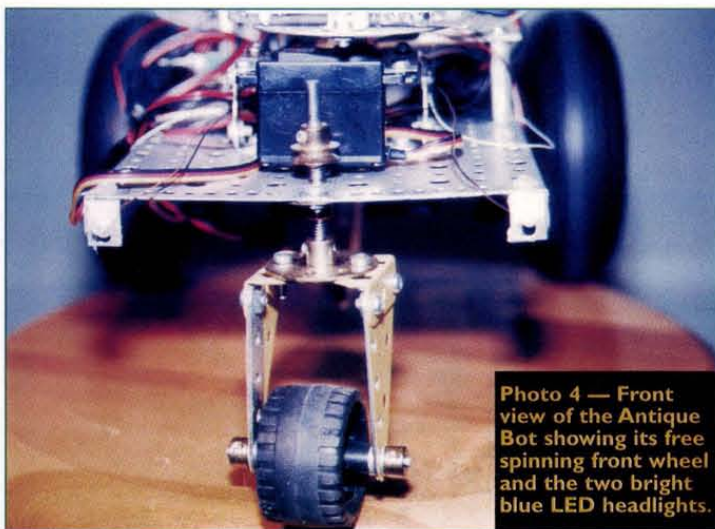


**Photo 3 — Rear view snapshot showing the LED stop lights/signals and the rear bumper.**

Sonar that is mounted on the constantly-panning sensor platform.

When an object is detected, the Antique robot takes steps to avoid it using the pre-programmed robot behaviors and generates audible beeps with a PC-mounted speaker. The three-wheeled robot uses two large model airplane tires directly connected to the wheel horns of two modified standard 44 oz-in RC servos, and a smaller, free spinning steering wheel located up front. The Antique Robot body frame is made from Erector Set girders and plates. Construction details are described below.

Some optional features including the Polaroid 6500 Sonar Ranger and the SERVO84 Controller Board, that I added to the robot to improve the robot's performance are described below. They will increase the robot's cost if implemented, but if a DIY approach is used, and freely available resources on the web are utilized, then the cost can be minimized, depending upon the construction skills and requirements of the builder. Otherwise, a low-cost,



**Photo 4 — Front view of the Antique Bot showing its free spinning front wheel and the two bright blue LED headlights.**


functional robot with minimal capabilities may be assembled using the information contained in this article. The optional sensor platform shown in Photo 5 is mounted on the front of the robot, using another unmodified standard RC servo for panning the platform 0 to 180 degrees. The sensors mounted on the platform are used for obstacle detection or target tracking. Notice how easy it is to add new sensors and hardware modules to the Antique Robot. PC boards can be mounted on the robot's frame using PC board standoffs.

It is very disconcerting to have this mechanical beast charge at you when you shine a flashlight at it, while it executes the Follow behavior, or to have the robot scurry away from you when executing the Cricket behavior.

These behaviors and others are described in great detail in the book *Mobile Robots* by Annita Flynn [1]. Another book that I recently bought titled *Robotic Explorations* from Fred G. Martin is geared towards LEGO Construction, but applicable to any other construction method, and promises to be a great reference on Robotics. It seems to have plenty of general robotic information, pictures, construction details, and algorithms including classic PD Control [2].


## ANTIQUE ROBOT'S ELECTRONICS

The main electronics consist of the Antique Robot Controller board

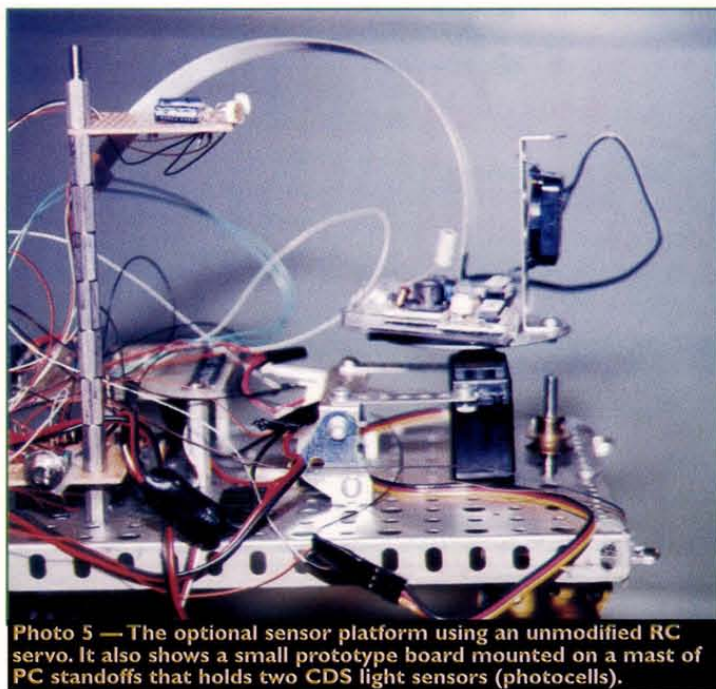


**Photo 5 — The optional sensor platform using an unmodified RC servo. It also shows a small prototype board mounted on a mast of PC standoffs that holds two CDS light sensors (photocells).**

shown in Figure 1 and Photo 2, a Polaroid 6500 Sonar Ranger Card, and a SERVO84 Controller board, also shown in Photo 2. The microcontroller is currently a Stamp BS2, but eventually I plan to upgrade it to a low-cost PIC18C452. It is responsible for sending PWM commands directly to the RC servos or sending serial commands to the SERVO84 Controller board (if used) in order to move the two main drive servos and the sensor platform servo. It is also responsible for taking readings from each of the available sensors and determining if a command has been sent via the Sony TV remote, or if there is an obstacle that needs to be avoided, which then causes the robot to change its direction or stop. As you can clearly see in the photos, I used the visually un-esthetic but very reliable wire-wrap method to build most of the robot electronics and connect the modules, although I also use stranded wire for connecting electronic components that move. This robot will certainly not win any beauty contests.

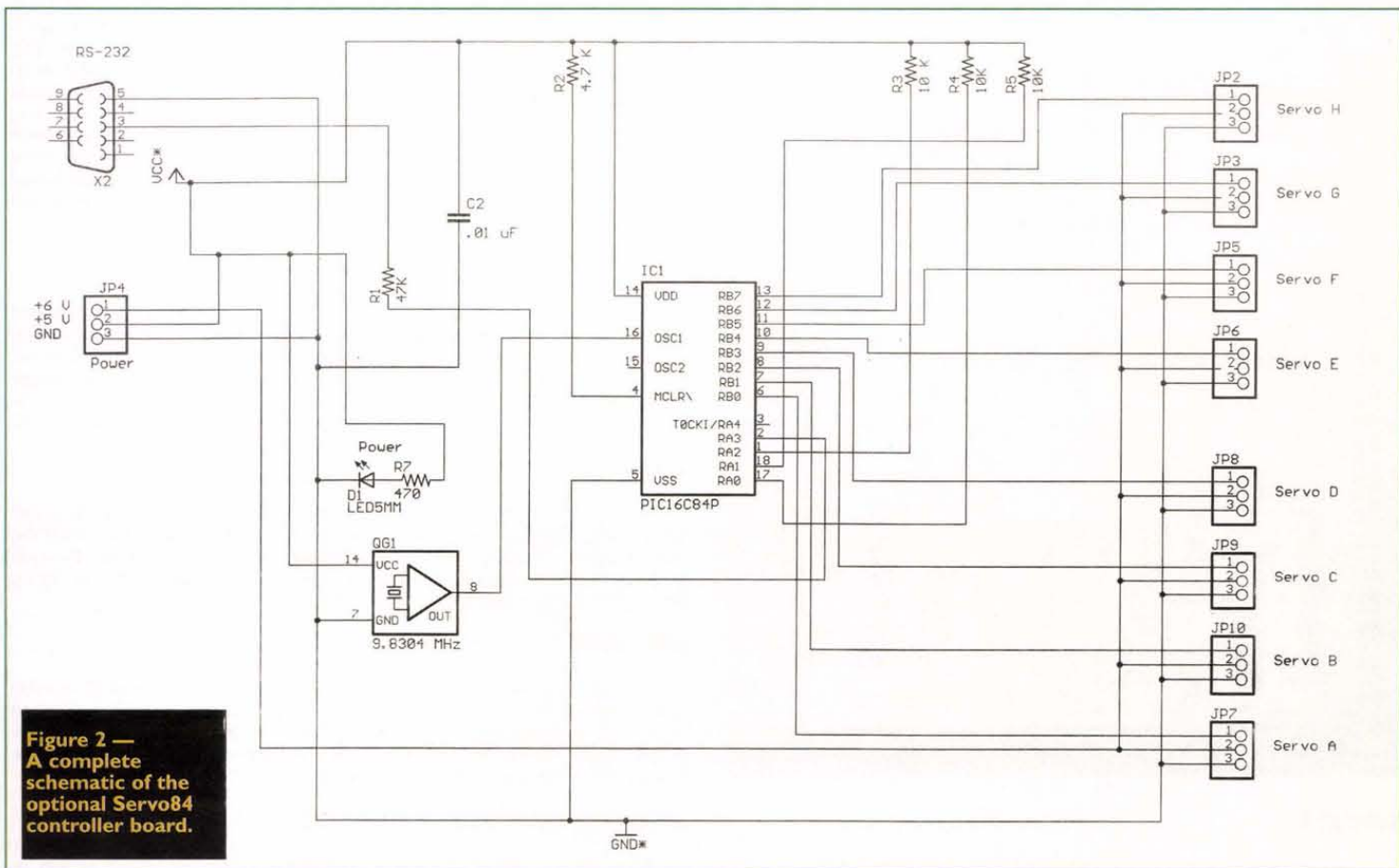


**Figure 2 — A complete schematic of the optional Servo84 controller board.**

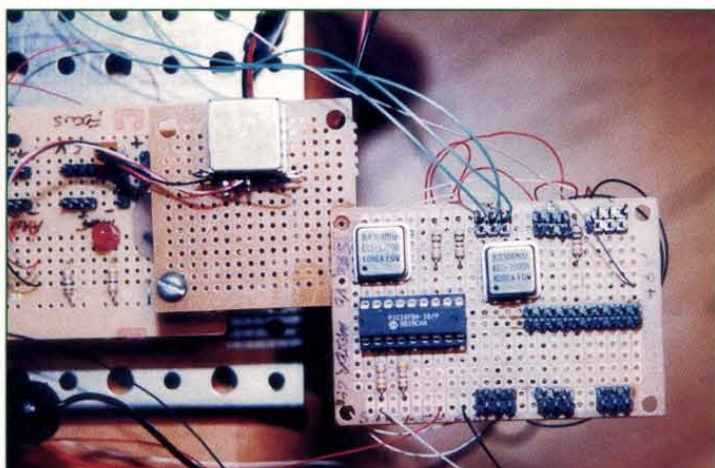


**Photo 6** — A wire-wrapped version of the PIC16C84-based SERVO84 controller board used for my tilt/pan camera platform. Ignore the second oscillator.

**Photo 7** — A surplus rechargeable lead-acid battery used to power all the electronics used in the Antique Bot including the RC servos. It also shows the battery holder made from Erector Set parts.

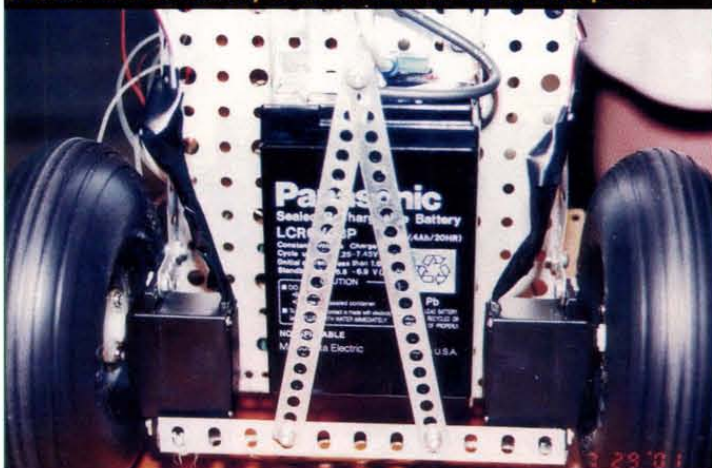

**Figure 3** — A connection diagram with the optional Polaroid 6500 sonar ranger board and the optional Servo84 controller board along with a +5 volt power supply board.

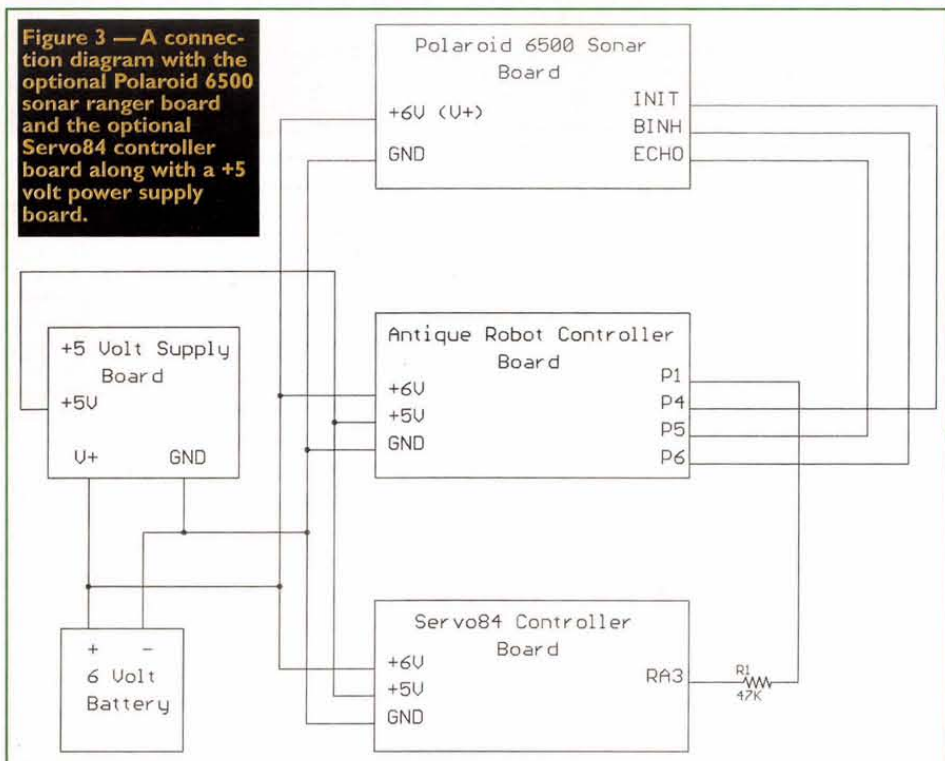

is mounted on the panning sensor platform, used to obtain distances to nearby objects by determining the time of flight (TOF). Also included is a Sharp GP2D02 IR Ranger that gathers similar information using light rather than sound. These distances are collected by the software executing on the Stamp, and are averaged and compared to thresholds in order to determine if a collision is imminent. Two Cadmium Sulfide (CDS) light sensors along with microswitches that will be mounted directly on bumpers made from Erector Set components complete the robot's sensors.

## POLAROID 6500 RANGING MODULE

The Polaroid 6500 is one of the more expensive robot components. It is available from Acroname.com, for \$45.00 and includes the Polaroid 6500 Ranging Module and the Polaroid 7000 Series Transducer. The Polaroid Sonar Ranger is very accurate and works great with a Stamp or PIC. There are less expensive DIY designs on the web and in a recent article titled "A New View" by Robert Lacoste [3]. There is also a Polaroid Sun hack that shows how to remove the Polaroid 6500 Module and the sonar transducer from old SUN cameras that can be found in antique stores or on e-Bay with prices ranging from \$10.00 to \$25.00. The SUN hack information titled "Hacking a Polaroid Sun 660" by Daniel Weatherford may be found at [www.seattlerobotics.org/encoder/200008/daniel.html](http://www.seattlerobotics.org/encoder/200008/daniel.html).

## ACTUATORS

The actuators for this robot include two modified RC servos and one unmodified RC servo (optional) for the Sensor platform. These servos may be purchased as either modified for continuous motion for \$21.00 or unmodified for \$11.00 from Acroname.com, or they may be modified by the reader using the FAQ titled "Hacking a Servo" by Kevin Ross to reduce cost. It is located on the web at [www.rdrop.com/users/marvin/explore/servhack.htm](http://www.rdrop.com/users/marvin/explore/servhack.htm).

## JOYSTICK


An optional joystick may be connected to the Antique Robot Controller Board, using Figure 1 as a guide. The joystick positions are read using the Stamp realtime command. With additional software, the joystick can be used as a teaching pendant for training the Antique Robot to move around using the trigger or fire button for Record or Play.

## SPEAKER

A built-in speaker mounted directly on the Antique Robot Controller Board generates audible beeps to indicate that an IR command was received or to warn the user of an impending collision. It may also be used for producing other interesting "sound" effects. The sounds are generated via the Stamp BS2 freqout and sound commands.

## SERVO84 CONTROLLER BOARD

The optional PIC16C84 based SERVO84 Controller board shown in

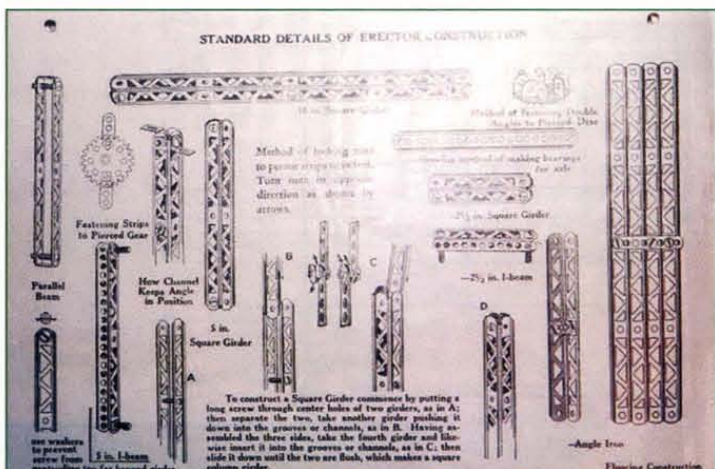

**Photo 8** — Some of the antique Gilbert Erector Set parts including the famous Square Girder.

## SENSORS

The sensor suite includes the optional Polaroid 6500 Sonar Ranger that

## INGREDIENTS NEEDED TO BUILD THE ANTIQUE ROBOT

The main ingredients used to build the Antique Robot are listed below. It is not an exact part list since it depends on various construction options used. I obtained most of my parts from Acroname, Jameco, Parallax, Digi-Key, RadioShack, surplus electronics stores, and antique stores. Both new Meccano and older Gilbert parts were used in the robot's construction. I have listed part numbers, prices, and sources for the more important Antique Robot components. Any equivalent components may be substituted. I used the following ingredients:

- 1) Old Erector Set with enough parts to build a robot. (A newer Meccano Erector Set may be used, if there are no old sets to be found), antique stores, flea markets, e-Bay, TOYS "R" US.
- 2) RadioShack prototype board, Cat. No. 276-147 for the project for \$3.99, qty. 1.
- 3) Wire-wrap sockets and pin headers are available from Digi-Key or Jameco.
- 4) Parallax Stamp BS2 or Stamp BS2, qty. 1, Parallax, Inc., [www.parallaxinc.com](http://www.parallaxinc.com).
- 5) Sony TV remote control (or compatible). You may be able to borrow and use your TV remote for this project in order to reduce cost.
- 6) Sharp GP2D02 IR Ranger, qty. 1, for \$21.00, Acroname, [www.acroname.com](http://www.acroname.com).
- 7) Sharp GP1U52X IR receiver, qty. 1, RadioShack.
- 8) RadioShack Cadmium Sulfide (CDS) light sensors, qty. 2.
- 9) 4" diameter model airplane tires, qty. 2.
- 10) 44 oz-in standard RC servo motors (modified for continuous motion), qty. 2, for \$19.00, Acroname, [www.acroname.com](http://www.acroname.com).
- 11) 44 oz-in standard RC servo motor (not modified), qty. 1, for \$10.90, Acroname, [www.acroname.com](http://www.acroname.com).
- 12) Polaroid 7000 Package (6500 Sonar Ranger, optional), qty. 1, for \$45.00, Acroname, [www.acroname.com](http://www.acroname.com).
- 13) Panasonic 6-volt, 4 AH, sealed lead-acid battery, qty. 1, Electronics Surplus and Supply (ESS), Manchester, NH (603) 624-9600.
- 14) 1.5-volt alkaline D cells, qty. 4 (optional).
- 15) Bright blue LEDs, qty. 2, RadioShack.
- 16) Bright red LEDs, qty. 2, RadioShack.
- 17) 78L05 low dropout voltage regulator, qty. 1 (Digi-Key or Jameco).
- 18) Mini SSC II board (optional), qty. 1, for \$44.00, from Scott Edwards Electronics, Inc., [www.seetron.com/ssc\\_faq.htm](http://www.seetron.com/ssc_faq.htm).
- 19) Wire-wrap wire, Electronics Surplus and Supply (ESS), Manchester NH (603) 624-9600.
- 20) Stranded wire, RadioShack.
- 21) MAX233 IC from Jameco, part #106163, for \$4.95, qty. 1.
- 22) PC mount RS-232 9-pin D shell connector (Digi-Key or Jameco).
- 23) RS-232 cable (Surplus, Jameco, or Digi-Key).
- 24) Discrete components (resistors, capacitors, diodes, and switches) from RadioShack or Digi-Key or Jameco.

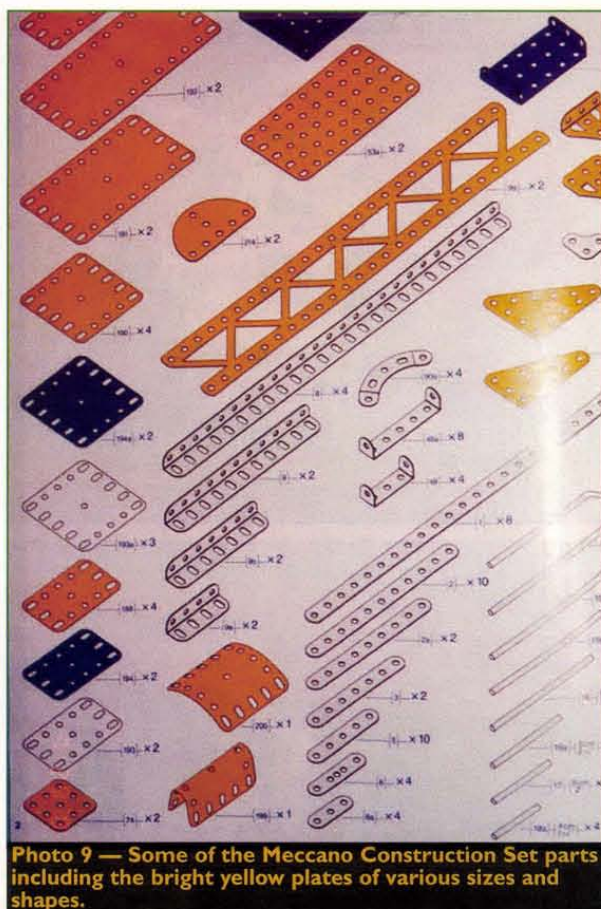


Photo 9 — Some of the Meccano Construction Set parts including the bright yellow plates of various sizes and shapes.

Figure 2 and Photo 2, is ideal for robotic and animatronic applications. It was designed for a PIC servo controller application developed by Mark Sullivan for robotics applications. Sullivan's code is highly optimized and can handle up to eight RC servos reliably. A wire-wrapped version of the board used for my Tilt/Pan Camera Platform is shown in Photo 6. I obtained Figure 2 by reverse engineering Mark's PIC 16F84 Assembly [5]. It is available freely on the web at <http://mks.niobrara.com/microtools.html>.

The SERVO84 accepts simple three byte servo position commands via the serial port from the Stamp BS2 and it maintains the proper PWM waveforms every 20 milliseconds, required to keep the RC servos positioned correctly. This board, in effect, acts as a co-processor to the Stamp to alleviate extra processing on the Stamp BS2 required to refresh each RC servo, so that the Stamp may be free to perform other more important tasks, and also increase its response to external events.

The SERVO84 Controller board is easy to make and not very expensive, if you already have the tools required, including a PIC programmer. I use the Warp13 programmer for all my embedded PIC programming tasks since it works directly with Microchip's MPLAB which is also freely available as a download from [www.microchip.com](http://www.microchip.com).

A DIY PIC 16F84 programmer that is easy to build and does not require a UV eraser is described in many FAQs and articles written by David Tait who was one of the first persons to design a cheap PIC programmer. He is responsible in part for the PIC revolution today. These articles can be found on the web at <http://members.optushome.com.au/donmck/dtait/index.html>. Another DIY PIC16F84 programmer that includes a PC board layout is described in Bob Blick's web site [www.bobblick.com/projects/PicProg/index.html](http://www.bobblick.com/projects/PicProg/index.html). Check out Bob's other great projects including his Persistence of Vision (POV) experiments, one of which is a "Propeller Clock."

There is another board available from Scott Edwards Electronics, Inc., [www.seetron.com](http://www.seetron.com) for \$44.00, that performs a similar function called a Mini SSC II Serial Servo Controller. It is a compact, well-designed surface mount board that measures 1.4" x 2.1", and is ideal for animatronics and robotics applications. In fact, there are many web-based projects including a unique wooden mirror <http://fargo.itp.tsoa.nyu.edu/~danny/mirror.html> that uses this board. A single board can handle up to eight servos, but can also be cascaded with other boards to handle up to 256 servos. If Scott Edwards's board is used, then small changes will have to be made to the Antique Robot BASIC code (check out Listing 2 available for download from *Nuts & Volts* website).

The changes to the serial I/O are only needed to conform to Scott's servo command syntax. By the way, Scott Edwards now has an updated version of his Stamp Classic *Programming and Customizing the BASIC Stamp*. I happen to own the first edition, which I still reference frequently and highly recommend [4]. It has plenty of information on controlling RC servos and building a Sonar Ranger from discrete components and was the book

Figure 4 — A complete schematic for building a low-voltage drop +5 volt power supply board. The power supply can be integrated on board with the Servo84 board, if desired.


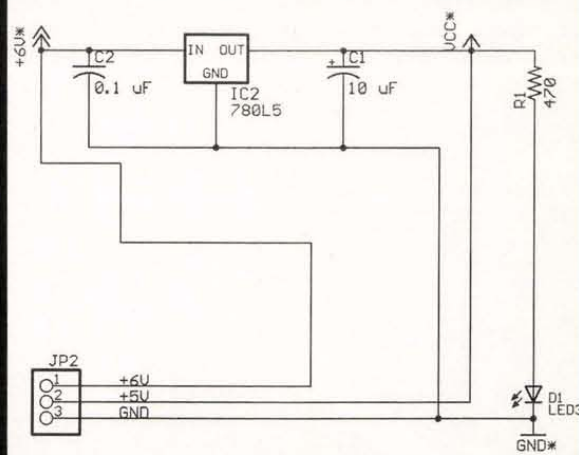


Photo 10 — A servo mount and linkage used in my tilt/pan web cam model. Notice how Erector Set parts may be conveniently attached to the RC servo horn.

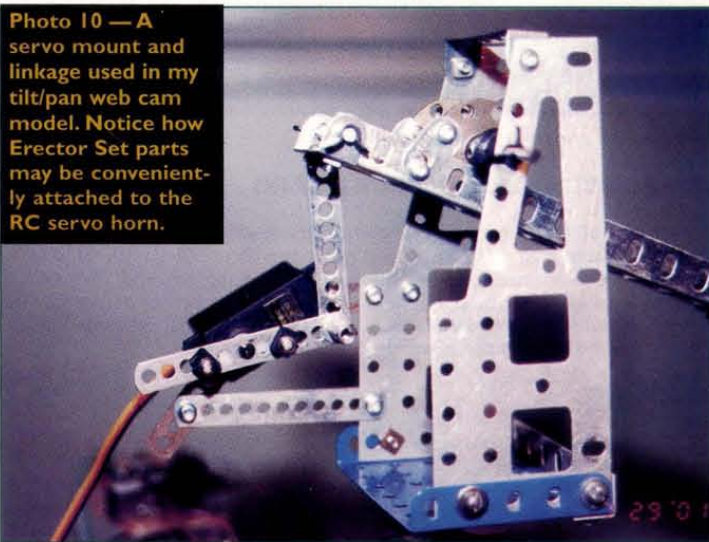


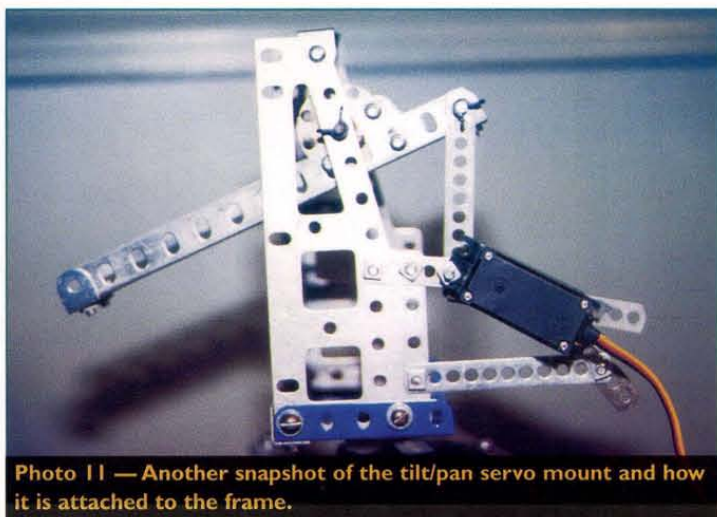




Photo 11 — Another snapshot of the tilt/pan servo mount and how it is attached to the frame.

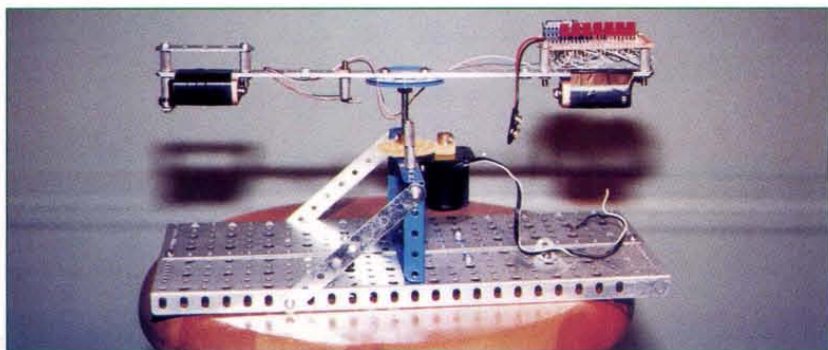

Photos 12a,b (top and bottom, respectively) — Two views of a tilt/pan/zoom web cam platform that I built.



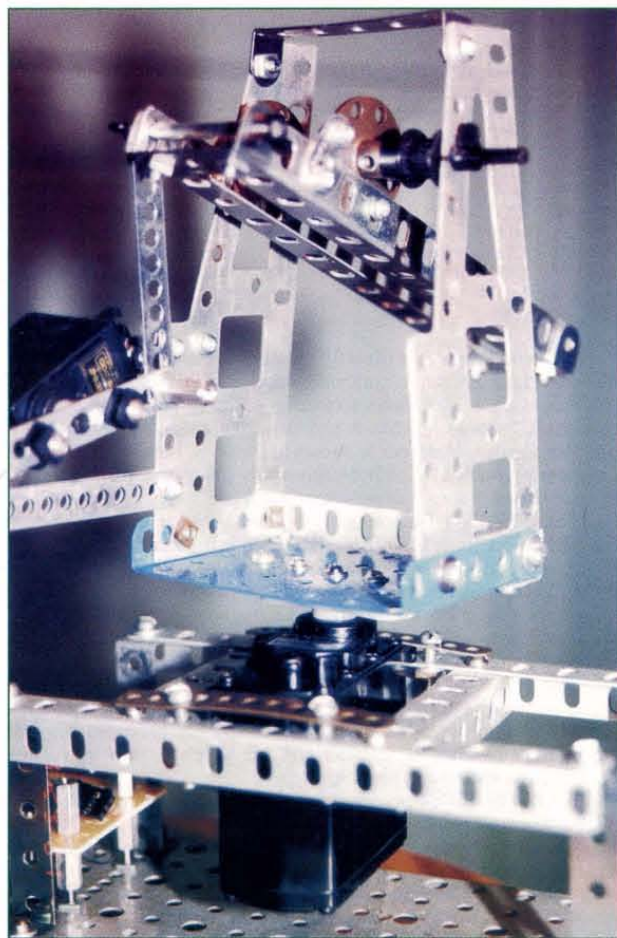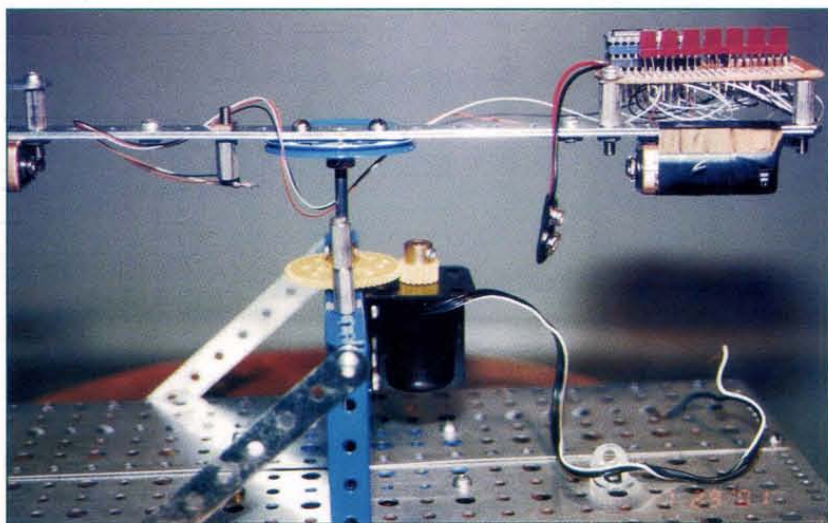Photos 13a,b (top and bottom, respectively) — Two views of a Persistence of Vision (POV) display model based on a POV project in Scott Edwards book *Programming and Customizing the BASIC Stamp* [4] that I built. Note the use of the Meccano six-volt DC motor and heavy duty plastic gears.



that got me started using the Stamp.

## IR RECEIVER ELECTRONICS BOARD

The small board mounted on a mast made from PC board standoffs is shown in Photo 5 and Figure 1, and holds the Sharp GP1U52X IR receiver used to receive commands from a Sony TV remote control and the two CDS light sensors are used for Light Look, Moth, and Cricket robot behaviors. The Stamp decodes the commands from the 40K Hz IR signal generated by the Sony TV remote using the 12-bit (SIRC) Sony IR protocol.

## LIGHTING

Glued to the front of the robot frame are two bright blue LEDs used as headlights, and glued to the rear of the robot are two bright red LEDs used for stop lights and turn signals. The LEDs are controlled by the control software currently loaded on the Stamp microcontroller. The robot looks really neat in a dark room with these LEDs lit. For a more interesting visual effect,

I intend to add bright red LEDs to the panning sensor platform. Now where did I see this panning red light before?

## THE POWER SUPPLY

Surplus rechargeable lead-acid batteries shown in Photo 7 are far better for powering robotic projects while also helping the environment by reducing the number of 9-volt and 1.5-volt D cell batteries needed for robotic applications that would end up at the dump. They usually have a very long life even after having been used for commercial emergency lighting applications.

A small Panasonic 6-volt, 4 AH rechargeable lead-acid battery mounted under the robot body conveniently powers the on-board electronics and motors, including the RC servos, the Polaroid 6500 Sonar Ranger, the Antique Robot Controller Board, and the SERVO84 Control Board (if used). I charge it using a Sears one-amp motorcycle charger. If desired, a battery pack consisting of four 1.5-volt alkaline D cells may be substituted for the 6-volt sealed lead-acid battery.

A +5 volt power supply circuit, shown in Figure 4, is required for the

optional Servo84 Controller Board. It may be located on the Servo84 Board if there is enough room or on a separate prototype board. The voltage regulator should be of the "low drop out" kind such as a 78L05, so that it can be powered from a single +6 volt battery.

## TOOLS NEEDED

In addition to the standard tools used for electronics projects, the following tools will be needed to build the Antique Bot:

- Erector Set Wrench
- Allen Wrench (for Meccano Sets)
- Electric Screw Driver (optional)
- Standard Screw Driver
- Pliers
- Wire Cutters
- File
- Wire-wrap Tool (optional) available at RadioShack, part #276-1570
- Wire-wrap Gun (optional) available at electronic surplus stores
- 1/4" Electric Drill (optional)
- Hot Glue Gun (optional)
- Dremel Tool (optional)
- Emery Cloth (optional)
- Parallax Stamp Programming Cable
- Warp13 PIC Programmer or equivalent (optional)

## CONSTRUCTION TECHNIQUES USED

To the horror of toy collectors everywhere, rusted Erector Set parts may be carefully cleaned with a Dremel Tool or fine Emery cloth, and then spray painted with aluminum enamel paint or any enamel paint of any other color, for a more durable and esthetic finish. Gilbert sets are particularly prone to rust since they were not originally painted. Holes can be easily widened to fit non-standard parts, using a power drill or a file. Of course, altering the parts devalues the set if you later plan to sell it to collectors.

In fact, new Erector Set parts can be machined from old parts by using an old part as a pattern and some scrap steel or aluminum pieces, if you happen to have an 8" drill press or machine shop available to you. Please wear goggles when using any power tools, especially the high-speed Dremel tool, and remove any remaining burrs from cut metal using a file, emery cloth, or the Dremel tool.

The robot's frame and servo mounts are all made from Erector Set girders and plates as shown in Photos 8 and 9. Any convenient design may be used for the robot's base, just be sure to leave enough room for your electronics boards, batteries, sensors, and actuators. The front wheel which works very well on smooth floors, is a free spinning wheel made from new Meccano Set parts, as seen in Photo 4. The spring is basically a shock absorber used to improve steering over rough terrain. Any convenient wheel including a swivel chair caster may be substituted.

One task that I always dreaded when working with Erector Sets was the endless cycle of loosening and tightening nuts and bolts. I found that using an electric screwdriver became an invaluable tool in fastening the Erector Set parts while also saving time. I also found an electric screw driver hex bit of similar dimensions to the Allen Wrench that is included with Meccano Sets,

## REFERENCES

### Books:

- [1] Jones, Joseph, L., *Mobile Robots — Inspiration to Implementation*, AK Peters, Limited.
- [2] Martin, Fred, G., *Robotic Explorations: A Hands-On Introduction to Engineering*, Prentice Hall, Inc., 2001.
- [3] Lacoste, Robert, "A New View," *Circuit Cellar*, Issue 132, July 2001.
- [4] Edwards, Scott, *Programming and Customizing the BASIC Stamp Computer*, McGraw-Hill.

\*(Available from the Nuts & Volts bookstore [www.nutsvolts.com](http://www.nutsvolts.com))

### Datasheets:

- [5] Microchip Technology, Inc., "PIC16F8X 8-Bit CMOS Flash/EEPROM Microcontrollers," document #DS30430B, 1996.

### Sources:

Microchip Technology, Inc., 1-800-344-4539, web site: [www.microchip.com](http://www.microchip.com)  
Parallax, Inc., 1-888-512-1024, web site: [www.parallaxinc.com](http://www.parallaxinc.com)

that works with the hex Mecanno bolts. Beware of the sudden kickback you may get if you over-tighten a screw.

Stiffness of assemblies can be increased by using multiple layers of steel girders or plates. For example, a heavy duty bumper may be assembled by layering thin girders and fastening them with long 1/2" 8-32 nuts and bolts. Sometimes layering Erector Set parts with other materials such as plywood can increase the strength and rigidity of mechanical assemblies (composites). Bumpers for the robot are assembled from layering girders together and bolting them together. Microswitches may then be attached to the bumpers for collision detection.

Servo mounts are easily adapted to the Erector Set form factor as shown in Photos 10-11. Various brackets may be put together depending upon the ingenuity of the builder. RC servo push rods, cams, and horn attachment hardware sold in hobby shops are great for making animatronic devices such as robot arms and hands, fingers, or any other device that requires linear motion.

The battery holder shown in Photo 7 is sturdy enough to hold the six-volt lead-acid battery to the bottom of the robot. A foam or cardboard box surrounded by Erector Set aluminum plates may also be used to protect the battery from harm. A similar battery holder for six D-cell batteries can also be put together. PC board standoffs fit very nicely with Erector Set parts and can be used to fasten PC boards, and other hardware to the robot.

LEDs, microswitches, and other sensors may be "hot glued" to the robot body, and later removed when re-using the Erector Set parts. Hot glue is also good for locking stubborn nuts and bolts that get loose due to vibrations.

## BUILDING THE ANTIQUE ROBOT CONTROLLER BOARD

To build the Antique Robot Controller, use the schematic shown in Figure 1. Parts placement and board fabrication techniques are not critical. Wire wrap, point-to-point, and PC board construction can all be used for this project. I chose to wire-wrap the Antique Robot Controller Board. The Antique Robot board may be built using the following procedure.

Start by soldering the pin-headers and IC sockets onto the RadioShack

<b>ECL-1200MN</b>  <b>\$67</b> 1.2 GHz MINIATURE VIDEO TRANS. 500 FT L.O.S.	<b>ECL-1200MC</b>  <b>\$98</b> HIGH POWER 1.2 GHz VIDEO TRANSMITTER 1000 FT L.O.S.	<b>ECL-372</b>  <b>\$39</b> 3.5 INCH B/W MINI DOME CAMERA 420 TVL 0.1 LUX	<b>ECL-1200MN</b>  <b>\$67</b> B/W MINI CAM WITH INFRA-RED ILLUMINATORS 0 LUX @ 10 FT	<b>ECL-377</b>  <b>\$67</b> WEATHERPROOF B/W BULLET CAM. 420 TVL 0.1 LUX	<b>ECL-380</b>  <b>\$89</b> WEATHERPROOF B/W CAM WITH INFRA-RED ILLUM. 420 TVL 0 LUX @ 10 FT
<b>ECL-2400MINI</b>  <b>\$47</b> 2.4 GHz MINI VIDEO TRANSMITTER 1 1/2 INCH LONG 500 FT L.O.S.	<b>ECL-2400VR</b>  <b>\$68</b> 2.4 GHz WIRELESS 4 CHANNEL RECEIVER AUTO SWITCHING 1.2 GHz : ECL-1200VR	<b>ECL-1202</b>  <b>\$96</b> 12 INCH B/W MONITOR 1000 TV LINES	<b>ECL-SW4</b>  <b>\$47</b> 4 CH. VIDEO SWITCHER ADJ. DWELL TIME	<b>ECL-400Q</b>  <b>\$87</b> 4 CHANNEL B/W REAL TIME QUAD WITH SWITCHER	
 <b>\$350</b> 4 CAMERA DIGITAL RECORDING AND MONITORING SYSTEM VIEW CAMERAS FROM ANY LOCATION - IP ADDRESSABLE GREAT PLAYBACK RESOLUTION		<b>SPECIAL: B/W CAMERA WITH 4MM AUTO IRIS LENS PLUS OUTDOOR HOUSING AND BRACKET: \$98</b> 			
<b>CALL NOW FOR YOUR FREE COLOR CATALOG!</b> <b>1-800-323-8746 WWW.CCTVOUTLET.COM</b>					

prototype board or PC board. Next, solder the 0.1uF bypass capacitors as close to the IC socket power pins as possible. Do not clip the leads, since they make handy wire wrap or point-to-point posts. Solder other discrete components such as resistors, capacitors, and diodes as designated in the schematic. Wire wrap labels can be purchased from Jameco to make the wire-wrapping task easier if the wire wrap method is used.

Next, wrap the power lines using red wire, and wrap the ground lines using black wire. Tie all ground wires to a single post if possible. Finally, wrap each logic signal using white, yellow, or blue colored wire, checking each one off from the diagram until all signals have been wired. Screw any PC standoffs to the prototype board and glue or solder the RS-232 connector directly to the prototype board.

At this point, it's time to check the circuit for shorts or open lines by using your digital voltmeter to check continuity on all power, ground, and logic signals. You can inspect the board using a magnifying glass.

Before populating the board with the ICs, power the board by connecting a 6-volt battery to the (+) and (-) power terminals and check to see if the power LED lights up. If it does, check for +5V at the VDD pin of each IC and V at the VSS pins. Once this has been done, you can populate the board with the ICs and fire it up for the first time. Build the +5 volt power supply circuit shown in Figure 4, if the optional Servo84 Board is going to be used. Check for +5 volts output when the 6-volt battery is connected to the input. The current is usually limited by the low voltage drop 78L05 voltage regulator to 50 or 100 mA. This is sufficient to power the PIC16F84 located on the Servo84 board. I used point-to-point techniques to build the IR receiver board using a small RadioShack prototype PC board and Figure 1 as a guide.

## BUILDING THE OPTIONAL BOARDS

A PC board was used to assemble the SERVO84 board using Figure 2. Detailed instructions for making the optional SERVO84 board are not provided due to article length limitations, although I did provide enough information to allow the reader to build one or to use a substitute Mini SSC II Serial Servo Controller. See Figure 3 for a general Antique Robot hook-up diagram.

Be sure to connect all ground and VCC lines between each module as shown in Figure 1. Make sure that the +5 volt and the +6 volt RC servo and

+6 volt Polaroid Sonar Ranger terminals are connected. Check power to any other optional modules including the +6 volts for the Polaroid 6500 Sonar Ranger Board, the +5 volts for IR receiver board, and the +5 volt and +6 volt for the SERVO84 board.

## SOFTWARE FOR THE ANTIQUE ROBOT

A complete listing of the Antique Robot Control Software that contains all the necessary Stamp BS2 code to give the robot a few simple behaviors including accepting simple commands from the user via the Sony Remote Control is shown in Listing 1, which is available for download from *Nuts & Volts'* website. The user commands that cause the robot to move are Forward, Reverse, Left, Right, Faster, Slower, and Stop. Code for other behaviors that are currently under development such as Follow and Avoid are also provided. This version of the software also takes advantage of the SERVO84 controller board. It provides added functionality and increased performance over using the Stamp to refresh the servo motor positions by eliminating the extra code needed to maintain the RC servo motor positions every 20 milliseconds. All the source code that accompanies this article, except for the SERVO84, may be found on the *Nuts & Volts* web site at [www.nutsvolts.com](http://www.nutsvolts.com).

The software required for the optional SERVO84 controller board may be found on Mark Sullivan's web site at <http://mks.niobrara.com/microtools.html> site, or if a board is purchased from Scott Edwards Electronics, Inc., the associated software and documentation may be found at his web site, [www.seetron.com](http://www.seetron.com). The Avoid behavior that I am currently developing prevents the robot from hitting obstacles in its way by comparing Sonar Ranger readings and IR Ranger readings to pre-selected thresholds. When an object is determined to be too close for comfort, the robot either stops, backs up, turns left or turns right, or combines any of these behaviors in order to avoid the object.

As I mentioned earlier, other robot behavior algorithms from previously published projects may be executed on this robot if the Stamp BS2 I/O pins are changed accordingly and any variable name conflicts are resolved. This opens up all the Parallax Boe-Bot robot software and experiments for use on the Antique Robot. Many other web sites, for example Acroname, Arrick Robotics, and Parallax, Inc., have advanced robot behavior software developed for various types of robots that may also be adapted to this robot.

## RIPPED OFF? GET EVEN WITH HIDDEN CAMERAS!

**www.cctvpros.com**

Discount Prices on Major Brand CCTV Products  
20 years of friendly, knowledgeable service!

(800) 486-2288 [info@cctvpros.com](mailto:info@cctvpros.com)

## Do You Repair Electronics?

For only \$9.95 a month, you'll receive a wealth of information:

Repair data for TV, VCR, monitor, audio, camcorder, & more.

Over 100,000 constantly updated problem/solutions plus...

- TechsChat live chat room.
- Private user discussion forums.
- Automated email list server.
- UL/FCC number lookup.
- Hot tips bulletin board.
- Manufacturer information.

To access RepairWorld, direct your internet browser to <http://www.repairworld.com>

**RepairWorld.com**

Electronix Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878

Circle #33 on the Reader Service Card.

## Catch the Bus USB or Ethernet


Full line of Test, Monitor and Control Products

- ✓ Web Module Control
- ✓ USB Module Control
- ✓ Relays
- ✓ Analog to Digital
- ✓ Opto I/O
- ✓ Quadrature Counters
- ✓ Digital I/O
- ✓ Temperature

Visit our web page for details on our complete line of products  
[www.j-works.com](http://www.j-works.com)  
[sales@j-works.com](mailto:sales@j-works.com)

**J-Works, Inc**  
12328 Gladstone St. #1  
Sylmar, CA 91342  
Voice (818) 361-0787  
Fax (818) 270-2413

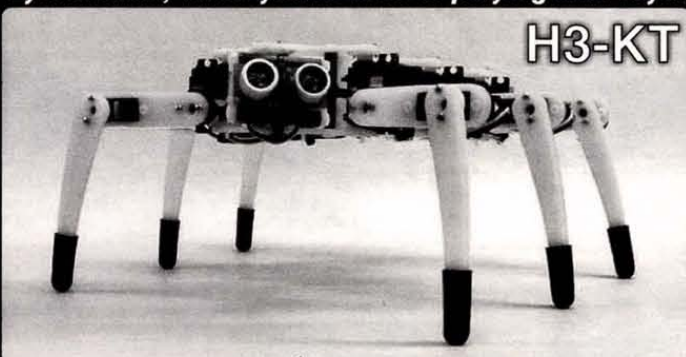**Lynxmotion, When you're tired of playing with toys!**



**H3-KT**

Lynxmotion, Inc.  
PO Box 818  
Pekin, IL 61555-0818  
[www.lynxmotion.com](http://www.lynxmotion.com)

**Lynxmotion**  
Visit our website or ask for our free catalog!

Tel: 309-382-1816  
Fax: 309-382-1254  
[sales@lynxmotion.com](mailto:sales@lynxmotion.com)  
[tech@lynxmotion.com](mailto:tech@lynxmotion.com)

Circle #35 on the Reader Service Card.

## AN ERECTOR SET FOR THE NEW MILLENNIUM

I can envision a new Erector Set geared towards robot builders as affordable, easy to use, and as versatile as the older generation Meccano and Gilbert Erector Sets. It combines the best features of Heathkit, Parallax, Meccano, and LEGO to allow robots as complicated as the Hero I or the Mars Lander or a robot hand to be assembled by the hobbyist:

- New girders, plates, and fasteners made of the latest alloys allow for light-weight, high strength and stiffness construction materials (poly-carbonate composites) space age NASA.
- Precision gears, pulleys, timing belts, chains, and cams.
- Muscle wire, memory shape metals, etc.
- Plastic coverings for models.
- Injection Molded clear domes, etc.
- The latest coreless DC motors, RC servos, and stepper motors would replace the old six-volt DC motor or the 120-volt geared AC motor.
- Electronics Modules.
- Electronic Speed Controllers (ESC) similar to those used on electric racing cars and Electric RC Planes.
- Sensor Controller Board.
- IR Remote Control.
- RF (900 MHz) transmitter/receiver communications link to PC or laptop host.
- Sensor modules similar to those provided by LEGO.
- Polaroid 6500 Sonar Ranger (or low-cost alternative).
- Sharp IR Rangers would be included in the set.

## OTHER ERECTOR SET PROJECTS

An interesting fact that I read while doing research on the web is that one of the largest Meccano models resides in Ripley's Believe It or Not in St. Augustine, FL. It is a giant model of a Ferris Wheel that was built when Meccano started selling its sets in the US. Another interesting fact is that a new theme park dedicated to A.C. Gilbert is being built in Oregon.

The web is full of other Erector Set and Meccano Models from all over the world, check out the web ring site at [www.meccanoweb.com](http://www.meccanoweb.com) for some excellent examples of models.

The following is a list of some other Erector Set projects that I have recently completed. Due to article length limitations, I can but provide a

short description of each.

Here is my list along with a photo of some of my completed projects, along with some new ideas. I leave it to the reader to take up the challenge of building the remaining models.

- 1) A tilt/pan/zoom web cam platform that I built is shown in Photos 12a,b.
- 2) A POV display based on a POV project in Scott Edwards book *Programming and Customizing the BASIC Stamp* [4] that I built is shown in Photos 13a,b.
- 3) A PUMA 6 Degrees of Freedom (DOF) robot.
- 4) A Pick and Place robot arm.
- 5) A Mars Lander Robot.
- 6) A Robotic Hand.
- 7) A Hexapod Robot.
- 8) A Walking Robot.
- 9) A Lost in Space Robot.
- 10) Kronos Robot, from the 50's Science-Fiction movie.

## BACK TO THE FUTURE

I have shown how an antique Erector Set combined with modern sensors, actuators, RC servos, and electronics makes a far better robot construction kit than many new "plastic" robot construction sets.

I also provided a design for a DIY Boe-Bot-like robot platform that may be used for education, training, and robotics experiments that costs far less than building a Boe-Bot or a Rug Warrior when using surplus electronic components and antique Erector Set parts. Much of the Stamp BS2-based robotics software available on the web or from Parallax may also be used on the Antique Bot with minor modifications to the hardware and software.

I also described other Erector Set based designs of projects that I have recently completed that demonstrate how versatile the Erector Set really is. It is a timeless invention that for over a century is still ahead of any other modern construction sets and is a great educational toy for learning mechanics and robotics.

Let's get these old Erector Sets out of the hands of toy collectors and antique dealers and into the hands of robot builders, so that they may again be used for their intended purpose. I'm sure that's a sentiment that Mr. Hornby and Mr. Gilbert (inventors of the Erector Set) would approve of. **NV**

**20 MS/s Pen-type Scope**  
US\$ 79.-

**Options**

PC Software V6.0 incl. Adapter Cable	29.90
BatteryPack (to hold 9V bloc)	16.90
AC Adapter	9.90
Rubber Protection Boot	17.90
Palm Software V2.0 incl. Adapter Cable	19.90
Active Opto-isolating RS232 Cable	39.90

**NEW**  
PC Software V6.0 features long term data logging, exporting data to EXCEL or text file, scrolling mode

**Wittig Technologies**  
Wittig Technologies, Inc.  
266 East Meadow Avenue  
East Meadow, NY 11554  
Phone (516) 794 4080, Fax (516) 794 1855  
[www.wittigtechnologies.com](http://www.wittigtechnologies.com)

**MORE POWER**

**THE ATOM**

**Setting a new standard in STAMPS**

The New BASIC MICRO ATOM, offers more in the same package you're already familiar with. With built-in features, like upgradeable firmware, get more power for your projects now and into the future!

**Software Features:**

- Graphical Debugging (ICD)
- More Software Commands
- 32 Bit Integer Math
- 32 Bit Floating Point Math
- Easy to use code editor
- BS2p Compatible Syntax
- Expanded BASIC library
- Firmware upgradeable
- Unlimited Support
- Free Software Updates
- Plus much more!

**Built in Hardware:**

- Over 300 Bytes of RAM
- 256 Bytes of Data EEPROM
- External & Internal Interrupts
- 5 10 bit A/D Converters
- 2 Capture and Compare
- Internal Adjustable Vref
- +/- External Vref
- 3 Timers
- 2 PWM
- UARTS
- I2C, SPI

**\$59.95 Complete**  
Also available in Development Combo and OEM package

**MORE FLEXIBILITY**  
**for PICmicro® MCU's**

**MBASIC**

Ever wanted to learn how to program PICmicro® MCUs? Now you can with easy to use BASIC. Our software is much simpler than C or Assembly. MBASIC for PICmicro® MCUs creates a one click solution that allows you to experiment and test code changes on-the-fly! From beginner to professional bring your projects to life quicker and easier with MBASIC for PICmicro® MCUs!

**New - In Circuit Graphical Debugger built in!**  
**Priced from \$99.95**

Educational and Dealer pricing available with all products  
PICmicro is a registered trademark of Microchip Inc.

**BASIC MICRO INC.**  
Order online or call 1-734-425-1744  
Basic Micro, 34391 Plymouth Rd., Livonia, MI 48150  
See More online at <http://www.basicmicro.com>

**\$59 PCBs**  
And our layout software is **FREE!**  
Download ▶ Design ▶ Send ▶ Receive

**Download our FREE layout software**  
**Design your two-sided plated-through PCB**  
**Send us your design with just a click**  
**Receive your boards in a few business days**  
Select our MiniBoard service and get three top quality 2.5" x 3.8" PCBs for \$59 - shipping included!

**expresspcb.com**

VISA MasterCard

**Classic guide to customizing BASIC Stamp computers for hobbyists and designers.**

**by Scott Edwards**  
(former Stamp Applications columnist for *Nuts & Volts*)

**Only \$39.95**  
Available from the *Nuts & Volts* bookstore  
[www.nutsvolts.com](http://www.nutsvolts.com)

# Stamp Applications

Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

by Jon Williams

## Weather On The Wire

*I've always had an interest in the weather. As a boy, I would read books on basic meteorology and simple weather forecasting. There was a moment, albeit brief, when I thought about being a TV weather man. After high school and a couple of years in the military, I went to work in the irrigation industry and spent most of that time in the golf course business — a business tied very directly to the weather.*

Even though I've been out of that business for a couple of years, my morning routine is the same: I wake, I stretch, I go out onto the front porch to see what the weather is like, and what I can expect for the day. Today (early January as I write) was really nice. It's clear in Dallas and the temperature on my front porch was 65 degrees and the air is clear. You can't beat that.

A couple of months ago I was contacted by a Stamp programmer named Tim. He lives in Tucson and has a big interest in the weather — very big. He told me about a low-cost weather station that used Dallas Semiconductor 1-Wire technology. I was under the impression that these stations were no longer available, but I was wrong. A company called AAG in Mexico has them and you can order them via the Internet using PayPal. A 1-Wire weather station seemed like a neat add-on for a BS2p, so I bought a few.

### 1-Wire Weather Station

Since we don't have to build the station, I'm not going to include the schematic here. It is available on the AAG web site if you'd like to review it as we go through the code. The key thing to understand is that there are three devices connected to the 1-Wire bus: a DS1820 thermometer, a DS2423 counter for the anemometer (wind speed), and a

DS2450 quad analog-to-digital converter that is connected to the wind vane.

The connection to the weather station is an RJ-11 (telephone) connector. If you have a BS2p Demo Board, this project is easy since there is an RJ-11 on the board. Even if you're making your own connections, please note that the 1-Wire pull-up is very stiff, 1 kOhm. This is necessary to overcome the impedance of the cable connecting the Stamp to the weather station. If you are using the Demo Board, remove jumper B2 and connect a 1 kOhm pull-up to the 1-Wire bus.

### Weather Code

With nothing to build, let's jump right into the code. Now ... before we even start, we need to know what the 1-Wire serial numbers are. I've worked with two of these stations and neither came with the serial numbers printed on the side of the box (nor was I expecting it). This is not a problem. What we need to do is run the 1-Wire SearchRom code we developed last April. If you don't have it, you can download the code from the *Nuts & Volts* web site.

When you run SEARCHDEMO.BSP you'll see that it doesn't know what a DS2423 is and lists it as an "Unknown Device." Don't worry about this. Just copy the serial numbers so that they can be plugged into the weather station code.



Okay, this listing is pretty long so we better jump right into it. The Initialization section opens the DEBUG window, displays a header for the screen, then gets down to work. The first piece of real work is to make sure that the 1-Wire bus is not shorted. This is done by making the 1-Wire comm pin an input then reading it to make sure we see it pulled up to +5 (will read 1). If zero is returned, the program is aborted to an error handler.

The next section of code is the reason we just did that check. There's a small power supply in the weather station. Okay, okay, it's just a diode and a capacitor. The cap provides Vdd to the 1-Wire devices and to pull-ups connected to the A2D converter. Since the supply "borrows" power from the 1-Wire bus, we start the program by charging it. This is done by making the 1-Wire bus pin high and waiting for 10 seconds. In our program, a message is displayed showing the charging time left.

Once the station is charged, labels for communication status and each of the sensors are printed. The program then enters the main loop. In the main loop, the program checks to see that the station has connected the branches to the current sensor. So long


as the station stays connected, the program will run the main loop. If the station gets disconnected, the initialization sequence will be re-run until contact with the station is reestablished.

We can check to see if the station is connected by issuing the SearchROM command and reading back two bits. If nothing is connected, all we'll see is the pulled-up bus and a value of %11. If there are devices connected, we'll get another pattern. The reason for checking is the same as looking for a short: there's probably a lot of wire between your desk and the station and accidents can happen. We'll assume that the world is a perfect place for wires and that there are not shorts and the station is connected. Now we can read and display the sensors.

### Temperature

The first sensor is the DS1820 temperature sensor. We've used this before so we'll be brief in the coverage. The routine starts by loading the device serial number into an array called romData. This process is facilitated by a small sub-routine called Load\_SN. What we'll do is load the DATA address of the device into eeData, then call this routine. The serial num-

## Stamp Applications

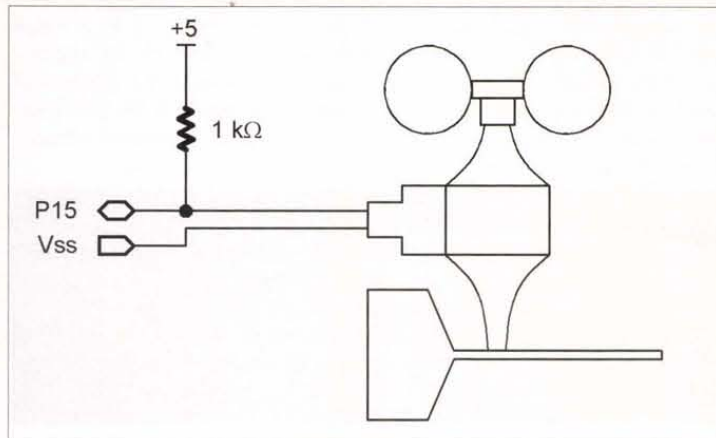

ber is read out of EEPROM and placed into the array.

With the serial number loaded, we'll issue a MatchROM command with the serial number, then the temperature conversion command. All of this happens in a single OWOUT statement. Then the 1-Wire bus pin is taken high and we wait for 750 milliseconds. This is the worst-case conversion time for the DS1820 and making the bus high provides power during the conversion process.

The nine-bit Celsius temperature is retrieved with OWIN and converted to Fahrenheit for display. Note that the temperature is a signed value. This time of year the temperature in many areas of the country falls below zero Celsius (32 Fahrenheit).

The temperature is displayed using a subroutine — RJ\_Print — developed by Stamp guru, Stamp list contributor, and all-around-nice-guy, Dr. Tracy Allen. To use this routine, we need to pass the width out of field in the variable width and our value to print in rjNum. Tracy's routine makes clever use of LOOKDOWN to determine how many spaces to print (pad) before the actual number. If the number is negative, a minus sign will be printed in front of the number.

### Wind Speed

The 1-Wire weather station measures wind by counting the number of pulses during a known time window. Mechanically, there is an arm connected to the anemometer cups that carries a couple of magnets to trip a reed switch connected to the DS2423 counter. Since the counter cannot be reset, what we'll have to do is get the current count, delay for some period, read the count

again and then subtract the first reading from the second to obtain the difference.

What Tim noticed and I confirmed is that the counter only seems to work properly when used in overdrive mode. Neither one of us can explain it, but I wanted to make you aware in case you decide to make modifications to the program.

To put the DS2423 in overdrive mode, we send the ODMatchROM value by itself. After that, we send additional data using the high speed setting of the OWOUT command. Since the DS2423 is actually a memory plus counter, we're forced to read the final byte of the page that precedes the counter value. It's a quirk of the DS2423 that you cannot reset the counter (it is reset on power-up) nor read it directly. There are actually two independent counters in the DS2423. The weather station ties the inputs together so reading either one will give us the same value.

Our OWIN ends up reading the lower 16 bits of a 32-bit counter. Then the program pauses for 2500 milliseconds and reads the counter again. The difference is computed and the wind speed is calculated.

The general formula for wind speed is given as:

$$\text{Speed (mph)} = \text{Revolutions\_Per\_Second} * 2.453$$

There are two magnets on the t-bar that rotates above the wind speed counter switch, so each revolution actually gives us two counts. If we paused for one second, our wind speed resolution would be 1.23 mph (2.453 mph / 2). Since I wanted a little better resolution than that, I used a PAUSE value of 2500. This brings



the resolution down to 0.49 mph — much better. What this means, though, is we have to wait for the wind speed reading. This is the reason the sensor indication was developed.

In order to maintain our resolution within the Stamp's integer math system, what we're actually going to do is use 24.53 to get tenths. Since our PAUSE value is 2500 — equivalent to waiting five seconds if one revolution equaled one count — we divide that by five and get 4.906. For use with the Stamp, we multiply 4.906 by 256 and use the /\* (star-slash) operator. The result is multiplication by a fractional value.

The variable speed now holds the wind speed in tenths of a mile per hour. For display, we extract the whole part by dividing the wind speed value by ten, then sending it off to RJ\_Print. Then we print a decimal point and the tenths digit by using the DEC1 modifier.

### Wind Direction

While many weather stations use a free-rotating potentiometer to determine wind direction, the 1-Wire station takes a different approach. It uses eight reed switches connected to a resistor array that is read by an DS2450 quad A2D converter. The way the resistors are connected means that a given A2D channel will

either see full scale, half-scale, or ground. Our trick will be to convert these four analog readings into a 1-of-16 direction value.

The DS2450 is configured to read all four channels, using eight-bit values with a 5.12 volt reference. Since the actual voltage at the station is going to be a bit less than five volts, our highest reading will be slightly less than 255 (full scale at 5.12 volts). I wrote a quick test program to decode the values for each of the 16 compass directions. High values tended to be around 235 to 240, middle values around 120, and low values between 0 and 3.

To get the A2D data, we issue a ReadMem command starting at address 0. We need to retrieve

### Resources:

#### Jon Williams

3718 Valley View Lane, #3040  
Irving, TX 75062  
(972) 659-9090  
jonwms@aol.com

#### Parallax

599 Menlo Drive, Suite 100  
Rocklin, CA 95756  
(888) 512-1024  
www.parallaxinc.com

#### Tim Bitson's Weather Page

www.timbitson.com/  
weather/index.html

#### AAG

www.aag.com.mx

# Stamp Applications

eight bytes of data since the DS2450 can be configured for 16-bit values. Since we don't need the romData array anymore, the A2D data is read into it. Next, we'll grab every other byte to create a single word value that can be used in a table to determine direction.

As each A2D channel is retrieved from romData, it is divided by 90. With integer math, this division will always return a value of two (high readings), one (middle readings), or zero. The result

of each division is placed into a separate Nib in the variable direction. At this point, direction holds a value that tells us the direction from which the wind is blowing. LOOKDOWN is used to convert this value into a zero to 15 value that can be used to point to a string. You can see how the large look-up table was split in two pieces and that the variable dFlag is set to an out-of-range value before LOOKDOWN is used.

If the value returned in direction is invalid (it happens — one of

my stations has a bad part), the value of dFlag will not be changed by LOOKDOWN. This can be used to flag an error as we've done with this program. If the value was good, the LOOKDOWN

tables will convert it to a value between zero and 15. We use this value to calculate the address of the string that tells us the direction and print it with the subroutine called Print\_String.

## That's A Wrap

Well, that about wraps it up for this month. For those of you interested in the weather, this should get you started. Be sure to take a look at Tim's site and the Dallas Semiconductor site for more sensors.

**Next month ...** GPS. Yes, I said I wouldn't write about it but I've been convinced that I should. We'll be using the BS2p again and taking advantage of the SPSTR modifier of SERIN.

*Until then, Happy Stamping. NV*

```

' -----[ Title ]-----
' File..... OW WEATHER.BSP
' Purpose... 1-Wire Weather Station Interface
' Author.... Jon Williams / Parallax (portions by Tim Bitson)
' E-mail.... jonwms@aol.com
' Started... 13 DEC 2001
' Updated... 06 JAN 2002

' { $STAMP BS2p }

' -----[ Program Description ]-----
' This program reads and displays the sensors from a Dallas 1-Wire Weather
' Station.
'
' NOTE: The 1-Wire bus requires a very stiff pull-up -- 1 kOhm or less.

' -----[ Revision History ]-----
'
' 15 DEC 2001 - Version 1 working
' 06 JAN 2002 - Updated error handling for bad wind vane

' -----[ I/O Definitions ]-----
OWpin          CON    15          ' 1-Wire bus

' -----[ Constants ]-----
' 1-Wire Support
OW_NoRst        CON    %0000      ' no Reset
OW_FERst        CON    %0001      ' Front-End Reset
OW_BERst        CON    %0010      ' Back-End Reset
OW_BitMode      CON    %0100
OW_HighSpd      CON    %1000

ReadROM         CON    $33        ' read ID, serial num, CRC
MatchROM        CON    $55        ' look for specific device
ODMatchROM      CON    $69        ' overdrive match rom
SkipROM         CON    $CC        ' skip rom (one device)
SearchROM       CON    $F0        ' search

' DS1820 control
CnvrtTemp       CON    $44        ' do temperature conversion
RdScratch       CON    $BE        ' read scratchpad

' DS2423 control
ReadMemCntr     CON    $A5        ' read memory + counter

' DS2450 control
ReadMem         CON    $AA        ' read memory
WriteMem        CON    $55        ' write memory
Convert         CON    $3C        ' do conversion

NoDevice        CON    %11        ' no device present
CommOkay       CON    1
NoComm          CON    0

Celsius         CON    0
Fahrenheit      CON    1
TMode          CON    Fahrenheit ' temperature display mode
DegSym         CON    176

MoveTo          CON    2          ' DEBUG cursor positioning
LF             CON    10          ' linefeed

' -----[ Variables ]-----
devCheck        VAR    Nib        ' device check return code
commStat        VAR    Bit        ' comm status
sensor          VAR    Nib        ' current sensor to display
eeAddr          VAR    Word       ' string pointer in EE
char            VAR    Byte       ' character to print
idx             VAR    Nib        ' loop counter
romData         VAR    Byte(8)    ' ROM data to devices

tempIn          VAR    Word       ' raw temperature
sign            VAR    tempIn.Bit11 ' 1 = negative temperature
tLo             VAR    tempIn.LowByte
tHi             VAR    tempIn.HighByte
tSign          VAR    Bit
tempC           VAR    Word       ' Celsius
tempF           VAR    Word       ' Fahrenheit

cntrA           VAR    Word       ' wind count start
cntrB           VAR    tempIn     ' wind count end
rps             VAR    tempC      ' revs per second
speed           VAR    tempF      ' wind speed

crcl6           VAR    tempIn     '
verify          VAR    char       '
direction       VAR    tempC      '
dFlag           VAR    tempF.LowByte

rjNum           VAR    Word       ' number to right justify
width           VAR    Nib        ' width of field
rjSign          VAR    Bit
digits          VAR    Nib

' -----[ EEPROM Data ]-----
DS1820          DATA    $10,$15,$32,$09,$00,$08,$00,$A9 ' temp sensor
DS2423          DATA    $1D,$82,$43,$01,$00,$00,$00,$6F ' wind speed
DS2450          DATA    $20,$AF,$FF,$00,$00,$00,$00,$5E ' wind direction

CommUp          DATA    "... Up", 0
CommDn          DATA    "... Down", 0

WindDir         DATA    " N", 0, " NNE", 0, " NE", 0, " ENE", 0
                  DATA    " E", 0, " ESE", 0, " SE", 0, " SSE", 0
                  DATA    " S", 0, " SSW", 0, " SW", 0, " WSW", 0
                  DATA    " W", 0, " WNW", 0, " NW", 0, " NNW", 0

BadDir          DATA    "Error", 0

' -----[ Initialization ]-----
Initialize:
  DEBUG CLS
  PAUSE 250 ' open DEBUG window

Splash Screen:
  DEBUG Home
  DEBUG "=====", CR
  DEBUG " BS2p <--> 1-Wire Weather Station ", CR
  DEBUG "=====", CR

Charge Station:
  INPUT OWpin
  IF (Ins.LowBit(OWpin) = 0) THEN Bus_Shorted ' possible wiring problem

  HIGH OWpin
  DEBUG MoveTo, 0, 4, "Charging station..."
  FOR idx = 10 TO 1
    DEBUG MoveTo, 20, 4, DEC idx, " "
    PAUSE 1000
  NEXT
  INPUT OWpin
  DEBUG MoveTo, 0, 4, REP " "\25

```

```

Weather_Labels:
  DEBUG MoveTo, 0, 4, "Comm..... "
  DEBUG MoveTo, 0, 6, "( ) Temperature... ", CR
  DEBUG MoveTo, 0, 7, "( ) Wind Speed.... ", CR
  DEBUG MoveTo, 0, 8, "( ) Direction.... ", CR

' -----[ Main Code ]-----
Main:
  GOSUB Comm_Status ' check 1-Wire comm
  IF (CommStat = CommOkay) THEN Show_Sensors
  PAUSE 2000
  GOTO Initialize ' "reboot" if comm went down

Show_Sensors:
  GOSUB Flag_Sensor ' show sensor in use
  BRANCH sensor, [Show_Temp, Show_Wind_Speed, Show_Wind_Dir]

Main2:
  sensor = sensor + 1 // 3 ' select next sensor
  GOTO Main
  END

' -----[ Subroutines ]-----

' *****
' A shorted condition on the 1-Wire bus has been detected
' -- we can't charge the station cap in this condition
' *****

Bus_Shorted:
  DEBUG CLS, "The 1-Wire bus is shorted.", CR
  DEBUG "Please repair before continuing.", CR
  END

' *****
' Print status of 1-Wire comms
' *****

Comm_Status:
  eeAddr = CommUp ' assume bus is up
  CommStat = CommOkay
  GOSUB Device_Check ' check bus for devices
  IF (devCheck <> NoDevice) THEN Print_Comm
  eeAddr = CommDn
  CommStat = NoComm
  DEBUG MoveTo, 19, 6, REP " \15 ' clear station data if down
  DEBUG MoveTo, 19, 7, REP " \15
  DEBUG MoveTo, 19, 8, REP " \15

Print_Comm:
  DEBUG MoveTo, 12, 4 ' show comm status
  GOSUB Print_String
  RETURN

' *****
' Check for presence of 1-Wire devices
' -- does not search for ROM codes
' *****

Device_Check:
  devCheck = 0
  OWOUT OWpin, OW_FERst, [SearchROM]
  OWIN OWpin, OW_BitMode, [devCheck.Bit1, devCheck.Bit0]
  RETURN

' *****
' Indicate sensor in use
' *****

Flag_Sensor:
  DEBUG MoveTo, 1, 6, " ' clear previous mark
  DEBUG MoveTo, 1, 7, "
  DEBUG MoveTo, 1, 8, "
  DEBUG MoveTo, 1, (6 + sensor), "+" ' mark current sensor
  RETURN

' *****
' Transfer OW serial number to RAM
' -- point to SN with eeAddr
' *****

Load_SN:
  FOR idx = 0 TO 7 ' load ROM pattern
    READ (eeAddr + idx), romData[idx]
  NEXT
  RETURN

' *****
' Retrieve and display temperature
' *****

Show_Temp:
  eeAddr = DS1820 ' load device serial number
  GOSUB Load_SN

  OWOUT OWpin, OW_FERst, [MatchROM, STR romData\8, CnvrtTemp]

  HIGH OWpin ' extra juice during conversion
  PAUSE 750
  INPUT OWpin

  OWOUT OWpin, OW_FERst, [MatchROM, STR romData\8, RdScratch]
  OWIN OWpin, OW_BERst, [tLo, tHi]

  tSign = sign ' save sign bit
  tempIn = tempIn >> 1 ' round to whole degrees
  IF (tSign = 0) THEN NoNeg1
  tempIn = tempIn | $FF00 ' extend sign bits for negs

NoNeg1:
  tempC = tempIn ' save Celsius value
  tempIn = tempIn * / $01CC ' multiply by 1.8
  IF (tSign = 0) THEN NoNeg2
  tempIn = tempIn | $FF00 ' if neg, extend sign bits

NoNeg2:
  tempF = tempIn + 32 ' finish C -> F conversion

  DEBUG MoveTo, 19, 6 ' move cursor to temp display
  rjNum = tempF ' prep for right justified print
  width = 5 ' five digits wide
  GOSUB RJ_Print
  DEBUG " ", DegSym, "F"
  GOTO Main2

' *****
' Retrieve and display wind speed
' -- mph = rps * 2.453
' *****

Show_Wind_Speed:
  eeAddr = DS2423
  GOSUB Load_SN

  ' get starting count
  OWOUT OWpin, OW_FERst, [ODMatchROM]
  OWOUT OWpin, OW_HighSpd, [STR romData\8, ReadMemCntr, $DF, $01]
  OWIN OWpin, (OW_HighSpd | OW_BERst), [cntrA.LowByte, cntrA.LowByte,
  cntrA.HighByte]

  PAUSE 2500 ' = revs for 5 seconds
  GOSUB Comm_Status
  IF (CommStat = CommOkay) THEN Get_End_Count
  GOTO Main2 ' abort if comm down

  ' get ending count
  Get_End_Count:
    OWOUT OWpin, OW_FERst, [ODMatchROM]
    OWOUT OWpin, OW_HighSpd, [STR romData\8, ReadMemCntr, $DF, $01]
    OWIN OWpin, (OW_HighSpd | OW_BERst), [cntrB.LowByte, cntrB.LowByte,
    cntrB.HighByte]

  Calc_CPS:
    rps = cntrB - cntrA ' get differential count
    IF (cntrB >= cntrA) THEN Calc_Speed
    rps = rps + $FFFF ' correct for rollover

  Calc_Speed:
    speed = rps * / $04E7 ' rps * 4.906 (tenths @ 5 seconds)
    DEBUG MoveTo, 19, 7
    width = 3 ' width of whole portion
    rjNum = speed / 10 ' get whole portion
    GOSUB RJ_Print ' print it
    DEBUG " ", DECl speed, " mph " ' then print tenths
    GOTO Main2

' *****
' Retrieve and display Wind direction
' *****

Show_Wind_Dir:
  eeAddr = DS2450
  GOSUB Load_SN
  OWOUT OWpin, OW_FERst, [MatchROM, STR romData\8, WriteMem, $08, $00]

  FOR idx = 1 TO 4 ' setup four channels
    OWOUT OWpin, OW_NoRst, [$08] ' 8-bit values
    OWIN OWpin, OW_NoRst, [crcl6.LowByte, crcl6.HighByte, verify]
    OWOUT OWpin, OW_NoRst, [$01] ' 5.12 volt scale
    OWIN OWpin, OW_NoRst, [crcl6.LowByte, crcl6.HighByte, verify]
  NEXT

  Start_Conversion:
    OWOUT OWpin, OW_FERst, [MatchROM, STR romData\8, Convert, $0F, $55]
    OWIN OWpin, OW_NoRst, [crcl6.LowByte, crcl6.HighByte]

    HIGH OWpin ' juice during conversion
    PAUSE 10
    INPUT OWpin

  Get_A2D:
    OWOUT OWpin, OW_FERst, [MatchROM, STR romData\8, ReadMem, $00, $00]
    OWIN OWpin, OW_BERst, [STR romData\8]

```

Stamp listing continued on page 61

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number. While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

**Nuts & Volts Magazine  
Events Calendar**  
430 Princland Court  
Corona, CA 92879  
**Phone** 909-371-8497  
**Fax** 909-371-3052  
**E-mail**  
events@nutsvolts.com

# FEB-MAR

## FEBRUARY 2002

### FEBRUARY 1-2

**MS - JACKSON** - State Convention. Jackson ARC, Ron Brown AB5WF, 601-956-1448. Email: ab5wf@arrl.net Web: http://www.jxnarc.org

### FEBRUARY 2

**KS - LACYGNE** - Hamfest. Mine Creek ARC, Ron Cowan KB0DTI, 913-757-4455. Email: kb0dti@arrl.net  
**MI - DEARBORN** - Antique Radio Swapmeet. Armenian Community Center, 19319 Ford Rd. Michigan Antique Radio Club, Don Colbert, 313-278-1948. Email: donsradio@aol.com

**MI - NEGAUNEE** - Hamfest. Hiawatha ARA, Robert Serfas N8PKN, 906-226-9782. Email: n8pkn@aol.com Web: www.qsl.net/k8lod/  
**SC - NORTH CHARLESTON** - Hamfest. Stall High School. Talkin: 146.79, 145.25, and 147.45. Charleston ARS, Jenny Myers WA4NGV, 843-747-2324. Email: brycemyers@aol.com Web: www.qsl.net/wa4usn/index.html

### FEBRUARY 2-3

**FL - MIAMI** - Tropical Hamboree. Dade Radio Club of Miami, Evelyn Gauzens W4WYR, 305-642-4139. Email: w4wyr@arrl.org

### FEBRUARY 3

**OH - LORAIN** - Hamfest. Gargus Hall, 1965 N. Ridge Rd. 8am-1pm. Talkin: 146.700- and 444.800+. NOARS, John Schaaf K8JWS, 216-696-5709. Email: noars@qsl.net

### FEBRUARY 4

**AZ - PHOENIX (SUN CITY)** - Auction, 7pm. St. Clement of Rome Catholic Church Social Hall, 15800 Del Webb Blvd. Talkin: 147.30+. West Valley ARC, Jerry W9JIF, 623-214-8136. Email: w9jif@juno.com

### FEBRUARY 8-9-10

**FL - ORLANDO** - Convention. Orlando ARC, Harold Prosser KK1B, 321-235-7513 (days) or 407-365-2444 (eves). Email: hal@mpinet.net Web: www.oarc.org/hamcat.html

### FEBRUARY 9

**ME - CHELSEA** - Hamfest. Augusta ARA, Tom Clay KD1KE, 207-382-6000. Email: kd1ke@uninets.net  
**MI - TRAVERSE CITY** - Hamfest. Cherryland ARC, Joe Novak W8TVT, 231-947-8555. Email: jnovak@traverse.net  
**MN - ST. CLOUD** - Hamfest. St. Cloud ARC, L. Scott Hall KA0DAQ, 320-252-4498.

Email: lscotth@aol.com  
Web: www.w0sv.org  
**OK - ADA** - Hamfest. Ada ARC, Charles Etier KC5TGA 580-436-4425  
Web: www.adacomp.net/~jewell/

### FEBRUARY 9-10

**TN - MEMPHIS** - Hamfest. Shelby County Bldg., Mid-South Fairgrounds. Sat: 9am-5pm, Sun: 9am-2pm. VE testing. Ben KU4AW, 901-372-8031, Melinda KE4DXN, 901-744-1737. Web: www.dixiefest.org

### FEBRUARY 10

**OH - MANSFIELD** - Hamfest. InterCity ARC & MASER, Scott Yonally N8SY, 419-522-9893. Email: n8sy@arrl.net Web: www.maser.org  
**VA - RICHMOND** - State Convention. The Showplace, 3000 Mechanicsville Tpke. 8:30am-3:30pm. Richmond Amateur Telecommunications Society, 804-790-0077, opt 4. Web: www.frostfest.com

### FEBRUARY 16

**CA - MONTEREY (SEASIDE)** - Hamfest. Naval Postgraduate School ARC, Brian Broggie W6FVI, 831-626-1501. Email: w6fvi@arrl.net Web: www.k6ly.org/radiofest  
**FL - SEBRING** - Hamfest. Highlands County ARC, Spencer Whitmire W4ERC, 863-452-0359. Email: w4erc@arrl.net  
**MA - MARLBOROUGH** - Hamfest. Algonquin ARC, Ann Weldon KA1PON, 508-481-4988 before 9pm.  
**OR - RICKREALL** - Hamfair. Salem Repeater Assn., Larry Quiring KC7NOS, 503-585-8897. Email: KC7NOS@juno.com  
**TX - SMITHVILLE** - Hamfest. Bastrop County ARC, Juan Vinton KB5YAE, 512-303-4743. Email: kb5yae@qsl.net Web: www.qsl.net/kb5yae/

### FEBRUARY 17

**CO - BRIGHTON** - Hamfest. Aurora Repeater Assn., Wayne

## COMPUTER SHOWS

**AGI Shows**, 317-299-8827  
E-Mail: info@agishows.com  
http://www.agishows.com

**Blue Star Productions**  
612-788-1901  
www.supercomputersale.com

**Computers And You**  
734-283-1754  
www.a1-supercomputersales.com

**Computer Central Shows**  
630-782-4625  
Fax 630-834-2594  
E-Mail: cc@gats.com  
www.computercentralshows.com

**Computer Country Expo**  
847-662-0811  
Web: www.ccexpo.com

**Five Star Productions**  
810-379-3333  
E-Mail: jeff@fivestar  
www.fivestarshows.com

**Gibraltar Trade Center, Inc.**  
734-287-2000 Taylor, MI  
E-Mail: taylor@gibraltartrade.com  
www.gibraltartrade.com

**Gibraltar Trade Center, Inc.**  
810-465-6440 Mt. Clemens, MI.  
E-Mail:  
mtclemens@gibraltartrade.com  
www.gibraltartrade.com

**KGP Productions**  
1-800-631-0062, 732-297-2526  
E-Mail: kgp@mail.com

**MarketPro, Inc.**, 201-825-2229  
www.marketpro.com

**MarketPro, Inc.**, 301-984-0880  
E-Mail: md@marketpro.com  
http://marketpro.com

**ComputerShow**  
770-663-0983  
E-Mail: narisaam@aol.com  
Web: www.showsale.com

**Northern Computer Shows**  
978-744-8440  
E-Mail: inquiries@ncshows.com  
Web: ncshows.com

**Peter Trapp Computer Shows**  
603-272-5008  
Web: www.petertrapp.com

# Events Calendar

Heinen N0POH, 303-699-6335.  
Email: n0poh@arri.net  
Web: www.qsl.net/n0ara

## FEBRUARY 23

**GA - DALTON** - Hamfest. Dalton ARC, Harold Jones N4BD, email: n4bd@ocsonline.com

**IN - LAPORTE** - Hamfest. LaPorte Civic Auditorium, 1001 Ridge St. 7am-1pm. Talkin: 146.52, 146.61- PL 131.8. LPARC, Neil Straub WZ9N, 219-324-7525. Email: nstraub@worldkey.net

Web: www.geocities.com/K9JSL/  
**ND - BISMARCK** - Hamfest.

Central Dakota ARC, Kurt Carufel KB0KDG, 701-222-0938. Email: carufel@home.com

**NY - HORSEHEADS** - Hamfest. The National Guard Armory.

8am-3pm. Talkin: 146.700-, 444.20. ARAST, Randy 607-738-6857. Email: n2synt@arast.org

Web: www.arast.org

**VT - MILTON** - State Convention. Milton High School, Rt. 7. 8am-1pm. Talkin: 145.15-. Radio

Amateurs of Northern VT, Mitch Stern W1SJ, 802-879-6589. Email: w1sj@arri.net

Web: www.ranv.org

## FEBRUARY 24

**FL - ZEPHYRHILLS** - Hamfest. Zephyrhills Area ARC, Ron Russell N8VFE, 813-782-1602. Email: ron301@aol.com

**NC - ELKIN** - Hamfest.

Briarpatch & Foothills ARCs, Pat Hill AE4HK, 540-236-6747. Email: CraigPatton @ kg4fla@hotmail.com

**NY - HICKSVILLE** - Hamfest. Levittown Hall. ARRL VE exams. Talkin: W2VL 146.85. Long

Island Mobile ARC, Rich Rosner N2STU, 631-563-1859. Email: hamfest@limarc.org

Web: www.limarc.org

**NY - WILLIAMSVILLE** - Hamfest. Lancaster ARC, Luke Cialianno N2GDU, 716-634-4667. Email: luke@towncountryflorist.com

Web: http://gbhamfest.hamgate.net

**OH - CUYAHOGA** - Hamfest. Emidios Party Center, 48 E. Bath Rd. 8am-2pm. Cuyahoga Falls ARC, Inc., Ted Sarah W8TTS, 330-688-2013. Email: w8tts@arri.net

## MARCH 2

**AR - RUSSELLVILLE** - Hamfest. Arkansas River Valley AR Foundation, John Evans

WB5BHS, 501-967-6001. Email: jevans@cswnet.com

Web: www.cswnet.com/~arvarf/hamfest.htm

**CA - REDDING** - Hamfest.

Shasta Cascade ARS, Jim Bremer KE6QUA, 530-222-8001. Email: ke6oua@arri.net

**FL - NEW PORT RICHEY** - Hamfest. Gulf Coast ARC, Rick Brown AG4JN, 727-934-8741. Email: ag4jn@arri.net

Web: www.gulfcoastarc.org/

**KY - CAVE CITY** - Hamfest. Cave City Convention Center, I-65, Exit 53. 7:30am-2pm. VE

testing. Talkin: 146.94/34.

Mammoth Cave ARC, Jim Erskine KD4GNN, email: mail@chirotoons.com

**NJ - PARSIPPANY** - Hamfest. PAL Bldg., 33 Baldwin Rd.

Splitrock ARA, Maria Turner KB2VKP, 888-511-SARA. Email: hamfest@splitrockara.org

Web: www.splitrockara.org

**OK - ELK CITY** - Hamfest. West

## Tired of Expensive Inkjet Cartridges? Save 90% on Inkjet Inks!

Refill kits Black (8 oz) Color (4 oz C, Y, M) Printer (Call for Others Not Listed!)	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP500 Series, 400, Officejet 300, 350, Fax	7	14	<b>4.71</b>	<b>2.85</b>	32.95	39.95
HP600 Series, Officejet 500, 570, 600, 610 630, 700	7	14	<b>4.71</b>	<b>3.21</b>	32.95	44.95
HP820C, 855C, 870C, 1000C, 1150C, Copier 120, 210	6	12	<b>6.67</b>	<b>3.33</b>	39.95	39.95
HP720C, 722C, 712C, 880C, 890C, 895C, 1120C, 1170C	6	12	<b>6.67</b>	<b>3.75</b>	39.95	44.95
HP900C Series, P1000 Series, Officejet G55, G85, G95	6	12	<b>6.67</b>	<b>3.75</b>	39.95	44.95
HP2000C Pro Color Printer, 2200, 2500	6	12	<b>6.67</b>	<b>3.75</b>	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple StyleWriter 1200, 1500	14	20	<b>2.15</b>	<b>2.00</b>	29.95	39.95
Canon BJC-4000 Series, 2000, 5000 Series, Multipass Series	60	60	<b>0.50</b>	<b>0.67</b>	29.95	39.95
Canon BJC-6000, 3000, S400, S450, S600, Multipass 755	14	8	<b>2.85</b>	<b>1.67</b>	39.95	39.95
Epson Stylus Color 500, 200	20	17	<b>1.50</b>	<b>2.35</b>	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	20	17	<b>1.50</b>	<b>2.65</b>	29.95	44.95
Epson Stylus Color 440, 660, 670, 740, 760, 860	20	17	<b>1.50</b>	<b>2.65</b>	29.95	44.95
Epson Stylus Color 480, 580, 880 <b>NEW</b>	20	17	<b>1.50</b>	<b>2.65</b>	29.95	44.95
Lexmark 3200, 5700, Z11, Z12, Z31, Z32,	15	17	<b>2.67</b>	<b>2.35</b>	39.95	39.95
Compaq IJ300, IJ600, IJ700, IJ750, IJ900 Xerox XJ8C	15	17	<b>2.67</b>	<b>2.65</b>	39.95	44.95
Lexmark Z42, Z51, Z52, Z83, Compaq IJ1200, A1000 <b>NEW</b>	15	17	<b>2.67</b>	<b>2.65</b>	39.95	44.95
Lexmark Photo kit for 3200, 5700, 7000, 7200, Z42, Z51, Z52	9			<b>3.11</b>		27.95
Lexmark 2030, 2050, Execjet II/IIc, Medley 4C, Compaq IJ200	10	17	<b>3.00</b>	<b>2.35</b>	29.95	39.95
Xerox HC 450, XJ4C, XJ6C	22	12	<b>1.36</b>	<b>3.33</b>	29.95	39.95
<b>New Combination Kits</b> Black dye 4 oz / Color 2 oz each						<b>44.95</b>
<b>New Combination Kits</b> Black pigmented 4 oz / Color 2 oz each						<b>49.95</b>

## Save 30 - 60% on New Compatible Cartridges Quantity Discounts for 3 or 6+ cartridges Mix and match

Printer (Call for Others Not Listed!)	BLACK Cartridge			COLOR Cartridge		
	Qty	1 / 3 / 6+		Qty	1 / 3 / 6+	
Canon BJC-4000 Series, 2000, 5000 Series, Multipass Series	4.50	3.83 / 3.69		10.95	9.31 / 8.98	
Canon BJC-6000, 3000, S400, S450, S600, Multipass 755	7.95	6.76 / 6.52		7.50	6.38 / 6.15	
Canon BJC-70, 80, 85 (3 pack Black / 3 pack color)	9.95	8.46 / 8.16		14.95	12.71 / 12.26	
Epson Stylus Color, Color Pro, Pro XL	9.95	8.46 / 8.16		13.95	11.86 / 11.44	
Epson Stylus Color II, IIs, 200	9.95	8.46 / 8.16		13.95	11.86 / 11.44	
Epson Stylus Color 400, 500, 600, 800, 850, 1520, Photo	9.95	8.46 / 8.16		13.95	11.86 / 11.44	
Epson Stylus Color 440, 660, 670, 740, 760, 860	9.95	8.46 / 8.16		13.95	11.86 / 11.44	
Epson Stylus Color 750, 900, 980, 1200	10.95	9.31 / 8.98		15.95	13.51 / 13.08	
Epson Stylus Color 480, 580, 880 <b>NEW</b>	10.95	9.31 / 8.98		14.95	12.71 / 12.26	
Epson Stylus Color 777, 870, 875, 1270 <b>Requires Empty Return !</b>	11.95	11.95 / 11.95		15.95	15.95 / 15.95	

### Quality Inks and Toners for:

**HP Epson Lexmark  
Canon Apple Xerox**

**Inkjet  
Southwest**



### New Combination Black / Color Kits

4 oz black dye / 2 oz C,M,Y color - **\$44.95**  
4 oz black pigmented / 2 oz C,M,Y - **\$49.95**

**Mon - Fri 8:30-5:30 PDT 11:30-8:30 EST**

**Call or see us online!**

**www.inkjetsw.com**  
**(480) 668-1069 Fax**

**1-800-447-3469**  
**(480) 668-0959**

**MARCH  
2002**

# ELECTRONIX EXPRESS

Visit Our Website At  
<http://www.elexp.com>

## WELLER SOLDERING STATION - MODEL WLC 100

- Variable power control (5 to 40 watts)
- Replaceable heating element
- Quality light-weight pencil iron

\$36<sup>95</sup>

## LOWEST PRICE 20MHZ

### INSTEK<sup>®</sup> OSCILLOSCOPE

MODEL GOS-620  
Dual Channel - 20MHZ  
(INCLUDES PROBES)

\$299<sup>00</sup>

### SCOPE PROBE 60 MHZ

SWITCHABLE X1, X10

\$12<sup>95</sup>

### DIGITAL MULTIMETER

32 Ranges - 3 1/2 Digit

MODEL MY-64

AC/DC Volt/Current, Res. Cap.,

Frequency, Rubber Holder Included

\$27<sup>95</sup>

### PAD-234

DIGITAL/ANALOG TRAINER

Complete portable

workstation. Variable and

fixed power

supplies, function generator,

digital I/O, rugged design,

high impact case.

Assembled \$150<sup>00</sup> Kit \$110<sup>00</sup>

### INSTEK<sup>®</sup> FUNCTION GEN.

WITH INT/EXT FREQ. COUNTER

3 MHz, Digital Display

MODEL 8216 \$199<sup>00</sup>

### ALLIGATOR LEADS

SET OF 10

\$2<sup>10</sup>

### SWITCHES

Mini Toggle SPDT

50¢ ea.

SOLDERING IRON 3-WIRE

HIGH PERFORMANCE

#060501 \$5<sup>25</sup>

### HIGH QUALITY TOOLS

With Cushion Grips and Return Spring

Needle Nose Pliers \$2<sup>95</sup>

Wire Stripper \$1<sup>50</sup>

Diagonal Cutter \$2<sup>95</sup>

DC POWER SUPPLIES

MODEL HY3003 - DIGITAL DISPLAY

Variable output, 0-30 VDC, 0-3 Amp \$89<sup>00</sup>

MODEL HY3003-3 - TRIPLE OUTPUT

Two 0-30 VDC, 0-3 Amp

variable outputs plus 5V 3A

fixed, Digital Display. \$215<sup>00</sup>

## RSR TELECOMMUNICATIONS TRAINER

HANDS-ON TELEPHONY, LAN, CATV EXPERIENCE  
WITH ONE SELF-CONTAINED UNIT

T-Comm Trainer (TCM-100) \$199<sup>95</sup>

Lab Manual / Work Book 26<sup>95</sup>

Component and Supplies Kit 37<sup>95</sup>

Tool Kit 119<sup>95</sup>

Only \$199<sup>95</sup>

MODEL TCM-100

## SOLDERLESS BREADBOARD

830 tie points. MB102PLT

model features 3 binding posts

and aluminum backplate.

Part No. 1-9 10+

MB102 5.95 5.00

MB102PLT 8.95 8.00

## MOTION DETECTOR

\$2 ea. - 10 For \$15

LM555 10 Min. 22¢ ea.

LM741 10 Min. 27¢ ea.

74LS00 10 Min. 18¢ ea.

7805 Regulator 10 Min. 30¢ ea.

2N3904 10 Min. 6¢ ea.

PN2222 10 Min. 6¢ ea.

Red LED T 1 1/4 10 Min. 6¢ ea.

Green LED T 1 1/4 10 Min. 7¢ ea.

Yellow LED T 1 1/4 10 Min. 8¢ ea.

Photo Cell 10 Min. 65¢ ea.

100K Pot, 1" Shaft PC Mt. 10 Min. 15¢ ea.

## PRESS-N-PEEL

PC Board Transfer Film

PNP Blue 5 Sheet \$9.90

PNP Wet 5 Sheet 9.90

PNP Blue 20 Sheet 28.95

PNP Wet 20 Sheet 28.95

## RESISTOR

KIT

1/4 W 5 %

film. 5 pieces

each of 73

values. 365

pieces total.

\$3<sup>95</sup>

## FREE CATALOG

MORE

Low-Priced

Items In Our

FREE

256-Page Catalog



TERMS: Min. \$20 + shipping. School Purchase Orders: VISA/ MC, Money Order, Prepaid. NO PERSONAL CHECKS, NO COD. NJ Residents: Add 6% Sales Tax.

In NJ: 732-381-8020

FAX: 732-381-1006

365 Blair Road • Avenel, NJ 07001-2293

800-972-2225

<http://www.elexp.com>

email: [electron@elexp.com](mailto:electron@elexp.com)

Circle #49 on the Reader Service Card.

OK ARC, Earl Bottom N5NEB,  
580-821-0633.

Email: [n5neb@logixonline.net](mailto:n5neb@logixonline.net)

TN - KNOXVILLE - Hamfest.

Kerbela Temple, 315 Mimosa

Ave. 8am-4pm. Talkin:

144.83/145.43 or 146.52 sim-

plex. Shriners of Kerbela ARS,

Paul Baird K3PB, 865-986-9562

PA - GREENSBURG - Hamfest.

Foothills ARC, Tim Bartlow

## MARCH 3

PA - GREENSBURG - Hamfest.

Foothills ARC, Tim Bartlow

K3TB, 724-834-6517. Email:

[k3tb@yahoo.com](mailto:k3tb@yahoo.com) Web:

[www.geocities.com/foothills007](http://www.geocities.com/foothills007)

VA - ANNANDALE - Hamfest.

Northern VA Community College,

8333 Little River Turnpike (Rt.

236). VE testing 9am. Talkin:

146.31/91 & 146.685. Vienna

Wireless Society, Jim Parsons

W4JTP, 703-392-0150.

Email: [w4jtp@aol.com](mailto:w4jtp@aol.com)

Web: <http://winterfest.home.att.net>

WI - WAUKESHA - Hamfest.

SEWFARS, Gary Pierce N9LGE,

email: [sewfars@hotmail.com](mailto:sewfars@hotmail.com)

Web: [www.sewfars.com](http://www.sewfars.com)

## MARCH 9

AR - HARRISON - Hamfest.

Boone County Fairgrounds, Hwy.

65B. VE testing. 8am-2pm. North

AR ARS, Bill Rose N5VKF, 870-

741-7074.

Email: [billrose@cox-internet.com](mailto:billrose@cox-internet.com)

Web: [www.qsl.net/naars/hamfest/index.html](http://www.qsl.net/naars/hamfest/index.html)

AZ - SCOTTSDALE - Hamfest.

Scottsdale ARC, Ed Nickerson

WU7S, 480-949-5162. Email:

[bnickers@qwest.net](mailto:bnickers@qwest.net)

FL - PORT CHARLOTTE -

Hamfest. EARS & PRRA, Larry

Brown KD4KVE, 941-625-0830.

Email: [kd4kve@aol.com](mailto:kd4kve@aol.com)

NC - CHARLOTTE - Hamfest.

Charlotte County Fairgrounds.

7am-5pm. Talkin: 147.255+.

PRRA & EARS, Vic Emmelkamp,

941-473-5560. Web: [www.fcrosby.com/hamfest/index.html](http://www.fcrosby.com/hamfest/index.html)

ND - WEST FARGO - Hamfest.

Red River Valley Fairgrounds.

8am-3pm. VE testing.

Web: [www.rra.org](http://www.rra.org)

WA - PUWALLUP - Hamfest.

Mike and Key ARC, Michael

Dinkelman N7WA, 425-867-4797

days or 253-631-3756 eves.

Email: [mwdink@eskimo.com](mailto:mwdink@eskimo.com)

Web: [www.mikeandkey.com](http://www.mikeandkey.com)

MARCH 9-10

LA - RAYNE - Hamfest. Rayne

Civic Center, 300 Frog Festival

Dr. VE testing. Talkin: 146.820-

600, 147.030+ 600 PL. LCARC,

web: [www.w5ddl.org](http://www.w5ddl.org)

NC - CHARLOTTE - Hamfest.

Mecklenburg ARS, Tom Hunt

KA3VVJ, 704-948-7373.

Email: [hamfest@w4bfb.org](mailto:hamfest@w4bfb.org)

Web: [www.w4bfb.org](http://www.w4bfb.org)

MARCH 10

CANADA - BC - NEW WEST-

MINSTER - AR & Electronics

Flea Market. Burnaby & New

Westminster ARC, Bob Kungl

VE7KW, 604-524-9177.

Email: [VE7KW@rac.ca](mailto:VE7KW@rac.ca)

MA - AMHERST - Hamfest.

Amherst/Pelham Regional Middle

School, 170 Chestnut St. Exams.

Talkin: 146.940- & 145.130+ 71.9

PL. Mount Tom Amateur

Repeater Assn., Bob Meneguzzo

K1YO, 877-481-8131.

Email: [k1yo@arri.net](mailto:k1yo@arri.net)

Web: [www.mtara.org/hamfest/flea.html](http://www.mtara.org/hamfest/flea.html)

MARCH 15-16

OK - CLAREMORE - Hamfest.

Green Country Hamfest

Committee, David Jackson

KE4OPA, 918-622-2277. Email:

[info@greencountryhamfest.org](mailto:info@greencountryhamfest.org)

Web: [www.greencountryhamfest.org](http://www.greencountryhamfest.org)

MARCH 16

CT - POMFRET - Hamfest.

Eastern CT ARA, Paul Rollinson

KE1LI, 860-928-2456. Email:

[ke1li@arri.net](mailto:ke1li@arri.net)

## The Standard for checking Capacitors in-circuit



Good enough to be the choice of Panasonic, Pioneer, NBC, ABC, Ford, JVC, NASA and thousands of independent service technicians.

Inexpensive enough to pay for itself in just one day's repairs. At \$179, it's affordable.

And with a 60 day trial period, satisfaction guaranteed or money-back policy, the only thing you can lose is all the time you're currently spending on trying to repair all those dogs you've given up on.

## CapAnalyzer 88A

Available at your distributor, or call 561-487-6103

Electronic Design Specialists

## Locate shorted or leaky components or conditions to the exact spot in-circuit

Still cutting up the pcb, and unsoldering every part trying to guess at where the short is?

\$179



Your DVM shows the same shorted reading all along the pcb trace. LeakSeeker 82B has the resolution to find the defective component. Touch pads along the trace, and LeakSeeker beeps highest in pitch at the defect's pad. Now you can locate a shorted part only a quarter of an inch away from a good part. Short can be from 0 to 150 ohms

## LeakSeeker 82B

[www.eds-inc.com](http://www.eds-inc.com)

Circle #50 on the Reader Service Card.

# Muffle The Loudmouths!

## Keep those loud TV commercials on the straight and level with the Blab Buster

By TJ Byers

**Y**ou know the scenario. It's late evening, the day is done, and you're settled in for a night of relaxation. On the screen, Sweet Jessica has finally found her secret love, Robert, Prince of Edonia, heir to the throne. Words fade to whispers, lusty lips part to meet, and a cloak of silence falls over the intimate scene. Suddenly, the TV cranks up the volume to an ear-shattering level to announce that Lloyd's Lotto Emporium is having a year-end clearance sale of previously-owned lottery tickets.

Don't you just hate that? TV commercials are annoying enough, but adding blasting sound to this manic madness is more than anyone should have to bear. Well, enough is enough. So enough, in fact, that it prompted me to build the Automatic Audio Attenuator, which I have affectionately nicknamed the Blab Buster. When you insert the Blab Buster between your TV and the speakers, those late-night hawkers are hushed to a level of near acceptability.

The Blab Buster is, in reality, an automatic volume control, or automatic level control (ALC), that levels the playing field for audio sounds. Soft passages get boosted up so that you can hear them without cupping an ear, and the loudmouth car guys are shut down to no more than a murmur. While it was specifically designed to quiet boisterous TV commercials, it works as a loudness control for any audio source, including VCRs, DVDs, cassette players — and even short-wave receivers.

### The Magic Behind The Blab Buster

Imagine you had a magic genie that would constantly monitor the sound output of your TV set and adjust the volume control as the audio level changes. Your genie would turn up the volume during soft passages and turn it back down when the noise level got too loud. Well, imagine no longer. That's exactly what the Blab Buster does — it's your personal volume control genie.

The Blab Buster is designed to be compatible with the audio input/output RCA jacks commonly found on today's VCRs and A/V receivers; that is, 200 mV at 10k for the input and 200 mV at 600 ohms for the output. However, the dynamic input range of the Blab Buster is wide enough that it automatically adjusts any input between 100 mV and 8 volts to 200 mV at the output. It's this extreme input range that makes the Blab Buster versatile enough to be used with a wide variety of audio devices — and more than powerful enough to knock the wind out of those night squawkers. My measurements show the frequency response to be within 3dB from 16 Hz to 20kHz, with good performance up to 50 kHz.

What's even more amazing is that all this power is packed into a single IC. The NE570 compander chip was originally developed by Signetics way back in the late 1970s, and is still in production under the Philips Semiconductor moniker. (See "Inside The NE570 Compander" for a better look at this chip's inner workings.)


### How It Works

The NE570 is a dual, controlled-gain circuit in which either channel may be used as a dynamic range compressor or expander that is well-suited for cell phone and communications applications. However, with a little clever rewiring here, and a gain limiter there, the NE570 can also function as an ALC.


The difference between a signal compressor and an ALC is the point where the input signal is sampled for processing. In a compressor circuit, the gain of the pass amplifier is determined by the voltage at the amp's output (Figure 1a). Response time is fast and the compression ratio is typically 2:1. An ALC, on the other hand, takes its gain control from the input to the pass amplifier (Figure 1b). Response time is slower, allowing for a larger dynamic

range within the controlled gain bandwidth, and the compression ratios extend to 10:1 and higher. This allows musical crescendos to peak within the given time frame.


The circuit diagram of the Blab Buster ALC is shown in Figure 2. Because the NE570 contains two identical compander devices — both of which we use for a complete surround sound effect — this discussion will focus on the right channel (upper) only. C1 provides the input of the pass amplifier (pin 6) with the feedback signal required for ALC operation as described above, whereas the gain is determined by the signal applied to the precision rectifier block (pin 2). C7 determines the amount of time it takes for a change in the input signal to cause a corresponding change in the gain of the ALC; if you wish a faster response time, reduce C7 to 1uF.

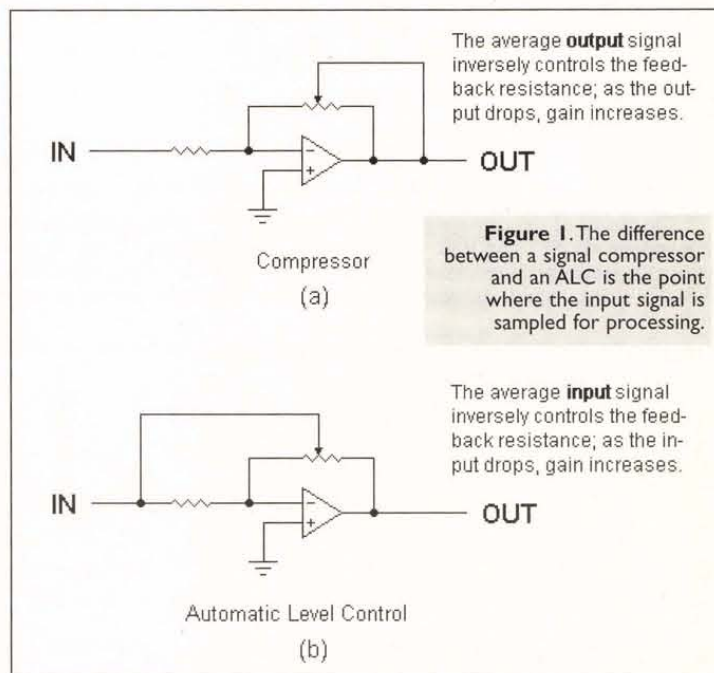

**Figure 3.** The Blab Buster fits between the audio source and the power amplifier.

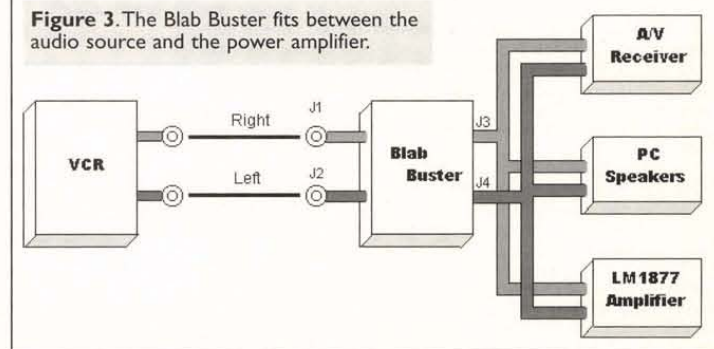

**Figure 2. Schematic of the Blab Buster, automatic level control.**

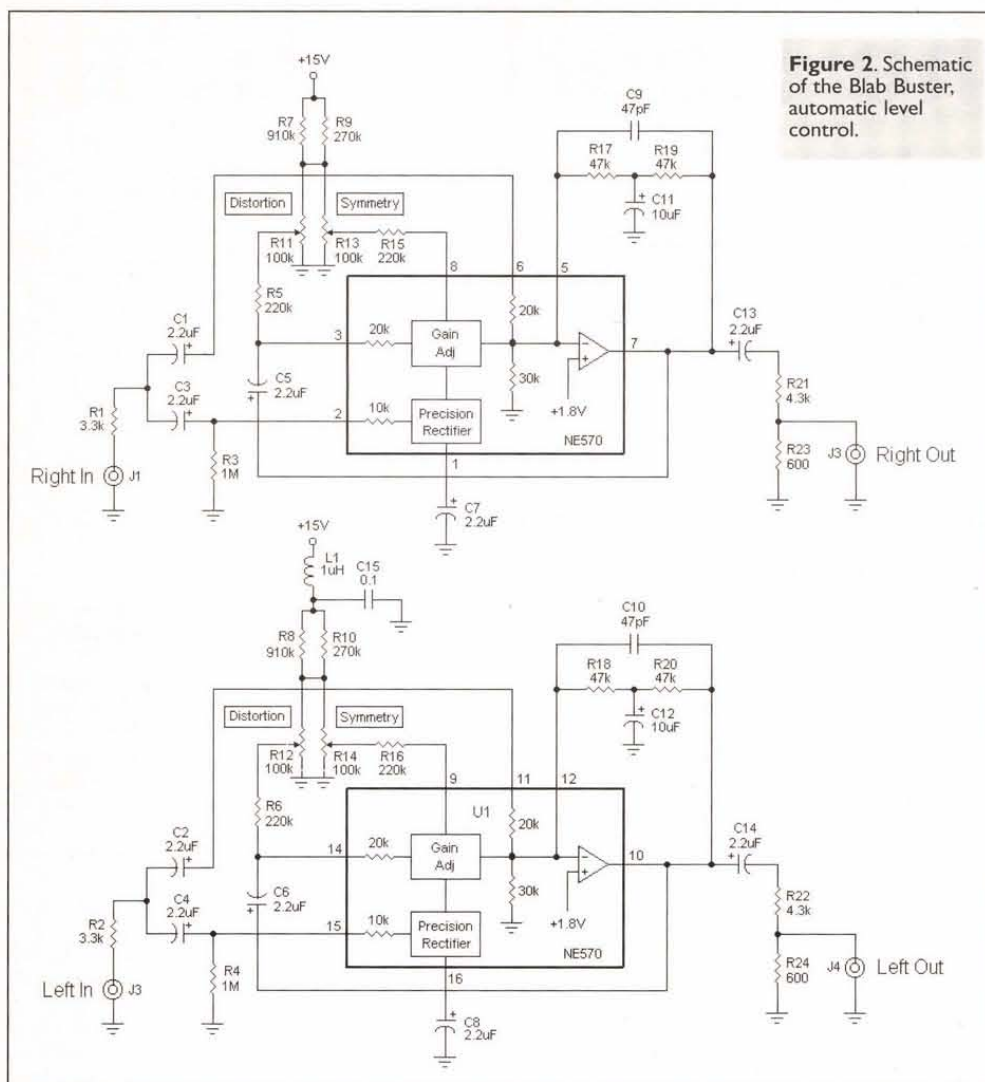

The output of the gain-controlled pass amp is a current that's converted to a voltage via R17 and R18. C11 acts as a low-pass filter and C9, placed across the feedback loop, prevents the op amp from breaking into oscillation at higher gains. In fact, runaway gain is a problem with ALC circuits at very

incorporated into your TV set, stereo, or radio. You're limited only by your imagination and building skills.

What makes Blab Buster construction so attractive is the fact that it has no moving parts. There are no knobs, switches, bells, or whistles. There's

## Construction

This is the best part of the project because there's no right way or wrong way to build the Blab Buster. It can be built as a stand-alone unit or

## Inside The NE570 Compressor — Behind The Smoke And Mirrors


Believe it or not, the NE570 compander actually uses smoky mirrors to accomplish its tasks. The NE570 houses two identical sets of building blocks in a single 16-pin package. Each unit consists of a delta-gain amplifier, a precision rectifier, an op amp, and a shared internal voltage reference. Ordinarily, the first half of the compander is used as a compressor, which reduces the dynamic swing of an input signal, while the second half is used as an expander that restores the compressed signal to its original dynamic range. Hence the name, compander for "compressor" and expander."

Why compress a signal just to decompress it, you ask? Noise reduction. Whenever an audio signal (or any signal, for that matter) passes through a transmission medium, it picks up noise along the way.

The NE570 was originally designed to satisfy the requirements of the telephone system. When several telephone channels are multiplexed onto a common line, the resulting crosstalk between channels results in a background noise that attaches itself to the voice channels in the form of static. The figure shows how a compander can reduce the amount of static on the line using compression and expansion.

Typically, the NE570 is configured to reduce the bandwidth of the input signal by a ratio of 2:1, which means a +20dB signal is compressed to +10dB and a -20dB signal is boosted up to -10dB; a 0dB signal is left unchanged. If the dynamic range of the original signal extends from +20dB to -80dB — a range of 100dB — the compressor reduces that to 50dB. Notice, however, that the compression takes place before the signal takes to the telephone wires. This ensures that the voice signals ride well above the noise on the lines.

At the receiving end (here's where the mirror comes into play), the entire output of the telephone line is expanded by a factor of 2:1, thus restoring the compressed +10dB signal back to +20dB, and the -10dB signal back down to its previous -20dB. Notice, too, that the noise on the line is given the same expansion treatment. What enters the phone line as -45dB of noise is reduced to -90dB by the expander, for a signal-to-noise reduction of 45dB.

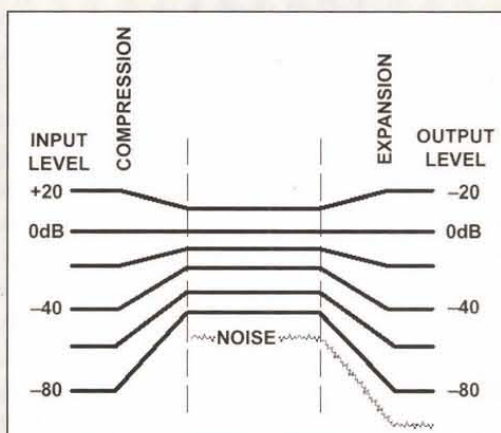

**Background noise is reduced considerably by first compressing the transmitted signal then expanding it afterwards.**

simply a black box that you place between the sound source — like a VCR — and the power amplifier (Figure 3). For this reason, I opted to place the complete Blab Buster on a 4-by-5-inch printed circuit board. The circuit board can easily slip inside a VCR, a project enclosure box, or speaker cabinet. A foil pattern of the circuit board is shown in Figure 4 and a corresponding parts layout is shown in Figure 5.

The board is powered by a small 15-volt power source, like a wall-wart. For those of you who wish to roll your own power supply, I've shown one in Figure 6. With the addition of an ON/OFF switch, the Blab Buster can even be run for several hours from a pair of nine-volt batteries wired in series (in this mode, Vcc equals 18 volts).

The output of the Blab Buster can plug into an A/V receiver, a pair of powered computer speakers, or the stereo amplifier design shown in Figure 7. This single chip power amp, built around an LM1877, delivers 1.5 watts per channel into an eight-ohm load. A companion printed circuit board and parts layout for the stereo amp are shown in Figure 8. The same power supply used for the Blab Buster can also power the stereo

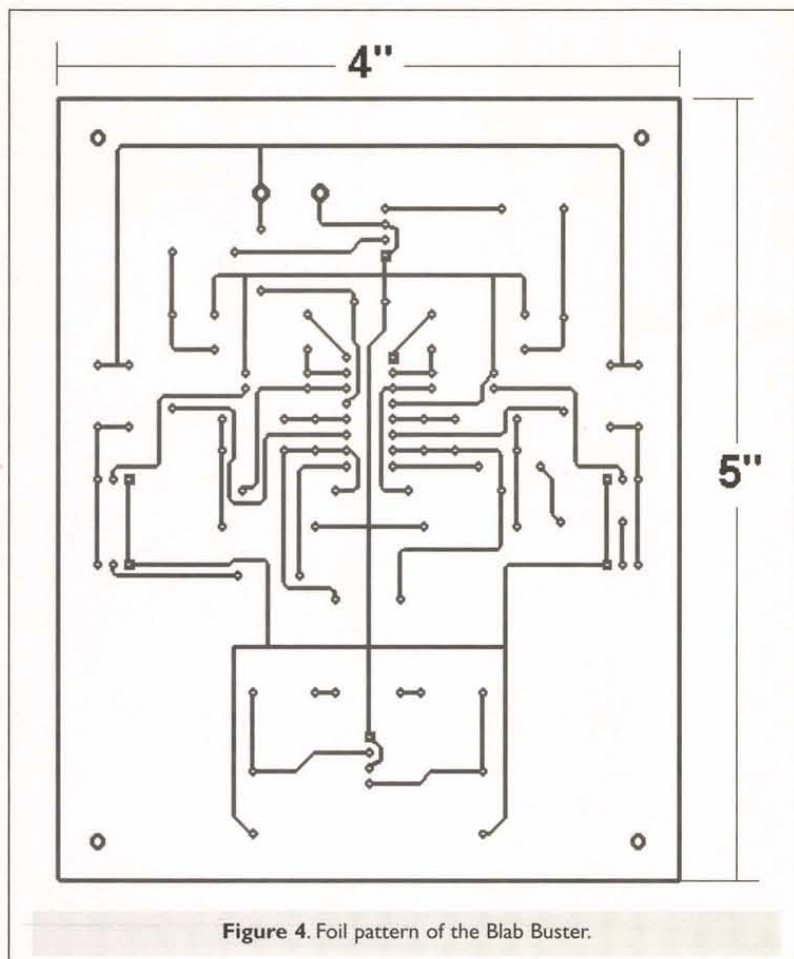


Figure 4. Foil pattern of the Blab Buster.

amplifier (note that the nine-volt battery version will be short-lived at high volume levels).

### Silent Nights

Meanwhile, back in Edonia, Robert (which isn't his real name) isn't really a prince, but a con artist who appeared on America's Most Wanted the week

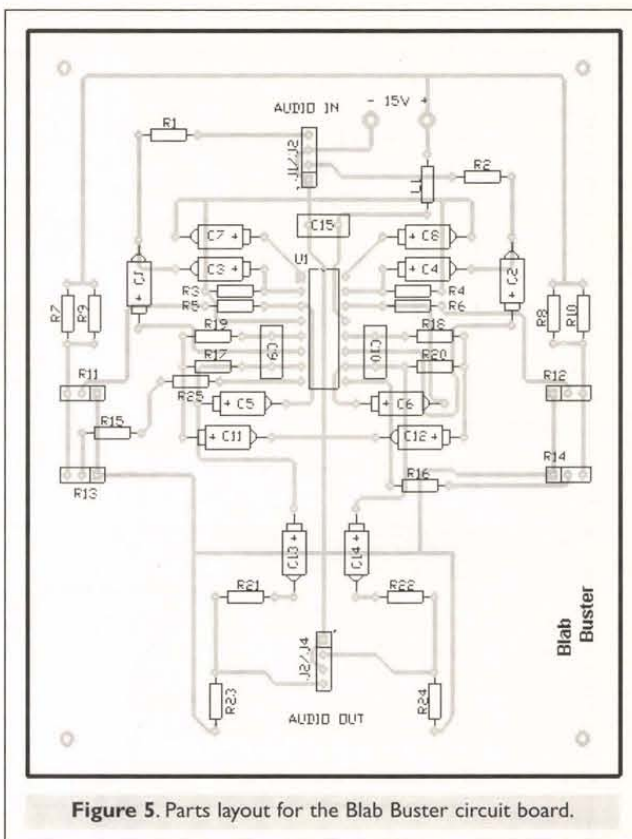


Figure 5. Parts layout for the Blab Buster circuit board.

before. Fortunately, Jessica had already seen that episode, phoned the FBI during the commercial, received a huge reward for his capture and conviction, and lived happily ever after.

Yes, the Blab Buster has made a difference in my life. My temperament is mellow, and I get up less often to raid the refrigerator when the commercials come on. I also notice that I enjoy the movies more and actually understand some of the plots. Whether you use it to muffle your TV, stereo, or radio, I'm sure you'll be as pleased with the results as I am. Now if I can just slip one of these boards into my kids' boom box for permanent muting ... now that would be something really worth writing about. **NV**

Article continues on page 56

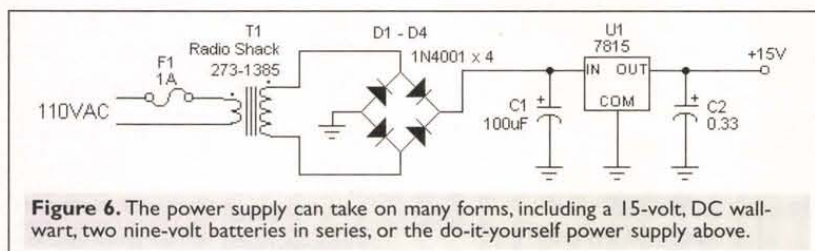


Figure 6. The power supply can take on many forms, including a 15-volt, DC wall-wart, two nine-volt batteries in series, or the do-it-yourself power supply above.

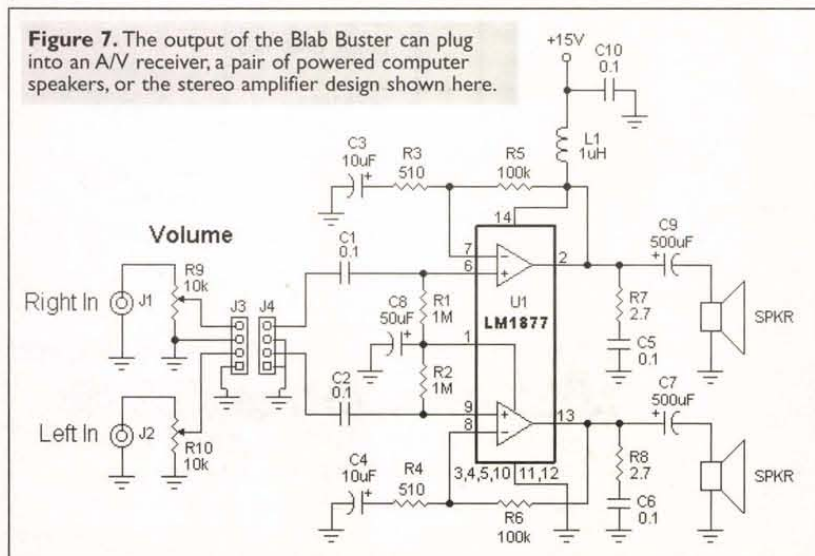


Figure 7. The output of the Blab Buster can plug into an A/V receiver, a pair of powered computer speakers, or the stereo amplifier design shown here.

### Parts List — Blab Buster

#### Resistors

R1, R2 — 3.3k  
R3, R4 — 1M  
R5, R6 — 220k (optional)  
R7, R8 — 910k (optional)  
R9, R10 — 270k (optional)  
R11, R12, R13 — 100k trimpot (optional)  
R14  
R17, R18, R19 — 47k  
R20  
R21, R22 — 4.3k  
R23, R24 — 600 ohms  
R25 — Jumper wire

R3, R4 — 510 ohms  
R5, R6 — 100k  
R7, R8 — 2.7ohms  
R9, R10 — 10k audio taper pot

#### Capacitors

C1, C2, C3, C4 — 2.2uF, 16V  
C5, C6, C7, C8, C13, C14  
C9, C10 — 47pF  
C11, C12 — 10uF, 16V  
C15 — 0.1uF

#### Semiconductors

U1 — LM1877

#### Misc.

J1, J2, J3, J4 — Four-pin berg connector (similar to PC motherboard speaker plug)  
L1 — 1uH choke  
Spkr — eight-ohm speaker

### Parts List — 15-Volt Power Supply

#### Capacitors

C1 — 100uF, 25V  
C2 — 0.33uF

#### Semiconductors

U1 — NE570

#### Misc.

F1 — 1A fuse  
T1 — 12.6VAC, 300mA transformer

D1-D4 — 1N4001 (four places)  
U1 — 7815 voltage regulator

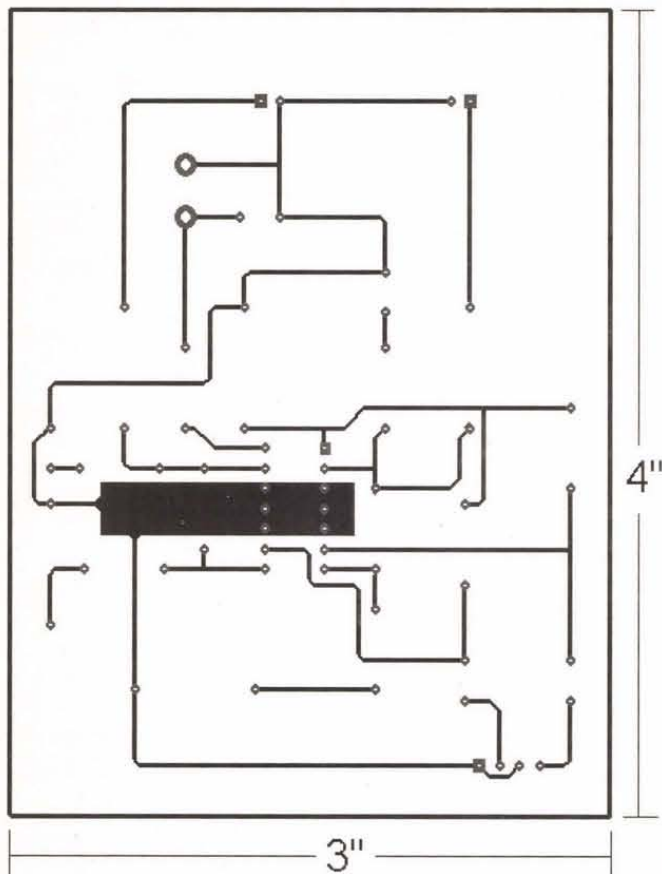


Figure 8. Foil pattern and parts layout for the LM1877 stereo power amplifier.

**PICmicro<sup>®</sup> MCU COMPILER**

A high order language with extraordinary optimization specifically designed for the PICmicro<sup>®</sup> MCU.

CUSTOM COMPUTER SERVICES, INC.

- Access to all PICmicro MCU hardware features from C.
- Built-in libraries that work with all chips for RS232 serial I/O, I<sup>2</sup>C, discrete I/O and precision delays.
- Source code drivers and ready to run programs included for LCD modules, keypads, 24xx and 93xx serial E<sup>2</sup> PROMS, X10, DS1302 & NUU6355 Real Time Clocks, Dallas Touch Memory Devices, DS2223 & PCF 8570 serial SRAM, LTC1938 & PCF8591 A/D converters and more.
- Integrates with simulators/emulators such as MPLAB.

**LINUX COMPILERS ALSO AVAILABLE**

```
#include <pic18c452.h>
#define delay(x) do { while (x) { } } while (0)
void main()
{
    print ("press any key to begin");
    getkey();
    printf ("the signal activated\n");
    while (TRUE) {
        output_high (pin_B0);
        delay_us (500);
        output_low (pin_B0);
        delay_us (500);
    }
}
```

- PCB Compiler for 12 Bit OPCODE Chips \$ 99
- PCM Compiler for 14 Bit OPCODE Chips \$ 99
- PCH Compiler for 16 Bit PIC18 Chips \$ 99
- PCW Compiler Professional Package
- Windows IDE CD-Rom with both PCB / PCM \$ 350
- PIC18 PCW add on (PCW) \$ 50

MENTION THIS AD WITH YOUR ORDER AND RECEIVE A FREE NIGEL GARDNER PIC C BOOK

**CUSTOM COMPUTER SERVICES, INC.**

P.O. Box 2409 • Boulder, CO 80509  
303-797-0455 ext. 35 • FAX: 303-797-0459  
http://www.pic-c.com  
EMAIL: ccs@ccscom.com

**Five-Pound Spool FAMOUS BRAND SOLDER**

0.125" diameter, 29% Tin, 71% Lead, solid core.

**92Z012 Spool - \$19.95**

**PC BOARD DRILLS**

Used. Carbide. Serviceable. Assorted sizes.

**99Z004 50 for \$19.95**

**ANTI-STAT MAT**

Approx. 21 1/2" x 11 3/4" (55cm x 30cm), with alligator clip. Handy size for many jobs.

**BM-402A \$19.95 each**

**3.5-DIGIT LCD MULTIMETER**

Small size (~2 3/4" W x 6" L x 1" D). AC/DC Volt and Amp scales, transistor, diode and resistance tests, test probes, and battery. Has 0.5% basic accuracy, instruction sheet and low battery indication. KRM #AEEC-1504.

**20Z012 \$9.95**

**ULTRABRIGHT WHITE LED**

T1 1/4 ultrabright white, 5600 mcd. This will stun your eyes!

**SE5084J \$4.95 each**

**BIPOLAR STEPPER MOTOR DRIVER IC**

600mA output current capability per channel. 1.2A peak output current (non-repetitive) per channel. 36V max. Enable facility. Temperature protection. Logical "0" input voltage up to 1.5V (high noise immunity). With documentation.

**L293B \$3.00 each**

**DIGITAL POCKET MULTIMETER**

Measures: Volts AC to 450 Volts, Volts DC in four ranges from 2 to 450 Volts. Measures: Amps DC to 200 mA. Measures: Ohms in four ranges from 0 to 20000K Ohms. Comes with test probes attached and full set of instructions.

**96Z004 \$14.95 each**

**VIDEO SWITCHING CENTER**

This switch box has four inputs and three outputs. Console-mounted switches and instructions allow you to switch between a wide choice of video sources.

**95V020 \$9.95 each**

**www.gatewayelec.com**

(Electronically Speaking, Gateway's Got It!)

**gateway ELECTRONICS, INC.**

MAIL ORDERS CALL TOLL-FREE 1-800-669-5810

**alltronics.com**

Mail Orders: PO BOX 730 - Morgan Hill, CA 95038-0730

Phone: (408) 847-0033 Fax: (408) 847-0133

Download our Catalog: <http://www.alltronics.com>

Dealers welcome by appointment. Visa, M/C, AmEx Accepted. All Sales Final. California Residents Add Sales Tax. Shipping Additional on All Orders. Prices Good 60 Days from Date of Publication and Subject to Change Without Notice.

# Classifieds

## HAM GEAR


**SATELLITE TV.** Complete selection of C & Ku band equipment.  
**WWW.DAVESWEBSHOP.COM**



**NEW ICOM IC-V8 VHF 5.5W** handheld with full keypad, CTCSS/DCS encode/decode, tone scan, 1100mAh battery and charger + optional battery case \$199.99. Easy modification for full TX 136-174MHz. To order call 1-800-977-0448 or visit <http://www.nsradio.com/>



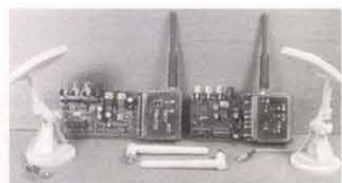
**2.4GHz ATV — 8 channel TRANSMITTERS AND RECEIVERS.** 35mV output power, 1 video channel, 2 audio. SMA connectors. NTSC/PAL compatible. Includes 1/4 wave rubber duck antenna. Standard frequencies are: 2398, 2405, 2412, 2416, 2420, 2428, 2435, 2442 MHz. Custom frequencies are available. See ad in this section for power amplifier. **\$79/each for transmitter. \$79/each for receiver.** EzATV. Visit our web-site for dealers or order on-line at [www.4atv.com](http://www.4atv.com)



**1.2GHz ATV — 8 channel TRANSMITTERS AND RECEIVERS.** 75mV output power, 1 video channel, 2 audio. SMA connectors. NTSC/PAL compatible. Includes 1/4 wave rubber duck antenna. Standard frequencies are: 1250, 1255, 1260, 1265, 1270, 1275, 1280, 1290 MHz. Custom frequencies are available. **\$79/each for transmitter. \$79/each for receiver.** EzATV. Visit our web-site for dealers or order on-line at [www.4atv.com](http://www.4atv.com)



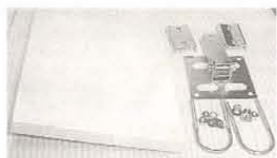**2.4GHz POWER** amplifier with power supply, 10-40 mV input, 1 (one) watt output with in-line SMA connectors and built-in heat sink. Approx. 2" x 2" x 5/8" size. Frequency range 2.3GHz-2.5GHz. **\$189/each.** Compatible with all ATV product lines. See our website for more info on accessories and transmitter and receiver modules. EzATV. Visit our web-site for dealers or order on-line at [www.4atv.com](http://www.4atv.com)



**SUPER HIGH GAIN 14 dbi flat antenna** with N or SMA connector tuned for 2.3-2.5 GHz. Use with 2.4GHz ATV 8 channel transmitter or receiver. **\$179/ea.** SPECIAL PRICE. EzATV. Visit our web-site for dealers or order on-line at [www.4atv.com](http://www.4atv.com)

## BATTERIES/CHARGERS



**THE SMART BATTERY CHARGER** for lead acid or gel cell batteries. Can be left connected to the battery **INDEFINITELY**, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MC/VISA accepted. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280. [www.a-a-engineering.com](http://www.a-a-engineering.com)

## CB — SCANNERS

**CB MODIFICATIONS!** Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBCI, Box 30655NV, Tucson, AZ 85751. [www.cbcentl.com](http://www.cbcentl.com)

**240+ CHANNEL CB/HAM/FRS/COMMERCIAL** radios: AM/FM/SSB/CW export/domestic: RCI, TEKK, Motorola, Uniden, Cobra, Alinco, Kenwood. Mics, antennas, liners, meters, mod books, manuals, schematics, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244. [www.penny-circus.net](http://www.penny-circus.net)

## COMPUTER HARDWARE

**NewComputer.com COMPARES** prices and detailed product specifications from top online sellers. Visit NewComputer.com to save time when shopping for new computer equipment.

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com



**VGA TO COMPOSITE (NTSC) VIDEO CONVERTER — ULT-2000.** Handheld. Powered from keyboard with S-video and RGB outputs, too. 3:1 zoom control with many extras. **\$99/ea.** Matco, Inc., Schaumburg, IL. 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)

**DATA ACQUISITION:** This very compact and low-cost kit will allow virtually any PC to be used for quick and easy data acquisition and control. It connects to any standard parallel printer port, and despite its tiny size provides eight analog inputs, four digital inputs, and four digital outputs. [www.electronickits.com](http://www.electronickits.com)

**EVERYTHING NEW w/warranty!** Best prices. Motherboards with CPU 900MHz \$195, custom configured systems. Pentium II systems \$225. Pentium III systems \$349. Modems, multimedia kits \$29, scanners, monitors, cases, \$20. Hard drives to 200 gigabytes. 540 megabyte \$15. Call 714-778-0450. Email: [ccis@surfside.net](mailto:ccis@surfside.net)



**850MHz AMD Duron computer system.** 40 gigabyte hard drive, 52X CD-ROM drive, 128MB memory, 64MB video, 2 USB ports in back and 2 in front, LAN, 56K modem/voice/fax, sound, speakers, keyboard, mouse, ATX case, many FREE applications, 2 year warranty! \$379. Visa/MasterCard/Amex/Discover, order toll free 1-877-882-0431, or online [www.saveware.com](http://www.saveware.com)




**PLAY BACKUP COPY of Sony Playstation CD.** Plug-in GAME ENHANCER \$25 or solder-in mod-chip \$15! You don't need the original to play backup! Sony Playstation 2 plug-mod \$49. Visa/MasterCard/Amex/Discover, order toll free 1-877-882-0431, [www.saveware.com](http://www.saveware.com)

## COMPUTER SOFTWARE

**KEYSTROKE LOGGER:** This new software hides in the background on your computer allowing you to view what other people have been doing on the installed computer. Great for monitoring the children or the wife. [www.spousewatcher.com](http://www.spousewatcher.com)

**LIQUIDATION WINDOWS** 95/98/2000, Office suites \$10-69. Windows companion \$5. Windows tutorials \$5, Norton bonus PACK \$15. 714-778-0450.

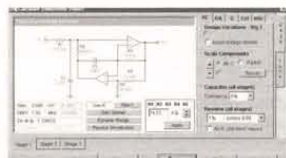**FREE!!! CD-ROM** and software disk catalog. **MOM 'N' POP'S SOFTWARE**, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. [momnpop@gate.net](mailto:momnpop@gate.net)



**WWW.SCHEMATICA.COM** FOR professional freeware and shareware. Active and passive filter design, 555 designer, linear simulators.

**CAM & MOTION SW/HW:** NC Z-trace I.22, PCB tool path. Plotcam motion control. <http://www.ddt-us.com>

## COMPUTER EQUIPMENT WANTED

**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

**6809 GIMIX CPU** card wanted. Doctor Gordon 305-653-8000. Office 301. 16800 NV 2nd Ave., Miami, FL 33169.

## TEST EQUIPMENT

**KENTRONIX TEST EQUIPMENT SPECIALS.** Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to buy test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3229 or FAX 732-681-3312. E-Mail: [brian@kentronix.com](mailto:brian@kentronix.com)

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

**TEST EQUIPMENT** technicians needed: calibration and repair techs. Three full-time openings. Our company sells, rents, repairs, and calibrates HP and Tek. We are located in Broomfield, Colorado, between Boulder and Denver. We perform electronic and physical/dimensional calibrations. Please send resume to [irl@calibration.com](mailto:irl@calibration.com)

**CHECK OUR** growing line of audio test instruments: data sheets, user guides, software. TDL Technology, Inc., [www.zianet.com/tld](http://www.zianet.com/tld)

**A-COMM ELECTRONICS:** we buy and sell test equipment. <http://www.a-comm.com> 11891 E. 33rd Avenue, Aurora, CO 80010. Tel: 303-341-2283, fax 303-341-2293.



**POCKET TESTBENCH.** inexpensive RS-232 virtual instrument, with oscilloscope, logic analyzer, counter, and generator modes. [www.oricomtech.com](http://www.oricomtech.com)

**GIANT DIRECTORY ONLINE:** Over 500 dealers in used test equipment, used semiconductor production equipment, surplus lasers, optics, vacuum equipment, etc. Test equipment auction and rental sites, US and foreign dealers, manual dealers, too! No registration or cookies. [www.big-list.com](http://www.big-list.com)

**CABLE WIZARD** Universal CableMeter & Fault Locator™, Model 321 quickly measures "open" length on most coax, twisted, semi-twisted, single-pair and multi-pair cable, on spools, in boxes, or already installed, also measures distance to "open" faults. For further information write or fax **CABLE DYNAMICS, PO BOX 34594**, Phoenix, AZ 85067, fax 623-931-6262.

## SECURITY

**ALARMLAND.COM SECURITY** devices for professionals. Motion detectors, panels, contacts, CCTV, and more. Fax your order to 732-840-1390.



**THE TLC-I** records automatically all telephone conversations up to 12 hrs. on a single tape, \$79. The **FMX-I** detects and locates bugging devices, \$69. The **TLP-I** stops others from listening in or recording your telephone conversations, \$49. Send check to Yakis, 2930 Pine Ave., Niagara Falls, NY 14301. Buy wholesale directly from manufacturers.



**COUNTER-SURVEILLANCE=\$250 HR!** Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: **1-800-732-5000**. [HTTP://WWW.SPY-CITY.COM](http://WWW.SPY-CITY.COM)



**INFRARED CAMERA for underwater or all-weather use, AX-808 (B/W) or AX-808-C (color).** Designed for lake water to depths of 85 feet. Enclosed LEDs illuminates up to a distance of 20 feet. 12 volt operation. **Color \$149, B/W \$99.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)

**SECURITY DISTRIBUTORS** needed for our complete line of products. See our product features in the center color spread on page 79. [www.matco.com](http://www.matco.com) and call **1-800-719-9605**.

**SURVEILLANCE EQUIPMENT:** Micro video cameras, tele-recorders, counter-spy and more. Direct from manufacturer. Buy direct, why not! Check out our great deals at [www.mjelectronics.com](http://www.mjelectronics.com) Phone 914-699-2294 open 7 days late.



**2.4GHz WIRELESS transmitter/receiver kit. ASK-2008-TR.** 8 frequencies up controlled 2.300 to 2.481 MHz, video NTSC/PAL with 2 channels of audio for development testing. 12VDC/100 mA for both transmitter and receiver. Includes 2 rubber duck antennas. **\$125.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**9 VOLT IR sensitive B/W high res 430 TVL camera** with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; works from **7.5-13 VDC**, highest voltage range in market. 0.08 lux, 1.27" x 1.27" x 0.5" D pinhole or 1" deep standard. **\$49 each.** Enclosure: \$8; optional lens: \$18. Dealers welcome. Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**AS-1004 WIRELESS 2.4GHz, FCC approved.** 2.4GHz transmitter & receiver with audio! Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 400 TV line. **Reduced price! \$179/system.** Additional cameras, \$110/ea. Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**CCD BULLET CAMERAS B/W & COLOR.** AX-800 series, weather resistant high impact design with swivel bracket. Will work with Matco's scanning motor. 3/4" diameter x 3" long approx. B/W: 400 line/0.2 lux. **\$79/each.** Color: 350 lines/2 lux, **\$119/each** — price reduction. Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**40 DAYS and 40 NIGHTS RECORDER.** Time lapse, with remote, can be activated by either contact closure or continuous duty operation with standard T-120 tape. **Models from \$349-\$529.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**SCANNING MOTOR — A-330SC** with universal mounting bracket accepts all standard 1/4 x 20 threaded CCTV cameras. No tilt, just PAN. 75 degrees of continuous motion with a scan rate of 5 seconds per cycle. 110 volt indoor operation, but can be adapted for outdoor use. Includes 12 foot power cord. Perfect solution to triple your effective camera viewing angle! **\$39/each,** or **\$25/each** in qty. of 4. Small size, 3-1/2"D x 2"H. Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**WEATHER RESISTANT OUTDOOR CAMERAS.** VVR-700 type, high impact tempered glass with stand. Black & white (430 lines), or color (420+ lines) available. Standard 3.6mm lenses with optional lenses of 6, 8, and 12 mm at \$20 extra. **B/W \$119/each. Color \$179/each.** Small compact size with sun shield. Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**INFRARED FILTER ELIMINATES 99.9% OF ALL VISIBLE LIGHT — IR-9000.** All B/W CCD cameras are IR sensitive. Place a 25 watt or less light behind the 3" x 3" filter, and you will see in the DARK. **\$18/each.** Purchase 2 for \$30. Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)

**SEE THE NEW MATCO PRODUCT FEATURES AND PRICES** in the color center spread on page 79.



**5" AND 5.5" LCD high definition color monitors w/stereo.** 960 x 240 pixels w/brightness and tint controls. Attractive enclosure with built-in speaker. Great for security or general purpose use. Both models have a small compact footprint, with an ultra-bright display, RCA inputs NTSC or PAL. Special price with regulated power **\$249/each.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**COLOR & B/W board cameras** w/cases, BX-120-LC (350 lines color) \$89; BX-125-LC (380 lines color) \$99, sub-miniature BX-123-AU (420 lines B/W with audio) \$69. Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**VGA TO COMPOSITE (NTSC/PAL) VIDEO CONVERTER — ULT-2000.** Small foot-print. Powered from keyboard with S-video and RGB outputs, too. 3:1 optional zoom control, simultaneous outputs with many extras. **\$99/ea.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)




**16 CHANNEL MULTIPLEXER MUX-1600.** Display 4, 8, and 16 video outputs directly on a TV or security monitor. This is the only device which allows full screen display of video on VCR playback (see 40 days and 40 nights recorder). Plenty of options including tilting, zoom, individual gain adjustments, etc. **Reduced price! \$799/each. Special 4 channel version, MUX-400, \$429/each.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**14" B/W high resolution SECURITY MONITOR.** A standard 12" monitor is just too small for most applications. Attractive dark gray enclosure with audio and built-in speaker. 75 ohm termination switch for balancing with all types of CCD board cameras and other video inputs. **\$139/each.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**14" COLOR — high resolution SECURITY MONITOR w/4 channel switcher.** High impact enclosure with modern front panel 4 channel video and audio switcher. High quality speaker built-in. Components purchased separately would exceed \$500. Price slashed to **\$249/each.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)

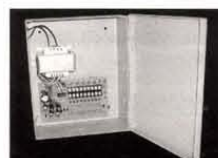

**CAMERA DISTRIBUTION Box. XF-250-DC/XF-250-AC.** Connect your cameras directly to power source with screw terminals or plug in using a 2.1 mm connector. **Special price: \$59 (DC version) and \$49 (AC version).** Can use pre-molded 50 foot video/power cable A-402-CA \$15. Matco, Inc., Schaumburg, IL, 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)

**SURVEILLANCE-COUNTERSURVEILLANCE:** I buy and sell used equipment. Steve 410-879-4035.



**WIRELESS COLOR rechargeable 2.4GHz system.** ASK-7003-TR. 150 foot range. Includes camera/transmitter, receiver and built-in battery pack with charging system. Range 150 feet. **High volume seller!** \$159. Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)



**QUAD PROCESSOR works with VGA monitor.** QVS-104-CV. NTSC inputs, composite outputs as well as output for direct connection to VGA monitor. Saves cost of expensive high-grade security monitor. \$269. Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)

**KEYSTROKE LOGGER:** This tiny piece of hardware installs between your keyboard wire and computer in seconds. Then it logs all keystrokes, which you can view at your convenience. [www.spousewatcher.com](http://www.spousewatcher.com)

## SATELLITE EQUIPMENT

**SATELLITE REPORT:** Find all the latest in satellite descrambling in this 54-page report. Lists all the cheapest and reliable sources for hacked cards and equipment. [www.electronickits.com](http://www.electronickits.com)

**SATELLITE TV.** Complete selection of C & Ku band equipment. [WWW.DAVESWEBSHOP.COM](http://WWW.DAVESWEBSHOP.COM)

**REVERSE ENGINEERED** schematics is our business. Each month we have been placing one of our 21 catalogs of prints on our website. This month it is cable and satellite prints. **Bomarc Services** rollo@trib.com **bomarc.org**

## MILITARY SURPLUS ELECTRONICS

**DOSIMETERS/RADIATION DETECTING KITS.** New Canadian military surplus, now illegal to import due to recent change in Arms Control laws. Ten dosimeters, two chargers, two radiation meters w/carrying cases. Single D cell powers chargers and meters. Survival, nuclear war, nuclear power plants. \$125 shipped US. Credit cards, checks. Dealers/quantities welcome. Steve 410-879-4035 or Steve@swssec.com

## AUDIO — VIDEO — LASERS

**STUDIO GEAR,** antique radios, tubes, pro video, and unusual collectibles at [WWW.bibbtek.com](http://WWW.bibbtek.com) Call Tom @ 856-222-0636, fax to 856-222-0638 for printed list. Credit cards welcome.

**SYNC-A-LINK UNIVERSAL video sync generators.** Phone 918-479-6451, Email: rlc@sstelco.com **Sync-A-Link**, PO Box 4, Locust Grove, OK 74352.

**COPPER BROMIDE** laser system 2.5W yellow, 5W green, 8 watts total. Norseld Cub D10 Medical laser. May be incomplete. More info @ [industrialswap.com](mailto:industrialswap.com) Make offer! 541-791-4411 ed4surplus@aol.com



**STEREOSCOPIC VR 3D generator.** 918-479-6451, email: rlc@sstelco.com. **Sync-A-Link**, PO Box 4, Locust Grove, OK 74352 USA.

**NEED POWER** supplies for: Coherent CR3000K super graphite ion laser, Spectra Physics 171 ion (Krypton) laser, Spectra Physics 125 He Ne laser. Also need any manuals, schematics, related materials on these lasers and their power supplies. Call, fax, or leave message John 801-964-6641.

## CABLE TV

**REVERSE ENGINEERED** schematics is our business. Each month we have been placing one of our 21 catalogs of prints on our website. This month it is cable and satellite prints. **Bomarc Services** rollo@trib.com **bomarc.org**

**CABLE CONVERTERS.** Brand new Viewmaster, Media Tech. Latest technology. Blowout wholesale prices. Guaranteed, ready to go. Call for flyer 412-833-0773.

**CABLE REPORT:** This 50 page report contains all the latest in how cable systems have been compromised. Including cheap and reliable sources for test chips and equipment. [www.electronickits.com](http://www.electronickits.com)

**CABLE PARTS!** Computer parts. Call for great prices or visit us on the Web: [WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

**POSITIVE AND** negative cable TV filters. [www.gofilters.com](http://www.gofilters.com) 1-800-235-8080. Mike is back, give us a call. We can help in all situations.

**CABLE TV converter wholesaler.** Brand new 125 channel converter, 10 lot \$45. Unmodified DPV 7212 \$19.95, SA 8600 \$25. Call us for lowest prices on other models such as BB, CFT, Pioneer, SA 8580. Dealers only, 1-888-860-6365.

**CABLE PARTS for all makes and models, raw boxes at low prices.** Call 1-888-817-8100. No NY sales. [www.chipplace.com](http://www.chipplace.com)

**DIGITAL CABLE TV** converters. Factory original General Instruments/Motorola, DCT 1234/1151/ABCDEFH/R2. Many other models available! We sell raw, unmodified units only! Call 763-684-4325. 9 to 5, M-F, CST.

**CABLE TV CONVERTERS.** Wholesale pricing, full warranties. SA 8580 \$20, SA 8600 \$25, GI DPV7 \$20, GI BB/CFT \$30, CFT 2254 \$40. Free shipping nationwide. 10 lot minimum orders. 125 channel MASTER-PIECE converters \$43 delivered case lot only. CODs welcome. Converters, parts and accessories. Call toll free 877-915-3727.

## TELEPHONE/FAX

**PHONE MANAGER:** This unit looks exactly like a Caller ID, except it records time, date, and length of all outgoing calls. [www.spousewatcher.com](http://www.spousewatcher.com)

## COMPONENTS

**ELECTRONIC KITS,** components, meters, software. School/club discounts. Hard-to-find items. Authorized ECG/NT distributor. Call J-Tron 1-888-595-8766, [www.j-tron.com](http://www.j-tron.com)

**WANT TO Buy:** ICs, military & aircraft relays, diodes, transistors, connectors, tantalum capacitors, electronic test equipment & most components. Hoffer Electronic Ent., E-Mail: [Hoffer1165@aol.com](mailto:Hoffer1165@aol.com) 818-718-1165, FAX 818-341-5506.

**PELTIER INFORMATION DIRECTORY ONLINE:** Information site on Peltier devices (thermoelectric cooler/heater/generator modules). Tips, manufacturer directory, surplus sources, etc. Free. No registration. [www.peltier-info.com](http://www.peltier-info.com)

**COMPONENT BLOWOUT!** Low low prices on ICs, capacitors, transistors, diodes, resistors, connectors, switches, pots, + computer accessories. Unbelievable low prices, free catalog, Abbott Electronics, 155 New Boston St., Woburn, MA 01801. T 781-935-2040 F 781-933-7127.

**ELECTRONIC COMPONENTS, kits, test equipment, books, tools, and supplies** for hams, hobbyists, and businesses. Many hard-to-find items like variable capacitors, vernier dials and drives, coil forms, magnet wire, toroids, more. [www.oselectronics.com](http://www.oselectronics.com)

**RF TRANSISTORS, TUBES, TEFLON WIRE, SILVER MICA CAPS.** 2SC2290, 2SC2879, SD1446, MRF455, MRF454, 2SC1969, 2SC2166, 2SB754, TA7222AP, 2SC2086, TA7222AP, MRF247, MRF317, SAV7, etc., 4CX250B, 4CX1000A, 4CX1500B, 3CX400A7/8874, 3CX3000A7, 4CX400A, 572B, etc. Teflon wire specials 1,000 ft. 16 gauge .15 cents ft., 1,000 ft. 18 gauge .14 cents ft., silver mica caps, resistors, see our catalog for other products. Westgate 1-800-213-4563.



**SWITCH SUPERMARKET** large variety toggle, rotary, LEDs bipolar 2 & 3 leads, grain of wheat, free list. Fertik's, 5249 "D" St., Philadelphia, PA 19120. Ph/fax 215-455-2121.

**MATCO WILL design, engineer,** and develop a 2.4GHz wireless 8 channel solution for your remote applications. FCC approved. Matco, Inc., Schaumburg, IL 1-800-719-9605. E-Mail: [nsales@matco.com](mailto:nsales@matco.com) Web site [www.matco.com](http://www.matco.com)

**MP820 POWER FILM RESISTOR** in a TO-220 package, 20 watts, 820 ohm, 5%, small size. Great for switching power supply designs. 6,000 pcs. available — 100 pcs. @ \$0.25 ea., 1,000 pcs. @ \$0.20 ea., all @ \$0.15 ea. Full data sheet available in Allied catalog. Call Roger at GS&E, 716-338-7001.

## MICROCONTROLLERS



**PIC & ATMEL PROGRAMMERS** from \$15.95 and \$29.95! Visit [www.electron.ics123.com](http://www.electron.ics123.com) for complete details. Amazon Electronics, Inc. Toll free 1-888-549-3749.

**PIC PROGRAMMERS:** Several different programmer kits that you can build yourself all the most popular PIC and Atmel chips. [www.electronickits.com](http://www.electronickits.com)

**PIC DESIGNS DONE CHEAP!** Midwest Micro-Tek, a leader in 8 and 16 bit controller design, is now offering their design services for PIC designs at a low price of \$60/hr for design, routing, and programming. For more info call 605-697-8521. [www.midwestmicro-tek.com](http://www.midwestmicro-tek.com)

**www.dontronics.com THE** world's largest range of AVR & PICmicro hardware and software. Home of the very popular SimmStick™. Hi-Tech PIC C compilers \$100 off. Biggest range of PICmicro/AVR C & Basic compilers from all over the world. Many delivered via a web download. On-line real-time shopping cart. World wide delivery. Microcontroller kits and associated components. Dealer for N&V, CCS, Bascom, Codevision, FED, Hi-Tech, DIY HK, Newfound Warp-13, Tato, Codedesigner, Lawicell, Wirz, Square One, PI6PRO/PICALL Rego, and many more. Customer satisfaction guaranteed.

## ANTIQUE ELECTRONICS

**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

**WESTERN ELECTRIC** wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dilog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 or fax 937-847-2350 or email [buyer@keyways.com](mailto:buyer@keyways.com)

**FOR SALE:** Good used radio tubes. Types 6D6, 41 and 58 \$2, 6A7 and 75 \$4, 80 \$5, 42 \$6. See [www.fathauer.com](http://www.fathauer.com) for list of others or email [tubes@qwest.net](mailto:tubes@qwest.net). George H. Fathauer & Assoc., 688 West First St., Ste. 4, Tempe, AZ 85281. 480-968-7686.

**WANTED: TOP** prices paid for globe shape and collector tubes, new or used. Send for buy list or send your list for offers. Write or email: [tubes@qwest.net](mailto:tubes@qwest.net). See [www.fathauer.com](http://www.fathauer.com) for tubes for sale. George H. Fathauer & Assoc., 688 West First St., Ste. 4, Tempe, AZ 85281. 480-968-7686.

## AVIATION ELECTRONICS

**KINGSLEY HOTSTAMP** foil machines for imprinting leather, etc., and electrical wire marking. Manual or automatic machines and type available. Call 760-749-0239. [bjnash@n2.net](mailto:bjnash@n2.net)

## PUBLICATIONS

**HIGH-TECH SURVIVAL:** Electronics, computers, internet, energy, phones, medical, financial, security, physical survival, unexplained phenomena. **CONSUMERTRONICS.** [www.tsc-global.com](http://www.tsc-global.com)

**BASIC STAMP 2 users:** "Inside the BASIC Stamp II" tells how the PBASIC interpreter works, how code is stored in EEPROM, how to optimize code for space and speed. 160 pages, 50 illustrations, many examples. See <http://members.aol.com/stamp2book> Send \$29.95 check or money order (US funds) to Brian Forbes, 147 Flying Cloud, Foster City, CA 94404-1301.

## ROBOTICS


**SEIKO D-TRAN** RT2000 in a dust proof enclosure. Includes teach pad. Asking \$2k FOB So Cal. 541-791-4411 [ed4surplus@aol.com](mailto:ed4surplus@aol.com) Web [industrialswap.com](http://industrialswap.com)

**ROBOT KITS:** Over 30 complete robot kits from beginner to advanced at [www.electronickits.com](http://www.electronickits.com)



**MOTOR CONTROLLERS, PWM, 12V, 24V, 35A,** many features from \$40 plus S&H. Info: 570-735-5053. Details: <http://www.diverseelectronicservices.com> Toll free orders (only) 1-888-314-6998.

**ROBOT WEAPONS** control. PIC controlled circuit boards use standard RC signals to turn any device up to 10A on or off. Selectable momentary or latched modes. Control motors forward or reverse. Four models control from 1 to 3 devices. On board diagnostic LEDs. Input 9 to 24 VDC. 5V output for RC receivers eliminates battery. Info: 570-735-5053 or [www.DiverseElectronicServices.com](http://www.DiverseElectronicServices.com)

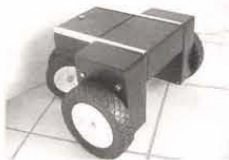

**MOBILE ROBOT PLATFORM.** Been wanting to build a powerful robot but don't know where to start? This 15" x 19" x 10" robot platform includes chassis body with four compartments, two-speed high-torque motors, large 8" drive wheels, and 6" rear swivel wheels. Plenty of surface area for adding sensors, cameras, etc. Only \$239 plus S&H. Mention this ad for a \$40 discount. Ph: 321-757-9280 or online: <http://www.kadtronix.com>.



**12V HIGH-TORQUE MOTOR & WHEEL.** Need a drive system for your robot or cart? This high-torque motor and 8 inch wheel are the answer. Motor has worm-gear drive and two speeds. Hook-up specs included. Only \$59 plus S&H. Mention this ad for a \$10 discount. Ph: 321-757-9280 or online: <http://www.kadtronix.com>

**PIC-BASED** controller boards and coprocessors for small bots, singleboard computers and other prototyping components. [www.oricomtech.com](http://www.oricomtech.com)



**ROBODYSSEY SYSTEMS, LLC,** Mobile Robotics. Robodyssey™ Systems, LLC has three new mobile robotics platforms — built to last, laser cut anodized aluminum; drilled and tapped mounting points require minimal hardware; control methods include Stamp™, tether, or analog. Designed to meet requirements of RobotMelee™ (see <http://dpein.home.net.com>), IEEE MicroMouse, F-180 Small Size RoboCup, Trinity College Fire Fighting Home Robot, or Beam. Contact: [sales@robodyssey.com](mailto:sales@robodyssey.com) [www.robodyssey.com](http://www.robodyssey.com)

**ROBOT BOOKS.COM** visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! [www.robotbooks.com](http://www.robotbooks.com)

**EASY RC.** Preprogrammed PIC accepts standard RC pulses and sends control signals to motor controller for direction and proportional speed control. Single channel or dual channel with mixing available. Info: 570-735-5053. <http://www.diverseelectronicservices.com> email: [carl@diverseelectronicservices.com](mailto:carl@diverseelectronicservices.com)

**SEIKO D-TRAN RT3000** asking \$2k ea OBO qty available FOB So Cal. 541-791-4411 [ed4surplus@aol.com](mailto:ed4surplus@aol.com) Web [industrialswap.com](http://industrialswap.com)

**ARobot KIT** from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/arobot>

## CNC

### AFFORDABLE CNC MACHINES



Simple to Use

Run From Any Version of Windows®

[www.flashcutcnc.com](http://www.flashcutcnc.com)

Automated Machine Tools to Produce  
• Panels • Chassis/Housings  
• PCB Prototypes • Any 3D Part

**FLASHCUT CNC™**

1263 El Camino Real, Menlo Park, CA 94025  
4949 St. Elmo Avenue, Bethesda, MD 20814  
Tel 888-883-5274 Fax 650-853-1405

## PLANS — KITS — SCHEMATICS

**ELECTRONIC KITS:** Hundreds of electronic kits and projects. Where else except [www.electronickits.com](http://www.electronickits.com)

**AMAZING KITS,** remote control, motor controllers, PIC experimenter boards. Fun and educational. Quality guaranteed. [www.dlrkits.com](http://www.dlrkits.com)

**HIGH-TECH SURVIVAL:** Electronics, computers, internet, energy, phones, medical, financial, security, physical survival, unexplained phenomena. **CONSUMER ELECTRONICS.** [www.tsc-global.com](http://www.tsc-global.com)

**ELECTRONIC KITS,** components, meters, software. School/club discounts. Hard-to-find items. Authorized ECG/NTE distributor. Call J-Tron 1-888-595-8766, [www.j-tron.com](http://www.j-tron.com)

**PLANS, BOOKS,** kits, surplus, AM/FM/SVW broadcasting supplies. Online ordering at [www.kenneke.com](http://www.kenneke.com)

## MISCELLANEOUS ELECTRONICS FOR SALE

**DIASONICS ULTRASOUND DRF400.** Missing probes and? Does have JVC BR6400 recorder, EDX scope. See pix @ industrial swap.com Make offer! 541-791-4411 [ed4surplus@aol.com](mailto:ed4surplus@aol.com) Web [industrialswap.com](http://industrialswap.com)

**HARD-TO-FIND parts:** PTV screens, modules, chassis, flybacks, tuners, tubes, for all brands. Manuals. 478-272-6561. Scarborough TV, 1422 Old River Road, East Dublin, GA 31027. [scarboroughstv@pcnow.net](mailto:scarboroughstv@pcnow.net)

**CLOSEOUT PRINTED** circuit and hybrid assembly operation equipment, flow solder machine, lead form and trim, PC scoring, ovens, misc assembly fixtures, card racks, laser trimmer, etcher, CNC drill. For list ph 1-888-594-7446, fax 724-962-1816 or email [rddblid@HTOL.net](mailto:rddblid@HTOL.net) (Give reply phone number or fax number for listing and information.)

## LedVision Holdings, Inc.



### Scrolling L.E.D. Signs

- Wireless Keyboard
- Includes Windows Software
- Text & Graphics
- Super Bright Multi-Color
- Clock Functions & Scheduler
- Real Time (ASCII) Mode
- 16K Flash Memory
- RS-232 & RS-485 Serial Ports

303 Sherman Ave., Ackley, Iowa 50601

(641) 847-3902 Fax: (641) 847-3889

[sales@ledvision.com](mailto:sales@ledvision.com)

[www.ledvision.com](http://www.ledvision.com)




### SOLAR-POWERED FAN HAT.

Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

## RS485/422/232/TTL

ASC24T \$45

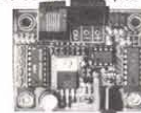

- Converters
- Repeaters
- Fiber Optics
- Digital I/O
- Multidrop RS232
- Custom Units
- Auto TX Enable

### Extensive Interface Product Line

RS232 "Extension Cords"  
Up to 115.2 Kbps, 4000 ft. ++  
Large Multidrop Networks.  
Isolated Units. Smart Units  
Remote Relay "Extension Cords"

Call the RS485 Wizards at  
(513) 874-4796

**RES = R.E. Smith**  
[www.rs485.com](http://www.rs485.com)



### ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE

since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. Wire cut & strip to specs. If interested, please call 1-800-626-7540, FAX: 714-563-8309. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anaheimwire.com> OR E-Mail: [info@anaheimwire.com](mailto:info@anaheimwire.com)

**SELLING ELECTRONICS** parts business! Over 1,000,000 components/assemblies. 30 year inventory (1970-2000). Consumer, industrial, military, medical parts. Call Jobe Electronics, Ph 618-993-6340 Marion, IL 62959.

## Electronics Manufacturing Technology a div. of Ledvision



ISO-9001 Compliant

[www.pcbboardsinc.com](http://www.pcbboardsinc.com)

### Bare Printed Circuit Boards

- Design & Layout
- Single, Double & Multi-Layer
- Automated Assembly**
- SMT & Thru-Hole
- Prototypes Thru Production
- Product Engineering
- Final Assembly & Test

303 Sherman Ave., Ackley, Iowa 50601

(641) 847-3902 Fax: (641) 847-3889

[sales@pcbboardsinc.com](mailto:sales@pcbboardsinc.com)




**PORTABLE CARD SWIPER.** Swipe any card with this incredible tiny device and the complete data on the magnetic stripe is stored instantly in its memory. Stores over 100 swipes at one time. Powered by a small camera battery. It can be use remotely on any type of card with a magnetic stripe. After the magnetic stripe information is saved, you may download the information to any computer or laptop. Applications: data collection, trade shows attendance, conference attendance, classroom attendance and many others. We have many different models and magnetic stripe reader/writers. See our web site: [www.mobilecardreaders.com](http://www.mobilecardreaders.com) Or write for free catalog. The Information Center, PO Box 876, Hurst, TX 76053. 817-589-7891.
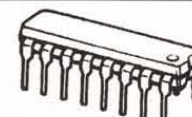
## MISCELLANEOUS ELECTRONICS WANTED

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dilog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 or fax 937-847-2350 or email [buyer@keyways.com](mailto:buyer@keyways.com)

**WANTED: BALANCING** machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanalysis, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.



**WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS; MILITARY COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL LPS 562-439-2453 FAX 562-439-0453.**

**WANTED: TUBES,** radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Monroe Twp., NJ 08831. Phone: 609-395-1116, FAX 609-395-1117.

**UNITEK MODEL DP-125 or DP-250** welder power supplies **WANTED.** 608-831-3443, fax 608-831-1082, ask for Everett.

## Classified Ad Instructions

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

**NUTS & VOLTS MAGAZINE**  
430 Princland Ct., Corona, CA 92879.

### RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00** minimum charge per ad per insertion.

### BOLD WORDS AND/OR CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

### PHOTOS, DRAWINGS, BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos. Photos may be emailed to [clasad@nutsvolts.com](mailto:clasad@nutsvolts.com).

### EMAILING/FAXING AD COPY

You may email or fax in ad copy or changes before the closing date (5:00pm on the **5th**) using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your *Nuts & Volts* account number. Email ad(s) to [clasad@nutsvolts.com](mailto:clasad@nutsvolts.com) or fax to 909-371-3052. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL, EMAIL, OR FAX BACK VERIFICATION OR QUOTES OF EMAILED AND FAXED-IN ADS.** For verification of emailed or faxed-in ads, please call 909-371-8497.

### DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

### IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in *Nuts & Volts* is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the **60¢** rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you *clearly* print or type your ad copy.


*Choose a category for your ad from these classifications.*

- |                                  |                                 |
|----------------------------------|---------------------------------|
| 10. Ham Gear                     | 125. Microcontrollers           |
| 20. Batteries/Chargers           | 130. Antique Electronics        |
| 30. CB/Scanners                  | 135. Aviation Electronics       |
| 40. Music & Accessories          | 138. Thermocouple Welder        |
| 50. Computer Hardware            | 140. Publications               |
| 60. Computer Software            | 145. Robotics                   |
| 70. Computer Equipment Wanted    | 148. CNC                        |
| 80. Test Equipment               | 150. Plans/Kits/Schematics      |
| 85. Security                     | 155. Manuals/Schematics Wanted  |
| 90. Satellite Equipment          | 160. Misc. Electronics For Sale |
| 95. Military Surplus Electronics | 170. Misc. Electronics Wanted   |
| 100. Audio/Video/Lasers          | 175. BBS & Online Services      |
| 110. Cable TV                    | 180. Education                  |
| 115. Telephone/Fax               | 190. Business Opportunities     |
| 120. Components                  | 200. Repairs/Service            |

**WESTERN ELECTRIC** wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

**REQUIRED: IC** chip ICM 72051 PG w/24-pin printout. Used for stopwatch ckt. 949-494-0072.

## BUSINESS OPPORTUNITIES

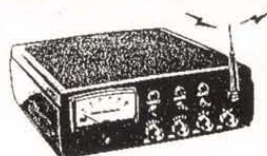

**COUNTER-SURVEILLANCE=\$250 HR!** Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn **\$250 HR** in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: **1-800-732-5000**. [HTTP://WWW.SPY-CITY.COM](http://WWW.SPY-CITY.COM)

**AFFILIATES WANTED:** If you have a website you can earn a 10% commission for every person that you refer to our site. See complete details at [www.spousewatcher.com](http://www.spousewatcher.com)

## EDUCATION

**FREE CONTROL and embedded systems tutorial.** [www.learn-c.com](http://www.learn-c.com) Optional interface board for hands-on learning. Eight 8-bit AD, two 8-bit DA, 27 digital lines and more. Bare board only \$20. Kits and assembled available.

**MAGICIAN IS** available to solve your RF problem. I will teach you in my laboratory how to do it. Young engineers and technicians are welcome. SMT prototyping up to 3GHz for customers. Minaret Radio, John Horvath ph: 909-943-3676. Ask for my resume.

## REPAIRS — SERVICES

**(E)EPROM PROGRAMMING** done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

**MECH ENGINEERING CONSULTING:** machine design & packaging from conceptual to manufacturing: detailing, bill of mat'l, part procurement, & proto build. **GSC, MECHANICAL ENGINEERING SERVICES 508-339-7837** or email: [SECGSC@aol.com](mailto:SECGSC@aol.com). (Ask for Greg.)

**SPECIAL PROJECTS HARDWARE:** Unique, original, made-to-order, special needs, controversial: power meters educational module, automated control signal replicator, KX radar emitter, radionics rife, subliminal mixer/amp, unseen/unknown presence detector, "aura" detector — many, many more! **LONE STAR CONSULTING, INC., [www.lonestartek.com](http://www.lonestartek.com)**

**CIRCUIT BOARDS** for projects, prototypes, or short runs. From your artwork. Low rates. No minimum order. Atlas Circuits 704-735-3943. Email: [atlas@conninc.com](mailto:atlas@conninc.com)

Subscribe to Nuts & Volts  
[www.nutsvolts.com](http://www.nutsvolts.com)

Stamp listing continued from page 49

```
Calc Direction:
FOR idx = 0 TO 3
    direction.LowNib(idx) = romData(idx * 2 + 1) / 90
NEXT
' convert word to 1 of 16

dFlag = 99
LOOKDOWN direction, [$2220,$1220,$1222,$1122,$2122,$2112,$2212,$2211], dFlag
IF (dFlag < 8) THEN Show_Direction
' found in first table

LOOKDOWN direction, [$2221,$0221,$0222,$0022,$2022,$2002,$2202,$2200], dFlag
dFlag = dFlag + 8
' adjust for second table

Show_Direction:
DEBUG MoveTo, 19, 8
eeAddr = BadDir
IF (dFlag < 16) THEN Good_Dir
GOTO Dir_To_Screen
' found in either table?

Good_Dir:
eeAddr = WindDir + (6 * dFlag)
' address of direction string

Dir_To_Screen:
GOSUB Print_String
GOTO Main2

' *****
' Print a right-justified number
' *****

RJ_Print:
rjSign = rjNum.Bit15
rjNum = ABS(rjNum)
digits = width
LOOKDOWN rjNum, [0,10,100,1000,65535], digits
DEBUG REP " \ (width-digits-1), 13 * rjSign + " ", DEC rjNum
RETURN

' *****
' Print string at current cursor position
' -- point to string with eeAddr
' -- string is zero-terminated
' *****

Print_String:
READ eeAddr, char
IF (char = 0) THEN Print_String_Done
DEBUG char
eeAddr = eeAddr + 1
GOTO Print_String
' get character from EEPROM
' if 0, string is done
' print it
' point to next character

Print_String_Done:
RETURN
```

# AMATEUR ROBOTICS

## Wiring and Testing the PDM Chassis

By Robert Nansel

**T**his month and next, I'll show you how to wire and test the Power Drive Module (PDM) chassis.

The PDM chassis holds the chopper board, the power supply, fans, and assorted connectors, switches, fuse holders, and indicators. It's not a complicated job, but if you've never done chassis wiring, there are an awful lot of individual wires to keep track of — over 50. I'll show you ways to keep it all from turning into a tangled ball of wire, as well as techniques to reduce EM/RF interference in the process.

As promised, this month I also have the winner of the Third Lonely Gearhead Contest: Congratulations to Eric Daine of Haddock, GA. Send me an e-mail telling me where you would like your Solarbotics BEAM experimenter board shipped.

I got a terrific response to this contest, particularly regarding the list of robotics clubs. In fact, I got so many new listings for robotics

clubs, that I don't have enough room for them this issue. Instead, I'll give the list of individuals looking for clubs this time and the club list next time. Thanks to all who sent in their information. (Even with splitting the lists up, I still had to edit down the thoughtful notes many of you sent to get them to fit; if your comments shown here aren't quite what you remember sending, that's why.)

Let's get down to wiring.

Figures 1 and 2 and the wiring table give road maps for all the chassis wiring. Figure 1 covers the DC power supply circuitry, and Figure 2 gives details of power distribution and chopper board wiring. Photocopy the figures and the wiring table, and as you wire the chassis, use a highlighter to mark each connection you make.

For clarity, the LED indicators have been omitted from Figure 2. All components — with the exception of the LEDs — are wired so they may be removed from the

chassis without unsoldering or cutting wires. This makes it much easier to troubleshoot and maintain the unit. The LEDs will be the last items to be wired in the chassis, after everything has checked out.

### Mounting the Transformers


First, prepare the two transformers by either trimming or folding the unused leads as shown in Photo 1. The ends of these lead must be insulated to prevent short circuits and shock hazards since 110 and 220VAC will be present on the high-voltage side of both transformers. There are two unused leads on each transformer. The unused lead on the primary side is the "top" red lead — the 220V tap as shown on the label on the transformer, and on the secondary side, the middle yellow lead is unused. Crimp .35" closed-end nylon crimp connectors on the unused lead ends. If you intend to fold the lines rather than cut them short, be sure to secure them with nylon cable ties.


Next, sand to bare metal both surfaces of what will be the upper mounting tab of one of the transformers. This tab will serve as the chassis safety grounding point and must make good electrical contact with both the chassis on one side and the ground strap on the other.

To make the ground strap, crimp a #10 stud ring-tongue terminal on the stripped end of a 3" length of 18 AWG stranded wire; this end will attach to the bare metal of the mounting tab. Crimp a 1/4" female quick disconnect terminal to the other end of the wire; this end will attach to the safety ground tab of the power entry module.


Each transformer mounts sideways in the chassis with its label side up (Photo 2). The transformer with the sanded tab mounts on the right side of the case (left in the photo). You can either use #10 machine screws or 3/16" pop rivets, but if you intend to paint the chassis, use screws for the time

**Figure 1**

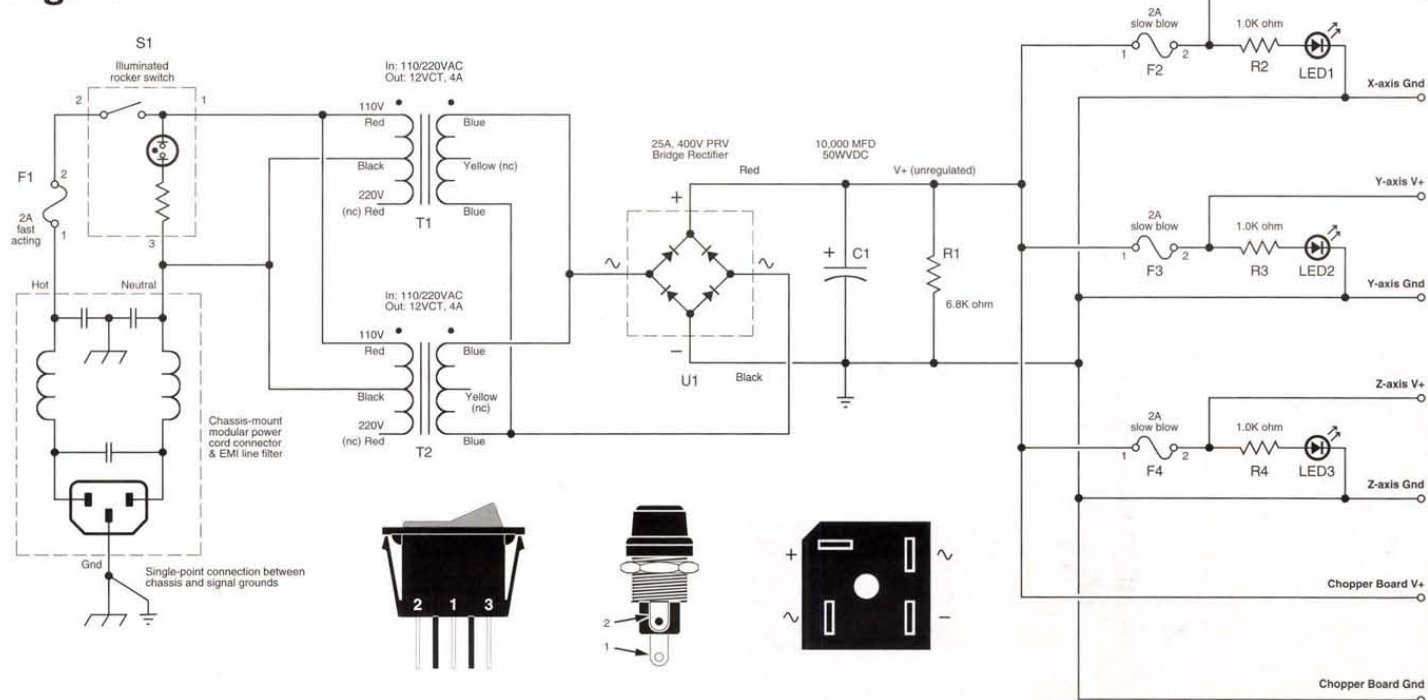

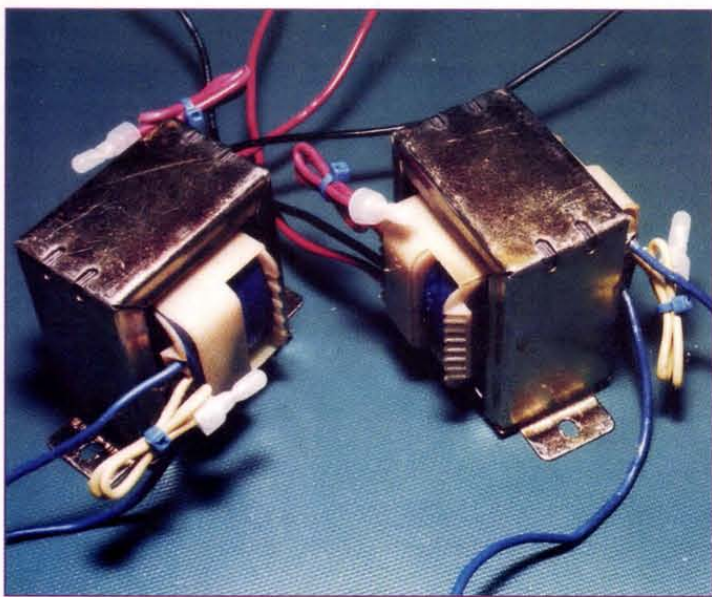

**Photo 1.** Transformers ready for installation. Unused wires are insulated with closed-end crimp connectors, then neatly bundled and tied with nylon cable ties.

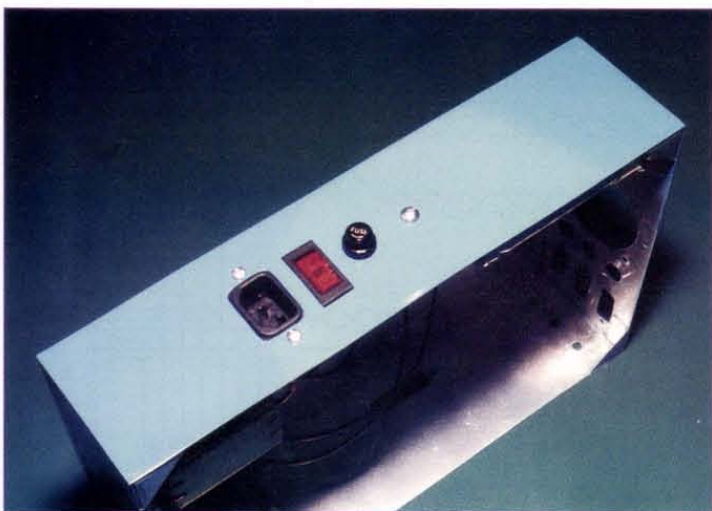

**Photo 3.** Chassis exterior, right side, showing power entry module, lighted power switch, and main fuse. The chassis has undergone many hours of sanding, multiple primer and paint coats, with yet more sanding between coats. After the power supply, chopper board, and all connectors are wired and installed, I'll temporarily remove everything and label the chassis.

being. In the photos, I've already painted my chassis but haven't yet done the labeling, so I use screws. If I were doing it over, I would delay painting until all of the wiring was done and all of the chassis components were removed. (More on paint next time.)

### Wiring the Primaries


Twist the stripped ends of the remaining red transformer leads together with a 4" length of red 18 AWG stranded wire and crimp them together in a .44" closed-end nylon connector. Crimp a 1/4" fully-insulated quick disconnect terminal to the other end of the 4" wire. This terminal connects to the middle terminal of switch S1, labeled "1" on the switch.

The black transformer leads get twisted and crimped together


with two 4" lengths of black 18 AWG stranded wire. Crimp 1/4" fully-insulated quick disconnects to the free ends of these wires. One wire connects to "neutral" on the power entry module and the other wire connects to terminal "3" of S1.

Install the power entry/EMI filter module next, oriented label-up (or safety-ground-down) and secure with two 6-32 x 3/8" pan-head screws, lock washers, and nuts. Installed this way, the "hot" terminal is toward the front of the chassis, and "neutral" is toward the back.

Next, snap in the power switch with the terminal labeled "3" toward the front (use a small straight-blade screw driver to separate the mounting ears). Remember, the chassis front is the closed side, while the

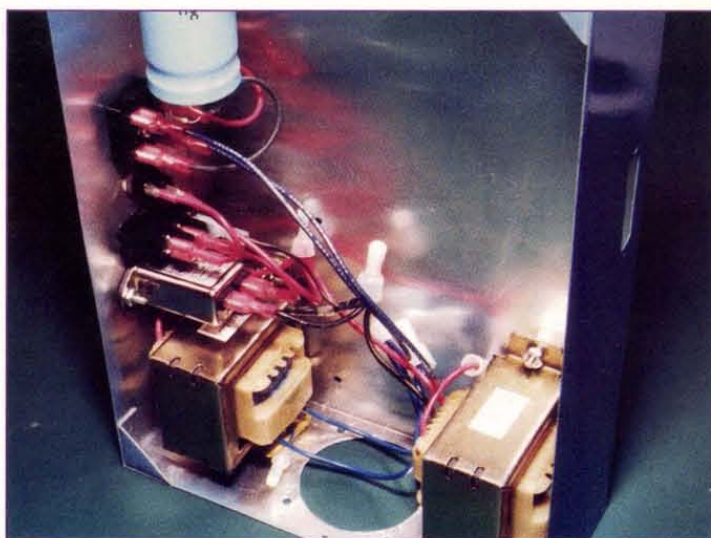

**Photo 2.** Power supply components installed in chassis. All connections to the transformers are made with closed-end crimp connectors, but all connections to the power entry module, switch, and rectifier bridge are made with insulated 1/4" quick disconnects. This way, all components can be changed out from the chassis without unsoldering or cutting any wires.

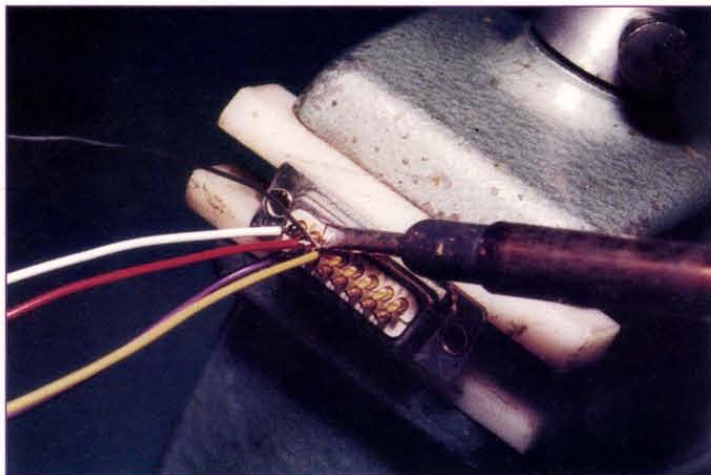

**Photo 4.** Wiring up one of the 15-pin axis connectors. I use solid wire for the stepper motor phases and stranded wire for the limit and home switches.

back is the open — or cover — side.

Now comes the main fuse holder. Note that in the preliminary schematic (September 2001 issue), the main fuse was shown connected between S1 and the transformers. For improved safety, I've since moved the fuse to between power entry "hot" and S1 terminal 2 so that S1 does not light when the fuse F1 is blown.

Prepare the fuse holder by soldering the stripped end of a 4" length of red 18 AWG stranded wire to terminal 1 and a 3" length of the same type wire to terminal 2 (see Figure 1). Slip 3/4" lengths of 3/16" diameter heat shrink tubing completely over the terminals and solder joints, and apply heat to shrink the insulation in place. Complete the fuse assembly by crimping 1/4" quick disconnects as above to the free ends of these wires.

Feed the wires and fuse holder through the panel mounting hole, slip the nut on, and tighten. The



longer wire (terminal 1) connects to the "hot" terminal of the power entry module, and the short wire (terminal 2) connects to S1 terminal 2. Connect the rest of the primary circuit up per Figure 1 and the wiring table. Don't forget the safety ground lead.

### Wiring the Secondaries

Before wiring the secondaries together, you should: **1)** Check continuity of all the wiring so far, highlighting all the connections on the schematic as you go (preferably with another highlighter color); **2)** Determine the phasing of the secondary windings. The latter step is a good idea even if you are using the exact transformers I specify because the consequence of wiring the secondaries backward — anti-parallel instead of parallel — is likely to be smoke.

With the transformers specified, the secondary wires are blue. For both transformers, temporarily connect with an alligator clip lead

# Figure 2

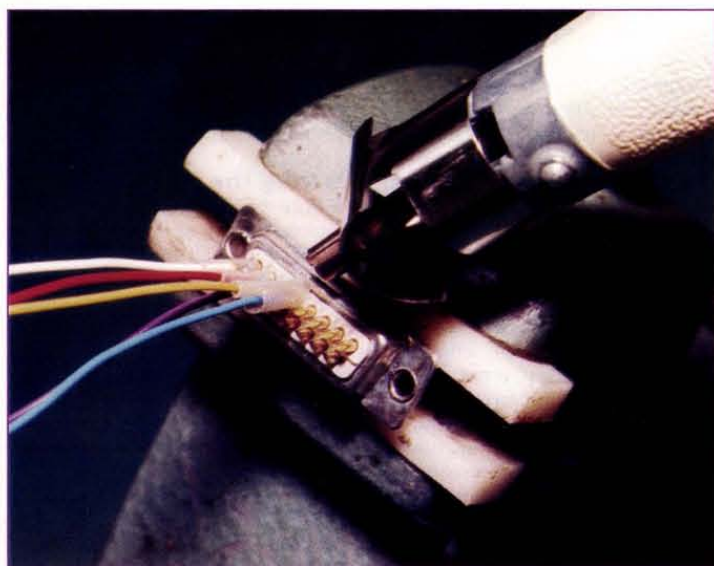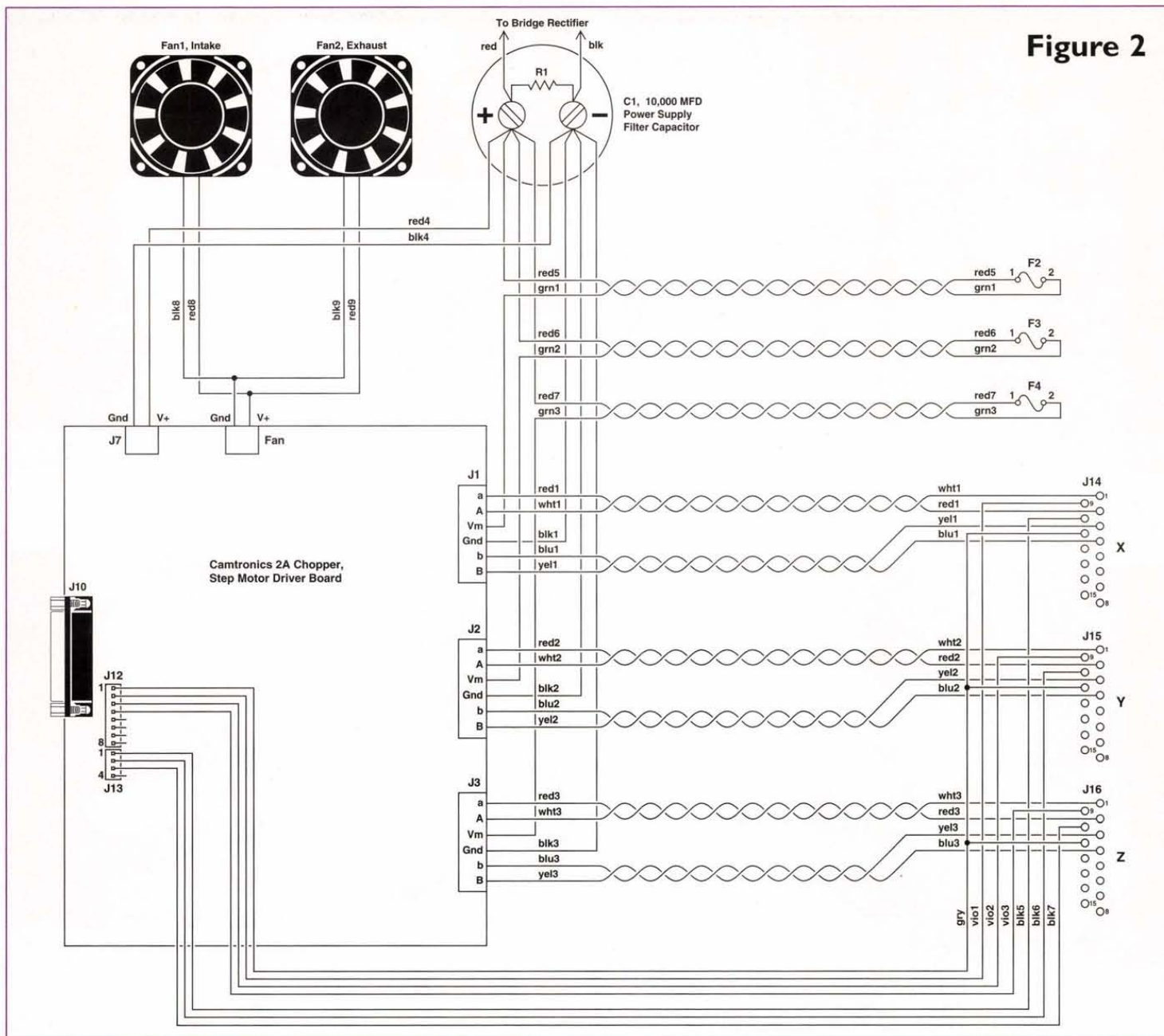

**Photo 5.** Each wire gets insulated with heat shrink tubing to prevent shorts and strengthen the connections.

the blue lead closest to the front of the chassis to the same lead of the other transformer. Leave the remaining leads unconnected except to the probes of a VOM or DVM set to measure AC voltage. Install F1, plug the modular cord set into the power entry module, and then plug the cord into an outlet of a switched-off power strip. Check everything one more time, then switch the power strip on. Everything okay? Now switch on S1.


If the secondaries are phased correctly, your meter should read zero volts across the two unconnected leads. If it reads zero volts, mark each lead connected by the clip lead with a black marker dot. If it reads somewhere around 26-28VAC, they are connected backwards, and you need to switch one of the leads.

(If the light of S1 fails to light, turn the power strip off and unplug

the cord. Check the fuse and recheck your wiring.)

Assuming everything is working, apply power again, and this time measure AC voltage across the secondary of each transformer. Both should read about 14VAC. Power down, connect the last two wires together with another clip lead, and repeat the measurement process; it should still read about 14VAC.

Once you've achieved this, twist the stripped ends of each set of blue leads together with an 8" length of blue 18 AWG stranded wire and crimp together with one .44" closed-end nylon connector each. Crimp a 1/4" fully-insulated quick disconnect terminal to the other end of each 8" wire. These terminals connect to the AC input terminals of U1. Figure 1 shows the terminal layout of U1. Note that the AC inputs are diagonal from each other.

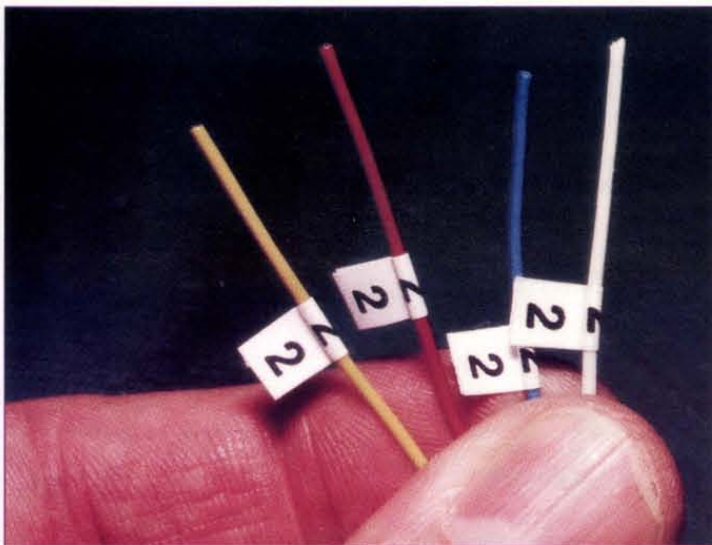

**Photo 6.** Since I use the same color combinations for each axis connector, I use numbered wire markers to identify the other end of each axis. These wires are the Y-axis phases.

### Wiring the DC Section

Install the vertical capacitor mount with 6-32 x 1/4" screws, lock washers, and nuts, but don't install C1 yet. Cut and strip the ends of one 3" red and one 3" black wire, both 18 AWG stranded. On one end of each, crimp a quick disconnect terminal and on the other end crimp a snap-spade terminal.

The red wire connects the positive output terminal of U1 to the positive screw terminals of C1, and the black lead connects the negative terminals. Before you install C1, first form the leads of R1 to go around the screw terminals. R1 is there to safely drain all charge from C1 within a minute or so of power being removed. Without this


bleeder resistor, C1 holds enough of a charge — even after hours — to melt a notch in the blade of a screwdriver (ask me how I know).

Install C1 and tighten the mounting clamp. Photos 2 and 3 show how everything should look when you're done. When you power up the circuit, you should read about 18VDC across the screw terminals of C1, and when you remove power, that voltage should decay to zero within a minute.

### Wiring the Rest

I don't have room to go into detail this time on the rest of the wiring. With Figure 2, the wiring table, and Photos 4 through 6, you should get
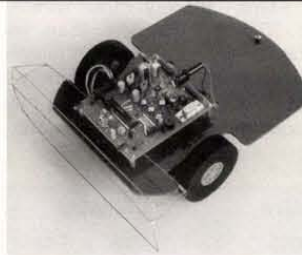
### QUICK and PAINLESS Programmable Robotics!



- COMES PRE-ASSEMBLED
- PRICED LOWER THAN A KIT
- Re-Programmable from your PC
- Co-Processor for IR proximity vision, Bumpers, Servo Controller, A/D, and MORE
- Drive servos have Dual Ball Bearings for longer life!
- Lots of free I/O, CPU power, and space for your modifications
- Genuine top of the line Basic Stamp 2p40® processor from Parallax Inc. Great tools, manuals, and books available for training or project development.

JUST ADD 6 AA BATTERIES AND GO!

Blue Bell Design Inc.

[www.bluebelldesign.com](http://www.bluebelldesign.com)

Circle #88 on the Reader Service Card.

a pretty good idea of what's involved. I'll make a few points, though.

First, I used solid 22 AWG wire for all connections from C1 to the chopper board, F2-F4, and J14-

Part	Description	Vendor	Vendor part #
C1	10,000 MFD, 50WVDC electrolytic capacitor	Mouser	539-CGS50V10000
F1	Miniature fuse (5mm x 20mm), 2A, fast-acting	Mouser	5765-35002
F2-F4	Miniature fuse (5mm x 20mm), 2A, slow-blow	Mouser	5765-39002
Fan1, Fan2	2-3/8" sq. x 9/16" 12VDC box fan	MPJA	12716-FN
J14-J16	DB15 15-pin female connector, solder cup, tin	Digi-Key	1115F-ND
J17-J19	DB15 15-pin male connector, solder cup, tin	Digi-Key	1115M-ND
J20	2-pin right-angle friction lock male header	Digi-Key	WM4300-ND
J21	2-pin center crimp terminal housing	Digi-Key	WM2000-ND
J22, J24	2-pin pocket header, "G" version	Digi-Key	WM2900-ND
J23, J25	2-pin pocket header, "A" version	Digi-Key	WM2533-ND
LED1-LED3	Red, diffused T-1 (3mm), panel-mount LED	Mouser	35CA001
R1	6.8K-ohm, 1/4W, 5% carbon film resistor	Digi-Key	6.8KQBK-ND
R2-R4	1.0K-ohm, 1/4W, 5% carbon film resistor	Digi-Key	1.0KQBK-ND
S1	Illuminated rocker switch, SPST 15A, 125VAC w. amber neon lamp & internal resistor	Mouser	10DS322
T1, T2	Transformer, 110/220VAC input, 12VAC output	MPJA	7840-TR
U1	25A, 400V PRV bridge rectifier	Mouser	625-GBPC2504
<b>Misc:</b>			
1 ea.	3-axis 2A Chopper/Step Motor Driver kit	Camtronics	539-VR3
1 ea.	Vertical capacitor mounting hardware	Mouser	441-R3-12
4 ea.	Panel-mount miniature fuse holder	Mouser	8660-FN
2 ea.	Fan guard for 2-3/8" fan	MPJA	173-63101
1 ea.	6-ft 3-wire IEC cord set	Mouser	562-857-06/27
1 ea.	IEC connector/line filter, 6A 250VAC 50-60Hz	Mouser	537-8123
1 ea.	8"W x 12"D x 3"H aluminum enclosure	Mouser	537-8123C
1 ea.	8" x 12" aluminum enclosure cover	Mouser	915CA-ND
3 ea.	DB-15 conn. backshell, shielded plastic	Digi-Key	160-10F-ND
6 ea.	4-40 female hex screwlock conn. hardware	Digi-Key	2209K-ND
4 ea.	Hex threaded standoff, alum. 6/32, .25" x .375"	Digi-Key	WM2200-ND
2 ea.	Crimp terminals for J21	Digi-Key	WM2510-ND
4 ea.	Box crimp terminals, female, for J22, J24	Digi-Key	WM2517-ND
4 ea.	Box crimp terminals, male, for J23, J25	Digi-Key	WM18237-ND
10 ea.	1/4" fully-insulated quick disconnect, female, crimp	Digi-Key	WM18317-ND
10 ea.	Snap-spade crimp terminals, #10 stud, insulated	Digi-Key	WM18394-ND
4 ea.	Nylon-insulated, closed-end crimp connector, .35"	Digi-Key	WM18395-ND
4 ea.	Nylon-insulated, closed-end crimp connector, .44"	Digi-Key	

### CHASSIS PARTS LIST

# Robots A to Z

Robot Store

800-374-5764

[www.RobotStore.com](http://www.RobotStore.com)

Circle #85 on the Reader Service Card.

### Mobile Robotics

Used world wide for research!



Mobile Robots  
Micro Controllers  
Artificial Intelligence  
Sonar Units  
Optics  
Vision Systems



Zagros Robotics  
PO Box 460342  
St. Louis, MO 63146-7342  
Phone (314) 768-1328 Fax (314) 576-5568  
<http://www.zagrosrobotics.com>  
[info@zagrosrobotics.com](mailto:info@zagrosrobotics.com)

Circle #87 on the Reader Service Card.

J16. These wires, once routed around the chassis, will only rarely need to be moved, and all of the connections made to the chopper board are made with screw terminal blocks, which work best with solid wire.

Second, twist together the wires carrying chopped current to

each stepper phase. This keeps down the electrical hash these lines would otherwise radiate.

Third, cut way more wire for the 15-pin connectors than you think you will use. I cut 18" lengths of each color needed for each connector so I would be sure to have enough once the wires were routed

to their destinations.

Forth, I'm a belt and suspenders kind of guy when it comes to wiring. I soldered wires to the connectors (Photo 4), checked for shorts and continuity from pin to wire end, then insulated each connection with 1/8" heat shrink tubing (Photo 5), and checked for

shorts and continuity again.

Finally, even before I trimmed wires to final length, I marked each line with wire label tape (Photo 6). After trimming, I mark them again so it's easy to tell which wire is what. And that is all the space for this month.

See you next time! **NV**



**The Robot Builders Bonanza**  
2nd Edition  
by Gordon McComb

Major revision of the bestselling "bible" of amateur robotics building — packed with the latest in servo motor technology, microcontrolled robots, remote control, Lego Mindstorms Kits, and other commercial kits.

**Only \$24.95**  
Available from  
the Nuts & Volts bookstore  
[www.nutsvolts.com](http://www.nutsvolts.com)



**2-Channel  
20 MS/s  
Scope**

US\$ 199.-

Options:  
PC Software V2.0 Incl. Adapter Cable..... \$9.00  
Signal Probe 11/16-1.60MHz..... \$4.95  
Rubber Protection Boot..... \$9.95  
AC Adapter..... \$9.95  
Hard-shell anti-static carry case..... \$9.95  
Complete Set Scope + options (2 Probes)..... \$349.00

**Wittig Technologies**  
Wittig Technologies, Inc.  
266 East Meadow Avenue  
East Meadow, NY 11554  
Phone (516) 794 4080, Fax (516) 794 1855  
[www.wittigtechnologies.com](http://www.wittigtechnologies.com)

Wire	Gauge	Connections	Description
BLK1	22 AWG, solid	C1- to J1.Gnd	X-axis ground
BLK2	22 AWG, solid	C1- to J2.Gnd	Y-axis ground
BLK3	22 AWG, solid	C1- to J3.Gnd	Z-axis ground
BLK4	22 AWG, solid	C1- to J7.Gnd	Chopper board ground
BLK5	22 AWG, stranded	J14.10 to J13.1	X-axis Limit/Home sw. ground
BLK6	22 AWG, stranded	J15.10 to J13.2	Y-axis Limit/Home sw. ground
BLK7	22 AWG, stranded	J16.10 to J13.3	Z-axis Limit/Home sw. ground
BLK8	24 AWG, stranded	Fan1- to Fan-	Intake fan ground
BLK9	24 AWG, stranded	Fan2- to Fan-	Exhaust fan ground
BLU1	22 AWG, solid	J14.4 to J1.b	X-axis step motor b-wire
BLU2	22 AWG, solid	J15.4 to J2.b	Y-axis step motor b-wire
BLU3	22 AWG, solid	J16.4 to J3.b	Z-axis step motor b-wire
GRN1	22 AWG, solid	F2.2 to J1.Vm	X-axis motor voltage, fused
GRN2	22 AWG, solid	F3.2 to J2.Vm	Y-axis motor voltage, fused
GRN3	22 AWG, solid	F4.2 to J3.Vm	Z-axis motor voltage, fused
GRY	22 AWG, stranded	J14.11, J15.11, & J16.11 to J12.1	Limit/Overtravel sw. sense
RED1	22 AWG, solid	J14.2 to J1.a	X-axis step motor a-wire
RED2	22 AWG, solid	J15.2 to J2.a	Y-axis step motor a-wire
RED3	22 AWG, solid	J16.2 to J3.a	Z-axis step motor a-wire
RED4	22 AWG, solid	C1+ to J7.V+	Chopper board V+
RED5	22 AWG, solid	C1+ to F2.1	X-axis motor voltage
RED6	22 AWG, solid	C1+ to F3.1	Y-axis motor voltage
RED7	22 AWG, solid	C1+ to F4.1	Z-axis motor voltage
RED8	24 AWG, stranded	Fan1+ to Fan+	Intake fan V+
RED9	24 AWG, stranded	Fan2+ to Fan+	Exhaust fan V+
WHT1	22 AWG, solid	J14.1 to J1.A	X-axis step motor A-wire
WHT2	22 AWG, solid	J15.1 to J2.A	Y-axis step motor A-wire
WHT3	22 AWG, solid	J16.1 to J3.A	Z-axis step motor A-wire
VIO1	22 AWG, stranded	J14.9 to J12.2	X-axis Home sw. sense
VIO2	22 AWG, stranded	J15.9 to J12.3	Y-axis Home sw. sense
VIO3	22 AWG, stranded	J16.9 to J12.4	Z-axis Home sw. sense
YEL1	22 AWG, solid	J14.3 to J1.B	X-axis step motor B-wire
YEL2	22 AWG, solid	J15.3 to J2.B	Y-axis step motor B-wire
YEL3	22 AWG, solid	J16.3 to J3.B	Z-axis step motor B-wire

WIRE SIZES AND CONNECTIONS

Don't miss another issue! Subscribe today online at [www.nutsvolts.com](http://www.nutsvolts.com)!!

## Graphic Interface With Touch Screen




GTC100 128x64 LED    GTC200 256x128 CCF    GTC300 320x240 CCF    GTC301 320x240 LED    GTC600 640x200 CCF

Priced From \$140 w/Touch QTY 1

**Graphic display**  
**Touch screen (optional) or 12x12 input matrix**  
**Serial communication (RS-232C)**  
**Eeprom or Flash for screen storage**  
**Only +5VDC power required (or 9-26VDC)**  
**Includes graphic controller board**  
**Easy to use development software**  
**Powerful friendly instruction interpreter**  
**Create screens by PC paintbrush**  
**Holds 100's of "canned" graphic screens**  
**Simple to place touch buttons software**  
**Easy interface with PC/104, 8051, 68HC11, PIC**  
**Embedded Computer Controller Also Available**

**Easy Operator Interface through serial connection**

**Designtech Engineering Co.**  
2001 S. Blue Island Ave.  
Chicago IL 60608  
Phone 312-243-4700  
Fax 312-243-4776  
[www.DESIGNTechENGINEERING.com](http://www.DESIGNTechENGINEERING.com)



**SUPPORTS DEVICES TO 32 MEG**

# EPROM+

A device programming system  
complete info at [www.arlabs.com](http://www.arlabs.com)

♦ EXCEPTIONAL POWER FOR THE PRO  
♦ EASY-TO-USE FOR THE NOVICE

**Here's what you get:** A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters\*. Comprehensive, easy-to-use software which is specifically designed to run under Windows 95, 98, ME and DOS on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

**Broad device support:** Including FIRST GENERATION EPROMS (2708, TMS2716\*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C80)(8 MEG), 40 and 42 PIN EPROMS\* (27C1024-27C322)(32 MEG) EPROMS (2816-28C010) PLUS ER5901, FLASH EPROMS (28F, 29C, 29LE, 29F)(32 MEG), NVRAMS (12,20,X2210/12) 8 PIN SERIAL EPROMS\* (24, 25, 85, 93, 95, 80011A) PLUS ER1400/MS8657\* BIPOLAR PROMS\* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS\* (874X, 875X, 87CSX, 87C75X, 89C) ATMEL MICROS\* (89S, 90S)(AVR) PIC MICROS\* 8, 18, 28, 40 PIN (12CXXX, 16CSX, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS\* (68705P3/U3/R3, 68HC705C8/C9/J2/P9, 68HC11 all families)

**\$289**

Includes step-by-step tutorial plus explanation of EPROM fundamentals \$7.00 SHIPPING ♦ \$6.00 C.O.D.  
1 YR. AR WARRANTY - 30 DAY MONEY BACK GUARANTEE VISA ♦ MASTERCARD ♦ AMEX  
\*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)

**ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150**  
(513) 831-9708 FAX (513) 831-7562  
website - [www.arlabs.com](http://www.arlabs.com) email - [arlabs@worldnet.att.net](mailto:arlabs@worldnet.att.net) MADE IN THE U.S.A.

Does anybody know of a robotics interest group in South Africa?

Andrew C. Smith  
CSIR B43, PO Box 395, 0001 Pretoria  
South Africa; www.icomtek.co.za

I live in Kearney, NE which is located in about the middle of the state. Thanks for trying to get people hooked up with one another. I'm looking for a local club or other gearheads in the area.

Scott Willson, boweeble@nebi.com  
Kearney, NE

I've been trying to break into robotics for about 10 years now. Being on my own, it's hard to get and stay motivated. Hopefully, you can help me find some interested people (or better yet, a club) in my area, and we can get together and motivate!

Patrick Innes, Frederick, MD  
Robotics@tinkersfolly.com

My name is Mark Sobanek and I am a lonely gear head from Shawnee, KS, a suburb of Kansas City. Not exactly the technology hub of America, but it could be worse. My schedule and budget are kind of tight with a wife, three kids, another on the way (due early February), and a dog. Needless to say, I would rather join an existing club, but if I have to I would be willing to start one.

Mark Sobanek  
Kenabos@aol.com

I hope to find others in the Cincinnati-Dayton area who are interested in robotics.

Mark Aulfinger  
5678 Yamassee Dr., Hamilton, OH 45011  
(513) 425-3776 (day phone)  
mark\_aulfinger@aksteel.com

I'm very interested in joining a local club and organizing events/contests/conferences/shows/exhibits "geared" (no pun intended) toward the amateur robotics enthusiast.

William T. Jahnke  
will@lulu.com; Lulu Holdings: www.lulu.com  
2019 Fairview Road, Raleigh, NC 27608  
(919) 833-5858 (office)  
(203) 722-6348 (cellphone)  
(919) 833-6550 (fax)

I live in Beckley, WV. I am a retired physician and also a senior EE student at West Va Univ Tech. We have entered the IEEE Region 3 robot competition several times in the past few years and have won it every time we've entered. We're so small a school that people from the bigger schools wonder just who we are!

Jim Wills; TopDocJim@aol.com  
Beckley, WV

If you know of any robotics club in the Nashville, or middle, Tennessee area, please let me know.

Steve Ghertner  
steveghertner@mindspring.com

Hi. I am either looking for or starting a robotics club in the Central New Jersey or Eastern Pennsylvania area. Please include my email address in your February column. If there is enough interest, I will start one.

Mike Adams  
Cnjrobots@aol.com

Please add me to your list of people in the Southeast Florida area who want to join a local robot club. My home is in a suburb of Ft. Lauderdale, FL.

Wayne Tytell  
3062 La Mirage Drive, Lauderhill, FL 33319-4246  
wtytell@mediaone.net

I am a lonely gearhead living near Haddock, GA, which is close to Macon. We live pretty far out in the country on a little subsistence-type Permaculture farm community/eco village. I don't know anyone in this area who is into electronics. My interest is not robot building specifically, but I am interested in all things mechanical and electrical. I have recently been creating sculpture from electric discards and am interested in finding new ways to transform found objects into something new. I would love to find some folks around here to collaborate with on projects. www page in progress, but what little info there is: www.gypsyfarm.com/souly\_solar

Eric Daine, Haddock, GA  
ed@cerebral.org

Looking for a robotics club — ideally in St. Mary's or Kingsland, GA. Feasible travel would be Brunswick, GA, or maybe Savannah, GA — or Jacksonville, FL to the south. Not too practical would be north to Atlanta or south to Orlando. I will consider helping to start a robotics club with others in my area, and may consider doing so as far as Jacksonville to the south or Brunswick to the north. I'm also looking to correspond with other robot builders on robotics projects and mechanics and electronics. I will send my telephone number to those write.

Larry W. Finch  
143 Cypress Lane, St. Marys, GA 31558

If you have suggestions, questions, or comments about amateur robotics topics, you can reach me at:

**Robert Nansel**  
Box 228  
Ambridge, PA 15003

E-Mail: bnansel@nauticom.net

## Electro Mavin

Great Buys - Great Products - Great Gadgets  
Check Out Our Great WebSite at

**http://mavin.com**

For Computer Items, Hobbist Projects,  
Microwave Goodies and Some of the  
Greatest Prices on the Web....

800-421-2442 or FAX 310-632-3557

E-Mail


john@mavin.com or sean@mavin.com

WWW.CONITEC.NET

**\$333**  
COMPLETE KIT

**GALEP-4**  
UNIVERSAL PROGRAMMER

Introducing a pocket programmer with true **Universal Output**



Latest generation Galep-4 uses ASIC universal pin technology for each pin of 40 pin ZIF-socket. 1300+ device library / lifetime free updates. Programs 8/16-bit EPROMs, EEPROMs, 0-Power RAM, FLASH, Serial EEPROMs, GAL, PALCE, microcontrollers such as 8789xxx, PIC, AVR, ST42, etc. Low voltage devices down to 1.3V. No adapter required for DIL devices. 8 Hrs. operation on battery (AC charger included). Runs WIN 98, NT, ME, 2000, XP with Hex/Fuse Editor. Remote control from other apps, (e.g. VisualBasic). Substitutes high priced universal programmers e.g. ALL-11 (HIL0) or LAB-TOOL-48 (ADVANTECH). Providing virtually matching performance at only 1/3-1/5 the price. Info, orders, softw: 619-702-4420

Info, downloads: www.conitec.net

CONITEC DATASYSTEMS - 1951 4TH AVE, SUITE 301 - SAN DIEGO, CA 92101 - TEL: 619-702-4420 FAX: 619-702-4419

Circle #89 on the Reader Service Card.

## 68HC11 & 68HC12 Microcontroller Modules!

Unique design-- just plug them right into your solderless breadboard!

### MicroStamp11™

• tiny 1-inch x 1.4-inch 68HC11 module from \$49

### MicroCope-11™

• compact 2-inch x 2-inch 68HC11 module from \$68

### Adapt-11™ Family

• 68HC11 modules with lots of I/O lines from \$63

Application Cards Available:

- stepper motor driver
- voice record/playback
- LCD/Keypad/PC keyboard
- data acquisition • DAC
- CAN • ethernet • more!

### Adapt812™ Family

• based on 68HC812A4

• from \$79

### Adapt912™ Family

• choice of B32, D60, DG128

• from \$99

### MicroBDM912™

• lowest-cost BDM pod!

• only \$79!

**Toll-free: 1-877-963-8996**

**Technological Arts**

Visa/MasterCard  
Discover/Amex

Phone: (416) 963-8996

Fax: (416) 963-9179


**www.technologicalarts.com**

# Kronos Crawler Phase 2
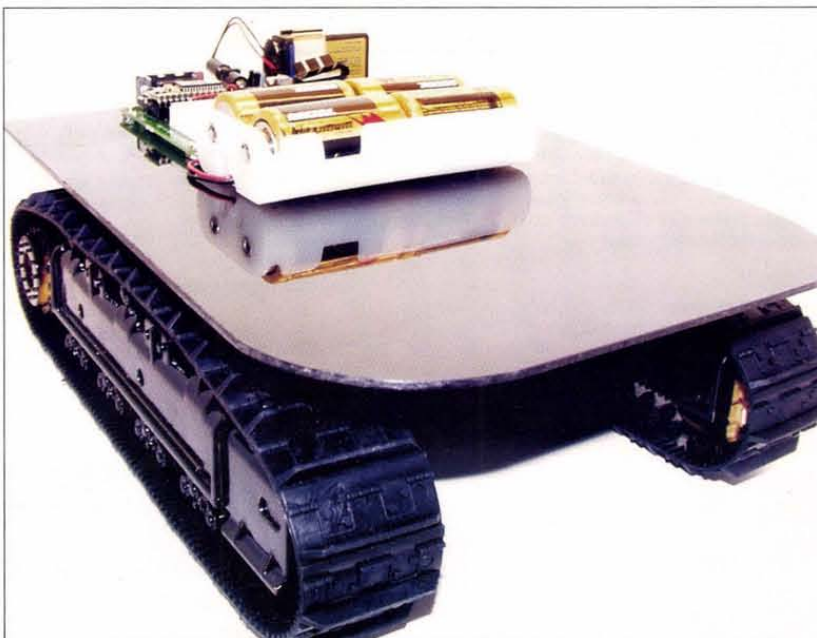
## The IR Connection

By Michael Simpson

*Last month, we assembled the base and connected the Atom development board along with an SN754410 motor controller. I felt it was time for a few sensors.*



Every time I have constructed a robot, I always wished I had a better way of testing the sensors as they were added. I decided to forgo the sensors and add an infrared remote control system that would make it easier to test and calibrate any sensors I might want to add.

I will be concentrating on the Vishay 1840 IR Module. This module operates at 40kHz and is well suited to our application. There are a great number of remotes available and protocols to match, but I will be concentrating on one in particular, the Sony® protocol.

- It is an easy protocol based on a pulse width bit stream which is very easy for microcontrollers to deal with.
- The remotes are readily available. You can pick up a universal remote for around \$10.00.

### The Protocol

I am not going to spend a great deal of time explaining the protocol in depth as it has been done many times. I will just go over a few important points regarding this protocol.

Let's start by diving into the Sony protocol. The IR module will output a pulse stream of bits with varying widths.

The widths are defined as follows.

Start Bit	2400ms
High State (1)	1200ms
Low State (0)	600ms

The world is not perfect and to compensate for the various manufacturers, we have expanded the specification as follows.

Start Bit	Any pulse greater than 2000ms wide.
High State (1)	Any pulse between 1000ms and 2000ms wide

Low State (0)      Any pulse less than 1000ms


The actual bits sent consist of a starting bit followed by 12 data bits. The data bits can be further broken down into command and device bits as shown below.

S C C C C C C C C D D D D D

These bits come with the least significant first and will be represented as the command byte and the device byte. We will get into this further when we look at the code.
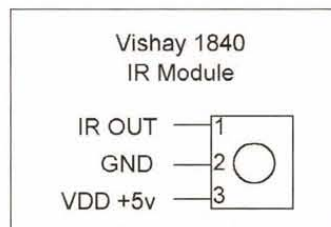
### The Modules

Let's look a little closer at the modules before we wire them up.



The end with the little round bump is the sensor side of the chip.

As far as the remote goes, you can use any Sony remote, as well as any universal remote that supports Sony. I use an RCA universal remote myself.

### The Circuit

Wire up the circuit as shown in the schematic. Pay particular attention to



Nuts &amp; Volts Magazine/FEBRUARY 2002 69

## Program Listing 1

I define a few variables to hold the recorded pulse data.

**'Define buffer to hold ir values**

```
IRbits var word(30)
x var byte
```

```
bitcount var byte
bitvalue var word
```

This is the main loop. Before checking for pulses, I clear all variables.

```
main:
'Clear the IRbits
for bitcount = 0 to 29
  IRbits(bitcount)=0
next
```

I then look at pin 12 and record the pulse width.

```
bitcount=0
```

**getstartbits:**

```
bitvalue = 0: PulsIN 12,0,bitvalue:IRbits(0)=bitvalue
if bitvalue < 2000 then goto getstartbits
```

If it is less than 2000 I go back and look again.

I now have the start bit.

```
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(1)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(2)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(3)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(4)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(5)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(6)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(7)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(8)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(9)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(10)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(11)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(12)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(13)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(14)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(15)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(16)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(17)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(18)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(19)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(20)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(21)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(22)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(23)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(24)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(25)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(26)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(27)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(28)=bitvalue
bitvalue = 0 : PulsIN 12,0,bitvalue : IRbits(29)=bitvalue
```

In this section I display all 30 recorded bits.

**displaybits:**

```
for bitcount = 0 to 29
  serout S_OUT,i9600,[dec IRbits(bitcount)," "]
next
```

I use the serout command. Use one of the terminal sessions and set it up as 9600 with No Parity.

```
serout S_OUT,i9600,[10,13]
goto main
```

## Program Listing 2

I define the two variables that the subroutine getsynocode is going to populate, devicecode and cmdcode.

```
devicecode var byte
cmdcode var byte
```

A few working variables are also created, bitvalue and level1value.

**'Holds the pulse width of the current bit under test**  
bitvalue var word

**'Holds the divisor for testing the width of each pulse**  
level1value var word

**'In this case 1200ms or longer will be a level 1**  
level1value = 1200

The bitvalue variable will contain the pulse width of each bit I test in the bit stream.

**'We will divide bitvalue by level1value to determine ' if bitvalue is less than 1200 (high state pulse ' width value). If it is then the bit is 0 other wise its 1.**

Level1value is a width

test variable. Bitvalue will be divided by level1value to determine if it is less than or greater than our high bit reference value.

**' By using some simple integer math I can still scan ' each bit in time for the next. Had I used an IF ' statement we would eat too much time between ' pulses in the stream.**

The main loop just calls the getsynocode subroutine over and over.

**main:**

```
gosub getsynocode
if devicecode > 0 or cmdcode > 0 then
  serout S_OUT,i9600,[ " ",dec devicecode," ",dec cmdcode,10,13]
endif
```

If both the devicecode and cmdcode contain valid values the results are displayed with the serout command.

goto main

First thing I do is clear all the variables so I have a fresh start.

**GetSonyCode:**

```
'Clear the IRbits
devicecode=0
cmdcode=0
```

I then look at pin 12.

**getstartbits:**

```
'We have to clear the variable used with the pulsing ' command as the Atom will not clear the variable if ' it times out.
bitvalue = 0
```

If it contains a value and it is less than 2000ms I go back and get another pulse.

```
Pulsin 12,0,bitvalue
```

I keep doing this until I have a valid start bit.

**'No spaghetti code here cause we have multi-line 'IF/Then's**

```
if bitvalue = 0 then
  return
endif
```

```
if bitvalue < 2000 then getstartbits
```

Record the next 12 bits.

**'At this point we are ready to get the command code**

```
pulsin 12,0,bitvalue
cmdcode.bit0 = bitvalue/level1value
pulsin 12,0,bitvalue
cmdcode.bit1 = bitvalue/level1value
pulsin 12,0,bitvalue
cmdcode.bit2 = bitvalue/level1value
pulsin 12,0,bitvalue
cmdcode.bit3 = bitvalue/level1value
pulsin 12,0,bitvalue
cmdcode.bit4 = bitvalue/level1value
pulsin 12,0,bitvalue
cmdcode.bit5 = bitvalue/level1value
pulsin 12,0,bitvalue
cmdcode.bit6 = bitvalue/level1value
```

**'Now lets get the device code**

```
pulsin 12,0,bitvalue
devicecode.bit0 = bitvalue/level1value
pulsin 12,0,bitvalue
devicecode.bit1 = bitvalue/level1value
pulsin 12,0,bitvalue
devicecode.bit2 = bitvalue/level1value
pulsin 12,0,bitvalue
devicecode.bit3 = bitvalue/level1value
pulsin 12,0,bitvalue
devicecode.bit4 = bitvalue/level1value
```

return

## The Parts

Item	Qty	Description	Source
IC2	1	Atom	Kronos Robotics #ATM1
IC3	2	SN754410	Kronos Robotics #MDR1
IC4	1	Vishay IR Module	Kronos Robotics #IR2
	1	Atom development board	Kronos Robotics #ATM3
C3	1	470uF Capacitor	Kronos Robotics #C470-50
LED1	1	LED with integrated resistor	Kronos Robotics #LED5YR
	1	Dip Heatsink	Kronos Robotics #HSDIP
	1	9V Battery connector with power connector	Kronos Robotics #CO5
	1	4 cell C battery holder	Kronos Robotics #BH4C
	1	9V Battery holder clip	Kronos Robotics #BH9V
	1	Crawler Base	Kronos Robotics #RB1
	1	Crawler Platform	Kronos Robotics #RB2
	4	1/2" 4-40 machine screws	Kronos Robotics #HWP46
	8	4-40 hex nuts	Kronos Robotics #HWHN3
	1	Sony Compatible Remote Control	Kronos Robotics #REM1

## Sources

**Kronos Robotics**  
www.kronosrobotics.com

**Basic Micro**  
www.basicmicro.com

## Program Listing 3

I define the two variables that the subroutine gets on code is going to populate, devicecode and cmdcode.

A few working variables

are also created, bitvalue and level1value.

The bitvalue variable will contain the pulse width of each bit I test in the

bit stream.

Level1value is a width test variable. Bitvalue will be divided by

level1value to determine if it is less than or greater than our high bit reference value.

I now set up the ports used to control the SN754410.

I also make a call to CrHigh which sets the PWM signal generator to output a nearly 100% duty cycle. This sets the fastest speed.

In the main loop I call the gets on code subroutine. This routine populates the cmdcode and devicecode variables.

We test to see if they are both 0. If they are I assume I had a time out and go stop the Crawler.

If I did get an IR code I turn the indicator light on and continue to test the command codes.

A small note. I am not using the device code for anything other than a test for valid codes. You could test it here and just go back to the main loop if it is not what you expect.

In this section I test the cmdcode variable to determine the action to take.

In each case I call the appropriate Crawler command.

**'IR Section**  
devicecode var byte  
cmdcode var byte

**'Holds the pulse width of the current bit under test**  
bitvalue var word

**'Holds the divisor for testing the width of each pulse**  
level1value var word

**'In this case 1200ms or longer will be a level 1**  
level1value = 1200

**'We will divide bitvalue by level1value to determine if bitvalue is less than 1200 (high state pulse width value). If it is then the bit is 0 otherwise its 1.**

**'By using some simple integer math I can still scan each bit in time for the next. Had I used an**

**'IF statement we would eat too much time between pulses in the stream.**

**'We use this as a form of IR indication**  
output 8

**'Motor Controller Section**

**'Sets up the constants for the motor controller**  
M2InputA Con 11  
M2InputB Con 10

M1InputA Con 14  
M1InputB Con 13

**'Setup the ports for motor controller**  
Output M1InputA  
Output M1InputB

Output M2InputA  
Output M2InputB

**'Setup the initial speed**  
gosub CrHigh

**main:**

**'Insert Sensor code here ....**

gosub gets on code

**'Time out (no key pressed)**  
if devicecode = 0 and cmdcode = 0 then  
gosub Crstop  
**'Turn indicator off**  
low 8  
goto main  
endif

**'Turn indicator on**  
high 8

**'Reverse — (CH -)**  
if cmdcode = 17 then  
gosub Crrev  
endif

**'Forward — (CH+)**  
if cmdcode = 16 then  
gosub Crfwd  
endif

**'spin left — (Vol -)**  
if cmdcode = 19 then  
gosub CrLspin  
endif

**'spin Right — (Vol +)**  
if cmdcode = 18 then  
gosub CrRspin  
endif

**'Set Low Speed (2 Keypad)**  
if cmdcode = 1 then  
gosub CrLow  
endif

**'Set Medium Speed (5 Keypad)**  
if cmdcode = 4 then  
gosub CrMed  
endif

**'Set High Speed (8 Keypad)**  
if cmdcode = 7 then

Motor speed routines

Crawler movement routines

Motor Routines

First thing I do is clear all the variables so I have a fresh start.

I then look at pin 12.

If there was no pulse, bitvalue will contain 0 and I will exit the subroutine.

If it contains a value and it is less than 2000ms, I go back and get another pulse.

I keep doing this until I have a valid start bit.

Once I have a valid start bit I record the next 12 bits.

gosub Crhigh  
endif

Goto main

**CrLow:**  
HPWM 1,9890,7000 : Return '81% Duty cycle  
Return

**CrMed:**  
HPWM 1,9890,8000 : Return '90% Duty cycle  
Return

**CrHigh**  
HPWM 1,9890,9890 : Return '99% Duty cycle  
Return

**Crfwd:**  
gosub rfwd : gosub lfwd : return

**Crrev:**  
gosub rrev : gosub lrev : return

**CrLspin:**  
gosub rfwd : gosub lrev : return

**CrRspin:**  
gosub rrev : gosub lfwd : return

**Crstop:**  
gosub loff : gosub roff : return  
**'Left Motor (M1)**

**Lfwd:**  
High M1InputA : Low M1InputB : Return

**Lrev:**  
Low M1InputA : High M1InputB : Return

**Loff:**  
Low M1InputA : Low M1InputB : Return

**'Right Motor (M2)**

**Rfwd:**  
High M2InputA : Low M2InputB : Return

**Rrev:**  
Low M2InputA : High M2InputB : Return

**Roff:**  
Low M2InputA : Low M2InputB : Return

**'This is the main IR routine**  
**'It populates cmdcode and devicecode variables**

**GetSonyCode:**

**'Clear the lrbits**  
devicecode=0  
cmdcode=0

**getstartbits:**

**'We have to clear the variable used with the pulsing command as the Atom will not clear the variable if it times out.**

bitvalue = 0

Pulsin 12,0,bitvalue  
if bitvalue = 0 then  
return  
endif

if bitvalue < 2000 then getstartbits

**'At this point we are ready to get the command code (7 bits)**

pulsin 12,0,bitvalue  
cmdcode.bit0 = bitvalue/level1value  
pulsin 12,0,bitvalue  
cmdcode.bit1 = bitvalue/level1value  
pulsin 12,0,bitvalue  
cmdcode.bit2 = bitvalue/level1value  
pulsin 12,0,bitvalue  
cmdcode.bit3 = bitvalue/level1value  
pulsin 12,0,bitvalue  
cmdcode.bit4 = bitvalue/level1value  
pulsin 12,0,bitvalue  
cmdcode.bit5 = bitvalue/level1value  
pulsin 12,0,bitvalue  
cmdcode.bit6 = bitvalue/level1value

**'Now lets get the device code (5 bits)**

pulsin 12,0,bitvalue  
devicecode.bit0 = bitvalue/level1value  
pulsin 12,0,bitvalue  
devicecode.bit1 = bitvalue/level1value  
pulsin 12,0,bitvalue  
devicecode.bit2 = bitvalue/level1value  
pulsin 12,0,bitvalue  
devicecode.bit3 = bitvalue/level1value  
pulsin 12,0,bitvalue  
devicecode.bit4 = bitvalue/level1value

return

## NEW! CREDIT CARD COMPUTER II



MVS PLUG-N-GO™ no cables/power supply to buy!  
Low-power RISC cpu 10x faster than PIC. Z80. 8051  
4m FLASH, ser, par, RTCC, 4ch 12bit ADC, ISA104 bus  
Built-in BASIC/Assembly, other compilers available  
Friendly instructions, RS232 download (DOS/WIN)  
Eval kit (1) \$75, oem (1k) \$21, CC computer I \$14.20

## \$95 UNIVERSAL SINGLE CHIP COMPUTER PROGRAMMER



Lowest cost, fastest, easiest to use! Do FLASH, NVRAM, EE, EPROM to 8m. Adapters for micros, plc, etc. Optional gang banger for up to 10 ICs. Parallel port version available for notebooks. UV eraser \$95

ZERO external components!  
Built-in BASIC / Assembly  
RS232 program download  
1K flash, 64x4, 319g, 21miers  
15 io bits, ADC, 20pin DIP  
20mips, faster than PIC/80  
oem(1k): eval kit(1):  
\$1.99 \$7.00



NEW! 8K SUPER CHIP  
40x the BASIC pgm space  
32 io, 12m, 31miers, bus  
8K flash, 512e, 512nvram  
watchdog w/interrupt timer  
40 pin DIP part #MVS8515  
eval(1) \$25, oem(1k) \$7.10

## SERIAL MINI-TERMINAL \$27 MINI-PC



RS232 terminal for Stamp, PC, Z80, AVR etc.  
-super low current, powers from serial line  
-LED backlit LCD, visible in all conditions  
-115.2kbaud, DB9 conn, simple commands  
-specify 20 customizable or 16 tactile keys  
eval(1) \$75, oem(1k) \$21.30, w/BASIC cpu \$27



Includes DOS, ADC, 2par, 3ser, ISA bus, keypad/LCD interface. Complete! not a "core/engine". All utilities & tutorial included. Use TurboC, BASIC, MASM etc. eval kit (1) \$95, oem (1k) \$27 386 version eval \$195, oem \$55

## STAMP DRIVE !!



Read/Write PC compatible hard disk, PCMCIA, Compact Flash. RS232 to ATA adapter for Stamp, Z80, 8051, AVR, PIC, x86. ANY cpu  
- 4 gigabyte capacity  
- low power (5ma @5v)  
- baud 115.2k and above  
eval \$95, oem \$27, IDE ver. \$14.20

WWW.STAR.NET/PEOPLE/~MVS

MVS Box 803  
Nash, NH 03060  
(508) 792 9507



5yr Limited Warranty  
Free Shipping  
Mon-Fri 10-6 EST

SERVING THE EMBEDDED  
COMMUNITY SINCE 1979!

Circle #47 on the Reader Service Card.

Celebrating our 19th Year Of Service !!  
VISIT US AT WWW.UNICORNELECTRONICS.COM

### What Do We Have ?

- |                        |                |               |
|------------------------|----------------|---------------|
| • TTL                  | • 74LS         | • 74C         |
| • EPROMS               | • EEPROMS      | • PAL's       |
| • GAL's                | • CMOS         | • Z80         |
| • Linear               | • Generators   | • 8000 series |
| • 6500 series          | • 6800 series  | • Capacitors  |
| • Oscillators          | • Connectors   | • Crystals    |
| • Trimpots             | • I.C. sockets | • Switches    |
| • Diodes               | • Kits         | • Tools       |
| • Vises                | • Laser Diodes | • LED's       |
| • Vises                | • Transistors  | • Resistors   |
| • And much, much more! |                |               |

• Order Line — (800) 824-3432 • International — (724) 495-1230 • Fax Orders — (724) 495-7882  
• Technical Support — (724) 495-1231 • \$25.00 Minimum Order • UPS 3 day, Blue, Red, & Fed. Ex.  
Shipping Available (Call for charges) • PA Res. Add 7 % Sales Tax • Open Mon-Fri 9:00 AM - 5:00 PM  
(EST) • Corporate Accounts / Quantity Discounts Available • We accept M/C, VISA, Discover & AMEX  
with no surcharge • Call For FREE Catalog (\$2.00 Outside U.S.)  
• We Carry A Complete Line Of Electronic Components • Email - unielec@aol.com  
Visit us on the web ! www.unicornelectronics.com

Visit us on the web ! www.unicornelectronics.com

Unicorn Electronics  
1142 State Route 18  
Aliquippa, PA 15001

FREE SHIPPING!! on pre-paid orders

Circle #45 on the Reader Service Card.


## RF Data Modules



### AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current. 4mA typical.
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 ..... \$12.10

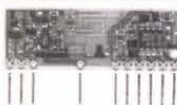

### AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current. 2.4mA typical
- 2kHz data rate. CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx ..... \$10.95



### FM TRANSCIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F ..... \$87.36

### RS232 TRANSCIVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- µController with user EEPROM
- RS232 interface protected to ±15kV
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 .... \$139.30



70 x 65 x 15mm

- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft.
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair (RTcomTX & RTcomRx)
- 7.5V-15Vdc operation
- RTcom-4xx..... \$247.90
- RTcomTx-4xx..... \$ 87.15
- RTcomRx-4xx..... \$105.52



ABACOM  
TECHNOLOGIES



Tel: (416)236-3858  
Fax: (416)236-8866  
www.abacom-tech.com  
abacomtech@compuserve.com

## Easy-to-Use Seetron Serial LCDs

Interface a sharp LCD display to your BASIC Stamp® or other micro-controller project with ease. No-solder wiring harnesses and easy mounting kits available too. See www.seetron.com today.

- 3.2 x 1.4 in. supertwist LCD
- 2400/9600 baud serial
- Low (~2mA) current draw
- Popular for use with BASIC Stamps®

\$45  
BPI-216N



- 3.2 x 2 in. backlit LCD
- 1200-9600 baud serial
- Advanced protocol, 4 switch inputs
- EEPROM for configuration settings
- Favorite for OEM applications

\$49  
ILM-216L




- 3.2 x 1.4 in. graphics LCD
- 2400/9600 baud serial
- Font and 15 screens in EEPROM
- Easily draw points, lines, screens

\$99  
SGX-120L



- 3 x 2 in. supertwist LCD
- 1200-9600 baud serial
- ESD-protected, 4x4 keypad input
- Store up to 95 screens in EEPROM

\$119  
TRM-425L

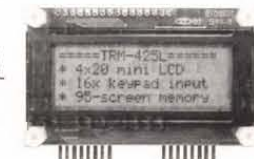

### Scott Edwards Electronics, Inc.

1939 S. Frontage Rd. #F, Sierra Vista, AZ 85635  
phone 520-459-4802 • fax 520-459-0623  
www.seetron.com • sales@seetron.com

More displays available,  
including bright VFDs.  
See www.seetron.com

# DEALER DIRECTORY

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

## ALABAMA

**Little Professor Book Center**  
2717 S. 18th St.  
Birmingham 35209

## ARIZONA

**Elliott Electronic Supply**  
1251 S. Tyndall Ave.  
Tucson 85713

## Tower Records

3 E. 9th St.  
Tempe 85281

## AUSTRALIA

**DonTronics**  
P.O. Box 595  
29 Ellesmere Cres.  
Tullamarine 3043  
www.dontronics.com

## CALIFORNIA

**Abletronics**  
9155 Archibald Ave. Unit E  
Cucamonga 91730

**All Electronics**  
905 S. Vermont Ave.  
Los Angeles 90006

14928 Oxnard St.  
Van Nuys 91411

## Alltronics

2300-D Zanker Rd.  
San Jose 95131

## Centerfold International

716 N. Fairfax Ave.  
Los Angeles 90046

## Del Amo Books & News

3758 Sepulveda Blvd.  
Torrance 90505

## Electro Mavin

2985 E. Harcourt St.  
Rancho Dominguez 90221

**HSC Electronic Supply**  
4837 Amber Ln.  
Sacramento 95841

3500 Ryder St.  
Santa Clara 95051

5681 Redwood Dr.  
Rohnert Park 94928

## JK Electronics

6395 Westminster Ave.  
Westminster 92683

## Lion Electronic Labs

4948 E. Townsend Ave.  
Fresno 93727

## Mar Vac Electronics

2001 Harbor Blvd.  
Costa Mesa 92627

12453 Washington Blvd.  
Los Angeles 90066

4747 Holt Blvd.  
Montclair 91763

2000 Outlet Center Dr.  
Ste. 150  
Oxnard 93030

1759 Colorado Blvd.  
Pasadena 91106

2537 Del Paso Blvd.  
Sacramento 95815

5184 Hollister Blvd.  
Santa Barbara 93111

## OPAMP Technical Books

1033 N. Sycamore Ave  
Los Angeles 90038

## Robots from Earth

6700 Eton Ave.  
Woodland Hills 91303

## Sav-On Electronics

13225 Harbor Blvd.  
Garden Grove 92643

## The Red Barn

Hwy. 299  
Bieber 96009

## Tower Books

211 Main St.  
Chico 95928

7840 Macy Plaza Dr.  
Citrus Heights 95610

1280 E. Willow Pass Rd.  
Concord 94520

630 San Antonio Rd.  
Mountain View 94040

1600 Broadway  
Sacramento 95818

2538 Watt Ave.  
Sacramento 95821

## Tower Records/Video

220 N. Beach Blvd.  
Anaheim 92801

6694 Amador Plaza Rd.  
Dublin 94568

5703 Christie Ave.  
Emeryville 94608

4118 Fremont Hub  
Fremont 9453

5611 Blackstone  
Fresno 93710

23541 Calle De La Louisa  
Laguna Hills 9265

6310 E. Pacific Coast Hwy.  
Long Beach 90803

2331 S. Atlantic Blvd.  
Monterey Park 91754

2525 Jones St.  
San Francisco 94133

871 Blossom Hill Rd.  
San Jose 95123

## Video Electronics

3829 University Ave.  
San Diego 92105

## CANADA

**Com-West Radio**

**Systems Ltd.**

611 Keeleumoku  
Honolulu 96814

454 N. Phillippi St.  
Boise 83706

## ILLINOIS

**Tower**

**Records/Video/Books**

383 W. Army Trail Rd.  
Bloomington 60108

8171 Main St.  
Vancouver, BC V5X 3L2

**Emma Marion Ltd.**

2677 E. Hastings St.  
Vancouver, BC V5K 1Z5

**Muir Communications Ltd.**

3214 Douglas St.  
Victoria, BC V8Z 3K6

2301 N. Clark St. #200  
Chicago 60614

1209 E. Golf Rd.  
Schaumburg 60173

## INDIANA

**Surplus Bargain Center**

2611 W. Michigan St.  
Indianapolis 46222

## KANSAS

**Hollywood At Home**

9063 Metcalf Ave.  
Overland Park 66212

## LOUISIANA

**Lakeside News**

3323 Severn Ave.  
Metairie 70002

## MARYLAND

**Tower Records/Video**

2566 Solomons Island Rd.  
Annapolis 21401

## MASSACHUSETTS

**Tower Records/Video**

1011 Middlesex Turnpike  
Burlington 01803

## MICHIGAN

**Anything Goes**

5108 Rochester Rd.  
Troy 48068

**Little Professors Book Center**

22174 Michigan Ave.  
Dearborn 48124

**Purchase Radio Supply, Inc.**

327 E. Hoover Ave.  
Ann Arbor 48104

**Spectrum Electronics, Inc.**

1226 Bridge St. NW  
Grand Rapids 49504

## MINNESOTA

**Radio City, Inc.**

2633 County Road 1  
Mounds View 55112

## MISSOURI

**Electronics Exchange**

8644 St. Charles Rock Rd.  
St. Louis 63114

## NEVADA

**Amateur Electronic Supply**

4640 Polaris  
Las Vegas 89103

**Radio World**

1656 Nevada Hwy.  
Boulder City 89005

**Sandy's Electronic Parts**

961 Matley Ln #100  
Reno 89502

**Tower Records/Video**

4580 W. Sahara Ave.  
Las Vegas 89102

6450 S. Virginia  
Reno 89511

## NEW JERSEY

**H.E.S. Electronics**

1715 Route 88  
Brick 08724

## NEW YORK

**Durston's Cigar Store**

515 W. Genesee St.  
Syracuse 13204

**Ham Central**

3 Neptune Rd.  
Poughkeepsie 12601

**Hirsch Sales Corporation**

219 California Dr.  
Williamsport 17221

**Tower Records/Video**

105 Old Country Rd.  
Carle Place 11514

350-370 Route 110  
Huntington 11746

1961 Broadway  
New York 10023

## NORTH CAROLINA

**United Electronic Supply**

920 Central Ave.  
Charlotte 28204

## OHIO

**Hosfelt Electronics, Inc.**

2700 Sunset Blvd.  
Steubenville 43952

**Keyways, Inc.**

204 S. 3rd St.  
Miamisburg 45342

## OKLAHOMA

**Taylor News & Books**

133 W. Main, Ste. 102  
Oklahoma City 73102

## OREGON

**News & Smokes**

1060 S.E. M St.  
Grants Pass 97526

**Norvac Electronics**

7940 S.W. Nimbus Ave. Bldg. 8  
Beaverton 97005

960 Conger  
Eugene 97402

1545 N. Commercial N.E.  
Salem 97303

**Tower Books**

1307 N.E. 102nd Ave.  
Portland 97220

## PENNSYLVANIA

**Tower Books**

425 South St.  
Philadelphia 19147

**Tower Records**

340 W. Dekalb Pike  
King of Prussia 19406

Land Title Bldg.  
100 S. Broad St.  
Philadelphia 19110

## TENNESSEE

**Tower Books**

2404 W. End Ave.  
Nashville 37203

**Tower Records**

504 Opry Mills Dr.  
Nashville 37214

## TEXAS

**BDL News, Inc.**

809 Pierce  
Houston 77002

**Electronic Parts Outlet**

3753-B Fondren Rd.  
Houston 77063

**Mouser Electronics**

958 N. Main St.  
Mansfield 76063

**Tanner Electronics**

1100 Valwood Pkwy #100  
Carrollton 75006

**Tower Records**

2403 Guadalupe St.  
Austin 78705

## VIRGINIA

**Tower Records/Video**

6200 Little River Turnpike  
Alexandria 22312

4110 W. Ox Rd. #12124  
Fairfax 22033

1601 Willow Lawn Dr.  
Richmond 23230

8389 E. Leesburg Pike  
Vienna 22182

## WASHINGTON

**A-B-C Communications, Inc.**

17541 15th Ave. N.E.  
Seattle 98155

**Supertronix**

16550 W. Valley Hwy.  
Seattle 98188

**Tower Books**

10635 N.E. 8th St.  
Bellevue 98004

20 Mercer St.  
Seattle 98109

## WISCONSIN

**Amateur Electronic**

**Supply, Inc.**

5710 W. Good Hope Rd.  
Milwaukee 53223

## WYOMING

**Western Test Systems**

2701 Westland Ct. #B  
Cheyenne 82001

# Advertiser INDEX

Abacom Technologies .....	72	DesignNotes.com .....	77	Gateway Electronics, Inc. ....	27, 56	Micromint .....	7	SolderingDesoldering.com ....	13, 28, 77
ActiveWire, Inc. ....	79	DesignTech Engineering .....	66	Halted Specialties Co. ....	3	Mr. NiCd .....	13	Square 1 Electronics .....	22
All Electronics Corp. ....	11	Detection Dynamics .....	44	H.T. Orr Computer Supplies .....	32	MVS .....	72	Technological Arts .....	67
Alltronics .....	56	Earth Computer Technologies .....	78	HVW Technologies, Inc. ....	79	Parallax, Inc. ....	Back Cover	Test Equipment Connection .....	16
Andromeda Research .....	66	ECD .....	78	IndustroLogic .....	34	PAIA Electronics .....	79	The RF Connection .....	77
Autotime Corp. ....	34	E.H. Yost & Co. ....	13	Information Unlimited .....	16	Polaris Industries .....	9	Texas Instruments .....	17
Basic Micro, Inc. ....	4, 45	Electro Mavin .....	67	Inkjet Southwest .....	51	Prairie Digital, Inc. ....	79	TNR Technical, Inc. ....	35
Bilocon Corp. ....	79	Electronic Design Specialists .....	52	Intronics, Inc. ....	32	Pulsar, Inc. ....	79	Unicorn Electronics .....	72
Blue Bell Design, Inc. ....	65	Electronix Corp. ....	44	J-Works, Inc. ....	44	Quality Kits .....	78	V & V Machinery & Equip., Inc. ....	78-80
C & S Sales, Inc. ....	23	Electronix Express .....	52	LabJack .....	28	R4 Systems, Inc. ....	78	Viking Systems International .....	27
CCTV Outlet .....	43	EMAC, Inc. ....	28	Lemos International .....	78, 79	Ramsey Electronics, Inc. ....	36	Western Test Systems .....	14-15
Circuit Specialists, Inc. ....	82	Embedded Systems .....	10	Linear Systems .....	13	Resources Un-Ltd. ....	12	Westshore Technologies .....	79
Conitec DataSystems .....	67	ExpressPCB .....	45	Lynxmotion, Inc. ....	44	Robot Store .....	65	Wittig Technologies, Inc. ....	45, 66, 77
Consumertronics .....	78	Fair Radio Sales Co. ....	35	M2L Electronics .....	22	Scott Edwards Electronics, Inc. ....	72	Zagros Robotics .....	65
Corporate Systems Center .....	2	Foss Warehouse Distributors .....	79	Matco, Inc. ....	79	SGC .....	77		
Cunard Associates .....	32	Future Horizons .....	32	Meredith Instruments .....	51	Shreve Systems .....	21		
Custom Computer Services .....	56	G2 Technology .....	27	microEngineering Labs .....	28				

## AMATEUR RADIO & TV

Alltronics .....	56
Gateway Electronics, Inc. ....	27, 56
Ramsey Electronics, Inc. ....	36
SGC .....	77
The RF Connection .....	11

## ASSEMBLY SERVICES

Bilocon Corp. ....	79
--------------------	----

## BATTERIES/CHARGERS

Cunard Associates .....	32
E.H. Yost & Co. ....	13
Mr. NiCd .....	13
Robot Store .....	65
TNR Technical, Inc. ....	35

## BUSINESS OPPORTUNITIES

## BUYING ELECTRONIC SURPLUS

Earth Computer Technologies .....	78
-----------------------------------	----

## CABLE TV

Foss Warehouse Distributors .....	79
-----------------------------------	----

## CB/SCANNERS

## CCD CAMERAS/VIDEO

Autotime, Corp. ....	34
CCTV Outlet .....	43
Circuit Specialists, Inc. ....	82
Detection Dynamics .....	44
Matco, Inc. ....	79
Polaris Industries .....	9
Ramsey Electronics, Inc. ....	36
Resources Un-Ltd. ....	12

## CIRCUIT BOARDS

Cunard Associates .....	32
ECD .....	78
ExpressPCB .....	45
IndustroLogic .....	34
Pulsar, Inc. ....	79
R4 Systems, Inc. ....	78
V & V Machinery & Equipment, Inc. ....	78-80

## COMPONENTS

ECD .....	78
Electronix Express .....	52
Linear Systems .....	13

Pulsar, Inc. ....	79
Unicorn Electronics .....	72

## COMPUTER

### Hardware

ActiveWire, Inc. ....	79
Autotime, Corp. ....	34
Corporate Systems Center .....	2
Earth Computer Technologies .....	78
Electro Mavin .....	67
Halted Specialties Co. ....	3
Shreve Systems .....	21

### Software

Consumertronics .....	78
Custom Computer Services .....	56
Electronix Corp. ....	44
R4 Systems, Inc. ....	78

### Microcontrollers / I/O Boards

Abacom Technologies .....	72
Basic Micro, Inc. ....	4, 45
Conitec DataSystems .....	67
EMAC, Inc. ....	28
Embedded Systems .....	10
G2 Technology .....	27
IndustroLogic .....	34
microEngineering Labs .....	28

Micromint .....	7
MVS .....	72
Parallax, Inc. ....	Back Cover
Prairie Digital, Inc. ....	79
Scott Edwards Electronics, Inc. ....	72
Square 1 Electronics .....	22
Technological Arts .....	67
Texas Instruments .....	17

### Printers/Printer Supplies

H.T. Orr Computer Supplies .....	32
Inkjet Southwest .....	51

## DESIGN/ENGINEERING SERVICES

Bilcon Corp. ....	79
DesignNotes.com .....	77
DesignTech Engineering .....	66
ExpressPCB .....	45
IndustroLogic .....	34
Prairie Digital, Inc. ....	79
Pulsar, Inc. ....	79
V & V Machinery & Equipment, Inc. ....	78-80

## EDUCATION

EMAC, Inc. ....	28
Embedded Systems .....	10
R4 Systems, Inc. ....	78

## EVENTS/SHOWS

## KITS

Alltronics .....	56
Autotime, Corp. ....	34
C & S Sales, Inc. ....	23
Earth Computer Technologies .....	78
EMAC, Inc. ....	28
Future Horizons .....	32
Gateway Electronics, Inc. ....	27, 56
HVW Technologies, Inc. ....	79
Information Unlimited .....	16
Inkjet Southwest .....	51
PAIA Electronics .....	79
Quality Kits .....	78
Ramsey Electronics, Inc. ....	36
Robot Store .....	65
S-5 Electronics .....	13
Scott Edwards Electronics, Inc. ....	72
Zagros Robotics .....	65

## LASERS

Future Horizons .....	32
Information Unlimited .....	16
Meredith Instruments .....	27
Resources Un-Ltd. ....	12
Unicorn Electronics .....	72

## MISC./SURPLUS

All Electronics Corp. ....	11
DesignTech Engineering .....	66
Fair Radio Sales Co. ....	35
Gateway Electronics, Inc. ....	27, 56
Halted Specialties Co. ....	3
Linear Systems .....	13
Picard Industries .....	45
Resources Un-Ltd. ....	12
Shreve Systems .....	21
SolderingDesoldering.com .....	13, 28, 77
Unicorn Electronics .....	72
Viking Systems International .....	27

## PROGRAMMERS

Andromeda Research .....	66
Conitec DataSystems .....	67
Embedded Systems .....	10
HVW Technologies, Inc. ....	79
Intronics, Inc. ....	32
M2L Electronics .....	22
microEngineering Labs .....	28
Basic Micro, Inc. ....	4, 45

## PUBLICATIONS

Consumertronics .....	78
Future Horizons .....	32
Square 1 Electronics .....	22

## RF TRANSMITTERS/RECEIVERS

Abacom Technologies .....	72
Lemos International Co., Inc. ....	78, 79

## ROBOTICS

Blue Bell Design, Inc. ....	65
HVW Technologies, Inc. ....	79
LabJack .....	28
Lemos International Co., Inc. ....	78, 79
Lynxmotion, Inc. ....	44
Robot Store .....	65
Zagros Robotics .....	65

## SATELLITE

## SECURITY

CCTV Outlet .....	43
Consumertronics .....	78
Detection Dynamics .....	44
Information Unlimited .....	16
Lemos International Co., Inc. ....	78, 79
Matco, Inc. ....	79
Polaris Industries .....	9

## STEPPER MOTORS

Alltronics .....	56
------------------	----

## TELEPHONE

Bilocon Corp. ....	79
--------------------	----

## TEST EQUIPMENT

C & S Sales, Inc. ....	23
Circuit Specialists, Inc. ....	82
Conitec DataSystems .....	67
DesignNotes.com .....	77
Electronic Design Specialists .....	52
G2 Technology .....	27
Intronics, Inc. ....	32
J-Works, Inc. ....	44
LabJack .....	28
Prairie Digital, Inc. ....	79
Test Equipment Connection .....	16
Western Test Systems .....	14-15
Westshore Technologies .....	79
Wittig Technologies, Inc. ....	45, 66, 77

## TOOLS

C & S Sales, Inc. ....	23
The RF Connection .....	77
SolderingDesoldering.com .....	13, 28, 77

## WIRE/CABLE & CONNECTORS

The RF Connection .....	11
-------------------------	----

# No-License Handhelds

By Gordon West

If you are planning a ski trip or winter camping adventure, bring along handheld radios for safety and staying in touch with base camp. Cross-country skiers swear by them — these little portable radios could very well get you out of a jam when a white-out occurs. But not all handheld radios qualify for cold weather land adventures. Some may work better than others, yet the "ultimate" handheld radio might be totally illegal to use on the slopes.

"I'm a sailor during the summer, so I pulled my two VHF marine radios off the boat and was planning to use them up in the mountains," comments an FCC-busted boater.

"I bought these at a marine store that told me I didn't need a license to transmit and receive over marine VHF, so you can imagine my surprise when I got hit with a \$5,000.00 fine for using them at my ski lodge."

Marine VHF handheld transceivers, operating on 55, 25-kHz-spaced channels at 156 MHz are permitted only for on-water radio service in strict accordance to channel assignments detailed in FCC Part 80.373. Although Federal Communications Commission maritime rules do not mandate a ship station license to operate this equipment, "no license" does not mean "no rules" on how these five-watt handheld marine radios work in the maritime FM marine radio service. Unfortunately, our boater-turned-ski-lodge operator arbitrarily picked a marine channel authorized only for the vessel traffic system service.

"No wonder they were telling me to get off of their channel!"

Handheld radios that don't require a FCC license may fall under FCC rules Part 15 and Part 95. Part 15 no-license handheld radios are the toy walkie-talkies sold to youngsters that typically transmit only for a couple hundred feet. These Part 15 FCC-defined "intentional radiators" may only transmit a few milliwatts of output power, and are usually limited by a field strength not to exceed 1,000 microvolts/meters at three meters. We see Part 15 toy walkie-talkies on higher frequencies as well, but their range is limited to usually less than a couple hundred yards — and because these little Part 15 handhelds are sold to kids, you can be assured that any RF output coming off the antenna is next to nothing for safety factors.

These toy walkie-talkies share the same range characteristics as 48 MHz/49 MHz cordless phone handsets. If you get a block of range, you're doing swell! Twenty-seven megahertz (27 MHz) CB handhelds do not require a license, and specific rules for their operation are found under Part 95,

Subpart D. CB radio manufacturers like RadioShack, Cobra, Maxon, and Midland have done a nice job of packaging these medium-weight, medium-sized, 27 MHz handhelds. Gone are the long telescopic whips and big battery packs.

Now the 27 MHz handheld works into a very inefficient rubber-duck antenna, and at three or four watts output, their battery packs only last for a few hours. The switch from nickel cadmium batteries to nickel metal hydride have almost doubled their playing time, but 27 MHz CB handheld radios run at high power don't stay on the air for long between battery changes.

If you have a 40-channel CB in your vehicle already, the little CB 27 MHz handheld could make sense. Range is limited to about one mile between mobile and handheld, and about a half mile between two portable 27 MHz radios with their little rubber antennas when skip conditions are pounding in. In the dead of night, you might get one mile at best between two CB walkie-talkies.

The FCC rules have been "plain language" for CB operation, preventing no more than four watts of AM carrier power, no linear amplifiers or radio contacts over 155.3 miles away, and no general chit-chat on CB Channel 9 used only for emergencies and traveler assistance. Other rules also prevent the CB 27 MHz radio from being hooked into the telephone system, and no deliberate jamming of other CB radio signals you hear on the air.

CB for traveling has merit in communicating with other motorists and truckers — listening into traffic conditions on CB Channel 19 is a good way to learn what is up ahead. For yakking back and forth between two handheld radios, 27 MHz CB will be noisy, frustrating, and battery power hungry.

Family Radio Service (FRS) is a BIG hit up on UHF with 14 channels. No license required, and only four FRS FCC rules dictate how this equipment is operated. Although the little FRS radio is only permitted a half-watt output on 14 UHF FM channels, their range is remarkable. Two FRS radios could span up to 10 miles distance from mountain top to mountain top, and easily cover several ski slopes if you pick one of the 14 channels not tied up with other operators on the same frequency. Up on the mountain slopes, FRS users have found Channels 8 through 14 relatively clear of general mobile radio service powerful repeater outputs situated on each side of FRS Channels 1 through 7. Channels 1 through 7 are also shared with more powerful GMRS handheld

This marine radio, with 25 watts output, may not be used at the ski lodge! On a boat, it is fine.



The very popular Pryme combo FRS and GMRS radio was a favorite with this author.



**Boaters do not need a handheld license for local marine VHF radio calls.**



radios sold to licensed GMRS operators, and these more powerful handheld radios will easily knock you off the air on the first seven channels.

There is a petition in front of the FCC to designate FRS Channel 1 as an emergency-only channel, or a call-only channel. There are so many people on the air, I really don't know if this is all that necessary because surely you should be able to reach someone else with similar equipment.

With that said, the exception are those operators using more expensive FRS equipment with scrambling turned on, or "privacy code" engaged. Scrambling indeed will make communications private, but the "privacy code" is nothing more than tone-coded squelch. Anything you say can and will be heard! Trying to break into a conversation that is scrambled or to another station on privacy code may be futile.

FRS radios have taken a nosedive in pricing. When they first came out, a good Kenwood FRS radio sold for over \$100.00 apiece. Same thing with Motorola. Now you can buy Kenwood and Motorola FRS full-feature radios in PAIRS for under \$79.00. You can buy pairs of inexpensive Cobra and Midland FRS radios for under \$39.00! But I recommend staying in the \$79.00 a pair bracket and enjoying such features as optional headset with voice-operated action, scrambling, privacy codes, and a tough exterior that will keep the snow out up on the slopes. The FRS radios cannot hook up to an external antenna, so the best way to get maximum range is to take the unit off of your belt, hold it up high, and place your call. The prices of FRS

**The tiny FRS radio transmits for about a mile in the mountains.**



**A brand new MURS portable radio, ideal for both land and boat use.**



radios can only go lower.

The latest license-free radio service is called MURS (Multiple Use Radio Service). Five VHF channels became available on July 12, 2000, but actual radio equipment designed specifically for MURS has not appeared until just recently. One reason was the almost immediate negative reaction by licensed radio operators on five VHF channels they were presently operating on. In fact, these radio users put so much pressure on professional two-way radio dealers that sold them the "color dot" equipment that both Motorola and RadioShack back-peddled on their endorsement for this radio service.

The five channels allocated to MURS landed right on the popular "anything goes" commercial radio service at 151 and 154 MHz. These were channels used primarily by construction workers and traveling shows to carry communications ranging from church usher comms to cranes picking up mega-ton loads. The blue and green dot channels at 154 MHz were also in use by fast-food vehicle speaker phone circuits, and you can imagine trying to stay in touch on a MURS channel and ending up with a burger and order of fries at the pick-up window.

MURS was also clouded with some rather vague rules, such as no more than two watts of effective radiated power output. This could lead someone to develop a system around a four-watt transmitter, 3 dB loss in coax, going to a unity gain antenna up 100 feet, perfectly legal! There was also a con-

**Fast chargers will replenish handheld batteries in less than an hour!**



cern that the rules did not forbid tie-in to your home phone system, nor any rule that would prevent two MURS radios from acting as a portable repeater tied into an external VHF, high-band, exotic antenna system.

Motorola continues to ask the FCC to further examine logical restrictions on telephone interconnect and repeaters, and more clarification for sending data over these five channels. It is apparent that Motorola is hoping to convert its present "color dot" users over to a more sophisticated radio system, and get them onto other bands and other frequencies before unlicensed MURS radio signals begin to clog these VHF channels.

Corwin Moore, well known for his Personal Radio Steering Group (PRSG) in Ann Arbor, MI, points out there are probably over a million licensed radio users on the present MURS channels, and these users will soon find that their legitimate radio system is now clogged with unlicensed radio operators tied into their home phone for an exotic cordless phone system, or sending data from one business to another over the airwaves.

With MURS equipment capable of attaching to an outside antenna, it will be interesting to see how far two watts of effective radiated power may go between two MURS base stations. In the clear, I could see a range of over 40

miles, point to point. Between two MURS handhelds, I see a quadruple of distance now enjoyed by little FRS radios on UHF. After all, the MURS handheld is four times as powerful as the little FRS.

Finally, licensed radio users on the General Mobile Radio Service (GMRS) look on to see what might adversely affect their present simplex and repeater channels sandwiched in between FRS walkie-talkies. That same FRS skier on the top of a mountain next to a licensed GMRS could easily inadvertently create interference to that GMRS repeater when using FRS channels 8 through 14. Something else to think about when mountain-topping with a little FRS radio.

Luckily, handheld battery manufacturers have seen the opportunity for longer lasting AA and AAA batteries. The new Maha battery cells and quick battery chargers are flying off the shelf because of their popularity with these little radio systems. New battery chemistry like nickel metal hydride and lithium ion handle the cold weather elements better than traditional nickel cadmium cells. Something to think about when your handheld dips below freezing.

Stay tuned — FRS will continue to gain popularity and equipment will continue to drop in price, and MURS is just coming on the scene. **NV**

**Subscribe today!**  
Call toll-free at 1-800-783-4624 or go online at [www.nutsvolts.com](http://www.nutsvolts.com)

**DesignNotes.com**  
Your Design Resource on the Web

Improve Your Design Skills, Find Project Advice and More

**Velleman's HPS5**  
Hand Held Oscilloscope  
**\$169.00**  
(Save over \$40.00)  
Complete with alkaline batteries, clip leads and carry bag (Probe extra)

Visit Our Online Forum

**On-Line Circuit Archive**  
Hundreds of Circuits.  
Over 23 Different Topics

#### Designing for Dollars

- 1) Submit your favorite circuit or program.
- 2) Each month the best design entry (Judged by your peers) wins \$100
- 3) Monthly winners are eligible for the yearly \$1200 Grand Prize!

NEXT GRAND PRIZE DRAWING IS OCT. 2002

Share What You Know and Learn What You Don't

Visit Us at [www.designnotes.com](http://www.designnotes.com)

Circle #57 on the Reader Service Card.

**20 MS/s Pen-type Scope**  
US\$ 79.-

**Options**  
PC Software V6.0 incl. Adapter Cable ..... 29.90  
BatteryPack (to hold 9V bloc) ..... 16.90  
AC Adapter ..... 9.90  
Rubber Protection Boot ..... 17.90  
Palm Software V2.0 incl. Adapter Cable ..... 19.90  
Active Opto-isolating RS232 Cable ..... 39.90

**NEW**  
PC Software V6.0 features long term data logging, exporting data to EXCEL or text file, scrolling mode

**Wittig Technologies**  
Wittig Technologies, Inc.  
266 East Meadow Avenue  
East Meadow, NY 11554  
Phone (516) 794 4080, Fax (516) 794 1855  
[www.wittigtechnologies.com](http://www.wittigtechnologies.com)

**The RF Connection**  
213 North Frederick Ave.  
Suite 111N  
Gaithersburg, MD USA  
20877

<http://www.therfc.com/>

**Complete Selection of MIL-Spec Coax, RF Connectors and Relays**

UG-21B/U N Male for RG-213/214 ..... \$5.00  
UG-21D/U N Male for RG-213/214 ..... \$3.25

**N Connectors for 9913/Flexi4XL/9096**

UG-21B/9913 ..... \$6.00 Pins Only ..... \$1.50  
UG-21D/9913 ..... \$4.00 Extra Gasket ..... .75

Amphenol 83-1SP-1050 PL-259 ..... \$0.90  
UG-176/U Reducer RG-59/8X .25 or 5/1.00 ..... \$1.00  
UG-175/U Reducer RG-58/58A .25 or 5/1.00 ..... \$1.00  
Silver Teflon PL-259/Gold Pin ..... \$1.00 or 10/\$9.00

**MIL-Spec Coax Available (Teflon, PVC IIA)**

**New Product:** Belden 9913F. 9913 with High Density PE Foam dielectric, stranded center cond. and Duobond III Jacket ..... .80/ft or \$76.00/100ft

**Also New:** 9092, RG8X with Type II Jacket  
Intro Price ..... \$23.00/100ft

**Call for Specials of the Month**

**Full Line of Audio Connectors for Icom, Kenwood, and Yaesu**

8 Pin Mike Female ..... \$2.50  
8 Pin Mike Male Panel ..... \$2.50  
13 Pin DIN for Kenwood ..... \$2.75  
8 Pin DIN for Icom ..... \$1.00  
8 Pin DIN for Kenwood ..... \$1.50

**Prices Do Not Include Shipping**


Orders 800/783-2666  
Info 301/840-5477  
FAX 301/869-3680

Circle #58 on the Reader Service Card.

**SolderingDesoldering.Com**  
Your SMD Rework Specialist  
**800-394-1984**

Enter the wide-open frontier of high-voltage electrostatics with Homemade Lightning — See Page 83 for details!!

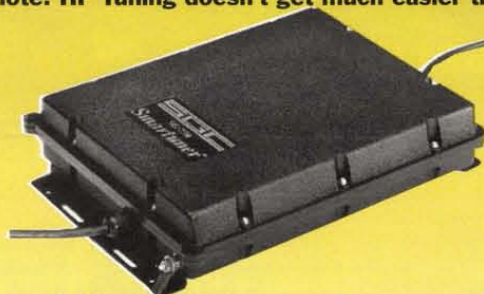**Two Step Tuning**  
**Step One: Pick up microphone.**  
**Step Two: Transmit.**  
(Please note: HF Tuning doesn't get much easier than this.)



## SGC Smartuner™ HF Automatic Antenna Couplers

"For me and my radio dollar, there isn't a better coupler made!"

Jack Huebschen N9XRO

**Power Input: From 1.5W - Up to 500W\***  
**HF Frequency Range: From 1MHz - Up to 60MHz\***  
**Up to 4,000,000 element combinations\***

**Five Sensor Devices**

\*Specs differ per model

"Undoubtedly the best piece of hamgear I have ever owned."

Ronnie Kane K9MNI

**Marine, Commercial, Amateur Radio,  
Aviation, Special Applications**

**Starting at \$249**



[www.sgcworld.com](http://www.sgcworld.com)

Toll Free (800) 259-7331 • Tel (425) 746-6310 • Fax (425) 746-6384 • Email: [sgc@sgcworld.com](mailto:sgc@sgcworld.com)

Mailing: PO Box 3526, Bellevue, WA 98009 • Shipping: 13737 SE 26th St. Bellevue, WA 98005 USA

Circle #59 on the Reader Service Card.

# Electronics Showcase

Special products and services  
for the electronics enthusiast.

Special  
Advertising  
Section!

**Top Secret Consumertronics**  
In business 25+ years - established professionals

Free Online Catalog!

**www.tsc-global.com**

Exciting Hi-Tech Survival Books, Manuals, Tapes

Stopping Power Meters Cellphone/Pager Manuals  
KW-HR Meters/VHS Fax Machine Security  
Polygraph Secrets Beyond Phone Color Boxes  
B. van Eck Tempest/VHS Caller ID & ANI Security  
ATM/Credit Card Security Radionics/ Heal Thyself  
Hacker Files/Dirty2Doz EM Brainblaster  
Computer/Internet Security Mind Control/Under Attack  
Identity Theft Manual Social Engineering  
High Voltage Devices Remote Office Strategies  
Stealth Technology Casino Secrets - 100 more!

Catalog has descriptions, prices, policies

**Consumertronics**

P.O. Box 23097, ABQ, NM 87192

(505) 321-1034 Printed Catalog: \$3

**UHF RADIO MODEM**  
RM-232-914  
FCC APPROVED

High Performance Low Power Wireless Data Link  
Capable of Through Put Rates of 9600bps

- Fully acknowledged data transfer
- Addressable point-to-point mode
- Extended range in repeater mode
- Built-in software configurator
- Remote over-air configuration
- Broadcast multi-drop mode
- DTE speed 600-115200bps
- Indoor range to 30m
- Outdoor range to 150m
- Low current consumption



IDEAL FOR ADDING WIRELESS CONNECTIVITY  
TO ANY RS232 LINK!

**www.lemosint.com**



**LEMO**  
INTERNATIONAL  
Microwave and RF Specialists

1305 Post Road  
Fairfield, CT 06430  
Tel: (508) 798-5004  
Fax: (508) 798-4782  
Email: Sales@lemosint.com

**SERIAL GRAPHIC LCD**



PICL-2464 \$99.00

Sharp LM24014 240 x 64 LCD  
E.L. Backlight  
5" x 1 5/16" Viewable Area  
PIC 16F877 Re-Programmable  
Switches, A/D & I/O Bits

**LCD MONITOR KIT**



A Complete 12.1  
TFT LCD Kit With  
Controller and 180  
Nit 16.7M Color  
XGA Panel- Just  
Plug Into VGA port  
and add 12 volts  
D.C.!

SK-2005R \$299

**12.1" LCD MONITOR**



Rugged Metal Case  
On Screen Display  
Free Z-Mount  
Resistive & Capacitive  
Touch Screen Options  
Available. 1024 x 768  
16.7 Million Colors  
VGA and SVGA

MTR-EVUE-12 \$399.00

**EARTHLCD.COM**

"The World Wide LCD Source"

32701 Calle Perfecto - San Juan Capistrano, CA 92675  
Ph: (949) 248-2333 Fax: (949) 248-2392

See the World's Largest Collection of LCD's and LCD  
Products at <http://www.EarthLCD.com>

## QUALITY KITS

SOLAR PANELS, Multimeters, Calipers,  
Oscilloscopes, Camera Modules, PIC & ATMEL  
Programmer Kits, Relay Cards, Electronic Lab  
Kits, RF Codelock Kits, Computer Interface Kits,  
Strobe Lights, and much more ...

Toll Free Order Line:  
**1-888-GO 4 KITS**

Secure On-Line Ordering  
**www.qkits.com**

Call 613-544-6333  
for free catalog  
49 McMichael St., Kingston, ON  
K7M 1M8, CANADA

**Download a Complete Virtual Workbench Today**

Shareware version [www.labcenter-electronics.com](http://www.labcenter-electronics.com)

PIC Micro Special \$99 includes: Graphical LCD, Logic Analyzer, Scope, Signal generator Probes, & more

**PROTEUS VSM**  
NEW  
Virtual System Modelling

[www.labcenter-electronics.com](http://www.labcenter-electronics.com)

**Build It In Cyberspace**

Develop and test complete micro-  
controller design without building a  
physical prototype. PROTEUS  
VSM simulates the CPU and any  
additional electronics used in the  
design. And it does it in real time.

Email, phone or fax for a  
free demo CD Today

**www.labcenter-electronics.com**

- CPU models for 8051 and PIC series, 68HC11 & ATMEL AVR micro-controllers available now. More CPU models under development.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Over 4000 standard SPICE models included.
- Integrates with PROTEUS PCB Design to form a complete electronics design system.

R4 Systems Inc.  
Tel: 905.898.0665  
Fax: 905.898.0683  
info@r4systems.com



ARES PCB



ISIS Schematic



- No tooling charge!
- Lot charges start at \$80
- Simple order process
- Quickturn, low quantities

TWO SERVICES FOR  
**CIRCUIT BOARDS**

**www.pcbpro.com**

- Quick price comparisons
- More options & added features
- Prototype & production quantities



**INSTANT  
ON-LINE QUOTES!**  
(NO SIGN-UP REQUIRED)

For a  
DISCOUNT  
on your next  
order enter this  
Code: NV1810

## SMT PCB ASSEMBLY



**SMT AND THROUGH HOLE AND OTHER LABOR  
INTENSIVE ELECTROMECHANICAL ASSEMBLY.**

USA Office: V&VMach. And Equip. Inc.  
Tel: (281) 397-8101, Fax: (281) 397-6220.

Please send blue prints or samples to:  
Marketing Tech. S.A. Alamo 93, 4. Piso Sta. Monica, Tlal. Edo. De  
Mexico 54040. Tel. 011 (525) 361-3351, Fax. 011 (525) 361-5996.  
ATTN: VICTOR M. MENDOZA. E-mail: [victor@vandvmachy.com](mailto:victor@vandvmachy.com)

PLEASE VISIT OUR SITE  
[www.vandvmachy.com](http://www.vandvmachy.com)

## CUSTOM PLASTIC PARTS

MODELS (WOOD AND RESIN). TO EVALUATE YOUR PARTS BEFORE YOU COMMIT TO MANUFACTURE A MOLD. MOLD DESIGN AND BUILDING.

We can also inject your parts on manual low pressure machines for very small runs or prototypes of parts up to 2 oz. At a surprisingly low price.

USA Office: V & V Mach. And Equip. Inc.  
Tel. (281) 397-8101, Fax. (281) 397-6220

Please send blue prints or samples to:  
Marketing Tech. S.A. Alamo 93, 4o. Piso, Santa Monica Tlal. Edo. De México. C.P. 54040.  
TEL. 011 (525) 3613351, Fax. 011 (525) 3615996  
ATTN: VICTOR M. MENDOZA.  
Mobil. 011 (525) 4398913

PLEASE VISIT OUR SITE  
[www.vandvmachy.com](http://www.vandvmachy.com)

PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TO SMALL OR TO BIG. VERY COMPETITIVE ON HIGH LABOR PARTS.

## CABLE CONVERTS

TV86/3	86/CH	TV86/3V/A
TRIVISION	550/3	\$37.95
VIEW MASTER	2600	

### 125 CHANNEL UNITS

TRI 860/3	10 LOT	\$49.95
TRI 860/3V/A	10 LOT	\$59.95
V/MASTER	3800/3V/A	

### FOSS WAREHOUSE DIS.

289 SCHENCK ST., N. TONAWANDA, NY 14120

800-473-0506 • 800-488-0525 FAX

716-694-6400 716-693-4322 FAX

E/M FOSS@BUFFNET.NET

WEB PAGE: WWW.FOSSW.COM

NO DESCRAMBLERS ONLY CABLE CONVERTS

Synthesizer Modules, Guitar Effects, Mixers, EOs, Tube PreAmps, and dozens of other kits for

**ELECTRONIC MUSICIANS**



**Theremin**  
The PAIA Theremin uses the same heterodyne principles as the original turn of the century instrument for classic tone and adds features made possible by modern ICs. Shown with optional lectern case.

**9308K Kit**  
\$154.00

**9505K Kit**  
\$89.75

**FatMan Analog MIDI Synth**  
A complete music synthesizer with all the big bottom and phat sound that makes analog famous. 20 knobs and controls for real-time sound sculpting. Compatible with standard MIDI sources like keyboards or computers. Desktop case or rack panel available.

Check out <http://Paia.com> for schematics, tech details, firmware source files and more...

PAIA Electronics • 3200 Teakwood Lane • Edmond, OK 73013  
405.340.6300 • fax:405.340.6378 • email:info@paia.com

## BIM2

433 MHz

900 MHz Available  
January 2002

High Speed Wireless Data Transceiver  
Physical Dimensions: 33 mm x 23 mm x 4 mm

- Data rates up to 160 kbps
- RX sensitivity -100dBm
- Usable range up to 200m
- SAW controlled FM transmitter
- 3V and 5V versions
- Low power requirements
- TX power 10mW @ 5V
- Fully screened
- Double conversion Superhet receiver
- Plug in replacement for BIM-433-F



[www.lemosint.com](http://www.lemosint.com)

**LEMOS INTERNATIONAL**  
Microwave and RF Specialists

48 Sword Street  
Auburn, MA 01501  
Tel: (508) 798-5004  
Fax: (508) 798-4782  
Email: Sales@lemosint.com

**SX-800**  
\$79

**BX-123**  
\$169

**ES-8960**  
\$359

**PC-103**  
(\$99)

**AX-800**  
\$79

**ASK-7003-TR**  
\$169

**A-330-SC**  
(4 pcs/\$25 ea)

**Wireless Light Camera**  
Call for Distributor Pricing!

Unbeatable Prices!

Canada: (877) 720-9222  
Fax: (847) 303-0660

## MATCO, INC

**EverSecure™**  
[www.matco.com](http://www.matco.com)

- On-Line Ordering
- OEM Security Products
- Monitors, Cables, Accessories
- Law Enforcement Equipment
- Discreet Wireless Systems (\$89-\$269)

Sales: (847) 303-9700  
Toll Free: (800) 719-9605

## HVW TECHNOLOGIES

HIGH-TECH SOLUTIONS TO HIGH-TECH PROBLEMS

BASIC Stamp™ Prototyping Made Easy...



\$32.95 (KIT)

Stamp Stacks™ mount directly on any breadboard to make prototyping easy. Complete - just assemble, connect power and a serial cable. 100% BASIC Stamp™ compatible. Robust, Repairable, Inexpensive. Starter kits available.

Pic Compilers/Programmers/Protoboard-Serial LCDs IR Ranging Sensors...

HVW Technologies Inc.  
Tel: (403)730-8603  
Fax: (403)730-8903

VISA/MC Accepted  
[www.HVWTech.com](http://www.HVWTech.com)

## CONTROL • MEASURE • INPUT

### MODEL 40-\$109

- RS-232 interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports



### MODEL 100-\$279

- 12-bit 100KHz A/D
- Four analog outputs
- Three timer counters
- 24 digital I/O

## PRAIRIE DIGITAL, INC.

920 SEVENTEENTH ST., INDUSTRIAL PARK  
PRAIRIE DU SAC, WI 53578  
TEL: (608) 643-8599 • FAX: (608) 643-6754

## ASSEMBLY & ENGINEERING

Producible designs since 1970

Contract Engineering

Embedded Microprocessors  
PCB Layout & Packaging Design  
Analog Including RF to 1 GHz  
Instrumentation  
A/D and D/A

Contract Assembly

High-Speed Fuji Surface Mount  
Through Hole  
Turn-key or Kit  
Run Sizes one through thousands  
Test and burn-in available

Bilcocon Corp.  
800-736-5927  
425-353-2276  
[www.bilcocon.com](http://www.bilcocon.com)

## PRINTED CIRCUIT BOARDS

QUALITY PRODUCT  
FAST DELIVERY  
COMPETITIVE PRICING

- \* UL approved
- \* Single & Double sided
- \* Multilayers to 8 layer
- \* SMOBC, LPI mask
- \* Reverse Engineering
- \* Through hole or SMT
- \* Nickel & Gold Plating
- \* Routing or scoring
- \* Electrical Testing
- \* Artwork or CAD data
- \* Fast quotes

We will beat any competitor's prices!!!

yogii@flash.net • flash.net/~yogii

10 pcs (3 days)  
1 or 2 layers **\$249**  
10 pcs (5 days)  
4 layers **\$695**

(up to 30 sq. in. ea.) includes tooling, artwork, LPI mask & legend

PROTOTYPE THROUGH PRODUCTION  
**PULSAR, INC**

9901 W. Pacific Ave.  
Franklin Park, IL 60131  
Phone 847.233.0012  
Fax 847.233.0013  
Modem 847.233.0014

## Oscilloscope Special

Wavetek Model 1910

**\$99<sup>00</sup>** Each + S&H

[www.westshoretech.com](http://www.westshoretech.com)

## ActiveWire® USB Simple USB Interface!



- Works with MacOS 8/9, Win98/2K/ME, FreeBSD and Linux
- 24Mhz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel Input/Output
- See web-site for add-on boards
- All drivers, manuals, demos are on our web-site for immediate download!


**\$59**  
plus shipping

ActiveWire, Inc.  
[www.activewireinc.com](http://www.activewireinc.com)

ph +1.650.493.8700 x203 fax +1.650.493.2200



**\$29.95  
each**

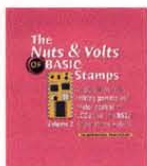

**Order Both Volumes For  
\$49.95!**

## The Nuts & Volts of BASIC Stamps Volumes 1 & 2

"... is as much of a BASIC Stamp reference book as it is an application idea guide ..."

Call our orderline at 1 800 783-4624  
Or order online from the Nuts & Volts Bookstore  
[www.nutsvolts.com](http://www.nutsvolts.com)

## SINGLE SIDED PCB'S SAVE MONEY

PROTOTYPES TO VERY HIGH VOLUMES NO  
MINIMUM SIZE ORDER, VERY COMPETITIVE  
**DOUBLE SIDED PCB'S**

\$1,000.00 MINIMUM ORDER, LOWEST PER UNIT PRICE  
IN THE INDUSTRY, FOR MEDIUM TO HIGH VOLUME ORDERS

OTHER SERVICES: MULTILAYER, FLEXIBLE PCB'S, DESIGN OF PCB'S,  
FROM YOUR HAND-DRAWN SCHEMATICS AND ASSEMBLY (SMT/PTH)

**V&V MACHY & EQUIP. INC.**

VIEW MACHY AND EQUIP. INC. (HOUSTON TX OFFICE)  
PH. (281) 287 0101 FAX (281) 287 6220  
MARKETING TECH. S.A. (MEXICO PLANT)  
PH. 011 525 3813351, FAX 011 525 3815886  
EMAIL: [sales@vandvmachy.com](mailto:sales@vandvmachy.com) SITE: [www.vandvmachy.com](http://www.vandvmachy.com)  
LOWEST PRICE IN THE  
INDUSTRY FOR SINGLE  
SIDED PROTOTYPES  
DELIVERY IN 5 DAYS.



## WIN with Nuts & Volts

PAID SUBSCRIBERS ARE AUTOMATICALLY  
ENTERED EACH MONTH!

**To Subscribe** — Just fill in and mail the card supplied in the magazine or call our toll free order line at (800) 783-4624 with a Visa or MasterCard. If you do not wish to order a subscription, but would like to be entered in our drawing, simply send or email your name, address, and telephone number to [Nuts & Volts, 430 Princesland Ct., Corona, CA 92879](mailto:Nuts & Volts, 430 Princesland Ct., Corona, CA 92879) or [drawing@nutsvolts.com](mailto:drawing@nutsvolts.com). No phone entries accepted. All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

This month's sponsor ...

## Square 1 Electronics

<http://www.sq-1.com>  
<http://www.stepperstuff.com>

**A \$69+ value!**



**NEW**

This month's winners ...

**Alan Fay of State College, PA**  
**Glenn Patsch of South Euclid, OH**

Check out Square 1's ad on **Page 22** for descriptions on these two excellent books!

# Computer Desktop Encyclopedia


Experience it today at the Nuts & Volts Web Site.

**For Experts and Novices** — The Encyclopedia contains more than 15,000 definitions, illustrations, photos, charts and diagrams, and covers the field from micro to mainframe.

**Everyone Needs This** — You can't escape computer and telecom lingo in this day and age. The Encyclopedia covers only the high-tech world, but makes it interesting for everyone.

**Twenty Years in the Making** — Starting as The Computer Glossary in 1980, the Encyclopedia is the longest-running computer dictionary. Edited by Alan Freedman, noted computer lexicographer with 40 years of experience in the industry, the Encyclopedia is the most comprehensive reference of its kind.

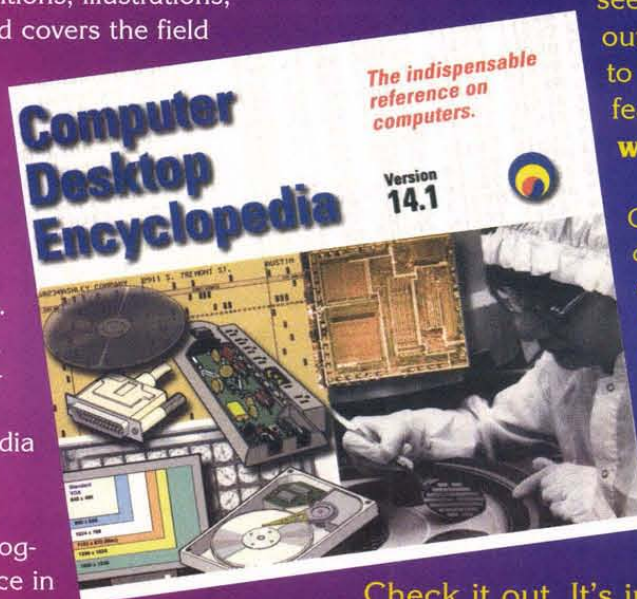If computer terminology or high tech mumbo jumbo seems to leave you on the outside looking in, you need to check out the latest new feature available now at **[www.nutsvolts.com](http://www.nutsvolts.com)**



Our new computer encyclopedia will have you up-to-speed on everything to do with computers, in nothing flat. As our lives become more integrated with and dependent on technology, this great resource will help you understand the concepts that drive this technological explosion.

Check it out. It's informative, it's here now, and it's brought to you free by Nuts & Volts.

# New Product News



## JUNGLE ROBOT

**L**ive, explore, and adventure the world of robotics with OWI's newest edition to their award winning line of robotic and science kits ... Jungle Robot.

Jungle Robot is a mysterious robot. One day, you may look up and catch a glimpse of Jungle Robot crossing hand-over-hand high across a string extended from tree to tree in the mist of the jungle air. Another day, you can catch him skipping through the fallen leaves on the ground. A condenser microphone and printed circuit board con-

trols your multi-function (walking or climbing) friend. When you think Jungle Robot is asleep, just cry "Wake UP!" Your robot will immediately start climbing or walking for a pre-set time and reset itself waiting for another command.

Jungle Robot is an excellent beginner series robot. This battery-controlled robot kit can teach the basic principles of robotic sensing and locomotion. It features a pre-assembled printed circuit board, hardware, and mechanical drive system that can be handled by almost anyone from age 10 and up. Only basic hand tools are required for assembly.

Educators, science museums, and hobbyists will surely appreciate the durability, educational value, and endless hours of amusement for children and adults too!

Suggested selling price: \$19.95 USD.

For more information, contact:

**OWI, INC.**  
17141 KINGSVIEW AVE., DEPT. NV  
CARSON, CA 90746  
310-515-1900 FAX: 310-515-1606  
EMAIL: owikitsales@pacbell.net

## ICON H-BRIDGE DC MOTOR CONTROLLER

**T**he ICON H-Bridge provides easy connectivity to a wide range of medium power brushed DC motors. An on-board microcontroller monitors current and temperature to provide protection if either trip point is exceeded. Various configuration registers may be monitored and programmed via the serial interface. These registers contain information such as the system load current, board temperature, over current trip point, over temperature trip point, and status information.

In serial mode, the H-bridge is enabled/disabled via a serial command set. In direct drive mode, the serial input line becomes the H-bridge enable control pin, while the serial output can be used to monitor the H-bridge status. In both operating modes each MOSFET in the H-bridge is controlled individually by a control input (four MOSFET control lines in all).


The ICON H-bridge is designed to operate with motor voltages up to 40V, and can carry continuous currents up to 12A with the active cooling solution available from Solutions Cubed. This robust H-bridge handles peak currents of 25A and can operate to 85°C.

Connectivity to the ICON H-bridge is simplified to two 1x8 0.156" receptacles capable of top or bottom insertion of 1x8 0.156" headers. With the small size (2.5" x 1.9" x 0.5") and versatile interface capabilities of the ICON H-bridge, it meets the requirements of many DC motor interface designs.

Pricing in single unit quantities is \$100.00.

For more information, contact:

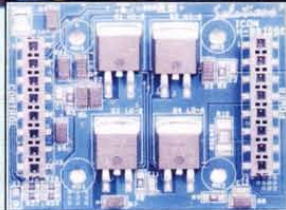**SOLUTIONS CUBED**  
256 E. FIRST ST., DEPT. NV  
CHICO, CA 95928  
530-891-8045 FAX: 530-891-1643  
EMAIL: solcubed@solutions-cubed.com  
WEB: <http://www.solutions-cubed.com>



## MSP430 Ultra-Low-Power Flash MCUs From Texas Instruments



## TI'S MIXED SIGNAL FLASH MCU DELIVERS THE WORLD'S LOWEST POWER SoC SOLUTION FOR EMBEDDED DISPLAY APPLICATIONS

**D**elivering ultra-low-power consumption and integrated high-performance analog, Texas Instruments Incorporated (TI) (NYSE: TXN) releases its most robust microcontrollers (MCUs), yet within its popular family of flash-based 16-bit RISC MCUs.

The new devices break the 1 mA barrier and are optimized for cost-sensitive, battery-powered measurement applications such as utility metering, portable instrumentation, and intelligent sensing.

With the highest level of analog integration and the industry's lowest power consumption, the MSP430F43x/F44x parts provide complete systems on a chip (SoC). The MSP430F43x/F44x devices include up to 60KB Flash, 2KB of RAM, a 160 segment LCD, a 200ksp/s 12-bit ADC, a comparator, two PWM timers, two hardware USARTs, a 16-bit hardware multiplier and an on-board supply voltage supervisor to combat brown-out.

The family's patented frequency locked loop enables applications to achieve a phenomenally low average current consumption. The MSP430's flexible clock system switches

## UHF RADIO MODEM RM-232-914 FCC APPROVED

**T**he RM-232-914 is a high-performance low-power UHF Radio Modem providing a reliable wireless data link capable of throughput rates to 9600bps. Its ease of use and many features make it ideal for adding wireless connectivity to any RS232 link.

The RM-232-914 features: Fully acknowledged data transfer; Addressable point-to-point mode; Broadcast multi-drop mode; DTE speed 600-115200bps; Flow control non/hardware/software; Indoor range to 30M; Outdoor range to 150M; Extended range in repeater mode; Built-in link diagnostics; Built-in software configurator; Remote over-air configuration; Low-current consumption; 9V PP3 or 7-15V DC operation; Low profile plastic enclosure; and Integrated PP3 battery compartment.

For more information, contact:

**LEMONS INTERNATIONAL**  
1305 POST RD., DEPT. NV  
FAIRFIELD, CT 06430  
TEL: (508) 798-5004  
EMAIL: [sales@lemonsint.com](mailto:sales@lemonsint.com)  
WEB: [www.lemonsint.com](http://www.lemonsint.com)



from a ultra-low-power 0.8uA standby mode to high performance processing in less than 6uS permitting the MCU to maintain battery saving standby mode up to 1,000 times longer than competing MCUs.

The extremely versatile high-performance 200-ksp/s + 12-bit ADC can be configured and optimized to meet the unique needs of customer's applications. The eight-channel ADC comes with a built-in programmable sample and hold, an on-chip RC oscillator, a temperature sensor, low-battery detection, and an auto scan with a 16-word buffer that supports high-speed mixed-signal processing. With the auto scan, the MCU is no longer burdened with servicing the high-speed data conversion.

In addition, the design cycle time is significantly reduced by the MSP430's embedded real-time JTAG emulation, which allows devices to be programmed either in stand-alone sockets or in system via the dedicated JTAG pins.

The entire clock system is driven by a single 32kHz watch crystal, which saves cost and reduces high-frequency EMI, eliminating the need for a second high-speed crystal. Another key advantage of the MSP430 product line is the 16-bit RISC CPU resulting in the industry's leading C code efficiency.

Samples of TI's new family of MSP430F43x/F44x are available now, with volume production planned for March 2002. The devices are packaged in a 100-pin PZ quad flat pack (QFP). Suggested pricing for the MSP430F449 in quantities of 1,000 is \$7.03. The Flash emulation tool, the MSP-FET430P440, is a complete integrated development environment available now for just \$99.00.

For more information, contact:

**TEXAS INSTRUMENTS, INC.**  
SEMICONDUCTOR GROUP, SC-01197  
LITERATURE RESPONSE CENTER  
P.O. BOX 954, DEPT. NV  
SANTA CLARITA, CA 91380  
1-800-477-8924, ext. 4500  
WEB: <http://www.ti.com>

## High Tech Video system w Audio

Includes TWO B/W Cameras w sound & I.R. (night vision) ONE 5.5" B/W Monitor with Built-In adjustable Switching (from 2 to 20 seconds) & two 60 ft. pre-wired cables. Everything you need to set up a high tech video monitoring system at home, office, restaurant warehouse or use it as a baby monitor. Easily hooks into VCR for



Video Recording also

item # Dual View  
Fantastic Price!

\$119.00 ea  
(\$109.00 ea. qty 4)  
view extensive details @ web site

2GHz RF  
Field  
Strength  
Analyzer  
ONLY  
\$1699

Best Price!

- Frequency Range: 100KHz to 2.0GHz
- Narrow Band FM (NFM)
- Wide Band FM (WFM)
- AM and Single Side Band (SSB) Modulated Signals May Be Measured
- PLL Tuning System for Precise Frequency Measurement and Tuning
- LED Backlight LCD (192x192 dots)
- Built-In Frequency Counter
- Hand-Held and Battery Operated
- All Functions are Menu Selected
- RS232C for PC Interface and Printer

#3201

See the web site for details

## Removable Hard Drive Rack

For IDE/Ultra DMA Hard Drives

This product can be used with any 3-1/2" IDE hard drive up to 1" high. It includes an electronic keypad for safe removal and insertion. Made of ABS 707 fireproof plastic. Use this product to protect sensitive hard drive data, take your hard drive between work and home or even set up different users with their own hard drives that they physically insert every time they use a PC. Other models available from C.S.I. include RH10 series and RH20 series, which are interchangeable within the same interface design (IDE or SCSI). Other Models are Available. See www.web-tronics.com under "hard drive and accessories" for more details and pictures.

We Sold Over  
18,000 in 2000!

ONLY  
\$14.95  
any qty.

RH-10C-IDE

## Removable Hard Drive Rack with Auto Door And Cooling Fan

- Auto door on the outer frame
- ABS material of outer frame, High efficiency cooling fan
- Worldwide patent pulling function handle
- CE Approved
- Coating iron bottom cover
- For IDE interface
- For 1" high 3.5" HDD
- Not compatible with our RH10 & RH20 series. Compatible with our RH17-IDE model.

ONLY  
\$18.95  
any qty.



#MR-27

Details at www.web-tronics.com

## Auto-Temp Solder Station with Ceramic Element

- With Ceramic Heating Element for More Accurate Temp Adjustment
- 3 Conductor Grounded Power Cord
- 250°C-480°C (470°F-900°F)
- Fast Heating Feature



SR-976

Extra Trip Options Available. See Web!

ONLY  
\$39

CTRL - D  
to bookmark  
this site

www.web-tronics.com

Don't forget  
the dash

Circuit  
Specialists  
Inc.

In Business  
Since 1971

- Easy to Navigate
- Includes a Search Engine That Really Works
- New Items Added Constantly

For More Info See www.web-tronics.com

## CCD B&W Board Cameras

- ASIC CCD Area Image Sensor
- Extremely Low Power Consumption
- 0.5 Lux Min Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation

Detailed Specs on the Web

- VM1030PA-B 30mmx30mmx25mm, Pinhole lens, 12V \$39.00 any qty.
- VM1030A 30mmx30mmx26mm, Standard lens, 12V \$39.00 any qty.
- VM1035A 42mmx42mmx25mm, Standard lens, 12V with back light compensation \$49.00 any qty.
- VMCB21 44mmx38.5mmx28mm, with 6 infra-red LEDs, 12V \$49.00 any qty.
- VM1036A 32mmx32mmx25mm, Standard lens 12V, reverse mirror image feature \$49.00 any qty.



## Bullet CCD Cameras

B&W and Color & Night Vision

- Smart Rugged Metal Housing
- Extremely Low Power Consumption
- 12 Volt
- CCD Area Image Sensor for Long Camera Life
- Built-In Electronic Auto Iris for Auto Light Compensation
- No Blooming, No Burning
- 0.1 Min Lux Illumination (B&W), 1 Lux Min Lux Illumination (color)
- VMBLT1020 B&W, 21mm(D)x55mm(L) \$54.00 any qty.
- VMBLT1020W B&W Weatherproof (no audio), 21mm(D)x58.5mm(L) \$79.00 any qty.
- VMBLTJC19BW COLOR Weatherproof (no audio), 17mm(D)x88mm(L) \$139.00 any qty.
- WDB-5007S Powerful night vision camera (56 IR LEDs) \$159.00 (\$139.00/5+)

Detailed Specs on the Web



new!

## COLOR CCD Mini Board Cameras

- Low Power Consumption
- 1 Lux Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation
- Internal Synchronization
- 12Volts
- 400 TV Lines

Detailed Specs on the Web

- VM3010PA 33mmx33mmx18mm, Pinhole lens with audio \$129.00 any qty.
- VM3011-A 45mmx40mmx24mm, Standard lens with audio, single board \$99.00 any qty.
- VM3010-A 33mmx33mmx32mm, Standard lens with audio \$129.00 any qty.



## DC to AC Power Inverters ! 150 watt up to 3000 watt models!

- 150w modified sine wave: \$29.95 (G-12-015B) Check Our Low Prices!
- 300w modified sine wave: \$39.95 (G-12-030)
- 150w pure sine wave: \$69.00 (G-12-150S)
- 300w pure sine wave: \$109.00 (G-12-300S)
- 800w modified sine wave: \$139.00 (G-12-800)
- 1000w modified sine wave: \$179.00 (G-12-100)
- 3000w modified sine wave (phase corrected), (G-12-300).....\$489.00

See Our web site for DETAILED Specs.!



G-12-030 300W

Our Most Sophisticated DMM We Sold Over 800 Last Year! with RS-232 Interface & Software, 3-3/4 Digit, 4000 Count, Auto-Ranging with Analog Bargraph

- True RMS Mode
- 10MHz Frequency Counter
- Time Mode with Alarm, Clock, and Stop Watch
- Dual Display
- 10 Location Memory
- Min, Max, Avg and Relative Mode
- Decibel Measurement
- Cap and Ind. Measurement
- Temperature Mode (C/F)
- K Type Temperature Probe Included
- Pulse Signal for Logic & Audible Test
- Continuity/Diode Test
- Logic Test
- Auto Power OFF/"Keep ON" Mode
- Fused 20A Input with Warning Buzzer
- Back Light
- Data Hold/Run Mode
- Safety Design UL1244 & VDE-0411
- Protective Holder
- Silicon Test Leads



NOW  
ONLY  
\$149

Reg. \$169

More Details  
on our  
Web Site

PROTEKT 506

\$129.00 ea. qty 10

## Bench Digital Multimeter w RS232C

\$99.00 !

Item#  
CSI9803R

- \*Digital & Analog Display, 3999 counts & 42 segment bar graph.
- \*Autorange & Manualrange
- \*DATA HOLD, Min/Max Relative Measurement
- \*Storage Data DISPLAY/RECALL
- \*True RMS f AC voltage & current
- \*Back Light
- \*ADP Measurement: 400mV +/- 3%
- \*Continuity & Diode test
- \*Power Source: AC or DC

See details @ web site



## O'Scope Offer

30MHz! ONLY \$299!

ONLY  
\$299



- Dual Channel
- Dual Trace
- Vert Trigger
- 1 Year C.S.I. Warranty!

Includes 1 oscilloscope probe  
Manufactured for CSI by a leading O.E.M. manufacturer. See our website for detailed specifications!

#OSC-1030

## Digital Read Out 3Amp Bench Power Supplies

Available in 0-30 volt & 0-50 volt versions

High stability digital read-out bench power supplies featuring constant voltage and current outputs. Short-circuit protection and current limiting protection is provided. Highly accurate LED accuracy and stable line regulation make the 3000 series the perfect choice for lab and educational use.

- Line Regulation:  $2 \times 10^{-4}$  / 1ma
- LED Accuracy: Voltage  $\pm 1\%$   $\pm 2$  digits
- Current  $\pm 1.5\%$   $\pm 2$  digits
- Wave Line Noise:  $\leq 1$  mVrms
- Dimensions: 291mm x 158mm x 136mm

New!  
Lower Prices

CSI3003:0-30v/0-3amp 1-4 / \$89.00 5+ / \$85.00


CSI5003:0-50v/0-3amps 1-4 / \$109.00 5+ / \$99.00

Bookmark our WEB Site! Many more Power Supplies are Available. Look Under Test Equipment



AS  
LOW AS  
\$85

# New Books

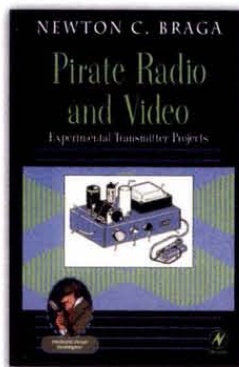

## Pirate Radio and Video **\$34.99**



Experimental Transmitter Projects by Newton C. Braga

Written with the electronics hobbyist in mind, each project includes basic diagrams, complete instructions as well as advice on how to make each project work best for you. The list of projects includes several different FM radio transmitters, AM radio transmitters, microwave transmitters, shortwave transmitters, UHF video transmitters, VHF video transmitters as well as nearly a dozen special projects for test equipment and system set-ups. If you are interested in setting up your own radio or television broadcasting system, this is the book you need!
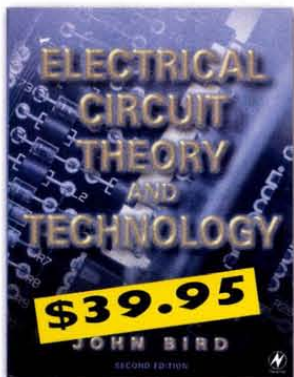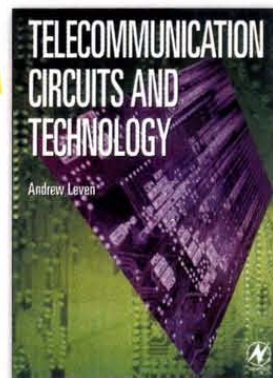
## Telecommunication Circuits and Technology **\$34.99**

by Andrew Leven

Telecommunication Circuits and Technology provides readers with a problem solving approach to understanding the fundamentals of telecommunications. The author covers the common telecommunication and data communication circuits that are currently taught at higher education level and also used in industry. Understanding is reinforced with frequent worked examples and problems for specific applications. Also includes industrial data sheets.



## Electrical Circuit Theory and Technology **\$39.95**

Second Edition by John Bird

Electrical Circuit Theory and Technology is a fully comprehensive text for courses in electrical and electronic principles, circuit theory and electrical technology. The coverage takes students from the fundamentals of the subject, up to and including first degree level. Thus, this book is ideal for students studying engineering for the first time, and suitable for pre-degree vocational courses, especially where progression to higher levels of study is likely.

John Bird's approach, based on 700 worked examples supported by over 1000 problems (including answers), is ideal for students of a wide range of abilities, and can be worked through at the student's own pace. Theory is kept to a minimum, placing a firm emphasis on problem-solving skills, and making this a thoroughly practical introduction to these core subjects in electrical and electronic engineering.



All of this month's books are available from the Nuts & Volts bookstore.  
online - [www.nutsvolts.com](http://www.nutsvolts.com) phone - 1-800-783-4624

## Homemade Lightning: Creative Experiments in Electricity **\$24.95**

by Richard Ford

Enter the wide-open frontier of high-voltage electrostatics with this fascinating, experiment-filled guide. You'll discover how to make your own equipment, how electricity is used in healing, and the workings of many experiments in high potential physics! Starting with electrostatic basics, R.A. Ford's highly praised *Homemade Lightning* entertains, instructs, and challenges. It's the only comprehensive electrostatics book packed with useful projects for serious hobbyists, students, inventors, and experimenters!

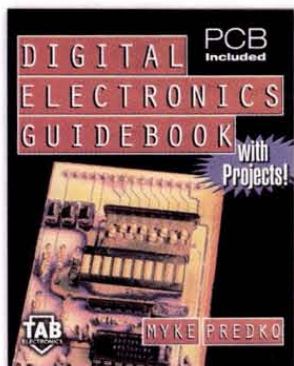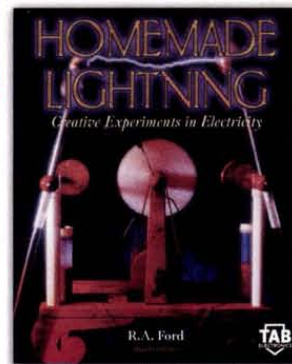Featuring beautiful illustrations from turn-of-the-century science journals of Victorian-era electrostatic generator designs, *Homemade Lightning* provides hard-to-find information on electrical anomalies — the key to the future of electrostatic research. This is a book that everyone interested in the mystery and power of lightning will treasure.



## Digital Electronics Guidebook: With Projects! **\$34.95**

by Myke Predko


Perfect for electronics hobbyists and students — even complete beginners — who want to understand digital logic and build their own low-cost logic circuits. Featuring more than 20 projects with step-by-step directions for designing, constructing, and interfacing easy-to-do TTL (Transistor-Transistor Logic) circuits.

Everything you need to rediscover the neglected art of pure digital electronics and create working projects — even a simple computer! Even includes a printed circuit board.

BASIC Stamps are
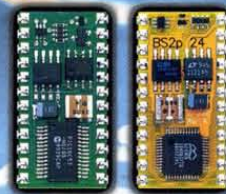
# SENSING THE WORLD

It's the unique applications and ease of use that have put the BASIC Stamp in all corners of the world. With over 50,000 customer web links and millions of BASIC Stamps in the field, chances are you can find an example of the project you want. Below is a sampling of applications available from our web site ([www.parallaxinc.com](http://www.parallaxinc.com)).




## TIME



**Project:** Set and measure time with the Phillips 8583 I<sup>2</sup>C protocol real time clock chip

**Hardware:** BASIC Stamp 2p module and Plus Pack

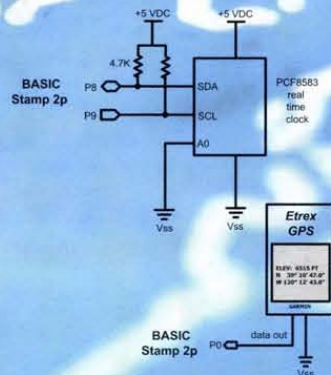**Application:** [www.parallaxinc.com/pluspack](http://www.parallaxinc.com/pluspack)




## LOCATION



**Project:** Log latitude and longitude records from a commercial GPS unit in EEPROM every two seconds

**Hardware:** BASIC Stamp 2p module and Etrex GPS

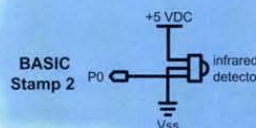**Application:** [www.parallaxinc.com/GPS](http://www.parallaxinc.com/GPS)




## INFRARED



**Project:** Read infrared remote control signals from a Sony-compatible handheld controller or detect nearby objects

**Hardware:** BASIC Stamp 2, universal remote and an infrared detector

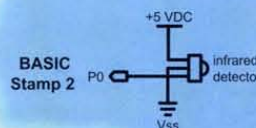**Application:** [www.parallaxinc.com/infrared](http://www.parallaxinc.com/infrared)




## LIGHT



**Project:** Measure and calibrate light levels using the sun and a photodiode in a resistor/capacitor circuit

**Hardware:** BASIC Stamp 2 and photodiode

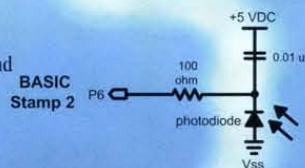**Application:** [www.parallaxinc.com/earthmeasurements](http://www.parallaxinc.com/earthmeasurements)




## TEMP.



**Project:** Construct a mini probe with an Analog Devices 592 to measure micro-climate and fluid temperatures

**Hardware:** BASIC Stamp 2 module and AD592 in resistor/capacitor circuit

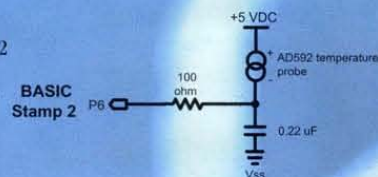**Application:** [www.parallaxinc.com/earthmeasurements](http://www.parallaxinc.com/earthmeasurements)



Visit our website to view the above projects and their corresponding products. Also, take advantage of our free documentation and software downloads.

# PARALLAX

For more on BASIC Stamps, [www.parallaxinc.com](http://www.parallaxinc.com)

BASIC Stamp and the Parallax logo are registered trademarks of Parallax, Inc.

Circle 154 on Reader Service Card.

NUTS & VOLTS MAGAZINE  
430 PRINCELAND COURT  
CORONA, CA 92879-1300

