

ROBOTICS • MICROCONTROLLERS • COMPUTER CONTROL • LASERS

Nuts & Volts

The Preferred Magazine Of The
Electronics Hobbyist/Industry

www.nutsvolts.com

August 2002
Vol. 23 No.8

Enter
The MSP430
Gadget-O-Rama 2002
Design Contest!
Cash Prizes Totaling
\$10,000!

Hands On Electronics

Build A Serial Port Thermometer

Build The Cook-Out Companion

Build The Com Port Tester

Build An FET Tester

Open Communication

Squeezing Higher Data Rates
Into Narrower Bandwidth

Amateur Robotics
Stamp Applications
Electronics Q & A

U.S. \$5.50 CANADA \$9.25



AUCTION BLOWOUT!

Over 2,000 Items on Ebay! Many from Distressed or Bankrupt Dot-Coms!



24GB Ultra SCSI DAT Tape Drives
No Minimum Bids!



Cisco Routers and Hubs
Bids Start at \$50



Sun Workstations and File Servers
No Minimum Bids!



15,000 RPM Ultra 160 Hard Drives
\$10 Minimum Bid

Disk drives cost too much. Take advantage of dot-com closeouts and bankruptcies. We're liquidating thousands of PCs, hard drives, and accessories. Visit www.scsidrives.com and name your own price! Join our mailing list for advance notice when special sale items arrive!



CORPORATE SYSTEMS CENTER

3310 Woodward Avenue, Santa Clara, CA 95054 (408) 588-1110

Adaptec ISA SCSI Cntrlr.



- ◆ AHA-1535/1535A - SCSI1 & SCSI2 conn.
- ◆ Special!! - \$17.50 with any SCSI HD!
- ◆ New units, OEM pkg, 90-day warranty

HSC#19397 \$24.95!

Cat5 Patch Cable



- ◆ Just under \$.50 each by the case!!
- ◆ Foxconn #CT88B12T88-A17
- ◆ Yellow, 12 ft. - 80 cables/case
- ◆ New, sold by case only

HSC#19234 \$39.95/case

PCMCIA SCSI!

- ◆ EPSON PCMCIA interface card
- ◆ Epson/Adaptec APA-1460B
- ◆ Up to 2MB/sec. bus rate
- ◆ For DOS, Win3.1, 95/98 & NT
- ◆ OEM pack, w/DB-25 cable
- ◆ 90-day warranty



HSC# 19160 \$49.50

PCMCIA Ethernet!

- ◆ EPSON Type II PCMCIA card
- ◆ 10Base2, 10BaseT cables incl!
- ◆ For laptops/PCs w/Type II slots
- ◆ For Windows 3.1, 95/98
- ◆ No jumpers or switches - LED status lights
- ◆ New, boxed, disk, manual, 90-day warr.



HSC# 19125 \$9.95

SuperStack II Switch



- ◆ 3Com SuperStack II Switch1000 10BaseT
- ◆ I2 MDIX ports, full duplex support,
- ◆ Multi-forwarding, advanced security,
- ◆ Virtual LAN...much more!
- ◆ New, no box - 90-day warranty

HSC# 19284 \$35.00!

PCMCIA Card Reader

- ◆ SSP Argus 2000 ISA-type reader/writer
- ◆ Dual PCMCIA Type I/II, or one Type III
- ◆ DOS/W3.1 driver diskette included
- ◆ Win95/98/NT ready
- ◆ New, w/interface, manual & cables



HSC# 19410 \$24.95

AT/ATX Motherboard

- ◆ Model 'GA-6BA' Pentium2/3
- ◆ P2s to 400MHz, P3s to 650MHz
- ◆ DIN-5 kybd skt, Intel 440BX chip
- ◆ AGP, IDE, 2SIO, PIO
- ◆ 4-PCI, 2-ISA slots & 4-DIMM
- ◆ New, OEM pack, w/CD, cables & manual



HSC# 19331 \$24.95

Disk Drive Deals!

9.1GB ULTRA SCSI

- ◆ Seagate ST19171WC, 80-pin
- ◆ 7200RPM, 4.6mS av. latency
- ◆ Wide to std. SCSI adapters - \$7.50!
- ◆ HSC 90-day warranty

HSC# 18753

\$19.95!

4.3 GB SCSI 1/2 HEIGHT

- ◆ ST15150N hard drive
- ◆ 21 Hds, 11 Disks, 3,711 Cyl.
- ◆ 7,200 RPM, 9.0 mS avg. seek
- ◆ HSC 90-day warranty

HSC# 18412

\$14.95!

4.0GB Laptop Drive

- ◆ Fujitsu MHC2040AT, 33.3MB/s(UDMA)
- ◆ 0.49"H x 2.75"W x 3.94"D
- ◆ OEM pkg, 90-day warranty
- ◆ HSC#18134 2.5" to std IDE conn. avail.

HSC# 19256

\$55.00



HSC Web Specials!

You can find these in the "Specials" area of our on-line shopping pages at
www.halted.com...
check them out, and use our secure site to place your order.

Check out our Weekly Specials!
www.halted.com

56K Modem/Hub HSC# 18942 \$17.50	10/100 Ethernet Card HSC# 19334 \$12.50	10-Base T card, ISA HSC# 18943 \$4.95
4MB PCI Video Card HSC# 19332 \$9.95!	Basic Clamp Meter HSC#AEEC2891 \$45.00	Initio SCSI Cntrlr, PCI HSC# 18218 \$9.95
Tower, cabinet, 7-bay HSC# 80544 \$42.50	Adaptec SCSI, ISA HSC# 17995 \$7.50	PCMCIA 10BaseT HSC# 19336 \$12.50
Color camera, digital HSC# 17503a \$4.95!	2000W Variable Xformer HSC#AEEC2090 \$95.00	CompactFlash Reader HSC# 19379 \$12.95!
Batt charger, NiMH HSC# 19151 \$17.50	6VDC, 12Ah lead-acid HSC# 19283 \$9.95	500W Variable Xformer HSC#AEEC590 \$45.00
A/V 'Firewire' card, HSC# 80613 \$45.00	AT Mid-Tower Cab. HSC# 19327 \$14.95	Pixie2 Tranciever Kit HSC# pixie \$9.95
SCSI scanner cntrlr. HSC# 19221 \$4.95	600 Watt Solder Pot HSC#AEEC60P \$97.50	Table Top Solder Pot HSC#AEEC10P \$32.00
ATX, 145W Power Supply HSC# 18350 \$9.95	Bargain DMM HSC#AEEC150 \$14.95	ATX 200W Power Supply HSC# 18665 \$14.95
Server Cabinet, ATX HSC# 80541 \$149.95	5V, 3.4A Power Supply HSC# 19312 \$9.95	

SCA to SCSI 1 Adptr

- ◆ Converts SCSI1 to SCA wide
- ◆ Standard 4-pin power connector
- ◆ Jumpers for LED, SYN, DLY, MTF, ID0-3
- ◆ Jumpers & config sheet incl.
- ◆ New, 90-day warranty
- ◆ Special!!...just \$7.50 with any SCSI Hard Drive



HSC#SCS3700 \$12.50!

Compact Keyboard!

- ◆ 88/89 enhanced key layout
- ◆ Finger glide mouse function
- ◆ Space Saving design
- ◆ Only 8.5" x 11.28"
- ◆ Free PS/2 connector adapters!
- ◆ New, w/mouse driver diskette and manual



HSC# 19328 \$14.95!

Call Recorder!

- ◆ Store thousands of calls on your hard drive
- ◆ Replay, sort, email, copy & transfer calls
- ◆ Software locates calls instantly
- ◆ Win 95, 98, 2000, ME, XP
- ◆ Factory refurbished
- ◆ Easy install, 5 year warranty



HSC# 19350 \$49.50

USB Network Adapter!

- ◆ Compact - perfect for notebook PCs
- ◆ Dual-speed 10/100 RJ45 jack
- ◆ Plug 'n play with Win 98, 2000
- ◆ Powered by USB port
- ◆ Compatible w/LinkSys, other USB hubs
- ◆ New, w/cable, manual, 90-day warranty



HSC# 19335 \$19.95


Win-based Terminal

- ◆ WYSE 'Winterm 2315SE'
- ◆ Virus-proof - high security
- ◆ Easy access to server apps.
- ◆ Up to 32 users/servers, tiny footprint
- ◆ VT220, VT100 and VT52 emulation
- ◆ Mouse, keyboard power supply included!



HSC#19346 \$89.50

LCD Display Modules!

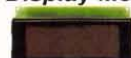

- ◆ 20 char. x 24 display
- ◆ 2.36"H x 3.86"W overall, 0.55" max. depth
- ◆ Data sheet @ <http://www.halted.com/online/index.htm>
- ◆ New, 90-day warranty

HSC# 19399 \$12.95



- ◆ 24 char. x 2 display with LED backlight
- ◆ Emerging Display Tech. # ED24200GLYU
- ◆ 1.406"H x 5.5625"W overall, 0.4375"D
- ◆ Data sheets: <http://www.halted.com/online/index.htm>
- ◆ New, OEM pack, 90-day warranty

HSC# 19400 \$9.95

HSC Electronic Supply

Since 1963!...

Silicon Valley's Electronic Marketplace

3 Retail/Wholesale Locations:

Main Office - Mail Orders...

3500 Ryder St. Santa Clara, CA 95051

Santa Clara

Sacramento

Rohnert Park

1-408-732-1573

1-916-338-2545

1-707-585-7344

Order Toll-Free:

1-800-4-HALTED (442-5833)

or...ONLINE, AT: www.halted.com

Terms: Some quantities limited; all items are subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped by UPS Surface unless otherwise specified. \$6.00 UPS charge added for COD. Visit our website for detailed information on domestic and international shipping methods.

What's in your next project ?


COMPLETE DEVELOPMENT KITS AVAILABLE



ATOM 24 MODULE
ONLY \$59.95



ATOM 40 MODULE
ONLY \$79.95

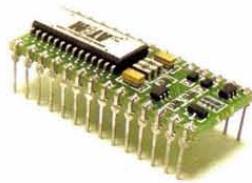

ATOM 28 MODULE
ONLY \$64.95



OEM ATOM
ONLY \$59.95



ATOM SUPER DEVELOPMENT BOARD
ONLY \$69.95

The Basic Atom is an easy to use self contained microcontroller. Download your program, apply 5 volts and your are up and running. From beginners to professionals, programming microcontrollers has never been easier !

Experiment and test code changes on-the-fly! Bring your projects to life quicker and easier with the Basic Atom IDE ! Stop wasting time strategically planting debug statements throughout your entire program. The Basic Atom software includes a built-in ICD (In Circuit Debugger). Watch your program run on screen with variables, SFRs and RAM values being updated as each line of code executes on the Basic Atom. The Basic Atom's ICD is so easy to use, even a first time user can have it up and running in minutes !

BS2p compatible syntax, with a complete expanded set of powerful and easy to use commands ! Serin, Serout, If..Then..Elseif..Else..Endif, Do..While, While..Wend, OWin, OWout, ADIn, Pulsin, Pulsout, PWM, Xin, Xout and more!

32 Bit Floating Point Math. The Basic Atom supports 32 bit floating point and integer math. This includes 32 x 32 bit divides and multiplies. With 32 bit math you can have variables containing values of up to 4 billion.

300 bytes of RAM. No more wasting time trying to save variable space in your program. Plus additional features include a built-in Analog to Digital converter, UART, 2 PWMs and more.

Order your Basic Atom today !

Explorer Robot

Introducing the Explorer Robot. The Explorer Robot is great for the robot enthusiast, educational programs, hobbyist or just about anybody interested in robotics !

The Explorer Robot chassis is made from anodized brushed aluminum. This high quality chassis provides a sturdy base for mounting servo motors, controller board and any number of add-ons. Each chassis includes elongated slots for mounting flexibility. Easily customize the Explorer Robot chassis to suit your needs.



Each Explorer Robot comes complete with two infrared obstacle sensors, ARC controller board (Based on the new Atom Pro), front caster wheel, chassis, modified servos, wiring, battery holder, software and manual. Plus the book "Experimenting with the Explorer Robot", which contains several useful projects for your new Explorer Robot.

Several Add-ons such as, Ni-Cad Cable adapter, Line Follower and more are available for the Explorer Robot.

The brains of the Explorer Robot, the ARC controller board, includes a socket for an I2C eeprom to give your robot memory, L293D motor driver to replace the servo motors or add DC motors. The ARC controller board is designed as the ideal robotics controller board. (The ARC controller board can also be purchased separately)

Order your Explorer Robot Today !

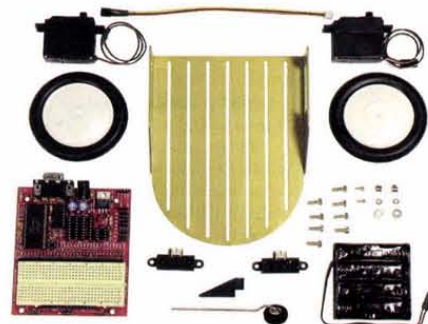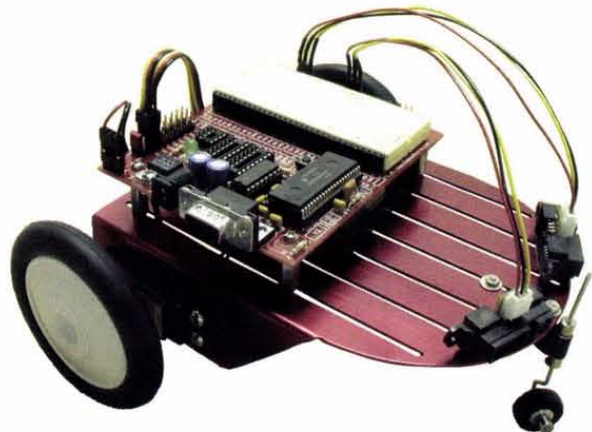AVAILABLE AUGUST 8TH
EXPLORER ROBOT KIT
ONLY \$199.95



PARTS ALSO AVAILABLE SEPARATELY



BASIC MICRO
TECHNOLOGY AT WORK

The Basic Atom is a registered trademark of Basic Micro Inc.

TO ORDER VISIT WWW.BASICMICRO.COM
OR CALL US AT 1-800-869-5095
(M-F 9 AM TO 6 PM EST)

6 A NEW AND SIMPLE WAY TO MEASURE TEMPERATURE WITH YOUR COMPUTER

Build a serial port digital period thermometer for under \$10.00.
By Ray Green

20 PRODUCT REVIEW: LINE6 GUITARPORT

If you're a "weekend warrior" musician looking for a practice or recording tool, then tune into *this* GuitarPort.
By Edward B. Driscoll, Jr.

22 A UNIVERSAL FET TESTER

When you're working with surplus FETs or FETs removed from previously used circuit boards, it's a good idea to test them prior to re-use.
By Peter Lehmann

42 THE COMPORT TESTER

You've just finished building that new gizmo of yours, plugged it into the ComPort on your PC and POOF! Smoke starts billowing from the gizmo! If only there was a way to test that ComPort to make sure it was still working ...
By Jon J. Varteresian

47 KENWOOD'S FREETALK RADIOS MAKE STAYING IN TOUCH EASY

Kenwood's series of FRS radios are well-equipped to keep communication lines open, whether you're keeping track of where your kids are or helping someone maneuver a motorhome into a tight spot.

49 UNDERSTANDING AND USING 'NORTON' OP-AMP ICs — PART 2

The operating theory and practical applications of the LM359 high-performance dual Norton op-amp are explained, plus a few more LM3900 applications are presented in this final installment.
By Ray Marston

60 BUILD THE COOK-OUT COMPANION


Play your stereo system indoors while listening to the same music outdoors with this wireless system.
By Anthony J. Caristi

62 LEARNING RVK-BASIC — PART 8

Answer the question of how to generate PWM from your AVR microcontroller and the generation and use of random numbers.
By Bob Van Kannon

75 SEPTEMBER IS BACK-TO-SCHOOL TIME

Get involved in helping to rewrite the Technician class Element 2 examination that will go into effect July 1, 2003.
By Gordon West

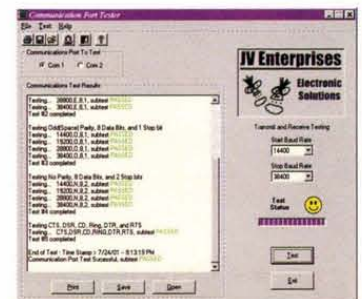

Page 42



Page 20

DEPARTMENTS

Reader Feedback	28
News Bytes	58
Tech Forum	82
Dealer Directory	48
Events Calendar	66
Electronics Showcase	45
Prize Drawing	81
New Product News	40
Classified Ads	69
Advertiser's Index	74
Gadget-o-rama Contest	57
NV Bookstore	88
Publisher's Info	28

COLUMNS

TECHKNOWLEDGEY 2002

Invasion of the robotic tunas; New technique for faster, smaller, cheaper chips; Software bugs cost big bucks; 10 GB ethernet standard approved; Single-chip audio IC for portable devices; Miniature DC motors offer high power-to-volume ratio; New low-power, zero-drift op-amps; and Computer industry achieves major milestone.
By Jeff Eckert



AMATEUR ROBOTICS

The last details of building a cheap linear actuator with some ideas for future improvements; Taking a quick dip into color; plus, a final announcement.
By Robert Nansel

ELECTRONICS Q & A



What's Up: Two IR remote control receivers, a simple KVM switch, and the definitive chart of TTL output driver circuits. Looking for hard-to-find parts?

Sources for custom panel meters, USB-to-serial port converters, and used Tektronix scopes. How to earn a CET or A+ Certification, and some very techie cool web sites.
By TJ Byers

STAMP APPLICATIONS

Digital Data Recording. Put together a simple event recorder that will monitor up to eight inputs and record changes in the state of these inputs to an external EEPROM.
By Jon Williams




LASER INSIGHT

Using a flashlamp to excite dye cells.
By Stanley York

OPEN COMMUNICATION

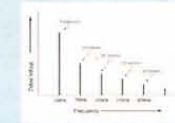Part 1: Baseband Communications. How to put 10 pounds into a five-pound bag — or — Squeezing higher data rates into narrower bandwidths.
By Louis E. Frenzel



A New and Simple Way to Measure Temperature With Your Computer

Building a Serial Port Digital Period Thermometer

By Ray Green

Here is a new and simple way to measure temperature and print it on your screen. It does this by using your computer's serial port. The best part is that you can build it for under \$10.00.

For years, I've experimented with various methods of using my computer to control various parts of my home. Many of these methods involved expensive and complex A/D and D/A converters, as well as "lookup" tables for converting a variable input to a digital interface. Throughout this time, I've been searching for a simple method to read temperature. One day while playing with a 555 timer circuit, it occurred to me that if I used a thermistor to control the duty cycle and measure it, I could convert that measurement to temperature. Sound like a dream? It was for me. Here are the results of my experiments.

You can use it to measure outside temperature, attic temperature, water heater, refrigerator, freezer or to control your heating system. It is amazingly stable and accurate, and operates over the temperature range of 0 degrees F to 120 degrees and beyond. All the parts are available at your local RadioShack and the part numbers are included in the parts list. For the sake of this article, I'll call it a "digital period thermometer" because temperature is read by measuring the period (length or duration) of a pulse.

Almost any PC-compatible computer can be used. It works fine with an old DOS-type PC or a newer one operating in DOS under any Windows program. Old computers have become so prolific that many people are giving them away. For my experiments, I used an old 486 computer.

In order to read temperature, we'll use the program SerTemp.bas as listed later in this article. It may either be typed in or downloaded from the *Nuts & Volts* web site at www.nutsvolts.com.

Now this is a most unusual way to use the serial port, since there is nothing serial about it at all and I'm simply using it as any other input/output port on your computer.

How It Works

The circuit uses a 555 timer IC connected as a one-shot multivibrator. It is operated from current stolen from the serial port so that no external power is required. A 10,000 ohm thermistor is connected to the IC in series with a 470 mH capacitor and the charge time is measured

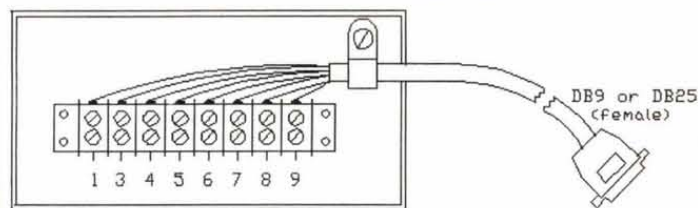
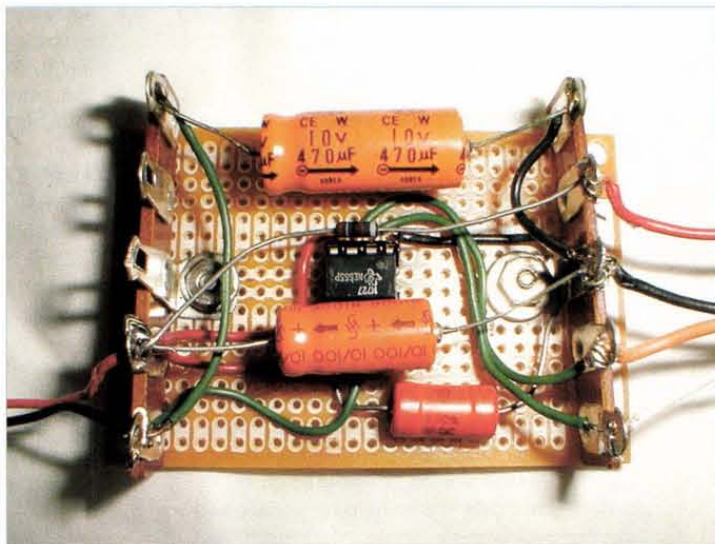


FIGURE 1

by the program. Typically, it takes nine seconds to charge the capacitor at 70 degrees Fahrenheit and about 21 seconds at 32 degrees. These long periods help achieve accurate results. The program uses a curve fitting formulae to convert the charge time to temperature and prints the value on your monitor. The wide temperature range possible is illustrated by the fact that the thermistor has a resistance of 10,000 ohms at 70 degrees, but increases to 27,280 ohms at 32 degrees Fahrenheit.

The Serial Port Connections

To use your serial port the easy way, mount an eight-position barrier strip — RadioShack part number 274-670 — on a block of wood as shown in Figure 1. Connect the eight-terminal strip through an eight-wire cable to a D-sub female connector. Use part number 276-1538 for a nine-position connector. Number the barrier strip as shown in Figure 1. These are the same pin numbers as those on the computer's nine-pin serial port. Omit pin 2 because it can't be used here. All external

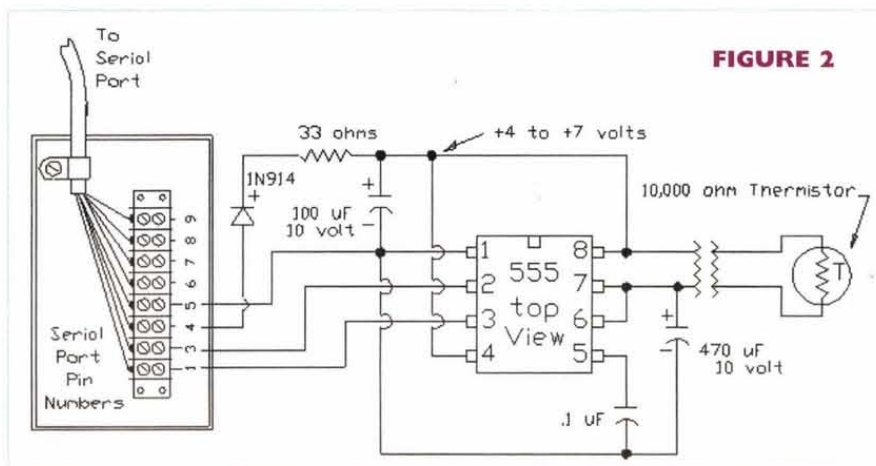


FIGURE 2

Building a Serial Port Digital Period Thermometer

devices will connect to this barrier strip.

If you are using a 25-pin serial port connection, use a DB25 part number 276-1548. Use the pin connection numbers under 25 pins on the chart, but still label the barrier strip as if it were a nine-pin port as demonstrated.

Serial Port Connector

9 pin		25 pin
Pin #1	Input	Pin #8
#3	Output	Pin #2
#4	Output	Pin #20
#5	Ground	Pin #7
#6	Input	Pin #6
#7	Output	Pin #4
#8	Input	Pin #5
#9	Input	Pin #22

The Base Addresses (like a street address) for serial port COM1: is &H3F8 and is used for all program examples in this article. If you are using COM2: as your serial port, then simply use &H2F8 as your base address in the program's line 120.

Construction

My favorite method of building most small circuits is to use a multi-purpose PC board with a five-lug tie point strip mounted at each end. This provides a platform to mount the parts on, as well as offering an easy way to connect to the circuit. I generally mount the parts on the PC board and run wires to the tie point eyelets. This leaves the actual tie point connections free for external wiring.

This is a very simple circuit using only an IC, a diode, a resistor, and two capacitors, so almost any layout will work. Figure 3 shows the board as I constructed it.

Making and Using the Temperature Probe

The temperature probe is simply a long two-conductor cable with the thermistor connected to the end, as shown in Figure 4. Any light-weight two-wire cable may be used. I found that 22- or 24-gauge stranded speaker or alarm wire works well. The thermistor, of course, measures the temperature. If used outdoors, it will be exposed to all kinds of weather so it must be covered to keep it dry. After years of trying to make thermistor probes waterproof, I finally hit on a method that works great as follows:

(1) Cut a piece of 1/8-inch diameter heat-shrink tubing about 3-1/2 inches long.

(2) Connect and solder the thermistor leads to one end of the two-conductor cable. Make your connections as small as possible and wrap each connection and the exposed wires with a small piece of plastic electrical tape. The thermistor and its connections must be small enough to slide inside the heat-shrink tubing.

(3) Use a house caulking gun and fill the tubing from one end with Dow Corning™ 100% Clear Silicone Sealant. You can also use clear bathtub caulk.

(4) Now slide the thermistor and its connections into the tube. The end of the thermistor should be about 3/4" from the filled end. Poke as much caulk back in as you can easily do.

(5) Finally, use a heat gun or a stove burner and carefully shrink the tubing around the cable and the thermistor. Take your time so you do not overheat in one spot and burn the tube (maybe you should experiment first). As you heat the tubing and it shrinks, excess caulking will come out of both ends of the tube, but wipe it away and it's no problem. Let the probe dry a day or two and you're done.

The best way to mount the thermistor probe outdoors is to strap it to a thermometer. I like to leave at least 10 feet of wire outdoors so room heat is not conducted to the thermistor. This gives you a good check on its accuracy over various temperature ranges. Of course, you will want



FIGURE 3

to calibrate it initially before you put it outdoors.

Running SerTemp.bas

You will need a copy of either the programmer's file GWBASIC.EXE or QBASIC.EXE in your computer. Practically all 386 and 486 computers prior to Windows95 have one of these files in their DOS directory. If you are using Windows 95/98/ME, copy either the file GWBASIC.EXE or QBASIC.EXE from the old PC and put it into your C:\WINDOWS\COMMAND directory. You will also need a copy of my file SerTemp.bas. Either run one of the BASIC files above and type it from the listing in this article and SAVE it, or download it from www.nutsvolts.com.

For GWBASIC, put your computer into DOS and load and run the program by typing GWBASIC SERTEMP<Enter>. As the program runs, it will display the temperature about every 10 seconds. To stop the program, hold down the Control Key and press the Break Key. The program must be stopped before you can exit or print a listing. To list the program, press F1. To run the program again in GWBASIC, press F2 or type RUN <Enter>. Don't forget to SAVE any changes you've made. To do this, press F1 to get a listing, and move your cursor to the bottom of the page to a blank line on the screen. Then press the F4 key so the word SAVE" appears and type SERTEMP",a. (the total command will read SAVE"SERTEMP",a). To exit the program in GWBASIC and go back to DOS, type the word SYSTEM on a blank line.

To run in QBASIC, put your computer into DOS and type QBASIC/RUN SERTEMP <Enter>. To stop the program, hold down the Control Key and press the Break Key. To run the program again in QBASIC, click on RUN. To exit, click on file then Exit. Note you will get an error message when you run SerTemp, if you have not connected the circuit to your computer.

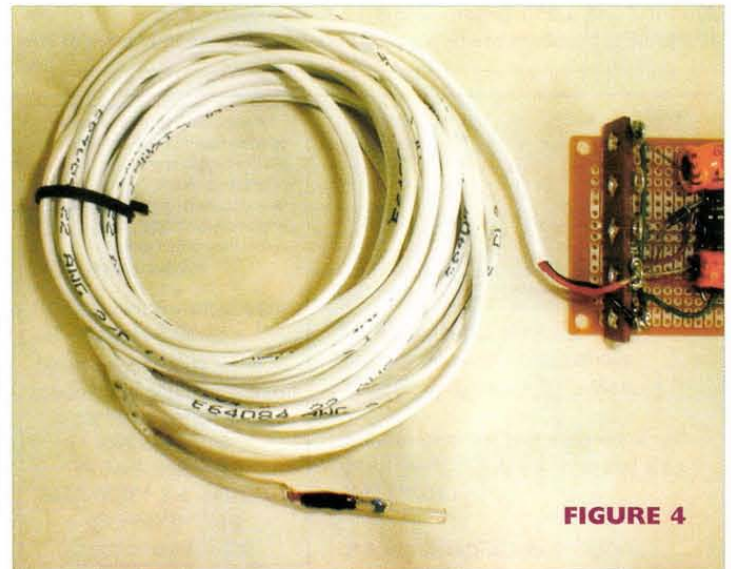


FIGURE 4

Building a Serial Port Digital Period Thermometer

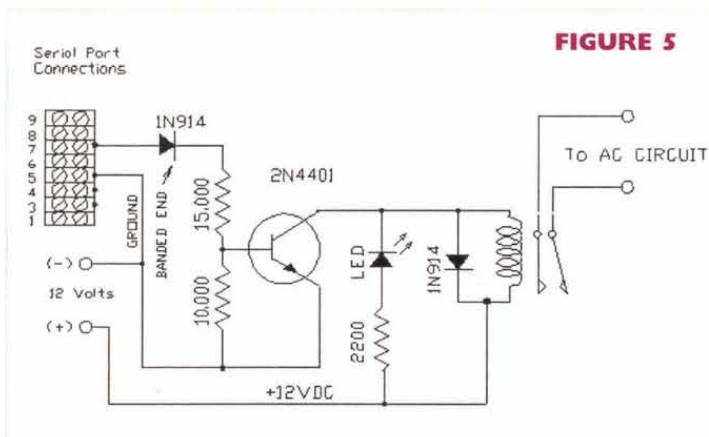


FIGURE 5

Calibrating the Temperature Readings

Due to the wide tolerance of the 470 mF charging capacitor, it is unlikely that your digital period thermometer will initially display the proper temperature. The easiest way to correct this is to simply increase or decrease the number 533 in line 240 (known as the constant) until it does so. Tie the probe to the thermometer so the probe and the thermometer bulb are touching. Let the program run for several minutes until you have a stable reading on your computer. If the temperature displayed is higher than the actual temperature, reduce the constant by about the same amount (or vice-versa).

Example: The thermometer reads 73 degrees and the computer prints 75 degrees. Changing the constant to 531 should cause the computer to print near the actual temperature of 73 degrees. The constant may also be a decimal number such as 548.3, etc. Because any unit built should exhibit a similar curve, your digital thermometer should also track over the whole temperature range. You may wish to check it at the cold end by putting the probe along with 10 feet of wire and a thermometer into your freezer.

The curve fitting equation in line 160 was calibrated by using a curve fitting program. I used 32 temperature vs. period readings over the range of 0 to 120 degrees Fahrenheit. I was able to achieve an accuracy of 1/4 degree over most of the range.

The temperature is a function of the logarithm of the period:

$$T = A + (B * \log(P)) + (C * \log(P)^2)$$

The Program

```
10 CLS : KEY OFF: REM "SERTEMP.BAS" 8/14/01
20 PRINT "'SerTemp' measures temperature by measuring time to
  charge Capacitor"
30 PRINT " in a 555 Timer using a 10 K ohm thermistor."
40 REM Pin Numbers are (9 pin plug) connections are to the Serial Port.
```


```
50 REM Program starts by switching on +4 to +11 Volts from Ser Out
  pin 4
60 REM Wait 2 Sec for warm-up.
70 REM Next Switches pin 3 'Lo' by using Command: OUT BAS + 3, 0
80 REM Next Switches Pin 3 'Hi' again with Command: OUT BAS + 3,
  64
90 REM This forms a trigger input pulse for the 555's input.
100 REM The 555 raises pin 1 'Hi' until cap is charged, sending pin 1
  'Lo'
110 REM When pin 1 goes 'LO', charge time is converted to tempera-
  ture
120 BAS = &H3F8: REM COM1: Base Address, Change to &H2F8 for
  COM2:
130 X = 1: OUT BAS + 4, X + Y: REM Puts Vdc on pin #4 thru IN914 for
  power
140 TI = TIMER: WHILE TIMER < TI + 2: WEND: REM 2 Sec Timer
150 LOCATE 4, 6: PRINT "Start time test"
160 OUT BAS + 3, 0: TIM = TIMER: OUT BAS + 3, 64: REM Pin 3
170 REM PRINT INP(BAS+6) AND 128
180 WAIT BAS + 6, 128, 128: REM Wait till Pin 1 goes 'LO'
190 REM PRINT INP(BAS+6) AND 128
200 P = (TIMER - TIM) * 100
210 LOCATE 4, 6: PRINT "Test Over "
220 X = 0: OUT BAS + 4, X + Y: REM Turn Off pin 4
230 LOCATE 8, 5: PRINT USING "Period = ###.## Seconds"; P / 100
240 T = 533 - 88.6299 * LOG(P) + 3.0209 * LOG(P) ^ 2: REM 10 K
  Therm
250 LOCATE 10, 7: PRINT USING "Temp = ###.##"; T
260 REM IF T < 70 THEN Y = 2 : LOCATE 12,6 : PRINT "Relay On "
270 REM IF T > 72 THEN Y = 0 : LOCATE 12,6 : PRINT "Relay Off"
280 REM OUT BAS + 4, X+Y: REM turn pin 7 On or Off
290 TI = TIMER: WHILE TIMER < TI + 2: WEND: REM 2 Sec Timer
300 GOTO 120
```

Note that the address in line 280 also contains a value for X which controls the output on pin 3, in line 130 in case it is also calling for output. Thus the value for X+Y may be 0, 1, 2, or 3.

Control Something Using Temperature or Time

I used the relay circuit in Figure 5 in my Nov. 2001 article "Control Lights, a Burglar Alarm, and Other Circuits using the Computer's Serial Port." I've found it to be reliable and easy to build. It connects to the output bit on pin 7 which is not used for the temperature measurement. Use it to control anything such as an attic fan, your heating system, or to sound a temperature freeze alarm. It may be operated with a battery using the #275-005 nine-volt relay or with a 12-volt DC adapter using the #275-248 12-volt relay.

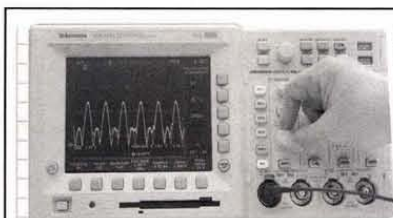To use the relay with the program "SerTemp.bas," remove the first REM in lines 260, 270, and 280. This is an example of using the relay for heating control. Set your on and off temperature desired in lines 260



Learn the fundamentals of oscilloscope operation expertly presented by a college professor!

Our **videotape** and **training manual** gets you on track to effectively using a scope **fast**.

Includes **certification** exam!

In this program, you'll **learn** how to:

- operate basic scope controls
- set the trigger level
- read the graticule
- take accurate measurements
- analyze waveforms
- select the correct probe
- ... and much more!

Introductory Price: \$24.95
+ \$5.00 S/H (US)

To order your vhs tape and training manual, send check or money order to:
SYSPEC INC.
PO Box 2546
Syracuse, NY 13220-2546
1-877-SYSPEC1
www.syspec.com


The IndustroLogic Advantage!

Complete control systems for the price of an SBC.

Great products that can be used as RS-232 serial data acquisition boards or as standalone industrial controllers with on-board Tiny Machine BASIC!


All include development software, programming examples, power supply, and RS-232 cable.

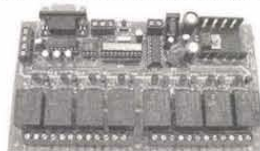RC51 \$129 - 8 10 amp relays, 4 digital I/O




Easy to use screw terminal connections

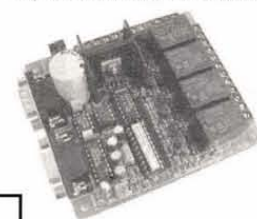TC51 \$129 - 2 12 bit A/D, 4 digital I/O, 4 10 amp relays, LCD support



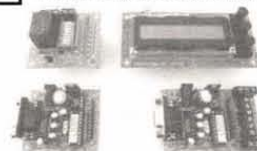T51 family starting at \$49 - Relay, LCD, and LED plug-ins



IndustroLogic

3201 Highgate St. Charles, MO 63301 USA
(636) 723-4000 (800) 435-1975
www.industrologic.com

Building a Serial Port Digital Period Thermometer

Parts List

All of the parts below are shown with their part numbers as listed in the RadioShack catalog.

- 1 - Multipurpose PC board #276-150
- 2 - Five lug wire tie points #274-688
- 1 - Eight-pin IC socket #276-1995
- 1 - 555 Timer IC #276-1723
- 1 - 10K ohm Thermistor #271-110
- 1 - 470 mF, 35V Capacitor #272-1018
- 1 - 100 mF, 35V Capacitor #272-1016
- 1 - .1 mF, 50V Capacitor #272-1069
- 1 - 33 ohm Resistor #271-1104
- 1 - Heat Shrink Tubing #278-1610
- 1 - Two-conductor speaker wire #278-1301 (24-gauge stranded)
- 1 - Nine-pin female connector #276-1538 (solder D-sub type)

Notes: The heat shrink tubing, speaker wire, and female connector are all optional if you already have something else to use. You will also need two 4-40 x 1/4" bolts, nuts, and washers to secure the tie points to PC board.

and 270. Connect the home thermostat contacts across the relay contacts and set the thermostat to turn off above the temperature in line 270 for fail safety.

Of course, you can modify the above lines to control anything you desire. Another example for night light switching:

```
260 Y = 0 : IF TIME$ > "19:30:00" AND TIME$ < "23:30:00" THEN  
    Y = 2  
270 IF Y = 2 THEN LOCATE 11,6 : PRINT "Relay On"  
275 IF Y = 0 THEN LOCATE 11,6 : PRINT "Relay Off"  
280 OUT BAS + 4, X + Y : REM turn pin 7 On or Off
```

Reading and Writing to the Serial Port

I'm presenting this section to help you understand how to read and write to the serial port. The serial port as we are using it has four available inputs and three available outputs.

Input Bit Connections

Here's how to read each of the four inputs using the BASIC com-

mand INP followed by the address as follows:

For pin #1 input: $IN1 = ((INP(\&H3FD) \text{ AND } 128) = 128)$
For pin #6 input: $IN6 = ((INP(\&H3FD) \text{ AND } 32) = 32)$
For pin #8 input: $IN8 = ((INP(\&H3FD) \text{ AND } 16) = 16)$
For pin #9 input: $IN9 = ((INP(\&H3FD) \text{ AND } 64) = 64)$
Pin #5 is circuit ground.

An input will read "0" when open and switch to "1" when an external voltage over +5 volts is applied. Example: The command to PRINT IN9 will return a "0" on your screen when pin 9 is open, and a "1" with a +6 volts battery connected to ground.

Output Bit Connections

In the "off" or "0" position, each output connection will measure about -1.1 volts between the output pin and ground. To switch any of the three output bits to "0," use the BASIC command OUT with the address followed by a zero:

Pin #3 Output: $OUT \&H3FA, 0$ (Base address + 3)
Pin #4 Output: $OUT \&H3FB, 0$ (Base address + 4)
Pin #7 Output: $OUT \&H3FB, 0$ (Base address + 4)
Pin #5 is circuit ground.

In the "on" or "1" position, each output connection will measure about +1.1 volts between the output pin and ground. To switch any of the three output bits to "1," simply use BASIC command OUT as follows:

For pin #3 Output: $OUT \&H3FA, 64$ (Base address + 3)
For pin #4 Output: $OUT \&H3FB, 1$ (Base address + 4)
For pin #7 Output: $OUT \&H3FB, 2$ (Base address + 4)
To switch both pin #4 and pin #7 to "1," use: $OUT \&H3FB, 3$

Each output may be connected to a similar relay circuit as used on pin 7 in this article.

The real reward for any author is hearing from his or her readers. Please let me know how you liked the article and if you have any questions.

My email address is raygreen@juno.com. NV


Save 62%
off the
newsstand price!

**Subscribe today
and get
Nuts & Volts
delivered to your
door each month.**

**Call
1-800-783-4624
or order online
at
www.nutsvolts.com**

Microprocessor Hands-On Training

The PRIMER Trainer is a flexible instructional tool featured in a Prentice Hall textbook and used by colleges and universities around the world. Ruggedly designed to resist wear, the PRIMER supports several different programming Languages including Assembler, Machine Language, C, BASIC, and FORTH. A comprehensive Instruction Manual contains over 25 lessons with several examples of program design and hardware control. The Applications Manual provides theory and sample code for a number of hands-on lab projects.

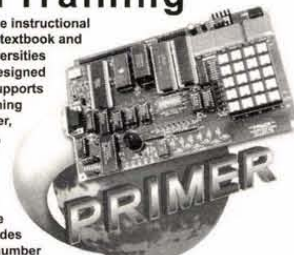

Application Projects Include:

- Scan Keypad Input & Write to a Display
- Detect Light Levels with a Photocell
- Control Motor Speed using Back EMF
- Design a Waveform Generator
- Measure Temperature
- Program EPROMs
- Bus Interface an 8255 PPI
- Construct a Capacitance Meter
- Interface and Control Stepper Motors
- Design a DTMF Autodialer / Remote Controller

The PRIMER can be purchased as an unassembled kit (\$120) or as an assembled/tested kit (\$170). Upgrades provide battery-backed RAM and PC connectivity via an RS232 serial port (shown in picture). Additional options include a heavy-duty keypad (shown in picture) and a 9V power supply - see our website. Quantity discounts are available. Satisfaction guaranteed.

Since 1985
OVER
16
YEARS OF
SINGLE BOARD
SOLUTIONS

EMAC, inc.
Phone 618-529-4525 Fax 618-457-0110
2390 EMAC Way, Carbondale, Illinois 62901
World Wide Web: <http://www.emacinc.com>

Circle #33 on the Reader Service Card.

Tools for the Imagination

Micro Modules



Specialty Products

RTC Processor Boards



With dozens of embedded controllers and countless configurations, we can help you turn your imagination into reality. For a complete look at our product line, visit our website at www.micromint.com.

Micromint

www.micromint.com

(800) 635-3355

Circle #34 on the Reader Service Card.

Simply said, the ultimate discount electronic parts site has arrived...

ELECTRONIX.COM

Electronix Corporation - 1 Herald Sq - Fairborn, Ohio 45324 (937) 878-1828

TechKnowledge 2002

Advanced Technologies

Invasion of the Robotic Tunas

Let's say you're on vacation at an oceanfront resort, and you scurry down to the beach and throw yourself into the surf. Suddenly an eight-foot, 300-pound yellow-fin tuna begins circling around you. The good news is that it is harmless. The bad news is that you won't be having it for dinner, because it is "Robotuna," a prototype from Draper Laboratory, Inc. (www.draper.com).

The unit's proper name is Vortical Control Unmanned Underwater Vehicle (VCUUV). Named after the vorticity control flow control mechanisms employed by fish to propel and maneuver, the VCUUV mimics the form and kinematics of a real tuna. Several times more maneuverable than conventional unmanned devices, this type of propulsion is said to offer significant advantage in tight quarters, and Draper envisions entire schools of the fish for use in undersea exploration, recovering unexploded mines, laying cable, and other practical applications.


According to Draper, across the broad spectrum of fish form and movement, tuna are most

desirable as a vehicle platform, as they are streamlined, relatively rigid in the forebody, and propelled with low-amplitude movements in conjunction with a high-performance hydrofoil (caudal fin). Most tuna swim continuously at one to two body lengths per second, but can burst to speeds in excess of 10 lengths per second. Additionally, tuna are highly maneuverable as compared to conventional underwater vehicle systems, due largely to the integrated nature of the main propulsor and maneuvering control surfaces.

New Technique for Faster, Smaller, Cheaper Chips

In a discovery that could significantly reduce the size and cost of computer chips, researchers at Princeton University (www.princeton.edu) have found a fast method for printing ultrasmall patterns in silicon wafers. According to a recent press release, the method could allow electronics manufacturers to increase the density of transistors on silicon chips by 100-fold while streamlining the production process.

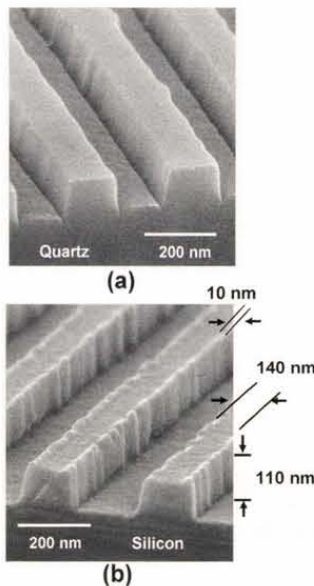The method — called laser-assisted direct imprint (LADI) — involves pressing a mold against a piece of silicon and applying a



The LADI Process: (a) quartz template used to press ultra-small patterns into silicon and (b) the pattern as it appears in silicon. The measurements are in nanometers (billionths of a meter).

laser pulse for just 20 billionths of a second. The surface of the silicon briefly melts and resolidifies around the mold. Researchers in electrical engineer Stephen Chou's lab have used the technique to create patterns with features measuring 10 nm only. The method avoids the step of etching (i.e., photolithography), which is typically used to make small patterns in silicon. While the etching process takes 10 or 20 minutes to produce a single chip, Chou's imprint method accomplishes it in a quarter millionth of a second.

The process is based on an excimer laser, which is commonly used in laser surgeries because it can heat just the thinnest surface layer of a material without causing damage underneath. Using conventional etching, Chou made a template of the pattern he wanted out of quartz, which is transparent to the laser beam, and pressed it against the silicon. A brief laser pulse melted the silicon

surface around the mold. The silicon does not stick to the quartz.

In addition to its commercial applications, the discovery opens an interesting avenue of scientific research, according to Chou. Understanding the physics behind melting and solidifying on such small scales will require input from many fields, including materials science, mechanics, and microfluidics.

Computers and Networking

Software Bugs Cost Big Bucks

There are very few product categories in which consumers actually believe that major defects are routine and inevitable, but computer software appears to be one of them. In 2000, total sales of software in the US reached the \$180 billion level, backed by a workforce of 697,000 software engineers and 585,000 computer programmers. We know that many software products are sold without being adequately debugged, but until recently, it was impossible to quantify the problem. But now we know.

According to a newly released study commissioned by the Department of Commerce's National Institute of Standards and Technology (NIST, www.nist.gov), software bugs are now so prevalent and detrimental that they cost the US economy an estimated \$59.5 billion annually. This represents about 0.6 percent of the gross domestic product (and about twice the recent value of Bill Gates' Microsoft stock holdings). More than half of the costs are borne by software users, with the remainder absorbed by software developers and vendors. The study also found that more than a third of the related costs (approx. \$22.2 billion) could be eliminated if developers would implement improved testing to identify and remove software defects earlier.



Draper's "Robotuna" may have applications in undersea exploration, clearing mines, and laying cable. Source: The Charles Stark Draper Laboratory, Inc., Cambridge, MA, USA.

Currently, more than half of all bugs are not found until "downstream" in the development process or when users discover them.

NIST funded the study, which was conducted by the Research Triangle Institute (RTI) in North Carolina as part of a joint process to help identify and assess means of improving software-testing capabilities. You can download a free copy of the 309-page NIST Planning Report 02-3 — The Economic Impacts of Inadequate Infrastructure for Software Testing — from www.nist.gov/director/prog-ofc/report02-3.pdf. Hopefully, software developers will get a copy and clean up their test processes. In the meantime, it is up to users to reject defective products, demand a refund, and pressure the software industry to do a better job.

10 GB Ethernet Standard Approved

The recently released IEEE Standard 802.3ae®, a new standard from the Institute of Electrical and Electronics Engineers (www.ieee.org), extends the speed of Ethernet operations to 10 Gbit/s and provides for linking Ethernet local area networks (LANs) to municipal and wide area networks (MANs and WANs). The new standard, which offers a direct upgrade path for Gigabit Ethernet backbones, is specified for fiber optic media and uses full duplex operation. Its optical interfaces provide options for single mode fibers at distances up to 40 km

and for multimode fibers at distances to 300m. The new standard uses the same management architecture as appears in earlier Ethernet standards. In enterprise applications, this will allow most users to keep using their installed architecture, software, and cabling.

The standard reaches beyond Ethernet's traditional LAN space and enables connection to other networking technologies. An optional WAN physical layer allows 10 Gbit/s Ethernet links to be extended over MAN and WAN distances. The WAN PHY maps the Ethernet frames into a synchronous optical network/synchronous digital hierarchy (SONET/SDH) payload. As a result, service providers can create high-speed, longer-distance Ethernet links at a competitive cost by using existing infrastructure. For further information on IEEE 802 standards projects, visit www.ieee802.org/.

Circuits and Devices

Single-Chip Audio IC for Portable Devices

National Semiconductor Corp. (www.national.com) recently introduced the LM4854, an integrated Boomer® stereo headphone amplifier and monophonic speaker amplifier designed for use in small portable electronics such as cellular phones, PDAs, and notebook computers. The LM4854 integrates a 1.9W mono speaker amplifier and an 85 mW stereo



Quick Without the Click!
National Semiconductor's LM4854 audio chip offers click suppression circuitry in a dual-amplifier package. Courtesy of National Semiconductor Corp.

headphone amplifier for use in 3V and 5V systems. This device has a 0.1 ms turn-on and turn-off time. Switching from mono BTL to an SE headphone configuration is accomplished using a headphone sense pin.

The device features pop and click suppression circuitry for quieter turn-on and turn-off, and the device eliminates output coupling capacitors, saving component count and board space. Other features include an active-low micropower shutdown mode, an "instant-on" low-power standby mode, and thermal shutdown protection circuitry. The LM4854 is available in 12-bump micro SMD, 14-pin LLP, and 14-pin TSSOP packaging, and the price is \$1.10 in 1,000-unit quantities.

Miniature DC Motors Offer High Power-to-Volume Ratio

A new family of precision miniature in-line DC motors, encoders, and gearheads from Micro-Motors Co. (www.micro-motors.co.uk/) offers a diameter of only 12 mm. The new coreless DC-micromotor type 1224 —

available with 6, 12, and 15V ratings — is designed to offer a high power-to-volume ratio. The ironless skew-wound rotor uses patented System Faulhaber® technology and features low inertia for fast acceleration and high efficiency. The motor delivers up to 1.3W, 13,900 rpm, and stall torque of 3.7 mNm.

A choice of two all-metal gearheads offers a variety of combination options. Type 12/4 provides true planetary gearing in a compact design with torque and load-carrying capacity of up to 450 mNm. The zero-backlash spur gearhead type 12/5, with pre-loaded gears, offers precision backlash-free output shaft movement with up to 100 mNm torque. Reduction ratios from 4:1 to 2,050:1 provide flexibility for applications that require a large speed range. The in-line magnetic encoder Type 30B uses solid-state Hall sensor technology for velocity and position control of the DC-micromotor. It features two-channel TTL-level output with 10 lines at a frequency range of up to 7.2 kHz. This miniature drive is intended for motion control applications in such fields as precision instrumentation, medical equipment, security devices, automation, robotics, and aerospace.

New Low-Power, Zero-Drift Op Amps

Texas Instruments (www.ti.com) recently introduced a line of low-power zero-drift operational amplifiers from the company's Burr-Brown product line. According to the company, they are particularly well suited for precision, power-sensitive applications such as handheld test equipment, medical instrumentation, temperature measurement, transducer signal amplification, electronic scales, automotive systems, and battery-powered instruments.

The OPA334 and OPA335 op-amps are available in micro-size SOT23 packages and feature low quiescent current (300 μ A), single supply operation, and rail-to-rail output swing within 10 mV of the rails. The devices use auto-zeroing techniques to provide ultra-low offset voltage (1 μ V typical) and near-zero drift over time and temperature (0.02 μ V/C).

The OPA334 family includes



Micro-Motors' Type 1224 miniature DC motor is available with 6, 12, and 15V ratings. Courtesy of Micro-Motors Co.

EPROM+

A device programming system
complete info at www.arlabs.com

♦ EXCEPTIONAL POWER FOR THE PRO
♦ EASY-TO-USE FOR THE NOVICE

Here's what you get: A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters*. Comprehensive, easy-to-use software which is specifically designed to run under Windows 95, 98, ME and DOS on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

Broad device support: Including FIRST GENERATION EPROMS (2708, TMS2716*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080) 8 MEG, 40 and 42 PIN EPROMS* (27C1024-27C322) 32 MEG) EEPROMS (2816-28C010) PLUS ER5901, FLASH EPROMS (28F29C, 29EE, 29F) 32 MEG), NVRAMS (12, 20, 22, 10/12) 8 PIN SERIAL EEPROMS* (24, 25, 85, 93, 95, 8001A) PLUS E1400/M58657* BIPOLAR PROMS* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS* (874X, 875X, 87C5X, 87C75X, 89C) ATME MICRO* (89S, 90S) (AVR) PIC MICRO* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICRO* (68705P3/U3/R3, 68HC705C8/C9/J2/P9, 68HC11 all families)

\$289

Includes step-by-step tutorial plus explanation of EPROM fundamentals \$7.00 SHIPPING + \$6.00 C.O.D.
 1 YE. AR WARRANTY - 30 DAY MONEY BACK GUARANTEE
*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150
 (513) 831-9708 FAX (513) 831-7562
 website - www.arlabs.com email - arlabs@worldnet.att.net

VISA • MASTERCARD • AMEX
 MADE IN THE U.S.A.

Tech 2002

a shutdown mode that allows it to be switched from normal operation to a standby current that is less than 1 μ A. The OPA334 and OPA335 operate on single or dual supplies as low as +2.7 V (± 1.35 V) and up to +5.5V (± 2.75 V). All versions are specified from -40°C to +125°C.


The OPA334 (single version with shutdown) comes in a SOT23-6. The OPA335 (single without shutdown) is packaged in a SOT23-5 and SO-8. The OPA2334 (dual with shutdown) comes in an MSOP-10. The OPA2335 (dual without shutdown) is available in an MSOP-8 and SO-8. The OPA334 and OPA335 are priced from \$0.95 retail in 1,000 piece quantities. The OPA2334 and OPA2335 are priced from \$1.50 in 1,000 piece quantities.

Industry and the Profession

Computer Industry Achieves Major Milestone

It has been said that the bravest man who ever lived was the one who was first to eat an oyster. Likewise, we can now look back and marvel at the courage of whoever bought the first personal computer. If we start by looking at machines that enjoyed moderate commercial success, we have to go back to 1975 and the 4.77 MHz Altair 8800 machine, powered by an Intel 8080 chip, loaded with 256 bytes of memory, and selling for \$439.00 (in kit form) or \$621.00 (preassembled). It came standard with 256 bytes of memory, but for an additional \$264.00, you could add a 4k memory board.

Not much more than a quarter of a century later, according to Gartner Dataquest (www.dataquest.com), someone, somewhere, bought the world's billionth personal computer in April 2002. While there is no way of telling what brand or configuration it was, we can be relatively certain that it bears little resemblance to the primordial Altair. Gartner is predicting that the two-billionth computer will probably be sold in 2008, quite possibly in China, Latin America, or Eastern Europe, where the greatest growth is expected to occur. **NV**



"Encyclopedia of Electronic Circuits" Vol 7
by Rudy Graff
Designed for quick reference and on-the-job use, the Encyclopedia of Electronic Circuits, Volume 7, puts over 1000 state-of-the-art electronic and integrated circuit designs at your fingertips. Organized alphabetically by circuit type, this collection includes designs from industry giants such as Advanced Micro Devices, Motorola, Tele-dyne, General Electric, and even right here in *Nuts & Volts*.


www.SMDRework.com

Your SMD Rework Specialist


800-394-1984

As a paid subscriber to *Nuts & Volts*, you'll receive **10% off** the list price!! Let's see, that's $\$39.95 - 10\% = \35.95 Wow! What a deal \$35.95 for over a thousand circuits. This book is huge! It weighs over **5 pounds** and has about a bazillion pages. If you don't have one already, what are you waiting for!!! It doesn't get any better than this!! (See page 88 to order.)

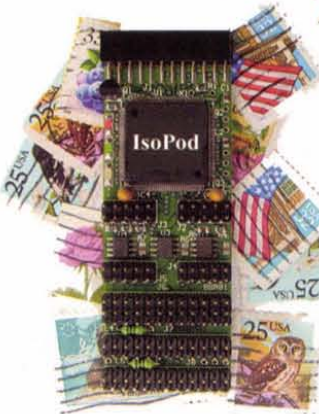IsoPod™ New First Class controller cancels old stamps.



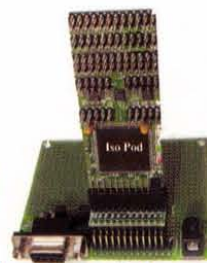New generation micro computer, tiny, and feature packed, yet connectorized so you can get to the good stuff! A wonderful motion control board.



Plugs into existing stamp sockets w/ option adapter

Feature for feature, the stamps are licked.

Feature	IsoPod™	Basic X-24 TM	Basic Stamp 2(R)	Basic Stamp SX(R)
I/O Lines	16 + 12 PWM + 8 A/D + SPI + CAN...	16 +	16	16
FLASH/EEPROM	64KBytes Prog. 8KBytes Data Flash	32KBytes EEPROM	2KBytes EEPROM	(2K X 8) = 16K
RAM	1KBytes Prog. 4KBytes Data	400 Bytes	32 Bytes	96 Bytes
Program Execution	200,000+ Instructions/sec.	65,000 Instructions/sec.	4000 Instructions/sec.	10,000 Instructions/sec.
Program Length	16000+ Instructions	8000+ Instructions	~500 Instructions	~500 instructions/2K
Analog Inputs	12 Bit ADCs (8Ch) separate pins	10 Bit ADCs (8Ch)	Timed R/C	Timed R/C
Multitasking	Yes! Coded w/Re-entrance in mind	Yes (sort of)	No	No
Programming Language	Forth (3rd party C now) (IsoMAX™, Basic, C soon)	Xbasic	Pbasic	Pbasic
Floating Point	Yes	Yes	No	No
Programming Interface	Parallel, Serial, JTAG/OnCE Interactive debugging with board	Parallel and Serial	Serial	Serial
RS232 Serial I/O	Yes, true levels	Yes	Yes	Yes
RS422 Serial I/O	Yes, on separate connector	No	No	No
SPI Interface	Yes, on separate connector w/4 I/O	Hardware, memory	Software	Software
CAN 2.0 A/B Bus	Yes, on separate connector	No	No	No
JTAG/OnCE	Yes, on separate connector	No	No	No
Servo PWM Outputs (Hardware)	12 Ch, on separate servo oriented connector, independent or 2per complementary pairs, 15-bit counter w/resolution to 25ns	2 Ch	Software	Software
Quadrature Decoder Inputs (Hardware)	2 Ch, Decoder logic, 32-bit Position Counter, 16-bit Revolution Counter, up to 40 MHz count rate	No	No	No
Motor Control	Up to 2 3-phase Brushless DC prog. complementary PWM w/dead time, or 12 independent h/w servo ch.	2 PWM	(PWM software)	(PWM software)
General Purpose Timers	2 Quads w/4 16-bit Timers each, Cascadable, Input Capture, Output Compare, Up/Down	Three	One	One
On-Board LEDs	3 (Red, Yellow & Green)	2 (Red & Green)	No	No
Package	1.2"x3", 24-pin DIP connection w/ribbon or module adapter	24-pin DIP module	24-pin DIP module	24-pin DIP module

NMII

New Micros, Inc.

1601 Chalk Hill Rd, Dallas TX 75212

Tel. (214) 339-2204 Fax (214) 339-1585

www.newmicros.com

BRAND NEW, VIDEO MOTION SENSOR. The model VM-10 connect to any standard video signal and you've got an electronic "watchman" diligently watching the entire scene. Or any adjustable sized area within the scene. Such as a doorway or even a drawer or cabinet. A state of the art security aid. The unit will close a contact when it senses a change. Auto or manual reset. Internal buzzer with volume control and adjustable on time. VCR record and VCR stop output. (use with time lapse VCR.) 110VAC powered. Adjustable sensitivity. Video loop through. **VM10...\$179ea.**



WE ARE LOOKING FOR UNIQUE ELECTRO-OPTICAL, MOTION CONTROL DEVICES AND RELATED. PLEASE FAX US YOUR LIST OF AVAILABLE MATERIAL.

SERIOUSLY SIZED SERVOMOTOR SLIDE, provides 21" of precise travel. But Wait...There's More!



These heavy duty, motorized linear slides, do their sliding on 3/4" diam. Thompson steel rail. The X axis is motivated by a substantial 3.4" diam. EG&G servomotor type: ME3515-191B with an EG&G 1000 count encoder driving a flex coupled 1/2" pulley which belt drives 2.2" diam. transfer pulley which direct drives the 1.5" final drive pulley which moves the 0.6" wide toothed belt which moves the carriage. The X axis carriage contains a motorized rotary unit with the same type EG&G servomotor driving a 5.5" diam. 1/4" thick aluminum platter mounted at about a 20 degrees angle to the base. Rotation is via an anti backlash gearing system directly driven by the motor. Supporting all these goodies is a welded, 3" wide steel channel frame. The system overall size is: 45" x 14.25" W x 8.75" H. These units must ship via truck. Very limited quantity. These are used in good condition. **XSIDE-ROTARY..... \$229 ea. or 2 for \$399**

NEW, GM960R TIME LAPSE VIDEO RECORDER

Finally a brand new, 4 head, 1/4" recorder with all the features at a price you can afford. Features: • Up to 960 hours on a standard 1-20 VHS tape • 12 different modes for record and playback • Audio recording in the 12H and 24H mode • 30Day memory backup • Easy mode setting • On-screen menus • Auto-Repeat recording mode • Serial or One-shot recording • Time, Date, speed, and Alarm indicators on screen. These deluxe units are front loading and are 14"W x 3.5"H x 12.2"D. 110VAC powered. **SPECIAL, GM960R-VCR\$379ea.**



SUPER, f1.8, 10x SURVEILLANCE LENS, Perfect for long range observation.



New, Fujinon, 11mm to 110mm ZOOM optics, standard C-Mount. Make any of our C-Mount camera a long range stealth-cam! WOW! Provides 20X on a 1/3" CCD camera. A super lens. Edmunds' price \$800 **11-1102M-1.....\$249ea.**

B&W QUAD PROCESOR,



The GM4-BQ is an unbeatable value. Four camera inputs with loop through. Full screen image, REAL TIME display, high resolution: 960 x480, brightness adj. for each chan. Alarm time 1-20 sec 1 alarm inputs. Auto Sequencing mode with dwell 1-4 sec. Quality video processing. Specs: • 4 video inputs • 1 monitor out and VCR in/out, • 4 alarm inputs • Buzzer • 2 Alarm Out • Dim: 239 x166 x55 mm. **GM4-BQ QUAD.....\$179**

SPECIAL, CARL ZEISS, S-PLANAR LENS, GCA type 37, 1.4/75, M1.5nA-0.30,

A fantastic lens with a current replacement cost of \$20K. Extremely flat field and extremely high quality.




Removed from water-lithography system, excellent condition. **ZEISS-PLANAR...\$495..NOW\$395**

A SECOND SERIOUSLY SIZED SERVOMOTOR SLIDE, By ANORAD, Provides 23.5" of Precise Travel. But Wait...There's a Z AXIS BONUS!



These SUPER HEAVY DUTY, motorized linear slides, do their sliding on crossed roller bearings. The X axis is motivated by a 2.25" diam. EG&G servomotor type: MT-2130-012BE or similar with encoder driving a flex coupled 0.75" diam. ball screw drive. The huge carriage is: 28" L x 5.5" W x 1.1" Thick. The X axis is a massive precision machined (Mehlanite) casting. Mounted to the carriage is a substantial Z axis unit sporting dual THK, YH2218, 0.6"H x 0.5"W rails or similar. Riding the rails are four recirculating ball carriages attached to a 1/4" thick aluminum plate. Two carriages on each side. Running down the center is a 1/2" diam. ball screw driven by a size 23 stepper motor. This motor provides the drive for the 10.5" travel, Z axis. These units were originally designed to be used in a "gantry" configuration, i.e. suspended over the workpiece with the workpiece moving in the Y axis. Overall size is 48"L x 17"W x 20"H. This is the perfect setup for heavy duty cutting or engraving. Slides of this quality don't come around very often. Don't miss it. We have a very limited quantity. These units must ship via truck. These are used in good condition removed from optical equipment. **ANORAD SLIDE... \$349 ea. or 2 for \$649**

NEW! 6.8" LCD COLOR, TFT, ACTIVE MATRIX DISPLAY, A huge 23sq. inch VIEWABLE AREA, Super Deal. 2.8X the VIEWING AREA of a 4" WOW! We wish you could see the color saturation and resolution of this superior LCD display. Excellent contrast ratio, high quality, full color images are comparable to a CRT. Perfect, portable, general purpose color monitor for standard NTSC color or B&W video. Fully compatible with all our cameras as well as Camcorders, VCR's, DVD's etc. OEM "component" style unit has no outer cabinet. Designed to be installed in YOUR housing via four mounting tabs as shown. Specs: Resolution, 1152H x 234V, 270K Pixels! Viewing angle, Top 10°, Down 30°, Left 45°, Right 45°. Brightness, 300 nit, Size: W x H x D 16mm/1, 157.2 x 122.6 x 8.0, 6.2" x 4.83" x 1.1". Weight, 10oz. Supplied with 30" input cable. Video input via BNC jack, 12VDC input via a standard barrel connector.

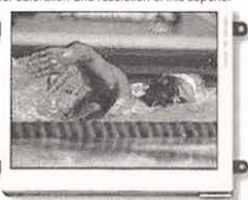

BRAND NEW, FIRST QUALITY, GMTFT68.....\$169ea. Regulated 12 VDC/110VAC power supply.....\$8.95ea.



POWER TO SPARE, 12 VOLTS at 17.2 Ah, NEW EXIDE SEALED RECHARGEABLE LEAD ACID BATTERY

Type NP-18-12, Now is your chance to perk up those power projects. Perfect for powering many portable devices such as GPS, laptop or telescope, fish finder or underwater camera. The list is endless. Don't be left out of this opportunity. The size is a manageable 7"W x 6.75"H x 3"D, weight is 14 lbs. Heavy duty post type connections. Use two in parallel for 34 Ah. WOW! Ltd. qty.

EXIDE-NP1812.....\$24ea. Case of 4, EXIDE-NP1812-4..\$89 1amp Charger, EX-CHGR..\$15ea.

SPECIAL, LINEAR SLIDES from DCI, Three models available: The large is 6"L x 2.6"W x 1"H with 4" of travel. The medium is 5"L x 2.6"W x 1"H with 3" of travel. The small is 1.75"W x 1.75"L x 0.75"H with 1" of travel with a removable spring return for use against a micrometer or similar. Features common to all include: Solid machined aluminum with anodized construction, hardened steel ways. Slides are usable in any position and can carry heavy loads. Over 100lbs for the large and medium and 25lbs for the small. Straight line accuracy of 0.00008"/inch of travel. All are new. Ltd. Qty.



DCI-LONG.....\$69ea. NOW \$59 DCI-MEDIUM.....\$59ea. NOW \$49 DCI-SHORT.....\$39ea. NOW \$29

NEW, 470 LINE, DSP COLOR Micro CAM The HIGHEST PERFORMANCE available. MICRO SIZED PACKAGE too!

Yes 470 lines with a 60dB S/N ratio to back it up! That's 16X better than a typical 460B standard camera! The GM-4500, CCD camera with its DSP technology provides high speed white balance with no color rolling. Auto shutter speed of 1/60 to 1/120,000 second. Truly state of the art. Sleek cast aluminum housing protects the 18mm x 26mm pc board inside. Mounting bracket & 18" cable with BNC video and DC pwr. jack for, no sweat hook up. requires only 12VDC @ 65mA. Optional mirror function available. Why fool around with an open P.C. board? This camera has it all. • 1/4" CCD • 1 Lux • AGC • Auto Shutter • 270k pixels • Std. 3.7 mm, 68° FOV lens • Focus: 10mm to infinity • 3-coupled • Size (mm): 33W x 29H x 30D **GM-4500-STD, SPECIAL...\$99ea.**



NEW! 0.005 Lux, COLOR NIGHT VISION CAMERA! UNBELIEVABLE LOW LIGHT PERFORMANCE. State of the Art Video, Exclusive ON SCREEN, menu driven setup of all camera parameters!

For covert, military & scientific applications that must be color. This is it. Unbelievable 0.005Lux @ f1.2 performance is enhanced through low speed electronic shuttering, digital frame integration and advanced DSP. Auto sensitivity mode starts as it becomes dark. 24 hour surveillance is possible with the optional f1.2 auto iris lens shown below. Seven Gain/Shutter modes are user selectable. Normal, X4, X8, X16, X24, X32, X64. These provide frame rates of 60, 15, 8, 4, 3, 2 and 1 per second. Auto/Man. white balance 3200° to 10000°K, auto/man BLC, S/N >52dB, Mirror on/off, Gain on/off, auto electronic shutter 1/60 to 1/120,000 sec., Alum. housing, dual 1/4x20 mtg. Specs: 1/2" CCD, 768H x 494V, with 380K pixels, 470 Lines, 12VDC @ 1V@200mA, Std. video out on BNC. Size: 51mm x 51mm x 155mm long. Regulated power adapter included. All functions can be externally controlled. Use standard C-mount lens not included. **GMV-3K-OSD.....\$49ea. High performance auto iris lens, 12mm, f1.2...\$199ea.**



ORDERS. 800.810.4070 Tech 603.668.2499

RESOURCES UN-LTD.

Fax 603.644.7825, All CCards, COD, 300 Bedford St. Manchester, NH 03101 WWW.RESUNLTD4U.COM

NEW! WEATHERPROOF B&W mini TUBE CAMERA Industrial strength, solid machined housing.

Sleek black anodized, BRASS, housing is O-Ring sealed & WATERPROOF. Adjustable mount included. Specs: 1/3" CCD, 400 Lines, resolution, 0.05 Lux sensitivity, AGC, Auto Shutter. Operates on 12VDC @ 200mA, 4mm, 78° FOV lens, A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR. Ultra small size. Only 1.25" diam. x 2" long. With 60 ft. cable. Great for outdoor use too. **NEW, GM300K-N.....\$99**

NEW, lower cost, High quality, MINI BOARD CAM, 1/3" CCD, 420 Lines Res. 0.3 Lux sens., AGC, Pwr. from 9 to 12VDC @ 100mA, 266k PIXELS, 3.7mm, 92° FOV lens, A real glass lens. Auto shutter from 1/60 to 1/100,000 sec. Focus from 10mm to infinity. Std. NTSC video out. 1/2 ounce! SENSITIVE to IR. Size: 1.25" sq. x 1". Connections via a 3" pigtail with PC board connector. **GM-1000B-STD.....\$45ea.**

PULNIX, TMC7 INDUSTRIAL 1/2", COLOR CCD CAMERA, with PENTAX Lens. For No Compromise Performance.

Specs: 1/2" CCD, 460 Lines resolution, 768H x 494V Pixels, 2 Lux sens. @ f1.4, Auto/Man AGC, Auto/Man Shutter. 1/60 to 1/10,000 remotely controllable via 6 pin connector (not incl.) Auto/Man white balance, Manual gain and hue controls are external. Complimentary color filter. 12VDC @ 320mA, Pwr supply incl. Pentax, 16mm f1.4 lens, A real glass lens. Included. Std. NTSC video out on BNC. Y/C S-Video output available on 12 pin connector supplied. Superior construction. Compact size only. 1.6"W x 1.25"H x 5.5" long. Perfect for use in process monitoring, medical, surveillance and microscopy. Used, excellent condition, Regular price \$600, limited quantity. **PULNIX, TMC-7.....\$149ea. or 2 for \$249**

NEW! 4 or 8 CHANNEL, VIDEO AUTO SWITCHERS Connect four or eight std. video signals and they will be sequentially output to the dual rear panel BNC outputs. Front panel user adjustable, variable dwell 1 to 15 sec per channel. Auto/manual switching with channel bypass. Compact only 8.6"W x 3.7"D x 1.75"H, ac powered. Video loop through. **GM-34, 4 Chan...\$65, GM38, 8 Chan...\$75**



NEW! 0.01 Lux, COLOR NIGHT VISION CAMERA! FANTASTIC LOW LIGHT PERFORMANCE. Exclusive ON SCREEN, menu driven setup of all camera parameters. NEW, STATE of the ART, GMV-35KOSD.


Perfect for covert, military & scientific applications that must be color. Unbelievable 0.01Lux @ f1.2 performance is enhanced through low speed electronic shuttering, digital frame integration & advanced DSP. Auto sensitivity mode starts as it becomes dark. 24 hour surveillance is possible with the optional f1.2 lens shown below. Specs: Shutter speed auto or manual, 1/60 to 1/120,000, 60dB S/N ratio, 154dB Smea rejection!, AGC gain 0 dB to 18 dB. Digital gain 0dB to 12dB. Digital zoom continuous from up to 2X in 0.1X steps. Masking mode allows hiding 4 programmable zones for privacy protection. Camera on screen name. Choose your own name for the camera and display it on monitor for easy identification. 1 White balance modes. Auto tracking, one push or selection from 3200K, 4800K, 5600K, 7800K, and "double white balance" independent white balance circuit for both bright and dark zone, maintains correct white balance even with combined indoor and outdoor lighting. Programmable 48 zone back light compensation mode for difficult lighting situation. Negative mode for negative film reading. Mirror image and up/down selection for rear view and camera mounted upside down. Seven Gain/Shutter modes are user selectable. Normal, X2, X4, X8, X16, X24, X32, X64. These provide frame rates of 60, 30, 15, 8, 4, 3, 2, and 1 per second. Alum. housing, dual 1/4x20 mtg. Specs: 1/3" CCD, 811H x 508V, with 412K pixels, 470 Lines, 12VDC @ 1V@250mA, Std. video out on BNC. Std S-Video out on 4Pin connector. Size: 2"H x 2"W x 4.5" long. Regulated power adapter included. C-mount lens not included. **GMV-35KOSD.....\$399ea. High performance lens, 4mm, f1.3....\$49ea.**

NEW, SECURITY MONITOR. NOW YOU HAVE THREE CHOICES! Commercial quality, Hi-resolution B&W and Color monitors. Brand new, 90 day warranty. BNC video in and loop through. Rugged black steel case. Three models are available: choose a 9" or 15" Black and White with 1000 lines of resolution, or a 14" color with 450 lines of resolution. You will be amazed at how much better they will make your video look! There is no substitute for a real monitor. With UL, FCC and FDA approvals.



SPECIAL, BWMONITOR-9HR.....\$94 ea. BWMONITOR-15HR.....\$159ea. COLORMON-14HR.....\$219ea.

MSP430F449: Imagine the possibilities.

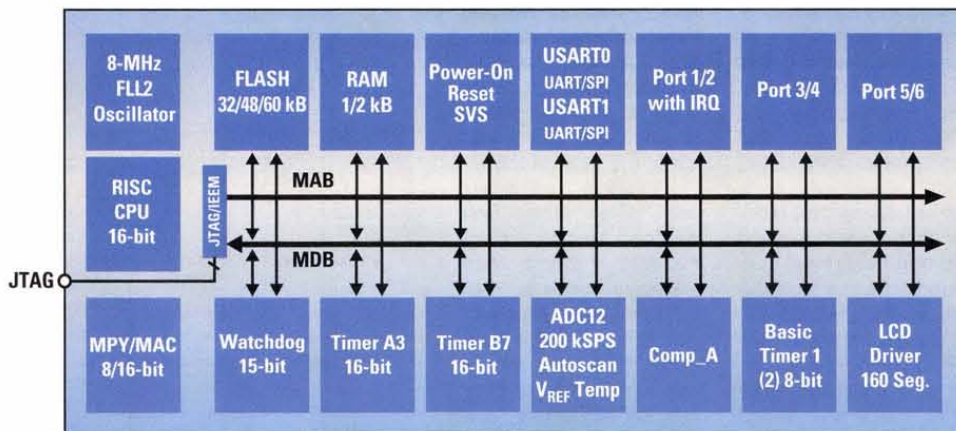

Features:

- Ultralow-power Flash MCU with high-performance 200-kSPS ADC and LCD driver on one chip
- Power consumption of <1 μ A in standby mode extends battery life
- Modern 16-bit RISC CPU enables new applications at a fraction of the code size
- In-system programmable Flash permits last-minute code changes, field upgrades and data logging to Flash

MSP430 – the choice in ultralow-power Flash MCUs

Experience the ultimate SOC solution for battery-powered measurement. A flexible clock system switches from ultralow-power standby to high-performance signal processing in less than 6 μ s. Embedded emulation reduces design cycle time. Get your design started today with the easy-to-use MSP-FET430P440 Flash emulation tool.

Device	Flash Memory	Price 1K
MSP430F449	60 kB	\$7.03
MSP430F448	48 kB	\$6.47
MSP430F447	32 kB	\$5.71

Device	Flash Memory	Price 1K
MSP430F437	32 kB	\$4.90
MSP430F436	24 kB	\$4.70
MSP430F435	16 kB	\$4.45



MSP-FET430P440
development tool-\$99

Contact us to request:
 development tools
 product bulletin (SLAB034C)
 MSP430F44x data sheets

www.ti.com/sc/hpa7227u

1-800-477-8924, ask for ext. 7227

Amateur Robotics

As I write, I am packing to drive 2,000 miles to my parent's log home in Three Forks, MT. Brouhaha. Confusion. Consternation. And a column to finish, aargh!

Boy, do I need a vacation.

This month, I finish up the last details of building the cheap linear actuator, and I'll also present some ideas for future improvements. Next, I dive into color. It may look like I'm just dipping my toes in the water, but I'm practically drowning in the sea of information on this topic. I'll close with an announcement.

First to the actuator.

Actuator Loose Ends

The actuator design as it stands has a few problems. First, though I wanted a quick actuator, this design is a little too zippy for some uses. It would benefit from some gear reduction, if only 2:1 or 3:1.

Second, it has a tendency to overshoot under a light load when using the simple limit switch circuit, since there's no position feedback and nothing to brake the motor other than friction. This is more a problem for extension than retraction, because the rod-end pivot provides a mechanical stop on retraction. Even then, it's possible for the motor's inertia to draw the slide tube in tight enough to jam. Using a silicone lubricant alleviates the jamming problem, at the expense of increasing overshoot.

Third, my initial design is just plain harder to build than it needs to be. I mentioned a simpler thrust bearing set-up last month, and I've got lots of other ideas for ways to improve its performance and make it easier to build.

One easy improvement is

using machine-cut threaded rod rather than rolled threads because machine-cut threads are more precise and have a smoother finish. Machine-cut threaded rod costs a little more, but the follower nut will last longer and there will be less friction.

Another improvement would be to use a pre-machined follower nut to avoid all the hassle of precisely drilling and tapping one yourself. Standard threaded standoffs are obvious candidates for premade follower nuts because they are cheap and readily available. Standoffs are available in round and hexagonal sections, in aluminum, brass, and nylon, and range from 2-56 to 10-32 threads. Metric threads are available, too.

None of the standard sizes are a direct fit inside any of the telescoping tubes that Small Parts carries, either square or round, so a bit of shimming before soldering or gluing would be in order.

Another alternative is threaded brackets such as those made by Keystone Electronics, Inc., and available from Mouser Electronics (www.mouser.com) — in particular Mouser part #534-631 and #534-708. You might also look into E-Z LOK threaded inserts, also available from Small Parts, though these require a tapped hole themselves to be installed.

Different Strokes

As I noted above, lack of position feedback is a major shortcoming of the present design. You know the actuator's position only when fully extended or retracted; it's an open-loop control system, and positions between the extremes are anyone's guess.

You could time how long the actuator takes to extend or

retract, then run the motor some fraction of that time in the hope of getting close to the desired position. The problem is the final position will depend on lots of factors beyond timing (wear, lubrication, and changing load come to mind). A better way is to incorporate positional feedback and close the control loop.

Optical encoders are often the first choice among robot builders because they interface easily to digital controllers. Absolute position encoders, either linear or rotary, will do the job, but they can be expensive, and there's really no need. A simple incremental encoder combined with a home-position switch allows determination of the absolute position of the slide tube.

This method will work with either rotary or linear incremental encoders. The main requirement for the encoder is that it be one with two quadrature channels so the direction of movement can be determined. Simply count the number and direction of pulses since the last time the slide was homed. With any luck, the position will be dead on (but home the slider early and often to be sure).

The retract limit switch can make a convenient home-position sensor, but if you do this, you won't be able to use the simple limit switch circuit described last month. Instead, you would need to use the retract limit switch as a sensor. Rather than directly interrupting current to the motor when the limit is reached, the switch would be wired to a free input pin of a microcontroller or other digital controller. The controller detects when the switch closes or

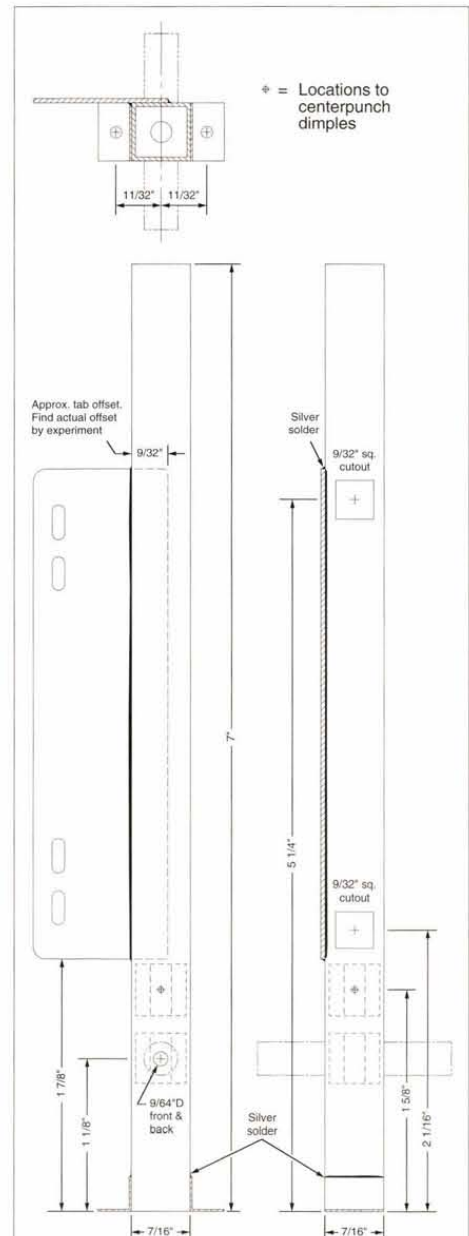



Figure 1: (a) TSLx257 spectral responsivities with no external filter; (b) spectral responsivities with external IR cutoff filter. (Graphs from TAOS, Inc. TAOS027A datasheet, p5.).

opens and outputs the appropriate PWM levels to the motor driver to start or stop the motor. A pull-up resistor to logic V+ is necessary for an input line that lacks an internal pull-up.

Linear Slide

On the analog side of things,

Photo 1. Rod end block assembly mounted in the slide tube.

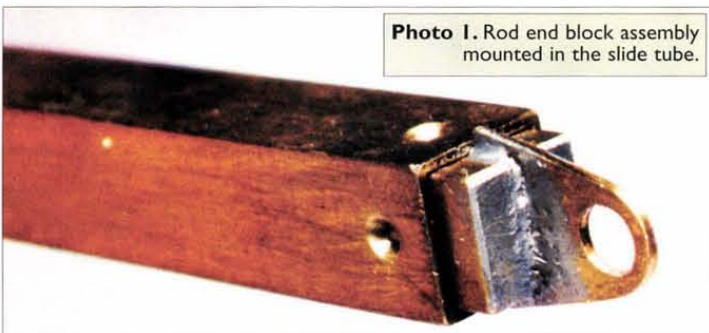

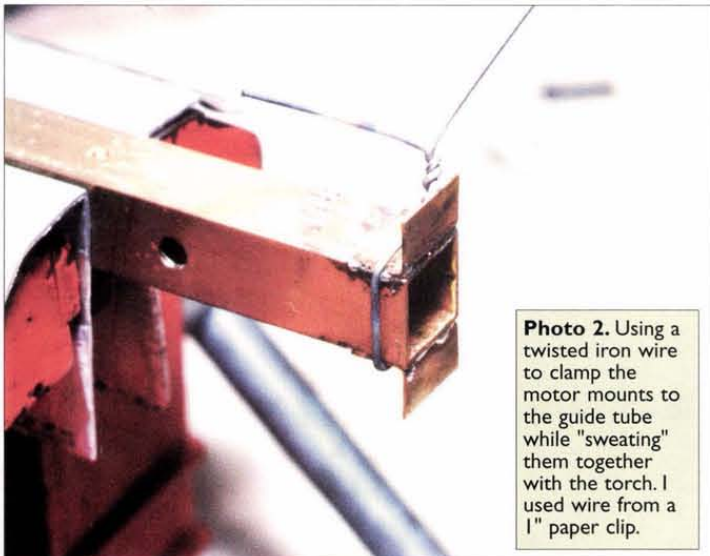


Photo 2. Using a twisted iron wire to clamp the motor mounts to the guide tube while "sweating" them together with the torch. I used wire from a 1" paper clip.

a linear slide potentiometer makes a fine position sensor, and it just so happens I designed this actuator with a travel compatible with commonly available slide pots. You may need to cut a slot in the guide tube for the pot lever, depending on how you mount the slide pot. The slot allows a more compact assembly, but it's more complex to build and it opens the assembly to environmental crud.

I have toyed with the idea of building a homebrew slide pot into the actuator slide. I envision broaching an internal groove in the guide tube and a matching external groove on the slide tube. The grooves would accept a strip of insulated resistance element and a sliding contact. If I can figure out a simple way to perform the broaching operations with simple hand tools, I might give this one a whirl.

Whatever potentiometer is used, it could be very interesting to use a hobby servo motor and electronics board to drive the linear actuator, either directly or through one stage of gear reduction. The slide pot would then directly replace the stock servo's rotary feedback pot. This way, the actuator would use a standard servo three-wire interface. What could be simpler?

I've had a lot of fun with this linear actuator project, and I'd love to hear from any of you who build your own versions of it. I've spent half this month talking about its flaws and fixes, and I have faith others will come up with better ideas than I have. For instance, I'd love to combine the function of shock absorber and linear actuator in one design, but I haven't come up with a clean design yet.

Now to shift gears to the

world of color sensing and perception.

Color!

As mentioned in past columns, I'm working on a two-pronged attack on low-cost color sensing for robots. I've got one of the CMUcam color vision systems on my shelf (available from from Seattle Robotics, www.seattle-robotics.com) just waiting for a robot in which to install it. It has 80 x 143 resolution and can track user-defined color blobs at 17 frames per second. It can also output a pulse train compatible with hobby servos such that the camera will tend to track the lateral movement of a defined color blob. All this for under \$100.00.

I have been about ready to bust, so eager have I been to try this vision system out. However, I've had other important projects in the queue ahead of it. One of those projects is a simple RGB color sensor.

Rather than a video camera with thousands of pixels, I just want a single pixel. I want a color sensor more like a phototransistor than a video camera, applicable in the same situations as a phototransistor. It should consume little power and be easy to use with simple robots (BEAM-style robots, for instance).

BEAM robots produce interesting emergent behavior using simple monochrome optosensors (phototransistors and CdS photocells and the like), and I've wondered what new kinds of behaviors might be possible with color sensors.

In the past year, the job of designing a color sensor has become much simpler with the TSLx257 series of color light-to-

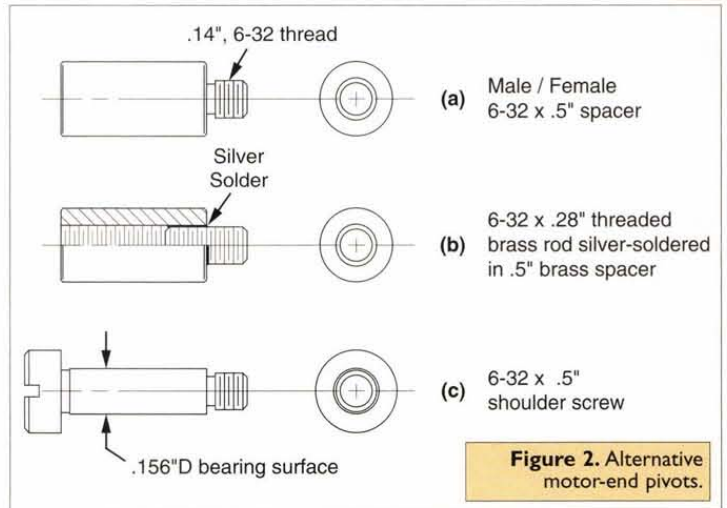


Figure 2. Alternative motor-end pivots.

voltage sensors from TAOS, Inc. (www.taosinc.com).

These parts include a photodiode, transimpedance amplifier, and integral color filter in a three-pin package, the same sort of package as phototransistors. You connect ground and +5V to pins 1 and 2 and read the sensed light intensity as a rail-to-rail analog voltage on pin 3. The TSLR257 senses red, the TSLG257 green, and the TSLB257 blue.

Despite the integral color filters, all three parts still respond to IR; you must add an external optical filter to block near IR wavelengths to get true measurements. Figure 1 shows the relative spectral responsivities for the TSLx257 sensors with and without an external IR cut-off filter.

Expensive Glass

I couldn't find the Hoya CM500 the datasheet calls for, and the cheapest alternative I could find was an unmounted 15mm square glass IR cut-off filter from Edmund Industrial Optics (part #L53-709). This piece of glass costs nearly \$30.00. There's got to be a cheaper filter out there since every color camera using a silicon imaging

chip has the same problem with IR. Junked camcorders or digital still cameras might be a source, but I've never taken any of these apart. (If any of you know of a good source for IR cut-off filters, I'd like to hear about it.)

In order to use my expensive little filter, I needed some sort of mounting cell for it and a diffuser, and I further needed an opaque tube to shield the sensors from stray light. The diffuser smears out the light so the sensors all see the same patch of color. Figure 2 shows my basic design.

The filter cell is made from a sandwich of three cardboard disks painted flat black. The cardboard is the kind used to back large pads of paper, and it needs to be about 1.1mm (.043") thick, the same as the filter. As for the opaque tube, I used two film canisters, the black plastic kind that Kodak 35mm film comes in. I made square cutouts in the bottom of both canisters, as well as holes for mounting screws, then attached them to both sides of my home-made filter cell. One end is left open for light to enter, and the sensor array mounts in a plastic film canister cap snapped on to the other end. This arrangement gives roughly a 45-degree field of



Photo 3. The motor mounts after scraping and sanding.

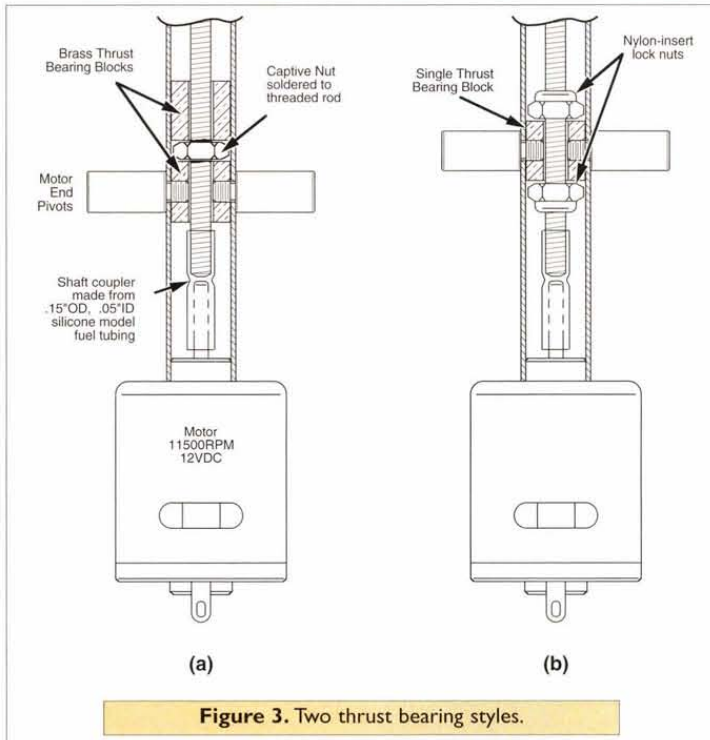


Figure 3. Two thrust bearing styles.

view. Though I have not tried it, you could mount a lense on another plastic cap to make the color sensor more directional.

The design is a bit bulky, but

it's easy and (except for the filter) cheap to build. Figure 3 shows how I propose to use this sensor.

Color Perception

If the robot resembles a classic Braitenberg vehicle, that is no coincidence. If it appears I've been a bit vague on what happens inside the Color Comparator function block, that's no coincidence, either. The RGB sensor does a good job of measuring energy in the red, green, and blue wavelengths of visible light, but color is a complex perceptual phenomenon only indirectly tied to RGB measurements. In terms of RGB values, it doesn't really make sense to talk about object colors such as "fire engine red" or "pastel green" or even "white." Those are purely human perceptions, and there are no unique values of R, G, and B that produce these colors.

For instance, you were probably taught in grammar school that white is just all three colors mixed together. However, if you had only just enough of each color to be visible in a dark room, you would most likely perceive it as gray. Another example is the rainbow. Physics tells us that a rainbow should spread the colors evenly across the spectrum, but we perceive rainbows as wide bands of green and red with much narrower bands of yellow, orange, and blue interspersed.

Object color is complicated enough, but there's also the color

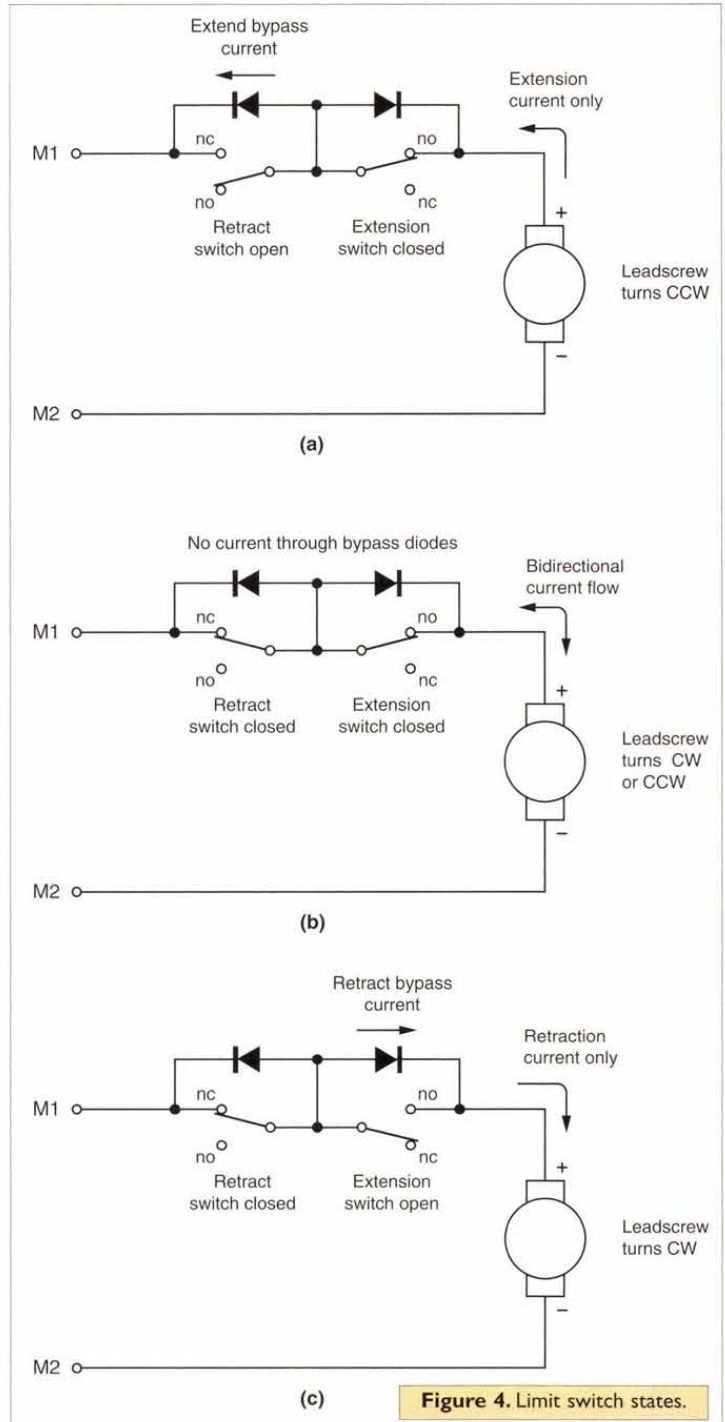


Figure 4. Limit switch states.

of illumination to reckon with. In 1977, Edwin Land (inventor of Polaroid photography) showed that you can illuminate a color painting with just two basis colors (say green and blue), yet still be able to perceive the colors correctly — even colors not present in the two illuminating wavelengths.

To understand how this can be, you need to understand the idea of color space. Figure 4 shows the basic idea.

Color Space

The most basic is RGB color

space, a unit cube containing all possible values of each basis color, and thus all possible colors. But as the above examples have shown, it doesn't explain color perception. Other color spaces are more useful when thinking about that, most notably the HSI color space, or Hue, Saturation, and Intensity.

Intensity is the same as the brightness control on a TV. Saturation is the amount a color is "diluted" by white; "fire engine red" is fully saturated, but if you mix enough white in, it will turn pastel pink. Hue is roughly pro-

Mobile Robotics

Used world wide for research!




Mobile Robots
Micro Controllers
Artificial Intelligence
Sonar Units
Optics
Vision Systems



Zagros Robotics
PO Box 460342
St. Louis, MO 63146-7342
Phone (314)768-1328 Fax (314)576-5568
<http://www.zagrosrobotics.com>
info@zagrosrobotics.com

Photo 4. Actuator slide assembly secured to the motor with two 2.5mm x 12 socket head cap screws. Though not shown here, grinding a bit of clearance into the sides of the motor brackets allows the screws to seat squarely.

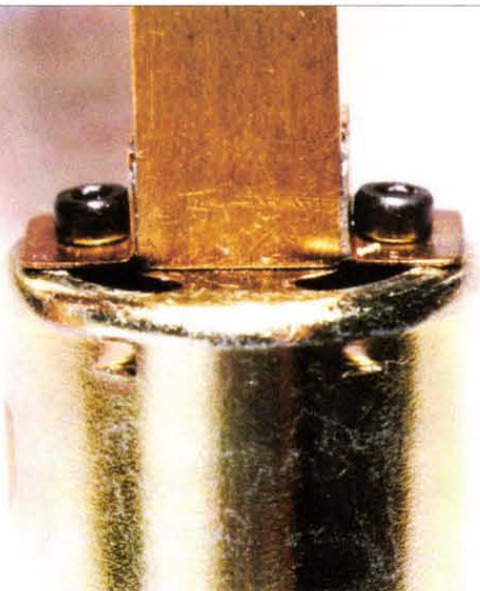

portional to the average wavelength of the color, and hence is what I want to use as the starting point for the color tracker. The color comparator will compare left and right values of hue to an internal reference; saturation and intensity will be used as threshold values. A color must be bright enough and saturated enough to be considered. I haven't tried this, but I think it is a good start.

Color space transforms can

be mind-bogglingly complex, and HSI is one of the more complex. I don't have the space here to go into the details, but HSI color space can be transformed from RGB by the equations in the sidebar. Figure 4 gives a visualization to the ideas embodied in those equations.

If you don't understand it at first, you're in lots of good company. I can recommend two textbooks to take you further in your understanding. The first is the college text from which I very nearly learned the material 20 years ago: *Computer Vision* by Dana Ballard and Christopher Brown (Prentice Hall, New Jersey, 1982, ISBN 0-13-165316-4). (n.b. They refer to HSI as IHS.)

A more recent text, a portion of which is available online for download, is Gonzalez and Woods' *Digital Image Processing* (Addison-Wesley, 1992). You can download the HSI conversion chapter at the following URL (no spaces or breaks): www.imageprocessingbook.com/downloads/material_from_last_edition/rgb-to-hsi-conversion.pdf

I'll have more to say about color sensing in future articles — and I welcome tips from anyone who works every day with this stuff — but I am flat out of room this month. And I still have to get to my announcement.

The End?

After much soul searching, I have very reluctantly come to the conclusion that I must end my role as the monthly robotics columnist for *Nuts & Volts*. Shoshana and I have spent many hours discussing this over the past year, and I have come to

believe that I cannot be the father I want to be for my two boys if I must sequester myself for the 30 or 40 hours each month it takes to research and write my column.

This was brought home to me this Spring when Yonatan, my three-year-old, told me he couldn't come play Silly Loud Dinosaurs with his brother Nadav and me because, he said, "I'm busy working on my computer" (in the same pleading tone of voice I apparently use when I'm on deadline). And Nadav is going through a phase where he needs to have either Shoshana or me in sight most of the day.

It's been a wild, fun, hilariously nerve-wracking four years, made all the better by letters and emails from you, the readers. To those who wrote to tell me you always read my column first, there were several months where such notes tipped the balance and kept me going. Thank you for the kindness.

It has been a privilege to write the Amateur Robotics column; the folks at *Nuts & Volts* are simply the best there is, and to them — Natalie, Larry, and, most of all, Robin — I thank you for your seemingly endless patience and faith in me.

Do not fear, folks, I am not retiring. I still intend to write robotics and other tech hobbyist articles, and you'll see them in these pages (and others) from time to time. I just can't do it on a monthly schedule anymore.

Although I will no longer be doing this column, I'm still interested in hearing from you. If you have suggestions, questions, or comments about amateur robotics topics, as always you can reach me at:

Robert Nansel
Box 228
Ambridge, PA 15003
Email: bnansel@nauticom.net

By the time you read this, I also will have a website to point folks toward information on my past columns and my current projects: www.countryrobot.com. It'll be pretty bare bones in the beginning, but you'll see lots more after I recover from vacation. Don't expect much fancy Java, animation, or sound — I'm on 56k dialup, and those things just cheese me off. I won't inflict them on you. Do expect lots of good information on robotics and general gadgeteering, much available nowhere else. Amateur Robotics is not dead. Long live Amateur Robotics! **NV**

DMOS & JFETS & MOSFETS & TRANSISTORS

@
LINEARSYSTEMS

Second Source Replacements
for Interfet, Motorola,
National, Siliconix

- ◆ Custom Screening
- ◆ Die, SMT, Thru-Hole


LINEAR SYSTEMS

Full Service U.S. Manufacturer
of Specialty Linear Products
4042 Clipper Court
Fremont, CA 94538
(TEL) 510-490-9160
(FAX) 510-353-0261
JFETS@LINEARSYSTEMS.COM
WWW.LINEARSYSTEMS.COM

Circle #43 on the Reader Service Card.

QUICK and PAINLESS Programmable Robotics!

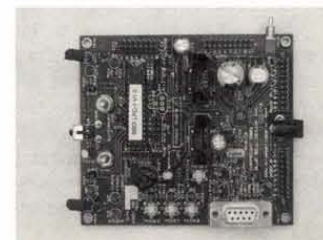Robot Builders - Ready
for something different?



Our Co-Processor adds the best of the standard features to some killer new ones. It really Steps up your Stamp — other controllers too.

Also look at our Controller Board. It adds a genuine top of the line Basic Stamp 2p40® processor, lots of available I/O, connectors, CPU speed, and DC power! It's the same PCB and Co-Processor we use in our robot.

Already have or are you building a Stamp based robot? Our Co-Processor and PCB will make superior upgrades.

Great for animatronics and walkers!

See how far they take YOU!

Blue Bell Design Inc.

www.bluebelldesign.com

Circle #45 on the Reader Service Card.

Product Review: Line6 GuitarPort

By Edward B. Driscoll, Jr.

If you're a "weekend warrior" musician looking for a practice or recording tool that you can plug into the USB port of your PC, then GuitarPort might just be right up your alley.

The instructions seem to say "plug your electric guitar into the USB port of your personal computer," which sounds like a pretty good deal. Back in the 1950s, when guitarists like Muddy Waters and Chuck Berry wanted a great guitar sound, they had to take a gigantic Eniac mainframe computer that took up the entire floor of an office building on the road with them.

Okay, so plugging a guitar into a personal computer is in reality a much newer phenomenon. (Which is too bad, because "Chuck Berry Eniac Tour 1956" would have made a great Micro Memories column. That was the tour where Chuck sang Johnnie B. Goode, I think.)

Line6, which has manufactured a line of amps and effects boxes for guitarists that recreate the vintage sounds of the 1950s and 60s vacuum tube-powered amps (beloved by electric guitarists for their warm tone and, when overdriven, their "musical" distortion), is betting that guitarists will want to plug into their computers, and they've invented a product that allows them to do just that.

A Variety of Uses

The GuitarPort — which retails for \$229.99, but can often be found on sale for well under \$200.00, and vaguely resembles some alien prop from "Star Trek: The Next Generation" — plugs into a PC's USB outlet, as well as its multimedia speakers and, in turn, has a quarter-inch jack into which you plug your guitar. Once connected, it features an amazing variety of pre-set sounds (most geared towards rock and blues), as well as an online capability (with a \$7.99 monthly fee that allows for not only additional tones to be downloaded, but also notational tablature, lessons, and several whole songs which have guitar parts that can be switched on or off to practice to (including several by Jimi Hendrix, thanks to a deal that Line6 cut with his estate). The downloads feel seamless for anyone with a broadband connection.

For guitarists looking to improve their "chops," the GuitarPort will transfer tracks from audio CDs into MP3s, and play them at an optional half-speed (while keeping the sound in the same key). So, for example, if a guitarist wanted to practice the George Harrison's solo from Something by the Beatles, the Abbey Road CD could be inserted into a PC, copied as an MP3, then Harrison's guitar tone on that song could be downloaded from the GuitarPort's accompanying web site, and finally Something could be played at both half and normal speeds until the solo is memorized.

What Does It Sound Like?

Even if it doesn't make sense to bother with the online component of the GuitarPort, there's a lot here to play with. Professional electric guitarists and serious amateurs spend years crafting the tone of the instrument, and most would probably say that a vintage amplifier sounds better or more authentic than Line6's computer-driven recreations. However, to my ears, the sounds of the GuitarPort are pretty darn good, and amazingly diverse. Plug a Gibson Les Paul in and dial-up the "British High Gain" pre-set, and you're instantly transported to a small London club where a hungry young Jimmy Page or Jeff Beck is jamming. Or for something completely different, switch to "Snow Dome," with a hypnotic and mystical combination of echo and reverb that almost seems to play the guitar itself.

The 78 or so other presets run the gamut from 1950s-style small amps perfect for B.B. King and Muddy Waters style blues leads, to shredding heavy metal buzz saw sounds and all points in between. And, of course, all of the unit's simulated amps, speaker cabinets, and effects can be tinkered with, assembled, and disassembled for even more tones.

Bucking the Hum

The GuitarPort also has a guitar tuner, a noise gate, and a hum-reducer. **20 August 2002/Nuts & Volts Magazine**



ing feature, which is especially helpful for anyone recording guitars with single-coil pickups (such as most Fender instruments). "The hum reducer is an interesting thing, because one of the early challenges that we identified is that if people are going to be sitting in front of a CRT, you're going to get hum through pickups, especially on a single-coil guitar," according to Mark McCrite, product manager for Line6. "So if you click on the hum reducer, it gives you graphic instructions, and what you basically do is try to isolate the hum."

This involves putting your guitar's noisiest pickup on and moving around the monitor until the pickup is humming at its worst, and "then you click on the Analyze button, and it will record a little bit of that hum, and then figure a way to 'suck it out,'" McCrite says. "We call it a hum reducer, and not a hum canceller, because if you took all of that out, it would be pretty invasive to the guitar's tone." And it definitely will leave some hum, but in many cases, this will be masked by other instruments when recording. Which leads us to ...

Home Recording

For recording programs, such as Cakewalk's Sonar XL 2.0 (see "Abbey Road in a Box" in the Nov. 2001 issue of *Nuts & Volts*), the unit works seamlessly, making it a natural for home recording (although it may be incompatible with version 1.3 of Sonar. Check with Cakewalk and/or Line6 to see if there's a workaround available if this version is your primary recording software).


While many guitarists will still prefer to mic a real amplifier rather than use an input device, others will appreciate the ability to get good sounds instantly, without having to wake the neighbors (or parents) in the process.

The software is designed to work with Windows 98, Me, and 2000. As of May, XP drivers were in the works to be released by the time this article appears in print. And Apples are not yet supported by GuitarPort.

Because of the driver issues, possible incompatibility with some home recording products, and the need for a reasonably fast PC with a USB port, GuitarPort isn't for everyone. But if you're a "weekend warrior" musician looking for a practice or recording tool, GuitarPort might just be right up your alley. **NV**

ANYTHING THEY CAN DO...
WE DO...

BASICX24™
\$49.95 (Qty 1)

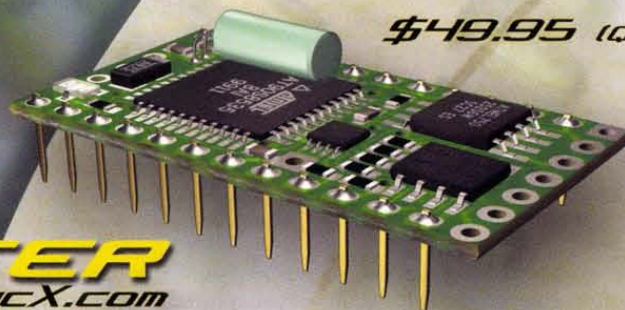

...FASTER
WWW.BASICX.COM

Executing 65,000 lines of Basic code per second the BasicX-24 is the KING of Basic programmable microcontrollers.

400 bytes RAM.
32K User program area.
19 I/O lines with 8 10Bit ADC's.
Real multitasking and Serial UARTs.

...SMALLER
WWW.SITEPLAYER.COM

Siteplayer is a true stand-alone mini web server.

Super easy to use.
Standard RJ-45 network interface.
Control or monitor anything over the web.



SITEPLAYER™
\$29.95 (Qty 1)

...BETTER
WWW.BASICX.COM

High quality serial 2x16 LCD with backlight

Easy to use.
2400 & 9600 Baud support
Software controllable backlight and contrast.

2x16 SERIAL LCD™
\$39.95 (Qty 1)



A Universal FET Tester

By Peter Lehmann

It's a good idea to test FETs prior to building circuitry with them.

When you are working with surplus FETs or FETs removed from the circuit boards of any of your previous projects or of scrapped equipment, it's a good idea to test them prior to building circuitry with them. Enter the Universal FET Tester ...

Field effect transistors or FETs that can be tested are junction gate FETs or JFETs, both N-channel and P-channel, and insulated gate FETs or IGFETs (MOSFETs being the most common type of IGFET), both N-channel and P-channel, both enhancement- and depletion-mode and three lead or four lead. The tester can also accommodate any package and particular pin sequence of a FET, that is, the arrangement of leads to the gate, drain, source, and substrate of the FET. Adding this tester to your collection of testing equipment will also prove advantageous for determining the type of unknown FETs and troubleshooting.

To make it work, the tester is connected between your existing function generator or oscillator capable of producing squarewaves and your general-purpose oscilloscope. The frequency and amplitude of the squarewave at input to the tester need to be, respectively, 1 KHz and 10V peak-to-peak into a 10KW load. The output signal from the tester should be DC-coupled to the vertical amplifier of the scope.

Uses for FETs and an explanation as to where FETs can be used to advantage in place of bipolar transistors can be found in the excellent series of articles by Ray Marston, "FET Principles and Circuits" in the May 2000 through August 2000 issues of *Nuts & Volts* magazine.

TESTING PURPOSES

IGFETs have a very thin dielectric or insulator between the gate and substrate of the FET forming a small and fragile capacitor. This capacitor can be easily damaged by a discharge of static electricity during handling. Also, IGFETs are most commonly manufactured in plastic TO-202 or TO-220 packages that must be soldered into working circuits. So being able to test the FET before soldering it into place is advantageous. Sockets for FETs in the TO-3 package are available, but FETs so packaged are a great deal more expensive than the ones in plastic packages. IGFETs are also available in the dual in-line pin or DIP package, but these are limited in terms of power dissipation.

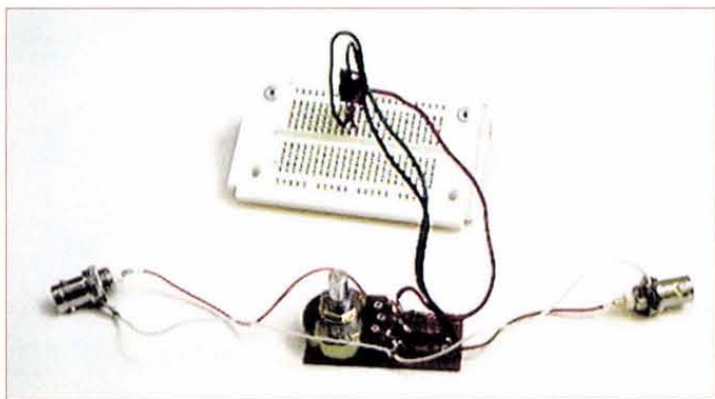


PHOTO 1: Interconnection of components of tester.

FUNCTIONAL METHOD

Figure 1 is a schematic diagram of the very simple circuit of the dynamic tester with FET Q1 being the transistor tested and showing the waveforms of the squarewave applied at the input and taken at the output of the tester. Resistor R1 provides a path of current leakage from the gate to the source of the FET being tested preventing an excessive accumulation of charge at the gate of the FET if the wiper of potentiometer R2 inadvertently lifts off its track. By voltage division, the setting of potentiometer R2 controls the peak voltage taken between the gate and source terminations of FET Q1. If FET Q1 were a JFET, then resistor R3 provides loading for the generator of the squarewave at input where the gate to source junction of the JFET is forward-biased. Resistor R4 is the load resistance for FET Q1 and connected from the drain of FET Q1 to 0V or ground.

The FET shown in Figure 1 is an N-channel enhancement-mode MOSFET with three leads and the substrate and source of the FET internally connected. An IGFET with four leads requires externally connecting the substrate and source leads for testing. The substrate is P-type material and the drain and source are N-type material implanted in the substrate. During the peak positive half-wave of the input signal, the voltage taken at the substrate with respect to that at the drain is positive, producing a forward bias across the substrate to drain PN junction. Potentiometer R2 varies the voltage of the gate relative to that of the substrate from 0V to -5V. The surface of the substrate directly under the gate insulator correspondingly changes from P-type material identical to that of the remainder of the substrate to material that locally has a net positive charge. A conductive channel from the source to the drain does not form regardless of the voltage of the gate relative to that of the substrate. Under these conditions, the FET can be modeled as a forward-biased diode and the positive half-wave viewed on the display of the scope essentially follows that of the input signal and has a peak voltage of nearly 5V.

During the peak negative half-wave of the input signal, the voltage taken at the substrate with respect to that at the drain is negative producing a reverse bias across the substrate to drain PN junction. Adjusting the gate to source voltage, V_{GS} , equal to 0V by rotating the shaft of potentiometer R2 causes the material of the surface of the sub-

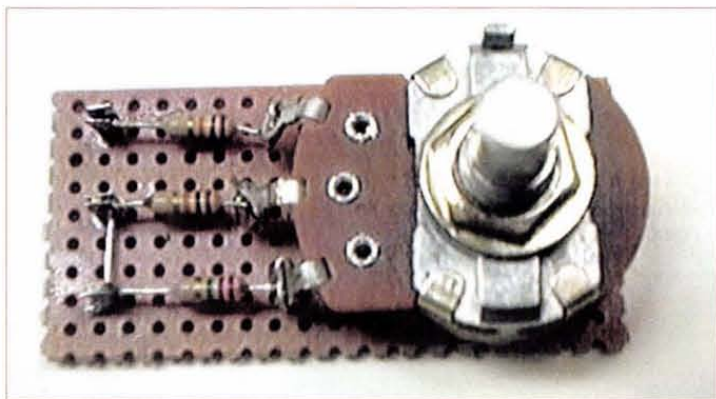


PHOTO 2: Resistive network.

A UNIVERSAL FET TESTER

strate directly under the gate insulator to be P-type material identical to that of the remainder of the substrate, and a conductive channel from source to drain does not form. Therefore, no current can flow through the FET and the negative half-wave of the input signal does not appear on the scope.

If during the negative half-wave of the input signal the shaft of potentiometer R2 is rotated causing VGS to be greater than +1V, then the surface of the substrate directly under the gate insulator becomes locally negatively charged and a conductive channel from source to drain is formed. The resistance of this conductive channel is very much less than that of load resistor R4. The waveform appearing on the scope corresponds to the voltage drop across resistor R4, so this adjustment to the setting of potentiometer R4 results in the appearance of a negative square half-wave on the scope with a peak amplitude of -5V.

In the case of the FET Q1 shown in Figure 1, if the FET is good, then the peak amplitude of the positive and negative half-waves on the scope are respectively equal to nearly +5V for any setting, and variable between 0V and -5V with the setting of potentiometer R2.

Alternatively, FET Q1 in Figure 1 might be a good N-channel JFET. For this type of JFET, the substrate is N-type material, the source and drain are ohmic contacts to the substrate, and the gate is P-type material implanted at the middle of the substrate. Note that all JFETs are depletion-mode devices, that is, with zero volts taken across the gate-to-source junction, maximum current flows from source to drain.

During the negative half-wave of the input signal, the position of the wiper of potentiometer R2 varies the gate with respect to source voltage from zero volts to +5V. For Q1 in Figure 1 alternatively being a good N-channel JFET, then the gate-to-source junction varies from zero bias to being forward-biased. Therefore, the JFET is ON for any setting of potentiometer R2 and the negative half-wave on the scope follows the input negative half-wave. During the positive half-wave of the input signal, the gate-to-source voltage is varied from zero volts to -5V by the setting of potentiometer R2. The PN junction between the gate and source of the JFET can thus be increasingly negatively biased by the position of the wiper of potentiometer R2 being moved closer to a position of no

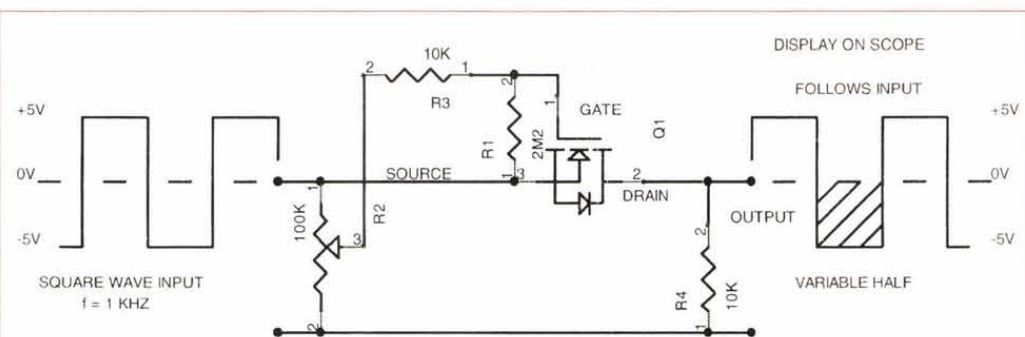


FIGURE 1: Schematic diagram of tester.

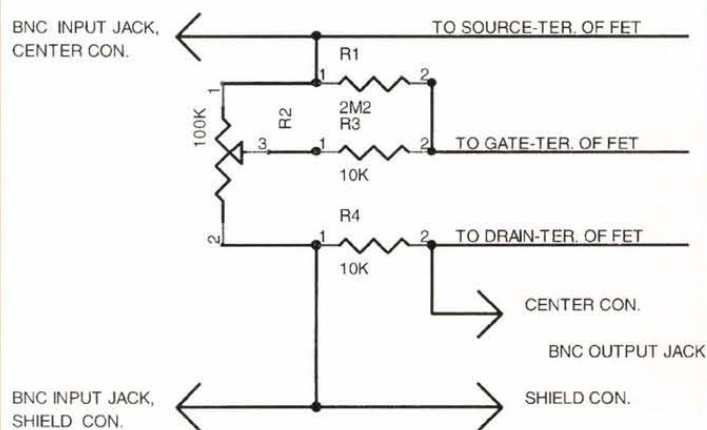


FIGURE 2: Layout and interconnection of resistive network of tester.

resistance between ground and the wiper. Current from source to drain is increasingly cut off in proportion to the negative bias of the gate-to-source junction, which means that the setting of potentiometer R2 varies the peak amplitude of the positive half-wave taken across load resistor R4 viewed on the scope.

For JFETs and depletion-mode IGFETs, the maximum absolute value of VGS produced by this tester equal to 5V is generally less than the turning OFF threshold voltage for these FETs. Therefore, the variable half of the output squarewave of a good FET of these types will be variable over a range of less than 5V.

CONSTRUCTING IT

Photo 1 shows how the components of the tester are connected omitting the enclosure. At the bottom of the photo is the resistive network which consists of a potentiometer connected to three 1/4W fixed resistors mounted on a small section of perfboard glued to the back of the potentiometer. The network is connected to a pair of input/output female BNC jacks and three color-coded 22 AWG stranded and insulated wires. The tinned opposite ends of the color-coded wires are inserted into the socket board at the top of the photo to connect to the pins of a FET to be tested which is also inserted into the socket board. Accompanying this article is a parts and materials list including stock numbers and the corresponding vendor name.

Photo 2 shows the resistive network. To construct it, first cut a 1" x 2" section of perfboard and glue it to the back of the 100KW pot, R2. After the glue has set, three push-in terminals are inserted into the perfboard in line with the terminals of the potentiometer R2. Solder the three fixed 1/4W resistors R1,

PARTS LIST

(Fig. 2)

Part #	Stock #	Value/Description	Vendor
R1	291-2.2M	2.2 Megohm 1/4W 5% carbon film resistor	Mouser Electronics
R2	31VA501	100K ohm linear taper 24mm potentiometer	Mouser Electronics
R3	291-10K	10K ohm 1/4W 5% carbon film resistor	Mouser Electronics
R4	291-10K	10K ohm 1/4W 5% carbon film resistor	Mouser Electronics
—	276-1394	4-1/2" x 6" IC-spacing perfboard	RadioShack
—	278-1224	22 AWG stranded & insulated hook-up wire	RadioShack
—	574-T42-1/C	Vector push-in terminals for .042" holes	Mouser Electronics
—	161-9323	BNC female jacks (2)	Mouser Electronics
—	276-175	Socket board 2-1/8" x 3-5/8" x 1/16"	RadioShack
—	270-1803	5" x 2-1/2" x 2" project enclosure	RadioShack
—	274-403	1/2" dia. plastic knob	RadioShack
—	—	Two of 1/8" dia. 1/2" Grip Al pop rivets, two of #6-1/2" sheet metal screws, Goop® or an epoxy adhesive	Local hardware store

Mouser Electronics — www.mouser.com — 1-800-346-6873

A UNIVERSAL FET TESTER

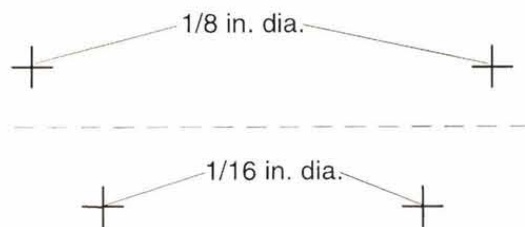


FIGURE 3: Full-size template for bracket supporting socket board.

R3, and R4 to potentiometer R2 and the push-in terminals as shown in Figure 2. At this time, also connect lengths of hook-up wire to the network to be connected to the pair of BNC jacks and for insertion into the socket board.

While waiting for the glue holding the small section of perfboard to the back of the potentiometer to set, you can construct the bracket for mounting the socket board in the enclosure. See Figure 3, which is a full-size template for cutting, drilling, and bending the aluminum lid supplied with the enclosure to form the right angle mounting bracket. The template is attached to the lid with paper-sticking glue between the existing mounting holes drilled in the lid. Reduce the size of the lid to the perimeter of the template. Drill the indicated holes of the template and then form a right angle bend along the dashed line of the template with a bending brake or a bench vise.

Attach the socket board to the mounting bracket with pop rivets through the 1/8" diameter holes in the bracket. With the plastic lid unattached to the enclosure, position the socket board and attached mounting bracket along a first side of the enclosure with the top surface of the socket board about 3/8" below the edge of the opening of the enclosure and centered horizontally. Using the two 1/16" diameter holes in the mounting bracket as a guide, mark the positions on the first side of the

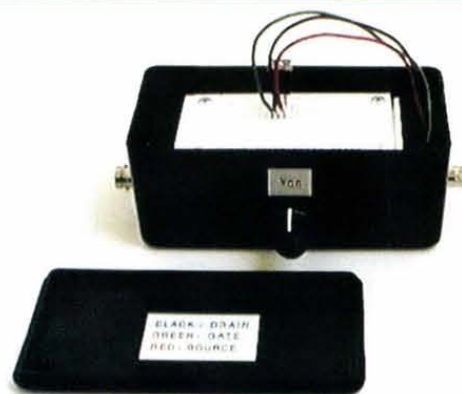


PHOTO 3: The completed tester.

enclosure where 1/8" diameter holes are to be drilled for attaching the bracket to the enclosure.

Drill 5/16" diameter and 1/8" diameter holes, respectively, 1-3/8" and 1-13/16" distance from the (top) edge of the opening of the enclosure along a vertical line equidistant from the ends of the second side of the enclosure for mounting the potentiometer. Drill 3/8" diameter holes at both ends of the enclosure 1-3/8" distance from the top edge of the opening of the enclosure and centered left to right for mounting the BNC jacks.

Mount the resistive network and BNC jacks in the enclosure and solder the connections from the resistive network to the jacks. Mount the socket board in the enclosure by attaching the mounting bracket to the first side of the enclosure with sheet metal screws. A note can be attached to the interior of the plastic lid of the enclosure indicating the colors of the wires to be connected to the gate, drain, and source leads of the FET to be tested. When the tester is not in use, the lid can be attached to the enclosure to protect the breadboard and contain the wires for making connections to a FET. See Photo 3. **NV**

www.nutsvolts.com

USB DAQ



**LabJack™
U12
\$99**

- * 12-bit analog inputs
- * 10-bit analog outputs
- * 20 digital I/O
- * 32-bit counter
- * Watchdog function
- * Built-in screw terminals
- * Easy-to-use USB
- * Everything included
- * Use with C, VB, LabVIEW
- * Windows 98SE/ME/2000/XP



LabJack Corporation
info@labjack.com
(303) 942-0228

www.labjack.com

The Pocket Programmer



The portable programmer that uses the printer port instead of an internal card. Now with easy to use Windows software that programs E(E)prom, Flash & Dallas Ram. 25/27/28 & 29 series from 16K to 8 Megabit with a 32 pin socket. Adapters available for MCU's 874X, 875X, Pic, Atmel, 40-Pin X16, Serial Eprom's, PLCC, Bi-Prom's, Eprom Emulator to 32K X 8 and More.... **Only \$149.95**

Same Name, Address & Phone # for 20 Years....
Isn't it Amazing ?

Intronics, Inc.

Box 12723 / 612 Newton St.
Tel. (913) 422-2094
Fax (913) 441-1623

Add \$7.00 COD
Add \$6.00 Shipping

WWW.IN-KS.COM

Visa/MC/Amex/Disc

**Subscribe to
Nuts & Volts
today and be
automatically
entered each
month in our
prize
drawing!**

**For more
details, and to
find out this
month's prize,
go to
Page 81.**

Polaris Industries, Inc.

WIRELESS VIDEO LIPSTICK CAMERA MONITORS **OVER 700 PRODUCTS IN STOCK!!** DIGITAL RECORDERS ANTENNAS MICRO CAMERAS

1/3" COLOR OUTDOOR CAMERA



Made in the USA



AV-48WC8 - \$235.95

This camera merges the gap between bullet (lipstick) camera and full-size housing with camera. Unlike bullet (lipstick) cameras with limited features, this unit has many features only found on larger, "cased" cameras. The AV-48WC8 keeps the best part of the bullet/lipstick line in that they install quickly and come pre-assembled, ready for installation. Auto iris and vari-focal lens options are available upon request.

We have 6 different configurations to meet your requirements for outdoor or indoor self-contained cameras.

Industrial "O" Ring Sealed Aluminum Case



220X ZOOM HI-RES CAMERA MODULE

Build your own speed dome or motor zoom camera with ease. The Polaris 220X camera module will fit right into your case easily. The life of the 220X motor is essentially 5 times longer than any other brand named camera available today.



AFZ-220X is compact and lightweight. This zoom camera will magnify images up to 220 times and fits into a variety of applications.



AFZ-220X - \$349.95

CAR REAR VIEW VIDEO SYSTEM

The RVK-01 adds visual safety to your car, truck and recreational vehicle. Each unit includes:

- Rear-view Mirror With Built-in TFT Display
- Weatherproof, Wide-Angle Infrared Camera
- Mounting Hardware & Accessories

RVK-01 \$449.95



BOARD CAMERAS



20 Different Models Available

MB-780U B/W BOARD CAMERA \$29.95

1/3" COLOR INFRARED CAMERA



The infrared LEDs make the ILC-300 excellent for video recording in low light situations up to a distance of 10 meters (32.8ft).

The weatherproof anodized aluminum housing and adjustable brackets for wall or ceiling mounts make this an ideal camera in a variety of applications.

ILC-300 - \$189.95

DIGITAL MONITORING & RECORDING SYSTEM

MULTI-ZONE VIDEO MOTION DETECTOR

Software Included!!!



The PV-140 Series turns your PC into a commercial grade digital security system in a few minutes. This incredible series integrates a color quad processor, multi-zone video motion detector, multiplexer, and a real time digital video recorder (DVR). By ordering additional cards, you can increase your surveillance up to 16 different cameras.



PV-140 PACK
4 Pieces/One Pack
\$1099.95

SAVE \$100



PV-140A/B/C/D - \$299.95

PV140 Card Configuration:

- PV-PACK= 140A+140B+140C+140D(4pcs in 1 pack)
- 140A 1st four cameras/windows
- 140B 2nd four cameras/windows (expands to = 8 windows)
- 140C 3rd four cameras/windows (expands to = 12 windows)
- 140D 4th four cameras/windows (expands to = 16 windows)

Cards MUST be utilized in this order.

System Requirements:

- Windows 98/ME/2000/XP
- Pentium III-550Mhz or higher with free PCI slot(s)
- 128 MB+ System Memory
- PCI/AGP bus graphics card (24 bit high color or 64 bit)
- Sound Card (optional)
- Hard Disk Space - 1 GB+ per camera; 10GB+ is recommended
- Microsoft DirectX or higher version
- CD-ROM / DVD-ROM device
- Cameras up to 1/2/4/8/12/16

Real-Time Video Digital Recorder

PENCAM



PENCAM is the newest member to our line of covert cameras. It's small, lightweight design allows the PENCAM to slip into your shirt or coat pocket. Each unit has a built-in mic for audio and works as a fully functional pen.

Call Today for More Information!

PENCAM - \$225.95



USB-01 \$89.95

Additional Features- Call Today!!!



USB-01 The USB Video Converter acts as an interface for your analog video sources and converts analog output to digital for your computer. The USB Video Converter accepts high resolution SVHS video and standard composite NTSC video.

5" WIRELESS OBSERVATION SYSTEM

Now you can enjoy peace of mind with our new wireless observation system. Each comes with a 5" wireless monitor & wireless camera. Just plug & play for perfect wireless video any time!

Great for around the house, office or technical field work.



GW-2400SA \$379.95



DX-7811S 1/3" HIGH RESOLUTION DSP COLOR CAMERA

DX-7811S Our NEW Digital Signal Processing (DSP) Camera offers you a Day/Night Camera with Digital Zoom, Mirror Function, 470 lines of resolution, backlight compensation, gain control & low lux. An excellent addition to your current security system or a great beginning to a new system.

This camera has all the features of the brand names without the brand name price!

DX-7811S \$169.96



800-308-6456 WWW.POLARISUSA.COM



WESTERN TEST SYSTEMS

WE BUY AND SELL

Inquiries 307-635-2269 • Fax 307-635-2291

Orders 800-538-1493

2701 Westland Court, Unit B, Cheyenne, Wyoming 82001

OSCILLOSCOPES & ACCESSORIES

OSCILLOSCOPES

PROBES

TEKTRONIX 1101 "Accessory Power Supply, for FET probes"	\$175.00
TEKTRONIX A6902B "Voltage Isolator, DC-20 MHz, 20 mV-500 V/division"	\$500.00
TEKTRONIX P6201 900 MHz 1X/10X/100X FET Probe	\$400.00
TEKTRONIX P6202 500 MHz 10X FET Probe	\$150.00

WAVEFORM GENERATORS

FUNCTION GENERATORS

HP 3310A "5 MHz Function Generator, 15V/50 Ohms"	\$225.00
HP 33120A-001 "15 MHz Function/Arb. Waveform Gen., phase lock option"	\$1250.00
HP 3324A "21 MHz Function Synthesized Generator, HP1B"	\$2250.00
HP 3325A "21 MHz Synthesizer/Function Generator, HP1B"	\$950.00
HP 3325B-002 "Synthesizer/Function Generator, 1 uHz-21 MHz, HP1B"	\$4000.00
TEKTRONIX AWG5102 "Arb. Waveform Gen., 20 MS/s, 12 bits, 50 ppm synthesis <1 MHz"	\$650.00
TEKTRONIX AWG5102-opt.2 "Arbitrary Waveform Generator, dual channel option"	\$800.00
TEKTRONIX DD501 "Digital Delay & Burst Gen., for function & pulse gen's"	\$200.00
TEKTRONIX FG5010 "Programmable 20 MHz Function Generator, TM5000 series"	\$600.00
TEKTRONIX FG502 "11 MHz Function Generator, TM500 series"	\$275.00
TEKTRONIX FG503 "3 MHz Function Generator, TM500 series"	\$250.00
WAVETEK 288 "20 MHz Synthesized Function Generator, GPIB"	\$650.00

PULSE GENERATORS

BERKELEY NUC 7085B "Digital Delay Gen., 0-100 mS, 1 nS res., 5 Hz-5 MHz"	\$400.00
HP 214B "10 MHz Pulse Generator, up to 50V/50 Ohms"	\$1200.00
HP 214B-001 "10 MHz Pulse Generator, pulse counting option"	\$1400.00
HP 8007B 100 MHz Pulse Generator	\$450.00
HP 8012B "50 MHz Pulse Generator, variable transition time"	\$600.00
HP 8013A 50 MHz Dual Output Pulse Generator	\$500.00
HP 8013B 50 MHz Dual Output Pulse Generator	\$600.00
HP 8112A "50 MHz Pulse Generator, HP1B"	\$3000.00
HP 8116A 50 MHz Pulse/Function Generator	\$2500.00
HP 8116A-001 "50 MHz Pulse/Function Generator, burst & log sweep option"	\$3250.00
TEKTRONIX PG502 "250 MHz Pulse Generator, TM500 series"	\$500.00
TEKTRONIX PG508 "50 MHz Pulse Generator, TM500 series"	\$350.00

VOLTAGE & CURRENT

VOLTMETERS

FLUKE 845AR High Impedance Voltmeter/Null Detector	\$350.00
HP 3456A "6-1/2 digit Voltmeter, HP1B"	\$450.00
HP 3478A "5-1/2 digit Multimeter, HP1B"	\$450.00
KEITHLEY 181 "6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB"	\$675.00
TEKTRONIX DM5010 "4-1/2 digit Multimeter, TM5000 series"	\$300.00
TEKTRONIX DM501A "4-1/2 digit Multimeter, TM500 series"	\$225.00

CALIBRATION

FLUKE 510A "AC Reference Standard, 10 VRMS, 0-10 mA"	\$450.00
FLUKE 5220A "Transconductance Amplifier, DC-5 kHz, 0-20 A"	\$1250.00

VOLTAGE SOURCES

HP 6114A "Precision Power Supply, 0-20 V 2 A/0-40 V 1 A"	\$650.00
HP 6115A "Precision Power Supply, 0-50 V 0.8 A/0-100 V 0.4 A"	\$650.00
TEKTRONIX PS5004 "Precision Power Supply, 0-20 V 0-300 mA, 1 mV res."	\$950.00

CURRENT METERS & SOURCES

HP 4140B "DCV Source/Picoammeter, HP1B"	\$3500.00
HP 6177C "DC Current Source, to 50 V, 500 mA"	\$500.00
HP 6181C "DC Current Source, to 100 V, 250 mA"	\$500.00
KEITHLEY 225 "Current Source, 0.1 uA-100 mA, 10-100 V compliance"	\$450.00
TEKTRONIX P6022 "AC Current Probe, 935 Hz-120 MHz, 6 A peak"	\$250.00
VALHALLA 2500 "AC/DC Current Calibrator, 2 uA-2 A, DC-10 kHz"	\$500.00

IMPEDANCE & COMPONENT TEST

L.C.R.

BOONTON 62AD "1 MHz Inductance Meter, 2-2000 uH"	\$500.00
BOONTON 72BD "1 MHz Capacitance Meter, 2-2000 pF f.s. 3 digits"	\$800.00
BOONTON 72C "1 MHz Capacitance Meter, 1-3000 pF f.s. analog"	\$800.00
GENERAL RADIO 1658 "RLC Digibridge, 120 Hz/1 kHz"	\$1000.00
HP 4262A "3-1/2 digit LCR Meter, 120 Hz/1 kHz/10 kHz"	\$950.00
HP 4274A "5-1/2 digit LCR Meter, 100 Hz-100 kHz, HP1B"	\$2750.00

STANDARDS

E.S.I. SR-1 "Standard Resistor, various values"	\$125.00
E.S.I. SR1010 "Resistance Transfer Standards, 1 Ohm-100 K/step"	\$500.00
GENERAL RADIO 1406-series "Standard Air Capacitors, GR900 connector, 0.1% acc"	\$275.00
GENERAL RADIO 1409-series "Standard Capacitors, 0.001-1.0 uF values available"	\$150.00
GENERAL RADIO 1433-J "4-Decade Resistor, 0-11.11 Kilohms, 1 Ohm steps"	\$150.00
GENERAL RADIO 1433-K "4-Decade Resistor, 0-1.11 Kilohms, 0.1 Ohm steps"	\$150.00
GENERAL RADIO 1433-P "5-Decade Resistor, 0-1.1111 Megohms, 10 Ohm steps"	\$200.00
HP 4440B "Decade Capacitor, 40 pF-1.2 uF"	\$750.00

HI & LO RESISTANCE

HP 4329A "High Resistance Meter, 500 Kilohms-2x 10e16 Ohms"	\$875.00
---	----------

T.D.R.

TEKTRONIX "1503B-03.04" "TDR, 0-50,000 feet; chart rec. & battery options"	\$2500.00
--	-----------

POWER SUPPLIES

SINGLE OUTPUT

HP 6011A "0-20 V/0-120 A/1000 Watts max., CV/CC Supply"	\$1800.00
HP 6028A "0-60 V/0-10 A/200 Watts max. Autorange Supply"	\$1000.00
HP 6033A "0-20 V/0-30 A/200 Watts max. Supply, HP1B"	\$1200.00
HP 6038A "0-60 V/0-10 A/200 Watts max. Supply, HP1B"	\$1200.00
HP 6203B "0-7.5 V/0-3 A CV/CC Power Supply"	\$175.00
HP 6205C "Dual Power Supply, 0-40 V 300 mA/0-20 V 600 mA"	\$300.00
HP 6207B "0-160 V/0-200 mA CV/CC Power Supply"	\$200.00
HP 6263B "0-20 V/0-10 A CV/CC Power Supply"	\$375.00
HP 6266B "0-40 V/0-5 A CV/CC Power Supply"	\$375.00
HP 6267B "0-40 V/0-10 A CV/CC Power Supply"	\$550.00
HP 6271B "0-60 V/0-3 A CV/CC Power Supply"	\$375.00
HP 6274B "0-60 V/0-15 A CV/CC Power Supply"	\$650.00
HP 6384A "0-5.5 V at 8 A CV/CC Power Supply"	\$125.00
HP 6443B "0-120 V/0-2.5 A CV/CC Power Supply"	\$375.00
HP 6515A "0-1600 V/5 mA CV/CC Power Supply"	\$275.00
HP 6525A "0-4000 V/0-50 mA CV/CC Power Supply"	\$650.00
HP 6552A "0-20 V/0-25 A CV/CC Power Supply"	\$1000.00
HP 6643A "0-35 V/0-6 A CV/CC Power Supply, HP1B"	\$1200.00
HP 6652A "0-20 V/0-25 A CV/CC Power Supply, HP1B"	\$1875.00
KEPCO ATE 36-8M "0-36 V/0-8 A CV/CC Power Supply"	\$300.00
SORENSEN SRL 20-12 "0-20 V/0-12 A CV/CC Power Supply"	\$350.00
SORENSEN SRL 60-8 "0-60 V/0-8 A CV/CC Power Supply"	\$450.00

MULTIPLE OUTPUT

HP 6228B "Dual Power Supply, 0-50 V/0-1 A, CV/CC"	\$375.00
HP 6236B "Triple Output Supply, +/-20 V/0.5 A & 0-6 V/2.5 A"	\$375.00
HP 6237B "Triple Output Supply, +/-20 V/0.5 A & 0-18 V/1 A"	\$375.00
HP 6253A "Dual Power Supply, 0-20 V/0-3 A, CV/CC"	\$375.00
HP 6255A "Dual Power Supply, 0-40 V/0-1.5 A, CV/CC"	\$375.00
HP 6622A "Dual Output Supply, 0-20V 0-4A or 0-50V 0-2A, HP1B"	\$1850.00
HP 6627A "Quad Output Power Supply, 0-20 V/2A or 0-50V 800mA"	\$2750.00

TEKTRONIX PS503A "Dual Power Supply, TM500 series"	\$200.00
--	----------

MISCELLANEOUS

ACME PS2L-500 "Programmable Load, 0-75 V/0-75 A/500 Watts max"	\$350.00
ACME PS2L-500 "Programmable Load, 0-75 V/0-75 A/500 Watts max"	\$300.00
HP 6826A "Bipolar Power Supply/Amplifier, +/-50 V/1 A max"	\$900.00
HP 6827A "Bipolar Power Supply/Amplifier, +/-100 V/+500 mA"	\$900.00
KEPCO BOP 50-2M "Bipolar Amplifier/Power Supply, to 50 V, 2 A"	\$400.00
TRANSISTOR DEV DAL-50-15 "Programmable Load, 0-50 V, 0-15 A, 100 Watts max"	\$200.00

TIME & FREQUENCY

UNIVERSAL COUNTERS

HP 5314A 100 MHz/100 nS Universal Counter	\$175.00
HP 5315A 100 MHz/100 nS Universal Counter	\$350.00
HP 5315A-003 "100 MHz/100 nS Counter, 1 GHz C-channel"	\$450.00
HP 5315B 100 MHz/100 nS Universal Counter	\$375.00
HP 5316A "100 MHz/100 nS Universal Counter, HP1B"	\$450.00
PHILIPS PM6672/411 "120 MHz/100 nS Universal Counter, 1 GHz C-channel"	\$300.00
TEKTRONIX DC5009 "135 MHz/10 nS Counter/Timer, TM5000 series"	\$350.00
TEKTRONIX DC503A "125 MHz/100 nS Universal Counter, TM500 series"	\$250.00
TEKTRONIX DC509 "135 MHz/10 nS Universal Counter, TM500 series"	\$275.00

FREQUENCY COUNTERS

EIP 548A-06 26.5 GHz Frequency Counter & mixers for 26-60 GHz	\$3950.00
---	-----------

EIP "578-02/05" "26.5 GHz Source Locking Counter, GPIB & power meter"	\$2750.00
EIP 578-06 "26.5 Source Locking Counter, extendable to 110 GHz"	\$3500.00
HP 5342A 18 GHz Frequency Counter	\$900.00
HP 5343A-001 "26.5 GHz Frequency Counter, OCXO reference"	\$2500.00
HP 5345A/55A/56B 26.5 GHz CW/Pulse Frequency Counter	\$3500.00
HP 5352B-010 "40 GHz Frequency Counter, OCXO reference option"	\$7500.00
HP 5384A "225 MHz Frequency Counter, HP1B"	\$450.00
XL MICROWAVE 3401 "40 GHz Source Locking Frequency Counter, GPIB"	\$5500.00

STANDARDS

HP 105B "Quartz Oscillator, 0.1/1.0/5.0 MHz, battery pwr."	\$1100.00
--	-----------

AUDIO & BASEBAND

SPECTRUM ANALYSIS

HP 3586C "Selective Level Meter, 50 Hz-32.5 MHz, 50k 75 Ohms"	\$1000.00
---	-----------

DISTORTION ANALYZERS

HP 8903A "Audio Analyzer, 20 Hz-100 kHz, HP1B"	\$1200.00
HP 8903B-001,010,053 "Audio Analyzer, 20 Hz-100 kHz, HP1B"	\$1850.00
HP 8903C "Audio Analyzer, 20 Hz-100 kHz, HP1B"	\$1650.00

RMS VOLTMETERS

FLUKE 8922A "True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz"	\$450.00
---	----------

OSCILLATORS

TEKTRONIX SG502 "Sine/Square Osc., 5 Hz-500 kHz, 70 dB step atten., TM500"	\$200.00
TEKTRONIX SG505-opt.2 "Oscillator, 10 Hz-100 kHz; IM test & 50/150/600 Ohms"	\$800.00
WAVETEK 98 "1 MHz Synthesized Power Oscillator, GPIB"	\$750.00

MISCELLANEOUS

HP 3575A "Phase-Gain Meter, 1 Hz-13 MHz, single display"	\$600.00
HP 3575A-001 "Phase-Gain Meter, 1 Hz-13 MHz, dual display"	\$750.00
KROHN-HITE 3200 "High Pass/Low Pass Filter, 20 Hz-2 MHz"	\$275.00
KROHN-HITE 3202 "Dual HP/LP/BP/BR Filter, 20 Hz-2 MHz"	\$375.00
Krohn-Hite 7600 "Wideband Amplifier, 0-42 dB gain, DC-1 MHz, 10 Watts"	\$750.00
ROCKLAND 852 "Dual Highpass/Lowpass Filter, 0.1 Hz-111 kHz"	\$650.00
TEK AM502 "1 MHz Differential Amplifier, TM500 series"	\$450.00

RF & MICROWAVE

SPECTRUM ANALYZERS

HP 11517A/19A/20A "Mixer Set, 18-40 GHz, for HP 8555A/8569A"	\$475.00
HP 11970A "WR28 Harmonic Mixer, 26.5-40 GHz"	\$1000.00
HP 11970K "WR42 Harmonic Mixer, 18.0-26.5 GHz"	\$1000.00
HP 11970Q "WR22 Harmonic Mixer, 33-50 GHz"	\$1400.00
HP 11970U "WR19 Harmonic Mixer, 40-60 GHz"	\$1600.00
HP 11971A "WR28 Harmonic Mixer, 26.5-40 GHz, for 8569B"	\$800.00
HP 11971K "WR42 Harmonic Mixer, 18.0-26.5 GHz, for 8569B"	\$800.00
HP 11974A "WR28 Pselected Mixer, 26.5-40 GHz"	\$8000.00
HP 11975A "L.O. Amplifier, 2-8 GHz"	\$1400.00
HP 3335A "Synthesized Level Generator, 200 Hz-81 MHz, -86.98 +13.01 dBm"	\$3250.00
HP 8562A "Spectrum Analyzer, 1 kHz-22 GHz, 100 Hz min.res. BW"	\$16000.00
HP 85640A "Tracking Generator, 300 kHz-2.9 GHz, for HP 8560 series"	\$4000.00
HP 8569B "Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min.res.bw"	\$5000.00
TEKTRONIX WM782V "WR15 Harmonic Mixer, 50-75 GHz"	\$1500.00

NETWORK ANALYZERS

HP 11650A Network Analyzer Accessory Kit	\$500.00
HP 11650A "Network Analyzer Accessory Kit, APC7"	\$600.00
HP 11665B "Modulator, 0.15-18 GHz, for HP 8755/6/7"	\$250.00
HP 11665B "Modulator, 0.15-18.0 GHz, for HP 8755/6/7"	\$250.00
HP 3577B "Network Analyzer, 5 Hz-200 MHz"	\$9500.00
HP 4191A "RF Impedance Analyzer, 1-1000 MHz, 1 milliohm-100 Kilohms"	\$3750.00
HP 4193A "Vector Impedance Meter, 400 kHz-110 MHz, 10 Ohms-100 K"	\$4500.00
HP 8502B "75 Ohm Transmission/Reflection Test Unit, 0.5-1300 MHz"	\$675.00
HP 85044B "75 Ohm Transmission/Reflection Test Unit, 300 kHz-2 GHz"	\$1250.00
HP 85054A "Type N Calibration Kit, for HP 8510 series"	\$1800.00
HP 8717B-001 Transistor Bias Supply	\$350.00
HP 8751A-001,002 "Network Analyzer, 5 Hz-500 MHz"	\$12500.00



90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



HP 8756A "Scalar Network Analyzer, HPIB" \$1375.00
HP R85026A "WR28 Detector, 26.5-40 GHz,
for HP 8757 series" \$1200.00

SIGNAL GENERATORS

FLUKE 6060B/AK "Signal Generator, 0.1-1050 MHz,
10 Hz res." \$1250.00
FLUKE "6060B-130,830" "Signal Generator, 0.1-1050 MHz,
10 Hz res., GPIB" \$1600.00
GIGATRONICS 1018 "Signal/Sweep Gen., 0.05-18 GHz,
1 kHz res., +8 dBm" \$5000.00
GIGATRONICS 600/6-12 "Synthesized Source, 6-12 GHz,
1 MHz res., GPIB" \$1500.00
GIGATRONICS 6000/8-16 "Synthesized Source, 8-16 GHz,
1 MHz res., GPIB" \$2250.00
GIGATRONICS 6061A-830 "Signal Generator, 0.1-1050 MHz,
10 Hz res., AM, FM, GPIB" \$1900.00
HP 11707A "Test Plug-in, for HP 8660 series" \$400.00
HP 11720A "Pulse Modulator, 2-18 GHz, 80 dB on/off ratio" \$450.00
HP 8341B "Synth. Signal Generator, 10 MHz-20 GHz,
1 kHz res., AM, FM" \$16000.00
HP 8642M "Signal Generator, 0.1-2100 MHz, 1 Hz res.,
HPIB" \$3750.00
HP 8656B-001 "Signal Generator, 0.1-990 MHz, 10 Hz res.,
HPIB, OCXO" \$2000.00
HP 8657A "Signal Generator, 0.1-1040 MHz, 10 Hz res.,
AM, FM, HPIB" \$3000.00
HP 8660C/603A/833B "Signal Generator, 1-2600 MHz,
1 or 2 Hz res., AM, FM, GPIB" \$3250.00
HP 8660D/603A-002 "Signal Generator, 1-2600 MHz,
FM/PM, includes 86635A" \$6000.00
HP 8671A "Signal Gen., 2.0-6.2 GHz, 1 kHz res.,
CW, FM, +8 dBm, HPIB" \$2750.00
HP 8672A "Signal Generator, 2-18 GHz, 1-3 kHz res.,
AM, FM, +3 dBm" \$4500.00
HP 8672A-008 "Signal Generator, 2-18 GHz, 1-3 kHz res.,
AM, FM, +8 dBm" \$5000.00
HP 8673C "Signal Gen., 0.05-18.6 GHz, 1 kHz res.,
AM, FM, Pulse, HPIB" \$14000.00
HP 8673D-H15 "Signal Gen., 0.05-26 GHz, 1 kHz res.,
AM, FM, HPIB" \$15000.00
HP 8673H-212 "Signal Generator, 2.0-12.4 GHz, 1 kHz res.,
AM, FM, +8 dBm" \$8500.00
HP 8673M "Signal Generator, 2-18 GHz, 1 kHz res.,
AM, FM, +8 dBm" \$9500.00
HP 8683B "Signal Generator, 2.3-6.5 GHz, cavity tuned,
AM/ WBIFM/ Pulse" \$2250.00
HP 8683D "Signal Generator, 2.3-13.0 GHz, cavity tuned,
AM/ WBIFM/ Pulse" \$3750.00
HP 8684B "Signal Generator, 5.4-12.5 GHz, cavity tuned,
AM/ WBIFM/ Pulse" \$2250.00
MARCONI 2019 "Signal Generator, 80 kHz-1040 MHz,
10 or 20 Hz res" \$850.00
WAVETEK 955 "Signal Generator, 7.5-12.4 GHz,
+7 dBm, AM, FM" \$750.00
WAVETEK 957 "Signal Generator, 12-18 GHz,
+7 dBm, AM, FM" \$750.00

SWEEP GENERATORS

HP 8350B/83522A "Sweep Oscillator, 10-2400 MHz,
+13 dBm levelled" \$3750.00
HP 8350B/83525A "Sweep Oscillator, 10 MHz-8.4 GHz,
+13 dBm levelled" \$5000.00
HP 8350B/83540A-002 "Sweep Oscillator, 2.0-8.4 GHz,
70 dB step atten." \$3250.00
HP 8350B/83545A-002 "Sweep Oscillator, 5.9-12.4 GHz,
+16 dBm, step atten." \$3750.00
HP 8350B/83550A "Sweep Oscillator, 8-20 GHz,
+20 dBm levelled output" \$5000.00
HP 8620C Sweep Oscillator Frame \$500.00
HP 86222B-002 "RF Plug-in, 10-2400 MHz, +13 dBm,
70 dB step atten." \$1250.00
HP 86222B-E69/8620C "Sweep Osc. & frame,
0.01-2 GHz & 2-4 GHz bands" \$1200.00
HP 86241A "RF Plug-in, 3.2-6.5 GHz, +8 dBm unlevelled" \$250.00
HP 86245A "RF Plug-in, 5.9-12.4 GHz, +16 dBm unlevelled" \$400.00
HP 86251A "RF Plug-in, 7.5-18.6 GHz, +10 dBm levelled" \$500.00
HP 86260A "RF Plug-in, 12-18 GHz, +10 dBm unlevelled" \$400.00
HP 86260A-H04 "RF Plug-in, 10-15 GHz, +10 dBm unlevelled" \$400.00
HP 86290B "RF Plug-in, 2.0-18.6 GHz, +10 dBm levelled" \$1500.00
HP 86290C "RF Plug-in, 2.0-18.6 GHz, +13 dBm levelled" \$1750.00
WAVETEK 2001 "Sweep Generator, 1-1400 MHz, +10 dBm,
70 dB atten." \$750.00
WAVETEK 2002B "Sweep Generator, 1-2500 MHz, +13 dBm,
GPIB" \$1750.00
WILTRON 6647M "Sweep Generator, 10 MHz-20 GHz,
+10 dBm, GPIB" \$4500.00
WILTRON "6699B-02.03" "Sweep Gen., 0.01-26.5 GHz/ K conn.
& 26-40 GHz/ WR28" \$7500.00
WILTRON 6717B-20 "Synthesizer/ Sweeper, 10 MHz-8.4 GHz,
+13 dBm, GPIB" \$6000.00

POWER METERS

BOONTON 42B/41-4E "Analog Power Meter,
with 1 MHz-18 GHz sensor" \$400.00
HP 11683A "Range Calibrator, for HP 435/6/7/8" \$750.00
HP 435B/8481A "Power Meter, -30 to +20 dBm, 10 MHz-18 GHz" \$900.00
HP 436A-022/8481A "Power Meter, -30 to +20 dBm,
10 MHz-18 GHz, HPIB" \$1200.00
HP 436A-022/8482A "Power Meter, -30 to +20 dBm,
100 kHz-4.2 GHz, HPIB" \$1200.00
HP 436A-022/8484A "Power Meter, -70 to -20 dBm,
10 MHz-18 GHz, HPIB" \$1200.00

HP 436A-022/8485A "Power Meter, -30 to +20 dBm,
50 MHz-26.5 GHz, HPIB" \$1500.00
HP 436A-022/8485D "Power Meter, -70 to -20 dBm,
50 MHz-26.5 GHz, HPIB" \$1700.00
HP 438A Dual Channel Power Meter \$3000.00
HP 8477A "Power Meter Calibrator, for HP 432 series" \$400.00
HP 8487D "High Sensitivity Sensor, -70 to -20 dBm,
50 MHz-50 GHz, 2.4mm" \$1850.00
HP 8900D/84811A "Peak Power Meter,
0.1-18 GHz, 0-20 dBm peak" \$2500.00
HP Q8486A "Power Sensor, 33-50 GHz,
-30 to +20 dBm, for 435/6/7/8" \$1500.00
HP R8486A "Power Sensor, 26.5-40 GHz,
-30 to +20 dBm, for 435/6/7/8" \$1500.00
HP R8486D "Power Sensor, 26.5-40 GHz,
-70 to -20 dBm, for 435/6/7/8" \$1750.00

RF MILLIVOLTMETERS

BOONTON 92C "RF Millivoltmeter, 3 mV-3 V f.s.,
10 kHz-1.2 GHz" \$500.00
RACAL-DANA 9303 "RF Millivoltmeter, -70 to +20 dBm,
10 kHz-2 GHz, GPIB" \$750.00

AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RES. 50AR15 "Amplifier, 50 Watts,
46 dB gain, 0.1-15 MHz" \$1000.00
BOONTON 82AD "Modulation Meter, AM/ FM,
10-1200 MHz" \$500.00
HP 11713A "Switch / Attenuator Driver, HPIB" \$800.00
HP 11729B-003 "Carrier Noise Test Set,
5 MHz-3.2 GHz" \$1900.00
HP 3730B/3738B "Downconverter,
5.9-8.9 GHz & 8.7-11.7 GHz" \$1200.00
HP 415E SWR Meter \$200.00
HP 8347A "RF Amplifier, 25 dB gain, 100 kHz-3 GHz,
+20 dBm, HPIB" \$2750.00
HP 8349A "Amplifier, 15 dB gain, 2-20 GHz,
+20 dBm output" \$1650.00
HP 8403A-002 "Pulse Modulator, 0.8-2.4 GHz,
80 dB dynamic range" \$450.00
HP 8406A "Comb Generator, 1/ 10/ 100 MHz increments,
to 5 GHz" \$500.00
HP 8447A-001 "Dual Amplifier, 20 dB, 0.1-400 MHz,
+6 dBm Po, NF <7 dB" \$650.00
HP 8447D-010 "Preamplifier, 25 dB gain,
0.1-1300 MHz, -8.5 dB NF" \$750.00
HP 8447E "Amplifier, 22 dB, 0.1-1300 MHz,
+13 dBm output" \$650.00
HP 8447F-H64 "Dual Amp., 0.01-50 MHz 28 dB
& 0.1-1300 MHz 25 dB" \$900.00
HP 8901A "Modulation Analyzer,
150 kHz-1300 MHz, HPIB" \$1350.00
HP 8901B-001 "Modulation Analyzer,
150 kHz-1300 MHz, HPIB" \$1900.00
MPD LAB-1510-10 "Amplifier, 48 dB gain,
500-1000 MHz, 10 Watts" \$750.00
RACAL 9009 "Modulation Meter, 30-1500 MHz, AM,
1.5-100 kHz pk FM" \$350.00
RF POWER LABS ML50 "Amplifier, 2-30 MHz,
47 dB gain, 50 Watts, metered, 28 V" \$200.00
ROHDE&SCHWARZ ESH2 "Test Receiver,
9 kHz-30 MHz" \$3250.00

COAXIAL & WAVEGUIDE

AEROWAVE 28-3000/10 "WR28 Directional Coupler,
10 dB, 26.5-40 GHz" \$300.00
AMERICAN NUC. AM-432 "Cavity Backed Spiral Antenna,
LHC, 2-18 GHz, TNC(I) NEW" \$95.00
AVANTEK AMT-400X2 "WR28 Active Doubler,
+10 dBm in 8 out" \$450.00
BIRD 8201 "500 Watt Oil Dielectric Load, DC-2.5 GHz,
100 Watts max., N(mf)" \$75.00
GENERAL RADIO 874-LTL "Constant Impedance Trombone Line,
0.44 cm, DC-2 GHz" \$400.00
HP 11590A-001 "Bias Network, 1.0-18.0 GHz, APC7" \$450.00
HP 11691D "Directional Coupler, 22 dB, 2-18 GHz,
N connectors" \$450.00
HP 11692D "Dual Directional Coupler, 22 dB, 2-18 GHz" \$800.00
HP 33327L-006 "Prog. Step Attenuator, 0-70 dB,
DC-40 GHz, 2.9mm" \$1000.00
HP 778D-011 "Dual Dir. Coupler, 20 dB, 0.1-2.0 GHz, APC7" \$450.00
HP 8498A-030 "30 dB Attenuator, 25 Watts, DC-18 GHz" \$500.00
HP 87300C-020 "Directional Coupler, 20 dB, 0.1-26.5 GHz, 3.5mm" \$475.00
HP K422A "WR42 Flat Broadband Detector, 18.0-26.5 GHz" \$350.00
HP K532A "WR42 Frequency Meter, 18.0-26.5 GHz" \$450.00
HP K752C "WR42 Directional Coupler, 10 dB, 18.0-26.5 GHz" \$450.00
HP K752D "WR42 Directional Coupler, 20 dB, 18.0-26.5 GHz" \$450.00
HP K914B "WR42 Slide Screw Tuner, 18.0-26.5 GHz" \$275.00
HP Q752D "WR22 Directional Coupler, 20 dB, 33-50 GHz" \$250.00
HP R281A "WR28 x 2.4mm(I) Adapter" \$650.00
HP R422A "WR28 Crystal Detector, 26.5-40 GHz" \$600.00
HP R752A "WR28 Directional Coupler, 3 dB, 26.5-40 GHz" \$450.00
HP R752D "WR28 Directional Coupler, 20 dB, 26.5-40 GHz" \$450.00
HP R914B "WR28 Moving Load, 26.5-40 GHz" \$250.00
HP V365A "WR15 Isolator, 25 dB, 50-75 GHz" \$750.00
HP V752D "WR15 Directional Coupler, 20 dB, 50-75 GHz" \$650.00
HP X870A "WR90 Slide Screw Tuner" \$150.00
HUGHES 45322H-1110/1120 "WR22 Directional Couplers,
10 or 20 dB, 33-50 GHz" \$350.00

HUGHES 45712H-1000 "WR22 Frequency Meter,
33-50 GHz" \$750.00
HUGHES 45714H-1000 "WR15 Frequency Meter,
50-75 GHz" \$900.00
HUGHES 45722H-1000 "WR22 Direct Reading Attenuator,
0-50 dB, 33-50 GHz" \$1000.00
HUGHES 45724H-1000 "WR15 Direct Reading Attenuator,
0-50 dB, 50-75 GHz" \$1000.00
HUGHES 45732H-1200 "WR22 Level Set Attenuator,
0-25 dB, 33-50 GHz" \$250.00
HUGHES 45752H-1000 "WR22 Direct Reading Phase Shifter,
0-360, 33-50 GHz" \$1400.00
HUGHES 45772H-1100 "WR22 Thermistor Mount,
-20 to +10 dBm, 33-50 GHz" \$400.00
HUGHES 47316H-1111 "WR10 Tunable Detector, 75-110
GHz, pos. polarity" \$600.00
HUGHES 47741H-2310 "WR28 Phase Locked Gunn Osc.,
32 GHz, +18 dBm" \$2000.00
HUGHES 47742H-1210 "WR22 Phase Locked Gunn Osc.,
42 GHz, +18 dBm" \$2750.00
KRYTAR 201020010 "Directional Detector, 1-20 GHz,
SMA(I)/SMC" \$200.00
KRYTAR 2616S "Directional Detector, 1.7-26.5 GHz,
K(I)/SMC" \$200.00
M/A-COM 3-19-300/10 "WR19 Directional Coupler,
10 dB, 40-60 GHz" \$450.00
NARDA 3000-series "Octave Band Directional Couplers,
N connectors" \$150.00
NARDA 3024 "Bi-Directional Coupler, 20 dB, 4-8 GHz" \$375.00
NARDA 3090 Precision High Directivity Couplers \$225.00
NARDA 368BNM "Coaxial High Power Load, 500 Watts,
2-18 GHz, N(m)" \$500.00
NARDA 3752 "Coaxial Phase Shifter, 0-180 deg./GHz,
1-5 GHz" \$900.00
NARDA 3753B "Coaxial Phase Shifter, 0-55 deg./GHz,
3.5-12.4 GHz" \$950.00
NARDA 4000-series "Octave Band Directional Couplers,
SMA connectors" \$75.00
NARDA 4247-20 "Directional Coupler, 20 dB, 6.0-26.5 GHz,
3.5mm(I)" \$200.00
NARDA 5070-series Precision Reflectometer Couplers \$300.00
NARDA 562 "DC Block, 10 MHz-12.4 GHz, 100 V max., N(m/I)" \$65.00
NARDA 765-10 "10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/I)" \$165.00
NARDA 791FM "Variable Attenuator, 0-37 dB, 2.0-12.4 GHz" \$500.00
NARDA 792FF "Variable Attenuator, 0-20 dB, 2.0-12.4 GHz" \$375.00
NARDA 793FM "Direct Reading Variable Attenuator,
0-20 dB, 4-8 GHz" \$225.00
NARDA 794FM "Direct Reading Variable Attenuator,
0-40 dB, 4-8 GHz" \$375.00
OMNI-SPECTRA 2085-6010-00 "Crystal Detector, 1-18 GHz,
neg. polarity, SMA m" \$50.00
PAMTECH KYG1014 "WR42 Junction Circulator,
18.0-26.5 GHz" \$250.00
SONOMA SCI. 21A3 "WR42 Circulator, 20 dB, 20-24.8 GHz" \$75.00
TEKTRONIX 2701 "Step Attenuator, 0-79 dB, DC-1 GHz" \$150.00
TEKTRONIX WM782U "WR19 Harmonic Mixer,
40-60 GHz" \$1500.00
TRG B510 "WR22 Direct Reading Attenuator, 0-50 dB,
33-50 GHz" \$900.00
TRG V551 "WR15 Frequency Meter, 50-75 GHz" \$600.00
TRG W510 "WR10 Direct Reading Attenuator, 0-50 dB,
75-110 GHz" \$1000.00
TRG W551 "WR10 Frequency Meter, 75-110 GHz" \$750.00
WAVELINE 100080 "WR28 Terminated Crossguide Coupler,
30 dB" \$200.00
WEINSCHEL 150-110 "Programmable Step Atten.,
DC-18 GHz, SMA" \$450.00
WEINSCHEL DS109 "Double Stub Tuner, 1-13 GHz, N(m/I)" \$150.00
WEINSCHEL DS109LL "Double Stub Tuner,
0.2-2.0 GHz, N(m/I)" \$150.00

COMMUNICATIONS

HP 37204A-003 "HPIB Extender, fiber-optic connection
"unused" \$250.00
HP 4934A-J02 TMS; CCITT option; battery power \$1650.00
HP 59401A HPIB Bus Analyzer \$375.00
TAMPA MW. LAB BUC1W-02W-CST "Ku band Upconverter,
1 Watt 14.0-14.5 GHz WR75 "NEW" \$150.00
TEKTRONIX 1411R-opt.04 "PAL Test Gen., w/SPG12.TSG11.TSP11,
TSG13,15" \$1400.00
TEKTRONIX 147A "NTSC Test Signal Generator,
with noise test signal" \$800.00

MISCELLANEOUS

EG&G P.A.R. 5302 / 5316 "Lock-in Amplifier, 100 mHz-1 MHz,
GPIB / RS232C" \$2250.00
FLUKE 2180A RTD Digital Thermometer \$500.00
HP 59307A HPIB VHF Switch \$200.00
P.A.R. 5206-95-98 "Two-Phase Lock-in Amp.,
2 Hz-100 kHz, GPIB" \$1250.00
TEKTRONIX TM5003 TM5000-series 3-slot Programmable
Power Module \$450.00
TEKTRONIX TM5006 TM5000-series 6-slot Programmable
Power Module \$500.00
TEKTRONIX TM503 TM500-series 3-slot Power Module \$150.00
TEKTRONIX TM504 TM500-series 4-slot Power Module \$175.00
TEKTRONIX TM506 TM500-series 6-slot Power Module \$250.00
TEKTRONIX TM515 TM500-series 5-slot Portable
Power Module \$250.00

Reader Feedback

Dear Nuts & Volts:

I am disappointed to see more time and energy wasted on the misguided building of regenerative receivers. They stink. Because they don't require alignment, there is little useful experience to be gained in building them and their performance is lousy compared to super-heterodyne receivers. With the possible exception of the passive TRF receiver for use in very specialized applications building anything besides superhets is a waste of effort.

Anonymous

Dear Nuts & Volts:

The most important observation in Louis Frenzel's article on current flow is that it really doesn't matter. For example, Kirchhoff's Laws — as universally applied by engineers, physicists, and technicians — are formulated in terms of "algebraic sums," with the sign of each quantity determined by convention. If it really irks you that someone has defined positive current flow at a junction to be conventional current flowing in, you can redefine it as electrons flowing out. The key is self-consistency.

But the convention of current flowing from the negative terminal of a battery to the positive is not self-consistent — at least not with the bigger picture. Positive current flow from point A to point B is defined as a movement of positive charges from point A to point B — or equivalently, negative charge from point B to point A. A positive potential difference between point B and point A means the electric field vector points from A to B, and the force vector on a positive charge points in the same direction. In the model, Frenzel advocates current appears to flow uphill.

Had Benjamin Franklin — the true culprit in this misunderstanding — guessed right about the direction of the charge carriers he was observing, everything would be exactly the same as it is now, except what is now labelled the positive terminal of a battery would be marked negative and vice versa. To compare changing over from conventional to electron flow and changing from English to metric units is a bit of an oversimplification. Either we could legislate some illogical sign changes into Maxwell's equations,

akin to drawing a mustache on the Mona Lisa, or we could fix the "real world" by shipping power supplies and batteries with their terminals marked opposite to present practice. The second choice would create disasters far greater than mere confusion. The current flow convention would then reflect "the truth" for most metals, but not for p-wafers or metals with complicated Fermi surfaces like tungsten. (Frenzel's sanctimonious description of his way reminds me of a certain right-wing radio talk show host. No wonder he sees such emotional responses to the subject.)

Franklin's true brilliance in this field — not to mention several hundred others — lay in the realization that a signed number is appropriate for describing any electric charge, and that which sign describes which charge is arbitrary. At the risk of adding fuel to the fire, I think engineers, physicists, and college professors resist standardizing on electron flow not because they are old, stodgy, and resist change (most professors are engaged in state-of-the-art research as a condition of their continued employment), but because they see a bigger picture than technicians.

David Liguori
Albany, NY

Dear Nuts & Volts:

I know of Louis E. Frenzel. I've known of Lou since I began writing about electronics in 1960 after reading many of his articles. I'm no Louis E. Fenzel — although I've written almost 100 articles for *Nuts & Volts*.

And now that Joe Carr, Anthony Charlton, Herb Friedman, and so many of the other prolific electronics writers of the last century have gone to the big master grid in the sky, Louis E. Frenzel is one of the few remaining deans of electronics scribes, together with Forrest M. Mims III, Don Lancaster and, of course, TJ Byers.

However, I must disagree with Lou's favoritism of electron flow (EF) versus conventional current flow (CCF). (July 2002, Page 40.) While EF makes physicists comfortable, as an electronics hobbyist, I prefer to "go with the flow" — positive to negative — for one basic reason: the arrows in semiconductor devices point that way! And, at 75, I'm old fashioned.

Whenever I look at a circuit to try to figure out what is happening, I follow the arrows. If I try to use EF reasoning, I get hopelessly confused — or more hopelessly confused!

In all my hundreds of articles in many electronics magazines in the last over-40 years, admittedly written mostly for beginners and intermediate electronics hobbyists, I've strived for practical explanations over theory, always using positive-to-negative current flow for explanations of circuit action. I leave the atoms, holes, valences, doping, and such to those who dabble in theory, while I crank up the iron and build something ... or I did until recently going partially blind.

In one of my recent books (*Simple Low-Cost Electronics Projects* — Butterworth-Heinemann), the circuit descriptions for all 22 projects are explained in detail using current flow rather than electron flow. I've had no complaints.

I'm a KISSer (Keep It Simple, Stupid), not a KICKer (Keep It Complicated, Knucklehead — or they'll figure it out for themselves, and won't need you!).

Fred "Sparks" Blechman

Dear Nuts & Volts:

The direction current "really" flows is the direction that positive charge flows while moving from greater potential to lesser potential. That is the only direction it can possibly flow in order for the math to work out. If we redefine current flow to be the direction that electrons happen to move, then we must also define protons to have negative charge and electrons to have positive charge. Is it really necessary to change the model of the atom simply to appease ornery individuals who are annoyed that the most common charge carrier happens to be negative?

Christopher J. Burian
Waltham, MA

Wanna win \$5,000
in a "Flash?"
Find out how on Page 57

Published Monthly By
T & L Publications, Inc.
430 Princland Court
Corona, CA 92879-1300
(909) 371-8497
FAX (909) 371-3052

E-Mail — editor@nutsvolts.com
URL — http://www.nutsvolts.com

Subscription
Order ONLY Line
1-800-783-4624

PUBLISHER
Jack Lemieux N6ZTD

EDITOR
Larry Lemieux KD6UWV

MANAGING EDITOR
Robin Lemieux KD6UWS

CONTRIBUTORS
Robert Nansel
Jon Williams
Jeff Eckert
TJ Byers
Stanley York
Gordon West
Bob Van Kannon
Louis Frenzel
Ed Driscoll
Ray Marston
Ray Green
Peter Lehmann
Jon Varteresian
Anthony Caristi

ON-THE-ROAD EXHIBIT
COORDINATOR
Audrey Lemieux N6VXW

STAFF
Natalie Sigafus
Mary Gamar

Copyright 2002 by
T & L Publications, Inc.
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. *Nuts & Volts Magazine* assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in *Nuts & Volts*. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in *Nuts & Volts*. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princland Court, Corona, CA 92879.

CALL TOLL-FREE

(800) 292-7711 Orders
Only

Se Habla Español

C&S SALES

Secure On-line Ordering @ cs-sales.com

CALL OR WRITE
FOR OUR
FREE

64 PAGE CATALOG!
(800) 445-3201

Digital Multimeters

Elenco Model M-1740



\$19.95

- 11 Functions:**
- Freq. to 20MHz
 - Cap. to 20µF
 - AC/DC Voltage
 - AC/DC Current
 - Beeper
 - Diode Test
 - Transistor Test
 - Meets UL-1244 safety specs.

Elenco Model LCR-1810



\$89.95

- Cap. 0.1pF to 20µF
- Inductance 1µH to 20H
- Resistance 0.01Ω to 2,000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Freq. up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

Elenco Model LCM-1950



\$65

- Large 1 1/3 3/4 Digit LCD
- Autoranging Freq. to 4MHz
- Cap. to 400µF
- Inductance to 40H
- Res. to 4,000MΩ
- Logic Test
- Diode & Transistor Test
- Audible Continuity Test

Capacitance Meter

Elenco Model CM-1555



\$29.95

- Measures capacitors from 0.1pF to 20,000µF
- 3 1/2 Digit LCD readout with unit indicator
- Zero control for test lead compensation
- Banana jack and special insertion jack included
- Compact size with tilt stand and holster

Deluxe Soldering Stations

Elenco SL-5 Series

Electronically controlled, ideal for professionals, students, and hobbyists. Available in kit form or assembled.

As Low As
\$22.95

Works w/ any iron! Turn any soldering iron into a variable iron.

Features:

- Cushion Grip Handle
- Soldering Iron (optional) with Grounded Tip for Soldering Static-Sensitive Devices. Easily Replaceable. Uses Long-Life, Plated Conical Tip.
- Heavy Steel, Non-Slip Base.
- Iron Holder Funnel - Reversible, left or right side.
- Steel Tray for Sponge Pad.
- Sponge Pad.



Quantity Discounts Available

Test Equipment

Elenco Four Functions in One Instrument Model MX-9300B

Features:

- One instrument with four test and measuring systems:
- 1.3GHz Frequency Counter
- 2MHz Sweep Function Generator
- Digital Multimeter
- Digital Triple Power Supply



\$450

Elenco Multi-Network Cable Tester Model TCT-255

This tester is a convenient instrument for testing different RJ-11 and RJ-45 connectors and coax cables. Cables can be tested before and after they are installed.

- Mapping Function
- Tests cables before or after their installation.
- Cable Identification (straight or reverse)
- Pair Identification (straight or reverse)
- Open or Short Testing
- Low Battery Indicator
- Auto Power-Off Function (30 s.)



\$75

Soft Vinyl Zippered Case (Model C-90) included!

20MHz Sweep / Function Generator with Frequency Counter Model 4040A

- 0.2Hz to 20MHz
- AM & FM Modulation
- Burst Operation
- External Frequency Counter to 30MHz
- Linear and Log Sweep



10MHz Model 4017A
5MHz Model 4011A
2MHz Model 4010A

\$325
\$259
\$225

\$445
BK PRECISION

Elenco Handheld Universal Counter Model F-2800



\$99

Sensitivity:

- <1.5mV @ 100MHz
- <5mV @ 250MHz
- <5mV @ 1GHz
- <100mV @ 2.4GHz

Features 10 digit display, 16 segment and RF signal strength bargraph.

Includes antenna, NiCad battery, and AC adapter.

C-2800 Case w/ Belt Clip.....\$14.95

Elenco RF Generator with Counter (100kHz - 150MHz) Model SG-9500



\$235

Features internal AM mod. of 1kHz, RF output 100MV - 35MHz. Audio output 1kHz @ 1V RMS.

SG-9000 (analog, w/o counter) \$135

Elenco Quad Power Supply Model XP-581

4 Fully Regulated Power Supplies in 1 Unit



\$75

4 DC Voltages: 3 fixed: +5V @ 3A, +12V @ 1A, 1 variable: 2.5 - 20V @ 2A • Fully Regulated & Short Protected • Voltage & Current Meters • All Metal Case

Elenco Power Supply Model XP-603



\$75

- 0-30VDC @ 3A Output
- 3A Fused Current Protection
- Current Limiting Short Protection
- 0.025Ω Output Impedance

Elenco 3MHz Sweep Function Generator w/ built-in 60MHz Frequency Counter Model GF-8046



Generates square, triangle, and sine waveforms, and TTL, CMOS pulse.

\$199.95

GF-8025 - Without Counter \$139.95

Ordering Information:

Model SL-5 - No iron.
(Kit SL-5K)

\$22.95

Model SL-5-40 - Includes 40W UL iron.
(Kit SL-5K-40)

\$27.95

Weller® Low Cost Soldering Iron Model WLC100



- Variable power control produces 5-40 watts.
- Ideal for hobbyists, DIYers and students.
- Complete with 40W iron.

\$32.95

Elenco Oscilloscopes

Free Dust Cover and x1, x2 Probes



UL

\$299


2 year Warranty

- S-1330 25MHz Delayed Sweep \$439
- S-1340 40MHz Dual Trace \$475
- S-1345 40MHz Delayed Sweep \$569
- S-1360 60MHz Delayed Sweep \$725
- S-1390 100MHz Delayed Sweep \$895

DIGITAL SCOPE SUPER SPECIALS

- DS-203 20MHz/10Ms/s Analog/Digital \$695
- DS-303 40MHz/20Ms/s Analog/Digital \$850
- DS-603 60MHz/20Ms/s Analog/Digital \$950

Elenco Snap Circuits™

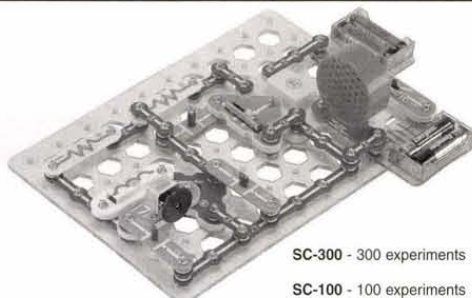

SC-300 - 300 experiments **\$49.95**

SC-100 - 100 experiments **\$29.95**

Elenco's new Snap Circuits™ make learning electronics a "snap". Just follow the colorful pictures in our manual and build over 300 projects, such as AM radios, burglar alarms, flash lights, doorbells, and much more. You can even play electronic games with your friends. All parts are mounted on plastic modules and snap together with ease. Enjoy hours of educational fun while learning about electronics. You can even create your own experiments! No tools required.

Elenco Educational Kits

Model MX-901SW

Short Wave Radio Kit



\$11.95

Model AM-780K

Two IC Radio Kit



\$9.95

Model AK-700

Pulse/Tone Telephone Kit



\$14.95

Model RCC-7K

Radio Control Car Kit



\$27.95

Model M-1006K

DMM Kit



\$18.95

Model K4001

7W Amplifier



\$12.95

K2637 - 2.5W Audio Amplifier - \$10.50

Electronic Science Lab

Maxitronix 500-in-1 Electronic Project Lab Model MX-909

Everything you need to build 500 exciting electronic projects:

- Learn the basics of electronics. 500 different electronic experiments, special lighting effects, radio transmitter and receivers, sound effects, cool games and MORE!
- Includes built-in breadboard and an LCD.
- Explore amplifiers, analog and digital circuits plus how to read schematic diagrams.
- Includes 11 parts.
- Lab-style manual included.
- Requires 6 "AA" batteries.



MX-908 - 300-in-1 Lab **\$59.95**
MX-907 - 200-in-1 Lab **\$44.95**
MX-906 - 130-in-1 Lab **\$29.95**
EP-50 - 50-in-1 Lab **\$18.95**

\$149

Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 5% (Minimum \$5.00)

OTHERS CALL FOR DETAILS

IL Residents add 8.25% Sales Tax

SEE US ON THE WEB

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 541-9904 (847) 541-0710
<http://www.cs-sales.com>



15 DAY MONEY BACK GUARANTEE

2 YEAR FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Electronics Q&A

With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist.

Feel free to participate with your questions, as well as comments and suggestions.

You can reach me at: **TJBYSERS@aol.com** or by snail mail at Nuts & Volts Magazine, 430 Princeland Ct., Corona, CA 92879.

Remote Control Tester

Q I am looking for a circuit to check TV/VCR remote controls. The circuit should consist of an IR detector and a corresponding circuit that would light an LED to show that the remote is working. It would be nice if I could fit the tester in a RadioShack 270-283 project box.

Bernie Petrasek
via Internet

A If all you want to do is check to see if the remote is emitting light, RadioShack sells a card (276-1099) that fluoresces when IR light strikes it. But I suspect you have other plans for the signal, otherwise you wouldn't have asked for an LED indicator. Figure 1 is a simple circuit built around a GP1U52X IR receiver module that will fit in your desired project box.

By the way, you don't need to drill a hole in the case to let in the IR light. It will penetrate the plastic, albeit the range will be reduced by about half.

Remote Control Relay

Q • I wish to drive a small five-volt relay from the output of a TV remote IR receiver. The receiver is housed in a metal can and has three pins: +5 volts, ground, and output.

Ken Schultis
via Internet

A From your description of the receiver, it sounds identical to the GP1U52X module I used in the Figure 1 circuit. This time, though, I'm adding an optoisolator. If you wish, the TLP624 can be replaced with a Darlington transistor, like an

MPSA14. The 10uF cap filters the output pulse and prevents the relay from chattering.

Roll Your Own Drivers

Q In the June 2001 issue, you made a circuit for a sequential timer that controlled 110 VAC lights. Recently, I restored an old railroad color position light — the B & O R.R. type. It's about 3.5 feet in diameter and has two red, two yellow, and two green lights. The bulbs are 12 volt (1156) and each color-pair are wired in parallel. Could you alter your circuit for my 12-volt application? My application would call for each color to be turned on for the same amount of time in the sequence.

Herb Henry
via Internet

A. Either of the circuits I published in the March and June 2001 issues will work for your project. I recommend the 4017 sequencer in Figure 3 because it gives the evenly-spaced intervals you desire

Now to your question: how to interface the output to your specific lights. I'm sure a lot of readers have the same question because I often publish schematics that almost fill their needs if only the output could be changed to match their specific device. So I'm going to serve up a medley of solutions that should let you interface any popular device to any TTL-compatible output. Refer to the drawings in Figure 4 on the next page.

In drawing **(a)**, the output drives an LED when it's low; in drawing **(b)**, the LED lights when the output goes high. R1 limits the drive current to about 10 mA.

What's Up:

Two IR remote control receivers, a simple KVM switch, and the definitive chart of TTL output driver circuits. Looking for hard-to-find parts? Sources for custom panel meters, USB-to-serial port converters, and used Tektronix scopes. How to earn a CET or A+ Certification, and some very techie cool web sites.

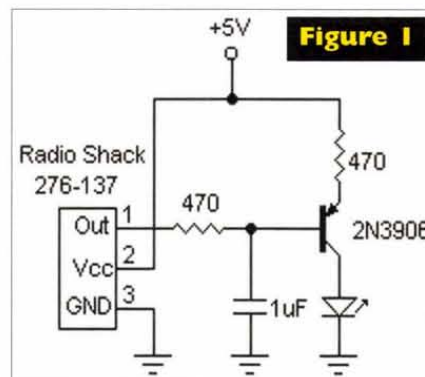


Figure 1

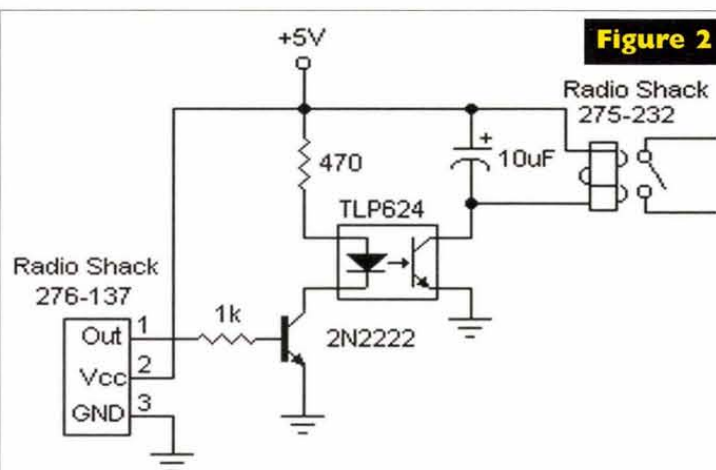


Figure 2


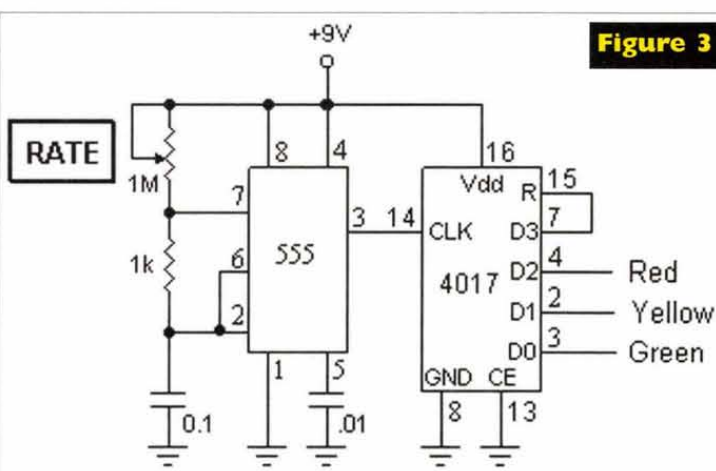


Figure 3

Figure 4

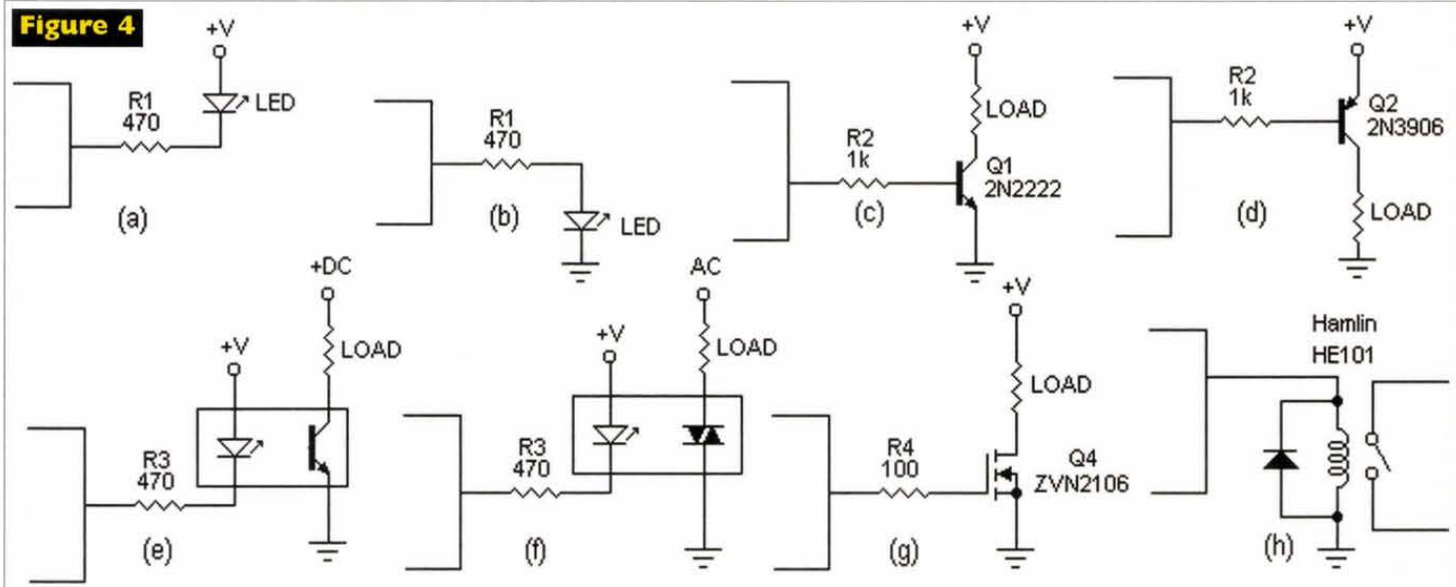

is an FET driver capable of delivering 450 mA when the output is high, and (h) drives a Hamlin reed relay capable of switching 0.5 amps at 200 volts.

Your project needs solution (d). Let's do a little math here to determine the type of transistor you need. Two 1156 lamps in parallel draw about four amps, which means you need to be looking at a power transistor and not a small 2N2222 often found in my designs. The drive current of a TTL gate is between 10 mA and 25 mA, where 10 mA is typical for chips like the 4017. That means we need a gain (Hfe) of 800 ($4A/5mA = 800$) using a value of 1k for R2.

To obtain that much gain and current in a single package, we have to turn to a Darlington transistor; I lean toward the popular TIP series, which includes the TIP125. It's rated 5A at 60 volts, and is available from a number of

sources. Of course, you'll need three TIP125 transistors, one for each color.

Customized Panel Meters

Q I need to locate a source for analog panel meters with a scale of 250 degrees, a 50 uA or 100 uA full scale that's not affected by the panel material, and fast pointer response. I want to use these as instruments for auto/ATV vehicles, so they have to be rugged, and would prefer new units over surplus. The major distributors seem to have dropped this line, and I'm definitely not interested in digital meter replacements. I would greatly appreciate any pointers that you can provide.

**Joseph F. Richmond
Joppa, MD**

A Yes, these once-popular movements have given way

to digital displays. However, they still make them, but get your pocketbook ready, because they ain't cheap. Here are your best bets.

Simpson Electric

www.simpsonelectric.com/pdf/webpdf/250%20ADC.pdf

Her Rong Electrical Works

www.herrong.com

Beede Electrical Instrument Co.

— build your own, USA built
www.beede.com/panel_meters.htm

However, there is an alternative to this expensive solution: LED gauges.

Become A Professional

Q Please recommend suggested reading material that would help me get up to speed for the National Occupational Competency Test for Electronics

(NOCTI). Although I have 35 years in electronics and vocational teaching, with a diploma from Devry of Chicago, I need this permit to teach electronics at the grade and high-school level. Much to my surprise, NOCTI did not offer much help.

**Bob Eichman
via Internet**

A Technology is advancing so fast that it takes a kid on a skateboard just to keep up with it. And you're not the only reader, young or old, who feels like you're being left in the dust. Fortunately, there are several sources available that can keep you up to speed or advance your education, no matter what your level of expertise.

The NOCTI test consists of two parts: written and performance. The written test consists of approximately 200 multiple-choice items and requires three hours to complete. It covers factu-

AUTOTIME

LCD FLAT SCREEN REPAIRS

\$79.00

+ PARTS





LAPTOP DISPLAYS

MONITOR DISPLAYS

KIOSK DISPLAYS

FOR DETAILS: WWW.REPAIRLCD.COM

AUTOTIME - 6605 SW Macadam Ave. - Portland, OR 97239
Phone: (503) 452-8577 Fax: (503) 452-8495 e-mail: info@autotime.com
Custom mounting and video walls at www.slim-screen.com


Circle #53 on the Reader Service Card.

RADIO RESTORATION VIDEO

Bret's Old Radios presents

ANTIQUE RADIO RESTORATION

Volume 1



A Step-By-Step Guide to Old-Radio Repair

Come along as a 1936 Philco is transformed from "flea-market-find" to working, museum-ready show-piece! Along the way, you'll get basic tube theory, basic receiver theory, plus learn to trouble-shoot your set, test voltages, rebuild Bakelite-block capacitors, repair an old lacquer finish without stripping, and much more. For beginning- and intermediate-level restorers, or any old radio lover!

"This is the only video that shows an actual restoration from start to finish. I liked the length; not rushed, or full of short cuts... well made, interesting & informative." - F. Drost

"As a recent recipient of your video, I am now attempting a cabinet improvement project on one of my favorite wooden table radios. Thanks!" - B. Arner

"It is about time somebody put a video together! It's clear and detailed without being drawn out. If there is someone who wants to start in vintage radio, this tape will help them get off on the right foot!" - C. Lucchesi

run time: 115 minutes
© 2001 Bret's Old Radios

ORDER TODAY! Send \$29.99+ \$3 S&H to:
Bret Menassa
c/o Bret's Old Radios
P.O. Box 51671
Denton, TX 76206
bretsoldradios@att.net

Circle #54 on the Reader Service Card.

al knowledge, technical information, understanding of principles, and problem-solving abilities related to the occupation. The second part is a performance test that's administered in a laboratory or industrial setting and consists of work assignments that require four to five hours to complete. It is designed to sample the manipulative skills required by an occupation and, in your case, is most likely optional.

I know, so far I haven't told you anything you don't already know. Yes, I can give you a long list of reading material that is much too boring and time consuming to make any sense. But I'll tell you a secret. If you can pass the CET (Certified Electronic Technician) test, you can pass the NOCTI test. Better news yet is that the people at CET encourage you to look at sample questions that are representative of the questions on the test (www.iscet.org/certification/associate.html), and they score your results. The results will point out your weak and strong points. I strongly recommend this free offer for all serious hobbyists and professionals.

Interested in other certifications that can improve your life and increase your income? Here is a short list.

A+ Certification for Information Technology (IT) professionals.
www.comptia.org

Microsoft certifications: MCP, MCSA, MCSD, and more.
www.microsoft.com/train/cert/mcp/default.asp

Novell certifications: CNA, CNE, CDE, and more.
www.novell.com/education/certinfo/

Certified Internet Webmaster
www.ciwcetified.com/

List and links of certifications around the web.
www.certcities.com/certs/other/

Serial To USB

Q. I'm looking for a circuit to interface serial devices to a USB port. My old computer (with four serial ports) in my ham shack died, and I replaced it with

a laptop/docking station with one serial port and one USB port. I'd like to build an adapter to convert a serial port to a USB port or, ideally, four serial ports into one USB port.

Don via Internet

A. Yes, I suppose you could make a converter built around TI's 8052-based TUSB3410VF serial-to-USB chip, but it's not an overnight project by any stretch of the imagination. Even if you could piece together all the hardware needed, there's still a small detail of programming the chip.

What I'd do is buy a serial-to-USB cable sold by many retailers. A single port interface cable costs between \$25.00 and \$50.00 (Figure 5), and a four-port interface box will set you back \$109.00 to \$229.00. My suggestion is to shop around. Here are a few places to start.



Figure 5

B&B Electronics

www.bb-elec.com/convert_serial_port/usb_chart_nonisolated.asp

Jameco

www.jameco.com/cgi-bin/ncommerce3/ProductDisplay?prmenbr=91&prfnbr=4849&cgrfnbr=501&ctgys=

USBHardware

www.sellusb.com/usb-serial-adapter.html

Simple KVM Switch

Q. I am trying to make a cheap KVM switch. I have two computers and one monitor, and want to switch between the two with one button. It seems like the monitor switching can easily be done with the analog multiplexers, but I'm not sure how to deal with the data lines for USB. Also, do I just connect all of the grounds for both computers and the monitor together, or should I switch them too?

Shawn Jordan via Internet

A. As the computer industry grew in the early 1980s, many server rooms and data centers were faced with the problem of having dozens and even hundreds of monitors, keyboards, and mice, taking up valuable rack space, and adding unnecessary heat issues. The KVM (Keyboard Video Mouse) switch was developed to solve the problem. These KVM switching products allow a single user to access multiple CPUs from a single monitor, keyboard, and mouse.

Both graphical environments and mice were not common in the early 1980s, so the first switches only supported keyboard and video switching, and were very basic A/B type push-button switches. In addition to improving server manageability, heat disbursement issues, and the space savings, there was a huge cost savings from not having to purchase a separate monitor, keyboard, and mouse for each CPU.

These type of KVM switches are still available, and sell for as little as \$49.00. However, for monitor switching alone, it's possible to build your own KVM using a

handful of relays, as shown in Figure 6. Notice that only two relays are shown (it simplifies the wiring on the drawing). When building the switcher, the coils of all relays in the related bank are wired in parallel and switched together. RF relays are preferred for optimum performance, and the coil voltage can be changed to any voltage that's convenient for you. Be sure to take care in dressing the wires to prevent crosstalk between the colors.

Shopping For A Tektronix

Q. T.J., didn't you once highly recommend some retired guy who refurbishes and sells Tektronix oscilloscopes? I've looked through all my back issues, and I cannot find it! Would you please tell me where to find him? It's about time I bought a decent scope, and the Model 454 looks pretty good: 150 MHz, dual trace, delayed sweep and, of course, Tektronix!

**E. Nicholas Cupery
Senior Consultant
Farba Research**

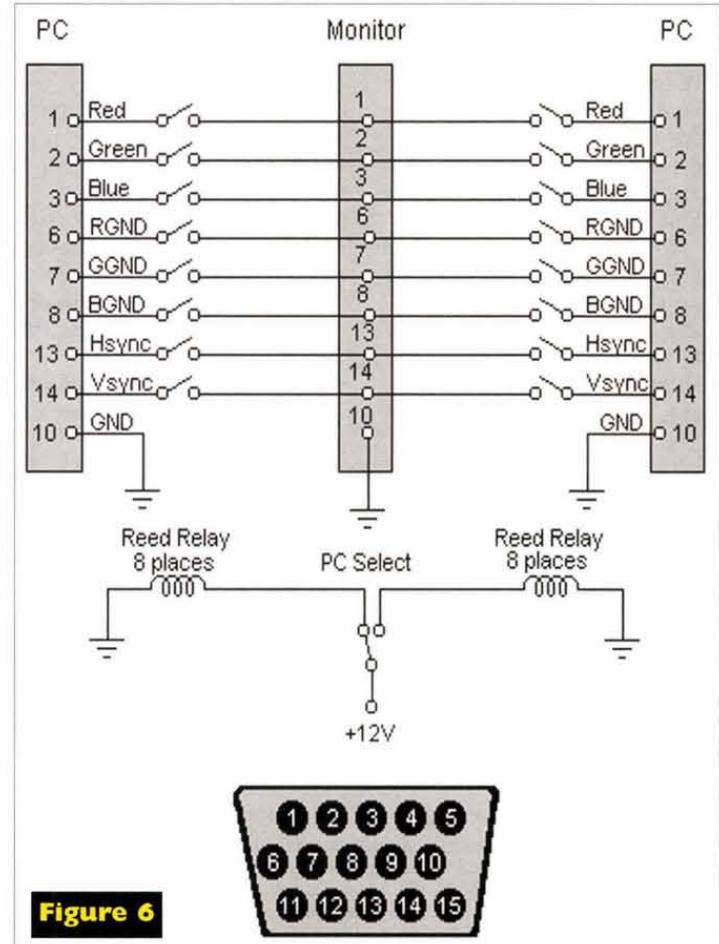


Figure 6

Electronics Q&A

Cool Web Sites

Wonder what Supreme Court Justices do with their time? **True tongue-in-cheek rulings.**

<http://forbes.com/fyi/2002/0513/088.html>

Nodal Analysis of Op Amp Circuits — very serious stuff; not for the faint of heart.

<http://a330.g.akamai.net/7/330/2540/5d687a213018af/www.e-insite.net/contents/pdf/A320orga.pdf>

How do ADCs work? — slightly lighter than above nodal analysis.
www.e-insite.net/index.asp?layout=article&articleID=CA224083&title=Search+Results&publication=e%2Dinsite&webzine=e%2Dinsite&verticalID=156

Stealing USB-Port Power. How to power your next project from the USB port. The file is also posted on our web site under USB_Power.pdf.

<http://a330.g.akamai.net/7/330/2540/41b8e6582fdc9a/www.e-insite.net/ednmag/contents/images/220400.pdf>

A. I haven't heard from this guy in a while, so I don't know what the story is. However, I was able to track down a handful of sources that sell this gem of a scope for a reasonable price. This list will be added to the PartFind file located on our web site (<ftp://nutsvolts.com/partfind.txt>).

Tech-Systems Electronics, Inc.
<http://shop.store.yahoo.com/techsystems>

Valley Computer Technologies
<http://home.earthlink.net/~vct/vc-tsale.htm>

Tektronix Oscilloscopes & Other Stuff!

<http://www.aactrinity.com/tektroni.htm> — fixer-uppers, too

Gootee

www.fullnet.com/u/tomg/tek.htm

Toronto Surplus & Scientific Inc.

www.torontosurplus.com/test/scope.htm

MAILBAG

Dear TJ:

In the July issue, you responded to a reader named Hank (WD5JFR) who was looking for a 32.768 kHz ultrasonic microphone. You might want to inform him that a pair of transmitting and receiving transducers for 32.8 kHz can be purchased from

Marlin P. Jones & Assoc., Inc. (www.mpja.com), for \$5.49 per pair. The part number is 12940-UT, described on page 66 of their newest catalog #02-06.

Jerry L. Wilson, AC5ZJ
via Internet

Dear TJ:

I have spent many an hour perusing the sources that you find and publish. However, the July column could use some clarification. In Figure 4, there is a symbol for an electret microphone that seems to be unique. I thought that a microphone would be symbolized differently. The schematic includes the necessary polarity and source load resistor. Then, in Figure 6, the same symbol is used to represent a raw piezo disc, also with polarity markings. Does this part indeed have polarity markings?

Phillip Milks
via Internet

Yes, all electret and most piezo devices are polarized.


TJ Byers
Q & A Editor

Check out the NV Bookstore on page 88. Our new expanded listing has something for just about everyone. If you don't find what you need here, check our website at www.nutsvolts.com

Secrets of RF Circuit Design

by Joseph J. Carr

\$39.95

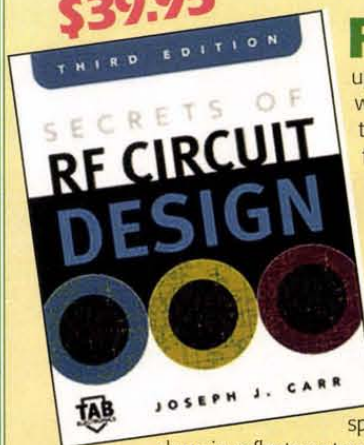

Following up on the best-selling previous editions, this revised and updated guide gives you the best ways to design, build, and test today's radio frequency circuits. It's filled with functional projects and experiments that make it easy to apply RF principles to real-life applications. Joe Carr provides parts lists and component sources for every project, in chapters that cover how to: Design and build radio receiver circuits, RF bridges, amplifiers, receiver preselectors, simplified spectrum analyzers, and time

domain reflectometers; Select, use, maintain, and repair variable capacitors; Design and wind inductor coils for radio circuits; Construct and ground simple wire antennas.

This book takes you inside wireless technology with step-by-step, illustrated directions for dozens of usable projects.

PERFECT FOR TECHNICANS, RADIO HOBBYISTS, AND ANYONE WHO WANTS TO PUT RF THEORY INTO PRACTICE

*Ideal for learning radio frequency circuitry

*Detailed coverage of simple RF instruments, as well as UHF and microwave components

*Complete troubleshooting guidance, too! Update of the favorite RF circuit guide of thousands of electronics enthusiasts!

Order today from the **Nuts & Volts Bookstore**


Call **1-800-783-4624** or order online at

www.nutsvolts.com

Practical Radio Communications

Volumes 1 & 2

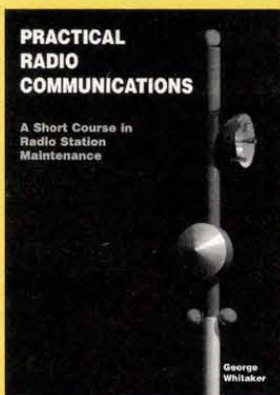This is a short course for beginners that teaches you how to work on broadcast equipment.



Most books assume you are going to design the equipment and use theory at the molecular level. This course keeps theory to an absolute minimum. We don't want to design it, we just want to know how to fix it.

Starting with things as simple as "How to wire a mike plug," information is given in a logical, small dose learning pattern. Each section provides a building block for eventually getting an understanding of FM stereo and AM directional arrays.

George Whitaker, the author, says, "When I was growing up in this business, every book I could find was nothing but mathematical formulas for designing equipment, with a little bit of practical information buried in them. I decided to turn it around and write a book with a lot of practical information and a little bit of math behind it. I never saw the need for me to know how to design a diode, I just wanted to know how to check to see if it was good or bad. I couldn't find anything that would teach me troubleshooting procedure for a transmitter control ladder; that was what I needed to know. What I wanted was a book that said 'If you have these symptoms, first you ...' After 40+ years in the business, I wrote one."

\$45.00 each Volume or Both Volumes for \$80.00!!

Order through the Nuts & Volts Book Store today!

Call our order only line at **1-800-783-4624**

or check out the On-Line Book Store at

www.nutsvolts.com

TEAM DELTA

BOTBASH

2002

Team Delta BotBash 2002 ROBOTIC COMBAT TOURNAMENT

September 14th and 15th
Tempe, Arizona

- ALL New Arena and Format
- 12, 30, 60, 120 lb. Classes
- Non-stop Competitions
- Live Music
- Special SOZBOTS 1 lb. Competition

WWW.BOTBASH.COM

Nuts & Volts
is an official sponsor
of BotBash

Tickets Available at
TICKETWEB
www.ticketweb.com

We accept Visa,
Mastercard, AmEx,
and Discover

Attention: TECHIESTUDS
To Order Call 1-800-227-3971

Fax: 318-424-9771

www.shrevesystems.com

MONITOR BLOWOUT!



H.P. 17" fixed res
832 X 724
ONLY....\$79
H.P. 17" fixed res
640 X 480
ONLY....\$79
14" VGA refurb ONLY....\$49

Using the force,
I will make you
spend much
MONEY...

UN F@#\$-ing BELIEVABLE!

16" Rasterops fixed
832 X 624
ONLY....\$69

15" 640x870
Raster Full Page
Display
Refurbished Macs
ONLY....\$19



14" Voxon VGA NEW
ONLY....\$59!!!
15" Voxon VGA NEW
ONLY....\$79



NTSC compatible!

\$49 Apple Color
Composite Display
Great for
Surveillance
Refurbished

\$5 and LESS SALE!!!

minimum of \$25, so start shoppin' cheap ass!



ONLY \$2

PDA Genuine Leather
Carry Case

Let your palm pilot
lead the life of luxury!

Peltier Junction Blowout!



with heat sink
1 3/16" x 1 3/16"

2 for \$5

(\$2.50 each for the slower nerds out there)

Apple II 256K
Memory
Expansion Kit
HM51256P-10
only 25 cents!

Paper Shredders
On Sale!
Protect your Privacy!
ONLY \$2
without AC Adapter

Global Village
Bronze
External
Modem
2400
Bps/9600
Fax
ONLY 25 cents!

PAS16 Audio
Spectrum
For Mac LC Family16
Bit Sound Editing Card



\$5

RAM
1 MB 30 Pin
4 MB 72 Pin
4 For \$1
2 For \$5

Be sure to check us out on the web at <http://www.shrevesystems.com> for the best prices on Vintage Mac gear!

Huge inventory! Huge savings!
\$25 minimum order.

Shreve Systems
1200 Marshall st
Shreveport, La 71101

Prices reflect a 2% cash discount and are subject to change without notice. Returns are subject to a 15% restocking fee. Not responsible for typographical errors.

Stamp Applications

Digital Data Recording

Our project this month is a simple event recorder that will monitor up to eight inputs and record changes in the state of these inputs to an external EEPROM. We'll use a real-time clock for accurate timing and our design will scan the inputs every second.

My first job after military service was working for a large turf irrigation company. With a background in electronics, my focus was, of course, directed at irrigation controllers [sprinkler timers]. I got pretty good at fixing them and was quickly promoted to the testing group where I got to work with new designs. Working with new ones was much more fun than fixing the broken ones.

Keep in mind that a sprinkler controller is a real-time device designed to sequentially activate selected stations [outputs] at some predetermined time. In our lab, the standard piece of equipment used to verify this behavior was a paper strip chart recorder (this was 18 years ago). We'd program the controller to run a test sequence and start the strip-chart

recorder, noting the time that the test was started. In the morning, we would verify the controller activity by reading the strip-chart markings.

Why am I dredging up what is — electronically — ancient history? Well, a recent posting on the BASIC Stamp mailing list caused me to remember my time in the test lab. A Stamp user was looking to build an event recorder using the BASIC Stamp. The post made me think about the good old days of paper strip-charts and the PC system we ultimately designed to replace them. I wondered what I could [simply] do with a stock BS2. As it turned out, the project is pretty neat.

Just Save The Changes


A big problem with the old strip chart-recorders is that they used paper to record activity and

would happily spit out loads of paper — even if nothing was happening. If we equate paper to memory, this is really just a waste. A more efficient plan is simply to note the time when something changes.

And that's what we'll do here. Our project this month is a simple event recorder that will monitor up to eight inputs and record changes in the state of these inputs to an external EEPROM. We'll use a real-time clock for accurate timing and our design will scan the inputs every second.


Inside The "Box"

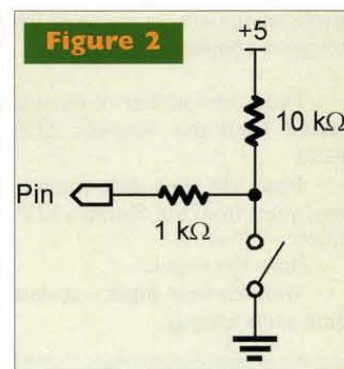I envisioned this project as something that would be used remotely — a smart "black box." This being the case, the interface



to the user is provided via the PC through the Stamp programming port. The heart of the circuit (Figure 1) is simply the Stamp and a couple of eight-pin dip components (the EEPROM and RTC). The circuit and battery can be easily packaged in a very small plastic or metal box.

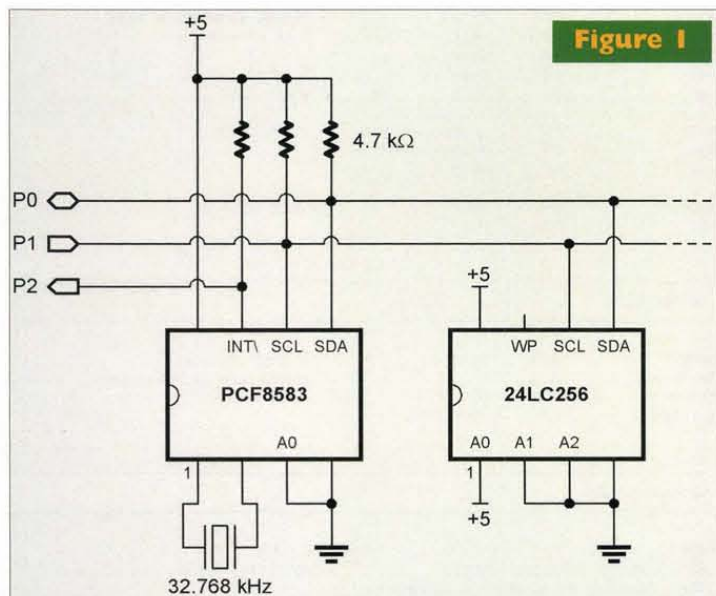I will leave input conditioning up to you. For my test, I used a simple N.O. switch circuit as shown in Figure 2. If you want to monitor high-voltage devices or AC, the switch could be replaced by the contacts of a relay. Or,



Stamp Applications

even better, you could use an optical isolator.

The hardware's pretty simple, isn't it? Well, the code really is too, albeit fairly long. As presented, the program uses up almost all of the Stamp's code space. Most of the program is fairly modular and we'll be taking advantage of some of the I2C code developed a couple of months ago — this time we'll put it to real use.

Before we get into the detailed explanation, let's review what the program should do:

- Read the number of records stored from the Stamp's EEPROM.
- Read the start date (month, day, year) from the Stamp's EEPROM.
- Draw the menu.
- Wait for user input —update time while waiting.

- Respond to the user input.

Response from the user can be:

- "T" : Enter new time (hours, minutes, seconds)
- "D" : Enter new start date (month, day, year)
- "R" : Start recording
- "V" : View stored records
- "C" : Clear records

The last part of our planning is the storage of an event. As discussed earlier, we will only store changes that are detected. Here's how the bytes in an event record are structured:

- 0 : Day (offset from start date)
- 1 : Hour
- 2 : Minutes
- 3 : Seconds
- 4 : Inputs

Let me just explain byte 0 a bit further. Instead of storing the event date in a record (which would take four bytes), we simply store an offset (number of days) from the start date of recording. This trims three bytes from the record, allowing more records to be stored. It also means that we don't have to send the date to or retrieve it from the PCF8583; the start date is simply recorded in the Stamp's memory for future reference. Let's get on with the code.

In the variables section, you'll notice a comment about not changing the order of a group of variables. In this program, we will take advantage of the Stamp's implicit array structure of variable memory. A group of variables of the same size can be accessed as an array by using the first of the

group as the array name and applying an index. Here's the group I'm referring to:

dayOfs
hours
minutes
seconds
scan

In the code, we can access to the same group using these names:

dayOfs(0)
dayOfs(1) — same as hours
dayOfs(2) — same as minutes
dayOfs(3) — same as seconds

dayOfs(4) — same as scan

As you've certainly deduced by now, we'll use a loop counter to iterate through these variables.

Let's move on to the EEPROM section; another place with some-

```

File..... EventRecord.BS2
Purpose... Simple Event Recorder
Author.... Jon Williams
E-mail.... jwilliams@parallaxinc.com
Started... 26 JUN 2002
Updated... 28 JUN 2002

{$STAMP BS2}

-----
' Program Description
-----
' This program scans the upper eight inputs for changes and, when detected,
' records the new inputs with the day [offset] and time to an EEPROM
'
' Event Record Structure:
' 0 : days offset from start date
' 1 : hours
' 2 : minutes
' 3 : seconds
' 4 : input scan

' Revision History
'
' I/O Definitions
'
SDA          CON    0      ' I2C serial data line
SCL          CON    1      ' I2C serial clock line
IntPin       VAR    In2    ' interrupt input pin from RTC
NewInputs    VAR    InH    ' inputs on pins 8 - 15
TermIO       CON    16    ' Terminal IO

' Constants
'
PCF8583      CON    %10100000 ' device code for RTC
EE24LC256    CON    %10100010 ' device code for EEPROM

ACK          CON    0      ' acknowledge bit
NAK          CON    1      ' no ack bit

RecSize      CON    5      ' five bytes per event record
MemSize      CON    32768   ' assuming 1 24LC256
MaxRecs      CON    MemSize / RecSize

-----
' Variables
'
device       VAR    Byte    ' device to write/read
devAddr      VAR    Word    ' address in device
addrSize     VAR    Bit     ' (bytes in address) - 1
i2cReg       VAR    Byte    ' register address
i2cData      VAR    Byte    ' data to/from device
i2cWork      VAR    Byte    ' work byte for TX routine
i2cAck       VAR    Bit     ' ACK bit from device

records      VAR    Word    ' events stored
recNum       VAR    Word    ' counter for view display
oldInputs    VAR    Byte    ' last event input data

' do not change order of next five variables
' -- program uses implicit array structure of user memory

daysOfs     VAR    Byte    ' offset from start date
hours        VAR    Byte    ' time of event
mins         VAR    Byte
secs         VAR    Byte
scan         VAR    Byte    ' event data

month        VAR    recNum.LowByte ' start date
day          VAR    recNum.HighByte
year         VAR    Word

response     VAR    Word    ' user response
idx          VAR    Nib

' EEPROM Data
'
NumRecs      DATA    Word 0      ' stored records
StartMonth   DATA    6          ' start date of recording
StartDay     DATA    28
StartYear    DATA    Word 2002

' Initialization
'
Init:
  READ NumRecs, records.LowByte ' retrieve record count
  READ (NumRecs + 1), records.HighByte

```

Listing 1

```

ByteSize    CON    0      ' byte-sized address (RTC)
WordSize     CON    1      ' word-sized address (EEPROM)

Yes          CON    0
No           CON    1

TermBaud     CON    84     ' 9600-8-N-1 (matches DEBUG)
CrsrXY       CON    2      ' DEBUG Position Control
ClrRt        CON    11     ' clear line to right

' -----
' Variables
' -----
device       VAR    Byte    ' device to write/read
devAddr      VAR    Word    ' address in device
addrSize     VAR    Bit     ' (bytes in address) - 1
i2cReg       VAR    Byte    ' register address
i2cData      VAR    Byte    ' data to/from device
i2cWork      VAR    Byte    ' work byte for TX routine
i2cAck       VAR    Bit     ' ACK bit from device

records      VAR    Word    ' events stored
recNum       VAR    Word    ' counter for view display
oldInputs    VAR    Byte    ' last event input data

' do not change order of next five variables
' -- program uses implicit array structure of user memory

daysOfs     VAR    Byte    ' offset from start date
hours        VAR    Byte    ' time of event
mins         VAR    Byte
secs         VAR    Byte
scan         VAR    Byte    ' event data

month        VAR    recNum.LowByte ' start date
day          VAR    recNum.HighByte
year         VAR    Word

response     VAR    Word    ' user response
idx          VAR    Nib

' -----
' EEPROM Data
' -----
NumRecs      DATA    Word 0      ' stored records
StartMonth   DATA    6          ' start date of recording
StartDay     DATA    28
StartYear    DATA    Word 2002

' -----
' Initialization
' -----
Init:
  READ NumRecs, records.LowByte ' retrieve record count
  READ (NumRecs + 1), records.HighByte

```


Stamp Applications

thing a little different. Storing data in the Stamp's EEPROM is easy and we do it quite frequently. I want to point out a little-used modifier of the **DATA** statement: Word. This lets us store a word-sized variable as easily as putting it into a variable. The compiler will store the variable as two bytes, using the "Little Endian" approach (low byte first). Keep in mind that this modifier only works with **DATA** and not with **WRITE** or **READ**. For **WRITE** and **READ**, we still must deal with bytes.

The initialization section is straightforward, simply reading the number of records stored and the start date from the Stamp's EEPROM. A short **PAUSE** is inserted to allow the **DEBUG** window to open before we get to draw the menu.

Drawing the menu is easy and since we're using the **DEBUG**

window, we'll take advantage of the cursor positioning command and later, the ability to clear a line from the cursor position to the right. These commands only work with the **DEBUG** window, so if you decide to change the program to work with a standard terminal, you'll need to write your own positioning and "clean up" code.

After the menu is displayed, we grab the current time from the PCF8583 — so let's go there. Jump down the routine called **Get_Clock**. This routine uses the low-level I2C code to access the seconds, minutes, and hours data from the PCF8583. When retrieving consecutive bytes from the PCF8583 (and other memory-type devices), we must first set the starting address with a write command. Once the address is set, we can perform sequential

reads from that address. The PCF8583 will automatically increment its address pointer so we can do subsequent reads without having to send the next address.

Since the PCF8583 uses BCD for the time registers, we will convert to decimal with a bit of code that takes advantage of the **HighNib** and **LowNib** variable modifiers. This really isn't necessary for the program, but as most of us are more comfortable dealing with decimal numbers, it make sense to do it.

With the time in hand, we'll put it in the display along with the current start date and wait for the user to press a key. If no key is pressed within 900 milliseconds, the **SERIN** line times out and goes back to the **Show_Time_Date** code. What this does is create a "live" display, showing us the current time in the

Resources:

Jon Williams
jwilliams@parallaxinc.com
.....
Parallax
www.parallaxinc.com

PCF8583.

When a key is pressed, it is decoded with a **LOOKDOWN** table. This will convert the response from a character to a value between zero and nine — if the key is valid. If the key isn't valid, the **LOOKDOWN** table will have no effect. Next, we divide by two, giving us a possible [legal] value between zero and four that will be used by **BRANCH** for our menu routines. If the key was legal, **BRANCH** will work. If not, the **BRANCH** statement will fall through and the code will restart at Main.

```

READ StartMonth, month          ' retrieve start date
READ StartDay, day
READ StartYear, year.LowByte
READ (StartYear + 1), year.HighByte

PAUSE 250                        ' let DEBUG window open

' -----
' Program Code
' -----

Main:
  DEBUG CLS                      ' display menu
  DEBUG "===== ", CR
  DEBUG " BASIC Stamp Event Recorder ", CR
  DEBUG "===== ", CR

  DEBUG CrsrXY, 0, 6

  DEBUG "[T] Set Current Time", CR
  DEBUG "[D] Set Start Date", CR
  DEBUG "[R] Start Recording", CR
  DEBUG "[V] View (", DEC records, ") Records", CR
  DEBUG "[C] Clear Records", CR

  DEBUG CrsrXY, 0, 12, "--> ", ClrRt

Show_Time_Date:                  ' show current time & date
  GOSUB Get_Clock
  DEBUG CrsrXY, 4, 4
  GOSUB Display_Time
  DEBUG " "
  GOSUB Display_Date

Get_User_Input:                  ' wait for response
  DEBUG CrsrXY, 4, 12
  SERIN TermIO, TermBaud, 900, Show_Time_Date, [response]
  LOOKDOWN response, ["tTdRvVc"], response
  response = response / 2
  BRANCH response, [Set_Time, Set_Date, Go_Record, View_Recs, Clear_Recs]
  GOTO Main

' -----
' Menu Routines
' -----

' --- Time ---

Set_Time:
  DEBUG CLS, "Set Current Time"

Enter_Hours:
  DEBUG CrsrXY, 0, 2, "Enter Hours (0..23).... ", ClrRt
  SERIN TermIO, TermBaud, [DEC2 hours]
  IF (hours > 23) THEN Enter_Hours

Enter_Minutes:
  DEBUG CrsrXY, 0, 3, "Enter Minutes (0..59)... ", ClrRt
  SERIN TermIO, TermBaud, [DEC2 mins]
  IF (mins > 59) THEN Enter_Minutes

Enter_Seconds:
  DEBUG CrsrXY, 0, 4, "Enter Seconds (0..59)... ", ClrRt
  SERIN TermIO, TermBaud, [DEC2 secs]
  IF (secs > 59) THEN Enter_Seconds

GOSUB Put_Clock                  ' send new time to PCF8583
GOTO Main

' --- Date ---

Set_Date:
  DEBUG CLS, "Set Start Date"

Enter_Month:
  DEBUG CrsrXY, 0, 2, "Enter Month (1..12)... ", ClrRt
  SERIN TermIO, TermBaud, [DEC2 month]
  IF (month < 1) OR (month > 12) THEN Enter_Month

Enter_Day:
  DEBUG CrsrXY, 0, 3, "Enter Day (1..31).... ", ClrRt
  SERIN TermIO, TermBaud, [DEC2 day]
  IF (day < 1) OR (day > 31) THEN Enter_Day

Enter_Year:
  DEBUG CrsrXY, 0, 4, "Enter Year (2002+).... ", ClrRt
  SERIN TermIO, TermBaud, [DEC4 year]
  IF (year < 2002) THEN Enter_Year

WRITE StartMonth, month          ' save start date in EEPROM
WRITE StartDay, day
WRITE StartYear, year.LowByte
WRITE (StartYear + 1), year.HighByte
GOTO Main

' --- Record ---

Go_Record:
  DEBUG CLS, "Recording... ", CR, CR

  daysOfs = 0                    ' start today
  oldInputs = ~NewInputs         ' force record on start

Wait_For_Int:
  IF (IntPin = No) THEN Wait_For_Int ' wait for new second
  GOSUB Get_Clock                 ' get current time
  IF (hours <> 0) OR (secs <> 0) THEN Check_Inputs
  daysOfs = daysOfs + 1          ' increment day counter
  IF (daysOfs = 0) THEN Stop_Recording ' if > 255 stop

Check_Inputs:
  scan = %11111111
  FOR idx = 1 TO 5                ' debounce inputs
    scan = scan & NewInputs
  PAUSE 5
  NEXT

```


Stamp Applications

The next section deals with code to handle each of the menu commands. The first two routines are identical, so we'll just discuss the first: Set_Time.

When we want to enter a new time, the screen is cleared and we're asked to enter the hours. To keep things simple (for the Stamp), we'll use the 24-hour format. The DEC2 modifier is used with **SERIN** to limit the number of characters accepted. If the value entered is out of range, we clear the entry and try again. The same technique is used to get the minutes and seconds.

Once a valid time has been entered, it is sent to the PCF8583 with the Put_Clock subroutine. This routine works very much like Get_Clock; just going the other direction (data to PCF8583).

The heart of the program is, of course, recording data. When

this option is selected, we'll clear the days offset counter, then collect the current inputs and invert them. The reason for this is that we want to force the recording code to create an entry at the beginning. This way we have stored the starting time and initial state of the inputs.

Let me get away from code for a bit and tell you about the Interrupt\ output of the PCF8583. This output is used to indicate alarms from the device (by being pulled low). By default, it outputs a 1-Hz squarewave. This is perfect for us to trigger our new scan cycle. Each time this output goes low, we know it's a new second. Monitoring the Interrupt\ line is more efficient than continuously reading the time and looking for a change.

The code will loop at Wait_For_Int until Stamp pin 2 is

pulled low. When this happens, we grab the current time from the PCF8583. At first, this may not seem necessary if there was no new event. We have to do it though since we're keeping track of the days ourselves. So, if the current hours is zero (midnight) and the current seconds value is also zero, we've just hit a new day and we increment the daysOfs variable. If not, we simply skip ahead and look at the inputs.

Since inputs can be "noisy," the code at Check_Inputs will debounce them. We've used this code before; it simply loops a few times and makes sure that an input doesn't change (bounce) during the loop. Any non-changing input is passed through the loop as a good input.

If there has been a change in the inputs, we'll save the change and record the event to our

24LC256 with the Put_Record subroutine. Let's go there.

The Put_Record subroutine updates the record count and checks to make sure we still have room in the 24LC256 for data. If not, the program stops, otherwise we'll save the current scan time and inputs. The current record number is stored in the Stamp's EEPROM so we can retrieve it after a power loss or reset. The next step is to set up for the Put_Byte subroutine by selecting our device type and the address size.

The Put_Byte routine is a general-purpose update from older code that lets us use it for either the 24LC256 or the PCF8583 (if we want to set something other than the time). The update includes passing the device as a variable and a flag for the number of bytes in the internal address.

Listing 2

```
IF (scan = oldInputs) THEN Wait_For_No_Int
oldInputs = scan
GOSUB Put_Record

DEBUG DEC3 daysOfs, " "
GOSUB Display_Time
DEBUG " -> ", BIN8 scan, CR

Wait_For_No_Int:
IF (IntPin = Yes) THEN Wait_For_No_Int
GOTO Wait_For_Int

' --- View ---

View_Recs:
IF (records = 0) THEN Main
DEBUG CLS
DEBUG "Records", CR
DEBUG "Start Date: "
GOSUB Display_Date
DEBUG CR, CR

DEBUG "Day Time Inputs ", CR
DEBUG "----", CR

FOR recNum = 0 TO (records - 1)
GOSUB Get_Record
DEBUG DEC3 daysOfs, " "
GOSUB Display_Time
DEBUG " ", BIN8 scan, CR
NEXT

DEBUG CR, "Press a key..."
SERIN TermIO, TermBaud, [response]
GOTO Main

' --- Clear ---

Clear_Recs:
records = 0
WRITE NumRecs, 0
WRITE (NumRecs + 1), 0
GOTO Main

' -----
' Subroutines
' -----

Display_Time:
DEBUG DEC2 hours, ":", DEC2 mins, ":", DEC2 secs
RETURN

Display_Date:
DEBUG DEC2 month, "/", DEC2 day, "/", DEC4 year
RETURN
```

```
Put_Record:
records = records + 1
IF (records > MaxRecs) THEN Stop_Recording
WRITE NumRecs, records.LowByte
EEPROM
WRITE (NumRecs + 1), records.HighByte

device = EE24LC256
addrSize = WordSize

FOR idx = 0 TO (RecSize - 1)
i2cData = daysOfs(idx)
devAddr = ((records - 1) * RecSize) + idx
GOSUB Write_Byte
NEXT
RETURN

Get_Record:
device = EE24LC256
addrSize = WordSize

FOR idx = 0 TO (RecSize - 1)
devAddr = (recNum * RecSize) + idx
GOSUB Read_Byte
daysOfs(idx) = i2cData
NEXT
RETURN

Stop_Recording:
END

' -----
' High Level I2C Subroutines
' -----

' Byte to be written is passed in i2cData
' -- address passed in devAddr

Write_Byte:
GOSUB I2C_Start
i2cWork = (device & %111111110)
GOSUB I2C_TX_Byte
IF (i2cAck = NAK) THEN Write_Byte
IF (addrSize = ByteSize) THEN Wr_Low_Addr
i2cWork = devAddr / 256
GOSUB I2C_TX_Byte

Wr_Low_Addr:
i2cWork = devAddr // 256
GOSUB I2C_TX_Byte
i2cWork = i2cData
GOSUB I2C_TX_Byte
GOSUB I2C_Stop
RETURN

' Byte read is returned in i2cData
' -- address passed in devAddr
```


Stamp Applications

```

Read Byte:
GOSUB I2C_Start
i2cWork = (device & %11111110)
GOSUB I2C_TX_Byte
IF (i2cAck = NAK) THEN Read_Byte
IF (addrSize = ByteSize) THEN Rd_Low_Addr
i2cWork = devAddr / 256
GOSUB I2C_TX_Byte

Rd_Low_Addr:
i2cWork = devAddr // 256
GOSUB I2C_TX_Byte
GOSUB I2C_Start
i2cWork = (device | 1)
GOSUB I2C_TX_Byte
GOSUB I2C_RX_Byte_Nak
GOSUB I2C_Stop
i2cData = i2cWork
RETURN

```

```

' Write seconds, minutes and hours .. sequential mode
' -- variables are converted to BCD before sending to PCF8583

```

```

Put Clock:
GOSUB I2C_Start
i2cWork = PCF8583
GOSUB I2C_TX_Byte
i2cWork = 2
GOSUB I2C_TX_Byte
i2cWork = ((secs / 10) << 4) | (secs // 10)
GOSUB I2C_TX_Byte
i2cWork = ((mins / 10) << 4) | (mins // 10)
GOSUB I2C_TX_Byte
i2cWork = ((hours / 10) << 4) | (hours // 10)
GOSUB I2C_TX_Byte
GOSUB I2C_Stop
RETURN

```

```

' Read seconds, minutes and hours .. sequential mode
' -- variables are converted from BCD storage format

```

```

Get Clock:
GOSUB I2C_Start
i2cWork = PCF8583
GOSUB I2C_TX_Byte
i2cWork = 2
GOSUB I2C_TX_Byte
GOSUB I2C_Start
i2cWork = (PCF8583 | 1)
GOSUB I2C_TX_Byte
GOSUB I2C_RX_Byte
secs = i2cWork.HighNib * 10 + i2cWork.LowNib
GOSUB I2C_RX_Byte
mins = i2cWork.HighNib * 10 + i2cWork.LowNib
GOSUB I2C_RX_Byte_Nak
hours = i2cWork.HighNib * 10 + i2cWork.LowNib
GOSUB I2C_Stop
RETURN

```

```

' -----
' Low Level I2C Subroutines
' -----

```

```

' --- Start ---

```

```

I2C_Start:
INPUT SDA
INPUT SCL
LOW SDA

```

```

Clock_Hold:
IF (Ins.LowBit(SCL) = 0) THEN Clock_Hold
RETURN

```

```

' --- Transmit ---

```

```

I2C_TX_Byte:
SHIFTOUT SDA,SCL,MSBFIRST,[i2cWork\8]
SHIFTIN SDA,SCL,MSBPRE,[i2cAck\1]
RETURN

```

```

' --- Receive ---

```

```

I2C_RX_Byte_Nak:
i2cAck = NAK
GOTO I2C_RX

```

```

I2C_RX_Byte:
i2cAck = ACK

```

```

I2C_RX:

```

```

SHIFTIN SDA,SCL,MSBPRE,[i2cWork\8]
SHIFTOUT SDA,SCL,LSBFIRST,[i2cAck\1]
RETURN

' get byte from device
' send ack or nak

' --- Stop ---

I2C_Stop:
LOW SDA
INPUT SCL
INPUT SDA
high
RETURN

```

The device code is actually supposed to be the write code for the device, but the program masks out the lower bit (read bit), just in case of an error.

After getting an ACK from the device (it's ready), we'll check the address size. For the 24LC256, we'll send two bytes (high byte first); for the PCF8583, we would only send one byte. After that, it's a simple matter of sending the data byte and generating a stop.

This code, as well as Get_Byte, are good copy-and-paste code chunks for programs that use I2C devices.

Back to Put_Record. A loop is used to iterate through the bytes in our event record. Now we can fully understand the earlier discussion of keeping the event variables in specific order in our definition section. It's not enough that they're defined, they have to be defined consecutively so that this loop code will send the correct information to the 24LC256. The 24LC256 address for a given byte in the record is calculated and finally stored with Put_Byte.

With the record stored, we'll display the change on screen and then check to the state of "interrupt" pin. As I told you earlier, what we'll see on the input of pin 2 is a 1-Hz squarewave generated by the PCF8583. If the storage and display of our record takes less than 500 milliseconds (I measured it at about 290 milliseconds with a BS2), then pin 2 will still be low when we're done. What we don't want to do, then, is go back to Wait_For_Interrupt — because we'll just do things again unnecessarily. So, we'll just wait for this pin to go back high, then we'll jump to Wait_For_Interrupt.

To stop recording, we'll reset the Stamp or cycle the power. Back to the menu, we should see the correct number of stored records indicated. Pressing "V" will display them on screen. The code at View_Recs is responsible for the display. It uses a loop and Get_Record to retrieve the data

from the 24LC256.

Finally, we will want to clear our records for a new cycle. This is a simple matter of clearing the variable and writing zeros to the EEPROM locations that hold our record count. There's no need to actually erase the 24LC256 — this would simply be a waste of its available write cycles.

Improvements

What you'll notice is that there isn't a whole lot of code space left for improvements — mostly because of all the **DEBUG** statements used to create our interactive display. We're going to solve that next time by using an external control program with Visual Basic. Until then, Happy Stamping! **NV**

Future Horizons Advanced Technology

Ambient Power Module

Low cost circuit provides up to 9 watts of electrical power from free-energy in the air. Can replace batteries in many devices.

#PWRM Plans- \$24.00
#PWRZ Ready to use- \$140.00

Electronic Mind Control

Control minds with this simple technology. Others will do anything you program them to. Get that raise you always wanted or reprogram your mind.

#MIND Info/plans- \$22.00
#MINZ Ready to use- \$190.00

Cordless Phone Extender

Extend your cordless phone range to 50 miles. Place calls all around town. Great alternative to cell phones.

#CPHE Plans- \$23.00

Ion Phaser

Device emits an electrified stream of special conductive fluid carrying 30,000 volts capable of stunning an individual from 20 feet away. battery powered Handheld non-lethal device.

#IPHA Plans- \$49.00
#IPHZ Ready to use- \$990.00

Traffic Light Buster

Has been known to turn traffic lights green in many cities by the touch of a button. Emergency vehicles use it to pass through traffic lights quickly. Opens security gates in gated communities too.

#TLBU Plans- \$20.00
#TLBZ Ready to use- \$250.00

Please add \$6.00 Shipping/handling

Call for a FREE Catalog

Po Box 125 Marquette, Mi 49855
(906) 249-5197 www.futurehorizons.net


RF MODULES

Great selection of...


- Transmitters
- Receivers
- Transceivers
- Antenna
- RF subassemblies
- Radio Modems
- Evaluation Kits
- Amplifiers
- Data encoders
- Data decoders

Typical Applications

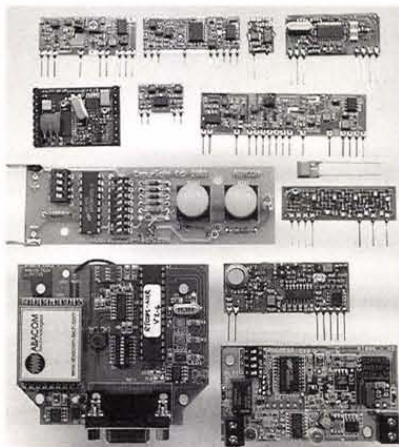- RF remote control
- Data communications
- Wireless Audio
- RF data acquisition
- Wireless Security
- Robotics
- Remote Sensing
- Remote Monitoring
- Wireless Networking



www.abacom-tech.com

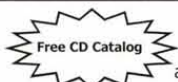

Tel: +1(416)236 3858
Fax: +1(416)236 8866
abacom@abacom-tech.com

Same Day Shipping—Visa, MasterCard, Amex, Diners Club cards welcome

SEARCH & BUY ONLINE
www.mouser.com

166,000+
ELECTRONIC
COMPONENTS

Semiconductors, Optos, LEDs, Lamps, Panel Meters, Wire, Cable, & Accessories, Connectors, Cable Assemblies, Sockets, Terminals, Resistors, Potentiometers, Thermistors, Varistors, Capacitors, Crystals, Oscillators, Resonators, Inductors, Transformers, Power Supplies, Switches, Relays, Circuit Breakers, Fuses, Batteries, Speakers, Audio Devices, Fans, Heat Sinks, Knobs, Hardware, Cabinets, Racks, Cases, Test Equipment, Tools, Prototyping . . .

MOUSER 
ELECTRONICS

New Product News

DIGITAL CLAMP METER MODEL ST1010

Elenco Electronics announces the introduction of a new Digital Clamp Meter that is rugged and ready to take on the tough jobs.

The new Model ST1010 has many new features and meets the rigid CE and CS standards, for safe use of current clamp meters.

The ST1010 is a 3-1/2 digit (2,000 count) LCD clamp instrument with the following features: AC current to 1,000 amp; AC voltage to 600 VAC; DC voltage to 1,000 DC; Resistance to 2M ohm; Frequency to 2KHz; Diode check; Continuity check (audible); and Data hold.

It comes in a soft zippered carrying case with a drop proof waist strap. Insulation testing is available (optional).

The ST1010 is an economical meter with a broad range of features and capabilities. The price is the lowest it has ever been and is affordable to every technician or student at \$49.95 each. It is available for immediate delivery.


For additional information, contact:

ELENCO ELECTRONICS, INC.,

150 W. Carpenter Ave., Dept. NV
Wheeling, IL 60090

847-541-3800 Fax: 847-520-0085

Web: www.elenco.com/press/st1010.pdf

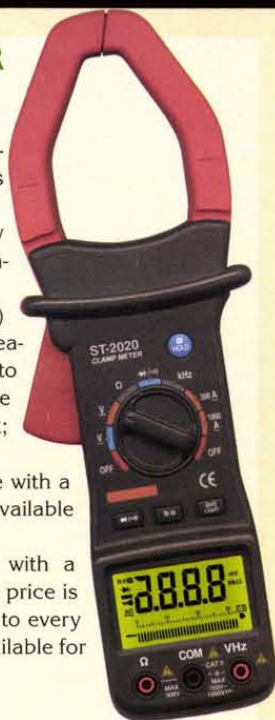

NEW TECHNICAL VIDEO TEACHES THE FUNDAMENTALS OF OSCILLOSCOPE OPERATION

SYSPEC announces a new technical video training tape designed to acquaint hobbyists and technicians with the fundamentals of using an oscilloscope.

The VHS videotape is designed to take the mystery out of using the instrument to make basic signal measurements. It assumes no prior oscilloscope knowledge and begins with a detailed presentation about scope controls, as well as interpreting displayed waveforms.

The training video provides details on how to set up the various controls for making voltage and period measurements for a wide range of signals including sine, square, and sawtooth waveforms. Duty-cycle and pulse-width measurements are also discussed. Practical examples of common measurements are provided, including how to measure the pulse width of a fuel injector.

The training video also includes a free oscilloscope technical training manual. The manual offers many examples of waveforms measurements and includes a number of exercises designed to increase the proficiency of the reader. A section on oscilloscope setup helps the



New Product News

user choose the proper time base, vertical sensitivity, and trigger mode based upon the type of signal being measured.

The videotape is introductory-priced at \$24.95 + \$5.00 shipping and handling (continental US).

For more information, contact:

SYSPEC, INC.


P.O. Box 2546, Dept. NV

Syracuse, NY 13220

1-877-SYSPEC I

Web: www.syspec.com

MBASIC VERSION 5.2

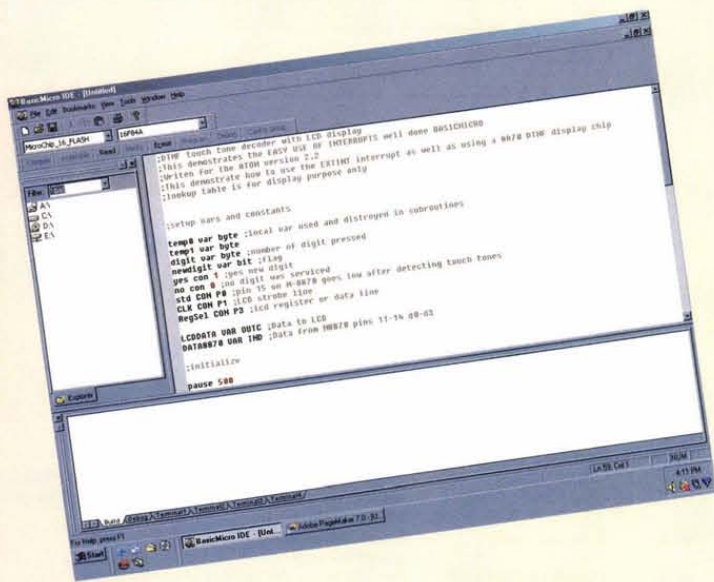

Basic Micro introduces the newest version of the MBasic Compiler. MBasic Version 5.2 offers: 32-Bit math; 32-Bit Floating Point; Dallas One Wire Support; If..Then..Else..Elseif..Endif; Hardware PWM; Expanded LCD command; Read and Write Memory with Basic command; Basic Interrupts; Hardware Timers; Hardware Serial UART Hserin/Hserout; In Circuit Debugger now has more features; New Oscilloscope Software built in; Free Boot Loader Builder Included; and Free Boot Loader Interface Included.

The ability to debug code in Basic without knowledge of Assembly makes this compiler one of the most versatile programming software packages available. With the added ability of being able to customize menu options, built-in task reporting, and multiple document support.

MBasic Pro Version has more commands such as LCD, I2C, POT, PEEK, POKE, SPI, DO, WHILE, SWAP, SERVO, SPMOTOR.

The compiler is ideal for the hobbyist, students, and professionals. With many applications you can control robotics, CNC, LCD, keypads, and more!

Starting at just \$99.95 for the MBasic Standard Compiler, with the ability to upgrade to MBasic Pro at any time.

For more information, contact:

BASIC MICRO, INC.

2882 Orchard Lake Road, Dept. NV
Farmington Hills, MI 48336

248-427-0040 Fax: **248-427-0051**

Email: info@basicmicro.com

Web: www.basicmicro.com

INEXPENSIVE 8052BASIC DEVELOPMENT SBC FOR HOBBYIST AND INDUSTRY

The 70691BASIC is designed to

allow hobbyists and engineers alike to create highly sophisticated computer programs using easy-to-understand BASIC-52 language.

Created by Intel, BASIC-52 is a high-level programming language that is stored as part of the internal Read Only Memory of the 80C52 microcontroller. By incorporating this "smart chip," the programming of the 70691BASIC is an easy matter.

BASIC-52 programs can be saved in either of two ways. Download programs in ASCII format from 70691BASIC memory for subsequent saving on a hard drive or floppy disk. Or you can save the program on the supplied 2864 EEPROM (using accompanying BASIC-52 Utility Program).

Interfacing and circuit expansion is also an easy matter for the 70691BASIC. Just like all of our SBCs; the '91BASIC contains a 40-pin header connector that picks up all major 80C52 terminals (ex. Port 1, Port 3, Hi-Order Address Line, etc.), thus allowing these points to be brought to your prototype board using an inexpensive ribbon cable (available from Digi-Key Corporation).

The best feature of the 70691BASIC is to allow fast, easy program development.

With your program working just the way you want, BASIC-52 can now be transformed into SUPER FAST .ASM code by converting it with the Binary Technologies BCX-51 Compiler. When converted, this new program can then be placed into the EPROM chip of our 70691RAM board. Both 70691RAM and the 70691BASIC are 100% compatible with compiled BASIC-52 programs.

For more information, contact:

HOME TECHNOLOGIES FLA 352-597-7337

Email: hometech@atlantic.net

Web: www.HomeTechFLA.com

Showcase your New Products here!

Send all press releases, photos, and information to:


Nuts & Volts

New Product News

430 Princland Court
Corona, CA 92879

or email to

newproducts@nutsvolts.com

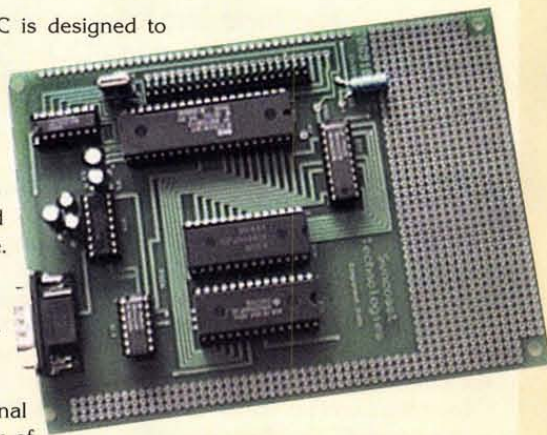

The ComPort Tester

By Jon J. Varteresian

You have just finished building that new Gizmo of yours, plugged it into the ComPort on your PC, and POOF! Smoke starts billowing from the Gizmo! If only there was a way to test that ComPort to make sure it was still fully operational ...



Introduction

Consider this ... You have just finished building that new Gizmo of yours, plugged it into the ComPort on your PC, and POOF! Smoke starts billowing from the Gizmo! You frantically unplug everything in a 20-foot radius, but then what? How do you know the ComPort on your PC has survived the 'incident?' If only there was a way to test that ComPort to make sure it was still fully operational ... But wait! There is!

Enter the ComPort Tester. The PC ComPort Tester will fully test all of your external PC ComPorts giving you detailed feedback and port status. Attach the loopback connector described here, and with just one mouse click, you can exercise your ComPort through all its supported baud rates, as well as all the flow control signals. You can also attach the loopback connector to the end of a cable and test the cable, as well! Test results are reported in a status window for immediate feedback. You can also print and save the test results. The loopback connector is easily built from spare parts hanging around your lab and the software is free! Before we get into the details of testing a ComPort, a brief review of the PC ComPort is in order.

The ComPort

Just what exactly is a communications port, or ComPort? Ever since the dawn of the personal computer, people have wanted their PC to interact with their surrounding environment. They wanted to control equipment, monitor various things, or even just play a game with somebody on another computer. Enter the ComPort, or serial communications port. The term serial communications is just a fancy way of describing how the data is actually transferred across the wires. All information inside a computer is made up of 'words' that contain 8, 16, or 32, or more bits. A bit is just a single piece of information. When these words are transferred across a serial port, they must be transferred one bit at a time since there is only one transmit wire. That is where the term serial comes from. Data transferred across the PC ComPort takes the form of eight-bit words.

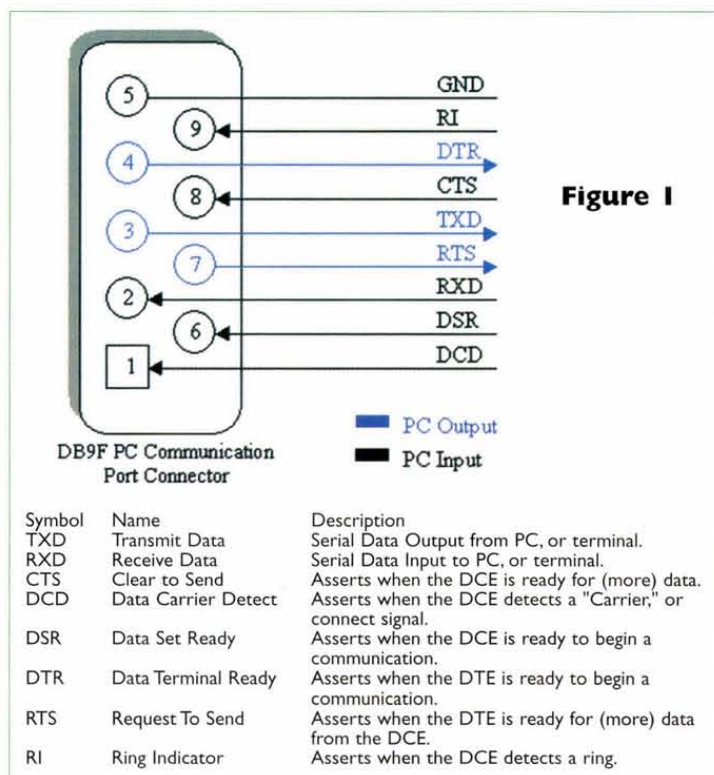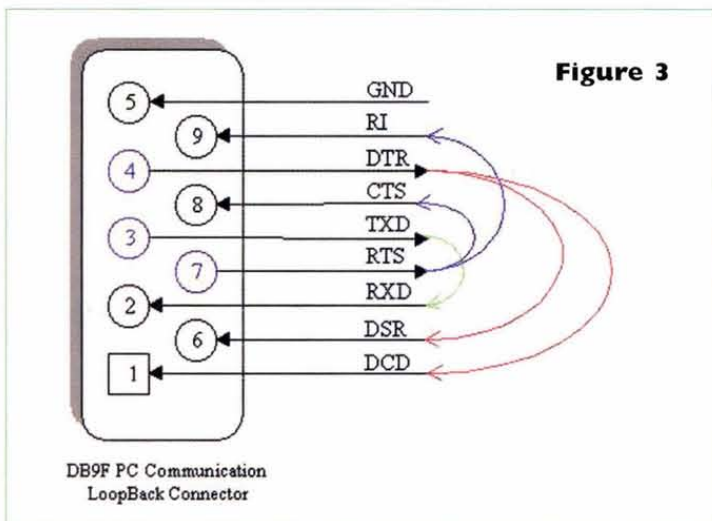

Hardware Properties

Devices that use ComPorts for their communications are split into two categories. They are DCE (Data Communications Equipment) and DTE (Data Terminal Equipment). Data Communications Equipment are devices such as your modem, plotter, etc., while Data Terminal Equipment are your computer or terminal. The job of the data terminal is to create and/or process all serial communications, and the job of the data communications equipment is to pass that data to and from the data terminal.

The electrical specifications of the ComPort are contained in the EIA (Electronics Industry Association) RS232-C standard. It states many parameters such as:

- A "Space" (logic 0) will be between +3 and +25 volts.
- A "Mark" (logic 1) will be between -3 and -25 volts.
- The region between +3 and -3 volts is undefined.
- An open circuit voltage should never exceed 25 volts. (In reference to GND.)
- A short circuit current should not exceed 500mA. The driver should be able to handle this without damage. (Take note of this one!)
- Maximum baud rate (bit transfer rate) of 20,000 bits per second.

The items listed above are just some of the more important specifications found in the EIA RS232-C standard. Most users never need to

The ComPort Tester

know more than this, but if you do, you have to go look it up.

ComPorts come in two "sizes:" The D-Type 25-pin connector and the D-Type nine-pin connector, both of which are male on the back of the PC (they have pins instead of sockets), thus you will require a female connector on your device. The D-type 25-pin connector is hard to find and slowly disappearing from today's PC. Mostly, you will see the D-type nine-pin connector. The pinout for this connector is shown in Figure 1. This is what you will see when you look directly at the ComPort connector on your PC. Most D-type nine-pin connectors have the pin numbers molded into the plastic of the connector itself. If you look closely, you should see them.

The Null Modem

A null modem (see Figure 2) is used to connect two DTEs or PCs together. This is commonly used as a cheap way to network games or to transfer files between computers using some protocol such as Zmodem or Xmodem.

The idea behind a null modem connection is to make a DTE or PC think it is talking to a modem or DCE, rather than another DTE, or PC. Any data transmitted from the first computer must be received by the second, thus TXD is connected to RXD. The second computer must have the same set-up, thus RXD is connected to TXD. Signal Ground (SG) must also be connected so both grounds are common to each computer.

The Data Terminal Ready is looped back to Data Set Ready and Carrier Detect on both computers. When the Data Terminal Ready is asserted active, then the Data Set Ready and Carrier Detect immediately become active. At this point, the computer thinks the virtual modem to which it is connected is ready and has detected the carrier signal.

All that is left to worry about now is the Request To Send and Clear To Send. As both PCs communicate at the same speed, flow control is not needed, thus these two lines are connected together on each computer. When the computer wishes to send data, it asserts the Request to Send high and as it's hooked together with the Clear to Send, it immediately gets a reply that it is okay to send and does so.

DTE/DCE Speeds

As stated before, a typical DTE is a computer and a typical DCE is a modem. Often people will talk about DTE-to-DCE and DCE-to-DCE speeds. DTE-to-DCE is the speed between your modem and computer, sometimes referred to as your terminal speed. This should run at the same or faster speed than the DCE-to-DCE speed. DCE-to-DCE is the link between modems, sometimes called the line speed. A DTE-to-DCE speed faster than DCE-to-DCE insures that all data that arrives at the DCE is processed by the DTE so no data is lost.


For a 28.8K or 33.6K modem, we should expect the DCE-to-DCE speed to be either 28.8K or 33.6K. Considering the high speed of the modem, we should expect the DTE-to-DCE speed to be about 115,200 BPS. (Maximum Speed of the 16550a UART.)

Modern modems should have data compression built into them. When set up correctly, you can expect compression ratios of 1:4 or even higher; 1:4 compression would be typical of a text file. If we were transferring that text file at 28.8K (DCE-DCE), then when the modem compresses it, you are actually transferring 115.2 KBPS between computers and thus have an effective DCE-DTE speed of 115.2 KBPS.

Some modem manufacturers quote a maximum compression ratio as 1:8. For example, a 33.6 KBPS modem may get a maximum of 268,800 BPS transfer between modem and PC.

Flow Control

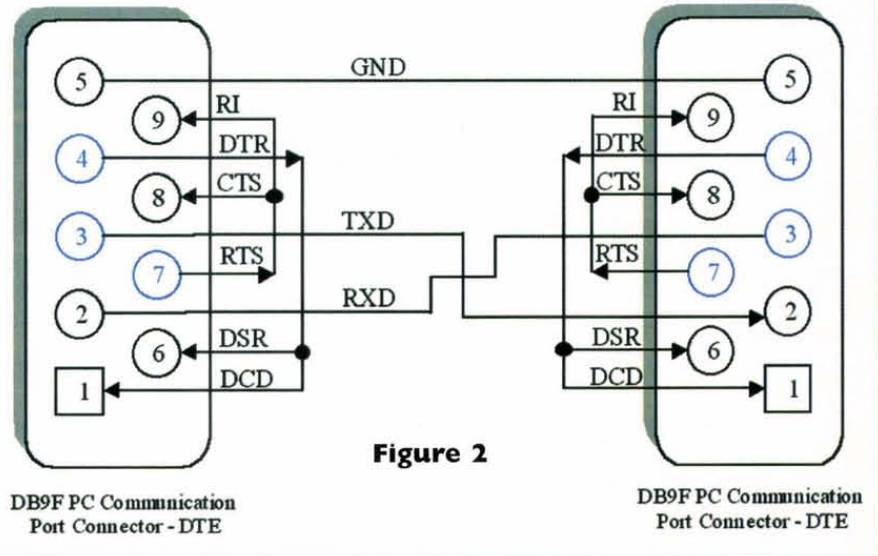
Eventually the data transfer rate between our DTE-to-DCE is going to



be faster than our DCE-to-DCE transfer rate. When this happens, data will probably get lost. You can't put jellybeans into a container faster than you are eating them. Sooner or later the jar will overflow making quite the mess, and probably getting you in trouble. In order to prevent this from happening, you have to have a way for the DCE to tell the DTE that it has too much data and it should stop sending it, and vice versa. Enter flow control.

Flow control comes in two flavors: hardware and software.

Software flow control, sometimes expressed as Xon/Xoff, uses two characters Xon and Xoff. The ASCII 17 character normally represents Xon, and the ASCII 19 character normally represents Xoff. In reality, a DCE will only have a small buffer (16 to 64 bytes is common), so when the DTE fills it up, the DCE sends an Xoff character to tell the DTE to stop sending data. Once the DCE has room for more data, it then sends an Xon character and the DTE sends more data. This type of flow control has the advantage that it doesn't require any more wires as the characters are sent via the TXD/RXD lines. However, it can substantially slow down communications on low baud rate links due to the extra traffic of the Xon/Xoff bytes. Flow control here is not automatic. The PC must monitor the incoming serial data from the DCE and adjust the output flow as needed. If the PC is momentarily busy and doesn't have time to mon-

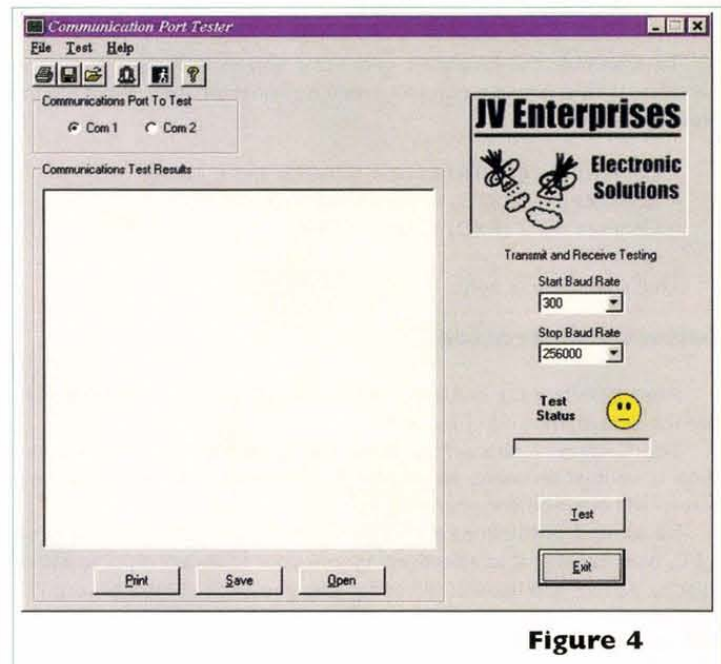

The ComPort Tester

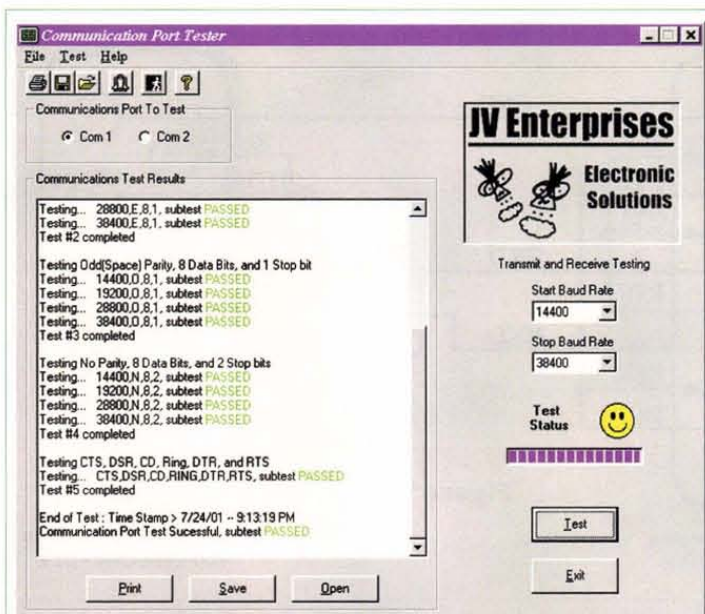


Figure 5

itor the incoming serial data from the DCE, it may send more data than the DCE can handle before shutting off the flow.

Hardware flow control is also known as RTS/CTS flow control. It uses two wires in your serial cable rather than extra characters transmitted in your data lines. Thus, hardware flow control will not slow down transfer times like Xon-Xoff does. Flow control here is usually performed directly at the hardware level, thus its effect is immediate. When the DTE wishes to send data, it asserts DTR and checks the state of CTS. If CTS is active, the DTE will send data, if it is not active, no data will be sent. When the DCE wishes to send data, it asserts DSR and checks the state of RTS. If RTS is active, the DTE is ready for data, if it is not active, no data will be sent. In this way, the DCE and DTE can control the flow of data thus insuring that their data queues do not overflow.

That's a pretty good overview of the ComPort and serial communications. There are many good books on this subject. Pick one up if you want more.

The Loopback Connector

To assemble the loopback connector shown in Figure 3, all you need is a D-type nine-pin connector and a connector shell. Make the following connections:

- Connect pin 4 (DTR) to pins 1 (DCD) and 6 (DSR)
- Connect pin 7 (RTS) to pins 8 (CTS) and 9 (RI)
- Connect pin 2 (RXD) to pin 3 (TXD)

That's all there is to it!

Software Operation

After installing the software and starting the program, you should see the screen shown in Figure 4.

The Communications Port tester has a full-featured help system. Help is context-sensitive, so just hit F1 wherever you are and a help screen will open before your very eyes.

Be warned, sometimes a corrupt ComPort can effectively hang up a PC, thus causing it to effectively ignore your futile attempts to abort. Just be patient and the test will end giving you back control of your PC.

The Main program screen consists of a Menu tree, a toolbar for commonly-accessed functions, a test results window, and some various

controls and buttons. Each section is described next.

Menu Tree

File->Open. Select this menu pick when you want to retrieve previously tested ComPort data. Information is stored in .RTF or Rich Text Format. Windows and most word processors easily display this format. Picking this menu item will present you with a Windows standard open screen allowing you to select the results file you want to open.

File->Save. Select this menu pick whenever you want to save the information shown in the test results window. Information is stored in .RTF. Windows and most word processors easily display this format. Picking this menu item will present you with a Windows standard save screen allowing you to change the preset file name and other great options.

File->Print. Select this menu pick whenever you want to print the information in the test results window. Note that after a test has completed, you can edit the information in the test results window in order to annotate them for other people's viewing pleasure. Picking this menu item will present you with a Windows standard print screen allowing you to choose the system printer and other great options. You can also select the print icon from the toolbar, or the print button in the test results window.

File->Exit. Select this menu pick whenever you want to exit this program.

Test->Test. Select this menu pick to begin testing the selected ComPort. When the test has begun, this menu item will automatically change to an Abort menu item. Selecting the abort will stop the current test. You can also select the test button on the main screen.

Test->Abort. Select this menu pick to abort the current test. When the test has been aborted, this menu pick will automatically change back to a test menu pick. You can also select the abort button on the main screen.

Test->Com1. Select this menu pick to choose Com1. A checkmark will appear next to the active ComPort in the menu list. The ComPort indicators on the main screen will also update, displaying the currently selected ComPort. You can also select the ComPort by clicking the menu buttons on the main screen.

Test->Com2. Select this menu pick to choose Com2. A checkmark will appear next to the active ComPort in the menu list. The ComPort indicators on the main screen will also update, displaying the currently selected ComPort. You can also select the ComPort by clicking the menu buttons on the main screen.

Help->About. Select this menu pick to get more information about this program such as build dates, versions, contact information, etc. You can also review all of your system resources from this screen.

Help->Help. Select this menu pick to get the help system.

The ComPort tester automatically tests the selected ComPort throughout its complete baud range. You can adjust the starting and stopping baud rates with the supplied pull downs. Just click the drop down arrow next to each box and choose the baud rate of your choice. If a baud rate is not supported, the ComPort tester will skip that particular baud. A sample test result is shown in Figure 5.

I have tested this software on every PC I could get my hands on including Windows 95, Windows 98, Windows NT, and Windows ME. I found that the flow control signals behaved slightly different on each system and the tests were adjusted accordingly.

Should you suspect any problems with the software, please contact me at jventerprises@att.net. **NV**

A CD with the program and an assembled loopback connector is available from **JV Enterprises**, P.O. Box 370, Hubbardston, MA 01452; or **www.jventerprises.com** for \$14.95 which includes the shipping. This covers the cost of the CD and loopback connector only. The software is free. You can download the software directly from **www.jventerprises.com**, just click on the 'downloads' section.

Electronics Showcase

Special products and services
for the electronics enthusiast.

MULTIMEDIA VIEWER

PLAYS JPEG, MPEG, & MP3 FILES
DIRECTLY TO YOUR TV OR MONITOR



- DISPLAYS JPEG PHOTOS
- UP TO 45 MINUTE FULL MOTION VIDEO/AUDIO
- REMOVABLE 16-512 MB MEMORY CARD
- REMOTE CONTROL & USB COMPATIBLE

SPECIAL! \$139
VOLUME DISCOUNTS AVAILABLE

LITEXPO INC

P: 800-719-9605 F: 847-303-0660
WWW.LITEXPO.COM

ElectronicKits.Com

THE NAME SAYS IT ALL!

- | | |
|---------------------|----------------------|
| Robot Kits | Surveillance Kits |
| Motor Control Kits | Camera Kits |
| RF Remote Kits | Timer Kits |
| IR Remote Kits | Amplifier Kits |
| FM Transmitter Kits | Solar Kits |
| Radio Kits | Learn to Solder Kits |
| Multimeter Kits | Microcontroller Kits |

New Power Player Video Game System
128 Classic Arcade Games on your TV!!!

Carl's Electronics Inc, 17 Laurelwood Road, Sterling MA 01564
sales@electronickits.com - www.electronickits.com

PRINTED CIRCUIT BOARDS

Lowest Price in the market for single sided PCB.



SAVE MONEY!
MANUFACTURE IN MEXICO



CONTRACT MANUFACTURING

Surface mount and/or through-hole.

CUSTOM PLASTIC PARTS

Mold manufacturing. Production of injection molded parts. No order too small or too big. Very competitive on high labor parts. For very small orders we can inject your parts on manual low pressure machines.



CUSTOM METAL STAMPING

We manufacture our own tooling

U.S.A. Office: V & V Machy and Equip. Inc. Ph. (281)397 8101 Fax (281)397 6220. Please send blue prints and samples to our Mexico Plant: Alamo 93, Cuartro Piso, Santa Monica, Tlal. Edo de Mexico 54040. Ph. 011(525)361 3351, and 011(525) 360 3646, Fax: 011(525)361 5996. Attn: Victor Mendoza, email: victor@vandymachy.com
Please visit our site at: www.vandymachy.com

The Nuts & Volts of BASIC Stamps Volumes 1 & 2

Order from the Nuts & Volts Bookstore



\$29.95 each


Order Both Volumes For \$49.95! + Shipping

1 800 783-4624

www.nutsvolts.com



BASIC Stamp™
Prototyping
Made Easy...

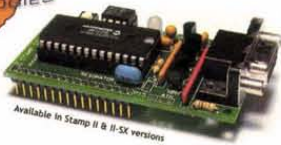

Stamp Stacks™ mount directly on any breadboard to make prototyping easy. Complete - just assemble, connect power and a serial cable. 100% BASIC Stamp™ compatible. Robust, Repairable, Inexpensive. Starter kits available.

Pic Compilers/Programmers/Protoboards-Serial LCDs IR Ranging Sensors...

HVW Technologies Inc.
Tel: (403)730-8603
Fax: (403)730-8903

VISA/MC Accepted
www.HVWTech.com

CONTROL • MEASURE • INPUT

MODEL 40-\$109

- RS-232 interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports



MODEL 100-\$279

- 12-bit 100KHz A/D
- Four analog outputs
- Three timer counters
- 24 digital I/O



PRAIRIE DIGITAL, INC.

920 SEVENTEENTH ST., INDUSTRIAL PARK
PRAIRIE DU SAC, WI 53578
TEL: (608) 643-8599 • FAX: (608) 643-6754

Scope + ScopeAlyzer™ = Logic Analyzer



- Attach to 20 MHz scope
- 100 MHz sample rate
- 16 channels
- 128K sample memory
- Trigger (0.1X, edges)
- Pan and zoom
- One key data snapshot
- Scope trigger output

The ScopeAlyzer™ is a precision emulated, professional grade instrument that attaches to an ordinary 20 MHz oscilloscope and extends its capability to a high performance logic analyzer.

Model 61050 \$395 Model 61100 \$595

Barrett Instruments

www.BarrettInstruments.com 800 272-1936

Battery Powered Wireless Color Surveillance Camera



\$149.95

Optional Monitor



See Website
http://www.4hrv.com



\$169.95

Camera/
Transmitter
Remote
Receiver

- 6 Month Camera Battery Life
- Remote Power Control with included Remote
- Built-in 5 sec-5 min timer
- Camera includes Microphone
- 510 x 492 Pixel Resolution
 - Works with TV, VCR or video monitor
- Includes Wall-Mount Screws
- User-adjustable Focus on 3-element Glass Lens
 - 100 Foot Range
- 2.4 GHz, 4-channel Receiver includes 3 cables and power transformer

Optionally Available:

- 4-inch Color TFT
- CCFL Backlight
- Internal Speaker
- Video/Audio Inputs
- Includes Wall Transformer

14-day, no-questions-asked, money back guarantee!

1-888-478-4204



Hangtown Remote Video
1390 Broadway, B341
Placerville, CA 95667

Go to www.4hrv.com for more detail and additional products

ActiveWire® USB Simple USB Interface!



- Works with MacOS 8/9, Win98/2K/ME
- FreeBSD and Linux!
- 24Mhz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel Input/Output
- See web-site for add-on boards
- All drivers, manuals, demos are on our web-site for immediate download!

\$59
plus shipping

ActiveWire, Inc.

www.activewireinc.com

ph +1.650.493.8700 x203 fax +1.650.493.2200

Electronic Surveillance Devices

\$39.99

This is the book that security professionals, security system installers and hobbyists have been waiting for. **Paul Brookes** launches straight into the practicalities of electronic surveillance with plenty of clear, detailed information on building the devices that are at the heart of surveillance and counter-surveillance. Self-build electronics projects are supported by principles and a brief survey of each type of device. \$39.99 plus S/H.

Call 1-800-783-4624 or visit our web site at www.nutsvolts.com

PRINTED CIRCUIT BOARDS

QUALITY PRODUCT
FAST DELIVERY
COMPETITIVE PRICING

- * UL approved
- * Single & Double sided
- * Multilayers to 8 layer
- * SMOBC, LPI mask
- * Reverse Engineering
- * Through hole or SMT
- * Nickel & Gold Plating
- * Routing or scoring
- * Electrical Testing
- * Artwork or CAD data
- * Fast quotes

We will beat any competitor's prices!!!
yogii@flash.net • flash.net/~yogii

10 pcs (3 days)
1 or 2 layers **\$249**

10 pcs (5 days)
4 layers **\$695**
(up to 30 sq. in. ea.) includes tooling, artwork, LPI mask & legend

PULSAR, INC

9901 W. Pacific Ave.
Franklin Park, IL 60131
Phone 847.233.0012
Fax 847.233.0013
Modem 847.233.0014

SERIAL GRAPHIC LCD



PICL-2464 \$99.00

Sharp LM24014 240 x 64 LCD
E.L. Backlight
5" x 1 5/16" Viewable Area
PIC 16F877 Re-Programmable
Switches, A/D & I/O Bits

LCD MONITOR KIT



A Complete 12.1 TFT LCD Kit With Controller and 180 Nit 16.7M Color XGA Panel- Just Plug Into VGA port and add 12 volts D.C.!

SK-2005R \$299

12.1" LCD MONITOR



Rugged Metal Case
On Screen Display
Free Z-Mount
Resistive & Capacitive
Touch Screen Options
Available. 1024 x 768
16.7 Million Colors
VGA and SVGA

MTR-EVUE-12 \$399.00

EARTHLCD.COM
"The World Wide LCD Source"

32701 Calle Perfecto - San Juan Capistrano, CA 92675
Ph: (949) 248-2333 Fax: (949) 248-2392
See the World's Largest Collection of LCD's and LCD Products at <http://www.EarthLCD.com>

EMERGING TECHNOLOGIES

32 Segment Serial LCD Controller (32SLCD)
Easily Control Digits or Individual Segments

\$34.95 (Controller Only)



use with your unique display



Shown w/Optional 4 digit Display plugged on

- Single line serial interface
- Two hardware selectable drive modes - Standard or 32 Segment
- Eight hardware selectable addresses (0-7)
- Use stand alone or with other Emerging Technologies Short Stack™ Products
- Use multiple units on a single serial line

Visit www.emergingtech-llc.com and click on "Products" link for more info

SPECIALISTS IN CUSTOM EMBEDDED AND SOFTWARE INTERFACES
Emerging Technologies, LLC. (920) 684-0216 www.emergingtech-llc.com

UHF RADIO MODEM
RM-232-914
FCC APPROVED

High Performance Low Power Wireless Data Link
Capable of Through Put Rates of 9600bps

- Fully acknowledged data transfer
- Addressable point-to-point mode
- Extended range in repeater mode
- Built-in software configurator
- Remote over-air configuration
- Broadcast multi-drop mode
- DTE speed 600-115200bps
- Indoor range to 30m
- Outdoor range to 150m
- Low current consumption



IDEAL FOR ADDING WIRELESS CONNECTIVITY TO ANY RS232 LINK!

www.lemosint.com

LEMO INTERNATIONAL
Microwave and RF Specialists

1305 Post Road
Fairfield, CT 06430
Tel: (203) 254-1531
Fax: (203) 254-7442
Email: Sales@lemosint.com

The new iSun™



— a complete solar charger for small electronics. Plugging accessories included that will enable you to run over 90% of all small electronics. 6 or 12 volt selectable!

Toll Free Order Line:
1-888-GO 4 KITS

Secure On-Line Ordering
www.qkits.com

Call 613-544-6333
for free catalog
49 McMichael St., Kingston, ON
K7M 1M8, CANADA

Download a Complete Virtual Workbench Today
Shareware version www.labcenter-electronics.com
PIC Micro Special \$99 includes; Graphical LCD, Logic Analyzer, Scope, Signal generator Probes, & more

PROTEUS
NEW VSM
Virtual System Modeling

www.labcenter-electronics.com
Build It In Cyberspace

Develop and test complete micro-controller design without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in the design. And it does it in real time.

Email, phone or fax for a free demo CD Today

www.labcenter-electronics.com

- CPU models for 8051 and PIC series, 68HC11 & ATMEL AVR micro-controllers available now. More CPU models under development.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Over 4000 standard SPICE models included.
- Integrates with PROTEUS PCB Design to form a complete electronics design system.

R4 Systems Inc.
Tel: 905.898.0665
Fax: 905.898.0683
info@r4systems.com



PCBexpress.com

PCBexpress - THE LEADING INTERNET SUPPLIER OF CIRCUIT BOARDS

PRODUCTS

Fast!
Quality
Proto-types up to 20pc
Low Cost!

- Prototypes up to 20 pcs
- Low cost - 2 boards \$80
- Quick-turn delivery
- No tooling charge

4-layers \$19 each!

TWO SIDED	TWO SIDED+	MULTILAYER	MULTILAYER+
Express #1 Ships Next Day 2-Sided PTH No Mask No Legend Reflowed T/L Routed Edges	Express #2 3 Day Lead 2-Sided PTH 2-Mask Legend SMOBC Routed Edges	Express #3 3 Day Lead 4-Layer PTH No Mask No Legend Reflowed T/L Routed Edges	Express #4 4 Day Lead 4-Layer PTH 2-Mask Legend SMOBC Routed Edges
ORDER	ORDER	ORDER	ORDER

ECD, Inc. Home of PCBexpress

AFFORDABLE CNC MACHINES

Simple to Use
Run From Any Version of Windows®

sales@flashcutcnc.com
www.flashcutcnc.com

Automated Machine Tools to Produce

- Panels
- PCB Prototypes
- Chassis/Housings
- Any 3D Part

FLASHCUT CNC™

1263 El Camino Real, Menlo Park, CA 94025
4949 St. Elmo Avenue, Bethesda, MD 20814
Toll Free 888-883-5274
Tel 650-853-1444 Fax 650-853-1405

Your own circuit boards
from design through
order are as easy as

PCB123

Circuit Boards with the
Click of a Mouse

- * Easy
- * Inexpensive
- * Fast

Your **FREE**
software features
real-time
pricing
as you go.

Visit us online at www.pcb123.com. 1

Download the **FREE** software. 2

Design what you want. 3

Small quantity circuit boards at
low prices and quick delivery.

PCB123™

Providing the complete
circuit board solution, design through order.

Synthesizer Modules, Guitar Effects, Mixers, EQs,
Tube PreAmps, and dozens of other kits for
ELECTRONIC MUSICIANS

PAIA

Theremin
The PAIA Theremin uses the same heterodyne principles as the original turn of the century instrument for classic tone and adds features made possible by modern ICs. Shown with optional lectern case.

9505K Kit \$89.75

9308K Kit \$154.00

FatMan Analog MIDI Synth
A complete music synthesizer with all the big bottom and phat sound that makes analog famous. 20 knobs and controls for real-time sound sculpting. Compatible with standard MIDI sources like keyboards or computers. Desktop case or rack panel available.

Check out <http://Paia.com> for schematics, tech details, firmware source files and more...

PAIA Electronics • 3200 Teakwood Lane • Edmond, OK 73013
405.340.6300 • fax:405.340.6378 • email:info@paia.com

BiM2 433 MHz

900 MHz
Available
January 2002

High Speed Wireless Data Transceiver
Physical Dimensions: 33 mm x 23 mm x 4 mm

- Data rates up to 160 kbps
- RX sensitivity -100dBm
- Usable range up to 200m
- SAW controlled FM transmitter
- 3V and 5V versions
- Low power requirements
- TX power 10mW @ 5V
- Fully screened
- Double conversion Superhet receiver
- Plug in replacement for BiM-433-F



www.lemosint.com


LEMOS
INTERNATIONAL
Microwave and RF Specialists

1305 Post Road
Fairfield, CT 06430
Tel: (203) 254-1531
Fax: (203) 254-7442
Email: Sales@lemosint.com

Volume Pricing
Available!

BX-123-AU \$69
BX-123-CAU
(color) \$149

PC-103
\$99

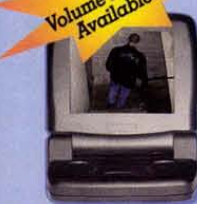

LCD-5.5 \$129, LCD-7 \$259
• Compact footprint, ultra-bright display, RCA inputs NTSC or PAL
• 960 x 240 pixels w/brightness & tilt controls
• Attractive enclosure w/built-in speaker

ASK-7003-TR
\$169

KX-880 \$89
KX-880-C
(color) \$129

WR-700
Weather Resistant
\$99

Fax: 847-303-0660
Canada: 877-720-9222

MATCO
EverSecure™
www.matco.com

- On-Line Ordering
- OEM Security Products
- Monitors, Cables, Accessories
- Law Enforcement Equipment
- Discreet Wireless Systems
{ \$89-\$269 }

Sales: 847-303-9700
Toll Free: 800-719-9605

Kenwood's FreeTalk Radios Make It Easy To Stay In Touch

It's all about communication these days. Who's got what best plan for where and can you connect to the Internet anywhere, anytime. How many minutes across how many states and how many family members can you get to sign up on a plan. Too complicated.

There is an alternative, however, that will accommodate most "communication" situations ...

One of the most overlooked methods available today for keeping in touch with loved ones — or whoever — is with FRS (Family Radio Service). You don't have to take a test and the air time is always free. Take, for example, Kenwood Communications new FreeTalk radio (Model UBZ-LH14). Designed for outdoor recreation activities, the UBZ-LH14 is easy to use and small enough to take anywhere. It is equipped with premium features like voice scrambling and automatic channel selection, and operates over a two-mile radius. FreeTalk radios operate on free airwaves designated as FRS by the Federal Communications Commission. In addition, two, three, four, or more people can take part in the same conversation.

There are virtually limitless scenarios to use these radios in. Say you're going to an amusement park and the kids want to go to a different area or ride. Or, if you're at a campground and part of your group wants to go for a walk or bike ride. FRS makes it easy to stay in touch with each other.

With the convenient headset, the "hands-free" capability is perfect for situations where you need use of both hands, but still need to talk. For example, if you're into boating, one of the hardest things about anchoring is having to either shout directions back and forth from one end of the boat to the other or else trying to use hand signals.

What about when you're maneuvering a trailer or motorhome into a tight spot and have to try to stay within view of the driver's mirrors? Or, maybe you're traveling in a group and need to change the off-ramp you're going to or have to pull over.

"Since their introduction, FRS two-way radios have become very popular," said Tom Wineland, Kenwood Communications president. "Our latest

generation of FreeTalks are designed with exclusive features to offer more convenience and reliability than those from any other manufacturer."

New to this year's model is a "range in/out" detector and "channel scan." The range in/out detector lets users know if they are within transmission range or not. An icon shows up on the radio's LCD if the user is in range, or disappears if the user is out of range.

Channel scan finds available channels for transmitting and receiving messages. If there's too much interference while you're having a conversation, the FreeTalk radio will automatically scan channels in ascending order until a clear channel is located.

An extra large liquid crystal display (LCD) allows users to quickly note channel settings and the status of all radio indicators. The display is illuminated for easy viewing at night or in darkened rooms.

FreeTalk radio provides users with 532 channel combinations (14 channels, each with 38 talk groups) to make it easy to find one for uninterrupted conversations. A scramble mode maintains privacy and keeps unintended listeners from eavesdropping. Easily recognizable call tones can be sent between radios to let others in a group know who is trying to contact them.

The new FreeTalk, offered in black, yellow and platinum, has a suggested retail price of \$114.95 each. Kenwood Communications also offers three optional accessories, including a remote control speaker microphone (SMC-34), a hands-free voice-activated headset (HMC-3), and a clip microphone with earphone (EMC-3). For more details go to www.kenwood.net.



Dealer Directory

ALABAMA

Little Professor Book Center
2717 S. 18th St.
Birmingham 35209

ARIZONA

Elliott Electronic Supply
1251 S. Tyndall Ave.
Tucson 85713

Tower Records
3 E. 9th St.
Tempe 85281

AUSTRALIA

DonTronics
P.O. Box 595
29 Ellesmere Cres.
Tullamarine 3043
www.dontronics.com

CALIFORNIA

Abletronics
9155 Archibald Ave. Unit E
Cucamonga 91730

All Electronics
905 S. Vermont Ave.
Los Angeles 90006

14928 Oxnard St.
Van Nuys 91411

Centerfold International
716 N. Fairfax Ave.
Los Angeles 90046

Electro Mavin
2985 E. Harcourt St.
Rancho Dominguez 90221

HSC Electronic Supply
4837 Amber Ln.
Sacramento 95841

3500 Ryder St.
Santa Clara 95051

5681 Redwood Dr.
Rohnert Park 94928

JK Electronics
6395 Westminster Ave.
Westminster 92683

Lion Electronic Labs
4948 E. Townsend Ave.
Fresno 93727

Mar Vac Electronics
2001 Harbor Blvd.
Costa Mesa 92627

12453 Washington Blvd.
Los Angeles 90066

4747 Holt Blvd.
Montclair 91763

2000 Outlet Center Dr.
Ste. 150
Oxnard 93030

1759 Colorado Blvd.
Pasadena 91106

2537 Del Paso Blvd.
Sacramento 95815

5184 Hollister Blvd.
Santa Barbara 93111

OPAMP Technical Books
1033 N. Sycamore Ave
Los Angeles 90038

Sav-On Electronics
13225 Harbor Blvd.
Garden Grove 92643

The Red Barn
Hwy. 299
Bieber 96009

Tower Books

211 Main St.
Chico 95928

7840 Macy Plaza Dr.
Citrus Heights 95610

1280 E. Willow Pass Rd.
Concord 94520

630 San Antonio Rd.
Mountain View 94040

1600 Broadway
Sacramento 95818

2538 Watt Ave.
Sacramento 95821

Tower Records/Video
220 N. Beach Blvd.
Anaheim 92801

6694 Amador Plaza Rd.
Dublin 94568

5703 Christie Ave.
Emeryville 94608

4118 Fremont Hub
Fremont 9453

5611 Blackstone
Fresno 93710

23541 Calle De La Louisa
Laguna Hills 9265

6310 E. Pacific Coast Hwy.
Long Beach 90803

2331 S Atlantic Blvd.
Monterey Park 91754

2525 Jones St.
San Francisco 94133

871 Blossom Hill Rd.
San Jose 95123

Video Electronics
3829 University Ave.
San Diego 92105

CANADA

Com-West Radio
Systems Ltd.
8171 Main St.
Vancouver, BC V5X 3L2

Emma Marion Ltd.
2677 E. Hastings St.
Vancouver, BC V5K 1Z5

Muir Communications Ltd.
3214 Douglas St.
Victoria, BC V8Z 3K6

COLORADO
Centennial Electronics, Inc.

2324 E. Bijou
Colorado Springs 80909

Tower Records/Video
2500 E. 1st Ave.
Denver 80206

CONNECTICUT
Archway News

64 Bank St.
New Milford 06776

Tower Records
1145 High Ridge Rd.
Stamford 06905

DELAWARE

Newark Newsstand

70 E. Main St.
Newark 19711

DISTRICT OF COLUMBIA

Tower Records
2000 Pennsylvania Ave.
Washington 20006

FLORIDA

Alfa Electronic Supply
6444 Pembroke Rd.
Miramar 33023

Clarks Out of Town News
303 S. Andrews Ave.
Fort Lauderdale 33301

Mike's Electronic
Distributing Co.
1001 N.W. 52nd St.
Fort Lauderdale 33309

HAWAII

SolarWorks!
525 Lotus Blossom Ln.
Ocean View 96737

Tower Records
4211 Wai'aleae Ave.
Honolulu 96816

611 Keeaumoku
Honolulu 96814

IDAHO

Current Source
454 N. Philippi St.
Boise 83706

ILLINOIS

Tower Records/Video/Books
383 W. Army Trail Rd.
Bloomington 60108

2301 N. Clark St. #200
Chicago 60614

1209 E. Golf Rd.
Schaumburg 60173

INDIANA

Surplus Bargain Center
2611 W. Michigan St.
Indianapolis 46222

KANSAS

Hollywood At Home
9063 Metcalf Ave.
Overland Park 66212

LOUISIANA

Lakeside News
3323 Severn Ave.
Metairie 70002

MARYLAND

Tower Records/Video
2566 Solomons Island Rd.
Annapolis 21401

MASSACHUSETTS

Tower Records/Video
1011 Middlesex Turnpike
Burlington 01803

MICHIGAN

Little Professors Book Center
22174 Michigan Ave.
Dearborn 48124

Purchase Radio Supply, Inc.
327 E. Hoover Ave.
Ann Arbor 48104

Spectrum Electronics, Inc.
1226 Bridge St. NW
Grand Rapids 49504

MINNESOTA

Radio City, Inc.
2633 County Road 1
Mounds View 55112

MISSOURI

Electronics Exchange
8644 St. Charles Rock Rd.
St. Louis 63114

NEVADA

Amateur Electronic Supply
4640 Polaris
Las Vegas 89103

Radio World

1656 Nevada Hwy.
Boulder City 89005

Sandy's Electronic Parts
961 Matley Ln #100
Reno 89502

Tower Records/Video
4580 W. Sahara Ave.
Las Vegas 89102

NEW JERSEY

H.E.S. Electronics
1715 Route 88
Brick 08724

NEW YORK

Durston's Cigar Store
515 W. Genesee St.
Syracuse 13204

Ham Central
3 Neptune Rd.
Poughkeepsie 12601

Hirsch Sales Corporation
219 California Dr.
Williamsville 14221

Tower Records/Video
105 Old Country Rd.
Carle Place 11514

OHIO

350-370 Route 110
Huntington 11746

1961 Broadway
New York 10023

NORTH CAROLINA

Digital Age
616 W. Fourth St.
Winston Salem 27101

United Electronic Supply
920 Central Ave.
Charlotte 28204

OKLAHOMA

Hosfelt Electronics, Inc.
2700 Sunset Blvd.
Steubenville 43952

Keyways, Inc.
204 S. 3rd St.
Miami 33130

OREGON

Taylor News & Books
133 W. Main, Ste. 102
Oklahoma City 73102

News & Smokes
1060 S.E. M St.
Grants Pass 97526

Norvac Electronics
7940 S.W. Nimbus Ave. Bldg. 8
Beaverton 97005

960 Conger
Eugene 97402

1545 N. Commercial N.E.
Salem 97303

Tower Books
1307 N.E. 102nd Ave.
Portland 97220

PENNSYLVANIA

Tower Books
425 South St.
Philadelphia 19147

Tower Records
340 W. Dekalb Pike
King of Prussia 19406

Tower Records
Land Title Bldg.
100 S. Broad St.
Philadelphia 19110

TENNESSEE
Tower Books

2404 W. End Ave.
Nashville 37203

Tower Records
504 Opry Mills Dr.
Nashville 37214

TEXAS

Electronic Parts Outlet
3753-B Fondren Rd.
Houston 77063

Mouser Electronics
958 N. Main St.
Mansfield 76063

Tanner Electronics
1100 Walwood Pkwy #100
Carrollton 75006

Tower Records
2403 Guadalupe St.
Austin 78705

VIRGINIA

Tower Records/Video
6200 Little River Turnpike
Alexandria 22312

4110 W. Ox Rd. #12124
Fairfax 22033

1601 Willow Lawn Dr.
Richmond 23230

8389 E. Leesburg Pike
Vienna 22182

WASHINGTON

A-B-C Communications, Inc.
17541 15th Ave. N.E.
Seattle 98155

Supertronix
16550 W. Valley Hwy.
Seattle 98188

Tower Books
10635 N.E. 8th St.
Bellevue 98004

20 Mercer St.
Seattle 98109

WISCONSIN

Amateur Electronic
Supply, Inc.
5710 W. Good Hope Rd.
Milwaukee 53223

WYOMING
Western Test Systems

2701 Westland Ct. #B
Cheyenne 82001

Understanding and Using 'Norton' Op-Amp ICs — Part 2

By Ray Marston

Ray Marston concludes his look at Norton Current-Differencing Amplifier op-amp principles and circuits in this final part of this mini-series.

Last month's opening episode of this two-part mini-series explained the basic operating principles of the Norton current-differencing amplifier (CDA) op-amp and presented a variety of practical applications of the popular LM3900 quad Norton op-amp IC. This month's concluding episode presents a few more practical LM3900 applications, and then explains the operating theory and practical applications of the LM359 high-performance dual Norton op-amp.

LM3900 CURRENT-REGULATOR CIRCUITS

Figures 1 to 4 show various ways of using individual op-amps from the LM3900 quad Norton op-amp IC to make simple current-regulator circuits; note when using the LM3900 ICs that unwanted op-amps can be disabled by wiring their two input terminals to the IC's GND or low-voltage line.

The Figure 1 circuit acts as a fixed (1mA) current source, which feeds a fixed current into a load connected between Q1 collector and ground almost irrespective of the load impedance (in the range zero to 14k). The circuit is powered from a regulated 15V supply. Potential divider R1-R2 applies a 14V reference (15V-1V0) to R3, so the op-amp output automatically adjusts to give an identical voltage at the R4-R5 junction. This produces 1V0 across R5, resulting in an R5 current of 1mA. Since this current is derived from Q1 emitter, and the emitter and collector currents of a transistor are almost identical, the circuit's collector acts as a fixed current source. The source current can be doubled (to 2mA), if desired, by halving the R5 value, etc.

Figure 2 shows a simple variation of the above circuit, in which the source current is independent of variations in supply rail voltage. In this case, the input is set at 2V7 below the supply rail value via Zener diode ZD1, so 2V7 is automatically set across R4, which has a value of 2k7 and thus produces a fixed 1mA source current from the collector of transistor Q1.

Figure 3 shows a simple 1mA current sink, in which a fixed current flows in any load connected between the positive supply rail and Q1 collector, almost irrespective of the load impedance. Here, the non-inverting terminal of the op-amp is disabled, and 100% negative feedback is used between the output of the circuit (Q1 emitter) and the inverting input terminal. The voltage across R1 thus equals the V_{be} of the inverting ter-

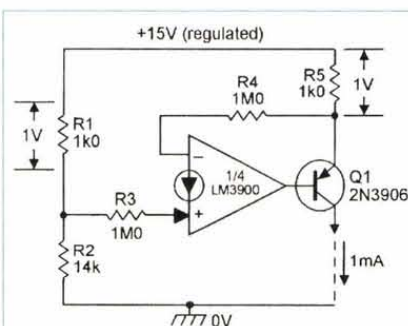


Figure 1. Fixed-current source (1mA).

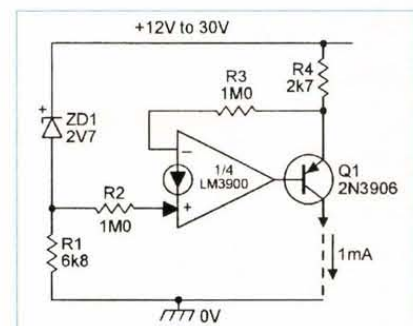


Figure 2. Alternative current source (1mA).

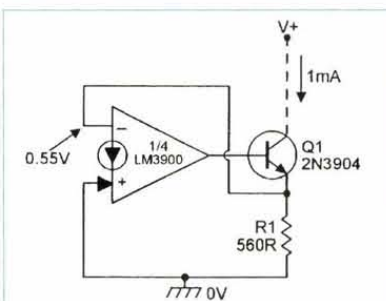


Figure 3. Simple 1mA current sink.

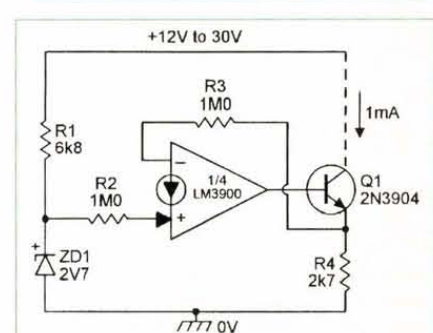


Figure 4. Improved current sink (1mA).

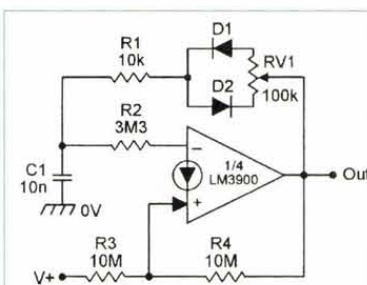


Figure 6. Variable mark/space ratio generator.

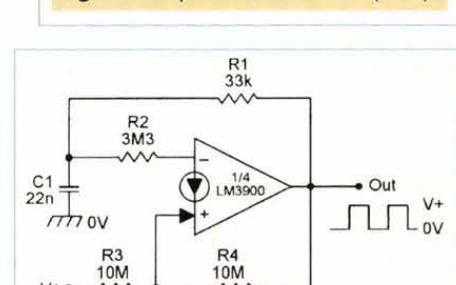


Figure 5. 1kHz squarewave generator.

minal and, since this is roughly 0.55V, a fixed current of about 1mA flows through Q1 emitter and R1, and thus into Q1 collector from any

Understanding and Using 'Norton' Op-Amp ICs — Part 2


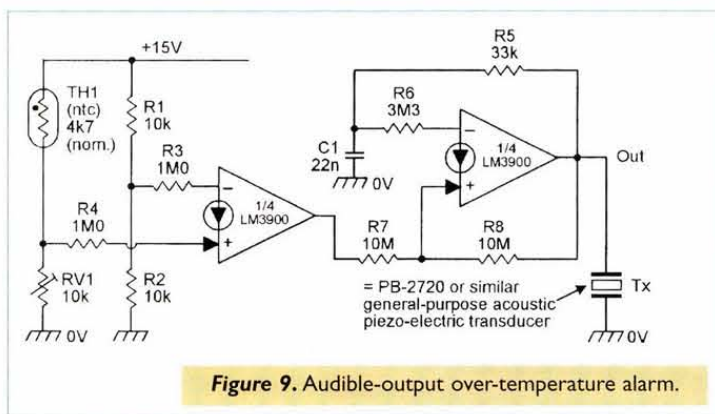
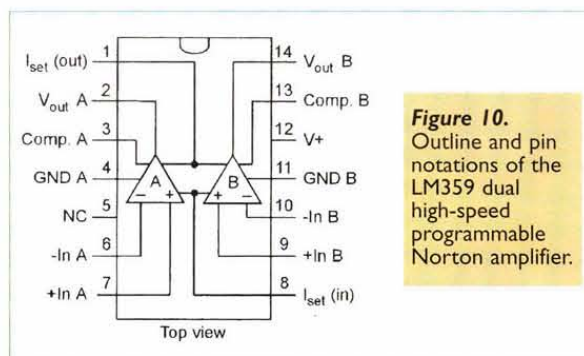
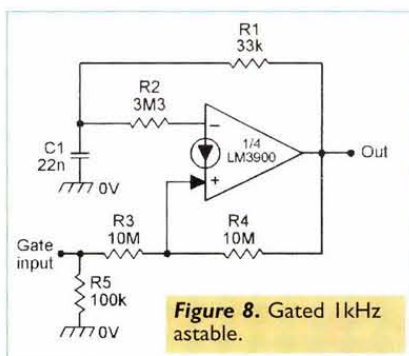
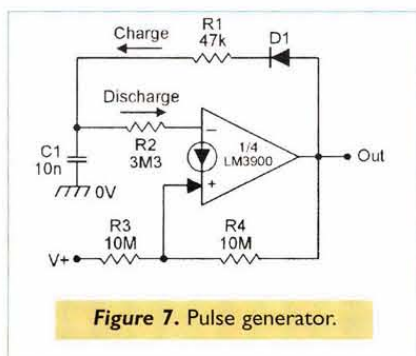
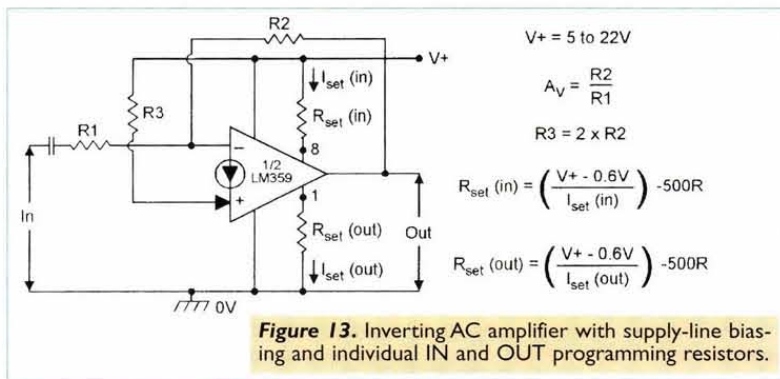
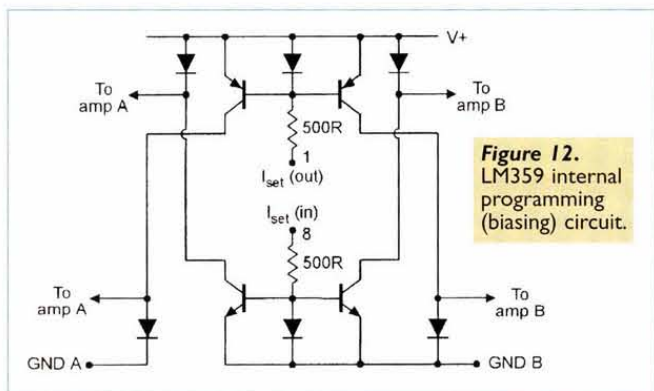


Figure 11. Basic circuit of each LM359 op-amp.

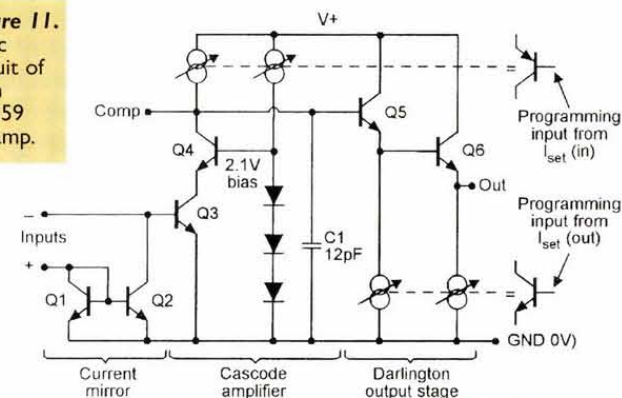

load that is connected. Note that the sink current of this circuit is not temperature compensated.

Finally, Figure 4 shows an alternative type of current sink. In this case, the op-amp is fully enabled, and has a fixed reference of 2V7 applied to its non-inverting terminal via R2. Consequently, the circuit automatically adjusts to generate 2V7 across R4 which, since it has a value of 2k7, generates a current of 1mA in the emitter and collector of Q1. This current can be varied, if required, either by varying the value of R4 or by varying the input voltage fed to R2.

LM3900 WAVEFORM-GENERATOR CIRCUITS

To conclude this look at the LM3900 quad Norton op-amp IC, Figures 5 to 9 show some useful ways of using its op-amps to make simple waveform-generator circuits. Figure 5 shows a 1kHz squarewave generator, in which C1 alternately charges and discharges via R1. When the output is high, R3-R4 are effectively connected in parallel, and C1 charges until the current flow into R2 equals that flowing into the non-inverting terminal of the op-amp; this point occurs when the voltage across C1 rises to roughly two-thirds of +V. At this point, the circuit switches regeneratively, the output switches low, and C1 starts to discharge via R1. Under this condition, R4 is effectively disabled and the input current to the non-inverting terminal is determined only by R3, so C1 discharges until the R2 current falls slightly below that of R3. This

point occurs when the C1 voltage falls to about one-third of +V. At this point the circuit again switches regeneratively, and the output goes high again. The action then repeats *ad infinitum*.

The Figure 5 circuit is useful for generating squarewaves with frequencies up to a maximum of only a few kHz; because of the poor slew rate performances of the LM3900 (0.5V/μS), the output waveform has fairly poor rise and fall times. The circuit generates a symmetrical squarewave output. Figure 6 shows how the circuit can be modified to give a variable mark-space (M/S) ratio output. In this case, C1 alternately charges via R1-D1 and the upper half of RV1, and discharges via R1-D2 and the lower half of RV1. The M/S ratio can be varied over the approximate range 1:10 to 10:1 via RV1.

Figure 7 shows a simple modification of the above circuit, which causes it to act as a free-running pulse generator. In this case, C1 alternately charges via R1-D1 and discharges via R2, producing an M/S ratio of about 1:60. Figure 8 shows how the basic Figure 5 circuit can be modified to act as a gated 1kHz astable or squarewave generator by taking R3 to ground via R5, rather than directly to the positive supply rail. The circuit becomes active only when the gate terminal is pulled high (to the positive supply rail).

Finally, to complete this look at LM3900 applications, Figure 9 shows how this month's Figure 8 and last month's Figure 16 circuits can be combined to make an audible-output over-temperature alarm, which generates a 1kHz tone in a general-purpose acoustic piezo-elec-

Understanding and Using 'Norton' Op-Amp ICs — Part 2

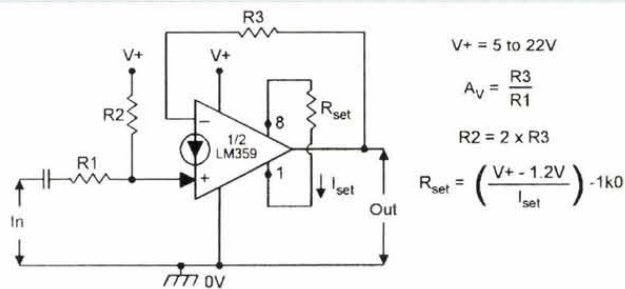


Figure 15. Non-inverting AC amplifier with supply-line biasing and single resistor IN/OUT programming.

tric transducer when the TH1 temperature exceeds a value pre-set via RV1.

THE LM359 DUAL NORTON OP-AMP IC

The LM359 is not as well known as the LM3900, but is an outstandingly useful Norton type of IC. The LM359 is, in fact, a high-performance IC that houses two identical Norton op-amps, plus a common biasing network, in a 14-pin DIL package (see Figure 10) and can operate from a single-ended 5V to 22V power supply. Each of its op-amps offers a 30MHz unity-gain bandwidth, a 60V/ μ S slew rate, and a 72dB open-loop gain, and has many of its parameters fully programmable via one or two external resistors.

The LM359's op-amps differ considerably from those used in the LM3900. Figure 11 shows the basic LM359 op-amp circuit in slightly simplified form. This consists, in essence, of a mirror-driven (via Q1-Q2) wide-band cascade amplifier (Q3 and Q4), which does not suffer from output-to-input Miller or parasitic feedback effects and thus gives an excellent high-speed performance, plus a Darlington emitter follower output stage (Q5 and Q6).

Note that a 12pF capacitor is internally wired between Q4 collector (accessible at the COMP terminal) and ground, and that the Q3-Q4 operating current can be programmed via the $I_{set(in)}$ current of the IC's internal biasing network, thus enabling the circuit's input bias current, slew rate, bandwidth, and supply current to be pre-set. Similarly, the operating currents of the Darlington output stage can be programmed via the $I_{set(out)}$ currents of the internal biasing network, enabling the output sink current and supply current to be pre-set.

Figure 12 shows the basic circuit of the IC's internal biasing network, which controls both op-amps. Thus, the $I_{set(in)}$ current can be set via suitable resistors wired between pin 8 and the positive supply rail, and the $I_{set(out)}$ current can be set via a suitable resistor wired between pin 1 and ground B. Alternatively, if $I_{set(in)}$ and $I_{set(out)}$ are to have equal values, the current can be set via a single resistor wired between pins 1 and 8.

USING THE LM359

The LM359 is usually used in linear amplifier applications and, in such cases, the design procedure involves two simple stages: the first being the design of the input biasing network, and the second the selection of the programming resistor value(s).

The LM359 is biased in exactly the same way as the LM3900, using either voltage-reference biasing, supply-line biasing, or $N \times V_{be}$ biasing, as shown in last month's Figure 6 and fully described last month. Programming involves the wiring of either a single resistor between pins 1 and 8 of the IC, or of individual resistors between pin 1 and ground

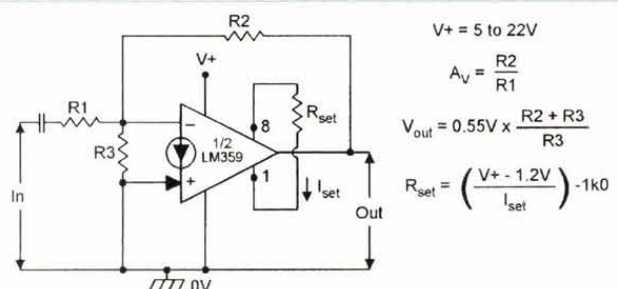


Figure 14. Inverting AC amplifier with $N \times V_{be}$ biasing and single resistor IN/OUT programming.

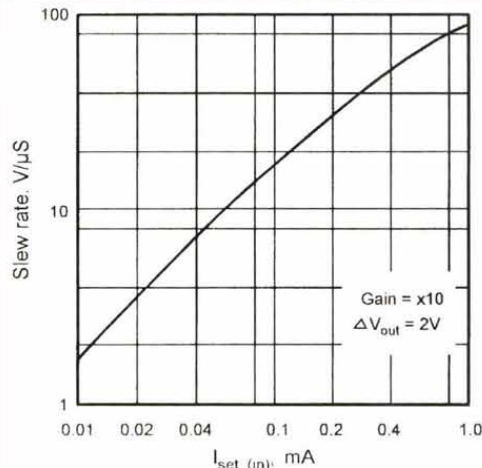


Figure 17. LM359 slew rate.


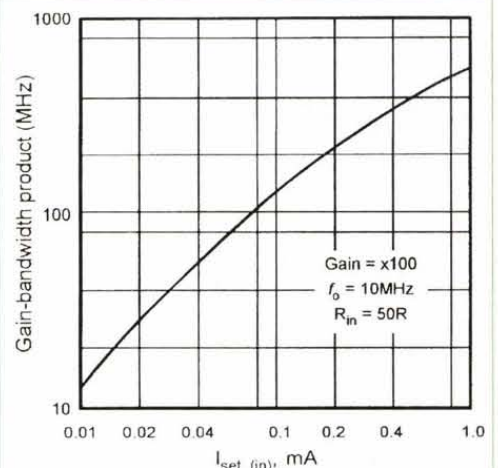


Figure 16. LM359 gain-bandwidth product.

Figure 18. LM359 inverting input bias current.

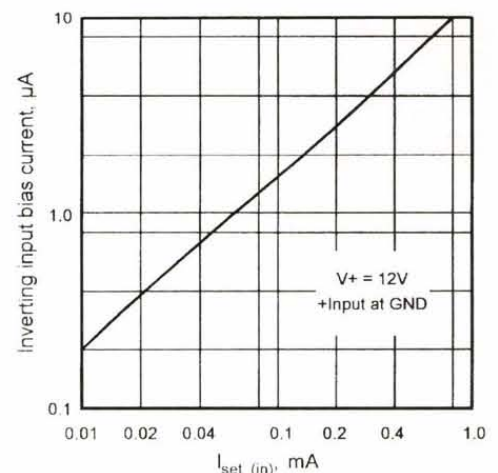

and between pin 8 and supply positive, as mentioned above. Figures 13 to 15 show three typical circuits that can result from the above options, together with their relevant design formulas. Thus, the Figure 13 circuit gives inverting AC amplifier action and uses supply-line biasing, and uses individual $R_{set(in)}$ and $R_{set(out)}$ programming resistors. The Figure 14 circuit also acts as an inverting AC amplifier, but uses $N \times V_{be}$ biasing and uses a single resistor for I_{in} and I_{out} programming. Finally, the Figure 15 circuit acts as a non-inverting AC amplifier and uses supply-line biasing and a single programming resistor.

I_{set} PROGRAMMING

The major operating parameters of the two LM359 op-amps can be

Understanding and Using 'Norton' Op-Amp ICs — Part 2

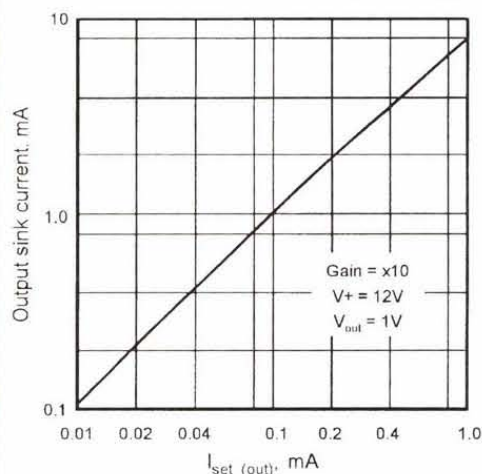


Figure 19. LM359 output sink current.

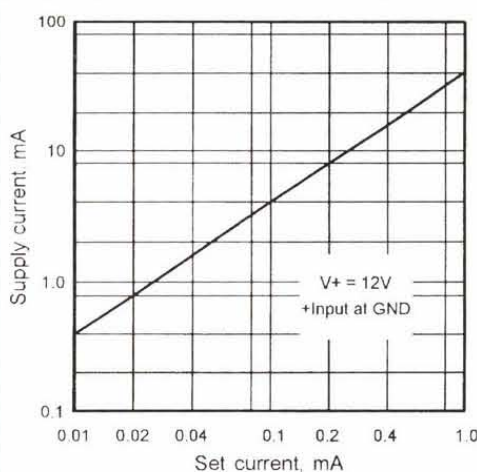


Figure 20. LM359 total supply current ($I_{set(in)} = I_{set(out)}$).

show the effects of this current on the individual parameters.

The gain-bandwidth product graph of Figure 16 is based on a x100 inverting amplifier fed with a 10MHz input signal, but is valid for all types of amplifier. Thus, with a 10MHz input, it gives a gain of x60 and a gain-bandwidth value of 600MHz at an $I_{set(in)}$ current of 1mA, and a gain of x1.1 and a gain-bandwidth product of 11MHz at 0.01mA. The gain-bandwidth of the circuit is thus directly proportional to the $I_{set(in)}$ value.

Note that the gain-bandwidth product of the IC is also inversely proportional to the op-amp's C_{comp} value (see Figure 11), which is a fixed 12pF, but which can be increased by wiring an external capacitor between the 'comp' terminal and ground. Thus, the gain-bandwidth values can be halved by

doubling the effective C_{comp} value via an external 12pF capacitor wired between these two points.

The slew rate (see Figure 17) of the op-amp is also directly proportional to $I_{set(in)}$, but inversely proportional to C_{comp} and can thus be varied via either of these quantities. The inverting input bias current values (Figure 18), on the other hand, are independent of C_{comp} and depend solely on the $I_{set(in)}$ values. The output sink current (Figure 19) is variable via the pin 1 $I_{set(out)}$ current and is roughly 10 times that value.

Note that, as already mentioned, the I_{set} values can either be set via individual resistors or, if both I_{set} values are equal, can be set by a single resistor wired between pins 1 and 8. If individual resistors are used, each value is determined by:

$$R_{set} = (V/I_{set}) - 500R$$

where $V = V+ - 0.6V$. In this case, the total current consumption of the IC (of the two op-amps) is roughly equal to:

$$I_{supply} = (27 \times I_{set(out)}) + (11 \times I_{set(in)})$$

If only a single programming resistor is used, its value is determined by:

$$R_{set} = (V/I_{set}) - 1k\Omega$$

where $V = V+ - 1.2V$. In this case, the total current consumption of the IC roughly equals $37 \times I_{set}$. Figure 20 shows the typical consumption graph when using a 12V supply.

WIDEBAND AMPLIFIERS

The most important application of the LM359 is as a video or wideband amplifier, and Figures 21 to 23 show three practical circuits of this type. The basic design principle of these circuits is as follows:

The Figure 21 circuit is designed to be powered from a 12V supply, and to act as an x10 (= 20dB) inverting amplifier that gives a bandwidth of at least 20MHz when driven via a terminated 75-ohm (75R) line. This last requirement sets the R1 value at 75R. The input is then AC-coupled via C1, which is shunted by C2 to minimize its high-frequency impedance. R2-R4 set the circuit's voltage gain. R2 must be small, but must not significantly shunt the R1 value; this gives R2 a sensible compromise value of 750R. To give a voltage gain of x10, R4 must be 10 times greater than R2, and this sets the R4 value at 7.5k.

To give maximum output voltage swing the op-amp output must be DC biased to a quiescent value slightly below half-supply volts, and this is achieved by making R3 a bit more than twice the R4 value. A good compromise is 20k, which sets the output at 5.1V.

To give the required gain and bandwidth, the op-amp needs a minimum gain-bandwidth product of 200MHz. An I_{bias} value of 0.5mA gives

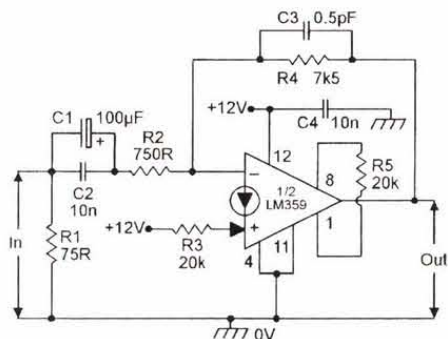


Figure 21. Wideband (>20MHz) x10 inverting amplifier.

Figure 22. Wideband (>20MHz) x10 non-inverting amplifier.

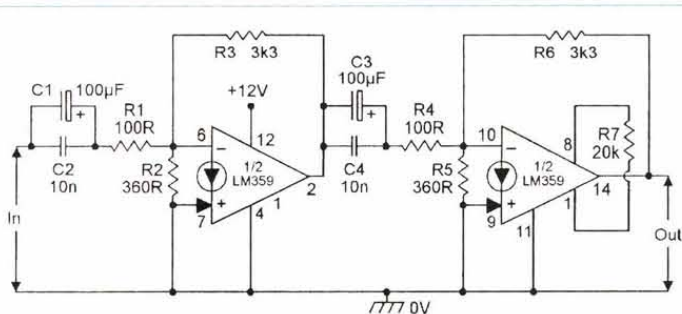
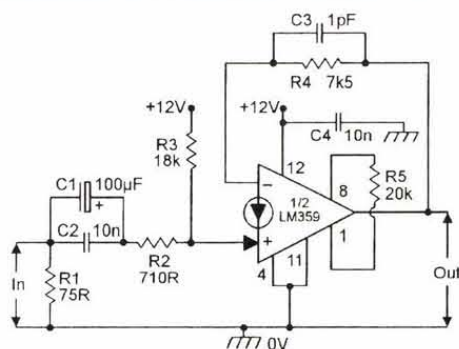


Figure 23. High-gain (x1000) general-purpose wideband (8MHz) amplifier.

programmed via the pin 1 and pin 8 I_{set} currents of the IC. The gain-bandwidth products, the slew rate, and the inverting input bias current can be programmed via the pin 8 $I_{set(in)}$ current, and Figures 16 to 18

Understanding and Using 'Norton' Op-Amp ICs — Part 2

a gain-bandwidth of 400MHz, which gives a good margin of safety, and this can be programmed by giving R5 a value of 20k.

To ensure a good high-frequency performance, the pin 12 supply pin is RF-decoupled to ground via C4. To give maximum bandwidth, C3 (two twists of insulated wire) is adjusted on test. In practice, this circuit gives a 3dB bandwidth that extends from 2.5Hz to about 30MHz, and is absolutely flat up to 20MHz.

Figure 22 shows a non-inverting version of the wideband amplifier. In this case, the gain is determined by the R2-R4 ratio, and the DC bias-

ing value by the R3-R4 ratio. The 3dB bandwidth of the circuit extends from 2.5Hz to 30MHz, and is almost flat to 20MHz.

Finally, to complete this look at Norton amplifier ICs, Figure 23 shows how both op-amps of an LM359 IC can be cascaded to make a general-purpose wideband amplifier with a nominal gain of x1000 and a 3dB bandwidth that extends from 10Hz to 8MHz. In this case, the op-amps are each wired in the inverting mode, with a x33 gain set by the R3/R1 or R6/R4 ratio, and use $N \times V_{be}$ biasing, with the N ratio set by R3/R2 or R6/R5. **NV**

We often have subscribers ask how to read their mailing label so they can tell when their subscription expires. To read the label, the first set of numbers is your account number which is then followed by a set of four numbers. This is the expiration date: year first, then month. For example, if the second set of numbers reads 0207, then your subscription expires with the July 2002 issue. **Better hurry and renew!**

DesignNotes.com

Your Design Resource on the Web

Improve Your Design Skills, Find Project Advice and More

****Hot Summer Sale****

Velleman's DVM345DI Multi-Meter with RS-232, Temp., and PC Software. **\$84.95**

For complete specs, Visit: www.designnotes.com

Visit Our Online Forum

On-Line Circuit Archive

Hundreds of Circuits. Over 23 Different Topics

Designing for Dollars

- 1) Submit your favorite circuit or program.
- 2) Each month the best design entry (Judged by your peers) wins \$100
- 3) Monthly winners are eligible for the yearly \$1200 Grand Prize!

NEXT GRAND PRIZE DRAWING IS OCT. 2002

Share What You Know and Learn What You Don't

Visit Us at www.designnotes.com

Circle #37 on the Reader Service Card.

SAVE MONEY - WHOLESALE PRICING

Roger's Systems

WE'LL GET YOU CONNECTED

Cables, Connectors & Accessories

for computers, networks, audio, video and telecommunications.

PC and MAC repairs, parts and much more.

The more you buy the more you save, quantity discounts available.

Call, Click or Visit!

800-366-0579 661-295-5577

www.RogersSystems.com

Shop anytime from our online store and catalog or by fax 661-295-8777

Monday - Friday 9 am-6 pm and Saturday 9 am-2 pm
25030-H Avenue Tibbitts, Santa Clarita, CA 91355



Tone Generator & Probe
Single or Multi-tone signal, 3 modes, traces wires & cables. Amplifier & LED readout.
TM-151 \$69.00



Soldering Station Kit
40w 2-wire soldering iron, helping hands magnifier, 5' rosin core solder, de-soldering tool.
KIT-SOLDER \$14.99



Screwdriver Set in Case
6 piece precision set: 1.0, 1.2, 1.8, 2.4, 3.0, & 3.5 mm. Regular & Phillips.
TM-315 \$1.59



12' Belkin Stereo Cable
RCA 24k gold plated contacts with twisted pair construction and heavy shielding for improved noise reduction.
AC-220 \$2.99



USB & Firewire Cables
6' & 10' from \$3.99



3' TOSLink Digital Cable
Gold body connectors at both ends, large diameter core for low loss. 6' & 10' lengths.
CC-PWC \$1.00



24" ATA Round ATA Cable
For hard drive, CD, DVD, and other IDE/ATA devices. Black, blue, yellow, red & green. ATA66/100/133/266 compliant.
CC-324-specify color \$9.99

Circle #36 on the Reader Service Card.

The Standard for checking Capacitors in-circuit



Good enough to be the choice of Panasonic, Pioneer, NBC, ABC, Ford, JVC, NASA and thousands of independent service technicians.

Inexpensive enough to pay for itself in just one day's repairs. At \$179, it's affordable.

And with a 60 day trial period, satisfaction guaranteed or money-back policy, the only thing you can lose is all the time you're currently spending on trying to repair all those dogs you've given up on.

CapAnalyzer 88A

Available at your distributor, or call 561-487-6103

Electronic Design Specialists

Locate shorted or leaky components or conditions to the exact spot in-circuit

Still cutting up the pcb, and unsoldering every part trying to guess at where the short is?

\$179



Your DVM shows the same shorted reading all along the pcb trace. LeakSeeker 82B has the resolution to find the defective component. Touch pads along the trace, and LeakSeeker beeps highest in pitch at the defect's pad. Now you can locate a shorted part only a quarter of an inch away from a good part. Short can be from 0 to 150 ohms

LeakSeeker 82B

www.eds-inc.com

Laser Insight

A couple of issues back, I described a simple dye cell you could use in conjunction with the nitrogen laser that was described earlier this year. This time, I want to show you another approach to exciting a dye cell, using instead a flashlamp.

If you have a still camera, there's a good chance that at some time you have used a flash attachment and taken pictures in dim lighting situations. These camera flash units can put out quite a bit of optical power, and I have done some experiments with flash units on various dyes, with some quite interesting results.

Did you know, for instance, that the dye found in washing powder fluoresces in the blue/green region of the optical spectrum? You can easily see this if you put a small quantity of dry washing powder in a shallow dish (use the kind of powder that has the blue specks in it), and go into a dark corner of your house. When your eyes have become dark-adjusted, take a camera flash and hold it in contact with the dish, such that the washing powder is exposed to the light when the flash is fired. Don't look at the dish when firing, because when you remove the flash unit, you will want to be able to see the afterglow of the dye (Figure 15-1). The fluorescence doesn't last long, so you have to be fairly quick to expose the powder, then remove the flash unit. You'll see that not just the blue specks glow!

I suspect that the dye involved here is one of the Coumarin variety, but none of the washing powder manufacturers will tell me. In

any case, this dye is worthy of investigation as a laser dye, and I want to propose here that the system I am about to describe may be used to excite the dye, thereby forming a simple pulse-pumped dye laser.


This is only an experiment, I haven't tried it myself yet, so I cannot guarantee that it will work, but it will make a very interesting challenge. So, you pioneers out there, test your ingenuity, build this system, and make it work. Share your achievements with all our readers. There are no prizes, just the satisfaction of achieving something no one has done yet. Who knows? We may be looking at a whole new breed of laser system ...

To dissolve the dye and separate it from the soap is the first challenge, because the dye solution will be a weak transparent color, and must not be contaminated by soap or water. Some of the solvents mentioned in the previous dye laser article may be tried. I suggest trying methanol first.

When you dissolve the dye, try to use fresh solvent, and if you can get it, use spectrophotometric grade. If you use solvent that's been sitting around for a while, it may have become contaminated by water. Most alcohols will pull water in from the air and quickly become saturated, rendering them useless for laser work.

If you have an old camera flash unit you can afford to sacrifice, you can try to convert it into a small laser. You'll have to disassemble the unit and modify the flash, because you need to mount a small glass tube parallel to

Figure 15-1. Exciting the powder with a camera flash.

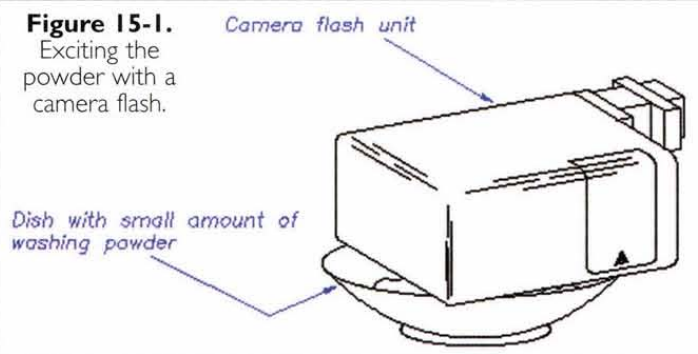


the flashlamp (Figure 15-2).

Remove the existing lens carefully, because you will need to replace it. Careful with the reflector too, it is very thin and fragile. Drill a hole through the side of the flash unit as close to the lamp as you can without touching it or the wiring to it. This will provide maximum optical coupling into the glass tube when it is mounted. As flash units vary widely in their construction, I'm using a simple type for illustration only. Your unit may be different, but you should follow the same basic modifications.

The glass tube running parallel to the flashlamp should be approximately the same size as the flashlamp itself, and should extend about 1/8"-1/4" beyond the flash housing on both sides.

Find a piece of 3/8" thick plex-

Figure 15-2. Modifying the camera flash.

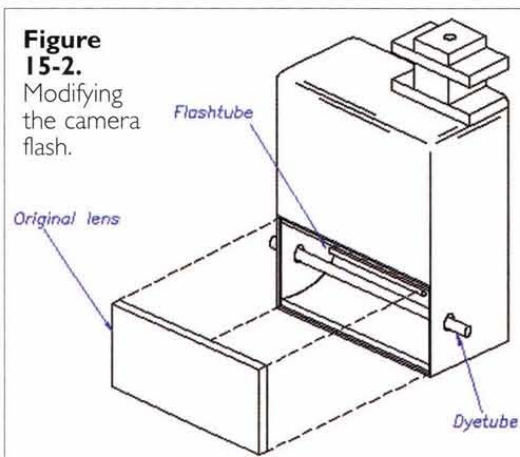

iglass, and make two blocks as shown in Figure 15-3. The only dimensions I will give here are for the thickness of the material. Other dimensions will vary, depending on your flash unit and glass tube. Drill the hole in the block for a snug fit around the glass tube. You will need to epoxy the glass into the blocks to prevent loss of dye solution, and epoxy the blocks to the side of the flash unit. Keep the glass tube approximately centered between the blocks, and make sure the dye entry and exit holes are not plugged with epoxy, and that the glass tube does not obstruct the holes.

Look at the enlarged section in Figure 15-3 for details of the tube placement. Put a bead of epoxy around the glass tube/Plexiglass interface, and a thin layer on the flash case, and hold the assembly together with tape or rubber bands until the epoxy sets. Figure 15-4 shows the assembly.

It is very important to get the two blocks as parallel as possible, as they will form the support for the end mirrors of this laser. Since

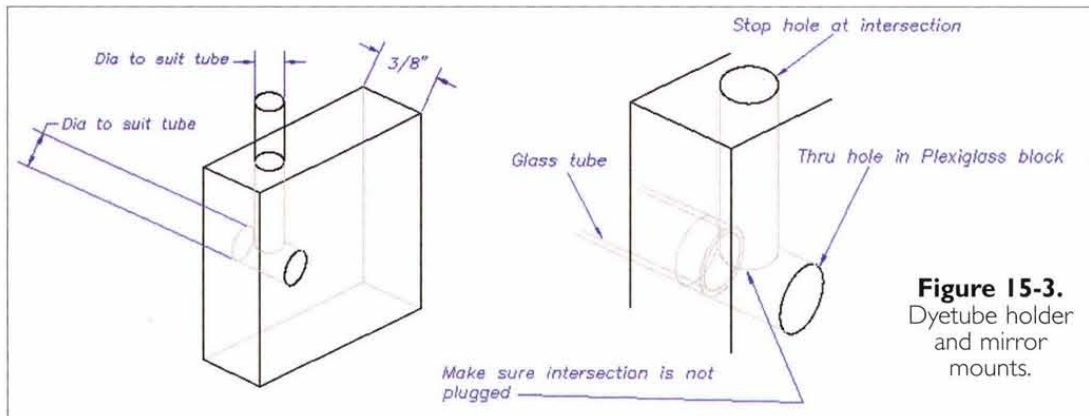


Figure 15-3. Dyetube holder and mirror mounts.

this is such a small laser, there cannot be any adjustments on the end mirrors. If there is a slight misalignment, the laser may still work, but at reduced output.

If you have some small pieces of first-surface mirror available, now you can put them to good use. If not, you may have to sacrifice one. Epoxy a piece of first-surface mirror to one block, so that the hole in the block is facing the silvered surface of the mirror. Place a bead of epoxy around the mirror, making sure to fill every small crevice. Be careful not to get epoxy on the mirror surface that faces the glass tube, though.

If you look down the opposite end of the glass tube, you should see your eye reflected in the piece of mirror epoxied to the far side. On the other end of the tube, epoxy a small piece of plain microscope slide.

When the epoxy has set, fit the

glass tubes with some flexible plastic tubing to serve as a dye feed. The flexible tubing should be a snug fit around the glass to minimize leakage. Get two glass jars, and partly fill one of them with plain solvent. Follow the arrangement in Figure 15-5 to siphon the solvent back and forth between the jars to make sure there are no leaks. When the upper jar is almost empty, reversing the positions of the jars should allow the solvent to flow in the opposite direction. If you make the two flexible tubes the same length, you'll be able to control the flow much easier.

You should adjust the heights of the two jars until you get a slow uniform flow in each direction. Use books or pieces of wood as spacers. The flow should be enough to cause a change of liquid volume during the flash recharge period. The flow should not be turbulent,

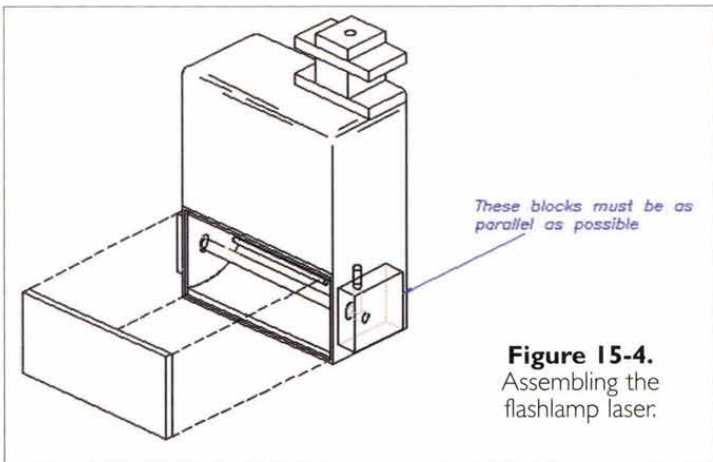


Figure 15-4.
Assembling the flashlamp laser.

as this will retard laser action.

If you have no leakage problems with the dye solvent, the next thing to do is replace the front lens on the flash unit. Before you do however, you should cover the inside face of the lens with a couple of layers of kitchen foil, shiniest

side out. This will prevent the flash from interfering with any testing or experiments you may be doing, and it will also couple more of the emitted light back into the dye tube. Be careful when you add the foil. Don't let it get too far inside the flash housing, or you run a risk of

www.gatewayelec.com

(Electronically Speaking, Gateway's Got It!)



MAIL ORDERS CALL TOLL-FREE 1-800-669-5810

Circle #70 on the Reader Service Card.


LASERS & ACCESSORIES

HELIUM NEON LASERS

- ☒ Complete Systems
- ☒ Plasma Tubes
- ☒ Power Supplies

ACCESSORIES

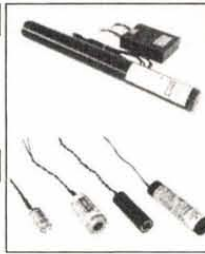- ☒ Optics
- ☒ Electro-Optics
- ☒ IR Viewers
- ☒ Books & More



MEREDITH
INSTRUMENTS

Phone: 623-934-9387 • Fax: 623-934-9482

DIODE LASERS

- ☒ Visible / IR
- ☒ Complete Modules
- ☒ Collimating Optics
- ☒ Drive Circuits

WEBSITE:

WWW.

mi-lasers.com

Circle #69 on the Reader Service Card.

Stepper Motor Book

Easy Step'n

NEW

- For the experimenter.
- Determine surplus stepper motor specs using simple easy to build test equipment.
- Design and build microcontroller-based control systems (flow charts and code examples included).
- Design and build stepper motor driver circuits.
- Analyze the mechanical characteristics of stepper motor-driven devices.
- The book is full of experiments, circuits and code.
- 8.5x11 format. 205 pages. \$34.95

Table Of Contents And Ordering Information On Web Site

<http://www.stepperstuff.com>

SQUARE 1 ELECTRONICS

P.O. Box 501, Kelseyville, CA 95451

Voice (707) 279-8881 Fax (707) 279-8883

We have been selling on the Internet since 1996. We will ship the day we receive your order or the next business day.

PICmicro® PIC16F87x Series and ICD Book

Easy Debug'n

NEW

- Features of PIC16F87x microcontrollers
- In-circuit debugging using Microchip ICD
- Companion for our PIC'n book series
- 8.5x11 format.
- 72 pages. \$12.95

Table Of Contents And Ordering Information On Web Site

<http://www.sq-1.com>

PICmicro® BOOKS

LEARN ABOUT MICROCONTROLLERS

- | | |
|--|---------|
| Easy PIC'n - Beginner | \$29.95 |
| <ul style="list-style-type: none"> • Programming Techniques • Instruction set, addressing modes, bit manipulation, subroutines, loops, lookup tables, interrupts • Using a text editor, using an assembler, using MPLAB • Timing and counting (timer 0), interfacing, I/O conversion | |
| PIC'n Up The Pace - Intermediate | \$34.95 |
| <ul style="list-style-type: none"> • Serial communication - PICmicro to peripheral chips • Serial EEPROMS • LCD interface and scanning keypads • D/A and A/D conversion - several methods • Math routines | |
| PIC'n Techniques - Intermediate | \$34.95 |
| <ul style="list-style-type: none"> • 8-pin PICmicros • Timer 1, timer 2 and the capture/compare/PWM (CCP) module • Talking to a PICmicro with a PC using a terminal program • Test equipment and data logger experiments | |
| Serial PIC'n - Advanced | \$49.95 |
| <ul style="list-style-type: none"> • Synchronous - bit-bang, on-chip UART, RS-232 • Asynchronous - I2C (Philips Semiconductor) • SPI (Motorola), Microwire (National Semiconductor) • Dallas Semiconductor 1-Wire bus | |

PICmicro and MPLAB are trademarks of Microchip Technology Inc.

Table Of Contents And Ordering Information On Web Site

<http://www.sq-1.com>

shorting to the flash tube. Glue it to the lens so that it cannot fall off or move around after you reassemble the flash unit.

If you have a military background, you may have used (or heard of) an infrared (eyesafe) laser rangefinder. These devices use an arrangement very similar to this set-up, but instead of using a dye solution, they use an Erbium-doped YAG rod as the laser medium. Erbium is one of the so-called rare-earth materials. This particular type of laser puts out an infrared beam at 1530-1660 nm. This wavelength is less likely to cause retinal damage to the eyes, and is favored for the use of laser rangefinders used by the military. This wavelength is generally referred to as the eye-safe region of the infrared. You may want to try other materials too. There are dyes in many household products, and some of these may fluoresce if driven hard enough. The difficult part is trying to extract the dye in its purest form from the host material.

Have fun with this project, but remember, it is a laser no matter how low the output power is, and it is still dangerous. The power supply in the flash unit is quite powerful, and can give a nasty shock if you aren't careful.

Next month, I'll discuss a few methods of aligning a laser, and give a few tips and tricks that I have learned over the years. **NV**


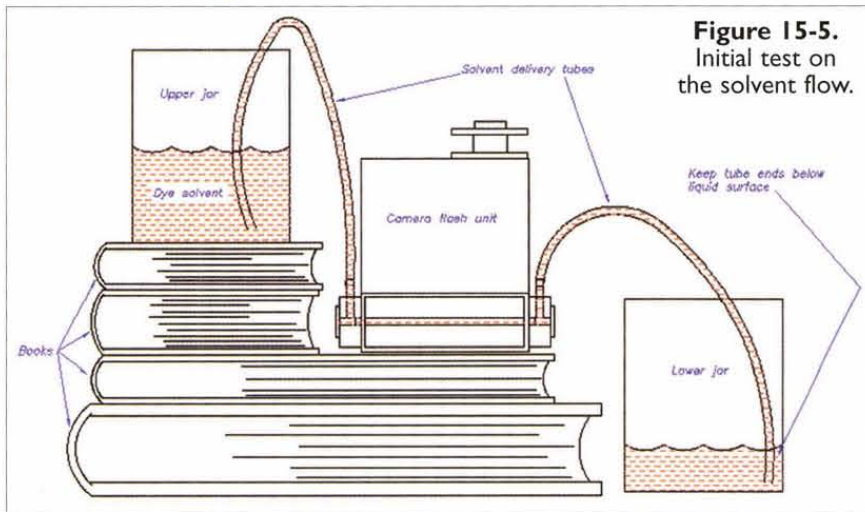


Figure 15-5.
Initial test on
the solvent flow.

Earn Your Degree at Home!

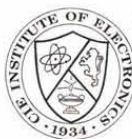

Cleveland Institute of Electronics offers comprehensive yet affordable independent study training programs in electronics and computer technology. Experience a step-by-step teaching method designed specifically for the independent study student.

Build on what you already know!

You may be eligible to apply for advanced standing in CIE's A.A.S. Degree Program based on your previous military training or academic history. If you're like most readers of this magazine, your electronics background can help you receive your degree in less time than you think!

Choose from many programs!

Earn an Associate in Applied Science in Electronics Engineering Technology or a Diploma from one of our other high tech programs. All the lab equipment and instructor support you need to succeed is included with every program.

Name _____	
Address _____	
City _____	
State _____ Zip _____	
Phone _____	ANV03
Send for a FREE Course Catalog	
CIE: 1776 E. 17th, Cleveland, OH 44114	

Call (800) 243-6446 or visit www.cie-wc.edu for a **FREE** Catalog!

FCC Course with Certificate

A Powerful 19 Lesson Self-Study Program on one CD!

After completing this course you will be ready to take the FCC examination for a General Radiotelephone Operator License.

The General Radiotelephone Operator License is required to adjust, maintain or repair any FCC licensed radiotelephone transmitters in the aviation, maritime and international fixed public radio services. It is issued for the lifetime of the holder.

19 FCC Lessons on CD ROM

Every lesson is presented in a clear and easy-to-understand format which makes learning this material fun and easy. After each lesson you'll take an exam. You can take it on-line or fill out one of the answer sheets we provide and mail it. After you finish the 19 lessons we'll send you a Certificate of Completion from Cleveland Institute of Electronics that's suitable for framing.

CIE Instructor Assistance with Priority Grading

Use our toll-free hot line to talk with our faculty if you ever need assistance with your lessons. Your exams will be graded and sent back to you within 24 hrs.

(800) 321-2155 or visit www.ciebookstore.com

CIE Bookstore: 1776 E. 17th, Cleveland, OH 44114
CA, HI & OH residents must add sales tax. \$5.25 shipping.



Weeder Technologies

www.weedtech.com
DATA SHEETS

RS-232 Stackable

1710-B Brighton Cove, Ft Walton Beach, FL 32547

850-863-5723

Digital I/O Module - 14 I/O channels individually configured for input or output. Turn on/off relays. Sense switch transitions, button presses and 4x4 matrix decoding using auto-debounce and typematic repeat with adjustable delay. One-shot pulse output. **\$59**

Analog Input Module - 8 single-ended or 4 differential inputs. Self-calibrated, 12-bit ADC, reads voltages from 0 to 4095 mV. High & Low alarm trip-points for each input. **\$69**

Analog Output Module - 4 outputs that span -10 to +10 volts using 12-bit DAC. Built-in ramp generator, software calibrated, user selectable POR defaults for each channel. **\$89**

Stepper Motor Driver - Directly drives a unipolar stepper motor rated up to 30VDC @ 2A. Self-generated S-curve accel/decel profiles provide smooth start and stop motion. Software programmable ramp-rate, velocity and idle current. Single-phase, dual phase, & half-step drive modes. 24-bit absolute motor position counter. **\$69**

Pulse Counter/Timer - Read frequency from 0.50000 Hz to 1,500,000 Hz using floating decimal point and 5-digit resolution throughout range. Measure period, RPM, duty cycle, pulse length, the velocity of a projectile using a pair of trip wires, 24-bit pulse count accumulator for event counting. **\$79**

Plug end-to-end
Stack 32 modules on the same RS-232 cable.

Solid State Relay Module - 5 opto isolated relays can be wired directly to existing low-current buttons and switches to provide software control of their operation. Built-in event sequencer. **\$69**

Electro Mavin
Great Buys - Great Products - Great Gadgets
Check Out Our Great WebSite at

<http://mavin.com>

For Computer Items, Hobbies Projects,
Microwave Goodies and Some of the
Greatest Prices on the Web....

800-421-2442 or FAX 310-632-3557

E-Mail

john@mavin.com or sean@mavin.com

ENTER THE NUTS & VOLTS MSP430

GADGET-O-RAMA!

MSP430



Nuts & Volts

**TEXAS
INSTRUMENTS**

Ultra-Low-Power Flash MCU Design Contest

Got a cool gadget, nifty toy or killer robot, but don't know what to do with it? Well, how about entering it in the MSP430 GADGET-O-RAMA! You could win loads of great prizes, including a grand prize of \$5,500! Any gadget equipped with a Texas Instruments MSP430 ultra-low-power Flash MCU is eligible to compete. (For those entering robots, please remember to switch settings to "Good" from "Evil" before submission.) Don't let the mad scientists have all the fun – enter the MSP430 GADGET-O-RAMA today!

For complete contest rules, prizes and entry form, visit
www.ti.com/gadgetorama2002

MR119R © 2002 TI

Nuts & Volts Magazine/AUGUST 2002 **57**

News Bytes

LULU ENTERPRISES ANNOUNCES LULU TECH CIRCUS — A THREE-DAY TECHNOLOGY EVENT

Lulu Tech Circus to be a place where Technology Lovers can Engage, Learn, and Interact in a Unique, Cutting Edge, and Entertaining Environment.

Lulu Enterprises announces Lulu Tech Circus, a three-day, multi-

ring technology event targeted at technology enthusiasts, hobbyists, user groups, and IT professionals who work and play in arenas as diverse as super-computing, animation, robotics, and wireless communications.

Lulu Tech Circus events will be scheduled throughout North America. The first Lulu Tech Circus event will be held in Raleigh, NC, from September 27-29, 2002.


"Lulu Tech Circus can meet the needs of the 'inner geek in all of us'"

www.SMDRework.com

Your SMD Rework Specialist
800-394-1984

MPU and PLD/FPGA Tools

**NEW!
From AWC**

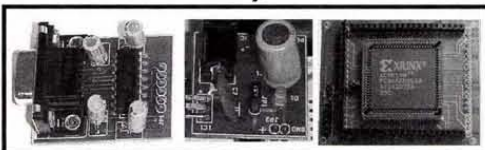

Prototyping Tools/Kits

- ▶ Programmable logic prototyping kits (Xilinx and Altera)
- ▶ RS-232 prototype boards
- ▶ Power supply kits
- ▶ MPU/Internet gateway software

PAK Coprocessors

- ▶ 32-bit floating point math (PAK-II)
- ▶ 8 channels of PWM/Pulse I/O (PAK-V, VII, VIII)
- ▶ Read PS/2 keyboards or mice (PAK-VI)
- ▶ Floating point A/D (PAK-IX)
- ▶ Data sheets and projects online


Check out our tools and PAK coprocessors for Basic Stamp, PIC, AVR, 805x, 68HC11, or any MPU. Our prototyping tools save your time and our PAKs add powerful features to your designs. Visit our Web site now for free tutorials, tools, and projects!

AWC
310 Ivy Glen
League City, TX 77573
(281) 334-4341
(281) 754-4462 (fax)

www.al-williams.com/awce

\$62 PCBs

And our layout software is **FREE!**

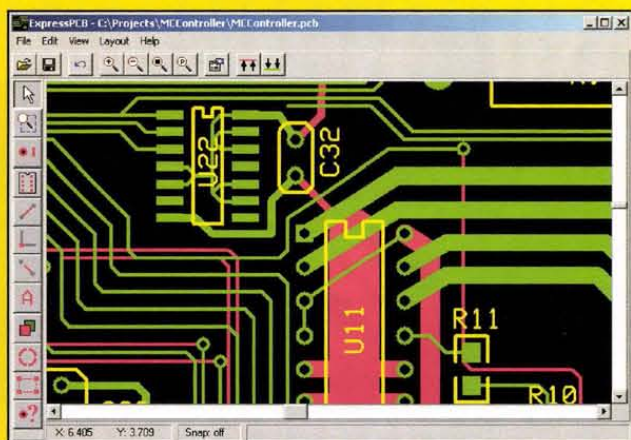

Download our **FREE** layout software
Design your two-sided plated-through PCB
Send us your design with just a click
Receive your boards in a few business days

Select our MiniBoard service and get three top quality
2.5" x 3.8" PCBs for \$62 — shipping included!



expresspcb.com



Professional 10 HOUR RECORDER
"BUILT LIKE A BATTLESHIP"

Factory Direct

SPECIAL Nuts&Volts Price ..

\$159

- Heavy duty commercial recorder — NOT improvised from consumer models
- 12, 14, and 16 hour models also available
- BUILT-IN voice activation (add \$30)
- Applications information included
- Dimensions: 11.5 x 7.0 x 2.75"

FREE AD-PAGE SPECIAL EQUIPMENT CATALOG!

COD's OK. Sorry, no credit cards. Free catalog USA only; other countries \$5. Price includes UPS to 48 States on Pre-Paid Orders

Viking Systems International 100 North Hill Drive #42, Brisbane, CA 94005
Phone (415) 467-1220 • Fax: (415) 467-1221 • Web: www.vikingint.com

Circle #87 on the Reader Service Card.

EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- www.m2l.com

Fast - Programs 27C010 in 23 seconds

Portable - Connects to PC Parallel Port

Versatile - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

Inexpensive - Best for less than \$200

- Correct implementation of manufacturer specified algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters listed below.

Available Adapters

EP-PIC (18C5x, 81, 62x, 71, 84)	\$49.95
EP-PIC64 (18C62, 5, 72-4)	\$39.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751, C51)	\$39.95
EP-11E (68HC11 E/A)	\$59.95
EP-11D (68HC11D3)	\$39.95
EP-16 (16bit EPROMs)	\$49.95
EP-Z8 (Z80E02, 3, 4, 6, 7, 8)	\$39.95
EP-SEE2 (93x24x, 25x, 85x)	\$39.95
EP-750 (87C750, 1, 2)	\$59.95
EP-PEEL (IC22v10, 18v4)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95

Many Other Adapters Available

M2L Electronics

970/259-0555

Fax: 970/259-0777

250 CR 218

Durango, CO 81301

CO orders please add 7% sales tax

<http://www.m2l.com>



Circle #88 on the Reader Service Card.

Mr. NiCd

SUMMER SPECIALS!

THE BEST BATTERIES IN AMERICA!

Packs & Charger for YAESU FT-50R / 40R / 10R:

FNB-40xh Slim-NMH	7.2v	650mAh	\$41.95
FNB-47xh (NMH)	7.2v	1800mAh	\$49.95
FNB-41xh (5w NMH)	9.6v	1000mAh	\$49.95

For YAESU FT-51R / 41R / 11R:

FNB-38 pack (5w)	9.6v	700mAh	\$39.95
FNB-26 pack (NMH)	7.2v	1500mAh	\$32.95
FNB-27s (5w NMH)	12.0v	1000mAh	\$45.95

For YAESU FT-530 / 416 / 816 / 76 / 26:

FNB-11 pack (5w)	12.0v	600mAh	\$24.95
FBA-10 6-Cell AA case			\$14.95

Packs for ALINCO DJ-580 / 582 / 180 radios:

EBP-20ns pack	7.2v	1500mAh	\$29.95
EBP-22nh pk (5w)	12.0v	1000mAh	\$36.95
EDH-11 6-Cell AA case			\$14.95

For ICOM IC-21A / T22-42A / W31-32A / T7A:

BP-180xh pk (NMH)	7.2v	1000mAh	\$39.95
BP-173 pack (5w)	9.6v	700mAh	\$49.95
For ICOM IC-W21A / 2GXAT / V21AT (Black or Grey)			
BP-132s (5w NMH)	12.0v	1500mAh	\$49.95

For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:

BP-83 pack	7.2v	600mAh	\$23.95
For ICOM 02AT etc & Radio Shack HTX-202 / 404:			
BP-8h pack	8.4v	1400mAh	\$32.95

For KENWOOD TH-79A / 42A / 22A:

PB-32xh pack (NMH)	6.0v	1000mAh	\$29.95
PB-34xh pack (5w NMH)	9.6v	1000mAh	\$39.95

For KENWOOD TH-78 / 48 / 28 / 27:

PB-13 (original size)	7.2v	700mAh	\$26.95
For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:			
PB-6xh (NMH, w/chg plug)	7.2v	1200mAh	\$34.95

Mail, phone, & Fax orders welcome! Pay with Mastercard / VISA / DISCOVER / American Express

Call 608-831-3443 / Fax 608-831-1082

Mr. NiCd - E. H. Yost & Company

2211-D Parview Road, Middleton, WI 53562

CALL OR WRITE FOR OUR FREE CATALOG!

Cellular / Laptop / Videocam / Commercial & Aviation packs tool

E-mail: ehyost@midplains.net

to get out and share experiences, advancements, and ideas," said Bob Young, CEO, Lulu Enterprises (also, co-founder of Red Hat, Inc.). "From Princeton mathematicians to the guy who keeps your office network running — the technology enthusiast market is a vast and underserved one."

"Let's face it, bass fishermen are better served by user-driven events than the much larger and more important technology user community. There are lots of technology events, but they are just too focused on the needs of the vendors and exhibitors to be much use or fun for the typical technology user. The mission of Lulu Tech Circus is to bring together the extraordinary people, innovations, and concepts that define technology culture today," said Young.

Plans for the first edition of Lulu Tech Circus include a wide variety of live and interactive experiences from which attendees can design their personalized days at the Circus — everything from master classes with animation experts and digital film screenings, to networking certification

Continued on Page 87

www.gatewayelex.com

(Electronically Speaking, Gateway's Got It!)



MAIL ORDERS CALL TOLL-FREE 1-800-669-5810

Circle #93 on the Reader Service Card.

Easy-to-Use Seetron Serial LCDs

Interface a sharp LCD display to your BASIC Stamp® or other micro-controller project with ease. No-solder wiring harnesses and easy mounting kits available too. See www.seetron.com today.


- 3.2 x 1.4 in. supertwist LCD
- 2400/9600 baud serial
- Low (≈2mA) current draw
- Popular for use with BASIC Stamps®

\$45
BPI-216N



- 3.2 x 2 in. backlit LCD
- 1200-9600 baud serial
- Advanced protocol, 4 switch inputs
- EEPROM for configuration settings
- Favorite for OEM applications

\$49
ILM-216L

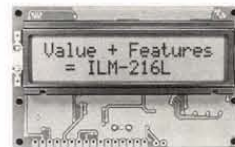

- 3.2 x 1.4 in. graphics LCD
- 2400/9600 baud serial
- Font and 15 screens in EEPROM
- Easily draw points, lines, screens

\$99
SGX-120L



- 3 x 2 in. supertwist LCD
- 1200-9600 baud serial
- ESD-protected, 4x4 keypad input
- Store up to 95 screens in EEPROM

\$119
TRM-425L



Scott Edwards Electronics, Inc.

1939 S. Frontage Rd. #F, Sierra Vista, AZ 85635
phone 520-459-4802 • fax 520-459-0623
www.seetron.com • sales@seetron.com

More displays available,
including bright VFDs.
See www.seetron.com

Circle #92 on the Reader Service Card.

P.C. MOUNT TRANSFORMER

120VAC in. 12.6V @ 800mA or 6.3V @ 1.6A out. Signal #PC-12-800. Size 1-7/8"W x 1-1/2"D x 1-5/8"H. Specs included.
98N007 \$3.95 each

UV Detector Subassembly

Programmable. Made by Esterline Instrument Corp for Bio-Rad. Part Number 201CE. Unit consists of a Deuterium Lamp, Beam splitter, Lens that couples to sample chamber, (not included), and stepper motor driven mirror assembly which balances the sample output to the reference output and produces a measurable value. Unit includes power supply for lamp, stepper motor and pc board 9-1/2" X 14" with 3 plug-in daughter boards. Units are new in box with final test sheets. Connections for power, serial port hardware control, channel 1 and 2 analog outputs. 11-3/4"W X 9-1/2"H X 19"D, weight 32lbs. Believe the units were used to sample air quality. Operates on 100-240VAC 50/60Hz
22Z003 \$64.95 each



0.015µF 6.5KV DC CAP 95P0175 20 for \$14.95

SEALED LEAD ACID RECHARGEABLE BATTERY

12V, 5A; 3 1/2"W x 2 3/4"D x 4 1/4"H; 4 lbs.; Panasonic LC-R125PI. Downloadable spec sheet with photo on our web site.
22E010 \$9.95 each

RESISTOR RIOT

1/8, 1/4, 1/2 Watt, power, precision, fixed, adjustable, etc. Thousands of pieces.
20P003 5 Lbs. - \$9.95

CAPACITORS BY THE POUND

A good variety of all kinds of caps.
20P004 5 Lbs. - \$9.95

50-LB. CARE PACKAGE

Surplus goodies from Silicon Valley. This is not junk, just material we've acquired in quantities too small to catalog. Assortments may include ICs, caps, connectors, bearings, diodes, hardware, circuit boards, cables. Weird and wonderful stuff. Most folks are happy with the assortments we send and we often get re-orders. Try one.
92U034 50 Lbs. \$49.95



GIANT FRESNEL LENS

Build a solar furnace with one of our giant Fresnel lenses the size is approx 31" x 41". The material is a plastic sheet approx 1/16" thick. NOTE: Shipping Via Airborne Express to the lower 48 states is \$40.00, inquire about shipping to other locations
22L004 \$89.95 each

STEPPER MOTOR CONTROLLER IC

This surface-mount IC may be used with either two-phase bipolar or four-phase unipolar motor configurations. Application notes and spec sheets included.
L6506D-S 10/\$14.95

MINIATURE BRASS PAD-LOCKS

Two keyed differently with 3 keys each. 3/4"W x 1-1/4"H X 5/16"D
22Z005 \$1.99 pair



alltronics.com

Mail Orders: P. O. Box 730, Morgan Hill, CA 95038-0730
Phone: (408) 847-0033 • Fax: (408) 847-0133
Download our Catalog: <http://www.alltronics.com>

Dealers Welcome by Appointment. Visa, M/C, Amex Accepted. All Sales Final. California Residents Add Sales Tax. Shipping Additional on All Orders. Prices Good 60 Days from Date of Publication and Subject to Change without Notice.



Circle #90 on the Reader Service Card.

Celebrating our 19th Year Of Service !!

VISIT US AT WWW.UNICORNELECTRONICS.COM

What Do We Have ?

- | | | |
|------------------------|----------------|---------------|
| • TTL | • 74LS | • 74C |
| • EPROMS | • EEPROMS | • PAL's |
| • GAL's | • CMOS | • Z80 |
| • Linear | • Generators | • 8000 series |
| • 6500 series | • 6800 series | • Capacitors |
| • Oscillators | • Connectors | • Crystals |
| • Trimpots | • I.C. sockets | • Switches |
| • Diodes | • Kits | • Tools |
| • Vises | • Laser Diodes | • LED's |
| • Vises | • Transistors | • Resistors |
| • And much, much more! | | |

- Order Line — (800) 824-3432 • International — (724) 495-1230 • Fax Orders — (724) 495-7882
- Technical Support — (724) 495-1231 • \$25.00 Minimum Order • UPS 3 day, Blue, Red, & Fed. Ex. Shipping Available (Call for charges) • PA Res. Add 7 % Sales Tax • Open Mon-Fri 9:00 AM - 5:00 PM (EST) • Corporate Accounts / Quantity Discounts Available • We accept M/C, VISA, Discover & AMEX with no surcharge • Call For FREE Catalog (\$2.00 Outside U.S.)
- We Carry A Complete Line Of Electronic Components • Email - unielec@aol.com

Visit us on the web ! www.unicornelectronics.com

FREE SHIPPING!! on pre-paid orders

Unicorn Electronics
1142 State Route 18
Aliquippa, PA 15001

Circle #89 on the Reader Service Card.

Nuts & Volts Magazine/AUGUST 2002 59

Build the Cook-Out Companion

By Anthony J. Caristi

The Cook-Out Companion allows you to play your stereo system indoors while listening to the same music outside. It's a wireless system that doesn't require you to set up speakers in your backyard.

Many of us like to cook lunch or dinner in the backyard, or have a barbeque with friends during the nice weather. Usually music is part of the scene. But suppose you are not exactly fond of what is being heard on commercial radio stations, and would much prefer to hear your favorite CDs? The answer to this is to build the Cook-Out Companion, which allows you to play your stereo system indoors while listening to the same music outside. It's a wireless system that doesn't require you to set up speakers in your backyard.

This method of transmitting music is accomplished by taking advantage of a miniature, low-power, VHF oscillator chip that operates in the FM broadcast band. Its power is low enough to be perfectly legal, and it will not disturb your neighbor's FM reception. Your music is heard on any portable FM receiver(s) that you bring outside. Of course, you will be able to hear just monaural, and not stereo sound.

Another use of this miniature FM transmitter is to use it to transmit voice and other sounds such as those in the bedroom of a sleeping baby or toddler. This is accomplished by adding a microphone to the circuit. This might come in handy if you have a small child and wish to listen in when he or she is sleeping in the bedroom.

A common nine-volt transistor radio battery powers the circuit. Current draw is a scant four milliamperes, which allows many hours of pleasant listening.

ABOUT THE CIRCUIT

Refer to the schematic diagram. Power to operate the circuit is provided by a common nine-volt transistor radio battery. Other DC sources that supply at least seven volts, and up to 12 volts, may also be used. The battery is used to drive U1, a fixed five-volt linear regulator IC, which powers the oscillator.

The heart of the circuit is U2, a six terminal, miniature, surface mount integrated circuit developed by MAXIM. This is a self-contained VHF oscillator chip that contains the necessary elements of a voltage controlled Colpitts oscillator. The only external tuning component is the inductor, L1. A built-in varactor is included on the chip so that frequency control and modulation is easily accomplished by applying a DC plus AC (audio) voltage to pin 3.

Choosing the correct value of inductance sets the operating frequency to within the FM transmitting band, 88 to 108 MHz. In this circuit, an inductor with a value of 390 nanoHenries (0.39 microHenries) allows the frequency of operation to occur near 100 MHz. R6 — the tuning control potentiometer — provides adjustment of the operating frequency within the FM broadcast band.

Since U2 is a voltage-controlled oscillator (VCO), any modulation present on pin 3 of the chip will cause its frequency to shift in accordance with the amount of voltage variation. The audio signal is provided by either the stereo system, or the output of the microphone (if so equipped).

The audio is presented to U2 through capacitor C5, where it is added to the DC bias provided by tuning potentiometer R6. The AC sig-

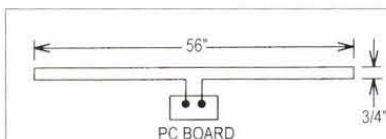


Figure 3. A half-wave folded dipole antenna, driven by C7 and U2 pin 4. May be used to transmit the RF signal.

Figure 1. Printed layout of the PC board shown full size, as seen from the copper side.


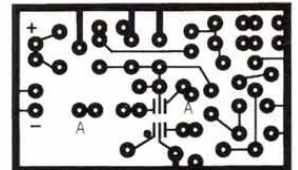


Figure 2. Parts placement shown from the component side of the board. U2 is placed on the opposite side.

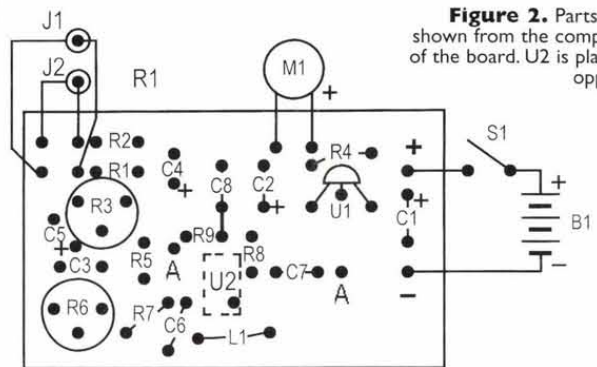

nal — riding upon the DC bias — will frequency modulate the oscillator. A nearby FM receiver, tuned to the carrier frequency, will be able to detect the modulation and recover the audio.

The output circuit of the chip consists of a differential output amplifier that is driven by the oscillator. This provides isolation between the two sections of the circuit and offers a differential output mode (pins 4 and 6) that can be used to drive a balanced antenna. Alternatively, a single wire, driven by one of the output terminals of the chip, can also be used as a quarter-wave whip antenna.

CONSTRUCTION

Since this circuit operates in the VHF band, printed circuit construction is mandatory. Figure 1 illustrates the printed layout of the PC board, shown full size as seen from the copper side of the board. An etched and drilled board is available from the source indicated in the Parts List.

The first component that should be mounted to the board is U2, the oscillator chip. This is a surface mounted miniature component that is soldered to the bottom of the board. Use the following procedure:

1. Gently clean the PC board using a steel wool pad. Be sure there are no contaminants, opens, or short circuits at or near the printed wiring. Pay special attention to the spaces between the copper pads for U2. Rinse and dry the board thoroughly.

2. Locate pin 1 of U2, which may be indicated by a small dot on the top side of the chip. Pin 1 will always be in the lower left-hand corner of the chip as you hold it so that you can read the ID lettering of the part. Pin 1 of the corresponding copper pattern is indicated by a small dot.

3. Place U2 in position, directly over and centered among the foil pattern.

4. Using a low-powered pointed soldering iron tip, carefully apply heat and solder between pin 1 of the module and the foil pad. Allow the

Build the Cook-Out Companion

melted solder to flow, ensuring a good connection. CAUTION: Do not use too much heat or too much solder; to do so may cause the foil to lift off the board or form a short circuit between adjacent foil pads.

5. Examine the assembly to be sure that all terminals of U2 are in the proper position over the pads. If not, repeat Step 4.

6. Solder the remaining terminals of U2 as described in Step 4.

7. Examine the assembly very carefully to be sure that all connections are solid, and there are no short circuits between adjacent foil pads.

The remaining through-hole components may be inserted in the board and soldered in place as indicated in Figure 2. Use very short lead lengths for L1, C6, and C8. Be sure to observe proper orientation for U1. An error here will result in an inoperative circuit and possible damage to U1 and U2.

Be sure to observe proper polarity of the electrolytic and tantalum capacitors, which are plainly marked on the body of the part. Follow Figure 2, which shows how these components are mounted to the board.

Note: If the microphone part of the circuit is not going to be used, do not install M1, R4, and C4. If the circuit is to be used as a microphone transmitter only, do not install R1 and R2. The electret microphone cartridge is polarized; be sure to observe proper polarity as indicated in the schematic diagram and Figure 2.

Use a clip for the battery. This may be obtained from electronic parts distributors. Alternatively, you can salvage a connector from an old nine-volt battery and solder a red (+) and black (-) wire to the terminals. When doing so, remember that the polarity of the clip will be opposite to that of a battery. When finished, attach a new battery to the clip and use a DC voltmeter to be sure that the polarity of the wiring is correct.

When the PC board is completed, check it carefully for any possible opens, shorts, errors, and bad solder connections. Any joint that is not shiny and smooth is suspect and should be redone by removing the old solder with braid. It is easier to correct mistakes now rather than later on if you discover that your transmitter does not work.

A small enclosure may be used to house the printed circuit board if the quarter-wave antenna option is chosen. The left and right audio connectors and S1 may be mounted to the enclosure. The battery may be

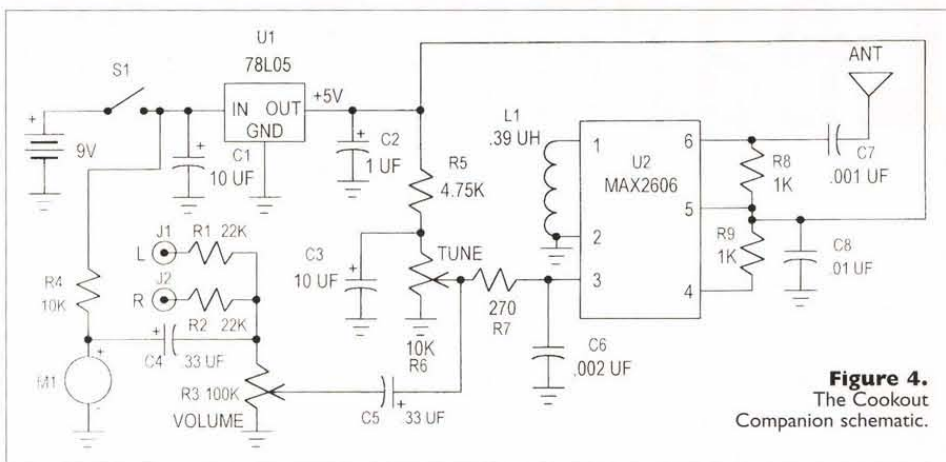


Figure 4.
The Cookout
Companion schematic.

secured inside the enclosure using a suitable battery holder.

ANTENNA

The builder has two options for an antenna. One choice would be to use a quarter-wave whip, composed of a straight piece of stiff wire about 28 inches long and fed from pin 6 of U2 through C7. Another method is to use a folded dipole half-wave antenna as depicted in Figure 3. This is a balanced antenna and is driven by the differential output of U2, terminals 4 and 6 (through C7). Using the dipole version provides twice the available RF driving voltage, and should provide greater operating range.

It is best if the dipole antenna is driven directly by the circuit without any connecting cable. This is accomplished by constructing the antenna on a flat piece of lumber about five feet long, and securing the printed circuit board in the center.

Once the antenna style is chosen and wired to the circuit, the transmitter is ready for test.

CHECKOUT

When you are certain that the circuit is properly wired, connect a source of audio (monaural or stereo) to one or both of the audio input jacks using the proper cable(s). If the microphone version of the circuit is to be tested, no audio source is required.

Clip on a fresh nine-volt battery to the circuit. Alkaline types will provide greater operating time.

Set up a portable FM radio nearby, and tune to the middle of the FM band where there are no broadcast stations operating.

With S1 turned on, adjust the tuning control, R6, until you hear the audio come through to the FM receiver, or you hear just silence if no audio is being applied to the transmitter. In this case, speak into the microphone to produce sound from the receiver. U2 requires a DC voltage level at pin 3 of about 1 to 2-1/2 volts. Adjust the volume control, R3, for best audio fidelity.

Once this adjustment is made, the checkout is complete and you may determine the operating range of the system by separating the FM receiver from the transmitter. Remember that best operating range will be attained when the transmitting antenna and receiving antenna are each oriented in the same direction, for identical polarization.

If you are not able to obtain an RF signal that can be detected by the FM receiver, the oscillator is either not working at all, or its frequency is out of the FM band. Measure the battery voltage to be sure it is at least eight volts. Check the voltage at pin 5 of U2. Normal indication is between 4.75 and 5.25 volts. If not, check U1, C1, and C2.

Check the value of L1. Check all components for the correct value and location in accordance with Figure 2. Examine U2 for solid solder connections, and be sure there are no solder bridges between adjacent foil pads and closely spaced conductors.

A new alkaline battery will provide many hours of use. At the end of battery life, the operating frequency may drift or the audio may become distorted. At this time, replace the battery with a new one. **NV**

- B1** — Nine-volt alkaline transistor radio battery
C1, C3 — 10 uF 25-volt radial electrolytic capacitor
C2 — 1 uF 50-volt radial electrolytic capacitor
C4, C5 — 0.33 uF 16-volt tantalum capacitor
C6 — 0.002 uF 50-volt polyester or mylar capacitor
C7 — 0.001 uF 50-volt ceramic disc capacitor
C8 — 0.01 uF 50-volt ceramic disc capacitor
J1, J2 — Mouser 164-4215 or similar
L1 — 390 nanoHenry inductor, Mouser 70-IM2-.39 or equal
M1 — Electret microphone Mouser 25LM040 or similar
R1, R2 — 22K 1/4 watt carbon resistor
R3 — 100K potentiometer, PC mount
R4 — 10K 1/4 watt carbon resistor
R5 — 4.75K 1/4 watt 1% metal film resistor
R6 — 10K potentiometer, PC mount
R7 — 270 ohm 1/4 watt carbon resistor
R8, R9 — 1K 1/4 watt carbon resistor
S1 — SPST toggle or slide switch
U1 — 78L05 regulator IC
U2 — MAX2606 VHF oscillator IC

Misc: Antenna, audio cables

SOURCES OF SUPPLY

Mouser: 1-800-346-6873; www.mouser.com
Digi-Key: 1-800-344-4539; www.digikey.com

Note: The following parts are available from **A. Caristi, 69 White Pond Road, Waldwick, NJ 07463**. Etched and drilled PC board @ \$12.75, U1 @ \$3.00, U2 @ \$9.75. Please add \$6.00 shipping/handling.

PARTS LIST

Learning RVK-Basic

Part 8

By Bob Van Kannon

RVK-Basic is a free Basic compiler for the Atmel AVR line of microcontrollers. You can download a copy of this compiler from the Nuts & Volts web site (www.nutsvolts.com). With this compiler, you can write and compile very fast, efficient programs for most of the AVR microcontrollers.

In this month's article, we will investigate the question of how to generate Pulse-Width Modulation (PWM) from your AVR microcontroller using RVK-Basic. Also this month, we will investigate the generation and use of random numbers.

What is PWM?

Figure 1 shows how PWM can be generated from a free-running timer. If an eight-bit counter runs freely, its states in time will be 0,1,2,...,254,255,0,1,... This is shown in the picture as a ramp function or sawtooth waveform at the top of the picture. In reality, there is no smooth, continuous ramp inside the microcontroller, just a series of well-defined states of the counter. It is very useful, however, to think of the counter state as being a ramp function.

Superimposed on the drawing of the Timer Counts are horizontal lines representing two different specific counter states. The two I have chosen for purposes of this example are 95 and 190.

I have constructed two possible output waveforms, which correspond to the two different horizontal lines. Both output waveforms are constructed such that the output is low whenever the Timer Counts are greater than the state chosen to produce the PWM. For example, the 95 OUTPUT is low whenever the Timer Counts are greater than 95.

It is obvious that the 95 output produces less time high than low, while the 190 output is high more than it is low. Clearly then, the choice of where we place the horizontal line allows us to change the output waveform. It should be obvious then that by controlling horizontal line position (or PWM Command), we could make the output vary from low all the time to high almost all the time or anywhere in between.

If we were using a microcontroller running on five volts, this would allow us to control the average output voltage from zero to essentially five volts, just by controlling the PWM command.

Why would we want PWM?

DC motors turn when you apply voltage to them. In general, the speed of the motor is proportional to the voltage you apply. That is, if you get X RPM at two volts, you should get 2X RPM at four volts.

When we consider the average voltage of a PWM signal, we will quickly realize that the average voltage is the percentage of the time the PWM spends high times the peak value of the signal. For example, if you're using a 5V AVR and the PWM Command can range between 0 and 255, the average voltage at the output of the PWM can be expressed by:

$$\text{Average Voltage} = (\text{PWM_Command} / 256) * 5 \text{ volts}$$

It is not generally practical to drive a motor from the raw output of

the microcontroller. But it is very practical to buffer the raw output with a transistor that connects to the motor and the motor is connected to a higher voltage rail. In this situation, the PWM command will vary the voltage to the motor between 0 and almost the voltage rail, whatever it may be. A possible way to do this is shown in Figure 2. For the MOSFET, the choice will depend on the voltage and current it must handle, but you will generally want to choose a logic-level FET, perhaps an IRLR3410 might be considered. You might also want to put a small resistor — like 10 ohms — in series with the gate of the FET to damp ringing at the PWM output. A diode could also be placed on the output with its anode to ground to clamp ringing below ground.

Another use for PWM driving a motor is to control the torque from a Torque Motor (a type of DC motor). This is commonly done in automobiles to implement a Cruise Control. With a Torque Motor, the more voltage you supply to it, the more torque it produces and thus pulls harder on the throttle. So by controlling the PWM output of a microcontroller, you could control the speed of your car.

In general, any gadget that can be controlled by voltage can possibly be controlled by PWM. So, if we can easily produce PWM from an AVR chip, we can control lots of things like cars, robotic arms and fingers, battlebots, aircraft, and even spaceships. With PWM, even the sky is not the limit.

How to generate PWM

RVK-Basic has two PWM commands. One statement — PWM — uses the TIMER1 which is available in all AVR chips to produce PWM. TIMER1 is actually a 16-bit timer, but the INIT mode of the statement allows you to set up the timer to be 8, 9, or 10 bits. There is also a PWM2 statement, which uses TIMER2, an eight-bit timer. TIMER2 is not generally available on all chips.

Let's suppose that we want to generate a PWM output of about 400 Hz from a 4 MHz processor, and we want it to be an eight-bit timer. The command to set this up is:

```
PWM INIT 400,8
```

Now to set the PWM to, let's say 50%, we would write

```
PWM THRESHOLD 127
```

We could also use an integer variable to do the same thing.

Prescale Value	8-bit counter	9-bit counter	10-bit counter
1	15.6 KHz	7.81 KHz	3.91 KHz
8	1.95 KHz	977 Hz	488 Hz
64	244 Hz	122 Hz	61.0 Hz
256	61.0 Hz	30.5 Hz	15.25 Hz
1024	15.25 Hz	7.6 Hz	3.81 Hz

TABLE 1

p% = 127
PWM THRESHOLD p%

That's how easy it is to control PWM.

It should be fairly noted that the PWM command cannot generate just any old frequency. The possible frequencies are limited by the prescaler for the counter timer and the clock frequency of the microcontroller. Table 1 is a simple example of what frequencies can be obtained when using a 4 MHz clock for the processor.

The RVK-Basic compiler will choose the prescale value for you that gives the frequency closest to and above the frequency you specify in the PWM INIT statement. To avoid surprises, check the ASM file produced after you compile your program. There the actual output frequency will appear as a comment next to your PWM INIT statement.

The pin for PWM output will vary from processor to processor. RVK-Basic always uses OC1 or OC1A for the PWM output.

A light dimmer

As an example of PWM control, I will write a program to control one LED on a development board. This will work on either the STK200 or STK500 boards.

What the program does is to gradually vary the brightness of the LED from off to on every 1.5 seconds. I have chosen a 2313 processor for this demonstration because it seems to be the smallest available, which has TIMER1.

DEVICE 2313

MHZ 3.68
REVISION RB8.BAS 011202.0-rvk

EQU "B,3","PWMOUT"
MAKEOUT "PWMOUT"


PWM INIT 200,8 '...8 bit counter at 400 Hz...

DO
INCR var
p% = var
PWM THRESHOLD p%
PAUSE 6 '...0.006 * 256 = 1.5 second repetition period..
LOOP

The reader is encouraged to change the INCR statement to a DECR statement and predict what the observable result will be before he actually runs the code on the development board.

The reader is also encouraged to look in the ASM file to see that the PWM INIT statement produces an output frequency of about 244 Hz. Then actually look at the PWM output from the AVR on an oscilloscope and verify its frequency.

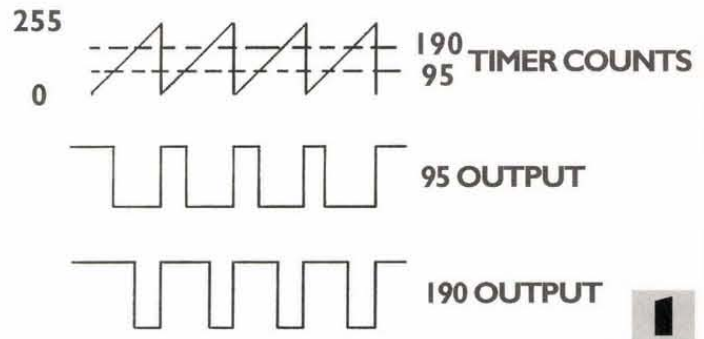The reader could change this program to run on a larger processor, perhaps an 8535, if he has one lying around. If so, don't forget to include an "XMEM OFF" statement for this processor. See RB.TXT for



details. Also remember that OC1A comes out on pin D,5 of the 8535.

It is also very possible to produce PWM in software for situations where you might need multiple PWM outputs. Just set up a timer to free-run at as slow a repetition rate as your application can handle. Then in software, write a routine to read the timer and compare it to your PWM command value and either set or reset the appropriate output bit based on the comparison. If you call this routine at least as often as the timer changes state, you will have PWM. So it is perfectly possible to turn a lowly AT90S1200 into a PWM engine with multiple outputs.

With PWM control in hand, the reader is now considered armed and dangerous and able to control large motors with a tiny chip.

Generating and using random numbers

Christmas at my parents' house means the inevitable and perhaps interminable game of Aggravation with my sisters. This might be all fine and good except that I am convinced that one of my sisters cheats with a die. I do not understand how she consistently rolls all those sixes. So this year, I did something about it! Warm up your STK500 development board and continue reading.

Why random numbers?

The ideal die, when rolled by normal people, will randomly produce an even distribution of numbers in the range of 1 through 6 (unless my sister is rolling). Such random numbers are the very basis of many games, Aggravation being only one of them.

Random numbers are also very useful in robotics. Consider an autonomous robot faced with an obstacle directly ahead of him. Should he turn right or left? Having the robot always turn right might work, but having him randomly choose a direction is much more interesting. And why not have the robot turn for a random amount of time before turning in a random direction?


How to generate random numbers

There is a conceptually simple method of generating apparently random numbers using a shift register and feedback.

The shift register is a simple idea, implemented in RVK-Basic with a SHIFT instruction. A picture of a shift register will show you exactly how one behaves. In the following table, each successive row shows the state of the register after a shift to the left. That is, on each shift, each bit moves one position to the left and a zero is filled in the LSB (Least Significant Bit).

1	0	1	1	0	0	1	1
0	1	1	0	0	1	1	0
1	1	0	0	1	1	0	0
1	0	0	1	1	0	0	0
0	0	1	1	0	0	0	0

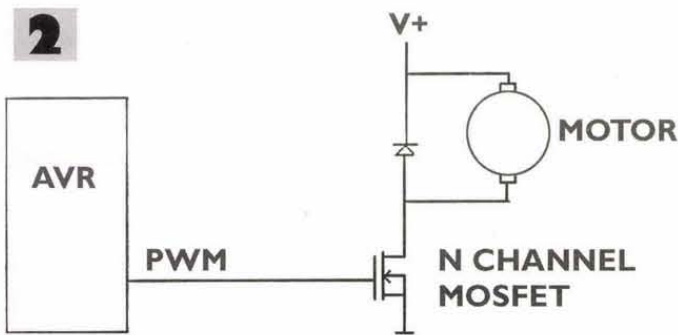Clearly, if this shifting process were carried on four more times, the shift register would become filled with zeros and remain in that dull state forever. So let's introduce a rule that will save the shift register from terminal boredom.



Instead of always putting a 0 in the LSB when we shift, let's put in the exclusive OR of the two most significant bits. That way, the bit introduced in the LSB will sometimes be a 0, and other times a 1. Then the shifting table would look like the following.

1	0	1	1	0	0	1	1
0	1	1	0	0	1	1	1
1	1	0	0	1	1	1	1
1	0	0	1	1	1	1	0
0	0	1	1	1	1	0	1

In this case, it is not at all clear where the shift register is going. Remember that interesting shift registers are happy shift registers!

In theory, if we use a shift register N bits long and apply proper feedback, the register can be shifted $2^N - 1$ times before it repeats a single state. So, using one byte for a shift register we could get 255 different numbers from it before it repeats. A 16-bit register could give us a sequence of 65,535 apparently random numbers before it repeats. Unfortunately, it's not always quite that simple.

In the example just given, we performed an exclusive-OR on bits 7 and 6 and fed that back into bit 0. In reality, this would give a sequence length of 63, not 255. If we had chosen bits 7 and 5 we would get a length of 30, while bits 7 and 4 give a length of 217. It is a very non-trivial problem to locate which configuration of feedback points will give a maximum length sequence

For my needs for a dice simulator, I chose a 16-bit pseudo-random sequence generator (PSRG). I readily found two feedback configurations that would both give a maximum non-recursive length sequence. These are indicated in the source code for the program.

I am reproducing the program here in Listing 1. I wrote the program for an 8515 because that chip is normally supplied with each STK500 kit and it has a full eight bits for both the B and D ports.

To make the STK500 work for this program, you must plug the B port to the LEDs and the D port to the switches. (This should also work on the older STK200 boards.)

The first new thing the reader of RVK-Basic will notice is the EEDATA statement. This statement simply places a byte or more of data in the EEPROM of your chip. This data will be read later in the program.

Note well, that the very first EEDATA statement assigns a label "FIRST:" to the first byte of EEPROM DATA. This will be used later as a base address when reading the data.

The EEPROM in this program contains two tables for the use of the program: referred to as "FIRST:" and "PATRN:". "FIRST:" is the table of which lights to turn on for each of the six possible results from rolling the die. A 1 indicates a lighted LED. "PATRN:" is the table of light patterns for display while the user has a key depressed. This is just a light show.

The main program is very simple. Wait for a key press, then compute a random number in the range of 1-6, then display the result.

The GETKEY routine deserves only a small comment. It waits until a key is pressed and while waiting, it continuously calls random numbers from the PRSG. This makes it impossible to predict the next number because the number depends both on the sequence produced by the PRSG and on the length of time the user holds the key down.

The RND routine simply calls the SHFGEN routine and returns a number in RND%.

SHFGEN is where the real work is done. It first uses fbmask% to look only at the bits in prsgen% which are required for feedback, then counts the number of those bits that are set and complements the actual feedback element, fb2-, each time a 1 is found. This is the equivalent of performing an exclusive-OR on all the bits indicated by fbmask%. The actual generator — prsgen% — is then shifted one left and feedback is applied to the LSB.

If you have a sister who cheats with the die at Aggravation (or Monopoly or whatever), just compile, assemble, and then download this program (both the program and the EEPROM data too) into an 8515 and you will put a stop to her shenanigans.

I found that this greatly reduced the occurrence of sixes that my sister rolled, but she still managed to win anyway. Some things never change.

I trust you will find ample use for this PRSG in many other projects, especially ones like BattleBots where your sister is not involved.

I also used the pseudo-random generator from the DICE program to create a Simple Simon program (see sidebar). In this one, the controller shows you increasingly complex patterns of lights and you are required to echo the pattern by pushing the buttons in the same order. When you get it right, lights race up and down the display. Get any but

```

DEVICE 8515
MHZ 4
XMEM OFF
REVISION DICE REV. 011224.0-rvk

DIRPORT D,IN      '..pushbuttons
OUTPUT D,&HFF      '..set pull-up resistors

DIRPORT B,OUT      '..LED output
GOSUB LITEOFF      '..all LEDs off

prsgen% = &HFFFF      '..initialize pseudorandom
                        '..sequence generator
prsmask% = &H9C00      '..initialize prs gen mask for
                        '..max length sequence
                        '..&H801C will also work...

EEDATA FIRST:,&B00000001
EEDATA ,&B00000011
EEDATA ,&B00000111
EEDATA ,&B00011011
EEDATA ,&B01101011
EEDATA ,&B01110111
EEDATA ,&B01111011
EEDATA ,&B01111111
EEDATA ,&B11111111

EEDATA PATRN:,&B01111110
EEDATA ,&B10111101
EEDATA ,&B11011011
EEDATA ,&B11100111
EEDATA ,&B11011011
EEDATA ,&B10111101

patcnt = 0

MAIN: DO
  GOSUB GETKEY      '..wait for new keypress ==> key
  DO
    GOSUB RND      '..get random number in rnd%
    rnd% = rnd% AND 7
    num = rnd%
    IF num > 5 THEN '..num must be 0-5 only
  ELSE

EXIT DO
END IF
LOOP

DO
  GOSUB RND      '..wait for release...
  INCR patcnt    '..scramble generator..
  IF patcnt > 5 THEN
    patcnt = 0
  END IF
  READ temp,PATRN:patcnt
  OUTPUT B,temp  '..display pattern while
                  '..waiting..
  PAUSE 100
  INPUT gkey-,D
  IF gkey- = &HFF THEN
    EXIT DO
  END IF
  LOOP
RETURN
=====END GETKEY=====

=====BEGIN GETKEY=====
' output: key =
' uses: gkey- =
' waits for key release =
=====
STACK 2
GETKEY: DO      '..wait for any key press
  INPUT key,D
  GOSUB RND      '..scramble generator..
  IF key | &HFF THEN
    EXIT DO
  END IF
END IF
LOOP

DO
  GOSUB RND      '..wait for release...
  INCR patcnt    '..scramble generator..
  IF patcnt > 5 THEN
    patcnt = 0
  END IF
  READ temp,PATRN:patcnt
  OUTPUT B,temp  '..display pattern while
                  '..waiting..
  PAUSE 100
  INPUT gkey-,D
  IF gkey- = &HFF THEN
    EXIT DO
  END IF
  LOOP
RETURN
=====END GETKEY=====

=====BEGIN LITEOFF=====
' output: port B =
=====
STACK 2
LITEOFF: OUTPUT B,&HFF
RETURN
=====END LITEOFF=====

=====BEGIN RND=====
' output = rnd% =
=====
STACK 2
RND: GOSUB SHFGEN      '..shift the generator
    rnd% = prsgen%
RETURN
=====END RND=====

=====BEGIN SHFGEN=====
' output = prsgen% =
' uses: fb% fb2- fb1% =
=====
STACK 2
SHFGEN: fb% = prsgen% AND prsmask%
    fb2- = 0
    FOR shfgn1- = 1 to 16
      fb1% = fb% AND 1
      IF fb1% | 0 THEN
        fb2- = fb2- XOR 1
      END IF
      SHIFT fb%,1,RIGHT
    NEXT
    SHIFT prsgen%,1,LEFT
    IF fb2- | 0 THEN
      prsgen% = prsgen% OR 1
    END IF
RETURN
=====END SHFGEN=====

```

LISTING 1

LEARNING RVK-BASIC

ton wrong and the controller squawks at you by flashing all the lights. Try this on your STK500 board. By all means have your sister play

the game. That will put her in her place. Better still, have my sister play the game! Happy computing! **NV**

DEVICE 8515

MHZ 3.68

XMEM OFF
REVISION SIMPLE SIMON REV. 020103.0-rvk

DIRPORT D,IN ..pushbuttons
OUTPORT D,&HFF '..set pull-up resistors

DIRPORT B,OUT '..LED output
GOSUB LITEOFF '..all LEDs off

DIM lites@[20] ..record of lite numbers...

prsgen% = &HFFFF '..initialize pseudorandom
..sequence generator

prsmask% = &H9C00 '..initialize prs mask for max
..length sequence

'..&H801C will also work...

oldkey = 0

maxgam = 20 '..max number of lites allowed in game

MAIN: DO
GOSUB getnky '..wait for new keypress ==> key

numlit = 0 '..start a new game
DO
INCR numlit
IF numlit > maxgam THEN
numlit = maxgam
END IF

'.....Set up a new game.....
oldnum = 15 '..any illegal number will work
GOSUB LITEOFF '..clear display
PAUSE 400
FOR i = 1 to numlit '..init the array lites@[
DO
GOSUB GETNM7 '..get rnd number 0-7 in nm7
IF nm7 | oldnum THEN
EXIT DO
END IF
LOOP
oldnum = nm7 '..remember last number
ptr = i - 1
lites@[ptr] = nm7
GOSUB DISPNM '..display the light for nm7...
PAUSE 400
GOSUB LITEOFF
PAUSE 200
NEXT

'.....Play the game.....

FOR i = 1 TO numlit
ptr = i - 1
curnum = lites@[ptr]
lost = 0
oldkey = 0
GOSUB GETNKEY '..wait for keypress into key..
GOSUB KEYPSEN '..convert key to its position
IF key | curnum THEN
lost = 1
EXIT FOR
END IF
NEXT

'.....end game.....
IF lost | 0 THEN
OUTPORT B,0
PAUSE 500
GOSUB LITEOFF

PAUSE 200
OUTPORT B,0
PAUSE 500
GOSUB LITEOFF
IF numlit > 2 THEN '..next game easier..
numlit = numlit - 2
END IF
ELSE
temp = 1
FOR i = 1 TO 7 '..walk light up...
bout = temp XOR &HFF
OUTPORT B,bout
PAUSE 100
SHIFT temp,1,LEFT
NEXT
temp = &H80
FOR i = 1 TO 7 '..walk light down...
bout = temp XOR &HFF
OUTPORT B,bout
PAUSE 100
SHIFT temp,1,RIGHT
NEXT
GOSUB LITEOFF
END IF
LOOP
LOOP

'=====BEGIN DISPNM=====
' output: port B =
' input: nm7 =
' uses: ctrdprn- =
'=====END DISPNM=====

STACK 2
DISPNM: bout = 1
ctrdprn- = 0
DO
IF ctrdprn- = nm7 THEN
EXIT DO
END IF
INCR ctrdprn-
SHIFT bout,1,LEFT
LOOP
bout = &HFF XOR bout
OUTPORT B,bout
RETURN
'=====END DISPNM=====

'=====BEGIN GETKEY=====
' output: key =
' uses: gkey- =
' waits for key release =
'=====END GETKEY=====

STACK 2
GETKEY: DO
INPORT key,D
GOSUB RND '..randomize generator
IF key | &HFF THEN
OUTPORT B,key '..display the key
EXIT DO
END IF
LOOP
key = key XOR &HFF
DO
INPORT gkey-,D
IF gkey- = &HFF THEN
GOSUB LITEOFF '..clear the display
EXIT DO
END IF
LOOP
RETURN
'=====END GETKEY=====

'=====BEGIN GETNKEY=====
' output = key =
' input oldkey =
' Gets any new keystroke into key =
'=====END GETNKEY=====

STACK 2
GETNKEY: DO
GOSUB GETKEY
IF key | oldkey THEN
oldkey = key

SIMPLE SIMON PROGRAM

EXIT DO
END IF
LOOP
RETURN
'=====END GETNKEY=====

'=====BEGIN GETNM7=====
' gets a number 0-7 into nm7 =
' uses: nm7 temp% =
'=====END GETNM7=====
GETNM7: FOR nm7 = 1 TO 3
GOSUB RND
NEXT
temp% = rnd% AND 7
nm7 = temp% '..random number, 0-7, in nm7
RETURN
'=====END GETNM7=====

'=====BEGIN KEYPSEN=====
' output: key =
' input: key =
' uses: kp1- kp2- =
' converts position to a number. if bit 5 is =
' pressed (key = &H20) key will become 5. =
'=====END KEYPSEN=====

STACK 2
KEYPSN: kp1- = 0
FOR kp2- = 0 TO 7
TEST kp3-, key, 0
IF kp3- | 0 THEN
key = kp2-
EXIT FOR
END IF
SHIFT key,1,RIGHT
NEXT
RETURN
'=====END KEYPSEN=====

'=====BEGIN LITEOFF=====
' output: port B =
'=====END LITEOFF=====

STACK 2
LITEOFF: OUTPORT B,&HFF
RETURN
'=====END LITEOFF=====

'=====BEGIN RND=====
' output = rnd% =
'=====END RND=====

STACK 2
RND: GOSUB SHFGEN '..shift the generator
rnd% = prsgen%
RETURN
'=====END RND=====

'=====BEGIN SHFGEN=====
' output = prsgen% =
' uses: fb% fb2- fb1% =
'=====END SHFGEN=====

STACK 2
SHFGEN: fb% = prsgen% AND prsmask%
fb2- = 0
FOR shfgn1- = 1 to 16
fb1% = fb% AND 1
IF fb1% | 0 THEN
fb2- = fb2- XOR 1
END IF
SHIFT fb%,1,RIGHT
NEXT
SHIFT prsgen%,1,LEFT
IF fb2- | 0 THEN
prsgen% = prsgen% OR 1
END IF
RETURN
'=====END SHFGEN=====

www.ti.com/gadgetorama2002

Find out how you could win over \$5,000!!

Moving? Moving? Moving?

Be sure and submit your address change to *Nuts & Volts* at least six weeks prior to moving. Unfortunately, we aren't able to replace missed issues due to unreported address changes or changes received after our mailing cut-off date.

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, name of the person to contact, and phone number. While we strive for accuracy in our calendar, we cannot be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:
Nuts & Volts Magazine Events Calendar
 430 Princeland Court
 Corona, CA 92879
Phone 909-371-8497
Fax 909-371-3052
Email
events@nutsvolts.com

Aug-Oct

AUGUST 2002

AUGUST 2-3-4

OH - MIDDLEBURG HEIGHTS - Convention. Buckeye Belles, 440-327-3832. Email: kc4iyd@arrl.net
OR - PORTLAND - Convention. Willamette Valley DX Club, 360-256-7437. Email: k7ar@arrl.net
 Web: www.wvdx.com

AUGUST 3

MI - ALPHA (UPPER PENINSULA) - Hamfest. Iron Range ARC, 906-875-3803
NY - ITHACA - Hamfest. Tompkins County ARC, 607-257-6066. Email: jdreid@lightlink.com
 Web: www2.compcenter.com/~tcarc/
OH - COLUMBUS - Hamfest.

Voice of Aladdin ARC, 614-846-7790. Email: kb8kpj@cs.com
PA - LEWISTOWN - Hamfest. Decatur Township Fire Co. grounds. JVARC & the Decatur Township Fire Co. 717-242-1882

AUGUST 3-4

KY - LEXINGTON - Convention. National Guard Armory. Bluegrass ARS, Inc., 859-253-1178. Email: jrbarnes@iglou.com
OH - CAIRO - Hamfest. Cairo Community Center. Northwest OH ARC, 419-641-5623. Email: w6mdn@hotmail.com

AUGUST 4

NY - WILLIAMSVILLE - Convention. Lancaster ARC, 716-683-8880. Email: luke@towncountryflorist.com Web: <http://hamgate1.sunyerie.edu/~larc>

AUGUST 10

IL - QUINCY - Hamfest. Western IL ARC, 217-222-4467. Email: w9awe@arrl.net
 Web: www.qsl.net/w9awe
MI - JACKSON - Hamfest. Jackson Community College. CARS, Inc., web: www.w8jxn.org
WI - BARABOO - Circus City Swapfest. Sauk County Fairgrounds, Hwy. 33. Yellow Thunder ARC, Inc., 608-356-2313, email n9udo@arrl.net or 608-643-6908 days, 608-643-6453 eves. Web: www.qsl.net/ytarc/hamfest.htm

AUGUST 11

IA - AMANA - Hamfest. 38th Ave., Summerfest grounds. 319-247-0558 eves. Email: kc0ek@mchsi.com
 Web: www.cvarc.org
IL - PEOTONE - Hamfest. Hamfesters Radio Club, 708-756-7984. Email: wb9wfr@arrl.net
 Web: www.hamfesters.org
IN - GREENTOWN - Hamfest. Kokomo & Grant County ARCs, 765-668-4814. Email: k9nqw@arrl.net Web: www.grantarc.com/greentown.html
MD - WESTMINSTER - Hamfest. Carroll County Ag Center, Email: n3sb@qis.net Web: www.qis.net/~k3pzn/tailgate.htm
PA - MATAMORAS - Hamfest. Matamoras Airport Park. Tri-State Amateur Radio Assn., 570-491-4808. Web: www.qsl.net/k3tsa/

PA - SHREWSBURY - Hamfest. Email: w3pn@yahoo.com

AUGUST 16-17-18

CA - ESCONDIDO - Convention. San Diego AR Council, 858-566-8887. Email: gwroos@aol.com
 Web: www.hamcon.net/sd2002/index.html

AUGUST 17

FL - FT. PIERCE - Hamfest. Indian River Community College, 3209 Virginia Ave. 561-465-5204, email: KD4SPW@arrl.net
KS - CHANUTE - Hamfest. Zion Lutheran Activity Center, 1202 W. Main. Chanutte Kansas AARC, 620-431-6402 or 620-431-0930.
OH - FRIENDSHIP - Hamfest. Portsmouth Radio Club, 740-456-1616. Email: kj8ww@zoomnet.net

AUGUST 17-18

AL - HUNTSVILLE - ARRL Alabama Section Convention. Von Braun Center, 700 Monroe St. 256-880-8004. Web: www.hamfest.org

AUGUST 18

IN - LAFAYETTE - Hamfest. Tippecanoe Country Fairgrounds. Tippecanoe ARA, 765-743-8305. www.w9reg.org
MA - CAMBRIDGE - Hamfest. MIT Radio Society/Harvard Wireless Club/MIT (JHF Repeater Assn., email: w1gsl@mit.edu (617-253-3776 9am-5pm.) Web: <http://web.mit.edu/w1mx/www/swapfest.html>
OH - WARREN - Hamfest. Trumbull Campus Kent State Univ. Work Force Bldg. Warren ARA, 330-847-8478. Email: mccaman@cboss.com
 Web: www.onecom.net/wara/

AUGUST 24

IN - LAPORTE - Hamfest. County Fairgrounds. LPARC, 219-324-7525. Web: www.k9jsi.org

AUGUST 24-25

MA - BOXBORO - Convention. Holiday Inn Conference Ctr. ARRL New England Division. www.boroboro.org

AUGUST 25

IL - CATLIN - Hamfest. VCARA Communications Center, Harrison

COMPUTER SHOWS

ACP Computer Show & Swapmeet 714-558-8813
jferguson@acpsuperstore.com
www.acpsuperstore.com

AGI Shows, 317-299-8827
 E-Mail: info@agishows.com
<http://www.agishows.com>

Blue Star Productions
 612-788-1901
www.supercomputersale.com

Computers And You
 734-283-1754
www.a1-supercomputersales.com

Computer Central Shows
 630-782-4625
 Fax 630-834-2594
 E-Mail: cc@gats.com
www.computercentralshows.com

Computer Country Expo
 847-662-0811
 Web: www.ccxpo.com

Five Star Productions
 810-379-3333
 E-Mail: jeff@fivestar.com
www.fivestarshows.com

Gibraltar Trade Center, Inc.
 734-287-2000 Taylor, MI
 E-Mail: taylor@gibraltartrade.com
www.gibraltartrade.com

Gibraltar Trade Center, Inc.
 810-465-6440 Mt. Clemens, MI.
mtclemens@gibraltartrade.com
www.gibraltartrade.com

KGP Productions
 1-800-631-0062, 732-297-2526
 E-Mail: kpg@mail.com

MarketPro, Inc., 201-825-2229
www.marketpro.com

MarketPro, Inc., 301-984-0880
 E-Mail: md@marketpro.com
<http://marketpro.com>

ComputerShow, 770-663-0983
 E-Mail: narisaam@aol.com
 Web: www.showsale.com

Northern Computer Shows
 978-744-8440
 E-Mail: inquiries@ncshows.com
 Web: ncshows.com

Peter Trapp Computer Shows
 603-272-5008
 Web: www.petertrapp.com

Events Calendar

Park W. Addition.
Email: VCARA@Talk.to
MI - LAPEER - Hamfest. Lapeer Center Bldg., 425 County Center Dr. LCARA, 810-245-3907, Email: w8lap@arrl.net Web: www.w8lap.com

AUGUST 31-SEPTEMBER 1

NC - SHELBY - Hamfest. Cleveland County Fairgrounds. SARC, 704-462-4910. Email: w4jl@shelby.net

SEPTEMBER 2002

SEPTEMBER 7

KY - LOUISVILLE - Hamfest. Bullitt County Fairgrounds. Greater Louisville Hamfest Assn., Inc., 812-294-4905. Email: wd4ixl@juno.com Web: www.thepoint.net/~glha
NY - BALLSTON SPA - Hamfest. Saratoga County Fairgrounds. Saratoga County RACES Assn., Inc., 518-587-2385. Email: lake@capital.net
PA - BARTONSVILLE - Hamfest. Monroe County Vo-Tech. Eastern PA ARA & Pocono AR Klub, 570-424-2174. Web: www.qsl.net/n3is

SEPTEMBER 8

OH - FINDLAY - Hamfest. 419-423-3402

SEPTEMBER 13-14-15

IL - PEORIA - Hamfest. Exposition Gardens Fairgrounds, 1601 W. Northmoor Rd. 309-692-3378. Email: w9uvi@arrl.net Web: www.w9uvi.org

SEPTEMBER 14

MI - GRAND RAPIDS - Hamfest. Forest Hills Northern High School. GRARA, 616-458-9029. Email: hamfest@w8dc.org Web: www.w8dc.org/swap.htm

SEPTEMBER 15

MA - CAMBRIDGE - Hamfest. MIT Radio Society/Harvard Wireless Club/MIT UHF Repeater Assn., email: w1gsl@mit.edu (617-253-3776 9am-5pm.) Web: http://web.mit.edu/w1mx/www/swapfest.html
NY - BETHPAGE - Hamfest. Briarcliffe College. LIMARC, 516-520-9311. Web: www.limarc.org

SEPTEMBER 21

FL - NEW PORT RICHEY - Hamfest. New Port Richey Recreational Center, 6630 Van

Buren Rd. Suncoast ARC, 727-848-0353. Email: trobin@homemail.com
PA - SCHNECKSVILLE - Hamfest. Schnecksville Fire Dept. The Delaware-Lehigh ARC, Inc., 610-258-9802. Email: malcolm4@ptd.net http://www.dlarc.org

SEPTEMBER 21-22

IL - GRAYSLAKE - Radio Expo.

Lake County Fairgrounds. Chicago FM Club, Web: www.chicagofmclub.org

SEPTEMBER 22

CT - NEWTOWN - Hamfest. Edmond Town Hall. Candlewood ARA, 203-438-6782. Email: w1jma@aol.com
OH - BEREIA - Hamfest. Cuyahoga County Fairgrounds. Hamfest

Assn., of Cleveland, Inc., 216-999-7388 or 1-800-CLE-FEST. Email: info@hac.org Web: www.hac.org

SEPTEMBER 28

NJ - LAWRENCEVILLE - Hamfest. NJ National Guard Armory, Eggerts Crossing Rd. DVRA, 609-882-2240. Email: abbott0903@aol.com Web: www.w2zq.com

Tired of Expensive Inkjet Cartridges? Save 90% on Inkjet Inks!

Refill kits Black (8 oz) Color (4 oz C, Y, M) Printer (Call for Others Not Listed!)	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP600 Series, Officejet 500, 570, 600, 610 630, 700	7	14	4.71	3.21	32.95	44.95
HP820C, 855C, 870C, 1000C, 1150C, Copier 120, 210	6	12	6.67	3.33	39.95	39.95
HP720C, 722C, 712C, 880C, 890C, 895C, 1120C, 1170C	6	12	6.67	3.75	39.95	44.95
HP900C Series, P1000 Series, Officejet G55, G85, G95	6	12	6.67	3.75	39.95	44.95
HP2000C Pro Color Printer, 2200, 2500	6	12	6.67	3.75	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple StyleWriter 1200,1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, 2000, 5000 Series, Multipass Series	60	60	0.50	0.67	29.95	39.95
Canon BJC-6000, 3000, S400, S450, S600, Multipass 755	14	8	2.85	1.67	39.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	20	17	1.50	2.65	29.95	44.95
Epson Stylus Color 440, 660, 670, 740, 760, 860	20	17	1.50	2.65	29.95	44.95
Epson Stylus Color 480, 580, 880 NEW	20	17	1.50	2.65	29.95	44.95
Lexmark 3200, 5700, Z11, Z12, Z31, Z32,	15	17	2.67	2.35	39.95	39.95
Compaq IJ300, IJ600, IJ700, IJ750, IJ900 Xerox XJ8C	15	17	2.67	2.65	39.95	44.95
Lexmark Z42, Z51, Z52, Z83, Compaq IJ1200, A1000 NEW	15	17	2.67	2.65	39.95	44.95
Lexmark Photo kit for 3200, 5700, 7000, 7200, Z42, Z51, Z52		9		3.11		27.95
Lexmark 2030, 2050, Execjet II/IIc, Medley 4C, Compaq IJ200	10	17	3.00	2.35	29.95	39.95
Xerox HC 450, XJ4C, XJ6C	22	12	1.36	3.33	29.95	39.95
New Combination Kits Black dye 4 oz / Color 2 oz each						44.95
New Combination Kits Black pigmented 4 oz / Color 2 oz each						49.95

Save 30 - 60% on New Compatible Cartridges Quantity Discounts for 3 or 6+ cartridges Mix and match

Printer (Call for Others Not Listed!)	BLACK Cartridge			COLOR Cartridge		
	Qty	1 / 3 / 6+		Qty	1 / 3 / 6+	
Canon BJC-4000 Series, 2000, 5000 Series, Multipass Series		4.50 / 3.83 / 3.69			10.95 / 9.31 / 8.98	
Canon BJC-6000, 3000, S400, S450, S600, Multipass 755		7.95 / 6.76 / 6.52			7.50 / 6.38 / 6.15	
Canon BJC-70, 80, 85 (3 pack Black / 3 pack color)		9.95 / 8.46 / 8.16			14.95 / 12.71 / 12.26	
Epson Stylus Color, Color Pro, Pro XL		9.95 / 8.46 / 8.16			13.95 / 11.86 / 11.44	
Epson Stylus Color II, IIs, 200		9.95 / 8.46 / 8.16			13.95 / 11.86 / 11.44	
Epson Stylus Color 400, 500, 600, 800, 850, 1520, Photo		9.95 / 8.46 / 8.16			13.95 / 11.86 / 11.44	
Epson Stylus Color 440, 660, 670, 740, 760, 860		9.95 / 8.46 / 8.16			13.95 / 11.86 / 11.44	
Epson Stylus Color 750, 900, 980, 1200		10.95 / 9.31 / 8.98			15.95 / 13.51 / 13.08	
Epson Stylus Color 480, 580, 880 NEW		10.95 / 9.31 / 8.98			14.95 / 12.71 / 12.26	
Epson Stylus Color 777, 870, 875, 1270 Requires Empty Return!		11.95 / 11.95 / 11.95			15.95 / 15.95 / 15.95	

Quality Inks and Toners for:
HP Epson Lexmark
Canon Apple Xerox

Inkjet Southwest



New Combination Black / Color Kits
4 oz black dye / 2 oz C,M,Y color - **\$44.95**
4 oz black pigmented / 2 oz C,M,Y - **\$49.95**

Mon - Fri 8:30-5:30 PDT 11:30-8:30 EST

Call or see us online!

www.inkjetsw.com
(480) 668-1069 Fax

1-800-447-3469
(480) 668-0959

Events Calendar

NY - HORSEHEADS - Hamfest.
Chemung County Fairgrounds.
ARAST, Inc., 607-738-6857. Email:
info@arast.org Web: www.arast.org

SEPTEMBER 28-29

VA - VIRGINIA BEACH - Hamfest.
Pembroke Mall.
Email: hamfest@exis.net
Web: www.vahamfest.com

OCTOBER 2002

OCTOBER 6

IA - WEST LIBERTY - Hamfest.
Muscatine County Fairgrounds.
ICARC, 309-537-3678.

Email: kc0aqs@qsl.net
Web: www.qsl.net/kc0aqs
IN - BEDFORD - Hamfest.
Lawrence Co. Fairgrounds. 812-
849-0095. Email: chairman@
hoosierhillshamfest.org
Web: www.hoosierhillshamfest.org
OH - MEDINA - Hamfest. County
Career Center, 1101 W. Liberty St.
Medina Hamfest Committee, 330-
273-1519 after 7pm.
Email: n8tzy@m3net.net

OCTOBER 12

NJ - WASHINGTON TOWNSHIP
- Hamfest. Westwood Regional
Jr/Sr High School, 701 Ridgewood
Rd. BARA, 201-664-6725. Email:
k2zo@arri.net Web: www.bara.org
TX - DENTON - Hamfest. Denton
Civic Center, 321 E. McKinney St.
Denton County ARA, 940-390-
5338. Email: kd5kjj@yahoo.com

OCTOBER 19

FL - JACKSONVILLE - Hamfest.
Morocco Shrine Auditorium, 3800
S. St. Johns Bluff Rd. Greater
Jacksonville Hamfest Assn., 907-
269-8714. www.jaxhamfest.com
FL - ORLANDO - Hamfest. Bahia
Shrine Center, 2300 Pembroke Dr.
Bahia Shrine, Bob KG4ECC, 407-
834-9481

MI - SAULT STE. MARIE -
Hamfest. Chippewa County
Fairgrounds. Eastern Upper
Peninsula Amateur Radio, 906-
635-0215.
Email: wa8old@sault.com
TN - OAK RIDGE - Hamfest.
Fraternal Order of Eagle's Bldg.,
1650 Oak Ridge Tpke. Oak Ridge
ARC, 865-670-1503.
Email: d.bower@ieee.org

OCTOBER 20

IL - GODFREY - Hamfest. Lewis &
Clark Community College. Lewis &
Clark RC, 618-462-4212.
Email: n9fhh@exi.com
MA - CAMBRIDGE - Hamfest. MIT
Radio Society/Harvard Wireless
Club/MIT UHF Repeater Assn.,
email: w1gsl@mit.edu (617-253-
3776 9am-5pm.) Web: http://web.
mit.edu/w1mx/www/swapfest.html
NY - QUEENS - Hamfest. NY Hall
of Science parking lot, Flushing
Meadow Corona Park, 47-01 111th
St. The Hall of Science Amateur
Radio Club, 718-898-5599.
Email: WB2KDG@Bigfoot.com
PA - SELLERSVILLE - Hamfest.
Fire House, Rt. 152. RH Hill ARC,
215-679-5764.
Web: www.rfhill.ampr.org

OCTOBER 26

MN - ST. PAUL - Hamfest.
Touchstone Energy Place,
Rivercentre. 763-535-0637.
www.hamfestmn.org
MO - KIRKWOOD - Hamfest.
Community Center, 111 S. Geyer
Rd. St. Louis ARC & Gateway to
Ham Radio, 314-638-4959.
Email: slw@partyline.net

OCTOBER 27

MD - WESTMINSTER - Hamfest.
Carroll County Ag Center, Email:
n3sb@qis.net Web:
www.qis.net/~k3pzn/tailgate.htm

ALL ELECTRONICS CORPORATION

QUALITY Parts
FAST Shipping
DISCOUNT
Pricing

CALL, WRITE, FAX
or E-MAIL For A
Free 96 Page
CATALOG.
Outside the U.S.A.
send \$3.00 postage.

3.6 Volt 1200 mA Lithium-Ion Cell

Sony # 18650. Rechargeable lithium-ion
cell with solder-tabs. Ideal for high
energy battery packs.
0.72" dia. x 2.56" long.
CAT # BTE-1200
50 for \$3.00 each



All-Weather Flexible Thin Film 6 Volt Charger



Flexible thin film solar module designed to
charge 6 Volt nickel cadmium, nickel metal
hydride or gel cell packs. Module encapsulated
in Tefzel/EV A for weatherproofing.
Flat copper leads extend outside of encapsu-
lation to facilitate connection. Can be
mounted on curved surfaces. 7.2 Volts @
100 mA. 11.31" x 3.87".
CAT # SPL-675 \$29.95 each

Mini-Right Angle Gearhead Motor w/ Control Circuit

Omron # R2DG-41. These
unusual little motors have
built-in control circuits
that allow them to be
used in a continuous
or a pulsed mode. In
continuous mode the final drive gear
turns at 22-45 RPM (3-6 Vdc). In the pulsed
mode the final drive gear turns one revolution
each time the controller is momentarily
pulsed. The motor assembly is 1.75" x 1.25"
x 0.5" overall. Motors are in good condition,
removed from equipment. Hook-up instruc-
tions included. Large quantity available.
CAT # DCM-110




NEW LOWER PRICE!

\$3.25 each
10 for \$3.00 each
100 for \$2.25 each

115 Vac Dual-Speed

Fasco # 7062-5301.
Two-speed
induced draft
blower for heating
and cooling
applications.
Thermally
protected,
ball-bearing,
shaded-pole
motor.
3000 / 1900 RPM. Rated 115 Vac @ 0.95
Amps. 5 MFD/ 370 Vac capacitor. Steel blower
housing and wheel, 9.75" x 8.75" x 3" with
3.75" x 2.75" exhaust port. Overall width,
including motor, 7.5". Four mounting flanges
on 2.75" x 10.25" centers. 12" pigtail leads.
UL, CSA.
CAT # CF-148 \$15.00 each
10 for \$12.00 each

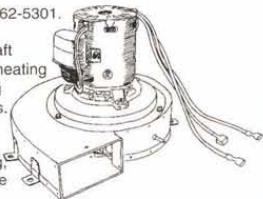

NCD/NMH Battery Charger with 4 AA Cells

Tysonic # TY-3969.
Charges AA, AAA
and 9 Volt nickel
metal hydride
(NiMH) and nickel
cadmium (NiCd) batteries.
Built-in charging control
charges at optimum
rate for safe charging
and maximum battery
life. Charges NiCd in
4 hours, NiMH in 7 hours. Reverse polarity pro-
tection. LED indicators show charging status.
Includes 4 NiMH AA 1600 mAh batteries. Don't
miss this opportunity to get batteries and a
charger at a special low price. Our regular price
for batteries, alone, is \$14.00.
CAT # BC-39 \$19.95 each



5mm Blue LED Special

High-brightness blue LED. 1000 MCD.
Water-clear in off state. Special price.
CAT # LED-86 \$1.75 each
10 for \$1.50 each
100 for \$1.15 each
1000 for 95¢ each



Jumbo Pushbuttons


Durable plastic S.P.D.T. momentary
pushbutton switch frequently found
in arcade games. Useful in any
application requiring a large,
rugged pushbutton switch.
Button operates a 10 Amp
snap-action switch. Plunger is
0.86" diameter. Bezel is
1.33" diameter. Threaded
bushing is 1.1" diameter and will
mount in panels up to 0.75" thick.
Includes large plastic mounting nut.
Available in two colors:



RED SWITCH CAT# PB-211 \$3.75 each
BLACK SWITCH CAT# PB-216 \$3.75 each

Incredible Price! Piercing Piezo Mini-Siren

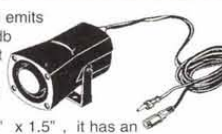This piezo siren emits
a piercing 100 db
warble tone that
is uncomfort-
able for anyone
nearby. Only
2.3" long x 1.7" x 1.5", it has an
adjustable metal mounting bracket and comes
with 6' of wire. Operates on 9-12 Vdc.
Includes a clip for operation with a 9V battery.
Ideal for auto or home alarms. Large quantity
available. CAT # ES-12
\$3.00 each
10 for \$2.50 each
100 for \$1.50 each



680 uf 40 Vdc Capacitor Switching Power Grade

Cornell Dubilier #300681M040JE8
Long life, ultra-low ESR capacitor
designed for switching power
supplies and UPS battery stiffening
applications. 20% tolerance.
105° C. 1" diameter x 1.23" high.
Three leads for stability and
reverse-proof mounting.
CAT # EC-684 65¢ each
100 for 40¢ each



ORDER TOLL FREE 1-800-826-5432
Shop ON-LINE www.allelectronics.com

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567 • VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail •
Orders Delivered in the State of California must include California State Sales Tax • N.O.C.D. • Shipping and Handling \$6.00 for the 48 Continental United
States - ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

Classifieds

HAM GEAR

SATELLITE TV. Complete selection of C & Ku band equipment, WWW.DAVESWEBSHOP.COM



2.4GHz ATV — 8 channel TRANSMITTERS AND RECEIVERS. 35mW output power, 1 video channel, 2 audio, SMA connectors. NTSC/PAL compatible. Includes 1/4 wave rubber duck antenna. Standard frequencies are: 2398, 2405, 2412, 2416, 2420, 2428, 2435, 2442 MHz. Custom frequencies are available. See ad in this section for power amplifier. **\$79/each for transmitter. \$79/each for receiver.** EzATV. Visit our web-site for dealers or order on-line at www.4atv.com



1.2GHz ATV — 8 channel TRANSMITTERS AND RECEIVERS. 75mW output power, 1 video channel, 2 audio, SMA connectors. NTSC/PAL compatible. Includes 1/4 wave rubber duck antenna. Standard frequencies are: 1250, 1255, 1260, 1265, 1270, 1275, 1280, 1290 MHz. Custom frequencies are available. **\$79/each for transmitter. \$79/each for receiver.** EzATV. Visit our web-site for dealers or order on-line at www.4atv.com



2.4GHz POWER amplifier with power supply. 10-40 mW input, 1 (one) watt output with in-line SMA connectors and built-in heat sink. Approx. 2" x 2" x 5/8" size. Frequency range 2.3GHz-2.5GHz. **\$189/each.** Compatible with all ATV product lines. See our website for more info on accessories and transmitter and receiver modules. EzATV. Visit our web-site for dealers or order on-line at www.4atv.com



SUPER HIGH GAIN 14 dbi flat antenna with N or SMA connector tuned for 2.3-2.5 GHz. Use with 2.4GHz ATV 8 channel transmitter or receiver. **\$179/ea.** SPECIAL PRICE. EzATV. Visit our web-site for dealers or order on-line at www.4atv.com

WANTED: ROCKWELL Collins HF-80 equipment, 851S-1, 237B-3 log periodic, Collins literature. Jim Stitzinger 661-259-2011, 661-259-3830 (fax), jstitz@pacbell.net



NEW ICOM IC-V8 VHF 5.5W handheld with full keypad, CTCSS/DCS encode/decode, tone scan, 1100mAh battery and charger + optional battery case \$199.99. Easy modification for full TX 136-174MHz. To order call **1-800-977-0448** or visit <http://www.nsiradio.com/>



ICOM F-11 16ch VHF 5W business band handhelds with rapid desktop chargers, 2-tone decode, scan, PL/DPL only \$269.99. Call **1-800-977-0448** or order online <http://www.nsiradio.com/>

VACUUM TUBES WANTED

BATTERIES/CHARGERS



THE SMART BATTERY CHARGER for lead acid or gel cell batteries. Can be left connected to the battery **INDEFINITELY**, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MC/VISA accepted. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280. www.a-engineering.com

SONEIL CHARGERS. Newest technology, constant current, switching chargers. Individual chargers at wholesale prices from authorized distributor. Guaranteed lowest prices. 570-735-5053 or http://www.DiverseElectronicServices.com/sonel_chargers.htm for prices and info.

CB — SCANNERS

240+ CHANNEL CB/HAM/FRS/COMMERCIAL radios: AM/FM/SSB/CW export/domestic: RCI, TEKK, Motorola, Uniden, Cobra, Alinco, Kenwood. Mics, antennas, linear, meters, mod books, manuals, schematics, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244. www.penny.circus.net

CB MODIFICATIONS! Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBCI, Box 30655NV, Tucson, AZ 85751. www.cbcontl.com

COMPUTER HARDWARE

DATA ACQUISITION: This very compact and low-cost kit will allow virtually any PC to be used for quick and easy data acquisition and control. It connects to any standard parallel printer port, and despite its tiny size provides eight analog inputs, four digital inputs, and four digital outputs. www.electronickits.com

BEST PRICES! 533 MHz systems loaded \$275. GigaHertz systems \$349. Scanners, printers, motherboards, software at liquidation prices. 714-778-0450 email ccis@surfside.net

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com



VGA TO COMPOSITE (NTSC) VIDEO CONVERTER — ULT-2000. Handheld. Powered from keyboard with S-video and RGB outputs, too. 3:1 zoom control with many extras. **\$99/ea.** Matco, Inc., Schaumburg, IL. 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com

UsedComputer.com IS your online used computer equipment marketplace. Notebooks, desktops, printers, parts, free classifieds, 100's of dealers, quantity deals, information. Visit UsedComputer.com today.


MicroPricer.com® SHOWS price comparisons on new equipment, and appraisals on used equipment. Visit MicroPricer.com today.

SAVE MONEY. wholesale pricing, cables, connectors, accessories for computers, networks, audio, video, and telecommunications. www.RogersSystems.com or 1-800-366-0579.

COMPUTER SOFTWARE

KEYSTROKE LOGGER: This new software hides in the background on your computer allowing you to view what other people have been doing on the installed computer. Great for monitoring the children or the wife. www.spousewatcher.com

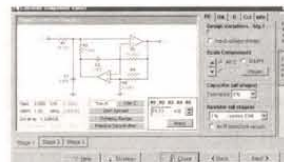FREE!!! CD-ROM and software disk catalog. **MOM 'N' POP'S SOFTWARE**, PO Box 15003-N, Springhill, FL 34609-0111. www.momnpopware.com



WWW.SCHEMATICA.COM FOR professional freeware and shareware. Active and passive filter design, 555 designer, linear simulators.

WANTED MICROSOFT: Windows, Office, Server software. Complete sealed packages, or manuals, or CDs only. 914-738-6830.

I-MAC MONITOR or power supply problems? We have schematics for this. Along with 4,000+ other reverse engineered prints in 21 catalogs. For retoming information, write or check out our web site. **Bomarc Services**, Box 1113, Casper, WY 82602. 307-234-3488. bomarc.org

COMPUTER EQUIPMENT WANTED

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-745-2322).

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

BUYING SCRAP PC motherboards and plug in cards; paying \$0.50 per pound. 386 & 486 CPUs (chips only) \$12 per pound. Pentium CPUs, \$4.50 per pound. Cables, \$0.15 per pound. New Jersey Tpk, exit #9, (New Brunswick). Other stuff, call Lee @ 732-651-9700. We pay cash or PayPal.

TEST EQUIPMENT

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

A-COMM ELECTRONICS: we buy and sell test equipment. <http://www.a-comm.com> 11891 E. 33rd Avenue, Aurora, CO 80010. Tel: 303-341-2283, fax 303-341-2293.



POCKET TESTBENCH, inexpensive RS-232 virtual instrument, with oscilloscope, logic analyzer, counter, and generator modes. **New WST-100.** www.oricomtech.com

CHECK OUR growing line of audio test instruments: data sheets, user guides, software. TDL Technology, Inc., www.zianet.com/tld.

GIANT DIRECTORY ONLINE: Over 500 dealers in used test equipment, used semiconductor production equipment, surplus lasers, optics, vacuum equipment, etc. Test equipment auction and rental sites, US and foreign dealers, manual dealers, too! No registration or cookies. **www.big-list.com**

MODEL 321 quickly and accurately measures virtually any type of cable, pinpoints breaks. No need to know manufacturer's specifications, or NVP. For further information write or fax: **CABLE DYNAMICS**, PO BOX 34594, Phoenix, AZ 85067, tel/fax 623-931-6262.

USED TEST equipment sale specials. Equipment on sale. Check our web page to see what equipment we are offering at our lowest prices! www.calibration.com Instrument Repair & Rental Labs, Inc., 1-888-573-5468, Colorado 303-469-5335. Mail to sales@testequip.com

FEITEK PROVIDES repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at WWW.FEITEK.COM 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

SECURITY

ALARMLAND.COM SECURITY devices for professionals. Motion detectors, panels, contacts, CCTV, and more. Fax your order to 732-840-1390.

SURVEILLANCE-COUNTERSURVEILLANCE: I buy and sell used equipment. Steve 410-879-4035.

KEYSTROKE LOGGER: This tiny piece of hardware installs between your keyboard wire and computer in seconds. Then it logs all keystrokes, which you can view at your convenience. www.spousewatcher.com



2.4GHz WIRELESS transmitter/receiver kit. ASK-2008-TR. 8 frequencies uP controlled 2.300 to 2.481 MHz, video NTSC/PAL with 2 channels of audio for development testing. 12VDC/100 mA for both transmitter and receiver. Includes 2 rubber duck antennas. **\$125.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



9 VOLT IR sensitive B/W high res 430 TVL camera with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; works from **7.5-13 VDC**, highest voltage range in market. 0.08 lux, 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. **\$49 each.** Enclosure: \$8; optional lens: \$18. Dealers welcome. Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



AS-1004 WIRELESS 2.4GHz, FCC approved. 2.4GHz transmitter & receiver with audio! Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 400 TV line. **Reduced price! \$179/system.** Additional cameras, **\$110/ea.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com

FIELD-STRENGTH RECEIVER - METER A Handheld Counter-Surveillance Meter So Sensitive It's Like a Wideband Receiver!

BROADBAND: 10 MHz to 4.5 GHz usable range
HIGHLY SENSITIVE: Detects - Covert Video and Audio Bugs at 20 ft. - 2.4 GHz "beamed" microwave ovens at 40 ft.
 For Computer Wireless Setup, RFI Sniffer, RF Line Leakage

DUAL MODE: LINEAR - For measuring weakest signals
DETECTION: LOGARITHMIC - 1000:1 dynamic signal range
SENSITIVITY CONTROL: > 20 dB manually adjusted gain
HR OPERATION (Approx.): With 2 AA alkaline batteries

ANALOG METER and LED DISPLAYS: The LED display for distance and nighttime
SILENT VIBRATE MODE: Switchable vibrator for signal detection without direct viewing

Including shipping and handling (CA residents add 8% Sales Tax) **\$89**

Alan Broadband Company Phone: (888) 369-9627
 93 Arch Street
 Redwood City, Ca. 94062 Fax/Phone: (650) 369-9627

www.zapchecker.com

SECURITY DISTRIBUTORS needed for our complete line of products. See our product features in the center color spread on page 47. **www.matco.com** and call 1-800-719-9605.



40 DAYS and 40 NIGHTS RECORDER. Time lapse, with remote, can be activated by either contact closure or continuous duty operation with standard T-120 tape. **ES-8960 at \$339.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



WEATHER RESISTANT OUTDOOR CAMERAS. VWR-700 type, high impact tempered glass with stand. Black & white (430 lines), or color (420+ lines) available. Standard 3.6mm lenses with optional lenses of 6, 8, and 12 mm at \$20 extra. **B/W \$119/each. Color \$179/each.** Small compact size with sun shield. Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com

SEE THE NEW MATCO PRODUCT FEATURES AND PRICES in the color center spread on page 47.

LOW-COST video cameras for home, hobby, robotics, nanny monitoring. **www.helltek.com**

HI-TECH SECURITY: Electronics, computers, internet, financial, energy, phone, communications, surveillance, privacy, polygraphs, physical survival, electronic harassment, stealth technology, vehicles, occupation, many more! **CONSUMERTRONICS. www.tsc-global.com** Catalog #3: PO 23097, Albuquerque, NM 87192.



5" AND 5.5" LCD high definition color monitors w/stereo. 960 x 240 pixels w/brightness and tint controls. Attractive enclosure with built-in speaker. Great for security or general purpose use. Both models have a small compact footprint, with an ultra-bright display, RCA inputs NTSC or PAL. Special price with regulated power **\$249/each.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com




16 CHANNEL MULTIPLEXER MUX-1600. Display 4, 8, and 16 video outputs directly on a TV or security monitor. This is the only device which allows full screen display of video on VCR playback (see 40 days and 40 nights recorder). Plenty of options including tilting, zoom, individual gain adjustments, etc. **Reduced price! \$799/each. Special 4 channel version, MUX-400, \$429/each.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



14" B/W high resolution SECURITY MONITOR. A standard 12" monitor is just too small for most applications. Attractive dark gray enclosure with audio and built-in speaker. 75 ohm termination switch for balancing with all types of CCD board cameras and other video inputs. **\$139/each.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



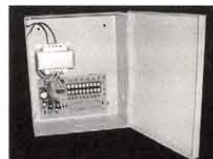
14" COLOR — high resolution SECURITY MONITOR w/4 channel switcher. High impact enclosure with modern front panel 4 channel video and audio switcher. High quality speaker built-in. Components purchased separately would exceed \$500. Price slashed to **\$249/each.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



CAMERA DISTRIBUTION Box. XF-250-DC/XF-250-AC. Connect your cameras directly to power source with screw terminals or plug in using a 2.1 mm connector. **Special price: \$59 (DC version) and \$49 (AC version).** Can use pre-molded **50 foot video/power cable A-402-CA \$15.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



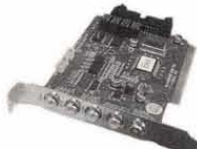INFRARED CAMERA for underwater or all-weather use. AX-808 (B/W) or AX-808-C (color). Designed for lake water to depths of 85 feet. Enclosed LEDs illuminates up to a distance of 20 feet. 12 volt operation. **Color \$149, B/W \$99.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



4 PORT video capture card with remote internet access, DVRC-4; \$339. Remotely view any 4 NTSC video cameras over your internet connection. Sophisticated motion sensing option allows camera to be activated by motion or time. 500 MHz or higher; 98/2000/XP, NT compatible. Installation time under 10 minutes. 16 channel unit is also available, bundled with PC. **Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com**




WIRELESS COLOR rechargeable 2.4GHz system. ASK-7003-TR. 150 foot range. Includes camera/transmitter, receiver and built-in battery pack with charging systems. Range 150 feet. **High volume seller! \$159.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com

HI-TECH SPECIAL PROJECTS SECURITY HARDWARE, CONSULTING: Numerous building, vehicle, personal, communications security devices, systems, technologies, countermeasures. **LONE STAR CONSULTING, INC.** Catalog online: www.lonestartek.net, 915-474-0334.



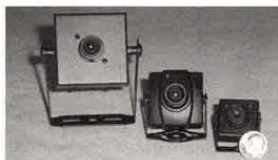QUAD PROCESSOR works with VGA monitor. QVS-104-CV. NTSC inputs, composite outputs as well as output for direct connection to VGA monitor. Saves cost of expensive high-grade security monitor. **\$269.** Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



COLOR & B/W board cameras w/cases, BX-120-LC (350 lines color) \$89; BX-125-LC (380 lines color) \$99, sub-miniature BX-123-AU (420 lines B/W with audio) \$69. Matco, Inc., Schaumburg, IL, 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



KX-880 AND KX-880-C. WITH SPECIAL sun shield and weatherproof/waterproof design with swivel bracket. Standard 3.6 mm lens. Will work with Matco Scanning Motor. 420 TVL **B/W \$89/each. Color 350 TVL, \$129/each.** Matco, Inc., Schaumburg, IL P: 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com



12 VOLT mobile 960 hour time lapse with audio. MS-6960 12 vdc/1000 mA operation with remote control and cigarette adapter connector. **\$349.** Shock-mounted optional case available for portable operation. **Matco, Inc., Schaumburg, IL. 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com**



LAW ENFORCEMENT. 2.4 GHz wireless cell camera system with receiver; \$429 with low-lux 5 volt Panasonic camera and detachable antenna. Omni-directional pattern; 4 hour run time; over-night charger included. Various RF power options available. **Matco, Inc., Schaumburg, IL. 1-800-719-9605, sales@matco.com or visit/order on-line at www.matco.com**

SATELLITE EQUIPMENT

SATELLITE REPORT: Find all the latest in satellite descrambling in this 54-page report. Lists all the cheapest and reliable sources for hacked cards and equipment. www.electronickits.com

SATELLITE TV. Complete selection of C & Ku band equipment, **WWW.DAVESWEBSHOP.COM**

WHOLESALE PRICING. Call, fax, or email for free catalog of over 1,600 items from satellites, cable, security, telephone wire and connectors. Quality pricing, fast shipping & great discount pricing. Your accessory connection. Call SkyMarketing @ 1-866-637-4965 or 219-489-7525. Fax: 219-489-2285. Email: skymark@fwi.com or visit us on the website at www.skymarktech.com



FREE SATELLITE TV Buyer's Guide. Low prices on big dish systems, upgrades and parts. Upgrade to digital with new 4DTV receiver or sidecar. Best prices on little dish systems, too. Backed by Skyvision's technical expertise, **YOU CAN** do it yourself! **www.skyvision.com** Call 1-800-334-6455.

SATELLITE UNUSUAL. free to air explained, preprogrammed receivers, parts, low prices, full line satellite. <http://www.mpeg2fta.com>

MILITARY SURPLUS ELECTRONICS

AUDIO — VIDEO — LASERS

PRO AUDIO & video gear, all types of tubes, components, and unusual collectibles at WWW.bibbtek.com Call Tom @ 856-222-0636, fax to 856-222-0638 for printed list. Credit cards welcome.

SAVE MONEY, wholesale pricing, cables, connectors, accessories for computers, networks, audio, video, and telecommunications. www.RogersSystems.com or 1-800-366-0579.

CABLE TV

CABLE REPORT: This 50 page report contains all the latest in how cable systems have been compromised. Including cheap and reliable sources for test chips and equipment. www.electronickits.com

CABLE PARTS! Computer parts. Call for great prices or visit us on the web: [HTTP://WWW.Chipwizards.com](http://WWW.Chipwizards.com) or call 407-739-7573.

POSITIVE AND negative cable TV filters. www.gofilters.com 1-800-235-8080. Mike is back, give us a call. We can help in all situations.

CABLE TV CONVERTERS. Wholesale pricing, full warranties. Scientific Atlanta 8580 \$20, SA 8590 \$23, 8600 \$25, Jerrold DPV7 \$20, BB/CFT \$25, CFT 2254 \$35. Free nationwide shipping, 10 lot minimum orders. Masterpiece 125 channel converters \$45 delivered. CODs welcome. Converters, parts, and accessories. Covers, lenses, remotes, cords, and data crystals. Call toll free 877-915-3727.

CATV. CABLE converters 125 channel \$45. SA 8600, SA 8580 converters \$19.99. Jerrold DPV 7212 \$19.99. CFT 2014 \$19.99. Pioneer 6310 \$22.99. Dealers call for more info. 214-552-0078. 1-888-959-5589.

ABC WHOLESALE, Inc. Importer & distributors of the Multitech 4500 & 5000 series 125 channel new basic converter. Our monthly unmodified specials in lots of 10 with new remote are Scientific Atlanta 8600 \$25 ea., SA 8580 \$19.95 ea., Jerrold BB 7312 \$25 ea., Jerrold DPV 7212 \$19.95 ea., Jerrold CFT 2014 & 2254, Pioneer 6310 \$25 ea. Large quantities please call for wholesale dealers price. We have all models replacement remotes. Se habla espanol. 1-800-510-1924.

125 CHANNEL converters: \$35. Also specializing wholesale on raw unmodified boxes, as low as \$5 each. 866-270-5838.

SAVE MONEY, wholesale pricing, cables, connectors, accessories for computers, networks, audio, video, and telecommunications. www.RogersSystems.com or 1-800-366-0579.

CABLE PARTS for all makes and models, raw boxes at low prices. Call 1-888-816-0800. No NY sales. www.chipplace.com

THE FOUNDER of Cool Box is now introducing the Premier & Optima Series to the public, with new RRI technology. For details, visit <http://www.alltrentusa.com>

TELEPHONE/FAX

PHONE MANAGER: This unit looks exactly like a Caller ID, except it records time, date, and length of all outgoing calls. www.spousewatcher.com

SAVE MONEY, wholesale pricing, cables, connectors, accessories for computers, networks, audio, video, and telecommunications. www.RogersSystems.com or 1-800-366-0579.

HI-TECH SECURITY, TECHNOLOGY BOOKS: Phones, cellphones, faxes, pagers, voice mail, answering machines, PBX, internet, communications, energy meters, many more! **CONSUMERTRONICS, www.tsc-global.com** Catalog \$3: PO 23097, Albuquerque, NM 87192.

HI-TECH SPECIAL PROJECTS TELEPHONE HARDWARE, CONSULTING: Phones, internet, communications, surveillance, security, remote interfaces, energy meter, much more! **LONE STAR CONSULTING, INC.** Catalog online: www.lonestartek.net, 915-474-0334.

CELL PHONE internal antenna booster. As seen on TV. \$5 ea. \$1 ea. per 100. 1-877-723-8584.

COMPONENTS

WANT TO Buy: ICs, military & aircraft relays, diodes, transistors, connectors, tantalum capacitors, electronic test equipment & most components. Hoffer Electronic Ent., E-Mail: Hoffel165@aol.com 818-718-1165, FAX 818-341-5506.

PELTIER INFORMATION DIRECTORY ONLINE: Information site on Peltier devices (thermoelectric cooler/heater/generator modules). Tips, manufacturer directory, surplus sources, etc. Free. No registration. www.peltier-info.com


PCB PROTOTYPES FOR \$26

<http://www.olimex.com/pcb>

FR-4, 0.062", 1/10z copper, 6.3"x3.9", double side, plated thru holes, solder mask, component print, production in 3-5 working days, made in Bulgaria, no import tax to USA and Europe


ELECTRONIC COMPONENTS, kits, test equipment, books, tools, and supplies for hams, hobbyists, and businesses. Many hard-to-find items like variable capacitors, vernier dials and drives, coil forms, magnet wire, toroids, more. www.oselectronics.com

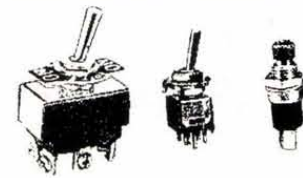MATCO WILL design, engineer, and develop a 2.4GHz wireless 8 channel solution for your remote applications. FCC approved. Matco, Inc., Schaumburg, IL 1-800-719-9605. E-Mail: nsales@matco.com Web site www.matco.com



SWITCH SUPERMARKET large variety toggle, rotary, LEDs bipolar 2 & 3 leads, grain of wheat, free list. Fertik's, 5249 "D" St., Philadelphia, PA 19120. Ph/fax 215-455-2121.

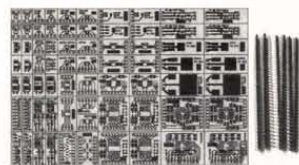Enter the Nuts & Volts/Texas Instruments design contest.
You could be the big cash winner!!



SMT ADAPTERS. Snap-apart PCBs, pin strips in many patterns. Soic, qfp, tssop, qsop, sot, and more. Find your solution at www.beldyns.com

MICROCONTROLLERS




PIC & ATMEL PROGRAMMERS from \$15.95 and \$29.95! Visit www.electronics123.com for complete details. Amazon Electronics, Inc. Toll free 1-888-549-3749.

PIC, AVR and MSP430 DEVELOPMENT TOOLS

<http://www.olimex.com/dev>

PIC - PROGRAMMERS, IC, PROTOTYPE BOARDS FOR 8, 18, 28 and 40 pin PICs, **AVR** - PROGRAMMERS, PROTOTYPE BOARDS FOR 8, 20, 28, 40 and ATMEGA AVR's, **MSP430** - JTAG FLASH EMULATION TOOL, PROGRAMMERS, PROTOTYPE BOARDS FOR F1121, F123, F413 and F149

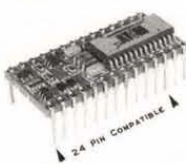PIC PROGRAMMERS: Several different programmer kits that you can build yourself all the most popular PIC and Atmel chips. www.electronickits.com



ATOM MODULES/Starter Packages. Lowest starter package prices. Program in Basic. In-Circuit Debugger. Modules starting at \$59.95. Starter packages at \$139.95. www.elproducts.com — Online ordering or call 248-515-4264.

PROGRAM THE 8052 in Basic with our inexpensive development single board computer. The 70691BASIC comes assembled/tested & contains Micromint's 80C52 controller, which allows programming through the serial port of PC. The 70691BASIC contains a large breadboard area, 8K RAM/ROM, hi-address decoder, 40-pin header connector and a 2864 EEPROM that allows auto-startup of your saved programs. Programming software included. \$75 plus \$4.75 S/H. Also learn how to program the 80C52 with this BASIC-52 Users Manual on 3.5in disk \$5. Sokolowski, 9356 Merriweather Dr., Brooksville, FL 34613 or www.HomeTechFLA.com

ANTIQUE ELECTRONICS

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-745-2322).

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

RADIO TUBES and phono. needles. 870-747-2281.

WANTED: OBSOLETE computers & electronics for ACP PC Museum. Contact Dave at 714-558-8813. dcfree@aol.com

AVIATION ELECTRONICS

PUBLICATIONS

BASIC STAMP 2 users: "Inside the BASIC Stamp II" tells how the PBASIC interpreter works, how code is stored in EEPROM, how to optimize code for space and speed. 160 pages, 50 illustrations, many examples. See <http://members.aol.com/stamp2book> Send \$29.95 check or money order (US funds) to Brian Forbes, 147 Flying Cloud, Foster City, CA 94404-1301.

ROBOTICS


ARobot KIT from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/robot>

ROBOT KITS: Over 30 complete robot kits from beginner to advanced at www.electronickits.com

MOTOR CONTROLLERS: PWM 20A to 50A, 12 to 36 volt models, from \$40. **Easy RC:** Control board accepts standard RC pulses to control speed and direction of motor controllers. **RC weapons** control boards: 1 to 3 devices. **Joystick interface** controllers. **Soneil chargers:** best pricing available. Mention this ad for free ground shipping. Info 570-735-5053. www.DiverseElectronicServices.com email carl@DiverseElectronicServices.com


ROBOT BOOKS.COM visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! www.robotbooks.com

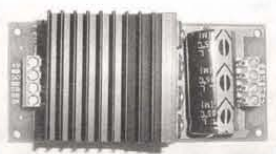PIC-BASED bot controller boards, OOPic-compatible and 28-pin versions, new multi-servo controllers, www.oricomtech.com



ZAGROS ROBOTICS sells, high current motor drivers, sonar units, optics, encoders, processors, and much more. Find everything you need to build your own robot! Zagos Robotics, 314-768-1328, PO Box 460342, St. Louis, MO 63146. info@zagrosrobotics.com <http://www.zagrosrobotics.com>

CNC

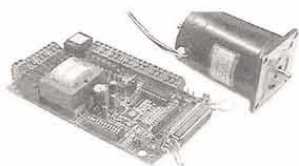

STEPPER MOTOR drivers, interfaces, breakout boards, and accessories for CNC projects. Use with DanCAM, CNC-Pro, TurboCNC, Master5, EMC, and others. Visit us at www.pmdx.com

PLANS — KITS — SCHEMATICS

ELECTRONIC KITS: Hundreds of electronic kits and projects. Where else except www.electronickits.com

TRUE COLOR ORGAN. Seven filters, adjustable. Mic or line fed. AC or DC light up your life. Schematic & all info., \$21.50. Dan M. Lawson, PO Box 1249, 239 Vernon St., Roseville, CA 95678.

HI-TECH SURVIVAL: Electronics, computers, internet, energy, phones, medical, financial, security, physical survival, electronic harassment, many more! **CON-SUMERTRONICS.** www.tsc-global.com Catalog \$3: PO 23097, Albuquerque, NM 87192.



BUILD A SOLAR PANEL — generate electricity cheaper and better than commercial panels! Complete illustrated instructions. E-book available for immediate download. www.buildasolarpanel.com

GENERATE STEREOSCOPIC 3D video using cheap board cameras for robots, R/C vehicles, telepresence and other projects. 50+ page booklet explains how schematics, parts lists, drawings and photos. Visit <http://stereo-video.home.att.net>

MISCELLANEOUS ELECTRONICS FOR SALE


Electronics Manufacturing
Technology, Inc.



Bare PC Boards

- Design & Layout
- Single, Double, & Multi-Layer
- PC Board Assembly**
- SMT & Thru-Hole
- Final Assembly & Test
- Product Engineering**
- "Prototype and Production"**

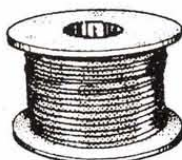10945 Reed Hartman Hwy., Suite 112
Cincinnati, Ohio 45242
(513)791-4000 Fax: (513)791-4408
sales@pcboardsinc.com
www.pcboardsinc.com



ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. Wire cut & strip to specs. If interested, please call **1-800-626-7540**. FAX: 714-563-8309. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anaheimwire.com> OR E-Mail: info@anaheimwire.com

BRITE LITE

Manufactured by, Electronics Manufacturing
Technology, Inc. (EMT)

Scrolling LED Signs

- ◆ Wireless Keyboard
- ◆ Includes Windows Software
- ◆ Text and Graphics Display
- ◆ Clock Functions & Scheduler
- ◆ Real Time (ASCII) Mode
- ◆ 16,000 Character Memory
- ◆ RS-232 & RS-485 Serial Ports for multiple sign networking

High Intensity Wide Viewing Angle Color LED's

10945 Reed Hartman Hwy., Suite 112
Cincinnati, Ohio 45242
(513)791-4000 Fax: (513)791-4408
sales@briteliteled.com
www.briteliteled.com

HARD-TO-find parts: PTV screens, modules, chassis, flybacks, tuners, tubes, for all brands. Manuals. 478-272-6561. Scarborough TV, 1422 Old River Road, East Dublin, GA 31027. scarboroughstv@pcnow.net



PORTABLE CARD SWIPER. Swipe any card with this incredible tiny device and the complete data on the magnetic stripe is stored instantly in its memory. Stores over 100 swipes at one time. Powered by a small camera battery. It can be use remotely on any type of card with a magnetic stripe. After the magnetic stripe information is saved, you may download the information to any computer or laptop. Applications: data collection, trade shows attendance, conference attendance, classroom attendance and many others. We have many different models and magnetic stripe reader/writers. See our web site: www.mobilecardreaders.com Or write for free catalog. The Information Center, PO Box 876, Hurst, TX 76053. 817-589-7891.

RS485/422/232/TTL

- ASC24T \$45
- Converters
- Repeaters
- Fiber Optics
- Digital I/O
- Multidrop RS232
- Custom Units
- Auto TX Enable

Extensive Interface Product Line

- RS232 "Extension Cords"
- Up to 115.2 Kbps, 4000 ft. ++
- Large Multidrop Networks.
- Isolated Units. Smart Units
- Remote Relay "Extension Cords"

Call the RS485 Wizards at
(513) 874-4796

RES R.E.Smith
www.rs485.com



ZENITH KEYBOARD terminal. 63 keys, DEC VT-52 compatible, TTL I/O, RS-232 serial and Centronics parallel ports, composite video output, built-in modem, unused in original box with manual and schematics. \$35. 619-449-9040, or order online at www.CBMart.com.

SURPLUS & REFURBISHED ELECTRONIC EQUIPMENT including repair and experimenter parts and accessories. Many hard to find and one of a kind items: audio, video, communications, computer, security, telephone, and test equipment. Service manuals, cables, cabinets, capacitors, connectors, displays, ICs, LEDs, motors, potentiometers, relays, resistors, switches, transformers, transistors, vacuum tubes, and much more. **SMC ELECTRONICS** www.smcelectronics.com


2 AXIS SOLAR TRACKER PCB assembly \$73. Add your 12VDC source & drive system to track the sun. Info: <http://members.shaw.ca/theanalogguy>

MISCELLANEOUS ELECTRONICS WANTED

WANTED: BALANCING machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanalysis, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

WANTED: TUBES, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Monroe Twp., NJ 08831. Phone: 609-395-1116, FAX 609-395-1117.

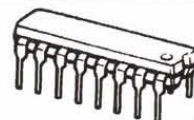DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com




WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS; MILITARY COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL LPS 562-439-2453 FAX 562-439-0453.

WANTED: TUBES & sockets. All kinds and quantities. A/B carbon resistors. Sprague black beauties/vit Q caps. Western Electric audio equipment & tubes. Contact Charlie 760-955-8279, fax 760-245-4760. cdlske60@earthlink.net

ONLINE SERVICES

EDUCATION

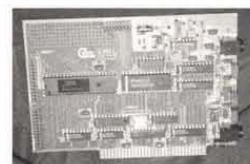

ISA DIGITAL/ANALOG BOARD. Great for experimenters, designers, and students. 27 digital I/O lines. Eight 8-bit DA inputs, one with mike preamp. Two 8-bit DA outputs, one with audio power amp. Buffered data, address and control lines, plus 3 spare selects for expansion. Bare board only \$20, kits and assembled available. More information, a **FREE** tutorial and source code at www.learn-c.com.

MAGICIAN IS available to solve your RF problem. I will teach you in my laboratory how to do it. Young engineers and technicians are welcome. SMT prototyping up to 3GHz for customers. Minaret Radio, John Horvath ph: 909-943-3676. Ask for my resume.

HOT INTERNET TIPS. Over 30 mind boggling internet ideas that will dazzle your senses! 1-900-740-1616 Ext. 5626 \$2.99 per min. Must be 18 yrs. Serv-U 619-645-8434.

BUSINESS OPPORTUNITIES

AFFILIATES WANTED: If you have a website you can earn a 10% commission for every person that you refer to our site. See complete details at www.spousewatcher.com

REPAIRS — SERVICES

(E)PROM PROGRAMMING done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**


HI-TECH HARDWARE, CONSULTING, PLANS: Unique, original, made-to-order, special needs, controversial **SPECIAL PROJECTS, TECHNICAL COACHING, WEBSITE DESIGNS.** Electronics, computers, internet, energy meters, phones, radionics, security, physical survival, electronic harassment. Design, create, modify, repair, consult! **LONE STAR CONSULTING, INC.** Catalog online: www.lonestartek.net, 915-474-0334.

WELD ALUMINUM WITH PROPANE! EZ, INEXPENSIVE, STRONG. DETAILS: WEEKS, 36 CAROLINA ST., TAYLORS, SC 29687. 1-800-547-WELD(9353) FAX 864-244-6349. <http://www.durafix.com>

ENGINEERING TECHNICIAN AND SERVICES: SMT 0402/fine pitch prototype, debug, testing DC - 3GHz. Protel 99SE schematic capture and PCB layout. Short projects to long-term R&D support. San Diego area. On-line portfolio: http://members.cox.net/sd_tech/. Email: sd_tech@cox.net

Subscribe to *Nuts & Volts*
1 800 783-4624
www.nutsvolts.com

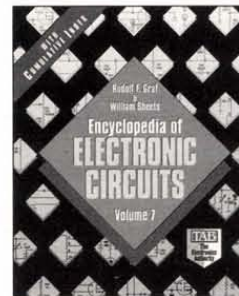"Encyclopedia of Electronic Circuits" Vol 7 by Rudy Graff



ONLY \$39.95

Designed for quick reference and on-the-job use, the *Encyclopedia of Electronic Circuits, Volume 7*, puts over 1000 state-of-the-art electronic and integrated circuit designs at your fingertips. Organized alphabetically by circuit type, this collection includes designs from industry giants such as Advanced Micro Devices, Motorola, Tele-dyne, General Electric, and even right here in *Nuts & Volts*.

As a paid subscriber to *Nuts & Volts*, you'll receive **10% off the list price!!**
(See ad on page 88 for ordering details and other titles currently available.)

Classified Ad Instructions

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY (not all caps)** on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable. Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label (if available)** for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

NUTS & VOLTS MAGAZINE, 430 Princeland Ct., Corona, CA 92879

RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00** minimum charge per ad per insertion.

BOLD WORDS AND/OR CAPS

Words to be set in **bold** or CAPS are each 10¢ extra PER WORD. **BOLD CAPS** are 20¢ extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

PHOTOS, DRAWINGS

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area.

EMAILING/FAXING AD COPY

You may email or fax in ad copy or changes before the closing date (5:00pm on the **1st**) using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your *Nuts & Volts* account number. Email ad(s) to classad@nutsvolts.com or fax to 909-371-3052. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL, EMAIL, OR FAX BACK VERIFICATION OR QUOTES OF EMAILED AND FAXED-IN ADS.** For verification of emailed or faxed-in ads, please call 909-371-8497.

DEADLINE

Prepaid ads received by 5:00pm on the **closing date (1st of the month)** will appear in the following month's issue. Ads postmarked through the **1st**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 1st. Cancellations and changes must be submitted in writing.

IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in *Nuts & Volts* is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you *clearly* print or type your ad copy.

Choose a category for your ad from these classifications.

10. Ham Gear	130. Antique Electronics
20. Batteries/Chargers	135. Aviation Electronics
30. CB/Scanners	140. Publications
40. Music & Accessories	145. Robotics
50. Computer Hardware	148. CNC
60. Computer Software	150. Plans/Kits/Schematics
70. Computer Equipment Wanted	155. Manuals/Schematics Wanted
80. Test Equipment	160. Misc. Electronics For Sale
85. Security	170. Misc. Electronics Wanted
90. Satellite Equipment	175. Online Services
95. Military Surplus Electronics	180. Education
100. Audio/Video/Lasers	190. Business Opportunities
110. Cable TV	200. Repairs/Services
115. Telephone/Fax	
120. Components	
125. Microcontrollers	

Secrets of RF Circuit Design

by Joseph J. Carr



Following up on the best-selling previous editions, this revised and updated guide gives you the best ways to design, build, and test today's radio frequency circuits. It's filled with functional projects and experiments that make it easy to apply RF principles to real-life applications. Joe Carr provides parts lists and component sources for every project, in chapters that cover how to: Design and build radio receiver circuits, RF bridges, amplifiers, receiver preselectors, simplified spectrum analyzers, and time domain reflectometers; Select, use, maintain, and repair variable capacitors; Design and wind inductor coils for radio circuits; Construct and ground simple wire antennas.

This book takes you inside wireless technology with step-by-step, illustrated directions for dozens of usable projects.

PERFECT FOR TECHNICANS, RADIO HOBBYISTS, AND ANYONE WHO WANTS TO PUT RF THEORY INTO PRACTICE

*Ideal for learning radio frequency circuitry

*Detailed coverage of simple RF instruments, as well as UHF and microwave components

*Complete troubleshooting guidance, too! Update of the favorite RF circuit guide of thousands of electronics enthusiasts!

Order today from the **Nuts & Volts Bookstore**

Call **1-800 783-4624** or order online at

www.nutsvolts.com

Advertiser INDEX

Abacom Technologies	40	Cunard Associates	86	Industrologic, Inc.	8	PAIA Electronics	47	The RF Connection	85
ActiveWire, Inc.	45	DesignNotes.com	53	Information Unlimited	81	PCB123	47	TNR Technical, Inc.	88
All Electronics Corp.	68	Earth Computer Technologies	46	Inkjet Southwest	67	Polaris Industries	25	Unicorn Electronics	59
Alltronics	59	ECD, Inc.	46	Intronics, Inc.	24	Prairie Digital, Inc.	45	V & V Machinery & Equipment, Inc.	45
Andromeda Research	12	E.H. Yost & Co.	58	LabJack	24	Pulsar, Inc.	46	Viking Systems International	58
Autotime Corp.	31	Electro Mavin	56	Lemos International	46-47	Quality Kits	46	Weeder Technologies	56
AWC	58	Electronic Design Specialists	53	Linear Systems	19	R4 Systems, Inc.	46	Western Test Systems	26-27
Barrett Instruments	45	Electronix Corp.	10, 84	Lynxmotion, Inc.	89	Ramsey Electronics, Inc.	86	Zagros Robotics	18
Basic Micro, Inc.	4	Emerging Technologies, LLC	46	M2L Electronics	58	Resources Un-Ltd.	14		
Blue Bell Design, Inc.	19	EMAC, Inc.	9	Matco, Inc.	45, 47	Rogers Systems Specialist	53		
BotBash	34	ExpressPCB	58	Meredith Instruments	55	Saelig Co. Inc.	81		
Bret's Old Radios	31	Flashcut CNC	46	microEngineering Labs	85	Scott Edwards Electronics, Inc.	59		
C & S Sales, Inc.	29	Future Horizons	39	Micromint	9	SGC	77		
Carl's Electronics, Inc.	45	Gateway Electronics, Inc.	55, 59	Mouser Electronics	40	Shreve Systems	34		
Circuit Specialists, Inc.	90-91	Halted Specialties Co.	3	Mr. NiCd	58	Square 1 Electronics	55		
Cleveland Institute of Electronics	56	Hangtown Remote Video	45	Net Media	21	Syspec, Inc.	8		
Conitec DataSystems	84	H.T. Orr Computer Supplies	86	New Micros, Inc.	13	Technological Arts	89		
Corporate Systems Center	2	HVV Technologies, Inc.	45	Parallax, Inc.	Back Cover	Texas Instruments	15		

Your company could be listed here, too. Call us today for advertising information. 909-371-8497

AMATEUR RADIO & TV

Alltronics	59
Gateway Electronics, Inc.	55, 59
Ramsey Electronics, Inc.	86
SGC	77
The RF Connection	85

ASSEMBLY SERVICES

BATTERIES/CHARGERS

Cunard Associates	86
E.H. Yost & Co.	58
Mr. NiCd	58
TNR Technical, Inc.	88

BUSINESS OPPORTUNITIES

BUYING ELECTRONIC SURPLUS

Earth Computer Technologies	46
Rogers Systems Specialist	53

CABLE TV

CB/SCANNERS

CCD CAMERAS/VIDEO

Autotime Corp.	31
Circuit Specialists, Inc.	90-91
Hangtown Remote Video	45
Matco, Inc.	45, 47
Polaris Industries	25
Ramsey Electronics, Inc.	86
Resources Un-Ltd.	14

CIRCUIT BOARDS

Cunard Associates	86
ECD, Inc.	46
ExpressPCB	58
PCB123	47
Pulsar, Inc.	46
R4 Systems, Inc.	46
V & V Machinery & Equipment, Inc.	45

COMPONENTS

ECD, Inc.	46
Linear Systems	19
Pulsar, Inc.	46
Unicorn Electronics	59

COMPUTER

Hardware

ActiveWire, Inc.	45
Autotime Corp.	31
Corporate Systems Center	2
Earth Computer Technologies	46
Electro Mavin	56
Electronix Corp.	10, 84
Halted Specialties Co.	3
Rogers Systems Specialist	53
Shreve Systems	34

Software

R4 Systems, Inc.	46
-----------------------	----

Microcontrollers / I/O Boards

Abacom Technologies	40
AWC	58
Basic Micro, Inc.	4
Conitec DataSystems	84
EMAC, Inc.	9
Emerging Technologies, LLC	46
Industrologic, Inc.	8
microEngineering Labs	85
Micromint	9
Net Media	21
New Micros, Inc.	13
Parallax, Inc.	Back Cover
Prairie Digital, Inc.	45
Scott Edwards Electronics, Inc.	59
Square 1 Electronics	55
Technological Arts	89
Texas Instruments	15
Weeder Technologies	56

Printers/Printer Supplies

H.T. Orr Computer Supplies	86
Inkjet Southwest	67

DESIGN/ENGINEERING SERVICES

DesignNotes.com	53
Emerging Technologies, LLC	46
ExpressPCB	58
Flashcut CNC	46
Prairie Digital, Inc.	45
Pulsar, Inc.	46
V & V Machinery & Equipment, Inc.	45
Weeder Technologies	56

EDUCATION

Bret's Old Radios	31
Cleveland Institute of Electronics	56
EMAC, Inc.	9
R4 Systems, Inc.	46
Syspec, Inc.	8

EVENTS/SHOWS

KITS

Alltronics	59
Autotime Corp.	31
C & S Sales, Inc.	29
Carl's Electronics, Inc.	45
Earth Computer Technologies	46
EMAC, Inc.	9
Future Horizons	39
Gateway Electronics, Inc.	55, 59
HVV Technologies, Inc.	45
Information Unlimited	81
Inkjet Southwest	67
PAIA Electronics	47
Quality Kits	46
Ramsey Electronics, Inc.	86
Scott Edwards Electronics, Inc.	59

LASERS

Future Horizons	39
Information Unlimited	81
Meredith Instruments	55
Resources Un-Ltd.	14
Unicorn Electronics	59

MISC./SURPLUS

All Electronics Corp.	68
Gateway Electronics, Inc.	55, 59
Halted Specialties Co.	3
Linear Systems	19
Resources Un-Ltd.	14
Shreve Systems	34
Unicorn Electronics	59
Viking Systems International	58

PROGRAMMERS

Andromeda Research	12
Conitec DataSystems	84
HVV Technologies, Inc.	45
Intronics, Inc.	24
M2L Electronics	58
microEngineering Labs	85
Basic Micro, Inc.	4

PUBLICATIONS

Bret's Old Radios	31
Future Horizons	39
Mouser Electronics	40
Texas Instruments	15
Square 1 Electronics	55

RF TRANSMITTERS/RECEIVERS

Abacom Technologies	40
Lemos International Co., Inc.	46-47
Matco, Inc.	45, 47

ROBOTICS

Blue Bell Design, Inc.	19
BotBash	34
HVV Technologies, Inc.	45
LabJack	24
Lemos International Co., Inc.	46-47
Lynxmotion, Inc.	89
Net Media	21
New Micros, Inc.	13
Zagros Robotics	18

SATELLITE

SECURITY

Information Unlimited	81
Lemos International Co., Inc.	46-47
Matco, Inc.	45, 47
Polaris Industries	25

STEPPER MOTORS

Alltronics	59
------------------	----

TELEPHONE

TEST EQUIPMENT

Barrett Instruments	45
C & S Sales, Inc.	29
Circuit Specialists, Inc.	90-91
Conitec DataSystems	84
DesignNotes.com	53
Electronic Design Specialists	53
Electronix Corp.	10, 84
Intronics, Inc.	24
LabJack	24
Prairie Digital, Inc.	45
Saelig Co. Inc.	81
Syspec, Inc.	8
Western Test Systems	26-27

TOOLS

C & S Sales, Inc.	29
Electronix Corp.	10, 84
The RF Connection	85

WIRE/CABLE & CONNECTORS

Rogers Systems Specialist	53
The RF Connection	85

September Is Back-To-School Time

By Gordon West

...You get to write next year's Technician test ...

Federal Communications Commission (FCC) Rule 97.503(b) indicates that a written examination for an entry-level ham license and an upgrade must be constructed as to prove that the examinee possesses the operational and technical qualifications required to properly perform the duties of an amateur service licensee. FCC Rule 97.507(b) states that each question set administered to an examinee must utilize questions from the applicable question pool. FCC Rule 97.523 indicates that it is the responsibility of all of the Volunteer Examiner Coordinators to cooperate in maintaining the question pools, and this responsibility is carried out in the VEC's Question Pool Committee (QPC).

The QPC is presently soliciting Technician class Element 2 questions and answers from the general public and ham radio operators for the new Technician class entry-level test that goes into effect July 1, 2003.

The process of rewriting an entire examination is enormous. It is carried out by the following QPC members:

- Scotty Neustadter W4WW, Chairman
- Bart Jahnke W9JJ
- Fred Maia W5YI
- John Johnston W3BE

The submission of new-ham, entry-level, Technician class, Element 2 questions for consideration by the QPC must be accomplished immediately! Licensed ham operators who wish to submit questions or suggestions to the QPC may do so at qpc@arrl.org. This will send their proposed questions and/or suggestions to all of the committee, and the



Write questions about guest operations at another ham station. Gordo (left) at the United Nation's station.

QPC indicates they have received some initial inputs on the proposed question pool syllabus, and are hopeful they will get more input to the actual question writing.


The proposed draft syllabus for the new Element 2 amateur radio examination was released for public comment a few months ago with a closing date of May 9, 2002. The closing date for question input to the QPC is August 31, 2002. This leaves us with not much time to get busy creating new, fresh, entry-level, Technician class questions that will fit into the following subelement sections:

- | | |
|-----------------------|---|
| Subelement T1 | FCC Rules, five questions on the examination |
| Subelement T2 | Methods of Communication, two questions on the examination |
| Subelement T3 | Radio Phenomena, two questions on the examination |
| Subelement T4 | Station Licensee Duties, three questions on the examination |
| Subelement T5 | Control Operator Duties, three questions on the examination |
| Subelement T6 | Good Operating Practices, three questions on the examination |
| Subelement T7 | Basic Communications Electronics, three questions on the examination |
| Subelement T8 | Good Engineering Practice, six questions on the examination |
| Subelement T9 | Special Operations, two questions on the examination |
| Subelement T10 | Electrical, Antenna Structure and RF Safety Practices, six questions on the examination |

For every one possible test question on the exam, the pool may contain up to 10 possible questions to study. With 35 test questions, the pool must contain at least 350 test questions. You may see the draft syllabus in detail with additional explanations of each group by logging onto the ARRL web page at www.arrl.org.



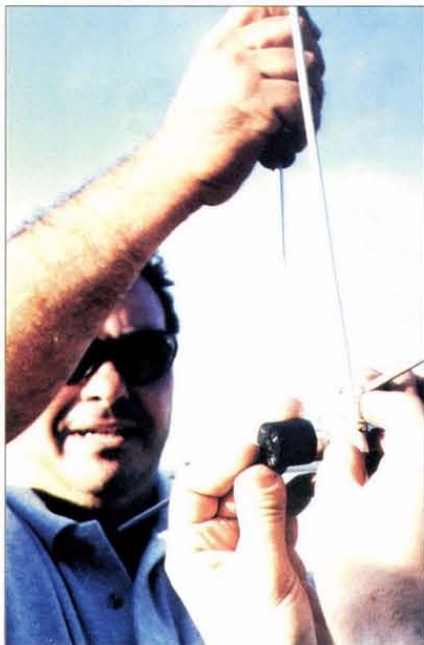Maybe some test questions on how long portable batteries last ...



Write some test questions on antenna assembly techniques.

Double-check the date that questions are due and make sure you are within the time frame for your question and four possible answers to be considered. FCC Rule 97.507(b) indicates that General and Technician class operators may prepare question sets for Element 2 exams. Grandfathered Advanced class operators and Extra class operators may also submit test questions.

If you're not a licensed amateur operator, I encourage you to take part in this Technician class examination rewrite by logging onto the ARRL web page, downloading the new Element 2 syllabus, and emailing the Question Pool Committee at qpc@arrl.org. Your suggestions to the committee will certainly be appreciated since they are coming from someone with a technical background who has not yet passed their entry-level Technician class ham test. So even though you are not a licensed amateur operator, your suggestions to the overall question pool for obtaining a brand new ham license will certainly be reviewed.

Suggested questions should specifically spell out exactly where in the syllabus the question is intended. The question is emailed to the QPC in your own words, as clear and as short as possible. You would then supply four multiple-choice answers which places a heavy burden on the author. It requires writing one absolutely correct answer, and three absolutely wrong, but very plausible, answers.

Further, each question and answer set must also indicate where the QPC may look up a reference to this question for authentication. This is

a job in itself; and unless the question you submit is really off the wall, I wouldn't worry about pouring over a textbook to find an exact match. Just get the question and four possible answers into the QPC within the time frame.

If you wish to view the present Element 2 entry-level Tech test, you can see it at www.hamtest.com, or www.arrl.org/arrlvec/pools.html.

John Johnston of the QPC comments, "... The questions should be such as to encourage learning of the material. Making the questions harder than required not only discourages possible candidates, it encourages rote memorization of the correct answers. An increasing number of successful examinees appear to openly admit they learned nothing from the qualifying examination experience. This development could be the underlying reason why there is so much concern about the exam being dumbed down." Johnston was formerly with the FCC and helped construct the brand new Element 2 entry-level examination syllabus with Fred Maia W5YI.

"The questioners, apparently, do not accept the notion that memorizing the answers to a series of questions is a valid way to learn how to operate an amateur station properly," adds Johnston, who wants to encourage all licensed ham operators to beat the deadline and propose new entry-level Element 2 Technician class questions that will replace old Element 2 Tech questions due to expire June 30, 2003.

So the new July 1, 2003, entry-level Tech test depends on input from both licensed amateur operators, as well as suggestions from those of you with a technical background who have yet to take your entry-level exam. The QPC members are a divergent group of individuals with backgrounds ranging from rocket scientists to retired FCC G-men. The committee, in my opinion, has become so rigid in the past to work with new ideas that all of the present question pools have become stagnant. For the past several years, each question pool receives a topical review and small change here and there, but no pool in the past — under the control of the QPC — has ever undergone a complete rewrite that is now before us for our comments, suggestions, and new-question input. The Question Pool Committee must spend hundreds of collective hours

pouring over the old and newly suggested questions, all this without pay and in between their normal work week. While any and all questions are appreciated, the QPC asks each question submitter to review the style of how old questions and answers have been incorporated in the old pool, and follow this style for new questions and answers. The more professional your question input, the greater chance of that question appearing on next year's entry-level examination.

If ever you wanted to make a difference on the ham radio entry-level



Write some test questions on RF safety procedures — very important on microwave X band frequencies.

How to Submit Suggested Element 2 Questions.

(1) All proposed questions must be no longer than 210 characters including spaces and punctuation. (Three lines of 70 characters each.) This requirement exists to facilitate implementation of computer testing and use of software-generated examinations by VE teams. Try to be concise as much as possible.

(2) Each question must be accompanied by four possible multiple-choice answers only one of which is correct. Be certain that the three incorrect answers are definitely wrong and cannot be construed as correct. Each multiple choice answer is limited to 140 characters. (Two lines of 70 characters.)

(3) Include any schematic diagrams or symbols that are necessary to answer the question. It is desirable to have more than one question relating to a single diagram. A text-only version of the question also would be helpful for use in examinations for the sight impaired.

(4) The question comprehension level should be on the Middle or Junior High School reading and math skills level. Remember that many youngsters are administered the beginning Technician Class examination.

(5) It is very helpful to include a reference from a published source confirming the correct answer. Questions on FCC Rules should reference the appropriate regulation.

(6) All suggested questions should be on the topics included in the syllabus (outline) listed here. Indicate the "Subelement" and "Topic" number at the top of the question. For example, a question on Ohms Law would list "Subelement: T7, Topic: T7A" above the question.

(7) Here is an example of a properly submitted question:

Subelement: T7, Topic: T7A

Correct Answer: D

Reference: Part 97.3(b)(6)

What is the term for the average power supplied to an antenna transmission line during one RF cycle at the crest of the modulation envelope?

There will be approximately 350 to 400 questions in the new Element 2 pool. It will be released to the public on December 1, 2002 and the new Element 2 questions must be used in all Technician Class examinations administered on or after July 1, 2003.

examination beginning next July 1, 2003, *now is the time*. You have only a few days to meet the deadline for submitting your new Element 2 Technician class questions and answers to the Question Pool Committee. If every ham submitted just one or two questions for the entire pool, the QPC would have more than enough material to work with.

Let's hear from you all, ham and non-ham alike! NV

NEW EXTRA CLASS STUDY MATERIALS

Gordon West WB6NOA announces the release of his new Extra class Element 4 FCC license preparation book and six long-play audio cassettes. Both the book and tapes cover the new Extra class test questions effective July 1, 2002, through June 30, 2006.

"My book and tapes will instantly explain that the new longer Extra class question pool is absolutely no harder to learn than the original question pool," comments West, well known for his humorous style of amateur radio and commercial radio training books and audio cassettes.

"The all new Extra class test is actually easier to prepare for because some of the complicated old questions were eliminated, and all new questions are actually reworked Advanced class and old Extra class questions," adds West, who has identified the most new questions on the Extra class test as the simple new rules and regulation topics.

The West six-tape audio course parallels the book and adds all of the radio sounds behind many topic areas within the question pool. You will hear the sounds of PSK-31, get a laugh out of some repeater calls, and you won't believe your ears when you hear the incredible sounds of phantom voices bouncing off an aurora.

The book and tapes cover all 801 questions, answers, and an upbeat description of the correct answer. West also reveals some of his classroom secrets on how to spot many of the technical correct answers before you begin to work out the problems on your calculator. All calculator keystrokes are clearly explained for those hams who may be a little rusty with trigonometry!

"I make the learning process fun — passing the Extra class test is simply a formal pre-requisite to the real learning that takes place after our students get onto their new privileges on the airwaves," adds West, best known for his training of eight out of 10 newly licensed hams and upgrade students with his nationwide classes, books, and audio tapes over the past 35 years.

All Gordon West training materials are published by **Master Publishing, Inc.**, and all of his materials are available at ham radio dealers throughout the country and mail order from the W5YI Group by calling 1-800-669-9594. Gordon West Technician and General class books for beginners are available at all RadioShack stores throughout the country.

West regularly travels throughout the country attending hamfests and offering training classes, and his on-the-air activities exemplify his active participation in the amateur radio service.

- A. Peak transmitter power
- B. Peak output power
- C. Average radio-frequency power
- D. Peak envelope power

(8) If you are offering a suggested revision to an existing question, indicate the number of the question you are revising. The current Element 2 question pool may be found at: www.arrl.org/arrlvec/pools.html.

(9) Suggestions for new multiple choice questions should be directed to each of the following four QPC members:

Scotty Neustadter W4WW — w4ww@arrl.net

Bart Jahnke W9JJ — vec@arrl.org

Fred Maia W5YI — w5yi@w5yi.org

John Johnston W3BE — Johnston.John1@worldnet.att.net

The ten topics and questions currently in effect are:

- (1) FCC rules, nine questions; (2) Operating procedures, six questions;
- (3) Radio propagation, three questions; (4) Amateur radio practices, four questions;
- (5) Electrical principles, three questions; (6) Circuit components, two questions;
- (7) Practical circuits, two questions; (8) Signals and emissions, two questions;
- (9) Antennas and feed lines, two questions; and (10) Radio frequency safety, three questions. (Total: 35 questions)

The ten topics in new Element 2 syllabus are:

- (1) FCC rules, five questions; (2) Methods of communication, two questions;
- (3) Radio phenomena, two questions; (4) Station licensee duties, three questions;
- (5) Control operator duties, three questions; (6) Good operating practices, three questions;
- (7) Basic communications electronics, three questions; (8) Good engineering practice, six questions;
- (9) Special operations, two exam questions, and (10) Electrical, antenna structure, and RF safety, six questions. (Total: 35 questions.)

Two Step Tuning Step One: Pick up microphone. Step Two: Transmit.

(Please note: HF Tuning doesn't get much easier than this.)



SGC Smartuner™ HF Automatic Antenna Couplers

"For me and my radio dollar, there isn't a better coupler made!"

Jack Huebschen N9XRO

Power Input: From 1.5W - Up to 500W*
HF Frequency Range: From 1MHz - Up to 60MHz*
Up to 4,000,000 element combinations*

Five Sensor Devices

*Specs differ per model

"Undoubtedly the best piece of hamgear I have ever owned."

Ronnie Kane K9MNI

**Marine, Commercial, Amateur Radio,
Aviation, Special Applications**

Starting at \$249



www.sgcworld.com

Toll Free (800) 259-7331 • Tel (425) 746-6310 • Fax (425) 746-6384 • Email: sgc@sgcworld.com

Mailing: PO Box 3526, Bellevue, WA 98009 • Shipping: 13737 SE 26th St. Bellevue, WA 98005 USA

Circle #42 on the Reader Service Card.

Nuts & Volts Magazine/AUGUST 2002 77

Open Communication

HOW TO PUT 10 POUNDS INTO A FIVE-POUND BAG Or Squeezing Higher Data Rates Into Narrower Bandwidths

Today, most communications and all networking are done digitally. The main exceptions are conventional telephones, AM/FM/TV broadcasting, and most two-way radio. But plans are already under way to make these digital before long. Most new cell phones use digital technology for voice. High definition (digital) TV is here now. Satellite TV is digital as are the new satellite car radios. And we will soon be getting Voice over IP (Internet Protocol) phones that transmit voice in digital packets via the Internet.

The essence of all this digital transmission technology is that information (voice, video, etc.) is translated into digital form and sent serially over some communications medium. The medium can be a twisted-pair cable, a coax cable, a fiber optic cable, or free space radio waves. Whatever.

The key specification of any data transmission system is speed, that is, how fast the bits can be streamed out over the transmission medium. And it is the bandwidth of the medium that really limits how fast the data can be transmitted. Bandwidth refers to the range of frequencies that the medium covers.

This article and the one to follow, explain how maximum speed is obtained with minimum bandwidth. **And you really need to know this!** The concept of how bandwidth and data rate are related is fundamental to the understanding of all modern communications systems and products. And knowing this explains so

much about what is going on in all communications devices and services whether it is cell phones, home networks enterprise networks, wireless radio, or the Internet. The really good news is that if you know this, all the future columns here and articles on communications in this magazine will be easier to understand and enjoy.

In this first part, "Baseband Communications," I explain about digital data, data rate, bandwidth, and how data is transmitted directly over a cable. In the second part (which will appear in the October issue), "Broadband Communications," I cover modulation techniques that not only speed up data on cables, but also make high-speed wireless data transmission possible.

Digital Data

Data communications take place by sending the binary 1s and 0s serially (one bit at a time) over some transmission medium like a cable or by radio. Figure 1 shows how the eight-bit word 10101100 is sent electronically with two voltage levels. The key characteristic of this serial bit-by-bit scheme is the data rate or speed of transmission. Data rate is expressed in terms of bits per second (bps), kilobits per second (Kbps), megabits per second (Mbps), or gigabits per second (Gbps). This speed or data rate is directly related to the time of occurrence of one bit (t).

$$\text{Data rate} = 1/t$$

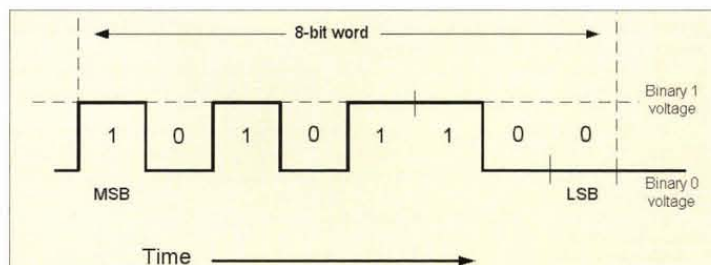


Figure 1. A binary serial data signal. Each bit is transmitted one at a time. This one shows the most significant bit (MSB) being transmitted first, but in some schemes, the least significant bit (LSB) is sent first.

If the bit time is 1 microsecond (1×10^{-6}), then the data rate is

$$\text{Data rate} = 1/1 \times 10^{-6} = 1,000,000 \text{ bps or } 1 \text{ Mbps}$$

If you happen to know the data rate and want to know the bit time, you just rearrange the formula:

$$t = 1/\text{data rate}$$

A data rate of 9600 bps has a bit time of

$$t = 1/9600 = .000104 \text{ second or } 104 \text{ microseconds } (\mu\text{s})$$

A good way to analyze a serial data stream like this is to assume alternating binary 0s and 1s so the signal looks like that in Figure 2. You can see that adjacent bits form one cycle (one positive pulse and one zero period) of a squarewave. The total time for this cycle (T) is called the period of the wave and is equal to two bit times or $T = 2t$. If we have a signal with a data rate of 50Kbps, the bit time is 20 microseconds. The period T then is 40 microseconds. Remembering the relationship between period and frequency — $f = 1/T$ — you can quickly figure out that we are dealing with a squarewave with a frequency of

$$f = 1/(40 \times 10^{-6}) = 25,000 \text{ Hz or } 25 \text{ kHz}$$

Now, the big question is how much bandwidth does it take to transmit this signal with minimum distortion and attenuation (loss)?

Duh ... what is bandwidth?

Bandwidth


Bandwidth is the frequency range passed by a given circuit or medium. Or it refers to the amount of frequency spectrum occupied by a specific signal, like the squarewave we just discussed. It is equal to the difference between the upper and lower cut-off frequencies of the circuit. $BW = (f_2 - f_1)$. See Figure 3. The lower (f_1) and upper (f_2) cut-off frequencies are those frequencies where the output voltage drops to 70.7% of its value over the pass band. Also known as the half-power or 3 dB down points, these frequencies define the upper and low limits of the circuit bandwidth.

For instance, bandwidth is the same as the frequency response of a circuit. A stereo amplifier may have a frequency range from 30 Hz to 22000 Hz. The bandwidth is $22000 - 30 = 21970$ Hz. Or, we can just round this off to 22000 Hz or 22 kHz. The amplifier passes audio signals with frequencies in this range.

Or consider the bandwidth of the ordinary telephone line which is from about 300 to 3000 Hz. That is a bandwidth of $3000 - 300 = 2700$ Hz. The frequency of voice fits in this range.

A low pass filter, or one that passes all frequencies up to an upper cut-off value including DC or 0 Hz, has a bandwidth equal to the upper cut-off frequency. An example is a voice filter that cuts off all frequencies over 4 kHz. Its

Figure 2. Alternating binary 1s and 0s produce a squarewave with bit time t and cycle period T .

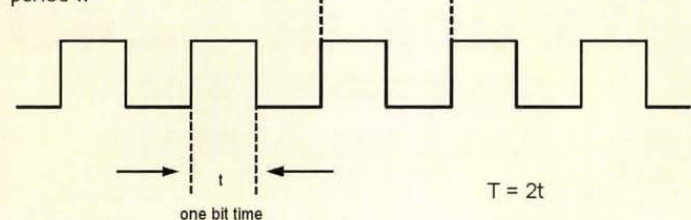

bandwidth is $4000 - 0 = 4000$ Hz or 4 kHz.

In radio or wireless, the bandwidth refers to the amount of electromagnetic spectrum assigned to a specific service. AM radio stations get 10 kHz, FM stations get 200 kHz, and TV stations get 6 MHz of bandwidth. Cell phones get 30 kHz, 270 kHz, or 1.25 MHz depending upon the type of system used.

Oh No ... Not Fourier!!

Okay. You now know about the speed of serial binary signals and bandwidth. Now let's put them together to see how they are related.

If you ever had any formal education in electronics, you have probably heard about the Fourier theory. Back in the 1700s, this French guy Fourier figured out that any non-sinusoidal wave can be described as being made up of a sinewave (called the fundamental) with a frequency equal to that of the frequency of the non-sinusoidal wave to which has been added one or more harmonic waves.

A harmonic is a sinewave that is some integer multiple of fundamental. For example, the second harmonic of a 1 kHz fundamental sinewave is a 2 kHz sinewave, the fifth harmonic is a sinewave with a frequency of 5 kHz, and so on. Fourier provided us with some higher level math that lets us figure out just what the frequency content is for any given non-sinusoidal wave.

The squarewave or alternating 1s and 0s we talked about earlier (Figure 2) is a classical Fourier case. It is made up of a fundamental sinewave to which has been added an infinite number of odd harmonics (3, 5, 7, etc.). Think of it as a signal generated by multiple signal generators all connected in series so that all the different sinewaves add together algebraically in phase. The composite output wave is the squarewave.

The higher frequency harmonics are responsible for the fast rise and fall times of the squarewave. But as it turns out, the higher harmonics have such low amplitude that we usually ignore them since they have such a small influence on the actual shape of the composite signal. Yet, when you see a squarewave, you should automatically think Fourier. That is, don't just see a

squarewave, instead, imagine that what you have is a bunch of harmonically related sinewaves traveling together. The best way to visualize this is in the frequency domain as Figure 4 illustrates. (See the sidebar on Time vs. Frequency Domains.)

Now, here is the point. If you want to transmit or amplify this squarewave, the transmission medium or amplifier must pass not only the fundamental sinewave, but most of the harmonics. Good squarewave transmission or amplification results if at least the 7th to 9th harmonics are passed.

Going back to the 50 kbps signal described earlier, remember that its frequency is 25 kHz. Let's assume that we get a good squarewave if we transmit up to the 7th harmonic or $7 \times 25 \text{ kHz} = 175 \text{ kHz}$. What this means is that the bandwidth of your transmission medium or amplifier must be at least 175 kHz. This is a pretty wide bandwidth. Bummer ...

If you limit the bandwidth by cutting off the higher harmonics, what happens is that the signal becomes rounded off. The rise and fall times of the squarewave increase and the abrupt changes of voltage levels are smoothed over resulting in a signal that looks more analog than digital. Figure 5 shows what happens as the upper cut-off frequency is lowered and bandwidth is narrowed. If you reduce the bandwidth to a frequency equal to the signal frequency, you effectively eliminate all harmonics from the output resulting in a sinewave of that frequency, in our case here 25 kHz.

In communications electronics, the major goal is more bandwidth. But so often, the case is we have no control over the bandwidth. We take what the cables give us or the spectrum assigned to us by the FCC.

You should realize that nearly all transmission media such as cables and most electronic circuits essentially act as low pass filters. All have some upper cut-off frequency because of the circuit or media characteristics. If that cut-off frequency is too low compared to the frequency content of the signal you are transmitting or amplifying, you eliminate or at least greatly attenuate the higher order harmonics and therefore distort the signal.

A quick, simple measure of the upper cut-off frequency and

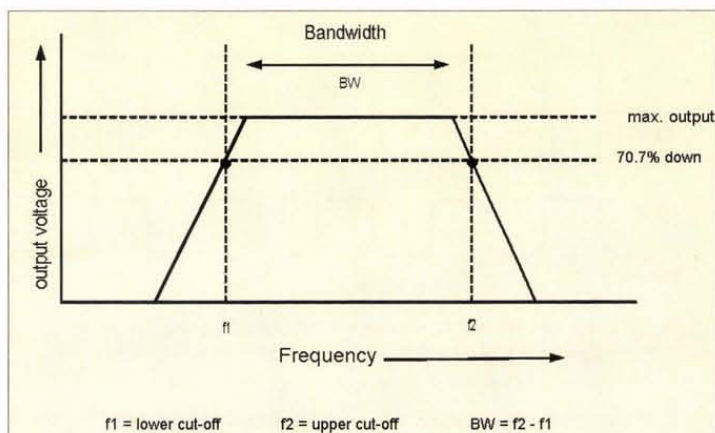


Figure 3. Bandwidth is the range of frequencies covered by a circuit or transmission medium and is the difference between the upper and lower cut-off frequencies.

bandwidth of a circuit or medium is to put a squarewave with a very fast rise time through it. Remember that the rise time (t_r) of a rectangular wave is the time it takes the signal to rise from its 10% amplitude point to its 90% amplitude point as Figure 6 shows. Then, measure the rise time of the squarewave at the output of the circuit or medium with an oscilloscope. Plug the output rise time value into the formula below to get the real bandwidth.

$$BW = .36/t_r$$

If the measured rise time is 80 nanoseconds, the bandwidth of the medium or circuit is:

$$BW = .36/(80 \times 10^{-9}) = 4.5 \text{ MHz}$$

To summarize the basic principle here, we can say that the wider the bandwidth, the higher the data speed can be before the filtering action of the medium or circuit rounds off the signal into a sinewave and begins attenuating the daylights out of it.

Narrower bandwidths can

only accommodate lower frequencies and slower data rates. Limit the bandwidth and you limit the speed. This is important to know because invariably it seems like virtually anything you do in electronics tends to limit or reduce bandwidth.

On the other hand, electronics is an on-going quest for higher speeds. Every engineering design battle being fought today has to reconcile this speed-bandwidth trade-off.

What Shannon Discovered

Earlier, we said that if the bandwidth was equal to 25 kHz, we could transmit a 50 kbps signal through it although the output will be a sinewave rather than a squarewave. Nevertheless, we could rejuvenate this signal by squaring it up in comparator or Schmitt trigger. This relationship holds up for any bandwidth and speed so we can express it mathematically as

$$C = 2B$$

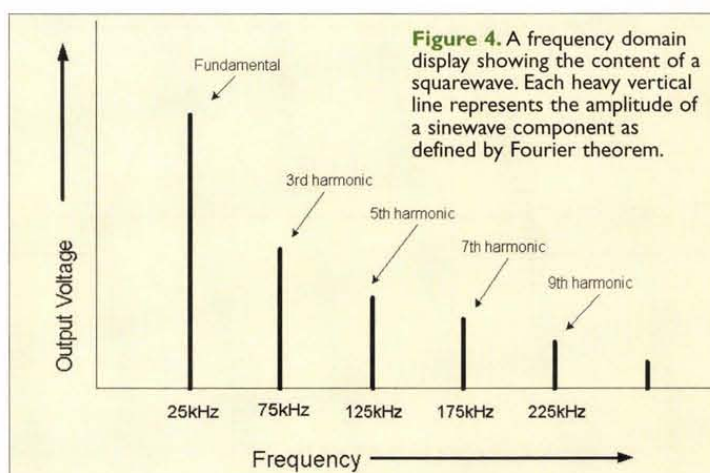


Figure 4. A frequency domain display showing the content of a squarewave. Each heavy vertical line represents the amplitude of a sinewave component as defined by Fourier theorem.

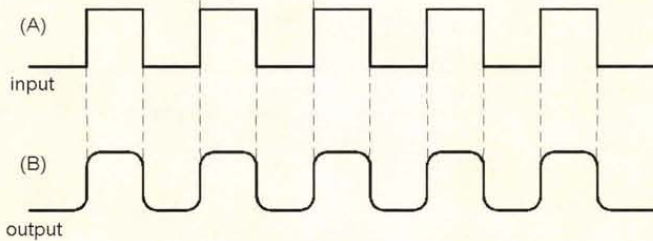


Figure 5. A squarewave or data signal is distorted by the circuit or medium and shows up as a rounding of the signal at the output.

C is the channel capacity or data rate in bps. B is just the bandwidth in Hz of the communications channel. If the bandwidth is 25 kHz, the data rate is

$$C = 2(25 \text{ kHz}) = 50 \text{ kbps}$$

You can rearrange this to find bandwidth from data rate or:

$$B = C/2$$

To transmit a 10 Mbps signal, you must have a bandwidth of at least:

$$B = 10 \text{ Mbps}/2 = 5 \text{ MHz}$$

This simple relationship pretty much defines the outer limits of data speed. In reality, the data rate is not only affected by the bandwidth, but also the noise in the system. Remember that noise is any random interference that occurs in a circuit or along a cable used for transmission. The greater the noise, the lower the speed for a given bandwidth. The relationship above just assumes no noise which is never the real case.

This basic relationship between speed, bandwidth, and

noise has been known for about 54 years since Claude Shannon of Bell Labs (now Lucent Technologies) discovered it and published it in 1948. Mathematically, it says that:

$$C = 3.32B \log(1 + S/N)$$

C and B are as defined earlier, while S/N is the power signal to noise ratio. The expression log means the common logarithm easily found on a calculator. For example, if the bandwidth is 25 kHz as before, but the signal-to-noise ratio is 1000/1 — which is sort of typical for a communication system — the maximum data rate would be:

$$C = 3.32 (25,000) \log(1001) = 249,036 \text{ Hz or about } 249 \text{ kbps}$$

Yikes! Adding in the effect of noise seems to give us even higher speeds in a given bandwidth. Unfortunately, Shannon's law gives us a maximum theoretical value that in reality cannot be achieved with a binary signal. As you will learn in the next article, it will take a multilevel signal to get that kind of data rate in a narrow bandwidth with noise.

TIME DOMAIN VS. FREQUENCY DOMAIN

There are two basic ways to look at a complex electronic signal. First, you can view the signal on an oscilloscope. What you see is the signal voltage varying over (with respect to) time as in Figure 2. This is how we normally look at or see signals in our minds. But there is another way.

Remembering that a complex, non-sinusoidal signal is made up of a fundamental sinewave plus many higher order harmonics, we can visualize the signal as a composite of individual sinewaves at different frequencies. This is what we call a frequency domain display. The squarewave in Figure 2 is made up of a fundamental sinewave plus odd harmonics. A frequency domain display is shown in Figure 4. Note that the display shows the amplitude of each sinewave as a line at its specific frequency. In many fields of electronics, a frequency domain display actually gives a better picture of what the signal really represents. This is especially true in communications.

To get a real frequency domain display, all you have to do is use a piece of test equipment called a spectrum analyzer. It looks like an oscilloscope in that it has a cathode ray tube (CRT) display. But what you see on the screen is frequency on the horizontal axis instead of time. You will actually see something like that in Figure 4 if you apply a squarewave.

Another way to get a frequency domain output is to use what is called the Fast Fourier Transform (FFT). This is a mathematical procedure carried out on a computer to give the frequency content of a signal. The complex signal is first digitized by a fast analog-to-digital converter. The binary output is then processed by a FFT algorithm program in a computer, usually a fast digital signal processor (DSP) chip. The output is a plot of the signal frequency spectrum. DSP FFT is widely used in communications applications.

Baseband Transmission

So, let's apply what you now know. First of all, baseband transmission is the process of applying the serial binary data signal directly to a cable so that it travels from transmitter to receiver. Much of network communications uses this method. The telephone system uses baseband. Ethernet local area networks (LANs) and SONET (synchronous optical network) fiber metro and wide area networks, and the Internet backbone use baseband. RS-232, USB, and IEEE1394 computer interfaces are baseband.

When you apply a high-speed digital signal to a cable, the cable has a major effect on the signal. The most commonly used cables are twisted-pair and coax. These cables are not just connecting wires as in AC power cords or speaker cables. Network cables are transmission lines. When the

length of the cable is greater than about $.1\lambda$ (one-tenth wavelength) of the signal to be transmitted, the cable becomes a transmission line and acts like a complex reactive circuit rather than just wire with resistance. (Note: One wavelength (λ) is equal to 300 divided by the frequency in MegaHertz or $\lambda = 300/f_{\text{MHz}}$) The equivalent circuit of a transmission line is shown in Figure 7. You may recognize it as a big low pass filter with series inductances and resistances and parallel or shunt capacitance.

Just imagine what happens when you apply pulses to this. The shunt capaci-

ties charge through the series resistances and inductances. Because of that thing called time constant, it takes a finite amount of time for the cable capacitance to charge. If the speed of the pulses is too fast, the capacitance will not fully charge before the pulse shuts off and the next one comes along. Therefore, the output of the cable is a somewhat rounded version of the input.

The cut-off frequency of a transmission line depends upon many factors such as the inductance and capacitance per foot and the length. Type of insulation (dielectric) in the cable has a major impact. In any case, twisted-pair telephone cable and category 5 (CAT5) Ethernet cable can handle low speeds nicely and high speeds over shorter lengths. Coax has a huge bandwidth and can handle signals up to almost 1 GHz depending upon length, but the attenuation is enormous for higher frequencies and greater lengths. But because both types of lines are low pass filters, they do filter out the higher-level harmonics in any digital signal applied to them.

The cut-off frequency of the equivalent low pass filter varies with the length. The result is severe rounding of the signal. As long as cable lengths are kept reasonably short (less than about 100 feet or so), the digital data shows up at the other end without too much attenuation, distortion and rounding. Now you can see why cable length and type are so important in any data transmission scheme.

To transmit data over longer distances, the signal can be reju-

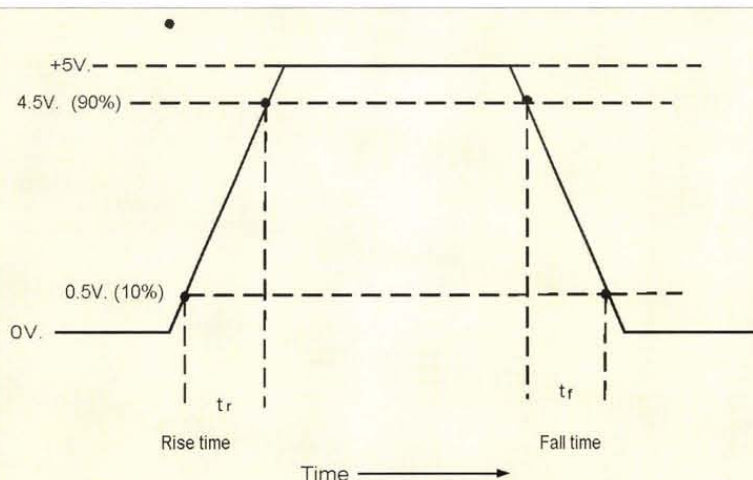


Figure 6. The way to figure the rise and fall time of a pulse.

Open Communication

venated every 100 feet or so, and reshaped and then retransmitted. This is a real pain and very expensive so we do everything we can to avoid this, but it is done.

Another approach is to switch to fiber optic cable where the digital data turns a laser off and on and transmits the data as infrared light pulses. Or finally, you can modulate the data onto a carrier

and transmit it on a cable or by radio (wireless). Transmitting data by modulating it on a carrier is known as broadband, and that is the subject of Part 2 of this article. **NV**

Open Communication is a bi-monthly column. Part 2 will appear in the October 2002 issue.

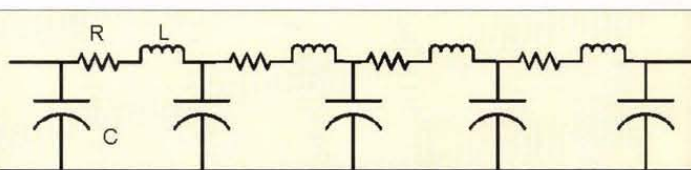


Figure 7. The equivalent circuit of a transmission line is a low pass filter whose cut-off frequency is determined by the cable length and characteristics and the signal frequency.

WIN with Nuts & Volts

PAID SUBSCRIBERS ARE AUTOMATICALLY ENTERED EACH MONTH!

This month's sponsor ...

BASIC MICRO, INC.

www.basicmicro.com

See their ad on Page 4!!



The New Basic Micro Atom offers built-in features like upgradeable firmware, Analog-to-Digital, Hardware Serial, In-Circuit Debugging, 32-Bit Math, 32-Bit Floating Point Math, and more! Watch your program run step-by-step as the Atom executes each line of code. Easily debug your code! Bring your programs to life quicker than you ever thought possible!

BIG WINNER Roy Lippin of Fort Lee, NJ

To Subscribe — Just fill in and mail the card supplied in the magazine or call our toll free order line at (800) 783-4624 with a Visa or MasterCard. If you do not wish to order a subscription, but would like to be entered in our drawing, simply send or email your name, address, and telephone number to *Nuts & Volts*, 430 Princeland Ct., Corona, CA 92879 or drawing@nutsvolts.com. No phone entries accepted. All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

AMAZING DEVICES

NVEN22001EVEN

See and Order from Our "Action" Web Site at www.amazing1.com

Laser Window Bounce Listener

Powerful listening system, yet simple in operation. You shine a laser at a window and intercept the reflected beam with our ultrasensitive filtered optical receiver. Vibrations on the window from internal sounds and voices are now clearly heard. Range can be up to several hundred meters depending on laser power and optics used.

LWB9 Plans for 3 Laser Window Bounce Systems.....\$20.00

LWB6K Kit of 100' visible red for Science Project.....\$129.95

High performance modules require housing and simple alignment to make a field worthy LASER WINDOW BOUNCE unit. Shows test tone circuitry, optics and our lab method of a completed assembly

LWB90 Assembled receiver, 10 mw IR laser, collimator etc.....\$449.95

Pain Field Pistol

Caution! Do not aim at people!

Blast out rodents with high power ultrasonics.

Handheld and battery operated with all controls.

Rental units available.

PPP1 Plans.....\$8.00

PPP1K Kit/Plans.....\$49.95

PPP10 Ready to Use.....\$79.95

Hover Board

28 pages of data related to the most revolutionary advance in transportation. Cutting edge R&D

HOVER Plans and Data.....\$25.00

Anti Gravity

Float an object using anelectric force field. With handbook

GRA3 Plans/book.....\$20.00

GRA3K Kit Pwr Sup.....\$99.95

GRA30 Assembled above.....\$149.95

Jacob's Ladder

A 1/2" arc expands to over 4" as it travels up the Jacobs

Ladder evaporating in space.

Adjustable arc control

Uses safe high frequency

Safety shock shut down

Full 20" ladder length

110/220 vac 150 watts

JACK3K Kit.....\$149.95

JACK30 Ready to Use.....\$249.95

PLASMA FIRE SABERS

Kits, Parts and Accessories

Duplicates effect in the motion picture epic of the century!

Specify blue, gm, pur, red or yel.

Moving light appears to evaporate into space

Blades screw into handle for easy replacement

We stock all size and color blades, mauler adapters, tubes

digital drivers, and parts for authentic designs. **Wireless interactive sound modules change tone with motion**

SAB15 Assembled with 15" Blade.....\$39.95

SAB24 Assembled with 24" Blade.....\$79.95

SAB24K Kit.....\$59.95

SAB36 Assembled with 36" Blade.....\$149.95

SAB36K Kit.....\$129.95

30" Spark Tesla Coil

Create a spectacular display of nature's own lightning. Many amazing experiments possible.

See coil in action on our web site!

BTC4 Plans.....\$20.00

BTC4K Kit.....\$899.95

BTC40 Ready to use.....\$1199.95

Smaller Version (8-10" Sparks)

BTC3 Plans.....\$15.00

BTC3K Kit.....\$349.95

BTC30 Ready to Use.....\$449.95

MINI TESLA COIL Lights 4" light tube!

MTC1 Plans.....\$5.00

MTC1K Kit.....\$19.95

MTC10 Assembled for 12 volts.....\$34.95

Take Control!! Electronic Hypnosis

Electronic circuitry places subject under your control! Induces ALPHA relaxed mind states.

HYP2 Plans.....\$10.00

HYP2K Kit/Plans.....\$49.95

HYP20 Ready to Use.....\$69.95

MIND2 Plans for Mind Control.....\$15.00

MIND2K Kit/Plans.....\$49.95

MIND20 Ready to Use.....\$79.95

6 Transmitter Kits

1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter.

2 1 Mile+ Telephone Transmitter.

3 Line Powered Phone Transmitter Never Needs Batteries!

4 Tracking/Homing Beacon Beeping Transmitter

5 Video/Audio Rebroadcaster 1 Mi.

6 TV/FM Radio Disrupter. Neat Prank! Discretion Required

Includes Hints Using Wireless Devices

COMBOX Above 6 Kits/Plans.....\$59.95

COMBOP Above 6 Plans Only.....\$10.00

4 KV HV MODULE for hovercraft, plasma guns, antigravity, pyrotechnics. 12vdc input.

MINIMAX4.....\$19.95

Information Unlimited PO Box 716 Amherst N.H. U.S.A. 03031 E-mail <info1@xtld.com>

1 800 221 1705 Orders/Catalogs Only! Fax 1 603 672 5406 Information 1 603 673 4730 Free Catalog on Request

Pay by MC, VISA, Cash, Check, MO. Add \$5.00 S&H Overseas Contact for Proforma

Circle #46 on the Reader Service Card.

Use your PC as a scope and datalogger!

Parallel Port Scope
spectrum analyzer, and digital multimeter




ADC Virtual Instruments turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 1.2MS/s 12-bit or 333ks/s versions. Great for schools, test depts, etc. Input to Excell LabView/NT drivers included.

Environmental Logging
record temperature, humidity, etc.



ENVIROMON - temperature (thermistors), humidity & light sensors, door position, etc. Record for 365/24 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use TC-08 for most thermocouples.

DRDAQ for PCs
sciencelogger with sensors

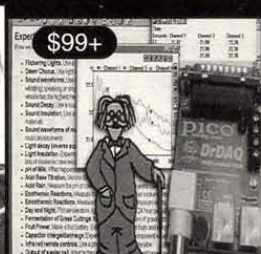

DRDAQ - is a PC adapter with sensors for light, pH, volts and temp. Great for science fairs! Supplied with ready-to-run software and lots of physics/chem exp'ts.

Download FREE demo software. Sales only: 1-888-7SAELIG

www.saelig.com 716-425-3753 • -3835 (fax) saelig@aol.com

Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITlink 2-wire networks, RS232/422/485, CANbus, etc. See www.saelig.com for Product of the Month!

Circle #47 on the Reader Service Card.

Nuts & Volts Magazine/AUGUST 2002 81

PC-based Instruments!

TECH FORUM

QUESTIONS

I need an RF generator for an AM radio and one for a two-meter radio. A chip is okay.

#8021 Steven Sabean
El Centro, CA

I am still using my Commodore 64C. I have a Memory Expander (COMMODORE 1764), but no program for using it. Can someone

tell me where to get a program or give me the listing for a basic program?

#8022 Robert W. Ritchey
via Internet

I need a high voltage power source, similar to what my high school chemistry teacher had, to conduct some electrical experiments. He could adjust the voltage and current using knobs and had various connectors for different implements. The voltage

This is a READER TO READER Column. All questions AND answers will be provided by Nuts & Volts readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and NO GUARANTEES WHATSOEVER are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

Send all material to *Nuts & Volts Magazine*, 430 Princland Court, Corona, CA 92879, OR fax to (909) 371-3052, OR email to forum@nutsvolts.com

ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed. Be sure to include your mailing address if responding by email or we can not send payment.
- Your name, city, and state, will be printed in the magazine, unless you notify us otherwise. If you want your email address printed also, indicate to that effect.
- The question number and a short summary of the original question will be printed above the answer.

- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

QUESTION INFO

To be considered

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

Information/Restrictions


- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

Helpful Hints

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address, Phone Number, and email. Only your name, city, and state will be published with the question, but we may need to contact you.

I would like to build a buzzer circuit that would wake me up at night whenever someone enters our backyard through our side gate.

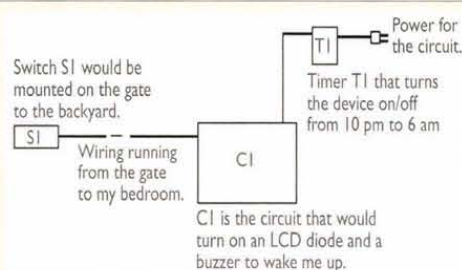I've provided a schematic of what I think it might look like and would be very thankful for any help.



George Peschke
hueygeorge@attbi.com

range was 10,000 to 250,000 volts and ran on a 120 volt outlet. I cannot locate this in any lab supply books or in any electronics supply places. Please help me so I may do some of the experiments in your magazine.

#8023 David Laney
daffet1968@hotmail.com

Does someone have a schematic and parts list of a LED third brake light that flashes a few times and then is on? Or where can I find a kit?

#8024 Dorian Pond
via Internet

I need to be able to measure and record the voltage coming into my house with my PC. I'm looking for a circuit that will translate 240 Vac into something that I can read through the serial port of my PC.

#8025 Duncan Hudson
Chagrin Falls, OH

I have an LED sign by Dynasty Classics in Compton, CA. It has a serial port on the back for the keyboard. Can it be interfaced to the serial port of a PC and what program would I need to change the message? I wrote to them, but didn't receive any response.

#8026 Robert W. Ritchey
via Internet

Does anyone have a cheap and dirty design for an analog video signal level monitor. I would like to use it with my CCD cameras to detect motion in their field

of view. Any help would be appreciated.

#8027 Norm Walton
KB0SAX
nw2258@micoks.net

ANSWERS

[5029 - MAY 2002]

Looking for a 230V circuit to raise the current into a lamp at dusk, and also remove the current surge into the filament and prolong its life.

Referring to "Edison" type lamps with tungsten filaments. To prolong your lamp life, lower the operating voltage. A 10% lower voltage will double the lamp's life; a 20% lower voltage will quadruple the lamp's life. This can be done with a small transformer that bucks out 10% of the voltage fed to the lamp. If you want to make your lamps last forever, connect two same-wattage lamps in series, so they run on half the voltage. They are not as bright, so use bigger lamps.

You can buy devices that stop the inrushing current when the lamp is turned on. PowerMizer is a disk that is inserted under each bulb, allowing the lamp to light more gently. On the web, go to: Galaxymall.com/products/EverlastProducts/PowerMizer.html.

Joseph Kish
Clackamas, OR

[6024 - JUNE 2002]

I have an application for salvaged motors from hard drives.


[7026 - JULY 2002]

I'm trying to build a remote control circuit to toggle four relays on/off using a Linx Technologies Keyfob CMD-KEYX-418 transmitter/encoder and a matching Linx RXD-418-KH receiver/decoder. Could someone design a circuit to do this or give me some suggestions.

The Apr. '02 issue of *Nuts & Volts* contained a remote control article that used Linx RF modules with Motorola encoder and decoder. The receiver circuit illustrated how a relay can be toggled on and off by the transmitter.

The Linx modules specified, include a different encoder and decoder, but the principle of operation is the same.

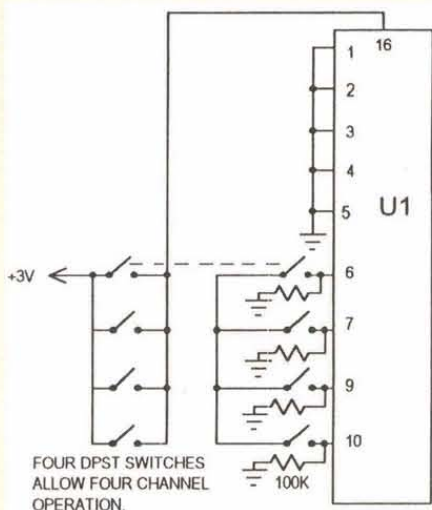If a MC145027 decoder is used instead of the MC145028 as shown in the Apr. '02 article, four relays can be toggled on and off by the transmitter. To accomplish this, the transmitter should be equipped with four DPST push-button switches as shown in the accompanying diagram.



The MC145027 decoder contains four data output terminals (pins 15, 14, 13, and 12) that correspond to the four data inputs of the encoder chip in the transmitter.

When one of the four switches is closed to transmit, one of the address lines of U1 is set to logic one for a unique data configuration. The corresponding data output terminal of the MC145027 in the receiver (pins 15, 14, 13, and 12) will then go to logic one. This voltage can then be used to operate a JK flip-flop — as shown in the article — to toggle the desired relay.

Anthony Caristi
Waldwick, NJ

My problem is that I don't know how to wire them. They appear to have some control circuitry built in, and have several connecting wires. For example, a Nidec 4515-3BCA-01 (P/N004060802) has six connecting wires. I'd like to get this motor to run at full speed.

The six wires indicates that it is most likely an electronically commutated DC motor. Three wires are for a three-phase brushless stator winding in delta connection and the other three are for the rotor position sensors.

There are several integrated brushless commutator ICs, such as the LM621 or MC33035 on the market, specifically designed to do just that. Look at which IC is being used and get the data sheet from the manufacturer.

Another approach is to find units where the motor control circuitry is on a separate board and use it with the motor (you need to identify power, enable, forward,

and maybe other signals).

Walter Heissenberger
Hancock, NH

[7028 - JULY 2002]

I'm looking for a parts source for a projection dial radio from the 1930s. Fair Radio Sales does not carry the projection dial film or other parts. I remember the name "Antique Electronics Supply" from a few years ago, but I do not know if they are still in business and have what I need.

Antique Electronics Supply is alive and well and can be found at: phone 480-820-5411; web www.tubesandmore.com.

Another company which may be more helpful is Rock-Sea Enterprises, who specializes in dial scales for antique radio gear. Their address is:


Rock-Sea Enterprises
323 E. Matilija St., #110-241
Ojai, CA 93023

[6026 - JUNE 2002]

I was wondering what circuit is behind the flash trigger on a 35mm SLR camera. I measured the flash trigger and it read around 0.05 VAC. When I press the shutter button it jumps to .33 VAC, then trickles back down.

I would like to trigger a relay or turn on a transistor, but this AC voltage is so low. What kind of simple circuit do I need?
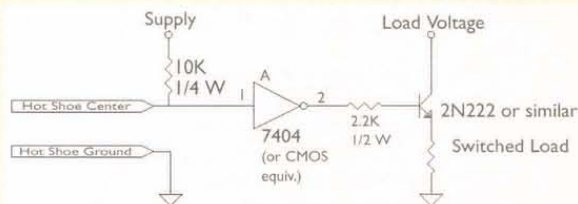
#1 A simple non-contact device that will provide a switched output is a slave strobe module, which should be available from better camera stores. Or, you could roll your own. Home-made or store bought, these devices utilize a phototransistor which detects the flash from the camera being fired and turns on an output transistor briefly, which fires a slave strobe connected to the module.



Or any other low-voltage, low-current apparatus attached to it. You will find "light detector" circuits in just about any electronics hobbyist magazine, including *Nuts & Volts*, or check RadioShack for any simple projects books. They are a good source for many parts also, should you wish to build your own.

Lee
via Internet

#2 The flash trigger (hot shoe or "coaxial" contact) is a simple low-current Normally-Open switch contact that closes when you depress the shutter. Just feed that contact into a TTL or CMOS inverter (i.e., 7404) and have the inverter drive the transistor (or other driver) controlling your "high current" device.

Ken Simmons
Auburn, WA

[6025 - JUNE 2002]


Cadmium zinc telluride (CZT) devices make great nuclear radiation detectors, but I've been unable to find any circuit diagrams to build one. Has anyone had any experience with these?

A radioactive source changes the resistance of the cadmium sulfide photocell.

The transistor amplification

converts the variation into a signal that actuates a relay or other control element. You can use more sensitive [or larger sensors] like the Cadmium Zinc cell and also increase the gain on the transistor amplifier circuit by using additional stages or higher gain transistors to increase the sensitivity.

Chris
Bieber, CA

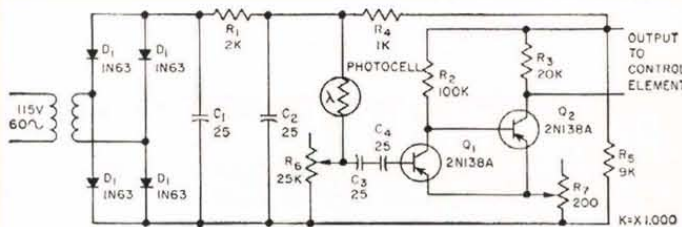

A web site that will also point you to other sources is: www.antiqueradios.com/.

Phil Shewmaker
Louisville, KY

[5022 - MAY 2002]

I need a circuit to convert component video (Y,Pb,Pr) from my HDTV display in the living room to standard NTSC output, to display on my standard ana-

log color TV in the kitchen, via its component video inputs.

There are four questions in this Tech Forum that revolve around converting video from one format to another and it's no wonder. Movies, television, and cameras developed as inventors sought ways of producing visual information or conveying it from one location to another or storing

[6023 - JUNE 2002]

I'm looking for a high-voltage circuit tied to a car spark plug, to be used as an ignitor on a gas cooking grill. The unit I remember ran on a 12-volt, one-amp battery and used a car automotive coil.

#1 Here is a circuit which I built a few years ago as a tester for automotive ignition coils. It should work as a gas grill ignitor. It is similar to the circuit used in the old "breaker points and condenser" ignition systems.

S1, a normally open push-button switch, replaces the points. The plug will fire each time the switch opens. (The circuit for electronic ignitions is almost the same, but the points are replaced by a power transistor. The electronics controls the power transistor.) S1 should be a large-type switch, as the current is fairly high while the switch is closed.

R1 can be 0.5 or 0.47 ohms, or two 1 ohm, 10-watt resistors in parallel.


The value of C1 was determined by measuring the capacitance of a cap used in an old

"points and condenser" car. C1 reduces sparking of the points and increases the high voltage produced.

T1 can be almost any car ignition coil, for either a "points and condenser" or electronic system, if it is easy to mount and connect.

One type which looks good is the one used on many Chrysler vehicles in most of the 80s, specifically on the 1983 Chrysler LeBaron, the 1987 Plymouth Caravelle, and the 1987 Dodge one-half ton full-size van.

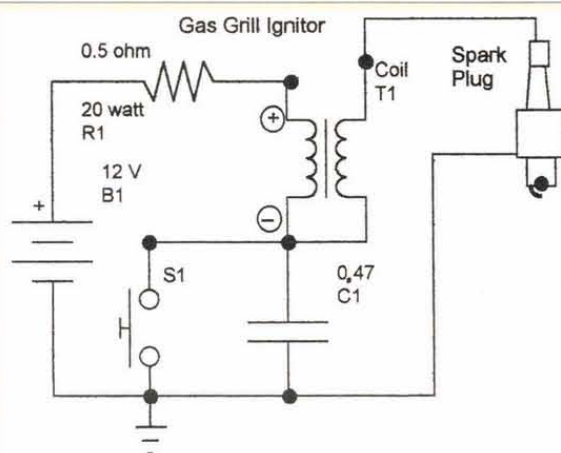This coil is a cylindrical shape with the + and - terminals clearly marked and easy to connect to. (If the + and - terminals are reversed, the circuit will still work, but the spark will be weaker.) If this coil is used, it will be necessary to make or buy a mounting clamp. If one is purchased, the type used on the 1983 Chrysler and the 1987 Plymouth should be



easy to mount (the one on the 1987 Dodge van is not).

Possible modifications include a larger resistance for R1 to reduce the current drawn and still get a satisfactory spark; changing the value of C1, which might make a better spark; and increasing the gap of the spark plug from that usually used in an engine.

An idea for improving the circuit — which I don't have time to try — is to use a solid-state circuit. A power transistor would replace S1, and be driven by a simple pulse generator. There have been circuits published for a single 555 IC with variable pulse rate and variable pulse width (duty cycle), which would drive the power transistor.

I think I would start with a pulse rate of about 20 Hz with a 50% duty cycle. It would be necessary to protect the transistor from pulses generated in the coil. To find a suitable protective circuit, I would start by looking at circuits for automotive electronic ignition. Several were published in electronic magazines in the 60s and 70s. If power to the circuit is switched by a push-button switch, a "continuous" spark will be produced as long as the switch is closed.

Bill Stiles
Hillsboro, MO


#2 A 555 timer chip operating in astable mode, driving an NPN power transistor such as 2N3055, makes a good driver circuit for an automobile ignition coil.

The timer chip generates a non-symmetrical squarewave at pin 3, which simulates the opening and closing of the breaker points of an automotive ignition system. The values of the resistors, and the timing capacitor connected to pins 2 and 6, determine the duty cycle and frequency of the squarewave. By experimenting with the resistor and

capacitor values, the spark characteristics can be controlled. A capacitor placed across the primary of the coil as shown may help in producing a stronger spark.

The high-voltage output of the ignition coil can be fed to an ordinary spark plug, which produces the spark. The body of the plug must be connected to circuit common (battery negative).

Anthony Caristi
Waldwick, NJ

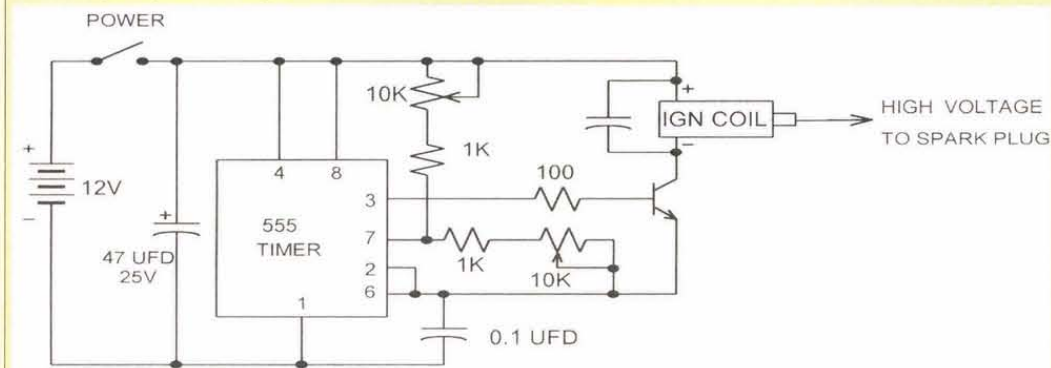

Do You Repair Electronics?

For only \$9.95 a month, you'll receive a wealth of information:

Repair data for TV, VCR, monitor, audio, camcorder, & more.

Over 100,000 constantly updated problem/solutions plus...

- TechsChat live chat room.
- UL/FCC number lookup.
- Private user discussion forums.
- Hot tips bulletin board.
- Automated email list server.
- Manufacturer information.

To access RepairWorld, direct your internet browser to <http://www.repairworld.com>

RepairWorld.com

Electronix Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878

WWW.CONITEC.NET

\$333
COMPLETE KIT

GALEP-4
UNIVERSAL PROGRAMMER

Introducing a pocket programmer with true **Universal Output**

Latest generation Galep-4 uses ASIC universal pin technology for each pin of 40 pin ZIF-socket. 1300+ device library / lifetime free updates. Programs 8/16-bit EPROM's, EEPROM's, 0-Power RAM, FLASH, Serial EEPROM's, GAL, PALCE, microcontrollers such as 87/89xxx, PIC, AVR, ST62, etc. Low voltage devices down to 1.3V. No adapter required for DIL devices. 8 hrs. operation on battery (AC charger included). Runs **WIN 98, NT, ME, 2000, XP** with Hex/Fuse Editor.

Remote control from other apps, (e.g. VisualBasic). Substitutes high priced universal programmers e.g. ALL-11 (HIL) or LAB-TOOL-48 (ADVANTECH). Providing virtually matching performance at only 1/3-1/5 the price. Info, orders, softw.: **619-702-4420**

Info, downloads: www.conitec.net

CONITEC DATASYSTEMS - 1951 4TH AVE, SUITE 301 - SAN DIEGO, CA 92101 - TEL: 619-702-4420 FAX: 619-702-4419

TECH FORUM

[7022 - JULY 2002]

Years ago, before complex counter chips, dividing a frequency was done with RS or JK flip-flops. It's easy to divide by a multiple of two, but 3, 5, or 7 required special configurations of the FFs. I wonder if anyone has retained these odd configurations so I don't have to reinvent them.

#1 Digging through dusty files, I found an article that answers your exact question: how to configure divide by N counters, using discrete flip-flops (and gates) for arbitrary N.

"Divide-by-N Circuit has 50/50 duty cycle" by David A Scott, Naval Weapons Center, China Lake in EDN magazine for July 5, 1973, pages 95 and 97.

This article provides a design technique, and demonstrates it for N = 3,4,5,6,7, and 11.

Other articles from the 70s show division techniques using shift registers (7496), presettable synchronous counters (74LS191), or CMOS counters (40161).

If you will send me an email address, I can scan it and email it to you.


Chuck
mcgregorc@yahoo.com

#2 It really makes no sense to use J-K flip-flops to

do this sort of dividing. However, here are the schematics to accomplish your task. Keep in mind the output is not a single clock pulse in width. For example, the divide by 5 circuit has a 3:2 duty cycle. Also, in order for these circuits to function, all of the Set and Reset pins must remain at ground potential.

A better way to accomplish this type of division would be to use 4017 counter. That way your output pulse would be 1 clock pulse in width for counts 0 through 9. The divide by 10 output has a 50% duty cycle.

Raymond Buck
Phoenix, AZ

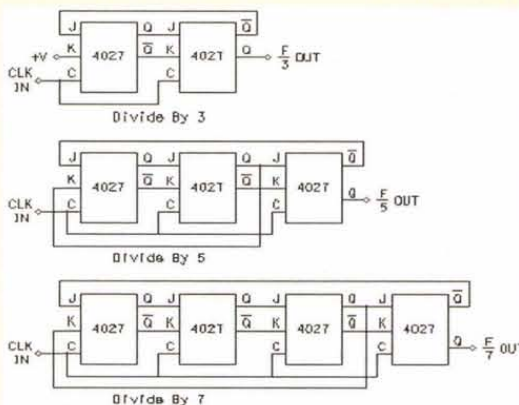

it for future use.

Industries grew up around these inventions using incompatible means to accomplish what on the surface seems to be a similar function.

Today "video" means NTSC, PAL, SECAM, DSS, composite, S-video (Y/C), YUV, RGB, and those are just some of the analog "standards."

"Video" also means HDTV, DTV, MPEG-2, YCrCb, and a few assorted digital "standards."

"Video" also means the signal we send to our computer monitors such as CGA, DVI, EGA, MDA, VGA, MAC, etc. "Video" even means the different resolutions possible on the same monitor (640 x 480 "video" is different from 800 x 600 "video").

Finally when you rent a "video" you are referring to a medium that can be VHS tape, DVD, or a pay-per-view video "stream" from a satellite.

Murphy's Law rules this entire kingdom and very few "standards" are easily inter-converted. Moreover, with 26 letters of the alphabet capable of forming over 17,000 three-letter acronyms (TLAs), I'm inclined to believe the number of types of "video" will increase for several years to come (and that ignores NTSC, MPEG, HDTV, and SECAM who have all broken through the three letter barrier).

[6028 - JUNE 2002]

I have heard that it's possible to control an air conditioner or other large motor, with PWM. I'd like to build a circuit that takes a TTL level PWM signal and switches 230 volts DC 20 or 30 amps at a 20 kHz rate to add specialized speed control to my table saw.

I've had IGBTs mentioned as a solution, but I don't know what they are.

#1 You are indirectly describing an inverter, a device which takes AC, converts it to DC and then back to AC, allowing you to vary the frequency. The bad news is that most inverters have a limited frequency range and current on output. Most inverter applications I've seen, involve modest speed control, are three phase, and handle 10-15 amps maximum.

In addition, many motors for these applications are listed as "inverter rated," and while I am not sure just what that means, I suspect it includes different construction techniques to allow the motor to perform well over a varied frequency range.

Inverters usually contain a modular IGBT (Insulated Gate Bipolar Transistor) array to perform the power switching function, with a microprocessor con-

trolled front end to determine frequency, control voltage and current, and monitor parameters such as phase loss, motor overload, etc. While it would be possible to control a table saw motor via inverter, it might be much cheaper to go "low-tech" and swap pulleys. Search the Internet for "inverters" and you will find a wealth of detailed information for your application.

Lee
via Internet

#2 First of all, you need to find out which motor is in your table saw. If it is an inexpensive one, with integral motor, you have most likely an AC series motor. Then you can use an inexpensive TRIAC type variable speed control (they are typically made for routers). These units sell for about \$25.00 and it will be hard to beat this. If you have an induction motor, then I suggest you read Electric Motors and Control Techniques by Irving M. Gottlieb. You will find all the necessary information there.

IGBT's are Insulated Gate Bipolar Transistors and are specifically designed for switching applications and have low drive requirements.

Walter Heissenberger
Hancock, NH

PICmicro MCU development tools
from microEngineering Labs, Inc.
www.melabs.com

LAB-X Experimenter Boards

Assembled development platforms. Each has RS-232 serial port, in-circuit programming connector, power supply, plus other hardware.

LAB-X1 for 40-pin (shown) - \$199.95
LAB-X2 for 28 or 40-pin MCUs - \$69.95
LAB-X3 for 18-pin MCUs - \$119.95



PicBasic and PicBasic Pro Compiler

Write programs for PICmicro MCUs in BASIC. Can be used in Windows or DOS (includes Windows editor/IDE software).

PicBasic Compiler - \$99.95
PicBasic Pro Compiler - \$249.95

EPIC Plus PICmicro Programmer

Programs the following PICmicro MCUs: PIC12Cxxx, 12CExxx, 14C000, 16C505, 16C55x, 6xx, 7xx, 84, 9xx, 16CE62x, 16F62x, 7x, 8x, 87x, 17C7xx, and 18Cxxx (some MCUs require adapters). Software for Windows and DOS. Requires two 9V batteries or AC adapter (not included). Adapters available for various device packages.

Bare PCB w/software - \$34.95, Assembled - \$59.95
Assembled w/AC adapter, cable and ZIF adapter - \$99.95



PICProto Prototyping Boards

\$8.95 to \$19.95

High-quality blank prototyping boards for PICmicro MCUs. Holds your microcontroller, 5-volt regulator, oscillator, capacitors, DB9-25 connector.

microEngineering Labs, Inc.

Phone: (719) 520-5323
Fax: (719) 520-1867
Box 60039, Colorado Springs, CO 80960

For product information
or to order online,
visit our website at: www.melabs.com

Circle #55 on the Reader Service Card.

The RF Connection
213 North Frederick Ave.
Suite 11NV
Gaithersburg, MD USA
20877

http://www.therfc.com/

Complete Selection of MIL-Spec Coax, RF
Connectors and Relays

UG-21B/U N Male for RG-213/214.....\$5.00
UG-21D/U N Male for RG-213/214.....\$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913.....\$6.00 Pins Only.....\$1.50
UG-21D/9913.....\$4.00 Extra Gasket......75

Amphenol 83-1SP-1050 PL-259.....\$0.90
UG-176/U Reducer RG-59/8X......25 or 5/\$1.00
UG-175/U Reducer RG-58/58A......25 or 5/\$1.00
Silver Teflon PL-259/Gold Pin.....\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F. 9913 with
High Density PE Foam dielectric, stranded
center cond. and Duobond III Jacket.....
.....80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket
Intro Price.....\$23.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom,
Kenwood, and Yaesu

8 Pin Mike Female.....\$2.50
8 Pin Mike Male Panel.....\$2.50
13 Pin DIN for Kenwood.....\$2.75
8 Pin DIN for Icom.....\$1.00
8 Pin DIN for Kenwood.....\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666
Info 301/840-5477
FAX 301/869-3680

Circle #56 on the Reader Service Card. 85

TECH FORUM

[6029 - JUNE 2002]

I have a portable CD player I'd like to play through the radio speakers in my car. I thought of buying a FM transmitter that would allow the player to act like another FM station - but they seem way overpriced.

Can someone provide me an inexpensive, circuit I can build?

#1 I think you are overlooking several limitations of your FM transmitter idea to transmit your CD player to your car radio.

1) Most of the FM transmitters you will find or can build are mono transmitters with only "phone" audio quality. 2) Even if you can find a stereo FM transmitter, you will have to modify it to accept a much higher level of audio from your CD earphone output.

You did not mention what kind of car radio you have. If your radio has a built-in cassette player as most standard car radios in the past 10 years are, your solution is much simpler. All you need is a simple Cassette Adapter (\$10-\$20), which is designed specifically for this purpose.


If your radio doesn't have a cassette player, you can probably replace the radio with a new one with a built-in CD player for about \$100.00, which is probably cheaper than your original FM transmitter idea.

Haim Sandel
Phoenix, AZ

#2 A simple FM transmitter can be constructed using a Maxim MAX2606 integrated circuit, as shown in the diagram. The MAX2606 is a voltage-controlled VHF oscillator chip that operates in the FM broadcast band. A nine-volt battery supplies power to the circuit.

The Left and Right audio output of the CD player is coupled to the voltage control input of the chip, where it will frequency modulate the oscillator. Two potentiometers are included in the circuit to control volume and oscillator frequency. Since this will be used inside of a vehicle, only a very short wire will be needed for an antenna.

Anthony Caristi
Waldwick, NJ

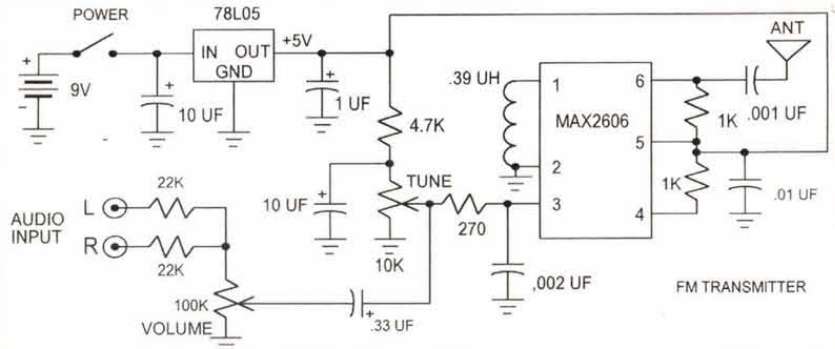

In short, a sense of humor and a sense of history are helpful in dealing with the present confusion.

I agree the MC1377 won't work and you are going to need some kind of scaling to get the 16:9 HDTV picture to look decent on your 4:3 TV. You face the same choice as broadcasters. Do you "chop off" the left and right sides of the screen or do you produce "letter box" video for the kitchen? Most video conversions are not do-it-yourself projects, but

that's for you to decide based on your own skill and desire.

Check the companies and sites below. This list spans \$89.00 to \$1,000.00+ products and some of the web sites have tutorials explaining the theory and trade-offs to various conversions.

Standards Organizations

www.atsc.org
www.fcc.gov
www.mpeg.org
www.smpet.org

Affordable Converters

www.aitech.com
www.focusinfo.com
www.jandr.com (PSC-1106 PC to TV \$90.00)
www.matco.com (UL-2000 VGA to Composite \$99.00)
www.polarisusa.com

Broadcast Quality Converters

Communication
Specialties, Inc.
55 Cabot Court

Hauppauge, NY 11788

Tel: (631) 273-0404

Fax: (631) 273-1638

www.commspecial.com

"Scan Do" video converters & "Deuce" video scalars

Analog Way

75 Maiden Ln.
New York, NY 10038
Tel: (212) 269-1902
Fax: (212) 269-1943
www.analogway.com

Extron Electronics

1230 S. Lewis St.
Anaheim, CA 92805
Tel: (714) 491-1500
Fax: (714) 491-1517
www.extron.com

FOCUS Enhancements

1370 Dell Ave.
Campbell, CA 95008
Tel: (408) 866-8300
Fax: (408) 866-4859
www.focusinfo.com

Folsom Research

11101-A Trade Center Dr.
Rancho Cordova, CA 95670
Tel: (916) 859-2500
Fax: (916) 859-2515
www.folsom.com

FSR

244 Bergen Blvd.
West Paterson, NJ 07424
Tel: (973) 785-4347
Fax: (973) 785-4207
www.fsrinc.com

Bob Miller
Trenton, NJ

PRIMECELL

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT
DON'T PITCH EM - SEND THEM FOR REBUILDING! - SAVE \$\$\$

- WE INSTALL NEW NI-CAD OR NI-MH BATTERIES INTO YOUR CASE.
- WE IMPROVE PERFORMANCE TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE. / EXTEND LIFE OF OLDER EQUIPMENT.
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US. / EST. 1986
- WE SAVE YOU \$\$\$ MONEY \$\$\$

WE SERVICE RECHARGEABLE BATTERY ASSEMBLIES FOR ALL TYPES OF ELECTRONICS.
RADIOS, SCANNERS, CORDLESS TOOLS, BAR CODE READERS, GPS, SCIENTIFIC, SURVEILLANCE

GENERAL ELECTRIC	UNIDEN	RADIO SHACK
MPD PLS MPA 4850P \$ 34.50	APX650 1050 1105 \$ 32.50	HTX 202/404 \$ 22.50
MPD PLS MPA 4860P \$ 39.50	1010 1070 1100 \$ 32.50	NEW NI-MH HTX pack
MPR MPS MPX 763/777 \$ 39.50	1120 1200 Series \$ 32.50	8.4V 1650mAh \$ 39.50
MONOGRAM 4506P/113 \$ 37.50	BP2500 650mAh \$ 19.50	
	BP205 1600mAh \$ 28.50	
MAXON SA-1155 1160 \$ 39.95		
	ICOM	KENWOOD
	BP2 / BP3 / BP22 \$ 19.50	PB2/6/33/34 \$ 28.50
	BP5 / BP23 / 24 \$ 27.50	PB7/8/9/13/14/18 \$ 34.50
	BP7 / CM7 / BP8 \$ 34.50	KNB6/7/12/14/16 \$ 34.50
	BP157/174/180 \$ 34.50	PB10/25/26/32 \$ 24.50
	CM140/141/166 \$ 41.50	
	YAesu	CORDLESS DRILLS
	FNB 3 4 12 14 16 \$ 32.95	50% MORE CAPACITY.
	FNB19 21 26 27 38 \$ 32.95	Any brand 7.2V \$ 21.50
	FNB 10 1117 26 36 \$ 23.95	Any brand 9.6V \$ 29.50
		Any brand 12.0V \$ 36.50
		Any brand 14.4V \$ 39.50
		Any brand 18.0V \$ 44.50

See our web pages about rebuilding battery packs used for Land Surveying.

BATTERY REBUILD SERVICE

FOR INFORMATION ABOUT YOUR REQUIREMENTS... CONTACT US:
USE THE EASY INFO. REQUEST PAGE AT <http://www.primecell.com>
PHONE OR FAX: (814) 623-7000 E-MAIL TO: sales@primecell.com
SEND PACKS FOR FREE QUOTATION BY: UPS, FEDEX, OR US MAIL

CUNARD ASSOCIATES INC., 9343 US RT 220, Bedford, PA 15522

REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Available for Canon, Epson, Hewlett Packard, Apple, Compaq, and Lexmark printers.

HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore, Texas Instruments, Centronics, Riteman, Apple, Printronix, Star

Over 300 different ribbons in stock.
All ribbons new, not re-inked.

Check our web page or write for complete price list.

H.T. ORR Computer Supplies
249 Juanita Way, Placentia, CA 92870-2216
714-528-9822 • FAX 714-993-6216
Toll Free 1-800-377-2023
e-mail: Htorr@aol.com
<http://home.adelphia.net/~htorr>

News Bytes

Continued from Page 59

and Local-Area-Network Gaming tournaments. Lulu Tech Circus also plans to actively involve user groups in the event via special meeting places and presentation opportunities.

Keeping with the circus theme, the event is divided into five rings — Artis Teka (Graphic and Media Arts), Expansive Education, Gear and Gadgets, Fun and Games, and Extreme Computing. More information specific to these "rings" can be found at www.lulutechcircus.com.

The format of Lulu Tech Circus gives attendees the freedom to focus on their area of interest, yet have the opportunity to experience the expanse the event has to offer in other technology areas. A signature feature is the Village Green, a gathering place for user groups and technology lovers of all ages. Information tables and meeting facilities are part of the Village Green, and are featured at each Circus event.

"Holding the first Lulu Tech Circus in Raleigh reflects on the overall health of the technology sector in the Southeast. For all the bad news about this industry recently, the number of new ventures and successful technology companies in the Research Triangle area is a positive statement for North Carolina," said Will Jahnke, President of Lulu Tech Circus, Inc.

Registration, future venues, and more information are available via the website at www.lulutechcircus.com.

Show hours and location for the Raleigh edition of Lulu Tech Circus: September 27-29, 2002; Friday 12-9, Saturday 10-9, and Sunday 10-6 at the North Carolina Fairgrounds.

CIRC Hosts New Remote-Controlled Robot Competition Series

The Central Illinois Robotics Club (CIRC) will be hosting Kilobots™ — a new RemoteControlled Robot Competition Series, November 9th. 'Kilo' refers to the robot's mass limit of 1kg (2.205 lbs).

There is no size limit; however, the robots will need to negotiate 12" wide halls, so a design of 7" to 9" wide would be a good idea.

There will be three main events the robots can compete in. The events are: Kilobot Challenge™, Kilobot Bash™, and Kilobot Sumo™. Each one is slightly different, but with a little ingenuity, one robot could easily

compete in all three events.

Robots can be a modified RC car or toy, a modified robot kit, or a totally homemade creation. Weapons will be allowed for most of the arenas, so builders can be creative. For more details, check out the CIRC website at <http://www.circ.mtco.com>.

www.SMDRework.com

Your SMD Rework Specialist

800-394-1984

RAMSEY

GET THE NEW CATALOG TODAY!

New Kits, New LPFM, New Cameras

www.ramseykits.com

35 WATT LPFM STEREO TRANSMITTER



- ✓ 35W RF output, VSWR protected
- ✓ Automatic audio & power controls
- ✓ Digital synthesized PLL
- ✓ Full front panel control
- ✓ 110/220VAC, 12VDC operation

Whether your application is export or LPFM, the PX1 has you covered. From the over-rated continuous duty power supply & power amplifier to the 2 line vacuum fluorescent display, your station will be the easiest to setup and the most reliable for continuous operation. Full microprocessor controls provide a "virtual engineer". Check out www.highpowerfm for full details.

PX1 35W Professional FM Stereo Transmitter \$1,795.95

ELECTROCARDIOGRAM HEART MONITOR



- ✓ Visible and audible display of your heart rhythm
 - ✓ Re-usable sensors included; just like visiting the hospital!
 - ✓ Bright LED "beat" indicator
 - ✓ Monitor output for oscilloscope display
- Enjoy learning about the inner workings of the heart while covering the stage by stage electronic circuit theory of ECG/EKG systems. Be heart smart and learn at the same time! Simple and save 9V Battery operation.

ECG1 Electrocardiogram Heart Monitor Kit \$34.95
CECG Matching Case & Knob Set \$14.95
ECGP10 Replacement Reusable Probe Patches (10-Pack) \$7.95

PLASMA GENERATOR



- ✓ Generate 2" sparks to a hand held screwdriver!
 - ✓ Build your own plasma balls!
 - ✓ 25KV at 20 KHz from a solid state source!
- Generate really impressive sparks, build your own plasma ball, light fluorescent tubes without wires! From a solid state source, generate over 25KV at 20KHz for the most dazzling displays!

PG13 Plasma Generator Kit \$59.95
PS12 14VAC Output Power Supply \$19.95

ION GENERATOR



- ✓ Generates negative ions with a blast of fresh air!
 - ✓ 7.5KV DC negative, 400uA - that's a lot of ions!
 - ✓ Steady state DC voltage, constant current, not pulsed!
- Learn the basics of ion repulsion by building this ion generator! Creates a continuous blast of fresh air charged with a ton of ions. Perfect for pollution and air freshening; just smell those ions! Solid state wind generation; you'll be amazed!

IG7 Ion Generator Kit \$59.95
AC125 110 VAC Power Adapter \$9.95

TOUCH-TONE TONE GRABBER



- ✓ New-built-in RJ11 phone jack
 - ✓ Large memory holds over 500 numbers
 - ✓ Big bold 8 digit display, auto insertion of dashes
 - ✓ New-output latch jack
- Diald phone numbers on the radio, repeater codes, control codes, anywhere touch-tones are used, you can read and store them! All new design for 2002. Capture those tones with the TG2!

TG2 Tone Grabber Tone Reader Kit \$59.95
CTG2 Matching Case & Knob Set \$14.95
AC125 110 VAC Power Adapter \$9.95

RCA TO XLR AUDIO CONVERTER



- ✓ Connect consumer outputs to XLR inputs
 - ✓ Left & right audio gain adjustments
- So you're trying to connect consumer audio outputs with RCA connectors (unbalanced) to XLR (balanced) inputs. Always a problem...Not anymore with the R2XL1!

R2XL1 Unbalanced to Balanced Audio Converter Kit \$49.95
CR2XL Matching Case & Knob Set \$14.95
PWR25 12VAC Power Adapter \$9.95

AUTOMATIC COLOR/BW IR CAMERA



- ✓ Color during the day, IR B&W at night!
 - ✓ Automatically turns on IR illumination!
 - ✓ Waterproof to IP57 standards!
 - ✓ Black anodized housing with universal mount
- Best of both worlds! This video camera is a waterproof COLOR camera during the day. When the light level drops, it automatically changes to B&W and turns on its built-in IR illumination, with 10 IR LEDs. Powered by 12VDC and terminated with a professional BNC connector. B&W only model

also available if color is not needed. Both in heavy anodized black housing.
CCD309 Color/B&W IR Waterproof Bullet Camera \$169.95
CCD308 B&W IR Waterproof Bullet Camera \$109.95
AC125 110 VAC Power Adapter \$9.95

MINI B&W CAMERA WITH IR ILLUMINATION



- ✓ Built in IR illumination!
 - ✓ Sees in total darkness!
 - ✓ Black aluminum housing with swivel bracket
- What a deal! This miniature B&W video camera has 6 high power IR LEDs built into it to provide illumination in total darkness! No need for external IR illuminators. Attractive black aluminum housing easily mounts at any angle with the built-in swivel bracket. Runs on 12VDC, and includes professional BNC output plug-in harness.

CCD303 Mini B&W IR Illuminated Camera \$59.95
AC125 110 VAC Power Adapter \$9.95
Check out all our other new cameras at www.ramseykits.com!

PROFESSIONAL FM STEREO RADIO STATION



- ✓ Synthesized 88 to 108 MHz with no drift!
- ✓ Built-in mixer - 2 line inputs and one microphone input!
- ✓ High power module available for export use
- ✓ Low pass filter for great audio response

Our FM100 is used all over the world by serious hobbyists as well as churches, drive-in theaters, and schools. Frequency synthesized PLL assures drift-free operation with simple front panel frequency selection. Built-in audio mixer features LED bargraph meters to make setting audio a breeze. The kit includes metal case, whip antenna and built-in 110 volt AC power supply.

FM100 Super-Pro FM Stereo Radio Station Kit \$249.95
FM100WT 1 Watt, Wired Export Version \$399.95

SYNTHESIZED FM STEREO TRANSMITTER



- ✓ All new design & features for 2002!
 - ✓ Fully adjustable RF output
- Our #1 kit for years has just gotten better for 2002! Totally redesigned, the FM25B has all the features you've asked for. From variable RF output, F connector RF output jack, line input, loop output, and more. Includes case, power supply, whip antenna, audio cables.

FM25B Synthesized FM Stereo Transmitter Kit \$129.95

AND...OUR FAMOUS MINI-KITS



- These are easy to build kits that can be used either stand-alone or as building blocks for more complex projects.
- TS4 Tickle-Stick Shocker \$9.95
 - BN9 Super Snooper Amplifier Kit \$8.95
 - BL1 LED Blinky Kit \$3.95
 - TD1 Tone Encoder/Decoder Kit \$6.95
 - TT7 Touch Tone Decoder Kit \$19.95
 - CP03 Code Practice Oscillator Kit \$9.95
 - UT5 Universal Timer Kit \$8.95

RAMSEY ELECTRONICS, INC.
793 Canning Parkway
Victor, NY 14564
716-924-4560
sales@ramseykits.com



Order Today! 800-446-2295
www.ramseykits.com

The Nuts & Volts

Robotics

The Robot Builder's Bonanza by Gordon McComb

A major revision of the bestselling "bible" of amateur robotics building — packed with the latest in servo motor technology, microcontrolled robots, remote control, Lego Mindstorms Kits, and other commercial kits. **\$24.95**



Microcontrollers

Handbook Of Microcontrollers by Myke Predko

This reference is the first guide to cover all the most common types of microcontrollers. With its from-the-bottom-up approach, this book/CD-ROM package gives you all the information you need to simplify the job of selecting the right microcontroller and writing an application for it. **\$54.95**



Programming & Customizing the 8051 Microcontroller by Myke Predko

Programming and Customizing the 8051 Microcontroller puts you in control of the 8051's architecture and instruction set — and even supplies a baker's dozen of ready-to-build example applications, programs, and circuits. Best of all, the included CD-ROM supplies source code for the book's experiments and applications. **\$39.95**



Programming & Customizing the HC11 Microcontroller by Tom Fox

Applications bazaar for the 68HC11 microcontroller. Squeeze every last drop of power out of Motorola's wildly popular family of 68HC11 true 8-bit single chip computers! From basics to complete applications. **\$39.95**




Programming & Customizing PICmicro Microcontrollers 2nd Edition by Myke Predko

This book is a fully updated and revised compendium of PIC programming information. Comprehensive coverage of the PICmicro's hardware architecture and software schemes complement the host of experiments and projects making this a true, "learn as you go" tutorial. **\$49.95**



PICmicro Microcontroller Pocket Reference by Myke Predko

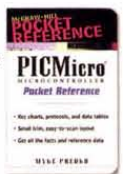Designed to complement Programming & Customizing the PICmicro, this book contains a minimum of verbiage and serves as an immediate device, code and circuit look-up for experienced PICmicro applications designers. **\$29.95**



Programming & Customizing the BASIC Stamp Computer by Scott Edwards

This edition moves you briskly from electronic foundations through BASIC Stamp "Boot Camps" and an intelligent traffic signal simulation to build a robotic bug with whisker sensors, a time/temperature display, and a data-logging thermometer. **\$39.95**



PIC Microcontroller Project Book by John Iovine

This project-oriented guide gives you 12 complete projects, including: using transistors to control DC and AC motors, DTMF phone number logger and distinct ring detector and router ... home automation using X-10 communications ... digital oscilloscope ... simulations of fuzzy logic and neural networks ... and many other applications. **\$29.95**



The Nuts & Volts of BASIC Stamps Vol. 1 & 2

In 1995, Scott Edwards began authoring a column on BASIC Stamp projects in *Nuts & Volts Magazine*. The column quickly became a favorite of *Nuts & Volts* readers and continues today with Jon Williams at the helm. *The Nuts and Volts of BASIC Stamps* is a collection of about 75 of these columns. **\$29.95 each**



Radio & RF


Secrets of RF Circuit Design 3rd Edition by Joe Carr

This revised and updated guide gives you the best ways to design, build, and test today's radio frequency circuits. It's filled with projects and experiments that make it easy to apply RF principles to real-life applications. **\$39.95**



Practical Antenna Handbook 4th Edition by Joe Carr

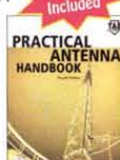The most popular book on antennas ever written. This edition blends "the theoretical concepts that enhance your electricity/electronics mastery, including 15 new to this edition, and appendices packed with commonly used equations, symbols, and supply sources. **\$49.95**




Beginners Handbook of Amateur Radio 4th Edition by Clay Laster

The revised edition of the most trusted guide in ham radio is here. This edition delivers all the guidance you need — from radio and electronics fundamentals needed to set up a transmitter to the newest equipment to revisions to the FCC rules and tests. **\$34.95**



Handbook of Radio & Wireless Technology by Stan Gibilisco

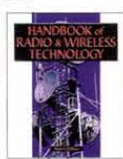Containing more than 1,000 concise articles, this one-stop source of user-friendly insight provides blanket coverage of one of the fastest-growing areas in communications from antennas and transmission lines, to analog and digital modulation techniques, to satellite, space, and laser communications. **\$44.95**



Electronics

Practical Electronics For Inventors by Paul Scherz

This experiment-oriented guide is loaded with over 750 hand-drawn images that support author Paul Scherz's crystal-clear, fully detailed instructions, showing you how to turn theoretical ideas into real-life gadgets. **\$39.95**



Guide To Understanding Electricity & Electronics by Randy Slone

For the true beginner, there's no better introduction to electricity and electronics. You'll also find 25 complete projects that enhance your electricity/electronics mastery, including 15 new to this edition, and appendices packed with commonly used equations, symbols, and supply sources. **\$24.95**



Digital Electronics Guidebook: With Projects by Myke Predko

Perfect for electronics hobbyists and students — even complete beginners — who want to understand digital logic and build their own low-cost logic circuits. Featuring more than 20 projects with step-by-step directions for designing, constructing, and interfacing easy-to-do TTL (Transistor-Transistor Logic) circuits. **\$34.95**



LASERS

superbrightleds.com

super bright leds and super bright led products

BATTERIES FOR EVERY ELECTRONIC APPLICATION

Authorized Sanyo Battery Distributor

See us at batterystore.com

21 years of Battery experience

TNR Technical, Inc.

Sanford, FL • 800-346-0601
Santa Ana, CA • 800-490-8418


Hobbyist Bookstore

Understanding Automotive Electronics Fifth Edition

by William B. Ribbens

This edition of *Understanding Automotive Electronics* covers the most recent technological advances in operation and troubleshooting of electronic systems and components. This is a practical text, suitable for the automotive technician, student or enthusiast. It includes low-emission standards, on-board diagnostics and communications, digital instrumentation, and digital engine control.


\$34.99

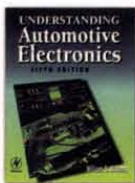

Encyclopedia of Electronic Circuits Vol. 7

by Rudy Graff

Designed for quick reference and on-the-job use, the *Encyclopedia of Electronic Circuits*, Volume 7, puts over 1,000 state-of-the-art electronic and integrated circuit designs at your fingertips. This collection includes the latest designs from industry giants such as Advanced Micro Devices, Motorola, Teledyne, GE, and others, as well as your favorite publications, including *Nuts & Volts*! **\$39.95**

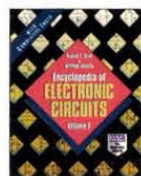


High Voltage

Homemade Lightning: Creative Experiments in Electricity

by R.A. Ford

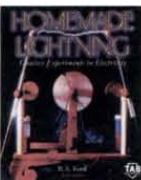Enter the wide-open frontier of high-voltage electrostatics with this fascinating, experiment-filled guide. You'll discover how to make your own equipment, how electricity is used in healing, and the workings of many experiments in high potential physics! **\$24.95**




Troubleshooting

Circuit Troubleshooting Handbook

by John D. Lenk

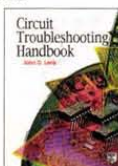
Heavily illustrated with diagrams and schematics, it uses a standard, easy-to-follow format to help readers understand and troubleshoot a wide range of circuit types, and provides proven circuit testing techniques for all levels of instrumentation. **\$39.95**



Electronic Troubleshooting 2nd Edition

by Dan Tomal and Neil Widmer

This updated tool gives all the fundamentals needed to do successful servicing and repair work, blending traditional theory with the very latest insight into modern electronics technology. Time-saving tables, charts, and illustrations pinpoint equipment problems in a snap. Numerous reference guides, rules of thumb, and tricks of the trade all combine to assist in troubleshooting the full spectrum of devices and products more easily than ever before. **\$39.95**

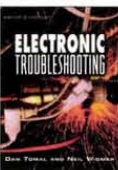


Miscellaneous

The Hacker Diaries: Confessions of Teenage Hackers

by Dan Verton

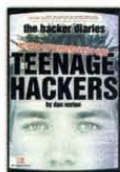Through fascinating interviews with FBI agents, criminal psychologists, law-enforcement officials—as well as current and former hackers—you'll get a glimpse inside the mind of today's teenage hacker. Learn how they think and understand the internal and external pressures that pushed them deeper and deeper into the hacker underground. **\$24.99**




This Month's Featured Titles

The Do-It-Yourself PC Book

An Illustrated Guide to Upgrading and Repairing Your PC

by Kyle MacRae

\$24.99

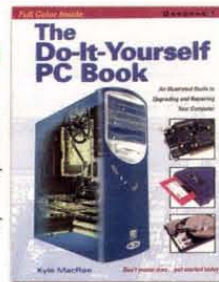

This highly illustrated full-color guide is the easiest way to master the art of upgrading, maintaining, and repairing your PC. Written with humor and simplicity, *The Do-It-Yourself PC Book* demystifies and explains the inner workings of your computer and makes it easy for anyone to give their old machine a boost or keep their new one in perfect working order. Each chapter features clear explanations and step-by-step instructions while the accompanying full-color photographs show you every procedure and component.

PICMicro Microcontroller Pocket Reference


by Myke Predko

\$29.95

Designed to complement *Programming & Customizing the PICMicro*, this book contains a minimum of verbiage and serves as an immediate device, code and circuit look-up for experienced PICMicro applications designers.

CONTENTS


Conventions Used In This Book.
PICmicro MCU Park Number Feature Comparison.
Device Pinouts.
PICmicro MCU Instruction Sets.
PICmicro MCU Processor Architectures.
PICmicro MCU Register Mappings.
Built-In Hardware Features.
PICmicro MCU Hardware Interfacing.
PICmicro MCU Programming.
PC Interfaces.
Useful Code Snippets.
16-Bit Numbers.
PICmicro MCU Operations Tables.
PICmicro MCU Application Debugging Checklist.
Constants and Data Tables.
Miscellaneous Electronics.
Formulas.
Resources.

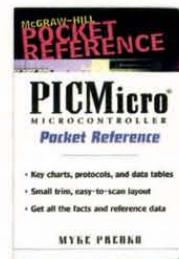

Call 1-800-783-4624 today! or order online at www.nutsvolts.com WE ACCEPT VISA, MASTERCARD, AMERICAN EXPRESS

Prices do not include shipping and may be subject to change. Ask about our 10% subscriber discount on selected titles.

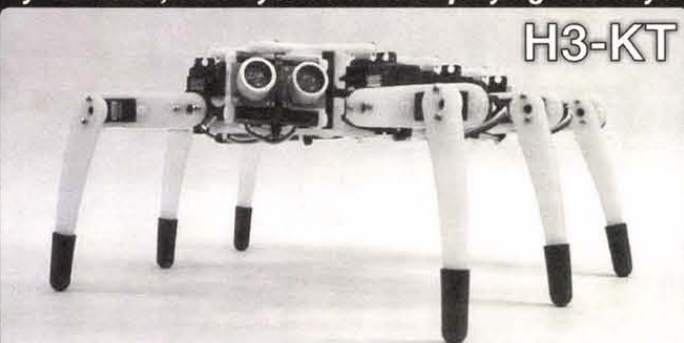Lynxmotion, When you're tired of playing with toys!



Lynxmotion, Inc.
PO Box 818
Pekin, IL 61555-0818
www.lynxmotion.com

Lynxmotion

Visit our website or ask for our free catalog!

Tel: 309-382-1816
Fax: 309-382-1254
sales@lynxmotion.com
tech@lynxmotion.com

68HC11 & 68HC12 Microcontroller Modules!

Unique design-- just plug them right into your solderless breadboard!

MicroStamp 1™

• tiny 1-inch x 1.4-inch 68HC11 module from \$49

MicroCore-11™

• compact 2-inch x 2-inch 68HC11 module from \$68

Adapt-11™ Family

• 68HC11 modules with lots of I/O lines from \$63

Application Cards Available:

• stepper motor driver
• voice record/playback
• LCD/keypad/PC keyboard
• data acquisition • DAC
• CAN • ethernet • more!

Adapt812™ Family

• based on 68HC12A4

• from \$79

Adapt912™ Family

• choice of B32, D60, DG128

• from \$99

MicroBOM912™

• lowest-cost BDM pod!

• only \$79!

Toll-free: 1-877-963-8996

Technological Arts

Phone: (416) 963-8996

Fax: (416) 963-9179

www.technologicalarts.com

High Tech Video system w Audio

Includes TWO B/W Cameras w sound & I.R. (night vision) ONE 5.5" B/W Monitor with Built-In adjustable Switching (from 2 to 20 seconds) & two 60 ft. pre-wired cables. Everything you need to set up a high tech video monitoring system at home, office, restaurant warehouse or use it as a baby monitor. Easily hooks into VCR for Video Recording also



item # Dual View
Fantastic Price!
\$119.00 ea
(\$109.00 ea. qty 4)
view extensive details @ web site

Auto-Temp Solder Station with Ceramic Element

- With Ceramic Heating Element for More Accurate Temp Adjustment
- 3 Conductor Grounded Power Cord
- 250°C-480°C (470°F-900°F)
- Fast Heating Feature



SR-976
Extra Tip Options
Available. See Web!

ONLY \$39

For More Info See www.web-tronics.com

CTRL - D
to bookmark
this site

www.web-tronics.com

- Easy to Navigate
- Includes a Search Engine That Really Works
- New Items Added Constantly

In Business Since 1971

CCD B&W Board Cameras

- ASIC CCD Area Image Sensor
- Extremely Low Power Consumption
- 0.5 Lux Min Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation

Detailed Specs on the Web

VM1030PA-B 30mmx30mmx25mm, Pinhole lens, 12V \$39.00 any qty.
VM1030A 30mmx30mmx26mm, Standard lens, 12V \$39.00 any qty.
VM1035A 42mmx42mmx25mm, Standard lens, 12V with back light compensation \$49.00 any qty.
VMCB21 44mmx38.5mmx28mm, with 6 infra-red LEDs, 12V \$49.00 any qty.
VM1036A 32mmx32mmx25mm, Standard lens 12V, reverse mirror image feature \$49.00 any qty.

Detailed Specs on the Web



B&W Color & Powerful Night Vision Model

- Smart Rugged Metal Housing
- Extremely Low Power Consumption
- 12 Volt
- CCD Area Image Sensor for Long Camera Life
- Built-In Electronic Auto Iris for Auto Light Compensation
- No Blooming, No Burning
- 0.1 Min Lux Illumination (B&W), 1 Lux Min Lux Illumination (color)

VMBLT1020 B&W, 21mm (D)x55mm (L) \$49.00 any qty.
VMBLT1020W B&W Weatherproof, 21mm (D)x58.5mm (L) \$69.00 any qty.
VMBLTJC19BW COLOR Weatherproof, 17mm (D)x88mm (L) \$109.00 any qty.
WDB-5007S Powerful night vision camera (56 IR LEDs) \$159.00 (\$139.00/ 5+)

Bullet CCD Cameras

Detailed Specs on the Web



COLOR CCD Mini Board Cameras

- Low Power Consumption
- 1 Lux Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation
- Internal Synchronization
- 12Volts
- 400 TV Lines

VM3010PA 33mm x 33mm x 18mm pinhole lens.....\$99.00 any qty.
VM3010-A 33mm x 33mm x 18mm standard lens.....\$99.00 any qty.

Detailed Specs on the Web



DC to AC Power Inverters ! 150 watt up to 3000 watt models!

150w modified sine wave: \$29.95 (G-12-015B)
300w modified sine wave: \$39.95 (G-12-030)
150w pure sine wave: \$69.00 (G-12-150S)
300w pure sine wave: \$109.00 (G-12-300S)
800w modified sine wave: \$139.00 (G-12-800)
1000w modified sine wave: \$179.00 (G-12-1000)
3000w modified sine wave (phase corrected), (G-12-300).....\$489.00

See Our web site for DETAILED Specs.!

Check Our Low Prices!



G-12-030 300W

Our Most Sophisticated DMM We Sold Over 800 Last Year!
with RS-232 Interface & Software, 3-3/4 Digit, 4000 Count Auto-Ranging with Analog Bargraph

- True RMS Mode
- 10MHz Frequency Counter
- Time Mode with Alarm, Clock, and Stop Watch
- Dual Display
- 10 Location Memory
- Min, Max, Avg and Relative Mode
- Decibel Measurement
- Cap and Ind. Measurement
- Temperature Mode (C/F)
- K Type Temperature Probe Included
- Pulse Signal for Logic & Audible Test
- Continuity/Diode Test
- Logic Test
- Auto Power OFF "Keep ON" Mode
- Fused 20A Input with Warning Buzzer
- Back Light
- Data Hold/Run Mode
- Safety Design UL1244 & VDE-0411
- Protective Holder
- Silicon Test Leads



NOW ONLY \$149
Reg. \$169

More Details on our Web Site
PROTEK 506
\$129.00 ea. qty 10



24-960 Hour Time Lapse VCR's
12VDC version and 120VAC version only \$349.00 !
Details @ web site under miniature camera section

Removable Hard Drive Rack
ALUMINUM FRAME & CARRIER!
3 COOLING FANS!
AUTO-CLOSE FRONT DOOR!
OUR NEW "BEST CHOICE" Hard Drive Rack features aluminum frame & carrier for rugged performance & heat dissipation. Also, 3 internal cooling fans provide even more help with heat dissipation. Includes key lock, LED activity light, Auto-eject handle design & ground wire. Available for IDE ULTRA DMA 66/100/133 & also ultra wide SCSI version.

BEST CHOICE! ONLY \$179.95
any qty.
Compare with models costing twice as much!



AMR-3F (IDE Ultra DMA).....\$17.95
AMR/UWSCSI (ultra wide SCSI).....\$22.95

Triple Output Bench Power Supply

with four 3 1/2 digit LCD Displays



Output : 0-30VDC x 2 @ 2 AMPS
& 1 ea. fixed output @ 5VDC
Source Effect: <0.02% +1mV
Load Effect: <0.01% +5mV
Ripple & Noise: <1mVrms
Dimensions: 365 x 265 x 164 mm
Input Voltage: 110VAC +/- 10%

CSI3002D-3.....\$169.00
(qty 5+.....\$159.00)

Details at www.web-tronics.com

Mini CCDs (B/W & Color)
Sensational NEW Design for Small Observation Cameras. Smaller and Better!

- Ultra Miniature Design
- Black & White Versions Only 25mm x 25mm
- Color Versions Only 32mm x 32mm
- Available in Standard Lens or Pinhole Lens
- All Include Pre-Wired Cable Harness for Video & Power
- 12V Regulated Power Supply Required (120mA typical power consumption)
- 0.1 LUX Rating (B/W), 1 LUX (color)
- CCD Area Image Sensor for Long Camera Life
- Back Light Compensation Circuit
- Built-In Electronic Auto Iris Lens



Detailed Specs on the Web

VMCW-H11A 32mmx32mmx30mm, Color CCD with standard lens, pre-wired cabling for video/audio, 12V DC Power \$109.00 / \$99.00 5 or more

VMCW-H12A 32mmx32mmx19mm, Color CCD with pinhole lens, pre-wired cabling for video/audio, 12V DC Power Input \$109.00 / \$99.00 5 or more

VMPS-718A 25mmx25mmx30mm, B/W CCD with standard lens, pre-wired cabling for video/audio, 12V DC Power Input \$49.00 / \$45.00 5 or more

VMPS-250A 25mmx25mmx15mm, B/W CCD with pinhole lens, pre-wired cabling for video/audio, 12V DC Power Input \$49.00 / \$45.00 5 or more

new!

Bench Digital Multimeter w RS232C

\$99.00 !

Item#
CSI9803R



- * Digital & Analog Display, 3999 counts & 42 segment bar graph.
- * Autorange & Manual Range
- * DATA HOLD, Min/Max Relative Measurement
- * Storage Data DISPLAY/RECALL
- * True RMS f AC voltage & current
- * Back Light
- * ADP Measurement: 400mV +/- 3%
- * Continuity & Diode test
- * Power Source: AC or DC

See details @ web site

O'Scope Offer

30MHz! ONLY \$299!

ONLY \$299



- Dual Channel
- Dual Trace
- Vert Trigger
- 1 Year C.S.I. Warranty!

Includes 1 oscilloscope probe

Manufactured for CSI by a leading O.E.M. manufacturer. See our website for detailed specifications!

Digital Read Out 3Amp Bench Power Supplies

Available in 0-30 volt & 0-50 volt versions

AS LOW AS \$85

High stability digital read-out bench power supplies featuring constant voltage and current outputs. Short-circuit protection and current limiting protection is provided. Highly accurate LED accuracy and stable line regulation make the 3000 series the perfect choice for lab and educational use.

Line Regulation: $2 \times 10^{-4} + 1\text{ma}$
LED Accuracy: Voltage $\pm 1\%$ +2 digits
Current $\pm 1.5\%$ +2 digits
Wave Line Noise: $\leq 1\text{mVrms}$
Dimensions: 291mm x 158mm x 136mm

New! Lower Prices

CSI3003: 0-30v/0-3amp 1-4 / \$89.00 5+ / \$85.00

CSI5003: 0-50v/0-3amps 1-4 / \$109.00 5+ / \$99.00

Bookmark our WEB Site! Many more Power Supplies are Available. Look Under Test Equipment



**Digital Storage Oscilloscope Module**

Convert any PC with USB interface to a high performing Digital Storage Oscilloscope. This is a sophisticated PC based scope adaptor providing performance compatible to mid/high level stand alone products costing much more! Complete details & software download @ our web site under test equipment.

item# 200DSO **\$799.00**



2 AMP
0-18V Bench
Power Supply
LCD Display

input voltage: 110VAC
output: 0-18VDC
Current: 0-2A
Source Effect: <0.02%+1mV
Load Effect: <0.01%+5mV
Ripple & Noise: <1mVrms

1 5+
\$59.95 \$52.95
item # CSI 1802D

NEW!

SoftTube Heatshrink
2:1 shrink ratio
Sold in 4 ft lengths
Sold Bulk on Spool
Extremely Low Prices
Many diameters
Many colors

LOW PRICES!**UL Recognized**

NEW!
PLEASE VISIT OUR WEB SITE
FOR SELECTION & PRICES
WWW.WEB-TRONICS.COM

**Intelligent DMM with PC Interface**

- *Auto-Ranging
- *Dual Display
- *Conforms to IEC1010
- *3999 counts & 38segment bar graph display
- *DC voltage (autoranging)
- *AC voltage (auto ranging)
- *Temperature measurement
- *Resistance (auto ranging)
- *capacitance
- *diode testing
- *transistor check
- *audible continuity

item# CSI345
Extensive Details @
www.web-tronics.com

\$44.50 !

Ships with Rubber
Boot, RS-232 cable,
Software
& Test Leads &
K-probe

**Intelligent Multi-function Digital Counter**

An intelligent multi-function counter controlled by an 8-bit micro-controller with eight-digit high bright LED display. Four measuring functions (frequency, period, total count & self-check). Also, a 10MHz OSC. OUT.

Frequency Measurements:
CH A, Range 10 to 100Mhz
CHB, Range 100Mhz to 1.3Ghz

NEW ITEM

DETAILS AT OUR
WEB SITE under TEST EQUIPMENT

item# CSI 6100
\$149.00 !! www.WEB-TRONICS.com

LED's/Megabright Blue, White, GREAT PRICES!

		luminescent intensity @ 20mA	1	10+	100+
Megabright Blue 5mm (L7113PBC/G)	1400	\$1.95	\$1.50	\$1.25	
Megabright Blue 3mm (L7104PBC/G)	600	\$1.95	\$1.50	\$1.25	
Megabright White 5mm (L7114PWC/G)	600	\$2.15	\$1.59	\$1.35	

more technical details @ our web site under SEMICONDUCTORS

FLASHING red 3mm (L36BHD).....as low as \$0.28 ea!

OUR NEW SELF-LOCKING CABLE TIES

UL approved Nylon 66, 94V-2, white color, acidproof, alkaliproof, good insulation & long lasting Sold in Bags of 100 pcs. Buy at prices usually reserved for large bulk purchasers !!!!!!! CHECK PRICES BELOW!

GL3 series = 2.5 m.m. width/ GL4 series = 3.5 m.m. width/ GL5 series = 4.8m.m. width/ GL8 series = 7.0 m.m. width/ GL10 series = 9.0 m.m width/ GL12 series = 12 m.m. width.....100 pcs per bag

item	length	price	item	length	price
GL3-100	4 inch	\$0.25/bag	GL5-400	16 inch	\$2.49/bag
GL4-150	6 inch	\$0.49/bag	GL8-200	8 inch	\$1.99/bag
GL4-200	8 inch	\$0.79/bag	GL8-300	12 inch	\$2.79/bag
GL4-250	10 inch	\$1.15/bag	GL8-400	16 inch	\$3.99/bag
GL4-300	12 inch	\$1.29/bag	GL10-400	16 inch	\$5.49/bag
GL5-200	8 inch	\$0.99/bag	GL10-500	20 inch	\$6.15/bag
GL5-250	10 inch	\$1.39/bag	GL10-600	23.5 inch	\$9.29/bag
GL5-300	12 inch	\$1.69/bag	GL10-800	31.5 inch	\$13.99/bag
GL5-350	14 inch	\$2.29/bag	GL12-650	25.5 inch	\$12.49/bag

Industry Best Pricing!**Single Turn 1/4" SQ. Cermet Pots (Horiz. & Vertical)**

Stocking standard values from 100 ohm to 1 Meg

(WIW1036 series)



"H"

	1	10+	100+	500+
	\$0.79	\$0.69	\$0.55	\$0.45

Cermet Prices shown are per value/ More Details @ www.WEB-TRONICS.com

Standard 5MM & 3MM LEDs/Red/Green/Yellow

More Details @ www.WEB-TRONICS.com

	1	10+	100+	1000+
Red-Diffused 5mm (L53HD)	\$0.12	\$0.08	\$0.05	\$0.04
Green-Diffused 5mm (L53GD)	\$0.14	\$0.09	\$0.06	\$0.05
Yellow-Diffused 5mm (L53YD)	\$0.15	\$0.10	\$0.07	\$0.06
Red-Diffused 3mm (L934HD)	\$0.12	\$0.08	\$0.05	\$0.04
Green-Diffused 3mm (L934GD)	\$0.14	\$0.10	\$0.07	\$0.04
Yellow-Diffused 3mm (L934YD)	\$0.15	\$0.11	\$0.08	\$0.05

GREAT LED PRICES!

Visit our website for a complete listing of our offers. We have over 8,000 electronic items on line @ www.web-tronics.com. PC based data acquisition, industrial computers, loads of test equipment, optics, I.C's, transistors, diodes, resistors, potentiometers, motion control products, capacitors, miniature observation cameras, panel meters, chemicals for electronics, do it yourself printed circuit supplies for PCB fabrication, educational D.I.Y.kits, cooling fans, heat shrink, cable ties & other wire handling items, hand tools for electronics, breadboards, trainers, programmers & much much more ! Some Deals you won't believe !

Are Stamps in your Class?

Stocking your classroom. 101



The **Stamps in Class** program was created to provide educators, students and engineers the material they need to learn microcontroller programming and interfacing. We've published six **curriculum** for you to choose from. Each curriculum has its own strengths in introductory PBASIC programming, sensor calibration and interfacing, data logging, motor control and PID control (proportional - integral - derivative). See the descriptions on our Stamps in Class web site (www.stampsinclass.com) or download the books for a quick review. Each text has an accompanying parts kit which you can purchase from Parallax or build your own.

Educators stock their classes with the **Board of Education Full Kit** (28102). The Board of Education is the project board for BASIC Stamp microcontroller projects, including the Stamps in Class curriculum. The board was designed in coordination with our educational customers to teach microcontroller interfacing and programming. Even if you aren't using the Parallax published curricula, the Board of Education is still an ideal set of hardware for instructor-authored lessons. The Board of Education is available in a Full Kit that includes a BS2-IC module, power supply, and serial cable, or may be purchased individually (#28150).




Getting the class started with our **Robotics!** curriculum is easy with Parallax products. The **Boe-Bot** (28132) is a wheeled robot with a well-developed educational tutorial demonstrating the essentials of motor control, sensor interfacing and program structuring. The Boe-Bot has a number of add-ons for line following, sonar and speech generation.



Once you've learned the Boe-Bot, try moving on to the **Advanced Robotics curriculum** featuring the **Toddler** (#27310, #27311). This bipedal robot has 34 unique movements, and is capable of almost everything a Boe-Bot can do but requires much more emphasis on programming and software/hardware interaction.

Educators can send students home with the new **BASIC Stamp HomeWork Board**. These boards were designed in response to requests from educators who desired a low-cost BASIC Stamp 2 that students could either take home or dedicate towards a permanent project. Less expensive than a Board of Education Full Kit. Available in 10 packs with either a breadboard (#28157) or through-hole (#28158) prototype area.

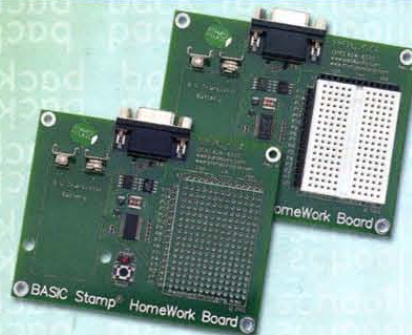

PARALLAX

BASIC Stamp is a registered trademark of Parallax, Inc.

For more information visit www.stampsinclass.com
or call toll-free in the US at 888-512-1024