

# 800-950MHZ FREQUENCY CONVERTER.

THIS CIRCUIT WILL TAKE AN 800-950MHZ SIGNAL AND MIX IT WITH A CARRIER FREQUENCY, OR 40.000MHZ. THIS MIXED SIGNAL IS THE OUTPUT.

THE OUTPUT FREQUENCY OF THE DEVICE WILL BE 400-450MHZ.

THEORY: THE SIGNAL IS FED INTO THE INPUT RCA JACK. THIS SIGNAL PASSES THROUGH A SERIES OF FILTERS AND IS MULTIPLEXED WITH A 40MHZ SIGNAL WHICH IS GENERATED BY THE OSCILLATOR. THIS MIXED SIGNAL IS FED INTO A MAR1 AMP MIXER WHERE IT IS TRULY MIXED AND AMPLIFIED. THIS SIGNAL IS THE OUTPUT.

## SCHEMATIC DIAGRAM

### PARTS LIST.

R1=220 OHM

R2=1K OHM

C1, 2, 3, 8, 10, 21=.001uF DISC

C4, 7, 17, 18, 19, 20=5pF DISC

C5, 6, 9=2pF DISC

C12, 13=10uF ELECT

C14, 15, 16=1pF DISC

L1, 5=10uH INDUCTORS

L6, 7, 8, 9=2 TURN INDUCTORS, USE VARIABLE FOR BEST RESULTS. 28-32 GA WIRE.

L2, 3, 4=1 TURN INDUCTORS, USE VARIABLE FOR BEST RESULTS. 28-32 GA WIRE.


Q1=2SC2498 NPN

MAR 1=MMIC AMP

REG1=5V DC REGULATOR


OSC1=40.000MHZ OSCILLATOR

J1, 2=RCA JACKS.

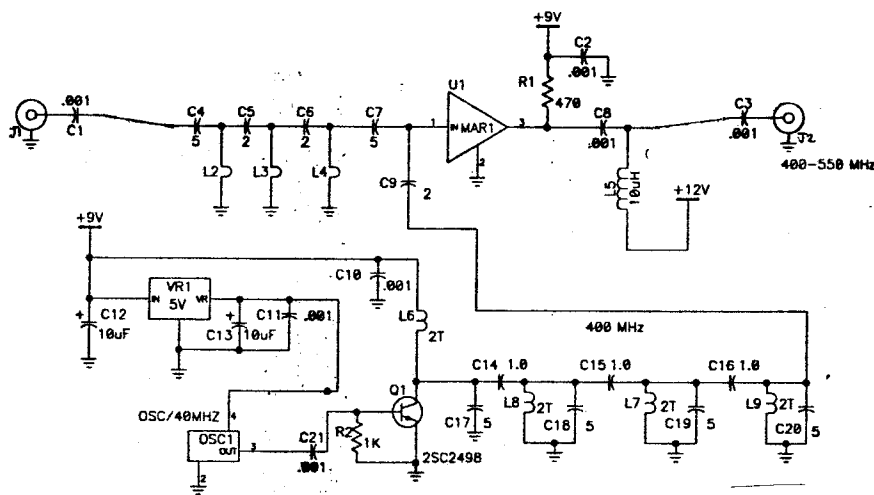

MAKE SURE ALL COMPONENTS ARE SOLDERED TOGETHER WELL. IF THE UNIT FAILS TO OPERATE CORRECTLY TRY USING A DIFFERENT SET OF INDUCTORS FOR THE 1 TURN ONES OR USE SHIELDED WIRE ON ALL WIRING. PUT THE DEVICE IN A METAL BOX. USE AN O-SCOPE TO VIEW THE CORRECT FREQUENCY FROM THE OUTPUT. EITHER A 40MHZ MODULATED SIGNAL OR 400-450MHZ MODULATED SIGNAL.

PICTORAL OF CIRCUIT BOARD.

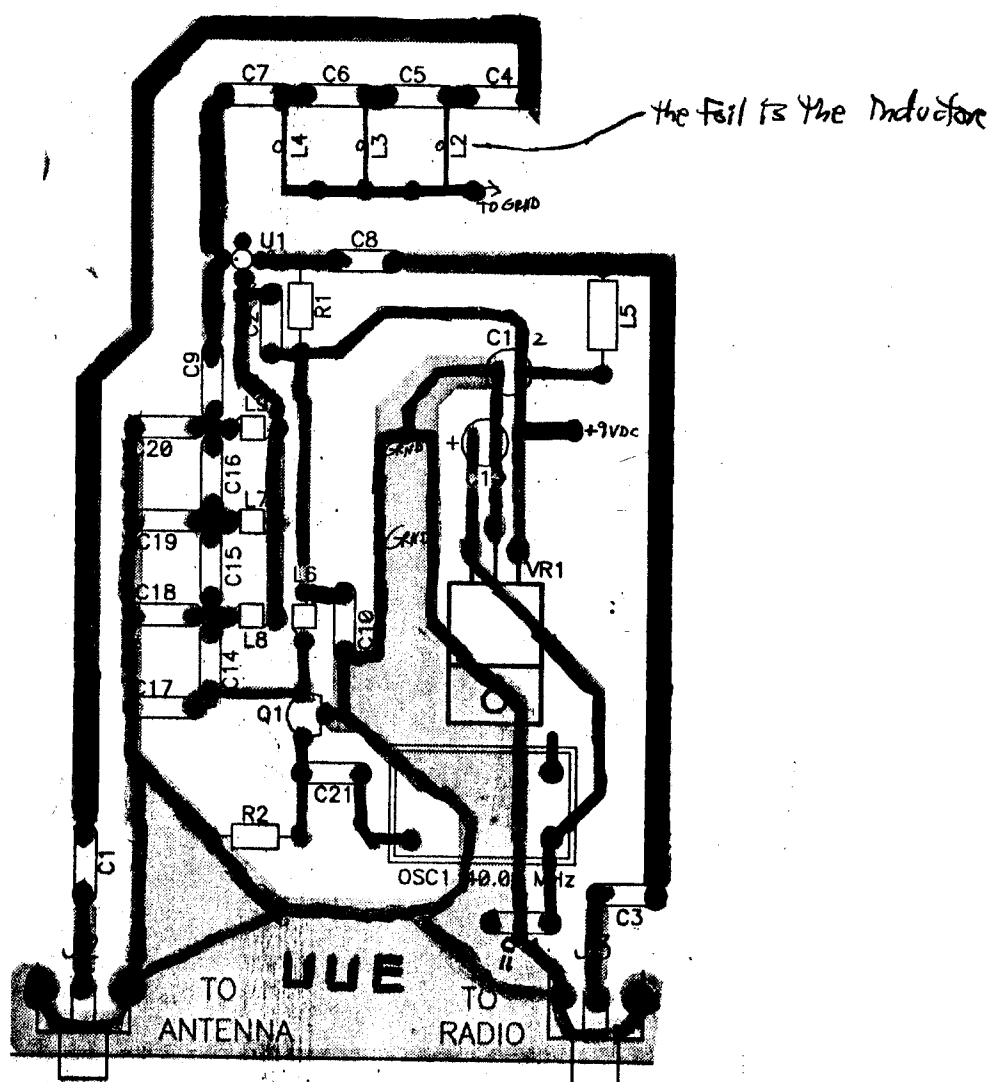


## 100KHZ-1.3GHZ RF PREAMPLIFIER

THIS CIRCUIT IS AN EXCELLENT UNIT. IT USES TWO MICROWAVE TRANSISTORS FOR WIDE RANGE AND EXCELLENT STABILITY. LOW LOSS, LOW SUSCEPTABILITY TO NOISE AND LOW POWER CONSUMPTION OF AROUND 15MA. THE CIRCUIT BOARD CAN BE A PERFBOARD. JUST MAKE SURE THE TRANSISTORS ARE SHIELDED FROM L1.

THIS UNIT WILL PUT OUT AROUND 100MW.

SCHEMATIC DIAGRAM.

---

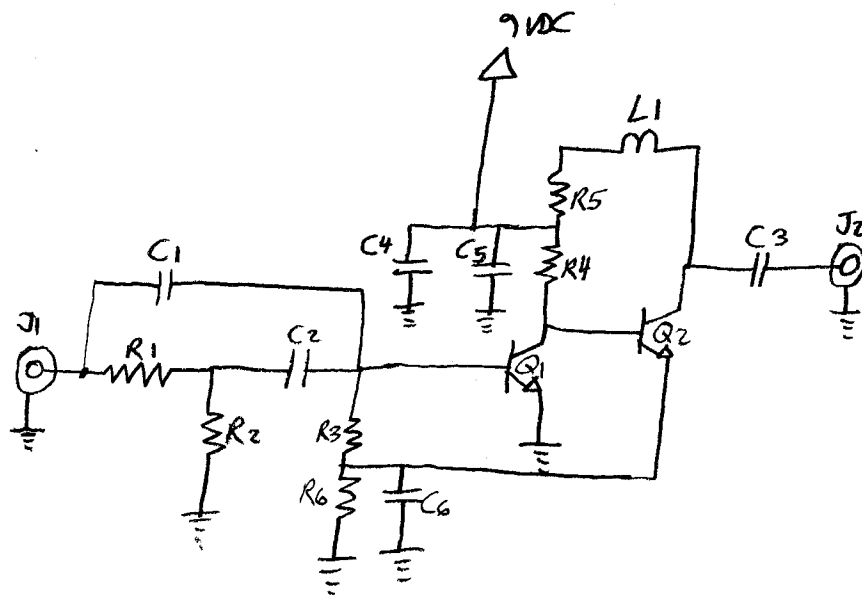

PARTS LIST:

R1,5=100 OHM  
R2=51 OHM  
R3=470 OHM  
R4=1K OHM  
R6=47 OHM  
C1=5pF DISC  
C2, 3, 5=.01uF DISC  
C4=10uF ELECT  
C6=2.2pF DISC  
L1=.04uH INDUCTOR  
Q1,2=2SC2498 TRANSISTORS (NPN)