



CIRCUIT SOUNDS BEEPER IF UNIT IS TURNED ON BUT LINE POWER IS LOST